

Dr. Eyad Abu Al-Feilat.

Tutorial (1) Solutions.

By Mohammad Abu Hashia.

Summer Semester  
2017


Q1 a)

$$|E_a| \propto f \cdot I_F$$

$$\frac{E_{a1}}{E_{a2}} = \frac{f_1 I_{F1}}{f_2 I_{F2}}$$

$$\Rightarrow E_{a2} = \frac{I_{F2} f_2 E_{a1}}{f_1 I_{F1}}$$

$$= \frac{(40)(2.4)(360)}{(60)(3.6)} \Rightarrow |E_{a2}| = 160 \text{ volt.}$$

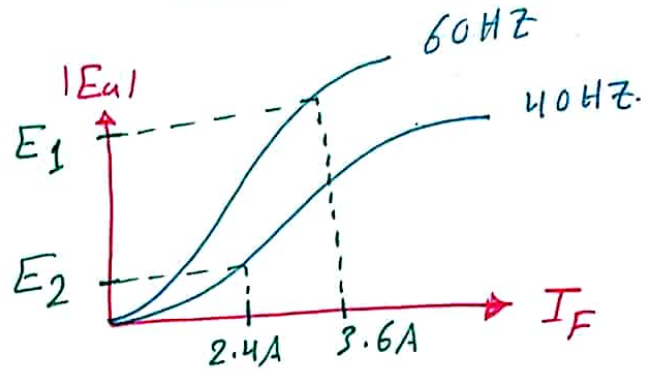

b)  $|V_t|_{NL} = |E_a| = 620 \text{ volt.}$   
 $f = 60 \text{ Hz.}$

if  $\phi_2 = 0.85 \phi_1$  &  $n_2 = 1.1 n_1$   
 $\Rightarrow I_{F2} = 0.85 I_{F1}$  &  $f_2 = 1.1 f_1$

$$\Rightarrow f_2 = 1.1 (60) = 66 \text{ Hz.}$$

$$|E_2| = \frac{f_2 I_{F2} E_1}{f_1 I_{F1}}$$


$$= (1.1)(0.85)(620)$$

$$\Rightarrow |E_2| = 580 \text{ volt.}$$

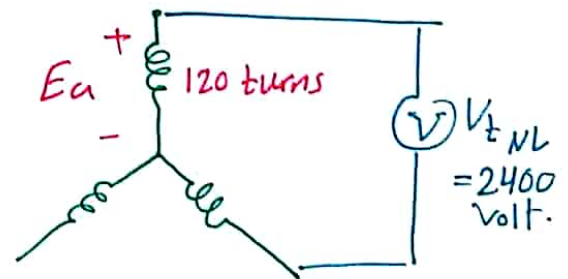Q2

$$\Rightarrow n_s = \frac{120}{p} f = \frac{120}{8} (f) = 900$$


$$\Rightarrow n_s = 900 \text{ rpm ; so } f = 60 \text{ Hz.}$$



$$E = 4.44 K_w f N_{ph} \phi$$



$$\phi = \frac{2400 / \sqrt{3}}{4.44 (0.9) (120) (60)}$$
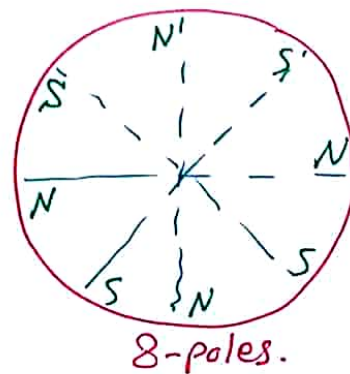
$$\Rightarrow \phi = 48.2 \text{ m Wb.}$$



**Q3**  $|S| = \frac{P}{PF} = \frac{750K}{0.8} = 937.5KVA.$

per-phase cct:

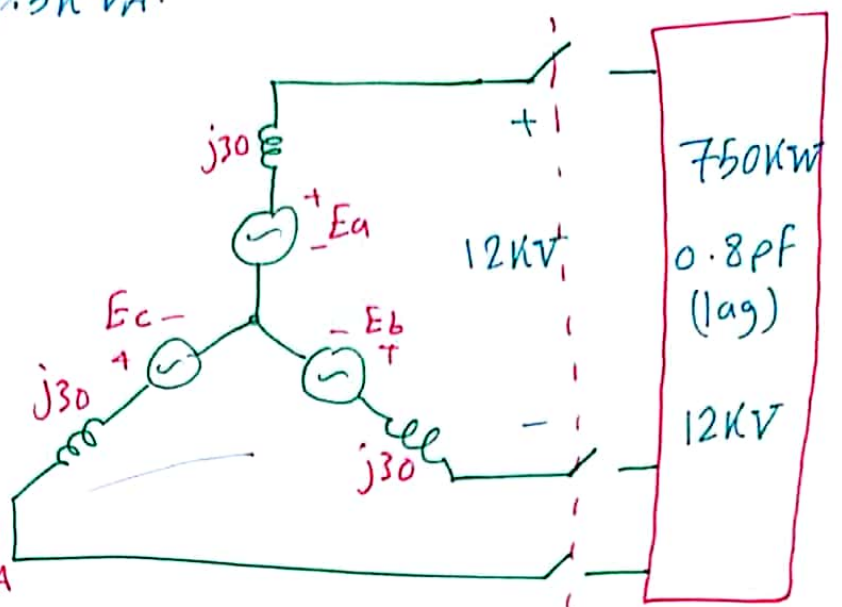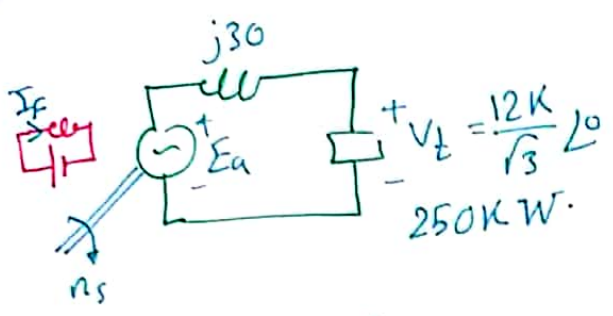



$I_a = \frac{937.5K}{\sqrt{3} * 12K} = 45.1 \angle -36.9^\circ A$

$E_a = V_t + jI_a X_s = \frac{12K}{\sqrt{3}} \angle 0 + j30 (45.1 \angle -36.9) \Rightarrow E_a = 7816 \angle 7.9 \text{ volt.}$   
 $|E_a|_{LL} = 13.5K \text{ volt.}$

$VR = \frac{V_{nl} - V_{fl}}{V_{fl}} * 100\% = \frac{13.5 - 12}{12} * 100\%$

$\Rightarrow VR = 12.5\%$


\* phasor diagram:

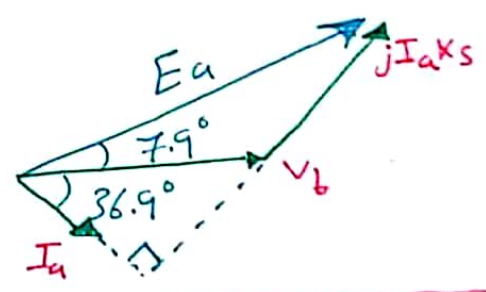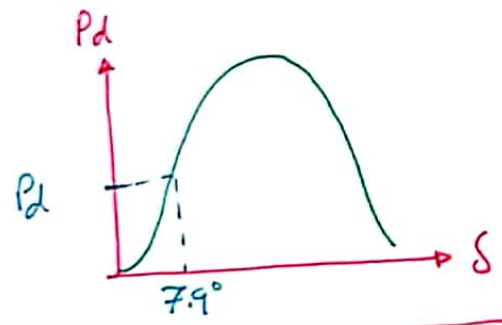

**Q4** @ Pf=1 :

$I_a = 524.9 \angle 0 A$   
 $E_a = 6412.7 \angle 3.1^\circ \text{ volt.}$   
 $|E_a|_{LL} = 11.1K \text{ volt.}$

$VR\% = 0.9\%$

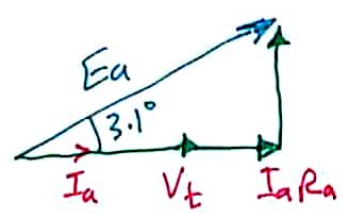


@ 0.8 pf lag:

$I_a = 656.1 \angle -36.9^\circ$   
 $E_a = 6670.4 \angle 2.6^\circ \text{ volt.}$

$|E_a|_{LL} = 11.5K \text{ volt.}$

$VR\% = 4.55\%$

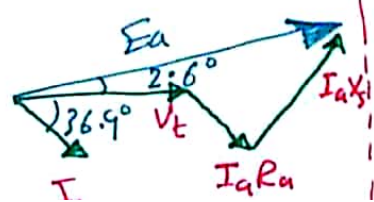


@ 0.8 pf lead:

$I_a = 656.1 \angle +36.9^\circ$   
 $E_a = 6155.4 \angle 3.6^\circ \text{ volt.}$


$|E_a|_{LL} = 10.7K \text{ volt.}$

$VR\% = -2.73\%$

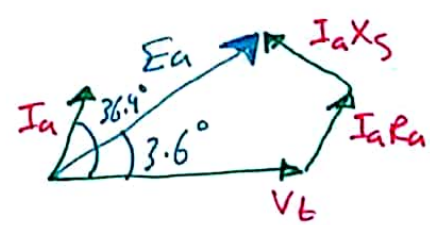

Q5

$$|I_a| = |I| = \frac{S_{3\phi}}{\sqrt{3} V_L} = \frac{1200 \times 10^3}{\sqrt{3} \times 6600} = 105 \text{ A}$$

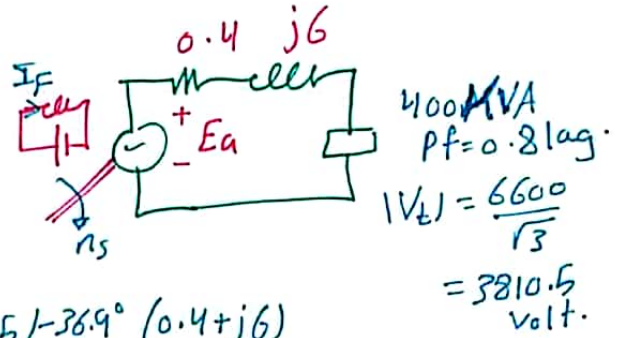

$$E_a = V_t + I_a (R_a + jX_s) = 3810.5 \angle 0^\circ + 105 \angle -36.9^\circ (0.4 + j6)$$


$$\Rightarrow \boxed{E_a = 4249.4 \angle 66^\circ \text{ volt.}}$$

$$\boxed{|E_a|_{LL} = 7360 \text{ volt.}}$$

$$V_t = E_a \angle \delta - I_a (R_a + jX_s)$$

Two unknowns.

so use:

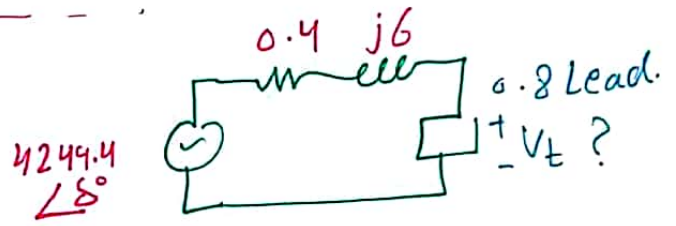

$$|E_a|^2 = (V_t \cos \theta + I_a R_a)^2 + (V_t \sin \theta - I_a X_s)^2$$

$$(4249.4)^2 = (0.8 V_t + 105 \times 0.4)^2 + (V_t \times 0.6 - 105 \times 6)^2$$

solve:  $\Rightarrow$   $\boxed{|V_t| = 4831.2 \text{ volt.}}$   
 $\boxed{|V_t|_{LL} = 8367.9 \text{ volt.}}$

Q6

o/c Test:  $I_f = 125 \text{ A}$ ,  $V_{toc} = 8000 \text{ V}$ ,  $n = n_s$   
 s/c Test:  $I_f = 125 \text{ A}$ ,  $I_{sc} = 800 \text{ A}$ ,  $n = n_s$

@ rated Full-load  $\Rightarrow V_{drop} = V_{Ra} = 3\%$  of the rated phase voltage.

$$|Z_s| = \frac{|E_{oc}|_{ph}}{I_{sc}} = \frac{8000/\sqrt{3}}{800} = 5.77 \Omega = \sqrt{R_a^2 + X_s^2}$$

$$I_{aFL} = \frac{6000 \times 10^3}{\sqrt{3} (6.6) \times 10^3} = 524.8 \text{ A}$$

$$|V_{Ra}| = R_a I_{aFL} = \frac{3}{100} \times \frac{6600}{\sqrt{3}} = 114.3 \text{ volt}$$

$$R_a = \frac{114.3}{524.8} \Rightarrow \boxed{R_a = 0.22 \Omega} \Rightarrow \boxed{X_s = 5.69 \Omega}$$



$$E_a = V_t + I_a Z_s = \frac{6600}{\sqrt{3}} + 524.8 \angle -36.9^\circ (0.22 + j5.69)$$

$$\boxed{E_a = 6148 \angle 22.1^\circ \text{ volt.}}$$

$$\boxed{|E_a|_{LL} = 10650 \text{ volt.}}$$

$$VR = \frac{10650 - 6600}{6600} \times 100\%$$

$$\boxed{VR\% = 61\%}$$

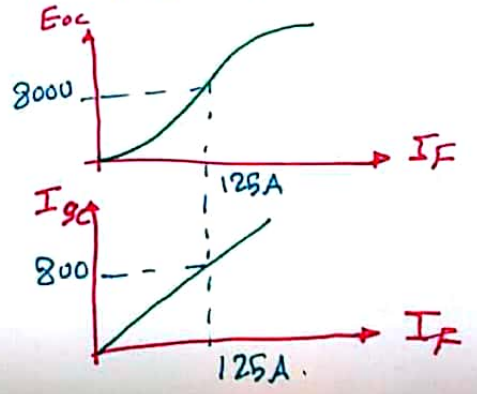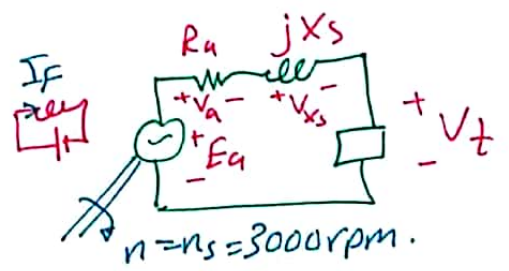

**Q7**



$$E_a = V_t + j I_a X_s$$

$$\Rightarrow I_a = \frac{6000}{\sqrt{3} (208) \times 0.85} = \underline{\underline{19.6 A}}$$

$$E_a = 120 + 19.6 \angle 31.8^\circ (2 \angle 90^\circ)$$

$$E_a = 144.6 \angle 13.3^\circ \text{ volt.}$$

$$|E_a|_{LL} = 250.5 \text{ volt.}$$

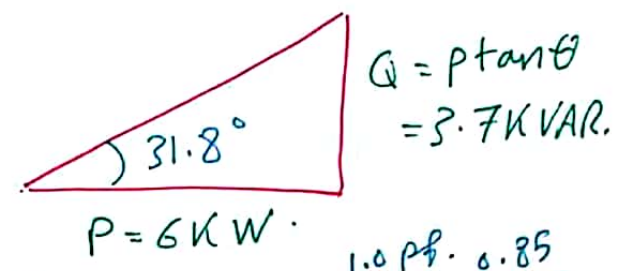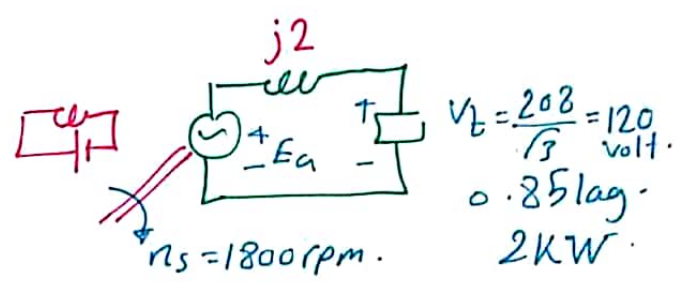

@ n=constant.  $E_a \propto I_f$



$$E_{a2} |_{1.0 \text{ pf}} = 120 \angle 0^\circ + 16.7 (2 \angle 90^\circ)$$

$$\Rightarrow E_{a2} = 124.6 \angle 15.6^\circ$$


$$I_a |_{1.0 \text{ pf}} = \frac{6000}{\sqrt{3} (208) (1)} = \underline{\underline{16.7 A}}$$

$$\frac{\Delta I_f}{I_{f1}} = \frac{I_{f2} - I_{f1}}{I_{f1}} = \frac{E_{a2} - E_{a1}}{E_{a1}}$$
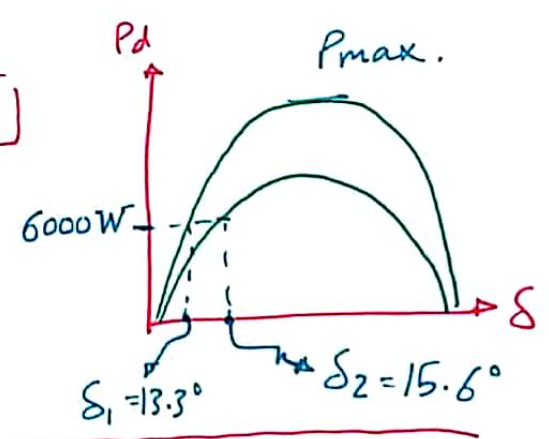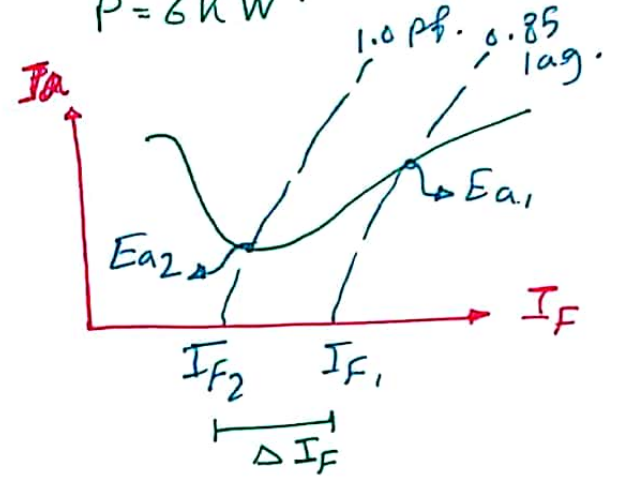
$$= \frac{124.6 - 144.6}{144.6} \times 100\% = \underline{\underline{-13.8\%}}$$



**Q8** find:

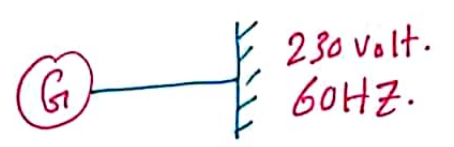

- $E_a$  at rated conditions,  $\text{pf} = 0.8 \text{ lag}$ . ?
- $I_{f2} = 1.2 I_{f1} \Rightarrow |E_{a2}| = 1.2 |E_{a1}|$ , find  $I_{a2}$ ,  $\text{pf}_2$ ,  $Q_2$  ?
- $I_{f3} = I_{f1}$ , find  $P_{max} = 3 \frac{V_t E_a}{X_s}$ ,  $\text{pf}_3$ ,  $I_{a3}$ ,  $Q_3$  ?








a)  $E_a = V_t + jI_a X_s$

$|I_a|_{FL} = \frac{S_{3\phi}}{\sqrt{3}V_L} = 62.8 A.$

$\Rightarrow I_{a1} = 62.8 \angle -36.9^\circ$

$\Rightarrow E_{a1} = 132.8 \angle 0 + 62.8 \angle -36.9^\circ * (1.5 \angle 90) \Rightarrow$

$E_{a1} = 203.8 \angle 21.7^\circ$   
 $|E_{a1}|_{LL} = 353 \text{ volt.}$

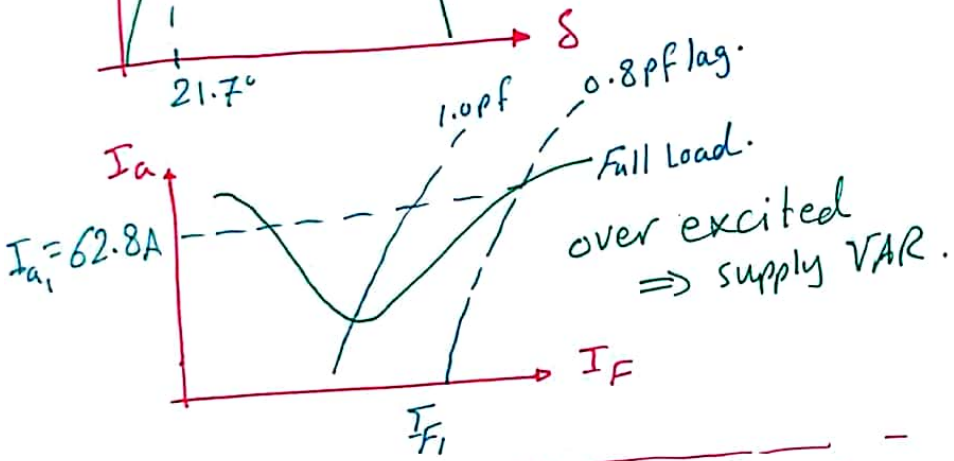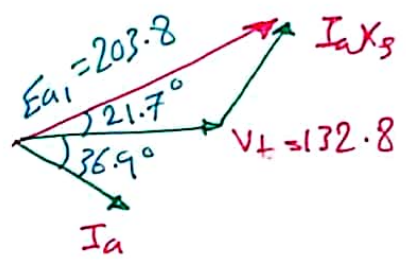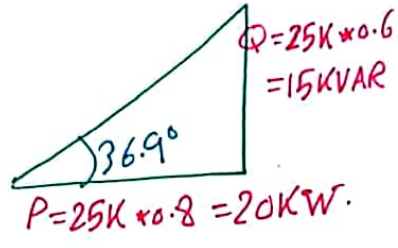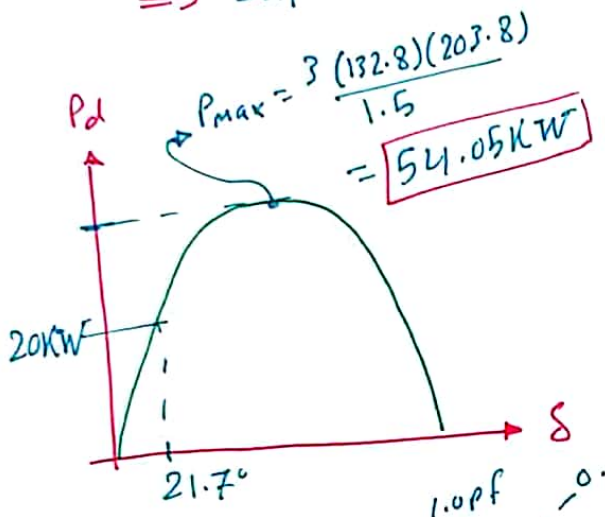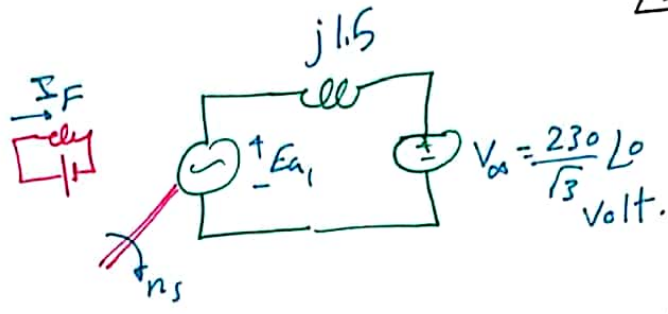

$P_d = \frac{3V_t E_a \sin \delta}{X_s}$   
 $P_d = P_{out} = 3 V_t I_a \cos \theta$

b)  $E_{a2} = 1.2 E_{a1} \Rightarrow E_{a2} = 244.6 \text{ volt.}$

$P_{d1} = P_{d2} = 20 \text{ KW} = \frac{3 (132.8) (244.6)}{1.5} \sin \delta_2$

$\Rightarrow \delta_2 = 17.9^\circ$

for  $I_{a2}$ :

$I_{a2} = \frac{E_{a2} - V_t}{jX_s} \Rightarrow I_{a2} = 83.4 \angle -53.1^\circ A.$

$\Rightarrow E_a = 244.6 \angle 17.9^\circ$




for Q:  
 method (1):

$Q_2 = 3 V_t I_{a2} \sin \theta = P_2 \tan \theta_2$   
 $= 26.5 \text{ KVAR.}$

method (2):

$Q_2 = \frac{3 V_t}{X_s} [E_a \cos \delta - V_t]$   
 $= 26.5 \text{ KVAR.}$

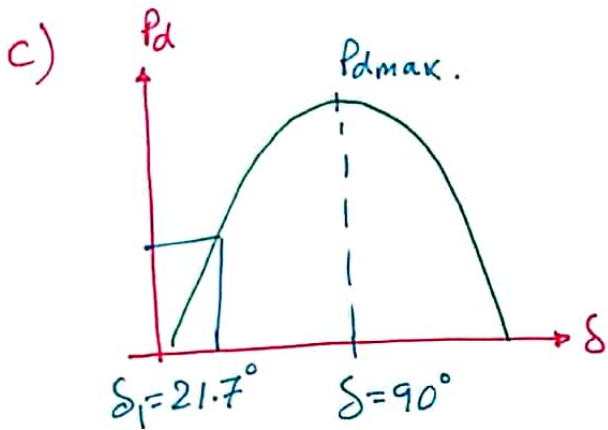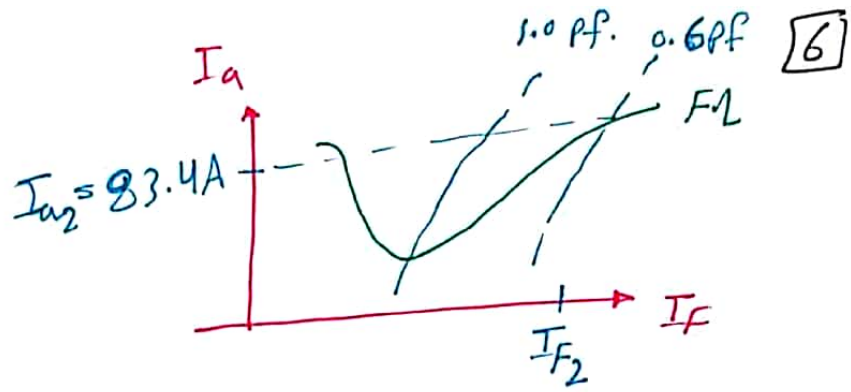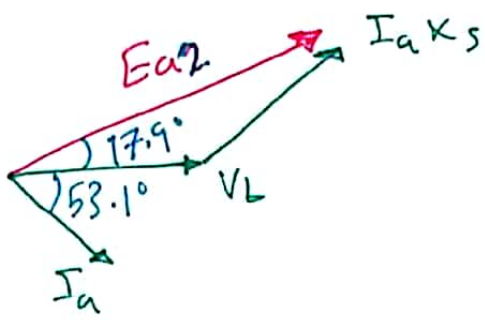$PF = \cos(53.1^\circ) = 0.6 \text{ Lagging.}$



$$|E_{a3}| = |E_{a1}| = 203.8 \text{ volt.}$$

$$\Rightarrow E_{a3} = 203.8 \angle 90^\circ$$

$$I_{a3} = \frac{E_{a3} - V_t}{jX_s} = \frac{203.8 \angle 90^\circ - 132.8 \angle 0^\circ}{1.5 \angle 90^\circ}$$

$$\Rightarrow I_{a3} = 162.2 \angle 33.1^\circ \text{ A}$$


$$PF_3 = \cos 33.1 = 0.838 \text{ Leading.}$$

$$Q_3 = 3V_t I_{a3} \sin \theta$$

$$Q_3 = -44.3 \text{ KVAR}$$

$$-35.27 \text{ KVAR}$$

under excited  
absorbing Q.

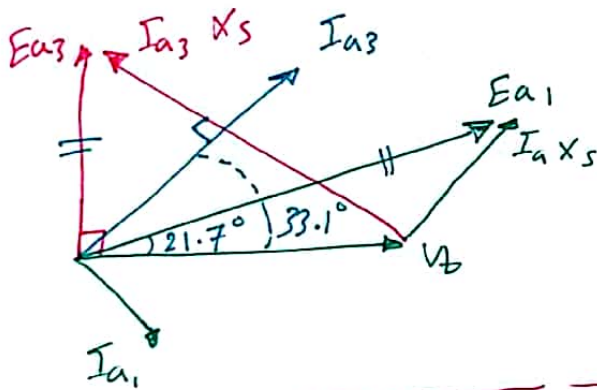


\* additional: if  $I_f$  is reduced without using steady state stability limit  $\Rightarrow$  Find  $I_{a4}$ ,  $PF_4$ ,  $Q_4$ ?

$$P_{max} = 20 \text{ kW} = 3 \frac{(132.8) E_{a4}}{1.5} \Rightarrow E_{a4} = 75.3 \angle 90^\circ \text{ volt.}$$

$$I_{a4} = \frac{E_{a4} - V_t}{jX_s} = \frac{(75.3 \angle 90^\circ) - (132.8 \angle 0^\circ)}{j1.5} \Rightarrow I_{a4} = 101.8 \angle 60.4^\circ \text{ A}$$
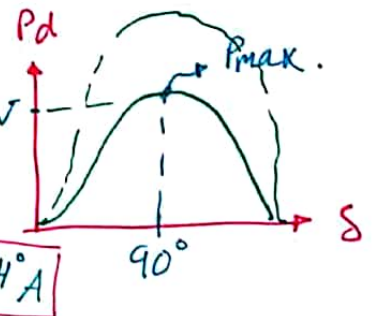
$$PF_4 = \cos(60.4) \Rightarrow PF = 0.494 \text{ Leading.}$$



for  $Q_4$ :

$$Q_4 = 3V_t E_{a4} \sin \theta = 3(132.8)(101.8) \sin(-60.4)$$


$$\Rightarrow Q_4 = -35.3 \text{ KVAR.}$$

Question(9) :

a)  $P_{max} |_{\delta=90^\circ} = \frac{3V_t E_a}{X_s} = \frac{V_{LL} E_{LL}}{X_s}$

$\Rightarrow P_{max} = \frac{12 \times 13 \times 10^6}{15} = 10.4 \text{ MW}$

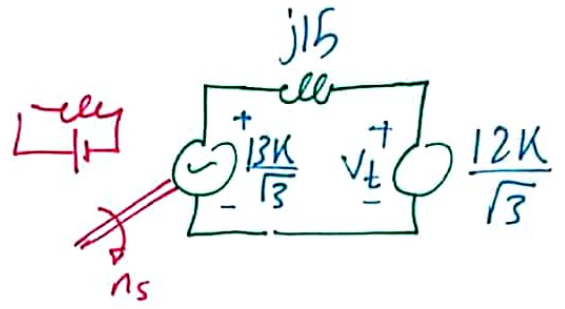$T_{d,max} = \frac{P_{max}}{\omega_s} = \frac{60}{2\pi} \frac{P_{max}}{n_s} \Rightarrow T_{d,max} = 55.1 \text{ kN.m}$   
 1800 rpm.



b)  $I_a = \frac{E_a - V_t}{jX_s} = \frac{\frac{13k}{\sqrt{3}} \angle 90^\circ - \frac{12k}{\sqrt{3}} \angle 0^\circ}{j15} \Rightarrow I_a = 680.9 \angle 42.7^\circ \text{ A}$

PF =  $\cos(42.7) = 0.7349$  Leading.

Q10

$I_a = \frac{\frac{2300}{\sqrt{3}} \angle 15^\circ - \frac{2300}{\sqrt{3}} \angle 0^\circ}{j4}$

$\Rightarrow I_a = 86.6 \angle 7.5^\circ \text{ A}$

PF:  $PF = \cos(7.5) = 0.991$  Leading.


$P_{out} = \frac{3V_t E_a \sin \delta}{X_s} = 3V_t I_a \cos \theta$

$Q_{out} = \frac{3V_t}{X_s} [E_a \cos \delta - V_t] = 3V_t I_a \sin \theta$

solving  $\Rightarrow$   
 $P_{out} = 1.323 \text{ MW}$   
 $Q_{out} = -45.03 \text{ kVAR}$

$\Rightarrow I_a |_{\delta=90^\circ} = \frac{\frac{2300}{\sqrt{3}} \angle 90^\circ - \frac{2300}{\sqrt{3}} \angle 0^\circ}{j4}$

$I_a = 469.5 \angle 45^\circ \text{ A}$

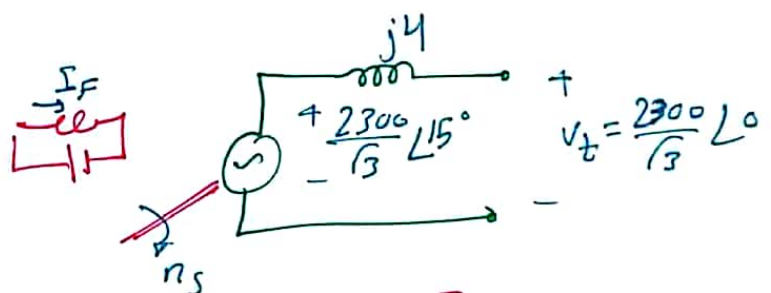



Q11

$I_{a,FL} = \frac{10 \times 10^6}{\sqrt{3} \times 12 \times 10^3} = 481.1 \text{ A}$



$P_{out} = P_{rated} \times PF = 8 \text{ MW}$

$P_{in} = P_{out} + \sum P_{losses} = P_{out} + P_{cu} + P_{rot}$

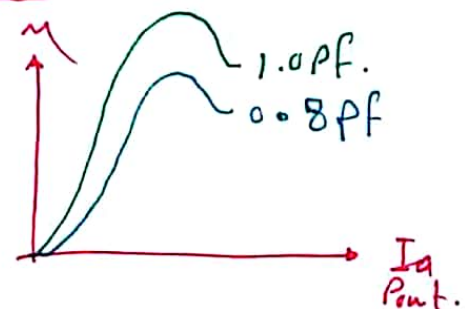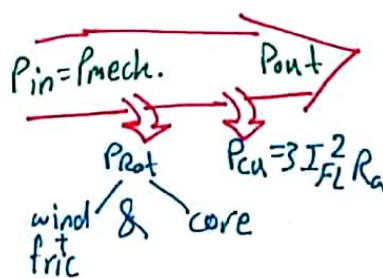$\eta = \frac{P_{out}}{P_{in}} \times 100\% \Rightarrow \eta = 97.6\%$



Question (12):

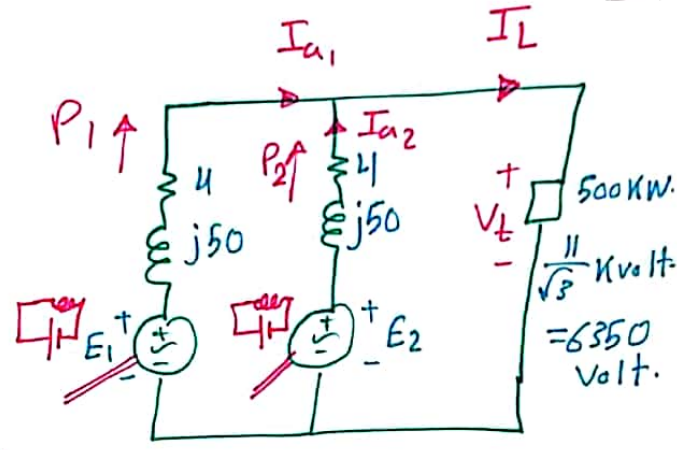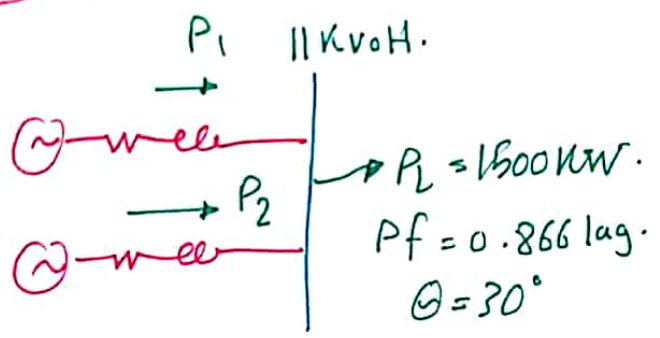

\* since they share the load equally:

$$P_1 = P_2 = \frac{P_L}{2}$$

$$|I_L| = \frac{S_L}{\sqrt{3} V_{LL}} = \frac{P_L / Pf}{\sqrt{3} V_{LL}} = \frac{1500 \text{ kW} / 0.866}{\sqrt{3} \times 11 \text{ kV}} \Rightarrow |I_L| = 90.9 \text{ A}$$

$$\Rightarrow I_L = 90.9 \angle -30^\circ \text{ A}$$

$$I_L = I_1 + I_2$$

$$P_1 = 3 V_t I_1 \cos \theta_1 = \sqrt{3} V_L I_1 \cos \theta_1 = 750 \text{ kW}$$

$$\Rightarrow \cos \theta_1 = Pf_1 = 0.7873 \text{ lagging} \Rightarrow \theta_1 = 38.1^\circ$$

$$I_2 = 90.9 \angle -30^\circ - 50 \angle -38.1^\circ \Rightarrow I_2 = 42 \angle -20.3^\circ \text{ A}$$

$$Pf_2 = \cos(20.3) = 0.937 \text{ lagging}$$

\* we can check the answer:

$$I_1 \cos \theta_1 \stackrel{?}{=} I_2 \cos \theta_2$$

$$50 \times 0.787 \stackrel{?}{=} 42 \times 0.937 \text{ (yes, equal each other)}$$

Now for VR:

$$E_{a1} = V_t + I_{a1} (R_a + jX_s) = 6350 \angle 0^\circ + 50 \angle -38.1^\circ (4 + j50)$$

$$\Rightarrow E_{a1} = 8258.5 \angle 12.9^\circ \text{ volt}$$

$$\%VR = \frac{8258.5 - 6350}{6350} \times 100\% \Rightarrow \%VR = 30.1\%$$

