

# Power Systems Analysis II

---

---

Second Semester  
2018

---

---

Dr. Eyad Feilat  
e. feilat@ju.edu.jo

Notebook:

By. Mohammad  
Abu Hashya.

---

---



**Question # 1**

For the distribution feeder, shown in Fig. Q1, use the per unit method to determine the magnitude of the fault current ( $I_{f-3ph}$ ) in Amperes for a three phase fault at the feeder end. Use a system MVA base of 100 MVA and a voltage base of 13.2 kV at the feeder.

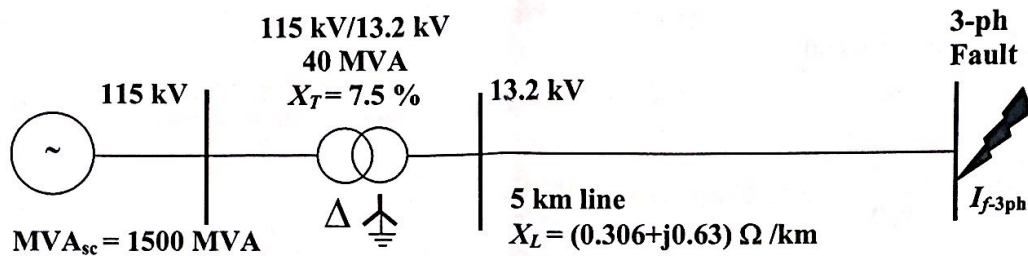


Fig. Q1

**Solution:**

$$X_{sc} = \frac{1}{MVA_{sc-pu}}, MVA_{sc-pu} = \frac{MVA_{sc}}{MVA_{base}} = \frac{1500}{100} = 15 pu, X_{sc} = \frac{1}{15} = 0.067 pu,$$

$$X_{sc\Omega} = X_{scpu} \times X_{base-13.2kV}, X_{base-13.2kV} = \frac{kV_{base}^2}{MVA_{base}} = \frac{13.2^2}{100} = 1.742 \Omega, X_{sc\Omega} = 0.067 \times 1.742 = 0.117 \Omega$$

$$X_{Tnew} = X_{Told} \times \frac{MVA_{basenew}}{MVA_{baseold}} = \frac{7.5}{100} \times \frac{100}{40} = 0.1875 pu, X_{T\Omega} = X_{Tnew} \times X_{base-13.2kV} = 0.1875 \times 1.742 = 0.327 \Omega$$

$$Z_{L1\Omega} = (0.306 + j0.63) \times 5 = 1.53 + j3.15 \Omega, \Rightarrow Z_{L1pu} = \frac{Z_{L1\Omega}}{Z_{base-13.2kV}} = \frac{1.53 + j3.15 \Omega}{1.742 \Omega} = 0.88 + j1.81 pu$$

$$Z_{L1\Omega} = 0.70 \angle 64.1^\circ \times 5 = 3.5 \angle 64.1^\circ \Omega \Rightarrow X_{L1pu} = 2.03 \angle 64.1^\circ pu$$

$$Z_{eq\Omega} = jX_{sc\Omega} + jX_{T\Omega} + Z_{L1\Omega} = j0.117 + j0.327 + 1.53 + j3.15 = 1.53 + j3.59 \Omega = 3.9 \angle 66.9^\circ \Omega$$

$$Z_{eq1pu} = jX_{sc1pu} + jX_{T1pu} + Z_{L1pu} = j0.067 + j0.188 + 0.88 + j1.81 = 0.88 + j2.07 pu = 2.24 \angle 66.9^\circ pu$$

$$I_{f3phA} = \frac{E_1}{Z_{eq1}} = \frac{\frac{13.2 \times 10^3}{\sqrt{3}} \angle 0^\circ V}{3.9 \angle 66.9^\circ \Omega} = \frac{7621 \angle 0^\circ V}{3.9 \angle 66.9^\circ \Omega} = 1954.1 \angle -66.9^\circ A$$

$$I_{f3phpu} = \frac{E_1}{Z_{eq1pu}} = \frac{1.0 \angle 0^\circ V}{2.24 \angle 66.9^\circ \Omega} = 0.446 \angle -66.9^\circ pu$$

$$I_{base-13.2kV} = \frac{MVA_{base}}{\sqrt{3}V_{LL}} = \frac{100 \times 1000}{\sqrt{3} \times 13.2} = 4373.9 A$$

$X_{sc} =$	<b>0.067 pu</b>
$X_T =$	<b>0.1875 pu</b>
$Z_{TL} =$	<b>0.88 + j 1.81 Pu</b>
$Z_{eq} =$	<b>0.88 + j 2.07 Pu</b> <b>2.24 <math>\angle</math> 66.9° pu</b>
$I_{f3ph} =$	<b>0.446 pu</b>
$I_b =$	<b>4373.9 A</b>
$I_{f3ph} =$	<b>1954.1 A</b>

**Question # 2:**

For the system shown in Fig. Q2, and starting from the data that are given, calculate the three-phase and single-line-ground fault in Amperes at the Buses 3, 2, and 1 using:

- The Ohmic method referring the system to the 115 kV bus.
- The per-unit method.

**Solution:**

- The Ohmic method

$$Z_{sc} = \frac{V_{LL}^2}{MVA_{sc}} = \frac{(115)^2}{950} = 13.92 \Omega \text{ referred to } 115 \text{ kV}$$

$$Z_{transformer} = Z_{pu} \times Z_{base}$$

$$Z_{base} = \frac{V_{LL}^2}{MVA-TX} = \frac{(115)^2}{25} = 529 \Omega \text{ referred to } 115 \text{ kV}$$

$$Z_{transformer} = \frac{4.8}{100} \times 529 = 25.39 \Omega \text{ referred to } 115 \text{ kV}$$

$$Z_{TL} = 1.125 \times \left( \frac{115}{13.2} \right)^2 = 85.35 \Omega \text{ referred to } 115 \text{ kV}$$

- Three-Phase Fault

$$\begin{aligned} I_{faultC} &= \frac{115 \times 10^3}{\sqrt{3}(13.92 + 25.39 + 83.35)} \\ &= 532.6 \text{ A referred to } 115 \text{ kV} \\ &= 532.6 \times \left( \frac{115}{13.2} \right) \\ &= 4640.2 \text{ A referred to } 13.2 \text{ kV} \end{aligned}$$

$$\begin{aligned} I_{faultB} &= \frac{115 \times 10^3}{\sqrt{3}(13.92 + 25.39)} \\ &= 1689.0 \text{ A referred to } 115 \text{ kV} \\ &= 1689.0 \times \left( \frac{115}{13.2} \right) \\ &= 14714.8 \text{ A referred to } 13.2 \text{ kV} \end{aligned}$$

$$\begin{aligned} I_{faultA} &= \frac{115 \times 10^3}{\sqrt{3}(13.92)} \\ &= 4769.8 \text{ A referred to } 115 \text{ kV} \end{aligned}$$

The L-G Fault = 0, because the TX is not grounded

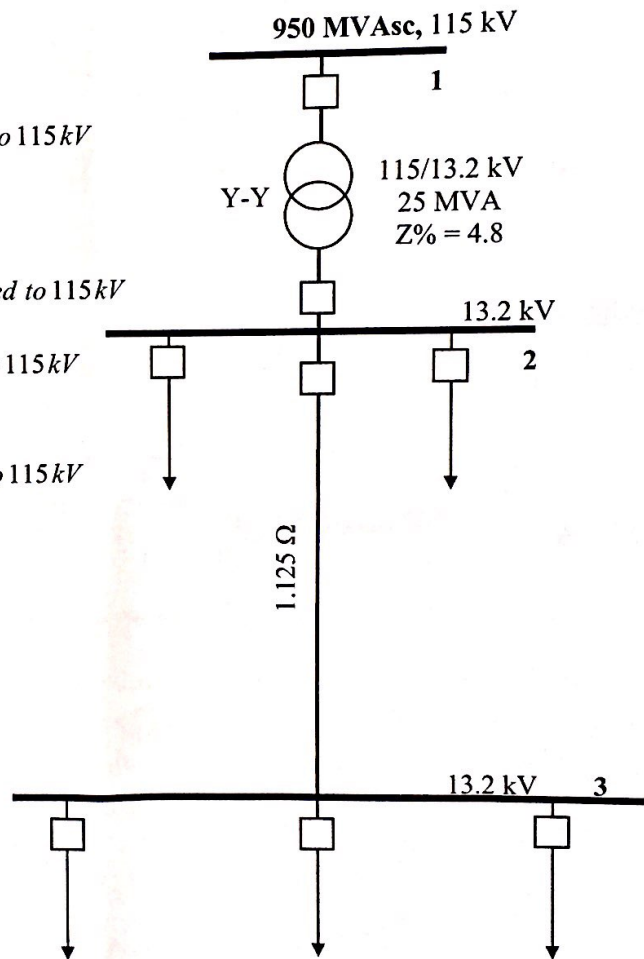


Fig. Q2

b. The per-unit method

Let  $MVA_{base} = 25 \text{ MVA}$

$kV_{base} = 13.2 \text{ kV}$  at the primary feeder.

$$Z_{base-HV} = \frac{V_{LL}^2}{MVA_{base}} = \frac{(115)^2}{25} = 529 \Omega \text{ referred to } 115 \text{ kV}$$

$$Z_{base-LV} = \frac{V_{LL}^2}{MVA_{base}} = \frac{(13.2)^2}{25} = 6.97 \Omega \text{ referred to } 13.2 \text{ kV}$$

$$Z_{TX-pu} = \frac{4.8}{100} = 0.048 \text{ pu}$$

$$MVA_{sc-pu} = \frac{MVA_{sc}}{MVA_{base}} = \frac{950}{25} = 38 \text{ pu}$$

$$Z_{sc-pu} = \frac{1}{MVA_{sc-pu}} = \frac{1}{38} = 0.0263 \text{ pu}$$

$$Z_{Line-pu} = \frac{1.125}{6.97} = 0.1614 \text{ pu}$$

a. Three-Phase Fault

$$V_{C-pu} = \frac{V_c}{V_{C-base}} = \frac{13.2}{13.2} = 1 \text{ pu}$$

$$I_{fault-C} = \frac{V_{C-pu}}{\sum Z} = \frac{V_{C-pu}}{Z_{Line} + Z_{TX} + Z_{sc}} = \frac{1.0}{0.1614 + 0.0263 + 0.048} = 4.24 \text{ pu}$$

$$I_{base-13.2kV} = \frac{MVA_{base}}{\sqrt{3} \times kV_{Base}} = \frac{25 \times 1000}{\sqrt{3} \times 13.2} = 1093.47 \text{ A}$$

$$I_{fault-C(A)} = I_{fault-C} \times I_{base-13.2kV} = 4.24 \text{ pu} \times 1093.47 \text{ A} = 4638.6 \text{ A}$$

$$V_{B-pu} = \frac{V_B}{V_{B-base}} = \frac{13.2}{13.2} = 1 \text{ pu}$$

$$I_{fault-B} = \frac{V_{B-pu}}{\sum Z} = \frac{V_{B-pu}}{Z_{TX} + Z_{sc}} = \frac{1.0}{0.0263 + 0.048} = 13.46 \text{ pu}$$

$$I_{base-13.2kV} = \frac{MVA_{base}}{\sqrt{3} \times kV_{Base}} = \frac{25 \times 1000}{\sqrt{3} \times 13.2} = 1093.47 \text{ A}$$

$$I_{fault-B(A)} = I_{fault-B} \times I_{base-13.2kV} = 13.46 \text{ pu} \times 1093.47 \text{ A} = 14713.8 \text{ A}$$

$$V_{A-pu} = \frac{V_A}{V_{A-base}} = \frac{115}{115} = 1 \text{ pu}$$

$$I_{fault-A} = \frac{V_{A-pu}}{\sum Z} = \frac{V_{A-pu}}{Z_{sc}} = \frac{1.0}{0.02638} = 38 \text{ pu}$$

$$I_{base-115kV} = \frac{MVA_{base}}{\sqrt{3} \times kV_{Base}} = \frac{25 \times 1000}{\sqrt{3} \times 115} = 125.5 \text{ A}$$

$$I_{fault-A(A)} = I_{fault-A} \times I_{base-115kV} = 38 \text{ pu} \times 125.5 \text{ A} = 4769.4 \text{ A}$$

### Question # 3

A portion of an 11 kV radial system is shown in Fig.Q3. The system may be operated with one rather than two source transformers under certain operating conditions. Assume high voltage bus of transformer is an infinite bus. Protection system for three-phase and line-to-line faults has to be designed. Transformer and Transmission line reactances in ohms are referred to the 11 kV side as shown in the Fig. Q3. Calculate the maximum fault currents ( $I_{fmaxi}$ ) and minimum fault currents ( $I_{fmini}$ ) at bus 1-5.

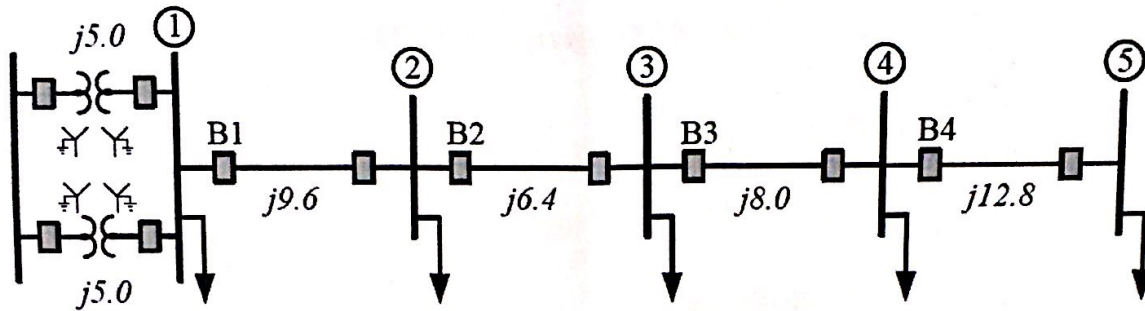


Fig. Q3

#### Solution Hints:

1. Maximum fault current will occur for a three-phase with both transformers in service.
2. Minimum fault in this case is assumed for a line-to-line fault. A line-to-line fault produces a fault current equal to  $\sqrt{3}/2$  times the three-phase fault. Also the minimum fault current happens for line-to-line faults with one transformer in service.

The maximum and minimum fault currents are given below for faults at bus 1-5

Fault Level	Fault at Bus				
	1	2	3	4	5
Max Fault Current (A)	2540	525	343	240	162
Min Fault Current (A)	1100	377	262	190	132

#### Max Fault Current (A)

$$|I_{f3ph1}| = \frac{V}{Z_{eq1}} = \frac{11 \times 10^3 / \sqrt{3}}{2.5} = 2540 \text{ A}$$

$$|I_{f3ph2}| = \frac{V}{Z_{eq2}} = \frac{11 \times 10^3 / \sqrt{3}}{(2.5 + 9.6)} = 525 \text{ A}$$

$$|I_{f3ph3}| = \frac{V}{Z_{eq3}} = \frac{11 \times 10^3 / \sqrt{3}}{(2.5 + 9.6 + 6.4)} = 343 \text{ A}$$

$$|I_{f3ph4}| = \frac{V}{Z_{eq4}} = \frac{11 \times 10^3 / \sqrt{3}}{(2.5 + 9.6 + 6.4 + 8)} = 240 \text{ A}$$

$$|I_{f3ph5}| = \frac{V}{Z_{eq5}} = \frac{11 \times 10^3 / \sqrt{3}}{(2.5 + 9.6 + 6.4 + 8 + 12.8)} = 162 \text{ A}$$

#### Min Fault Current (A)

$$|I_{fLL1}| = 0.866 \times \frac{V}{Z_{eq1}} = 0.866 \times \frac{11 \times 10^3 / \sqrt{3}}{5} = 1100 \text{ A}$$

$$|I_{fLL2}| = 0.866 \times \frac{V}{Z_{eq2}} = 0.866 \times \frac{11 \times 10^3 / \sqrt{3}}{(5 + 9.6)} = 377 \text{ A}$$

$$|I_{fLL3}| = 0.866 \times \frac{V}{Z_{eq3}} = 0.866 \times \frac{11 \times 10^3 / \sqrt{3}}{(5 + 9.6 + 6.4)} = 262 \text{ A}$$

$$|I_{fLL4}| = 0.866 \times \frac{V}{Z_{eq4}} = 0.866 \times \frac{11 \times 10^3 / \sqrt{3}}{(5 + 9.6 + 6.4 + 8)} = 190 \text{ A}$$

$$|I_{fLL5}| = 0.866 \times \frac{V}{Z_{eq5}} = 0.866 \times \frac{11 \times 10^3 / \sqrt{3}}{(5 + 9.6 + 6.4 + 8 + 12.8)} = 132 \text{ A}$$

**\* Fault Calculation :**

- Three main types of fault :
    - 3-ph fault.
    - L-G fault.
    - L-L fault.
  - Three main parts of any power system : Generation - Transmission - Distribution.
- Source → Load called "down-stream."  
 Load → Source called "up-stream."



\* The voltages 400V, 380V, 415V are called: "Low Tension Class" OR "Low Voltage class".

\* The voltages 11KV, 33KV are called: "Medium Voltage Class".

132KV ⇒ "High Voltage"      >220KV ⇒ "Extra High Voltage".

Tutorial #1 :

Q1

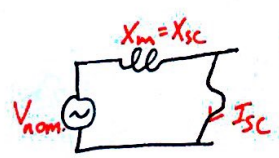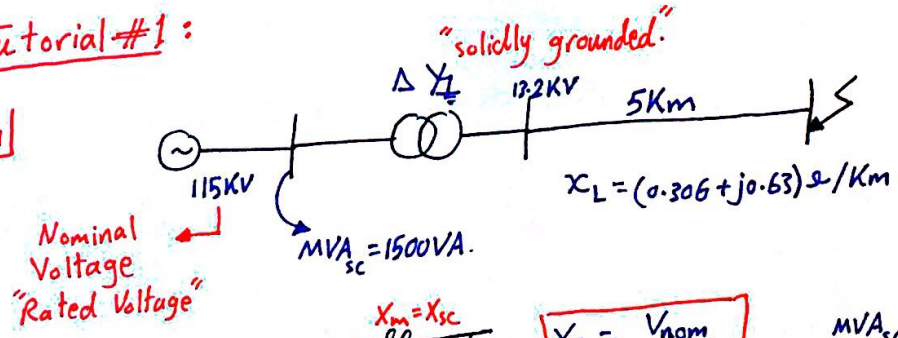

$$X_s = \frac{V_{nom}}{I_{sc}}$$

$$MVA_{sc} = \sqrt{3} \frac{V_{LL, nom}}{I_{sc}}$$

$$X_{sc} = \frac{V_{LL, nom} / \sqrt{3}}{I_{sc, pu}}$$

• from  $MVA_b$  &  $KV_b$  one can find  $I_b$  &  $Z_b$ .

$$Z_b = \frac{(KV_{LL})^2}{MVA_b}$$

$$I_b = \frac{MVA_b}{\sqrt{3} V_{LL}}$$

- Transformer Ratio : it is the effective turns ratio. "Line-line voltages" Ratio.
- Turns Ratio : Ratio of the phase voltages.

$$X_L = 5 \text{ Km} * (0.306 + j0.63) \frac{\Omega}{\text{Km}} \Rightarrow \underline{\underline{X_L = 1.53 + j3.15 \Omega}}$$

$$Z_b |_{13.2KV} = \frac{(13.2)^2}{100} = \underline{1.742 \Omega}$$

$$X_L (PU) = \frac{1.53 + j3.15}{1.742} = \underline{2.03 \angle 64.1^\circ} \text{ PU}$$

$$X_{T_{new}} = X_{T_{old}} \frac{S_{new}}{S_{old}} = 0.075 * \frac{100}{40} = \underline{0.1875 \text{ PU}} \quad \text{OR} \quad Z_{T_{new}} = \underline{j0.1875 \text{ PU}}$$

\*  $X_{sc}$  can be found by two methods:

• method (1):

$$X_{sc \text{ PU}} = \frac{1}{MVA_{sc \text{ PU}}}$$

$$MVA_{sc \text{ PU}} = \frac{1500}{100} = 15 \text{ PU} \Rightarrow X_{sc \text{ PU}} = \frac{1}{15} = \underline{0.067 \text{ PU}} \quad \#$$

• method (2):

alternatively:  $X_{sc} = \frac{(KV_{LL})^2}{MVA_{sc}} = \frac{115^2}{1500} = \underline{8.81 \Omega}$

$$Z_{b \text{ HV}} = Z_b |_{115KV} = \frac{115^2}{100} = \underline{132.25 \Omega} \Rightarrow Z_{sc \text{ PU}} = j \frac{8.81}{132.25} = \underline{j0.067 \text{ PU}} \quad \#$$

\* proof for  $X_{sc \text{ PU}} = \frac{1}{MVA_{sc \text{ PU}}}$ :

$$S_{sc \text{ PU}} = V_{pu} I_{sc \text{ PU}} ; V_{pu} = 1 \angle 0 \Rightarrow S_{sc \text{ PU}} = I_{sc \text{ PU}}$$


$$X_{pu} = \frac{V/V_b}{I/I_b} = \frac{1}{I_{sc \text{ PU}}} = \frac{1}{S_{sc \text{ PU}}} \quad \#$$

The equivalent circuit as follows:


$$Z_{eq} = jX_{sc} + jX_T + Z_L = 0.38 + j2.07 \text{ PU} = \underline{2.24 \angle 66.9^\circ} \text{ PU}$$

$$I_{sc \text{ 3}\phi} = \frac{1}{Z_{eq}} = \frac{1}{2.24 \angle 66.9^\circ} = \underline{0.442 \angle -66.9^\circ} \text{ PU}$$
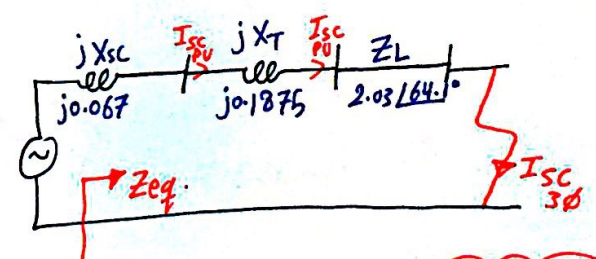
$$I_b = \frac{MVA_b}{\sqrt{3} V_{LL_b}} = \frac{100 \times 10^6}{\sqrt{3} \times 13.2 \times 10^3} = \underline{4373.9 \text{ A}}$$



$$\Rightarrow I_{sc(A)} = I_{sc \text{ PU}} \times I_b |_{13.2K} \Rightarrow \underline{I_{sc(LV)} = 1954.1 \text{ A}}$$

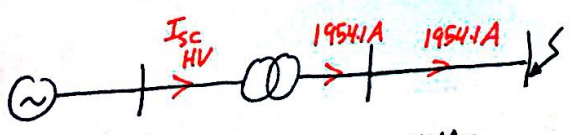

$$I_{LV} = \frac{MVA_T}{\sqrt{3} V_{LL_{LV}}}, \quad I_{HV} = \frac{MVA_T}{\sqrt{3} V_{LL_{HV}}}$$


$$\Rightarrow \frac{I_{HV}}{I_{LV}} = \frac{V_{LL_{LV}}}{V_{LL_{HV}}} = \frac{13.2}{115}$$

$$\Rightarrow I_{sc \text{ HV}} = 1954.1 \times \frac{13.2}{115}$$

$$\underline{I_{sc \text{ HV}} = 224.3 \text{ A}}$$

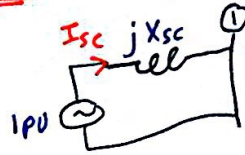Q2] for fault @ Bus ①:

$$I_{sc_{3P①}} = \frac{MVA_{sc}}{\sqrt{3} V_{LL}} = \frac{950 \times 10^6}{\sqrt{3} \times 115 \times 10^3} = \underline{4769.4 \text{ A}}$$



another method to find  $I_{sc_{3P①}}$ :

$MVA_b = 100$

$$MVA_{sc_{PU}} = \frac{950}{100} = 9.5 \text{ PU}$$


$$I_{sc} = MVA_{sc_{PU}} \Rightarrow I_{sc} = \frac{1}{X_{sc}} = 9.5 \text{ PU}$$

$$I_{b_{115KV}} = \frac{MVA_b}{\sqrt{3} V_{LL}} = 502 \text{ A}$$

$$X_{sc} = \frac{1}{9.5} \text{ PU}$$

$$I_{sc(A)} = I_{sc_{PU}} \times I_b = 9.5 \times 502 \Rightarrow I_{sc(A)} = \underline{4769.4 \text{ A}} \#$$

Equivalent cct as follows:

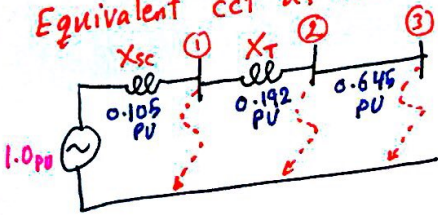

• Using PU concept:

$$X_{T_{old}} = \frac{4.8}{100} = 0.048 \text{ PU}$$

$$X_{T_{new}} = 0.048 \times \frac{100}{25} = 0.192 \text{ PU}$$

$$X_{TL_{PU}} = \frac{X_{L\Omega}}{X_b} = \frac{1.125}{1.7424} = 0.645 \text{ PU}$$

$$X_b = \frac{V_{LL}^2}{S_b} = \frac{(13.2)^2}{100} = 1.7424 \Omega$$

for fault @ bus ②:

$$I_{sc_{3P②}} = \frac{1}{0.105 + 0.192} = 3.367 \text{ PU}$$


$$I_b = \frac{100 \times 10^6}{\sqrt{3} \times 13.2 \times 10^3} = 4373.8 \text{ A}$$

$$\Rightarrow I_{sc_{3P②}} = 3.367 \times 4373.8 = \underline{14.73 \text{ KA}} \#$$

for fault @ Bus ③:

$$I_{sc_{3P③}} = \frac{1}{0.105 + 0.192 + 0.645} = 1.06 \text{ PU} \Rightarrow I_{sc_{3P③}} = 1.06 \times 4373.8 = \underline{4636.2 \text{ A}} \#$$

• Using Ohmic concept:

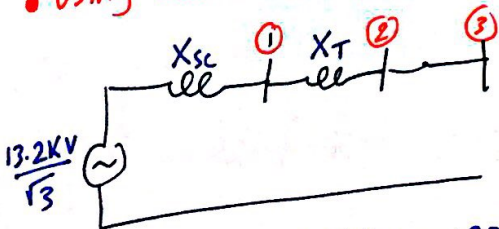

$$X_{sc} = 0.105 \times 1.74 = 0.1827 \Omega$$

$$X_T = 0.192 \times 1.74 = 0.334 \Omega$$

$$X_L = 1.125 \Omega \quad \frac{115}{13.2} = \underline{8.7}$$

for fault @ Bus ①:

$$I_{sc''①} = \frac{13.2 \times 10^3 / \sqrt{3}}{0.1827} = \underline{41.71 \text{ KA}}$$


$$I_{sc①} = \frac{41.71 \text{ K}}{8.7} = \underline{4794.3 \text{ A}}$$

$$I_{sc②} = \frac{13.2 \times 10^3 / \sqrt{3}}{0.1827 + 0.334} = \underline{14749.4 \text{ A}}$$

$$I_{sc③} = \frac{13.2 \times 10^3 / \sqrt{3}}{0.1827 + 0.334 + 1.125} = \underline{4642.2 \text{ A}}$$



\* for L-L fault:

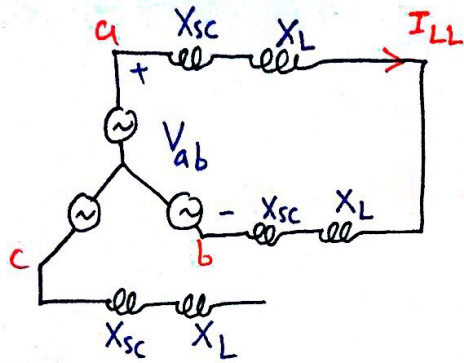

$$I_{LL} = \frac{|V_{ab}|}{2(X_L + X_{sc})} \quad ; \quad X_{eq} = X_L + X_{sc}$$

$$\Rightarrow I_{LL} = \frac{|V_{ab}|}{2 X_{eq}} = \frac{\sqrt{3} V_{ph}}{2 X_{eq}} \quad ; \quad I_{3\phi f} = \frac{V_{ph}}{X_{eq}}$$

$$\Rightarrow I_{LL} = \frac{\sqrt{3}}{2} \times I_{3\phi f} \Rightarrow I_{LL} = 0.866 I_{3\phi f}$$

\*Note:



in fault calculations one consider the system "flat" sand we neglect the loads.

Now for L-G Fault:

$$I_{LG} = I_{a1} + I_{a2} + I_{a0} \Rightarrow (I_a^+ + I_a^- + I_a^0) = I_{LG}$$

Here we need :  
 +ve seq. network.  
 -ve seq. network.  
 zero seq. network.

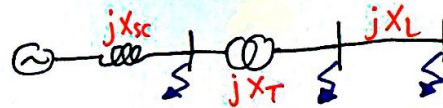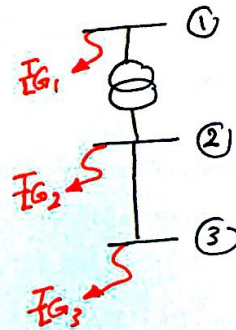
• if the system is Balanced, Then we just have +ve seq. network.




The +ve seq. Network is given by:




The -ve seq. Network is given by:

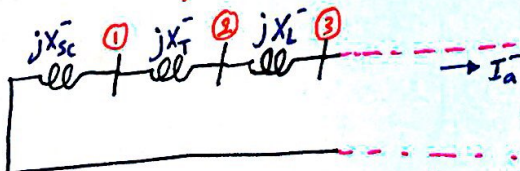

The 0-seq. Network is given by:

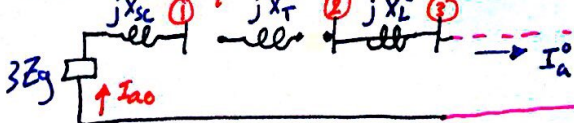

for the following system:

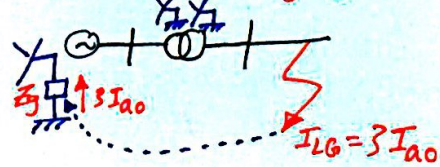

$$I_a = I_a^+ + I_a^- + I_a^0$$

$$I_b = I_b^+ + I_b^- + I_b^0$$

$$I_c = I_c^+ + I_c^- + I_c^0$$


since there is an o/c:

$$I_{LG} = \text{Zero}$$


• if the previous circuit was closed, then the current is found by:

$$I_{LG} = 3I_{a0} = \frac{3V_{ph}}{\sum Z^+ + \sum Z^- + \sum Z^0}$$

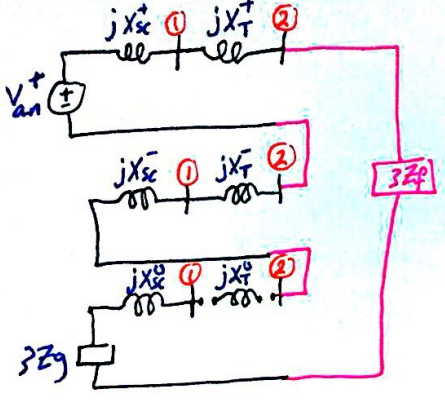• The connection for L-G fault @ Bus 2 as follows:



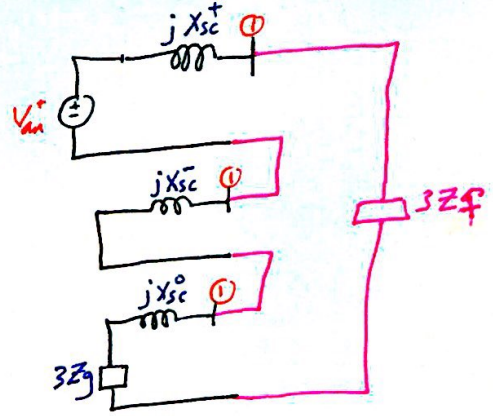
• The connection for L-G fault @ Bus 1 as follows:



Note:

- ⇒ Reflecting the impedance to the Low voltage side, it will decrease ( $/a^2$ ).
- ⇒ Reflecting the impedance to the High voltage side, it will increase ( $*a^2$ ).



\*Review:

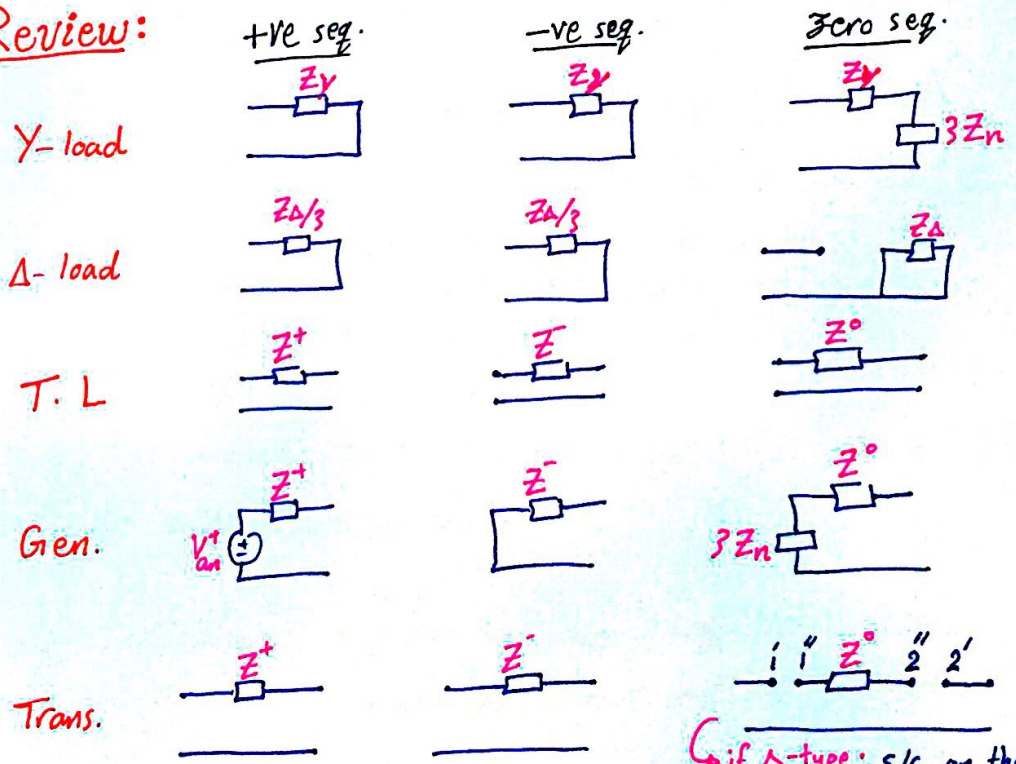

↳ if Δ-type: s/c on the Δ-side 1 or 2  
 if Y-type: connect 3Z\_n if it is grounded.

Q<sub>3</sub> for Fig. Q<sub>3</sub> represent a "distribution substation".

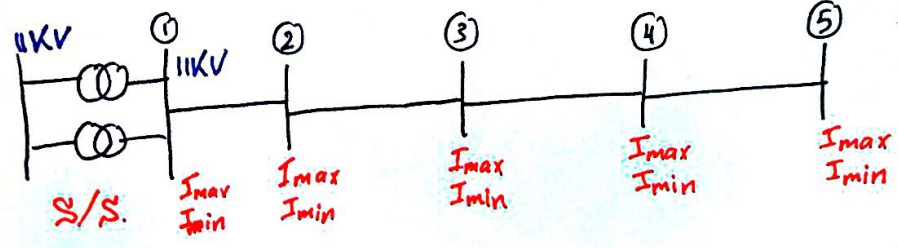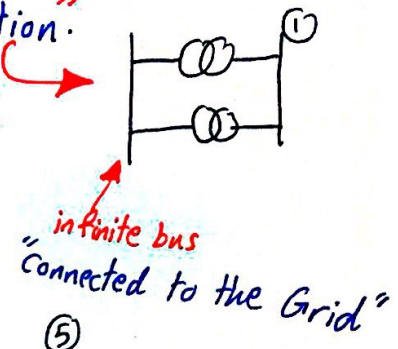for substation we will use the shortcut "S/S".



$I_{min}$  is found when one transformer connected.  
 $I_{max}$  is found when Both transformers are in service.

$$I_{f_{max}}^{(1)} = \frac{11 \times 10^3 / \sqrt{3}}{2.5} = 2540 \text{ A.}$$

$$I_{f_{max}}^{(2)} = \frac{11 \times 10^3 / \sqrt{3}}{2.5 + 9.6} = 525 \text{ A.}$$

$$I_{f_{max}}^{(3)} = \frac{11 \times 10^3 / \sqrt{3}}{2.5 + 9.6 + 6.4} = 343 \text{ A.}$$

$$I_{f_{max}}^{(4)} = \frac{11 \times 10^3 / \sqrt{3}}{2.5 + 9.6 + 6.4 + 8} = 240 \text{ A.}$$

$$I_{f_{max}}^{(5)} = \frac{11 \times 10^3 / \sqrt{3}}{2.5 + 9.6 + 6.4 + 8 + 12.8} = 162 \text{ A.}$$

Note:

$\Rightarrow I_{min}$  is found for  $I_{LL}$  with one Tx in service

$$I_{f_{min}}^{(1)} = \frac{11 \times 10^3 / \sqrt{3}}{5} \times \frac{\sqrt{3}}{2} = 1100 \text{ A.}$$

$$I_{f_{min}}^{(2)} = \frac{11 \times 10^3 / \sqrt{3}}{5 + 9.6} \times \frac{\sqrt{3}}{2} = 377 \text{ A.}$$

$$I_{f_{min}}^{(3)} = \frac{11 \times 10^3 / \sqrt{3}}{5 + 9.6 + 6.4} \times \frac{\sqrt{3}}{2} = 262 \text{ A.}$$

$$I_{f_{min}}^{(4)} = \frac{11 \times 10^3 / \sqrt{3}}{5 + 9.6 + 6.4 + 8} \times \frac{\sqrt{3}}{2} = 190 \text{ A.}$$

$$I_{f_{min}}^{(5)} = \frac{11 \times 10^3 / \sqrt{3}}{5 + 9.6 + 6.4 + 8 + 12.8} \times \frac{\sqrt{3}}{2} = 132 \text{ A.}$$

\* The minimum current is represented by L-L fault current since it is smaller than 3-ph fault current. (i.e.  $I_{f_{LL}} = 0.866 \times I_{f_{3-ph}}$ ).

**\* Power Systems Protection:**

• The Relay that connected to the CT has a symbol "51" which indicates that is an over-current Relay;

• Voltage Transformer: primary has large # of turns.  
 secondary has small # of turns.

\* Instrument Transformer:



- CCVT  $\equiv$  Capacitor Couple Voltage Transformer.
- IED-Relay  $\equiv$  Intelligent Electronic Device.

\* Disconnect Switch  $\Rightarrow$  "Isolator".

• Remember:  $\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$  if  $I_2 \ll I_1 \Rightarrow N_2 \gg N_1$

\* Voltage Transformer:

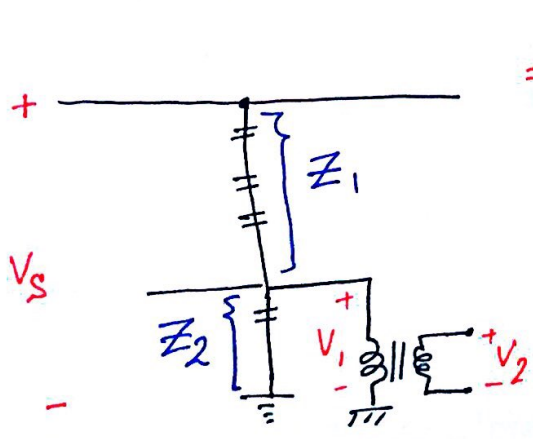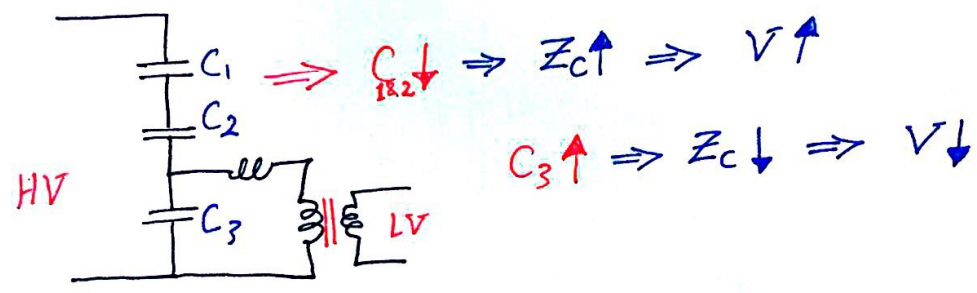we step-down the voltage using capacitor divider:




$$\Rightarrow V_1 = V_s \frac{Z_2}{Z_1 + Z_2}$$

$$= V_s \frac{1/\omega C_2}{\frac{1}{\omega C_1} + \frac{1}{\omega C_2}} = V_s \frac{1}{\frac{C_2}{C_1} + 1}$$


$$\Rightarrow V_1 = V_s \frac{C_1}{C_1 + C_2}$$

\* Electromagnetic Voltage Transformer:

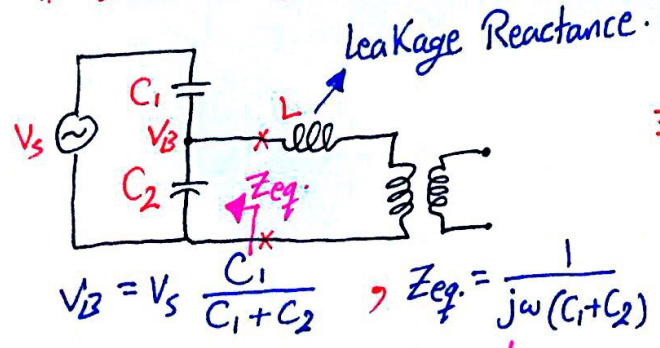

$$V_B = V_s \frac{C_1}{C_1 + C_2} \Rightarrow Z_{eq} = \frac{1}{j\omega(C_1 + C_2)}$$

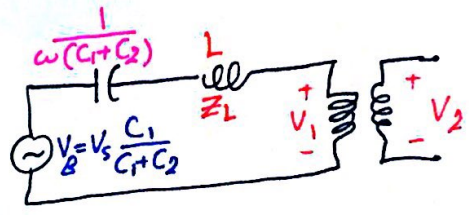@ High Freq. it will act as "LPF". ( $Z_L = j\omega L$ )



@ Resonance:

$$\omega L = \frac{1}{\omega(C_1 + C_2)}$$

$$\Rightarrow L = \frac{1}{\omega^2(C_1 + C_2)}$$

To deal with the phase shift.

\* VT Ratio:

The ratio 1:1 is used for "Isolation".

\* Current Transformer:

• Doughnut type:

⇒ what will happen when the CT circuit is opened in loading condition? it will induce a very High Voltage with a large sparks which will cause an explosion if the CT is isolated by oil.


• The oil is used for: cooling & Isolation.

• CT ratio:


Ex. for 1000:1 A

$$\frac{N_1}{N_2} = \frac{I_2}{I_1} \Rightarrow \frac{N_1}{N_2} = \frac{1}{1000} \text{ so need } 1:1000 \text{ turns.}$$

• CT - Excitation Characteristics:

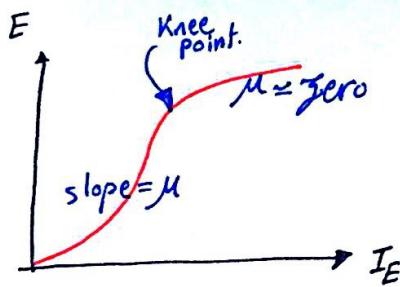

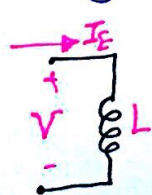$\mu \equiv$  Permeability: it is a measure of how it is ease to establish the magnetic flux.




$$L = \frac{N^2}{\mathcal{R}} ; \mathcal{R} \equiv \text{Reluctance} = \frac{l}{\mu A}$$

$$\Rightarrow L = \frac{N^2 \mu A}{l}$$

• we always work below the knee point.

• CT-General Equivalent Circuit:

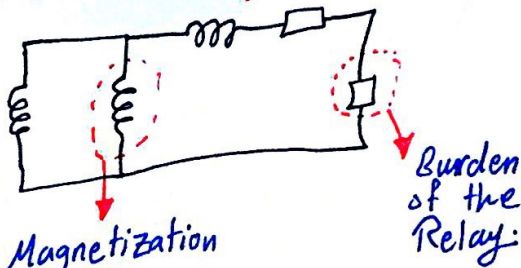

Magnetization Branch  
it is the source of the error in the CT.

\* CT Ratio  $\equiv$  CTR:  $\frac{N_p}{N_s} = \frac{I_s}{I_p}$

**Question # 1:**


For the power system shown below, use either the Ohmic or PU method to calculate the maximum 3-phase fault currents at buses 1, 2, 3, 4 and 5. For the PU method use an MVA base  $S_b$  of 100 MVA and a base voltage  $V_b$  of 13.8 kV at bus # 1.

Handwritten calculations:

$$X_T = \frac{(13.8)^2}{15}$$

$$I_{sc\ max} = \frac{(13.8)^2}{250}$$

$$I_{sc\ min} = \frac{(13.8)^2}{200}$$

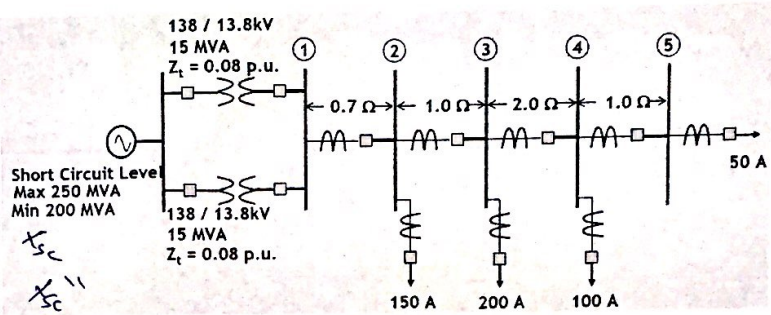


Bus #	①	②	③	④	⑤
$I_{fmax}$ (A)					

**Question # 2:**

For the system shown below, use the per unit method to find the fault line currents in Amperes seen on the HV side of the transformer with those seen by at the fault location (LV side) for:

- Three phase fault,  $I_{F3ph-LV}$  and  $I_{F3ph-HV}$ .
- Line-to-line fault,  $I_{FLL-LV}$  and  $I_{FLL-HV}$ .
- Line-to-ground fault,  $I_{FLG-LV}$  and  $I_{FLG-HV}$ .

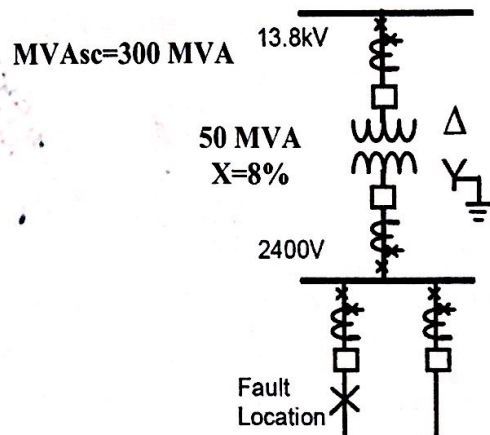
Use an  $MVA_{base} = 50$  MVA and  $kV_{base} = 13.8$  kV at the HV side of the transformer .



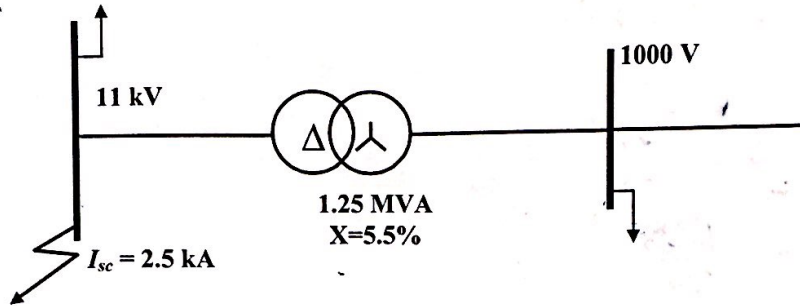**Question # 3:**

For the system shown below, consider a base MVA=1.25 MVA, then calculate:


- The short-circuit MVA at the 11 kV bus,  $MVA_{sc}$ .
- The system short circuit impedance  $X_{sc}$  in Ohms and p.u.
- Total system impedance in Ohms and p.u. from the source to the 1000 V bus,  $X_{tot}$ .
- Three-phase fault current in Amperes at the 1000 V bus using Ohmic method,  $I_{F-1000V}$ .
- Verify the three-phase fault current calculation at the 1000 V bus using the p.u. method.



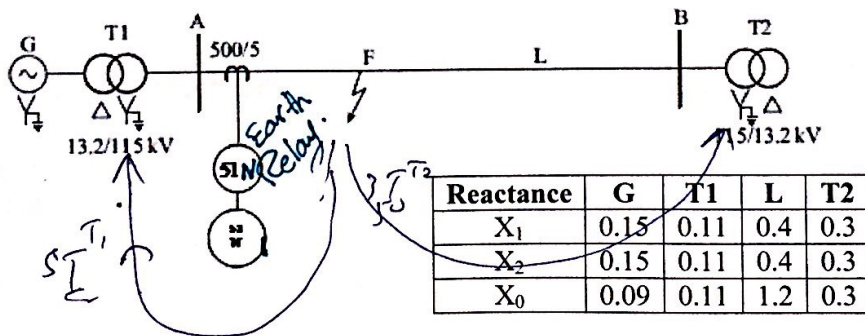**Question # 4:**

A solid line-to-ground fault on phase A is represented by the arrow at the point F near Bus A in the power system shown below. The per unit +Ve, -Ve and zero-sequence reactances of the Generator, Transformers and Transmission line is given in the Table.

- Draw the +Ve, -Ve and zero-sequence networks for the entire system.
- Find the LG fault current  $I_{LGF}$  at the fault point F in pu.
- Determine the current in Amperes that flow on both sides of the Dy1 transformer T1 and the Yd11 transformer T2. The bases at the Generator location are 13.2 kV and 100 MVA.
- Indicate which relay(s) operate on the occurrence of the fault.



\* Tutorial #1: Fault Calculations "part 2"

Q1  $Z_b = \frac{(13.8)^2}{100} = 1.9 \Omega \Rightarrow Z_{T(LV)} = (1.9)(0.53) = \underline{1.01 \Omega}$   
 $Z_{T(HV)} = 0.08 \times \frac{100}{15} = \underline{0.53}$


Max:  $X_{sc(HV)} = \frac{(138)^2}{250} = 76.2 \Omega \Rightarrow X_{sc(LV)} = \left(\frac{13.8}{138}\right)^2 \times X_{sc(HV)} = \underline{0.7 \Omega}$

for max fault current:  $1.01 \parallel 1.01 = \underline{0.505 \Omega}$

$I_{f(1)} = \frac{13.8 \times 10^3 / \sqrt{3}}{0.7 + 0.505} = 6612 \text{ A}$   $I_{f(3)} = \frac{13.8 \times 10^3 / \sqrt{3}}{0.7 + 0.505 + 0.7 + 1} = 2742.7 \text{ A}$   
 $I_{f(2)} = \frac{13.8 \times 10^3 / \sqrt{3}}{0.7 + 0.505 + 0.7} = 4182.4 \text{ A}$   $I_{f(4)} = \frac{13.8 \times 10^3 / \sqrt{3}}{0.7 + 0.505 + 0.7 + 1 + 2} = 1624.3 \text{ A}$   
 $I_{f(5)} = \frac{13.8 \times 10^3 / \sqrt{3}}{0.7 + 0.505 + 0.7 + 1 + 2 + 1} = 1349.3 \text{ A}$

Bus #	(1)	(2)	(3)	(4)	(5)
$I_f$ (A)	6612	4182.4	2742.7	1624.3	1349.3
$I_{max}$					

Q2

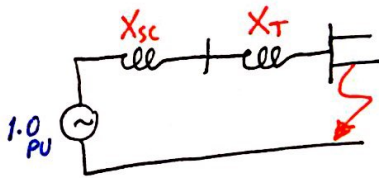

$MVA_{pu} = \frac{300 \text{ M}}{50 \text{ M}} = 6 \text{ pu}$   
 $X_{sc \text{ pu}} = \frac{1}{6} = 0.167 \text{ pu}$   
 $X_T = 0.08 \text{ pu}$

$I_f = \frac{1}{0.167 + 0.08} = 4.05 \text{ pu}$


$I_b(LV) = \frac{50 \times 10^6}{\sqrt{3} \times 2400} = 12028 \text{ A}$

$I_{f_{LV}} = 48713.4 \text{ A} \Rightarrow I_{f_{LL}} = 0.866 I_{f_{3-ph}}$

$I_{f_{LL}} = 42185.8 \text{ A}$

$I_{f_{HV}} = I_{f_{LV}} \times \frac{2400}{13.8 \times 10^3} \Rightarrow I_{f_{HV}} = 8471.9 \text{ A}$

$I_{f_{LL}} = 7336.7 \text{ A}$

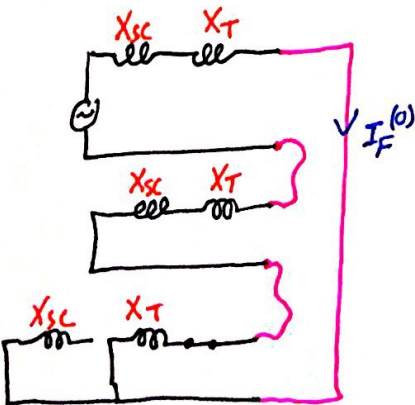

$I_{f_{LG}} = 3 I^{(0)} = \frac{3}{2 X_{sc} + 3 X_T} = 5.23 \text{ pu}$

$I_{LG_{LV}} = 62906.4 \text{ A}$

$I_{LG_{HV}} = 10940.3 \text{ A}$




... Continue.

Q3


a)  $MVA_b = 1.25 \text{ MVA}$   
 $MVA = \sqrt{3} V_{LL} I_{sc}$   
 $= \sqrt{3} (2.5 \text{ kV}) (11 \text{ kA})$   
 $= 47.6 \text{ MVA}$   
 $\Rightarrow MVA_{pu} = \frac{47.6}{1.25} = 38.1 \text{ pu}$

b)  $X_{sc} = \frac{1}{MVA_{pu}}$   
 $= \frac{1}{38.1}$   
 $\Rightarrow X_{sc} = 0.026 \text{ pu}$   
 $Z_{b(LV)} = \frac{(1000)^2}{1.25 \times 10^6} = 0.8 \Omega$   
 $\Rightarrow X_{sc} = 0.021 \Omega$

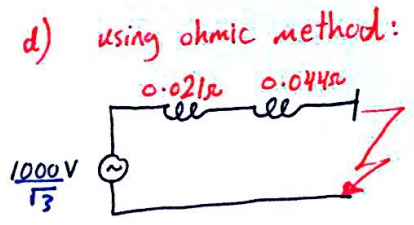c) in pu:  $X_{tot} = 0.026 + 0.055 = 0.081 \text{ pu}$   
 in ohm:  $X_{tot} = 0.021 + X_T$   $\rightarrow X_T = (0.055)(0.8) = 0.044 \Omega$   
 $= 0.021 + 0.044 = 0.065 \Omega$




$\Rightarrow |I_f| = \frac{1000/\sqrt{3}}{0.065} = 8882.3 \text{ A} \approx 8.9 \text{ kA}$

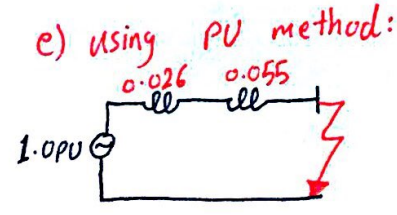

$\Rightarrow I_f = \frac{1}{0.081} = 12.35 \text{ pu}$   
 $I_{b(LV)} = \frac{1.25 \times 10^6}{\sqrt{3} \times 1000} = 721.7 \text{ A}$   
 $|I_f| = 721.7 \times 12.35 = 8913 \text{ A} \approx 8.9 \text{ kA}$

Q4

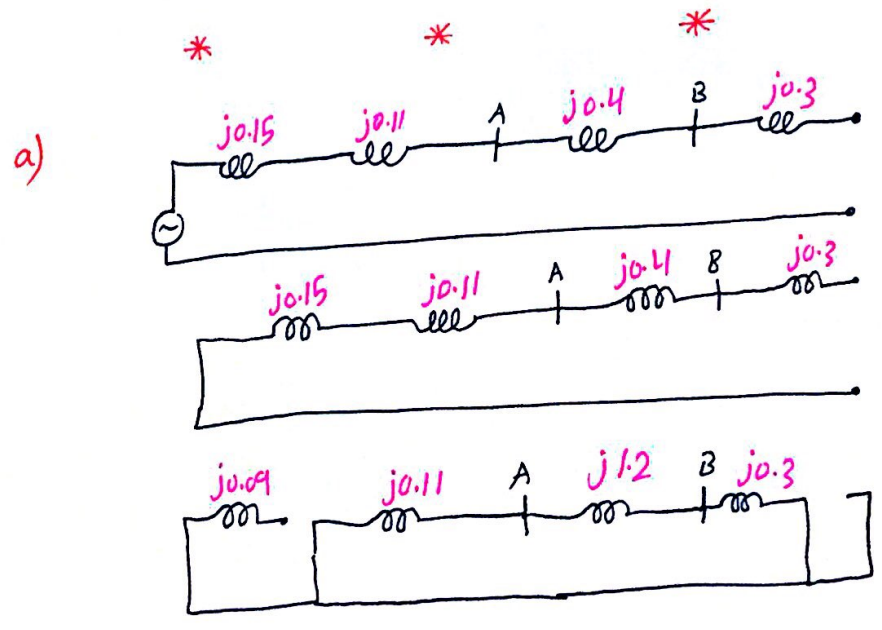


... Continue

b) for a LG fault @ point F:

$$Z^+ = j0.11 + j0.15 = j0.26$$

$$Z^- = j0.11 + j0.15 = j0.26$$

$$Z^0 = (j0.11) // (j1.5) = j0.102$$

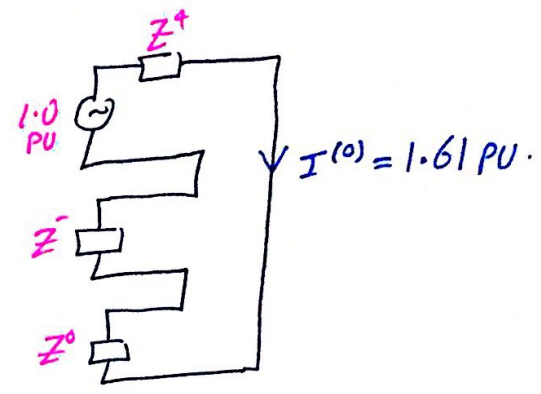

$$I_{LG} = 3 I^{(0)} = \frac{3}{Z^+ + Z^- + Z^0} = \underline{\underline{4.82 \text{ PU}}}$$

c) By using Current Division:

for T<sub>1</sub>:  $I^{(0)} = 1.61 \frac{1.5}{1.5 + 0.11} = \underline{\underline{1.5 \text{ PU}}}$

for T<sub>2</sub>:  $I^{(0)} = 1.61 - 1.5 = \underline{\underline{0.11 \text{ PU}}}$

$$I_b = \frac{100 \times 10^6}{\sqrt{3} \times 115 \times 10^3} = \underline{\underline{502 \text{ A}}}$$

⇒ for T<sub>1</sub>:

$$I_{LG} = 3 I^{(0)} = 4.5 \text{ PU}$$

$$I_{LG (HV)} = (4.5) \times (502)$$

$$\Rightarrow \underline{\underline{I_{LG (HV)} = 2259 \text{ A}}}$$

$$\Rightarrow I_{LG (LV)} = 2259 \times \frac{115}{13.2}$$

$$\Rightarrow \underline{\underline{I_{LG (LV)} = 19680.7 \text{ A}}}$$

⇒ for T<sub>2</sub>:

$$I_{LG} = 3 I^{(0)} = 0.33 \text{ PU}$$

$$I_{LG (HV)} = (0.33) \times (502)$$

$$\Rightarrow \underline{\underline{I_{LG (HV)} = 165.66 \text{ A}}}$$

$$\Rightarrow I_{LG (LV)} = 165.66 \times \frac{115}{13.2}$$

$$\Rightarrow \underline{\underline{I_{LG (LV)} = 1443.25 \text{ A}}}$$


\*

\*


\*

\* for Example 6 in slides:

• Two-phase fault: (B&C)

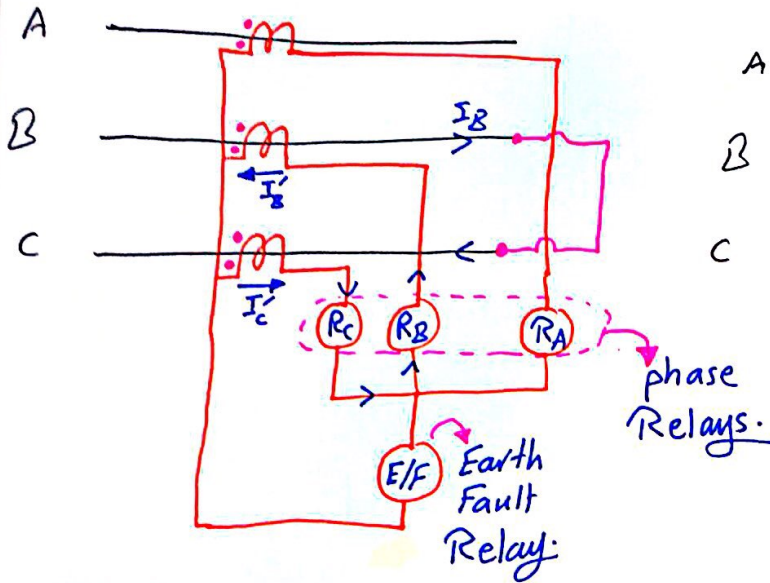

• Three-phase Fault:

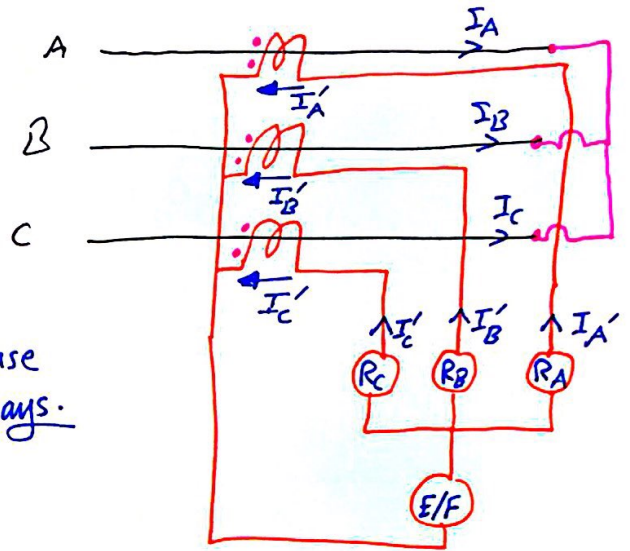

\* Dot Convention:

- if the current entering the Dot in the primary, then it is leaving the Dot in the secondary.
- if the current leaving the Dot in the primary, then it is entering the Dot in the secondary.

\* Phase Relays discover:  $\begin{cases} \rightarrow & L-L-L \text{ fault.} \\ \rightarrow & L-L \text{ fault.} \end{cases}$

\* Earth Fault Relay discover:  $\begin{cases} \rightarrow & L-G \text{ fault.} \\ \rightarrow & L-L-G \text{ fault.} \\ \rightarrow & \text{Unbalanced fault.} \end{cases}$

\* Criteria of Choosing CT's :

1) Voltage operate below the Kneel point value.

2) Current base on Max. load seen by the CT.

The conductor of one phase of a three-phase transmission line operating at 345 kV, 600 MVA, has a CT and a VT connected to it. The VT is connected between the line and ground as shown in Fig. 1. The CT ratio is 1200:5 and the VT ratio is 3000:1. Determine the CT secondary current and VT secondary voltage.

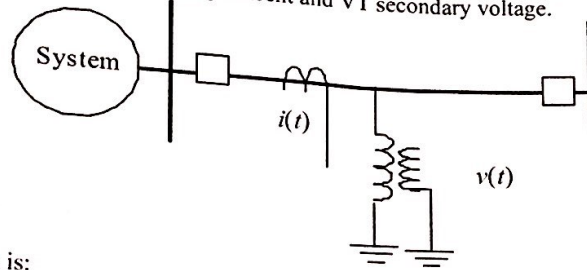


Fig. 1

The VT secondary voltage is:

$$V' = \frac{345/\sqrt{3} \times 10^3}{3000} = 66.4 \text{ V}$$

The current flowing through the line is:

$$I = \frac{600 \times 10^6}{\sqrt{3} \times 345 \times 10^3} = 1004.24 \text{ A}$$

Therefore the CT secondary current is:

$$I = \frac{1004.24 \times 5}{1200} = 4.2 \text{ A}$$

Question # 2:

Consider the single-phase CVT shown in Fig. 2. The open circuit voltage requirement of the CVT is 100 V, while the line voltage connected across terminal A is 100 kV. Find the values of C1 and C2 such that there is no phase displacement between the line voltage and the output of the CVT. The leakage inductance (L) of the transformer is 1 mH and the supply frequency is 50 Hz.

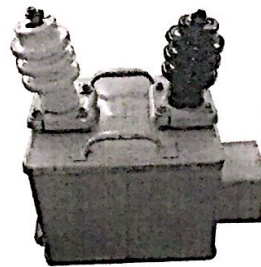
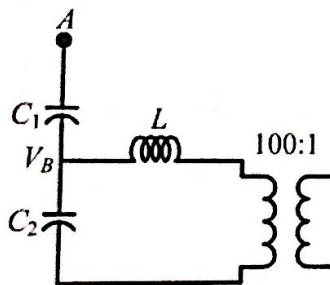


Fig. 2

Consider the circuit of Fig. 2. The open-circuit voltage across C2 is given by

$$V_B = \frac{V_A(1/j\omega C_2)}{1/j\omega C_1 + 1/j\omega C_2} = V_A \frac{C_1}{C_1 + C_2}$$

Now we want 100 V at the output of the VT, which has a turns ratio of 100:1. Therefore,

$$100 \times 100 = 100 \times 10^3 \frac{C_1}{C_1 + C_2} \Rightarrow C_1 + C_2 = 10C_1 \Rightarrow C_2 = 9C_1$$

Again from the phase shift requirement, we have

$$L = \frac{1}{\omega^2(C_1 + C_2)} \Rightarrow C_1 + C_2 = \frac{1}{\omega^2 L} \Rightarrow 10C_1 = \frac{10^3}{(2\pi \times 50)^2} \Rightarrow C_1 = 1013.2 \mu F$$

$$C_2 = 9C_1 = 9 \times 1013.2 \mu F \Rightarrow C_2 = 9118.9 \mu F$$

**Question # 3:**

The circuit has an A phase to ground fault on the line, with fault current magnitude of 16 kA at 0°. The circuit of Fig.1 has 1000:5 class C100 CTs. Given the following:  
 CT Winding Resistance  $R_C = 0.342 \Omega$   
 Burden resistance for phase relay  $R_{ph} = 0.50 \Omega$   
 Burden resistance for E/F relay  $R_E = 0.59 \Omega$   
 Lead Resistance (One lead)  $R_L = 0.224 \Omega$

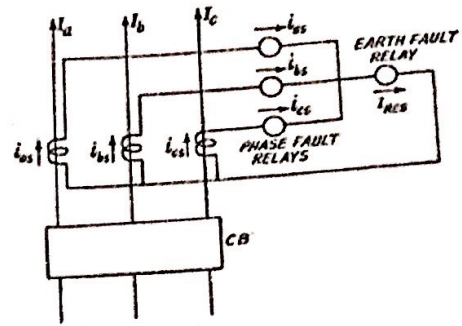


Fig. 1

Calculate,

- the current seen by the secondary of the CT,  $I_{as}$ .
- the total connected resistance seen by the phase CT,  $R_T$ .
- the CT Secondary Voltage for phase to ground fault,  $V_s$ .
- Does the CT get Saturated at the above LG fault current?

**Solution**

- Secondary Fault Current  
 $I_{as} = I_f / CTR = 16000 / (1000/5) = 16000 / 200 = 80 \text{ A}$ .
- Total connected resistance seen by the phase CT,  
 $R_T = R_C + R_{ph} + R_E + R_L$   
 $R_T = 0.342 + 0.50 + 0.59 + 0.448 = 1.88 \Omega$ .
- CT secondary voltage for ground fault:  
 $V_s = I_{as} R_T$   
 $V_s = 80 \times 1.88 = 150.4 \text{ V} \sim 150 \text{ V}$

A CT with a saturation voltage of 100 V would experience substantial saturation for this fault. This saturation would cause a large reduction in the current delivered

**Question #4:**

A distribution feeder has 600 / 5 C 100 CT with a knee point 100 Volt. A three phase fault of  $I_f = 10200 \text{ A}$  occurs at F as shown in Fig. Q3.

- Calculate the voltage developed across CT if the phase relay burden resistance  $Z_R = 0.10 \Omega$ , the lead resistance  $R_L = 0.50 \Omega$ , and the CT resistance  $R_S = 0.40 \Omega$ .
- Will this fault current lead to CT saturation?
- If not, at what fault level, the CT will saturate?

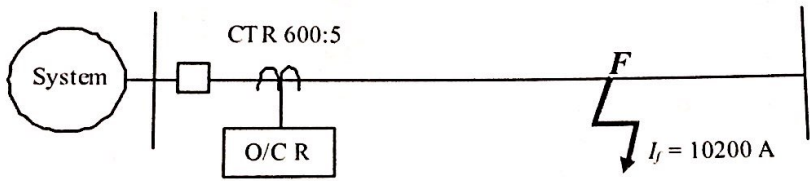


Fig. Q4

**Solution:**


Effective impedance seen by the CT

$$\begin{aligned}
 &= R_S + R_L + Z_R \\
 &= (0.40 + 0.5) + 0.10 \\
 &= 1.0 \\
 &= I_s \times 1 \\
 &= (10200 / 120) \times 1.0 = 85 \text{ V}
 \end{aligned}$$

Not Saturated.

Since, the knee point is 100 V the CT will saturate at 100 V corresponding to  $I_f = 12000 \text{ A}$ .

\* Example 7 in slides:

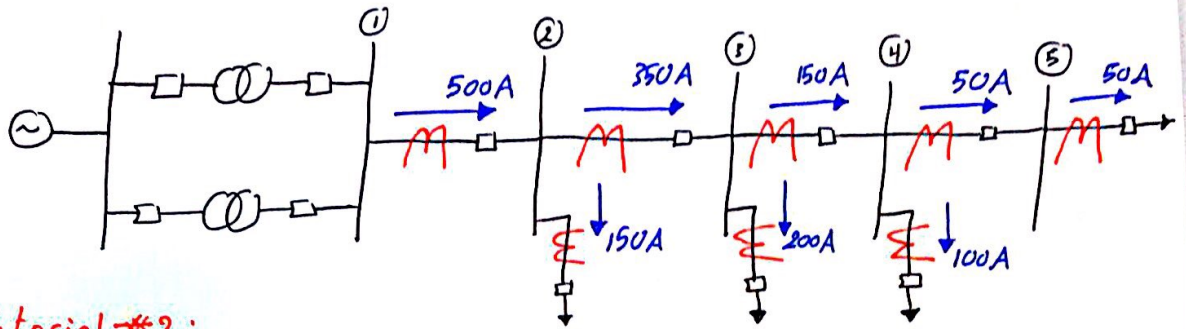

\* Tutorial #2:

Q1 Assume Y-Y-connected

$$CTR = \frac{1200}{5} = \frac{N_2}{1}$$



$$VTR = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{3000}{1}$$

$$I_L = \frac{600 \times 10^6}{\sqrt{3} \times 345 \times 10^3} = 1004.1 \text{ A}$$

$$I_{sec} = \frac{I_L}{CTR} = \frac{1004.1}{1200} = 4.2 \text{ A}$$

$$V_{sec} = \frac{345 \times 10^3}{3000} = \frac{345}{3} = 115 \text{ V}_{LL}$$

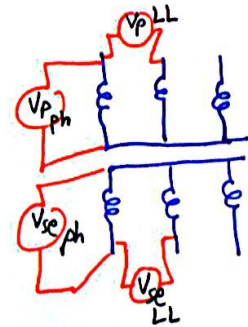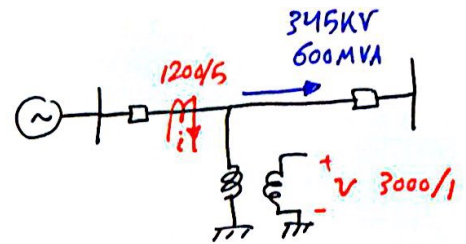
$$V_{sec_{ph}} = \frac{115}{\sqrt{3}} = 66.4 \text{ Volt}$$



we can deal with both LL & phase they will give same Ratio.

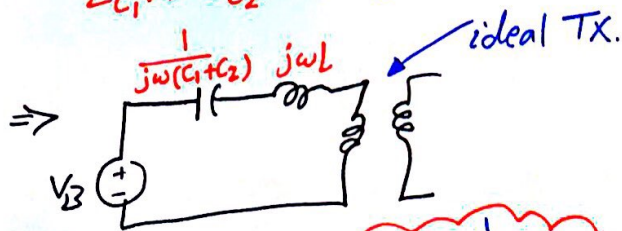Q2

$$Z_{C1} \gg Z_{C2} \Rightarrow C_2 \gg C_1$$



@ Resonance:


$$L = \frac{1}{\omega^2 [C_1 + C_2]} \dots \textcircled{1}$$

which will cancel the phase shift.

$$\Rightarrow V_B = V_A \frac{C_1}{C_1 + C_2} \dots \textcircled{2}$$

from equ. ①:
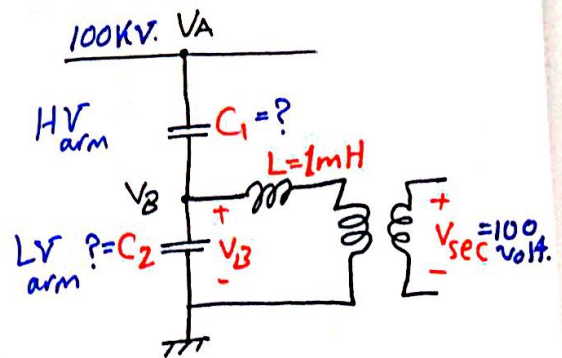
$$C_1 + C_2 = \frac{1}{\omega^2 L} = \frac{1}{(314)^2 \times 10^{-3}} = 10.132 \text{ mF} \dots \textcircled{3}$$



Continue.

⇒ from equ. (2):

$$V_B = \frac{C_1}{C_1 + C_2} V_A$$

$$10K = \lambda \times 100K$$

$$\Rightarrow \lambda = \frac{1}{10} = \frac{C_1}{C_1 + C_2} \Rightarrow C_2 = 9C_1 \dots (4)$$

14

Solving (3) & (4):

$$C_1 = 1013.2 \mu F$$

$$C_2 = 9118.8 \mu F$$

Q3

$$V_{sec} = I_f'' (R_{ph} + R_{E/F} + 2R_L + R_c)$$

$$I_{sec} = \frac{16000}{1000} \times 5 = \underline{80 A}$$

$R_c$ : Secondary Winding Resistance.  $3I_{a0}$

$R_{ph}$ : Relay A resistance. (0.5Ω)


$R_{E/F}$ : E/F relay resistance (0.59).

$$R_{Total} = R_c + 2R_L + R_{ph} + R_{E/F}$$


$$= 0.342 + 2 \times 0.224 + 0.5 + 0.59 = \underline{1.88 \Omega}$$

$$V_{sec} = 80 \times 1.88 \approx \underline{150 \text{ volt}}$$

Y-connected Tx.

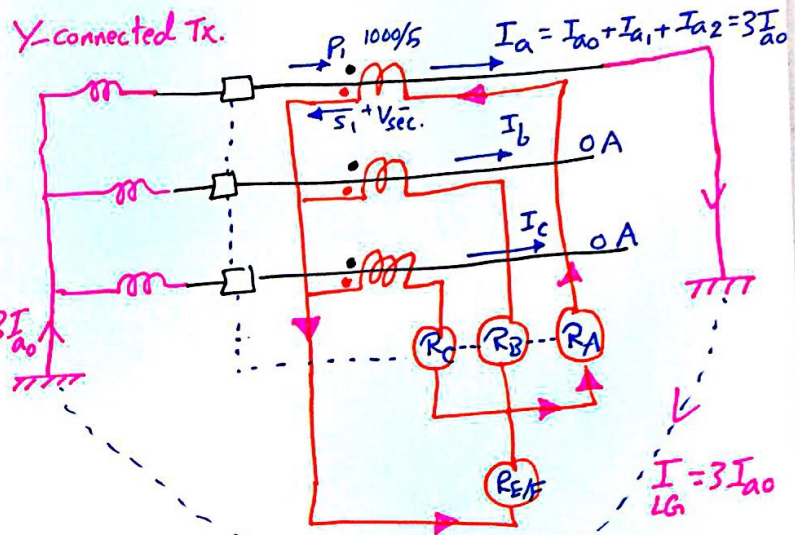

Q4

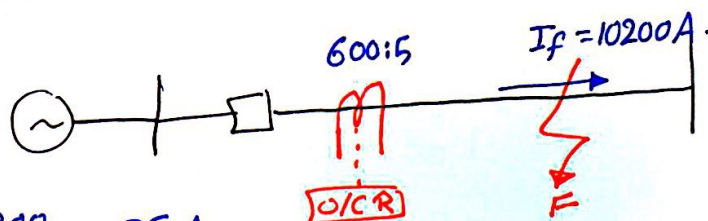

$$I_{sec} = \frac{I_f}{CTR} = \frac{10200}{\frac{600}{5}} = \underline{85 A}$$

$$R_T = R_L + R + R_s = 0.5 + 0.1 + 0.4 = \underline{1 \Omega}$$

$$V_s = (I) \times (R_T) = \underline{85 \text{ volt}}$$

**Question # 1:**

The current plug (tap) settings (CTS) of a GEC 5-A overcurrent relay can be varied from 1 A to 12 A and the TMS can be varied from 0.5 to 10 as shown in Fig. 1. If the input current to the overcurrent relay is 10 A, determine the relay operating time for the following current tap setting (CTS) and time dial setting (TDS):

- (a) CTS = 1.0 and TDS = 1/2;
- (b) CTS = 2.0 and TDS = 1.5;
- (c) CTS = 2.0 and TDS = 7;
- (d) CTS = 3.0 and TDS = 7; and
- (e) CTS = 12.0 and TDS = 1.

Use the overcurrent relay characteristics

$$t_p = TDS \times \left( \frac{A}{I_r^p - 1} + B \right)$$

$t_p$  is the pickup or operating time

$I_r$  is the ratio of  $|I|/|I_p|$

$A = 28.2$ ,  $B = 0.1217$  and  $p = 2.0$

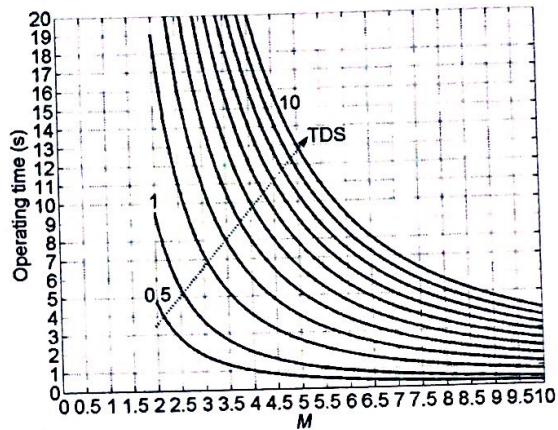


Fig. 1

**Solution:**

(a) CTS=1.0, then  $I_r=|I|/|I_p|=10$ . Therefore,

$$t_p = 0.5 \times \left( \frac{28.2}{10^2 - 1} + 0.1217 \right) = 0.2033 \text{ sec}$$

(b) CTS=2.0, then  $I_r=|I|/|I_p|=5$ . Therefore,

$$t_p = 1.5 \times \left( \frac{28.2}{5^2 - 1} + 0.1217 \right) = 1.945 \text{ sec}$$

(c) CTS=2.0, then  $I_r=|I|/|I_p|=5$ . Therefore,

$$t_p = 7 \times \left( \frac{28.2}{5^2 - 1} + 0.1217 \right) = 9.0769 \text{ sec}$$

(d) CTS=3.0, then  $I_r=|I|/|I_p|=3.33$ . Therefore,


$$t_p = 7 \times \left( \frac{28.2}{3.33^2 - 1} + 0.1217 \right) = 20.418 \text{ sec}$$

(e) CTS=12.0, then  $I_r=|I|/|I_p| < 1$ . Therefore, the relay does not operate.



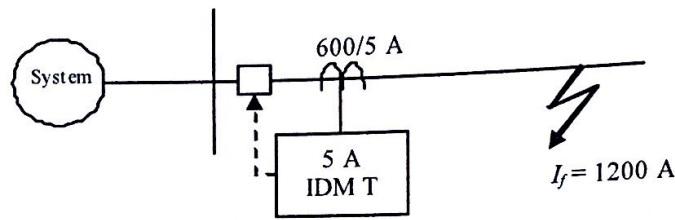**Question # 2:**

The calculated short-circuit current through a feeder is 1200 A. An overcurrent relay of rating 5 A is connected for the protection of the feeder through a 600/5 A CT as shown in Fig. 2.



PS = 50%, TMS = 0.8

Fig. 2

Calculate the operating time of the relay when it has a plug setting (PS) of 50% and time multiple setting (TMS) of 0.8. The characteristic of the relay is as follows:

<b>PSM</b>	1.3	2	4	6	10	20	
<b>Time (sec)</b>	30	10	6.5	3.5	3	2.2	

**Solution:**

$$I_{pickup} = PS \times I_{rated} = 0.5 \times 5 = 2.5 \text{ A}$$

$$I_{f-relay} = \frac{I_f}{CTR} = \frac{1200}{600/5} = 10 \text{ A}$$

$$PSM = \frac{I_{f-relay}}{I_{pickup}} = \frac{10}{2.5} = 4 \rightarrow \text{operating time at TMS} = 1 \text{ is } 6.5 \text{ s}$$

$$\text{Actual operating time } t_p = 6.5 \times TMS \rightarrow t_p = 6.5 \times 0.8 = 5.2 \text{ s}$$

**Question #3:**

Figure 3 shows a radial distribution system having identical IDMT overcurrent at A, B and C. For a time delay step ( $\Delta t$ ) of 0.5 s, calculate the time multiplier settings (TMS) at A and B.

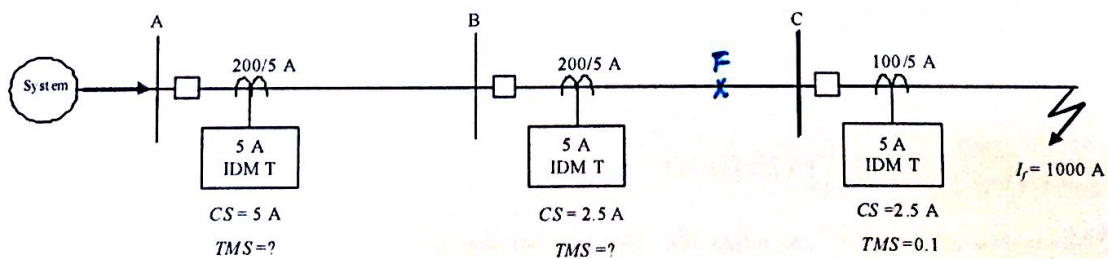


Fig. 3

The characteristic of the IDMT relay is as follows:

<b>PSM</b>	2	3	5	10	20
<b>Time (sec)</b>	10	6	4.5	3	2

**Solution:**

**For relay C,**

$$TMS_C = 0.1, I_{C-pickup} = 2.5 A \quad I_{C-relay} = \frac{I_f}{CTR_C} = \frac{1000}{100/5} = 50 A \quad PSM_C = \frac{I_{C-relay}}{I_{C-pickup}} = \frac{50}{2.5} = 20$$

→ operating time at TMS = 1 is 2 s

Actual operating time of relay C is  $t_p = 2 \times TMS \rightarrow t_p = 2 \times 0.1 = 0.2 s$

**For relay B,**

$$I_{B-pickup} = 2.5 A \quad I_{C-relay} = \frac{I_f}{CTR_C} = \frac{1000}{200/5} = 25 A \quad PSM_C = \frac{I_{C-relay}}{I_{C-pickup}} = \frac{25}{2.5} = 10$$

→ operating time at TMS = 1 is 3 s

Actual operating time of relay B is  $t_p = 0.2 + 0.5 = 0.7 s = 3 \times TMS \rightarrow TMS_B = \frac{0.7}{3} = 0.233$

**For relay A,**

$$I_{A-pickup} = 5 A \quad I_{A-relay} = \frac{I_f}{CTR_A} = \frac{1000}{200/5} = 25 A \quad PSM_A = \frac{I_{A-relay}}{I_{A-pickup}} = \frac{25}{5} = 5$$

→ operating time at TMS = 1 is 4.5 s

Actual operating time of relay A is  $t_p = 0.2 + 0.5 + 0.5 = 1.2 s = 4.5 \times TMS \rightarrow TMS_A = \frac{1.2}{4.5} = 0.266$

**Question #4:**

A 20 MVA Transformer which is used to operate at 30% overload feeds an 11 kV busbar through a circuit breaker (CB) as shown in Fig. 4. The transformer CB is equipped with a 1000/5 CT and the feeder CB with 400/5 CT and both CTs feed IDMT relays having the following characteristics

PSM	2	3	5	10	15	20
Time (sec)	10	6	4.1	3	2.5	2.2

The relay on the feeder CB has PS = 125% and TMS = 0.3. If a fault current of 5000 A flows from the transformer to the feeder, determine

- operating time of feeder relay.
- Suggest suitable PS and TMS of the transformer relay to ensure adequate discrimination of 0.5 s between the transformer relay and feeder relay.

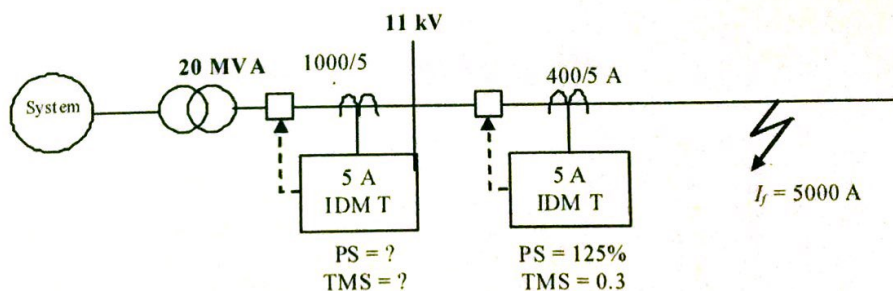


Fig. 4

**Solution:**

**For Feeder relay**

$$TMS_{Feeder} = 0.3, PS = 125\% \rightarrow I_{Feeder-pickup} = PS \times I_{rated} = 1.25 \times 5 = 6.25 A$$

$$I_{Feeder-relay} = \frac{I_f}{CTR_{Feeder}} = \frac{5000}{400/5} = 62.5 A \quad PSM_{Feeder} = \frac{I_{Feeder-relay}}{I_{Feeder-pickup}} = \frac{62.5}{6.25} = 10$$

→ operating time at TMS = 1 is 3 s

Actual operating time of the Feeder relay is  $t_p = 3 \times TMS \rightarrow t_p = 3 \times 0.3 = 0.9 s$

**For Transformer relay,  $I_{Transformer-pickup} = PS \times I_{rated}$**

$$\text{Transformer overload current, } I_T = 1.3 \times \frac{S_{rated}}{\sqrt{3}V_{LL}} = 1.3 \times \frac{20 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 1365 A$$

$$I_{Transformer-relay} = \frac{I_{Transformer-overload}}{CTR_{Transformer}} = \frac{1365}{1000/5} = 6.825 A$$

Since the transformer relay must not operate to overload current,  $PS_{Transformer} > \frac{I_{Transformer-relay}}{I_{relay-rated}}$

$PS_{Transformer} > \frac{6.825}{5} > 1.365$  or 136.5%, the PS are restricted to standard values in steps of 25%, so the

nearest value but higher than 136.5% is 150% →  $PS_{Transformer} = 150\%$

$$I_{Transformer-pickup} = PS_{Transformer} \times I_{rated} = 1.5 \times 5 = 7.5 A$$

$$PSM_{Transformer} = \frac{I_{f-Transformer-relay}}{I_{Transformer-pickup}} = \frac{5000/(1000/5)}{7.5} = \frac{25}{7.5} = 3.3$$

Operating time corresponding to  $PSM_{Transformer} = 3.3$  and TMS=1 from the PSM-time curve is

$t_p = 5.6 s$ , Actual operating time of transformer relay is  $t_p = 0.9 + 0.5 = 1.4 s = 3 \times TMS$

$$\rightarrow TMS_{Transformer} = \frac{1.4}{5.6} = 0.25$$




### \* Over Current Protection:

• every 50HZ cycle  $\Rightarrow$  20msec period.

#### • Note:

- $\Rightarrow$  If the current is high, then the contact will be opened faster.
- $\Rightarrow$  If the current is low, then the contact will take a longer period to be opened.

### \* Over current Types: "slide 7"

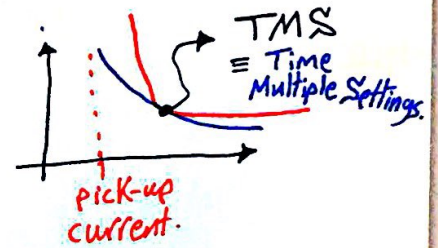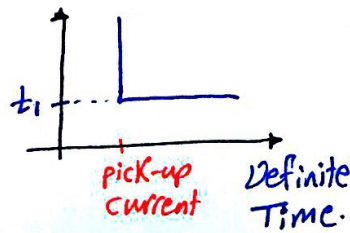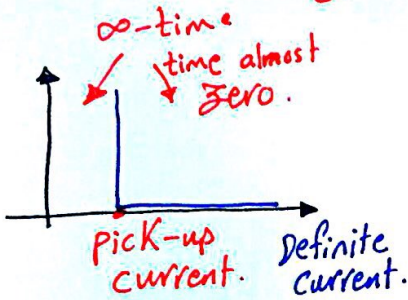

### \* IDMT Relay:

$\Rightarrow$  The movement of the disc needs force (Torque) depends on:  
 The induced current & the flux which is also produced by the current, so  $\tau \propto I^2$ . ( $\tau = K \phi I$ )

• PSM could be found from the ratio of primary currents or secondary currents

Ex in slides:  $PSM = \frac{1000}{100}$  or  $\frac{50}{5} = 10$

$$PSM = \frac{I_{relay}}{I_{pick\ up}} = \frac{I_f''}{I_p}$$

\*

\*

\*

# \* Tutorial #3 :

Q1 | Note that it could be given an equation for  $t_p$  or the characteristics table for finding  $t_p$ .

Here an equation is given.

$$t_p = TDS \times \left[ \frac{28.2}{I_r^2 - 1} + 0.1217 \right]$$

(a)  $CTS = 1$  &  $TDS = 1/2$ .

$$I_r = \frac{I_f''}{I_{pick-up}} = \frac{10}{1} = 10 \Rightarrow t_p = \underline{\underline{0.2033 \text{ sec.}}}$$


& so on for the other parts ...

(e)  $CTS = 12$  &  $TDS = 1$

since  $I_r = \frac{10}{12} < 1 \Rightarrow$  the relay does NOT operate.

\* \* \*

Q2 |  $PS = 50\% \Rightarrow \underline{\underline{2.5A}}$   
 $TMS = 0.8$

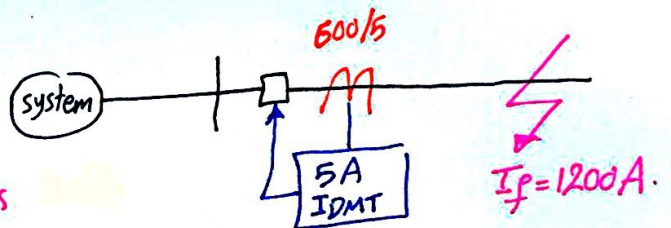

The equation that corresponds to this is given (@  $TMS = 1$ ):  $t_p = \frac{3}{\log(PSM)} \times TMS$ .

$$I_f'' = \frac{1200}{\frac{600}{5}} = 10A \Rightarrow \text{so } PSM = \frac{I_f''}{I_p} = \frac{10}{2.5} = 4$$

\* This Table is given @  $TMS = 1$ .


$$t_p \text{ @ } TMS=1 \text{ \& } PSM=4 = 6.5 \text{ sec.} \Rightarrow t_p \text{ @ } TMS=0.8 = 6.5 \times 0.8 = \underline{\underline{5.2 \text{ sec.}}}$$

\* By using the equation:

$$t_p = \frac{3}{\log(4)} \times 0.8 = \underline{\underline{4 \text{ sec.}}}$$

\* \* \*

Q3

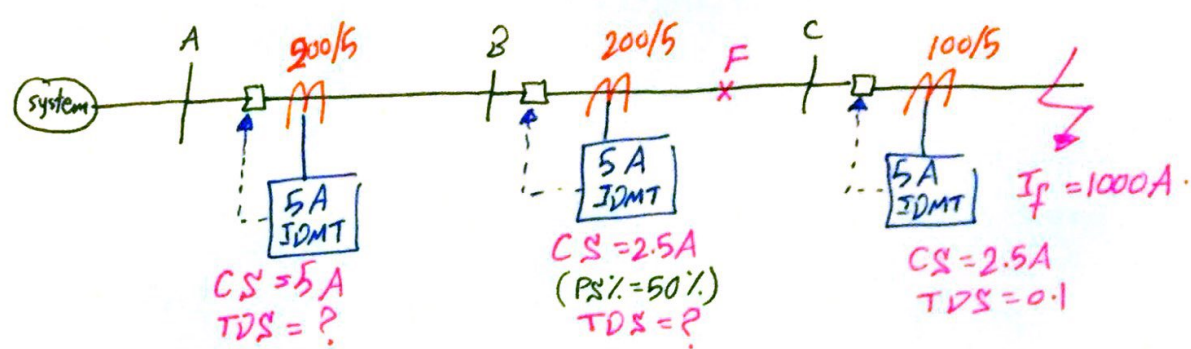

$\Delta T(CI) = 0.5s$   
 ↳ Coordination Interval.

$PSM = \frac{I_f}{I_P}$  → the current seen by the relay.  
 ↳ the current setting.

Need to find  $TDS_A$  &  $TDS_B$  ?

• for C:  $I_f'' = \frac{1000}{\frac{100}{5}} = 50A$ .

$t_{op} = [f(PSM)] \times TDS$

$PSM_C = \frac{I_f''}{I_{P_C}} = \frac{50}{2.5} = \frac{50}{2.5} = 20$

from the table:  $t_p = 2 \text{ sec}$  for  $PSM = 20$  @  $TDS = 1.0$

so for  $TDS = 0.1 \Rightarrow t_p = 2 \times 0.1 = \underline{0.2 \text{ sec}}$ . #

• for B:  $\Delta T$

$t_{p_B} = t_{p_C} + 0.5 = 0.7 \text{ sec}$ .

$PSM_B = \frac{I_f''}{I_{P_B}} = \frac{1000/200/5}{2.5} = 10$

from the table:

$t_p = 3 \text{ sec}$  for  $PSM = 10$   
 @  $TDS = 1.0$

$\Rightarrow t_{op} = f(PSM) \times TDS$

$\Rightarrow TDS_B = \frac{t_{op_B}}{f(PSM)} = \frac{0.7}{3} = \underline{0.233}$  #


• for A:

$t_{p_A} = t_{p_C} + 0.5 + 0.5 = 1.2 \text{ sec}$ .

$PSM_A = \frac{I_f''}{I_{P_A}} = \frac{25}{5} = 5$

from the table:  $t_p = 4.5 \text{ sec}$ .

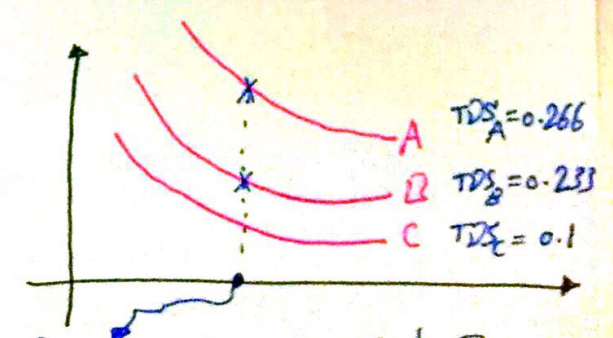$TDS_A = \frac{1.2}{4.5} = \underline{0.266}$  #




if a fault occurs @ point F  
 B & A will work.

\*

\*

\*

Q4

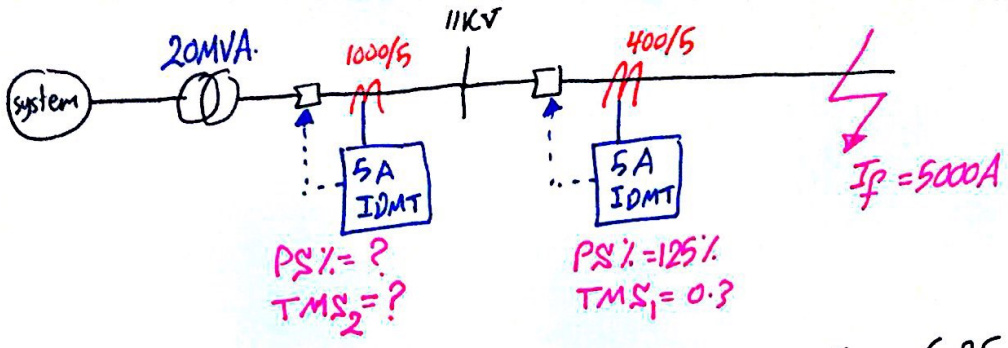

$$I_{f1}'' = \frac{5000}{400/5} = 62.5A, \quad PS\% = 125\% \Rightarrow I_{pickup_1} = 1.25 \times 5 = 6.25A.$$

$$PSM_1 = \frac{62.5}{6.25} = 10 \Rightarrow \text{from the table: } top = 3sec. \text{ for } TMS = 1.0$$

$$top = f(PSM_1) \times TMS_1 = 3 \times 0.3 = \underline{0.9sec}.$$

$$top_2 = 0.9 + 0.5 = \underline{1.4sec}.$$

$$I_{f2}'' = \frac{5000}{1000/5} = 25A. \Rightarrow PSM_2 = \frac{25}{I_{P2}}$$

• since it operate @ 30% overload, then:

$$I_{P2} = 1.3 \times I_{FL}$$

$$I_{FL} = \frac{S_{FL}}{\sqrt{3} V_L} = \frac{20 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 1049.7A.$$

$$\Rightarrow I_{P2} = 1.3 \times 1049.7 = \underline{1364.6A}.$$

@ secondary:

$$\Rightarrow \frac{1364.6}{\frac{1000}{5}} = 6.82A.$$

As a percentage:

$$\% PS_2 = \frac{6.82}{5} \times 100\% = 136.4\%$$

from the standards we choose 150% #

$$\text{so Now } I_{P2} = 1.5 \times 5 = \underline{7.5A} \text{ "in Secondary"}$$

$$\text{OR } I_{P2} = 1.5 \times 1000 = \underline{1500A} \text{ "in primary"}$$

• Now calculating  $PSM_2$ :  $PSM_2 = \frac{25}{7.5} = 3.3$

$\Rightarrow 3.3$  is between  $PSM = 3 \& 5$ , By interpolation find  $top$  @  $PSM = 3.3$

solving  $\Rightarrow top = 5.6sec$

$$top = f(PSM) \times TDS_2 \Rightarrow 1.4 = 5.6 \times TDS_2 \Rightarrow TDS_2 = \frac{1.4}{5.6} = \underline{0.25} \#$$



**Question # 1:**

Consider the 11-kV radial system shown in Fig 1-a. Assume that all loads have the same power factor. Determine relay settings to protect the system assuming relay type CO-7 (with characteristics shown in Fig 1-b) is used.

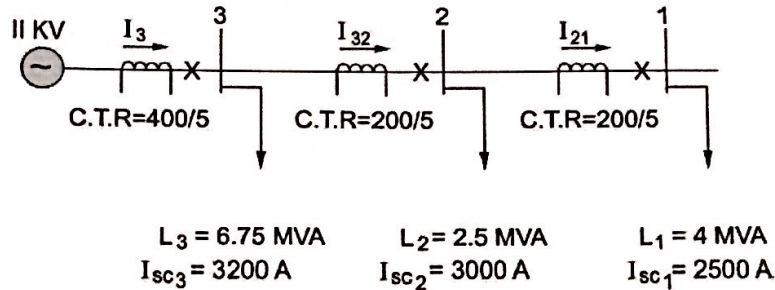


Fig.1-a: An Example Radial System

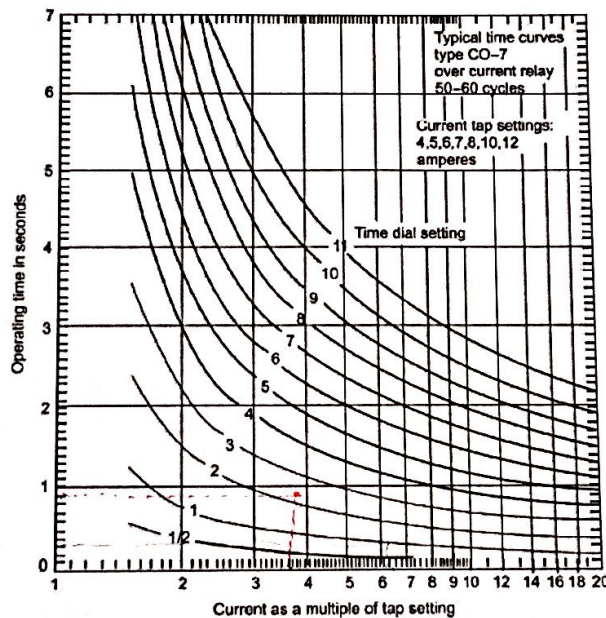


Fig. 1-b: CO-7 Time-Delay Overcurrent Relay Characteristics

**Solution:**

$$I_1 = \frac{4 \times 10^6}{\sqrt{3}(11 \times 10^3)} = 209.95 \text{ A} \quad I_2 = \frac{2.5 \times 10^6}{\sqrt{3}(11 \times 10^3)} = 131.22 \text{ A} \quad I_3 = \frac{6.75 \times 10^6}{\sqrt{3}(11 \times 10^3)} = 354.28 \text{ A}$$

The normal currents through the sections are calculated as

$$I_{21} = I_1 = 209.95 \text{ A} \quad I_{32} = I_{21} + I_2 = 341.16 \text{ A} \quad I_S = I_{32} + I_3 = 695.44 \text{ A}$$

With the current transformer ratios given, the normal relay currents are

$$i_{21} = \frac{209.92}{\frac{200}{5}} = 5.25 \text{ A} \quad i_{32} = \frac{341.16}{\frac{200}{5}} = 8.53 \text{ A} \quad i_S = \frac{695.44}{\frac{400}{5}} = 8.69 \text{ A}$$



We can now obtain the current tap settings (C.T.S.) or pickup current in such a manner that the relay does not trip under normal currents. For this type of relay, the current tap settings available are 4, 5, 6, 7, 8, 10, and 12 amperes.

- For position 1, the normal current in the relay is 5.25 A; we thus choose  $(C.T.S.)_1 = 6 A$ ,
- For position 2, the normal relay current is 8.53 A, and we choose  $(C.T.S.)_2 = 10 A$ ,
- Similarly for position 3,  $(C.T.S.)_3 = 10 A$ .

Observe that we have chosen the nearest setting higher than the normal current.

The next task is to select the intentional delay indicated by the time dial setting (T.D.S.). We utilize the short-circuit currents calculated to coordinate the relays. The current in the relay at 1 on a short circuit at 1 is

$$i_{sc1} = \frac{2500}{\left(\frac{200}{5}\right)} = 62.5 A$$

Expressed as a multiple of the pickup or C.T.S. value, we have

$$\frac{i_{sc1}}{(C.T.S.)_1} = \frac{62.5}{6} = 10.42$$

We choose the lowest T.D.S. for this relay for fastest action. Thus

$$(T.D.S.)_1 = \frac{1}{2}$$

By reference to the relay characteristic, we get the operating time for relay 1 for a fault at 1 as

$$T_{11} = 0.15 s$$

To set the relay at 2 responding to a fault at 1, we allow 0.1 second for breaker operation and an error margin of 0.3 second in addition to  $T_{11}$ . Thus,

$$T_{21} = T_{11} + 0.1 + 0.3 = 0.55 s$$

The short circuit for a fault at 1 as a multiple of the C.T.S. at 2 is

$$\frac{i_{sc1}}{(C.T.S.)_2} = \frac{62.5}{10} = 6.25$$

From the characteristics for 0.55-second operating time and 6.25 ratio, we get  $(T.D.S.)_2 \approx 2$ . The final steps involve setting the relay at 3. For a fault at bus 2, the short-circuit current is 3000 A, for which relay 2 responds in a time  $T_{22}$  obtained as follows:

$$\frac{i_{sc2}}{(C.T.S.)_2} = \frac{3000}{\left(\frac{200}{5}\right)_0} = 7.5$$

For the  $(T.D.S.)_2 = 2$ , we get from the relay's characteristic,  $T_{22} = 0.50 s$ .

Thus allowing the same margin for relay 3 to respond to a fault at 2, as for relay 2 responding to a fault at 1, we have

$$T_{32} = T_{22} + 0.1 + 0.3 = 0.90 s$$

The current in the relay expressed as a multiple of pickup is

$$\frac{i_{sc2}}{(C.T.S.)_3} = \frac{3000}{\left(\frac{400}{5}\right)_0} = 3.75$$

Thus for  $T_3 = 0.90$ , and the above ratio, we get from the relay's characteristic,  $(T.D.S.)_3 \approx 2.5$

We note here that our calculations did not account for load starting currents that can be as high as five to seven times rated values. In practice, this should be accounted for.

**Question # 2:**

**Relay coordination on radial feeders using Use Extremely Inverse Relay Characteristics**

For the radial power system shown in Fig. 2.1 the CTR of the CTs and the relay current settings at buses 1-5 are given in Table 2.1. The relay current setting (CS) are given in % and in primary Amperes. Also, the minimum and maximum faults at buses 1-5 are given in Table 2.2.

Design an overcurrent protection for the above radial feeder using Extremely Inverse Relay Characteristics:

$$t = \left( \frac{28.2}{M^2 - 1} + 0.1217 \right) \times TDS$$

i.e. find the TDS considering a coordination time interval set to 0.4 s, and a TDS of relay at bus 5 (R5) set to TDS5 = 1.0.

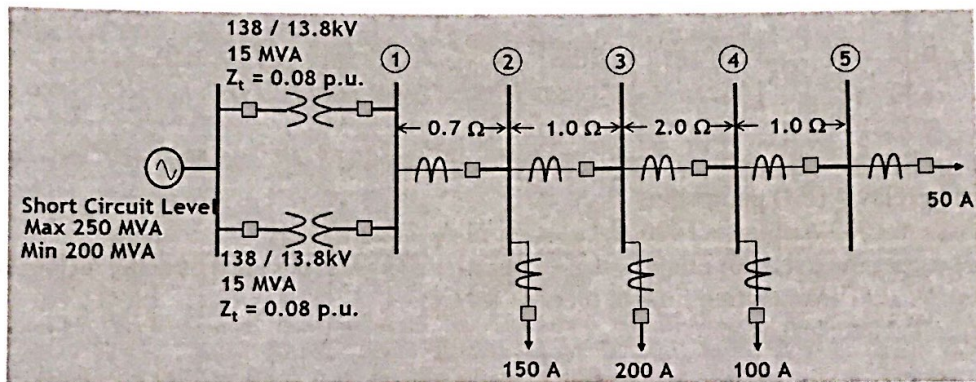


Figure 2.1: Radial system considered for relay overcurrent relay coordination study.

**Table 2.1: CT Ratio and Relay Current Settings**

Relay Location Bus	Maximum Load Current (A)	Selected CT Ratio	Relay Current Setting	
			Percent	Primary Current (A)
1	500	800/5	75 %	600
2	350	500/5	100 %	500
3	150	200/5	100 %	200
4	50	100/5	75 %	75
5	50	100/5	75 %	75

**Table 2.2: Fault Current Calculations**

Fault Location Bus	Minim Fault Current (A)	Maximum Fault Current (A)
1	4049	6274
2	2986	4045
3	2172	2683
4	1406	1603
5	1195	1335



Arreva P14x O/C protective devise.

**Solution:**

The principle of backup protection with O/C relays is that for any relay X backing up the next downstream relay Y, relay X must pick up:

- For one third of the minimum fault current seen by Y.
- For the maximum fault current seen by Y but not sooner than 0.4 s after Y should have picked up for that current.

Extremely Inverse overcurrent characteristic:  $t_p = \left( \frac{28.2}{M^2 - 1} + 0.1217 \right) \times TDS$

1. Choosing relay 5 (R5) parameters

$$I_{5fmax} = 1335 \text{ A}, I_{5fmin} = 1195 \text{ A}, I_{5pickup} = 75 \text{ A}, TDS_5 = 1.0$$

$$t_{p5} = \left( \frac{28.2}{\left( \frac{1335}{75} \right)^2 - 1} + 0.1217 \right) \times 1.0 = \left( \frac{28.2}{(17.8)^2 - 1} + 0.1217 \right) \times 1.0 = 0.21 \text{ s}$$

2. Choosing relay 4 (R4) parameters

$$I_{4fmax} = 1603 \text{ A}, I_{4fmin} = 1406 \text{ A}, I_{4pickup} = 75 \text{ A}, TDS_4 = ?$$

The operating time of relay 5 (R5) for  $I_{5fmax} = 1335 \text{ A}$  is 0.21 s. The relay 4 (R4) will pickup for  $I_{5fmax}$ . The operating time of relay 4 (R4) is:

$$t_{p4} = 0.21 + 0.4 = 0.61 \text{ s.}$$

$$t_{p4} = \left( \frac{28.2}{\left( \frac{1335}{75} \right)^2 - 1} + 0.1217 \right) \times TDS_4 \Rightarrow 0.61 = \left( \frac{28.2}{(17.8)^2 - 1} + 0.1217 \right) \times TDS_4$$

$$0.61 = 0.21 \times TDS_4 \Rightarrow TDS_4 = \frac{0.61}{0.21} = 2.9 \Rightarrow TDS_4 = 3$$

The actual operating time of relay 4 (R4) for  $I_{5fmax}$  and  $TDS_4 = 3.0$  is:

$$t_{p4} = \left( \frac{28.2}{(17.8)^2 - 1} + 0.1217 \right) \times 3 = 0.63 \text{ s}$$

The operating time of relay 4 (R4) for  $I_{4fmax} = 1603 \text{ A}$  is:

$$t_{p4} = \left( \frac{28.2}{\left( \frac{1603}{75} \right)^2 - 1} + 0.1217 \right) \times TDS_4 = \left( \frac{28.2}{(21.37)^2 - 1} + 0.1217 \right) \times 3 = 0.55 \text{ s}$$

The operating time of relay 4 (R4) for  $I_{4fmin} = 1406 \text{ A}$  is:

$$t_{p4} = \left( \frac{28.2}{\left( \frac{1406}{75} \right)^2 - 1} + 0.1217 \right) \times TDS_4 = \left( \frac{28.2}{(21.37)^2 - 1} + 0.1217 \right) \times 3 = 0.20 \times 3 = 0.60 \text{ s}$$

### 3. Choosing relay 3 (R3) parameters

$$I_{3fmax} = 2683 \text{ A}, I_{3fmin} = 2172 \text{ A}, I_{3pickup} = 200 \text{ A}, TDS_3 = ?$$

The operating time of relay 4 (R4) for  $I_{4fmax} = 1603 \text{ A}$  is 0.55 s. The relay 3 (R3) will pickup for  $I_{4fmax}$ . The operating time of relay 4 (R4) is:

$$t_{p3} = 0.55 + 0.4 = 0.95 \text{ s.}$$

$$t_{p3} = \left( \frac{28.2}{\left( \frac{1603}{200} \right)^2 - 1} + 0.1217 \right) \times TDS_3 \Rightarrow 0.95 = \left( \frac{28.2}{(8.015)^2 - 1} + 0.1217 \right) \times TDS_3$$

$$0.95 = 0.568 \times TDS_3 \Rightarrow TDS_3 = \frac{0.95}{0.568} = 1.67 \Rightarrow TDS_3 = 1.7$$

The actual operating time of relay 3 (R3) for  $I_{4fmax}$  and  $TDS_3 = 1.7$  is:

$$t_{p3} = \left( \frac{28.2}{(8.015)^2 - 1} + 0.1217 \right) \times 1.7 = 0.568 \times 1.70 = 0.965 \text{ s}$$

The operating time of relay 3 (R3) for  $I_{3fmax} = 2683 \text{ A}$  is:

$$t_{p3} = \left( \frac{28.2}{\left( \frac{2683}{200} \right)^2 - 1} + 0.1217 \right) \times TDS_3 = \left( \frac{28.2}{(13.415)^2 - 1} + 0.1217 \right) \times 1.7 = 0.48 \text{ s}$$

The operating time of relay 3 (R3) for  $I_{3fmin} = 2172 \text{ A}$  is:

$$t_{p3} = \left( \frac{28.2}{\left( \frac{2172}{200} \right)^2 - 1} + 0.1217 \right) \times TDS_3 = \left( \frac{28.2}{(21.37)^2 - 1} + 0.1217 \right) \times 1.7 = 0.363 \times 1.7 = 0.62 \text{ s}$$

### 4. Choosing relay 2 (R2) parameters

$$I_{2fmax} = 4045 \text{ A}, I_{2fmin} = 2986 \text{ A}, I_{2pickup} = 500 \text{ A}, TDS_2 = ?$$

The operating time of relay 2 (R2) for  $I_{3fmax} = 2683 \text{ A}$  is 0.48 s. The relay 2 (R2) will pickup for  $I_{3fmax}$ . The operating time of relay 2 (R2) is:

$$t_{p2} = 0.48 + 0.4 = 0.88 \text{ s.}$$

$$t_{p2} = \left( \frac{28.2}{\left( \frac{2683}{500} \right)^2 - 1} + 0.1217 \right) \times TDS_2 \Rightarrow 0.88 = \left( \frac{28.2}{(5.366)^2 - 1} + 0.1217 \right) \times TDS_2$$

$$0.88 = 1.136 \times TDS_2 \Rightarrow TDS_2 = \frac{0.88}{1.136} = 0.77 \Rightarrow TDS_2 = 0.8$$

The actual operating time of relay 2 (R2) for  $I_{3fmax}$  and  $TDS_2 = 0.8$  is:

$$t_{p2} = \left( \frac{28.2}{(5.366)^2 - 1} + 0.1217 \right) \times 0.8 = 1.136 \times 0.8 = 0.90 \text{ s}$$

The operating time of relay 2 (R2) for  $I_{2fmax} = 4045A$  is:

$$t_{p2} = \left( \frac{28.2}{\left( \frac{4045}{500} \right)^2 - 1} + 0.1217 \right) \times TDS_2 = \left( \frac{28.2}{(8.09)^2 - 1} + 0.1217 \right) \times 0.9 = 0.50s$$

The operating time of relay 2 (R2) for  $I_{4fmin} = 2986A$  is:

$$t_{p2} = \left( \frac{28.2}{\left( \frac{2986}{500} \right)^2 - 1} + 0.1217 \right) \times TDS_2 = \left( \frac{28.2}{(5.972)^2 - 1} + 0.1217 \right) \times 0.9 = 0.935 \times 0.9 = 0.84s$$

#### 5. Choosing relay 1 (R1) parameters

$I_{1fmax} = 6274 A$ ,  $I_{1fmin} = 4049 A$ ,  $I_{1pickup} = 600 A$ ,  $TDS_1 = ?$

The operating time of relay 2 (R2) for  $I_{2fmax} = 4045A$  is 0.5 s. The relay 1 (R1) will pickup for  $I_{2fmax}$ . The operating time of relay 1 (R1) is:

$$t_{p1} = 0.5 + 0.4 = 0.9 s.$$

$$t_{p1} = \left( \frac{28.2}{\left( \frac{4045}{600} \right)^2 - 1} + 0.1217 \right) \times TDS_1 \Rightarrow 0.9 = \left( \frac{28.2}{(6.74)^2 - 1} + 0.1217 \right) \times TDS_1$$

$$0.9 = 0.756 \times TDS_1 \Rightarrow TDS_1 = \frac{0.9}{0.756} = 1.19 \Rightarrow TDS_1 = 1.2$$

The actual operating time of relay 1 (R1) for  $I_{2fmax}$  and  $TDS_1 = 1.2$  is:

$$t_{p1} = \left( \frac{28.2}{(6.74)^2 - 1} + 0.1217 \right) \times 1.2 = 0.756 \times 1.2 = 0.908s$$

The operating time of relay 2 (R2) for  $I_{1fmax} = 6274A$  is:

$$t_{p1} = \left( \frac{28.2}{\left( \frac{6274}{600} \right)^2 - 1} + 0.1217 \right) \times TDS_1 = \left( \frac{28.2}{(10.46)^2 - 1} + 0.1217 \right) \times 1.2 = 0.46s$$

The operating time of relay 1 (R1) for  $I_{1fmin} = 4049A$  is:

$$t_{p1} = \left( \frac{28.2}{\left( \frac{4049}{600} \right)^2 - 1} + 0.1217 \right) \times TDS_1 = \left( \frac{28.2}{(6.748)^2 - 1} + 0.1217 \right) \times 1.2 = 0.755 \times 1.2 = 0.905s$$

**Table 2.3: CT Ratio and Relay CS and TD Settings**

Relay Location Bus	Selected CT Ratio	Relay Current Setting			Time Dial Setting
		Percent	Primary Current (A)	Secondary Current (A)	TDS
1	800/5	75 %	600	3.75	1.2
2	500/5	100 %	500	5	0.8
3	200/5	100 %	200	5	1.7
4	100/5	75 %	75	3.75	3
5	100/5	75 %	75	3.75	1


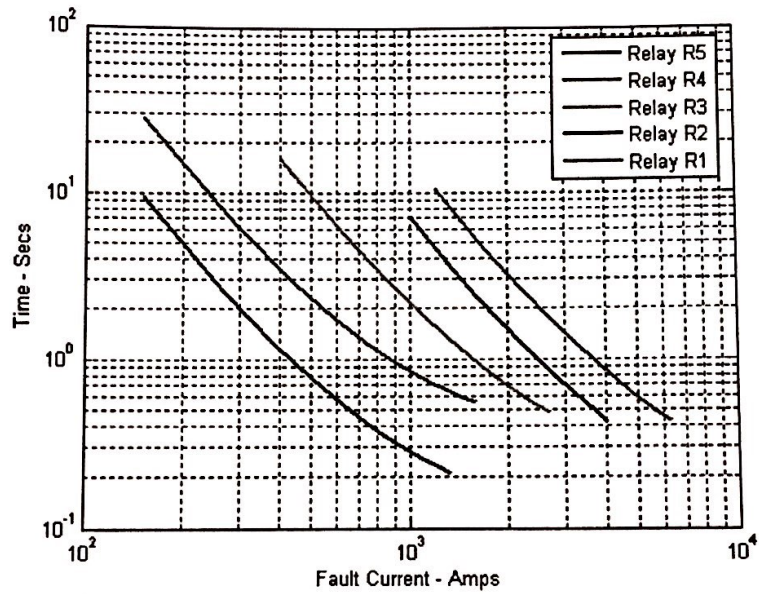
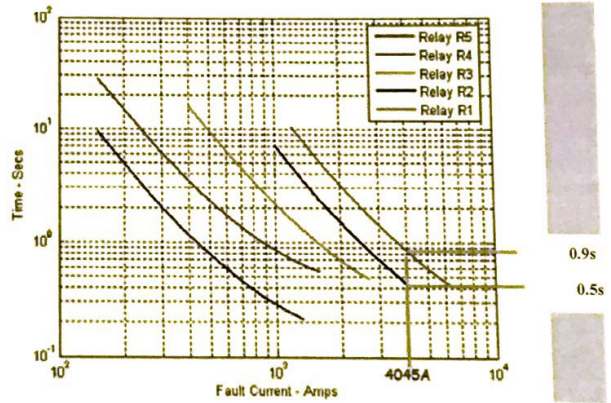
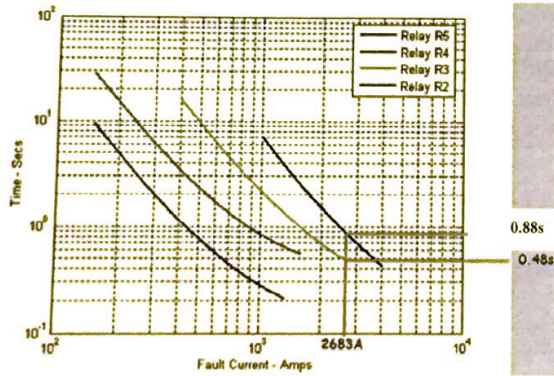
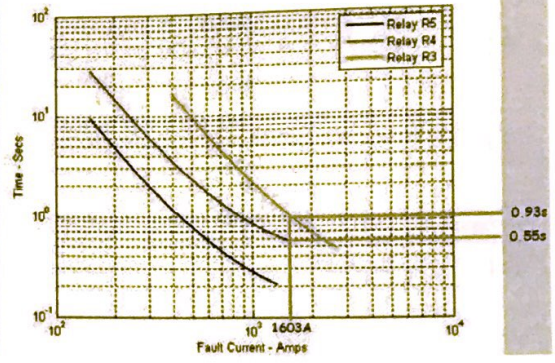
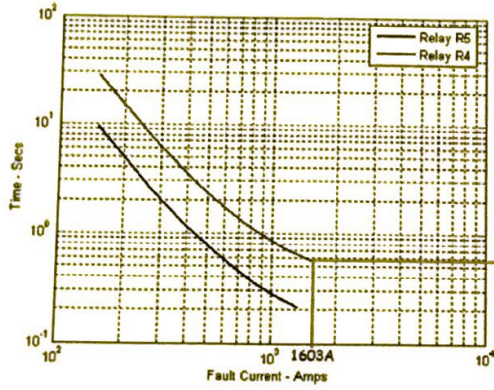
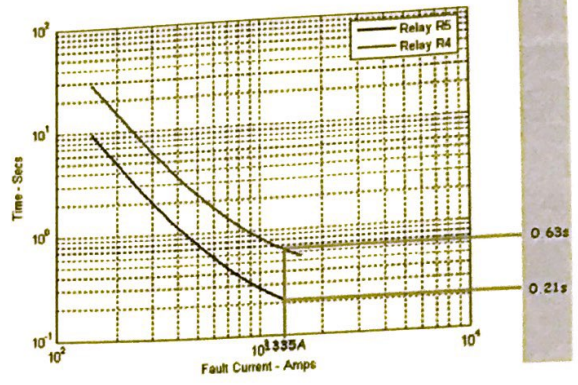


Fig. 2.2: overcurrent relay operating characteristic of R1-R5

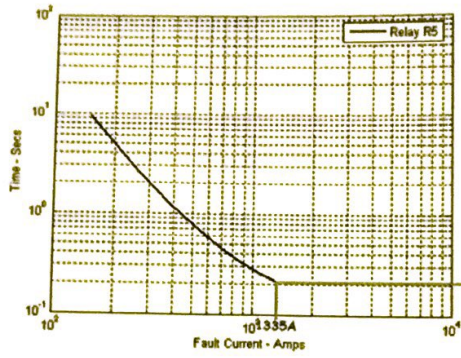

**Question # 3:**

Figure 3 shows a network that is protected by Normal Inverse Overcurrent IDMT relays whose  $t-I$  relay characteristic and  $PS\%$  are given by:

$$t = \frac{3}{\log_{10}(PSM)} \times TSM = \frac{3}{\log_{10}\left(\frac{I_f}{I_{pickup}}\right)} \times TSM$$

$PS\%$ : 50%, 75%, 100%, 125%, 150%, 175% and 200%.

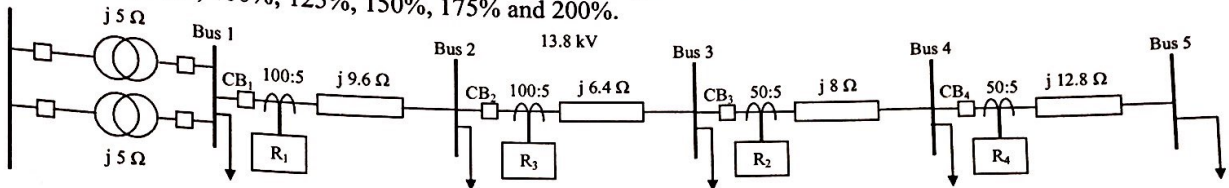


Fig. 3.

The minimum and maximum fault currents are given in Table 3-a.

**Table 3-a: Minimum and Maximum Fault Currents**

Bus No.	1	2	3	4	5
Minimum Fault Current (A), $I_{fmin}$	1380	472.6	328.6	237.9	165.1
Maximum Fault Current (A), $I_{fmax}$	3187	658	431	301	203

- Select the plug setting multiplier (PSM) and time dial settings (TMS) for the relays  $R_4$ ,  $R_3$ ,  $R_2$ , and  $R_1$  of the above system and fill the results in Table Q3-b, by evaluating the minimum CT pickup current ( $I_{pickup}$ ), the plug setting multiplier (PSM), plug setting ( $PS\%$ ) and time setting multiplier ( $TMS$ ). Set the  $TMS$  of  $R_4$  at its minimum  $TMS=0.5$ . Use a grading margin (coordination time) of **0.3 seconds**.
- Sketch the o/c characteristics of the four relays on a  $t-I$  characteristic.

**Table Q3-b: PS and TSM of O/C Relays**

Parameter	$R_1$	$R_2$	$R_3$	$R_4$
CT ratio	100:5	100:5	50:5	50:5
$PS\%$				
$TMS$				0.5

**Solution:**

The principle of backup protection with O/C relays is that for any relay X backing up the next downstream relay Y, relay X must pick up:

- For one third of the minimum fault current seen by Y.
- For the maximum fault current seen by Y but not sooner than 0.4 s after Y should have picked up for that current.

**Setting for Relay  $R_4$ :** This relay must operate for a current above 165.1 A (the minimum fault current at Bus-5). However for reliability, we must set this relay such that it picks up a current that is one third of the minimum, i.e.,

$$I'_{pickup4} = \frac{I_{fmin}}{3} = \frac{165.1}{3} = 55.03 \text{ A}$$



For a CT ratio of 50:5, the pickup current at the secondary of the CT will be

$$I_{pickup4} = \frac{I'_{pickup4}}{CTR_4} = \frac{55.03}{50/5} \times 5 = 5.5 A \Rightarrow PS\% = \frac{5.5}{5} \times 100 = 110\% \Rightarrow \text{Select } PS\%_4 = 125\%.$$

$\therefore$  Pick up Current (Effective Current) = Rated CT Primary Current  $\times$  PS

$$I'_{pickup} = 50 \times 1.25 = 62.5 A \text{ (Secondary current) or } I_{pickup} = 5 \times 1.25 = 6.25 A \text{ (Secondary current)}$$

This means if the CT primary current exceeds 62.5 A (6.25 A secondary current), relay will start operating after some time delay.

Since the relay  $R_4$  is located at the end of the network, i.e. does not coordinate with downstream relays. The TMS is restricted to a minimum of  $\frac{1}{2}$  for electro-mechanical relays  $\Rightarrow TMS_4 = 0.5$ .

**Setting for Relay  $R_3$ :** This relay must provide backup for  $R_4$ . Therefore it must pick up the minimum current seen by relay  $R_4$ . We therefore choose the same CT ratio  $CTR_4 = 50:5$  and pick up current  $I_{pickup3} = 6.25 A$ . To determine the TMS<sub>3</sub>, we must provide a discrimination time of 0.3 s. This time is provided such that  $R_3$  operates 0.3 s after the highest (not lowest) fault current seen by  $R_4$ . Therefore,  $R_3$  operates in no less than 0.3 s after every possible fault seen by  $R_4$ .

For a maximum fault immediately after Bus 4, it will see a fault current that is equal to the fault current seen by Bus 4. Therefore the highest fault current seen by  $R_4$  is 301 A (see Table 1). The current seen by both secondary of CTS of relay  $R_3$  and  $R_4$  for this fault will be

$$I_{f \max(\text{sec})4} = \frac{I'_{f \max 4}}{CTR_4} = \frac{301}{50/5} = 30.1 A$$

$$\text{Hence, } PSM_4 = \frac{I_{f \max 4}}{I_{pickup4}} = \frac{30.1}{6.25} = 4.82. \text{ The tripping time with } TMS_4 = 0.5 \text{ is}$$

$$t_4 = \frac{3.0}{\log(PSM_4)} \times TMS_4 = \frac{3.0}{\log(4.82)} \times 0.5 = 2.2 s, \text{ therefore for any failure of } R_4, \text{ relay } R_3 \text{ must operate at } 2.2 + 0.3 = 2.5 s.$$

Since relay  $R_3$  also has  $PSM_3 = 1.25$  (6.25 A), we can calculate the TMS<sub>3</sub> from

$$t_3 = \frac{3.0}{\log(PSM_3)} \times TMS_3 = \frac{3.0}{\log(4.82)} \times TMS_3 = 4.39 \times TMS_3 = 2.5 s$$

$$\Rightarrow TMS_3 = \frac{2.5}{4.39} = 0.569 \Rightarrow \text{Let } TMS_3 = 0.6$$

$\Rightarrow TMS_3 = 0.6$ . This gives an operating time of

$$t_3 = \frac{3.0}{\log(PSM_3)} \times TMS_3 = \frac{3.0}{\log(4.82)} \times 0.6 = 2.64 s. \text{ This maintains a minimum discrimination time of } 0.3 s.$$

**Setting for Relay  $R_2$ :** This relay must provide a backup for relay  $R_3$ . The smallest fault current seen by  $R_2$  to provide a backup for  $R_3$  is 237.9 A (see Table 1). For reliable operation, we choose one-third of this current, i.e., 79.3 A. For a  $CTR_2 = 100:5$ .

$$I_{pickup(\text{sec})2} = \frac{I_{f \min 3}/3}{CTR_2} = \frac{237.9/3}{100/5} = \frac{79.3}{100/5} = 3.97 A \Rightarrow PS\% = \frac{3.97}{5} \times 100 = 79.3\%$$

$\Rightarrow$  Select  $PS\%_2 = 100\%$ . We now have to determine TMS<sub>2</sub> of  $R_2$  from the maximum fault current seen by  $R_3$ .

The maximum current seen by  $R_3$  is 431 A. Then, at  $R_3$ , for a CT ratio of  $CTR_3=50:5$  and a  $PS_3=6.25$  A, we get a  $PSM_3$  of

$$PSM_3 = \frac{\left(\frac{I_{f \max 3}}{CTR_3}\right)}{I_{pickup3}} = \frac{\left(\frac{431}{50/5}\right)}{6.25} = 6.9. \text{ For the above } PSM_3=6.9 \text{ and a } TMS_3=0.6, \text{ the operating time of relay } R_3 \text{ is}$$

$$t_3 = \frac{3.0}{\log(PSM_3)} \times TMS_3 = \frac{3.0}{\log(6.9)} \times 0.6 = 2.15 \text{ s}$$

Thus, relay  $R_2$  should add discrimination time of 0.3 s., i.e., the operating time should be  $2.15 + 0.3 = 2.45$  s.

Now relay  $R_2$  is a backup for relay  $R_3$  and therefore, it will see the same fault current of 431 A.

$$\text{Then, } PSM_2 \text{ for this fault is } PSM_2 = \frac{\left(\frac{I_{f \max 3}}{CTR_2}\right)}{I_{pickup2}} = \frac{\frac{431}{100/5}}{5} = 4.31$$

For this value of  $PSM_2$ , we get a  $TMS_2$  from

$$t_2 = \frac{3.0}{\log(PSM_2)} \times TMS_2 = \frac{3.0}{\log(4.31)} \times TMS_2 = 4.73 \times TMS_2 = 2.45 \text{ s}$$

$$\Rightarrow TMS_2 = \frac{2.45}{4.73} = 0.518 \Rightarrow \text{Let } TMS_2 = 0.6$$

$$\text{This gives an operating time of } t_2 = \frac{3.0}{\log(PSM_2)} \times TMS_2 = \frac{3.0}{\log(4.31)} \times 0.6 = 2.84 \text{ s}$$

**Setting for Relay  $R_1$ :** This relay must provide a backup for relay  $R_2$ . The smallest fault current seen by  $R_2$  to provide a backup for  $R_3$  is 328.6 A. For reliable operation, we choose one-third of this current, i.e., 109.5 A. A CT ratio  $CTR_1=100:5$  is suitable.

For a  $CTR_1=100:5$ .

$$I_{pickup(sec)1} = \frac{I_{f \min 3}/3}{CTR_1} = \frac{328.6/3}{100/5} = \frac{109.5}{100/5} = 5.48 \text{ A} \Rightarrow PS\% = \frac{5.48}{5} \times 100 = 109.5\%$$

$\Rightarrow$  Select  $PS\%_1=125\%$  ( $PS_1=5 \times 1.25=6.25$  A).

We now have to determine  $TMS_1$  of  $R_1$  from the maximum fault current seen by  $R_2$ . Thus we choose the same CT ratio and  $PS\%$  for this relay as well. The maximum fault current seen by  $R_2$  is 658 A. Then, at  $R_2$ , for a CT ratio of  $CTR_2=100/5$  and a  $PS_2$  of ( $5 \times 100=5.00$  A), we get

$$PSM_2 = \frac{\left(\frac{I_{f \max 2}}{CTR_2}\right)}{I_{pickup2}} = \frac{\frac{658}{100/5}}{5} = 6.58. \text{ For } PSM_2=6.58 \text{ and } TMS_2=0.6, \text{ the operating time of relay } R_2 \text{ is}$$

$$t_2 = \frac{3.0}{\log(PSM_2)} \times TMS_2 = \frac{3.0}{\log(6.58)} \times 0.6 = 2.2 \text{ s.}$$

Thus relay  $R_1$  should add discrimination time of 0.3 s., i.e., the operating time should be  $2.2 + 0.3 = 2.5$  s.

Now relay  $R_1$  is a backup for relay  $R_2$  and therefore it will see the same maximum fault current of 658 A. Then for the same  $PS\%_1=6.25$

$$PSM_1 = \frac{\left( \frac{I_{f \max 2}}{CTR_1} \right)}{I_{pickup1}} = \frac{658}{6.25} = 105.28. \text{ Then, } TMS_1 \text{ can be calculated from}$$


$$t_1 = \frac{3.0}{\log(PSM_1)} \times TMS_1 = \frac{3.0}{\log(105.28)} \times TMS_1 = 4.16 \times TMS_1 = 2.5 \text{ s} \Rightarrow TMS_1 = \frac{2.5}{4.16} = 0.60.$$

**Table Q3-b: PS and TSM of O/C Relays**

Parameter	R <sub>1</sub>	R <sub>2</sub>	R <sub>3</sub>	R <sub>4</sub>
CT ratio	100:5	100:5	50:5	50:5
PS %	125%	100%	125%	125%
TMS	0.6	0.6	0.6	0.5

# # Coordination:

consider the following system:

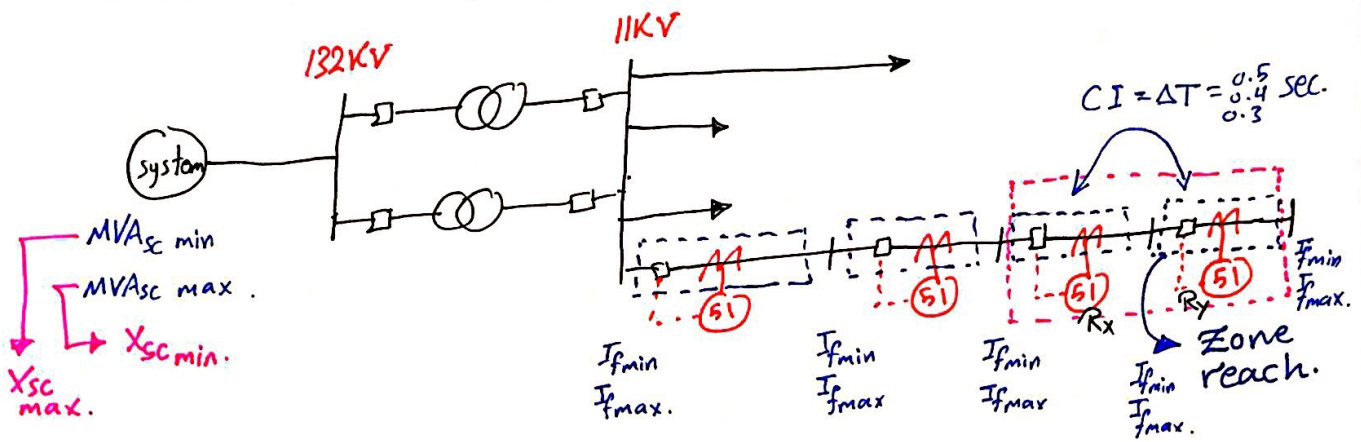


## Notes:

- \*  $R_x$  should back up Relay  $R_y$  & pick-up for min fault seen by  $R_y$ .
- \* The weak fault current is that at the most right of the system.
- \*  $I_{pick-up}$  Based on MAX. Load.
- \* The minimum fault current obtained from (L-L) when one transformer working.

## Tutorial #4:

Q1

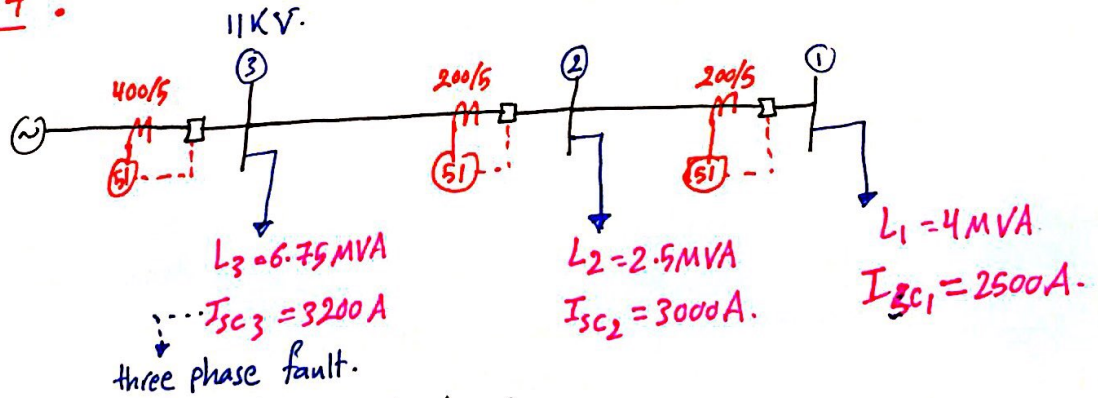

• we always start calculating for the last relay:

$$I_{L1} = \frac{4 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 210 \text{ A.}$$

$$I_{L2} = \frac{2.5 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 131 \text{ A.}$$

$$I_{L3} = \frac{6.75 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 354 \text{ A.}$$

$$I_{21} = 210 \text{ A.}, \quad I_{32} = 341 \text{ A.}, \quad I_{source} = 695 \text{ A.}$$

$$I'_{21} = I'_{r1} = \frac{210}{\frac{200}{5}} = 5.25 \text{ A.} \Rightarrow CTS_1 = 6 \text{ A.}$$

$$I'_{32} = I'_{r2} = \frac{341}{\frac{200}{5}} = 8.5 \text{ A.} \Rightarrow CTS_2 = 10 \text{ A.}$$


$$I'_s = I'_{r3} = \frac{695}{\frac{400}{5}} = 8.7 \text{ A.} \Rightarrow CTS_3 = 10 \text{ A.}$$

COF-CTS {4, 5, 6, 7, 8, 10, 12}

CUT - TDS = { 1/2, 1, 2, ... } #

⇒ Now choose  $TDS_1 = \frac{1}{2}$  # "since it is the top of the right relay we choose the min. time TDS"  
 $TDS_2 = ?$   
 $TDS_3 = ?$

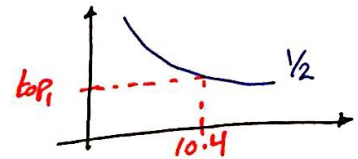$CTS_1 = 6A \equiv 240$  primary.  
 $CTS_2 = 10A \equiv 400A$  primary.  
 $CTS_3 = 10A \equiv 800A$  primary.



for  $I_{sc1} = 2500A \Rightarrow PSM_1 = \frac{2500}{240} = 10.4$

from the c/c  $\Rightarrow \underline{top_1 = 0.15 \text{ sec.}}$

\* choose  $CI = 0.4 \text{ sec.}$


$top_2 = 0.4 + 0.15 = \underline{0.55 \text{ sec.}}$

$\Rightarrow top_2 = f(PSM_2) \times TDS_2$

$PSM_2 = \frac{2500}{400} = 6.25$

from the given curve:

$\Rightarrow \underline{TDS_2 = 2}$  #

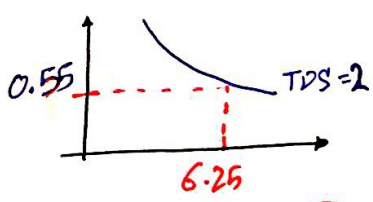

Now for  $R_3$  & a fault @ Bus 2:

$PSM_2 = \frac{3000/2045}{10} = 7.5$

$\Rightarrow TDS_2 = 2$

from the curve:


$top_2 = \underline{0.5 \text{ sec.}}$

$\Rightarrow top_3 = 0.5 + 0.4 = 0.9 \text{ sec.}$

$PSM_3 = \frac{3000/400/5}{10} = 3.75$

from the curve:

$\underline{TDS_3 = 2.5}$  #

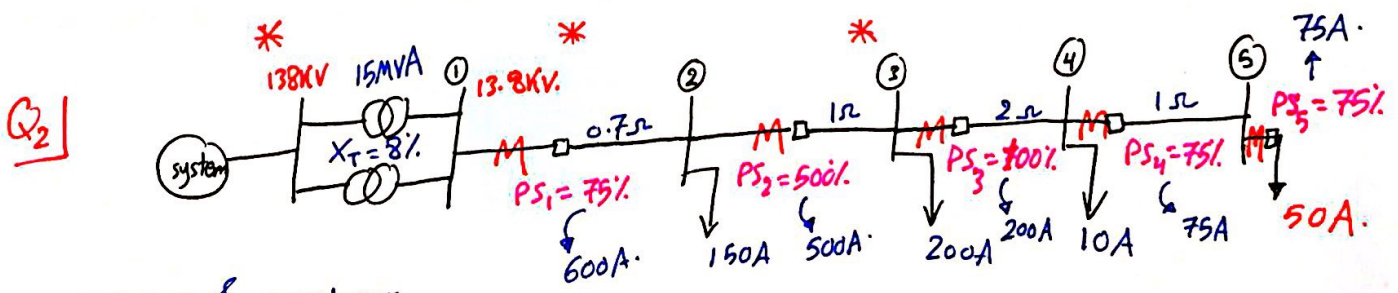

minimum & maximum fault current given @ each busbar.

we want to find  $TDS_{1,2,3,4,5}$ .

$\Rightarrow$  choose  $\underline{TDS_5 = 1}$

\* We calculate for the MAX. Fault current.



$$t_{p5} = \left[ \frac{28.2}{\left(\frac{1335}{75}\right)^2 - 1} + 0.1217 \right] \times 1.0 = \underline{0.21 \text{ sec.}}$$

\* CI = 0.4 sec.

R<sub>4</sub> will back-up R<sub>5</sub> after 0.4 sec.  $\Rightarrow t_{op4} = 0.4 + 0.21 = \underline{0.61 \text{ sec.}}$

Back to the main equation:  $0.61 = \left[ \frac{28.2}{\left(\frac{1335}{75}\right)^2 - 1} + 0.1217 \right] \times TDS_4$   
 $\Rightarrow TDS_4 = 2.9 \Rightarrow$  choose TDS<sub>4</sub> = 3

$$\Rightarrow t_{op4} = \left[ \frac{28.2}{\left(\frac{1335}{75}\right)^2 - 1} + 0.1217 \right] \times 3 \Rightarrow \underline{t_{op4} = 0.63 \text{ sec.}}$$

$$t_{op4} = \left[ \frac{28.2}{\left(\frac{1603}{75}\right)^2 - 1} + 0.1217 \right] \times 3 \Rightarrow \underline{t_{op4} = 0.55 \text{ sec.}}$$

$$t_{op3} = 0.55 + 0.4 = 0.95 \text{ sec.} = \left[ \frac{28.2}{\left(\frac{1603}{200}\right)^2 - 1} + 0.1217 \right] \times TDS_3$$


$$\Rightarrow \text{TDS}_3 = 1.7$$

for R<sub>3</sub>:

$$I_{fmax3} = 2683A.$$

$$t_{op3} = \left[ \frac{28.2}{\left(\frac{2683}{200}\right)^2 - 1} + 0.1217 \right] \times 1.7$$
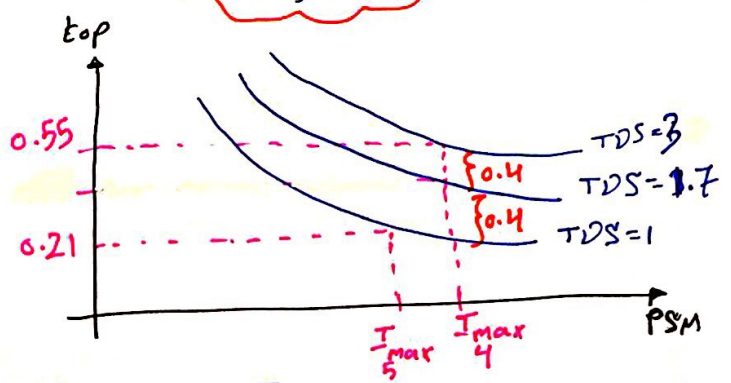
$$\Rightarrow \underline{t_{op3} = 0.48 \text{ sec.}}$$



$$t_{op2} = 0.48 + 0.4 = 0.88 \text{ sec.} = \left[ \frac{28.2}{\left(\frac{2683}{500}\right)^2 - 1} + 0.1217 \right] \times TDS_2 \Rightarrow \text{TDS}_2 = 0.8$$

@ Bus 2 I<sub>fmax2</sub> = 4045A.


$$t_{op2} = \left[ \frac{28.2}{\left(\frac{4045}{500}\right)^2 - 1} + 0.1217 \right] \times 0.8 = \underline{0.45 \text{ sec}}$$

$$R_1 \text{ back-up } R_2: t_{op1} = 0.45 + 0.4 = 0.85 \text{ sec.} = \left[ \frac{28.2}{\left(\frac{4045}{600}\right)^2 - 1} + 0.1217 \right] \times TDS_1$$

$$\Rightarrow \text{TDS}_1 = 1.1$$


\* \* \*

Q3

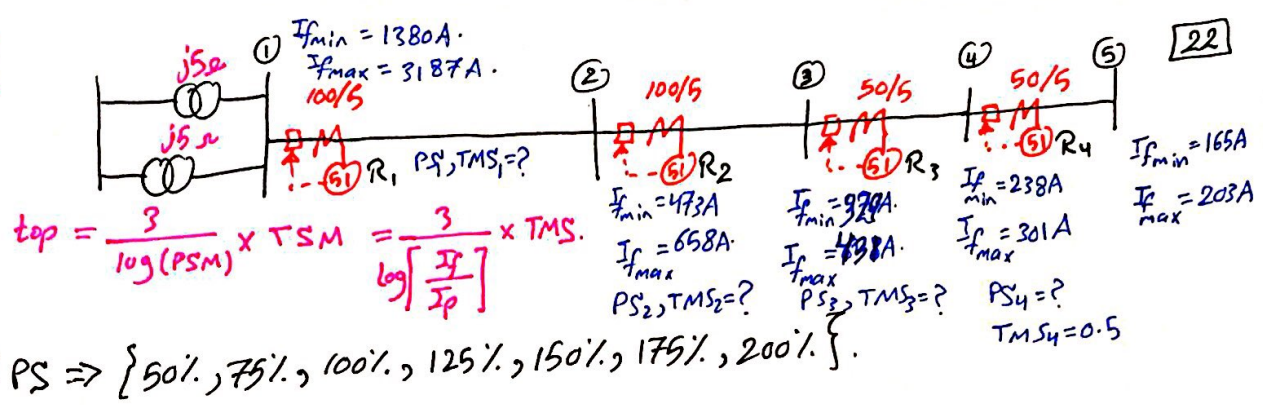

$I_{pick-up} = \frac{1}{3} I_{p_{min}} = \frac{1}{3} \times 165 = 55A$  (primary).  
 $I'_{pick-up} = 5.5A$  (secondary).

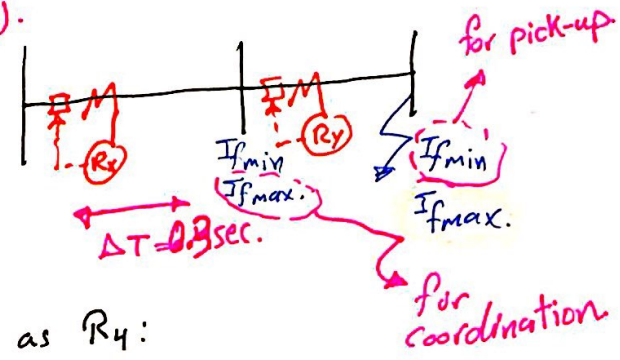so  $\% PS_4 = \frac{5.5}{5} \times 100\% = 110\%$   
 choose  $PS_4\% = 125\%$  #



for  $PS_3\%$  it must be the same setting as  $R_4$ :

$PS_3\% = 125\%$  #

$t_{op4} = \frac{3}{\log\frac{301}{62.5}} \times 0.5 = 2.2 sec \Rightarrow t_{op3} = 0.3 + 2.2 = 2.5 sec = \frac{3}{\log\frac{301}{62.5}} \times TMS_3$   
 $\Rightarrow TMS_3 = 0.6$  #

$I_{pick-up2} = \frac{1}{3} \times 238 = 79.3A$   
 $I'_2 = \frac{79.3}{20} \approx 4A$

so  $\% PS_2 = \frac{4}{5} \times 100\% = 80\%$  choose:  $PS_2\% = 100\%$  #

$t_{op3} = \frac{3}{\log\frac{431}{62.5}} \times 0.6 = 2.15 sec \Rightarrow t_{op2} = 0.3 + 2.15 = 2.45 sec = \frac{3}{\log\frac{431}{100}} \times TMS_2$   
 $@ I_{f_{max}} = 431A \Rightarrow TMS_2 = 0.6$  #

$I_{p1} = \frac{1}{3} \times 329 \approx 110A$   
 $I'_{p1} = \frac{110}{20} = 5.5A$

so  $\% PS_1 = \frac{5.5}{5} \times 100\% = 110\%$  choose:  $PS_1\% = 125\%$  #

$t_{op2} = \frac{3}{\log\frac{658}{100}} \times 0.6 = 2.2 sec \Rightarrow t_{op1} = 0.3 + 2.2 = 2.5 sec = \frac{3}{\log\frac{658}{125}} \times TMS_1$   
 $@ I_{f_{max}} = 658A \Rightarrow TMS_1 = 0.6$  #



# Power Systems Analysis II

---

---

Second Semester  
2018

---

---

Dr. Eyad Feilat  
e.feilat@ju.edu.jo

Notebook:

By. Mohammad  
Abu Hashya.

---


---




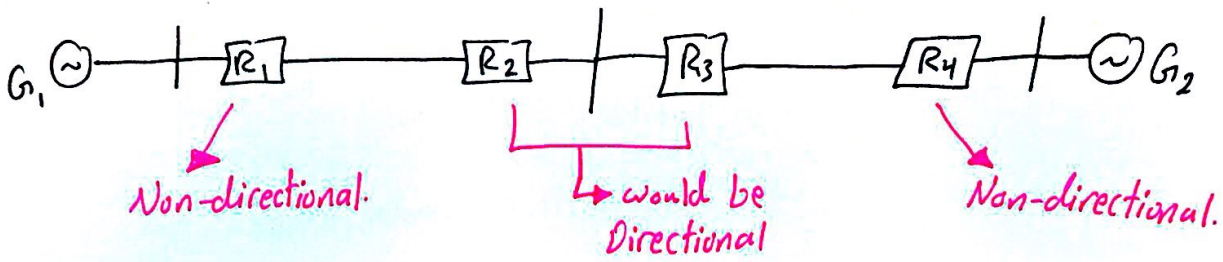
### \* Over Current Protection :

• Unit Relay: it protect a certain part of the system.




\* Example: Consider the following simple ring main:

Given that:  $t_p = \frac{0.14}{I_r^{0.02} - 1} \times TMS$

R<sub>1</sub> & R<sub>8</sub> are Non-directional.  
R<sub>2</sub> - R<sub>7</sub> are directional.

a) Draw the radial networks when CB<sub>1</sub> & CB<sub>8</sub> are open?

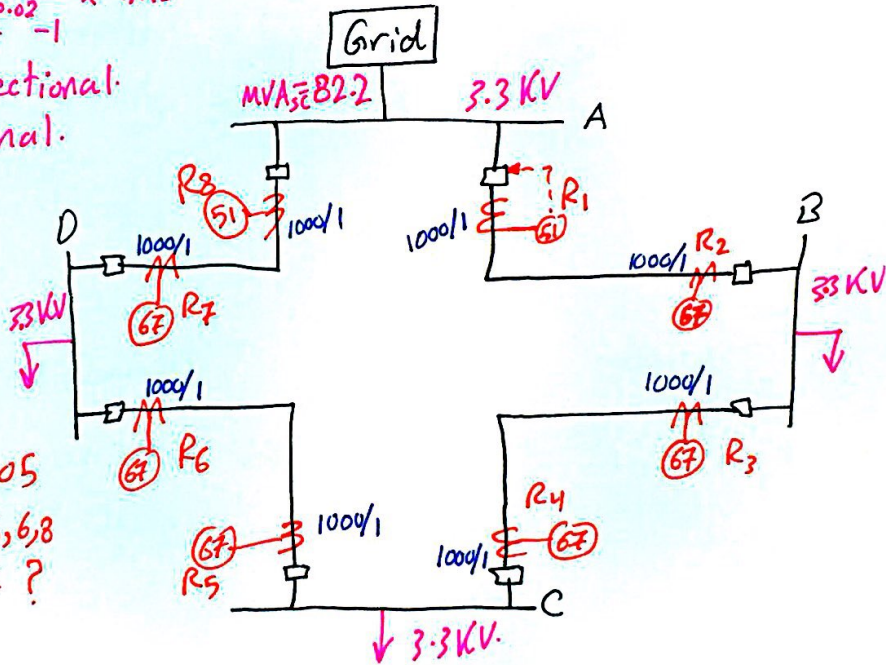
b) Given R<sub>2</sub> & R<sub>7</sub> TMS = 0.05  
Then find TMS<sub>1,3,4,5,6,8</sub>  
using  $\Delta T = 0.35 \text{ SEC}$ ?



Also the following informations are given:

CW (CB <sub>8</sub> open)			CCW (CB <sub>1</sub> open)		
Bus	I <sub>r</sub> (KA)	PS%	Bus	I <sub>r</sub> (KA)	PS%
D	3376	R <sub>7</sub> (80)	B	3376	R <sub>2</sub> (80)
C	4259	R <sub>5</sub> (88)	C	4259	R <sub>4</sub> (88)
B	7124	R <sub>3</sub> (97)	D	7124	R <sub>6</sub> (97)
A	14387	R <sub>1</sub> (107)	A	14387	R <sub>8</sub> (107)

Solution: for the breaker 8 open:

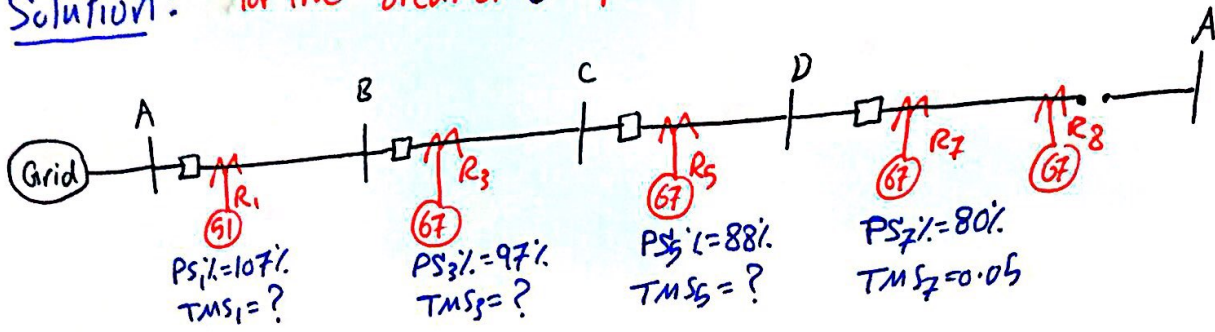

\*  $PS_7\% = 80\%$ . (800A prim. = 0.8A secondary)

$$t_{op7} = \frac{0.14}{\left(\frac{3376}{800}\right)^{0.02} - 1} \times 0.05 = \underline{0.24 \text{ sec}}$$

\*  $PS_5\% = 88\%$ . (880 A primary) ;  $t_{op5} = 0.3 + 0.24 = \underline{0.54 \text{ sec.}}$

$$0.54 = \frac{0.14}{\left(\frac{3376}{880}\right)^{0.02} - 1} \times TMS_5 \Rightarrow \boxed{TMS_5 = 0.105} \#$$

$$t_{op5} = \frac{0.14}{\left(\frac{4259}{880}\right)^{0.02} - 1} \times 0.105 = \underline{0.46 \text{ sec.}}$$

@  $I_f = 4259A$

\*  $PS_3\% = 97\%$ . (970A primary) ;  $t_{op3} = 0.3 + 0.46 = \underline{0.76 \text{ sec.}}$


$$0.76 = \frac{0.14}{\left(\frac{4254}{970}\right)^{0.02} - 1} \times TMS_3 \Rightarrow \boxed{TMS_3 = 0.163} \#$$

$$t_{op3} = \frac{0.14}{\left(\frac{7129}{970}\right)^{0.02} - 1} \times 0.163 = \underline{0.56 \text{ sec.}}$$

@  $I_f = 7129A$


\*  $PS_1\% = 107\%$ . (1070A primary) ;  $t_{op1} = 0.3 + 0.56 = \underline{0.86 \text{ sec.}}$
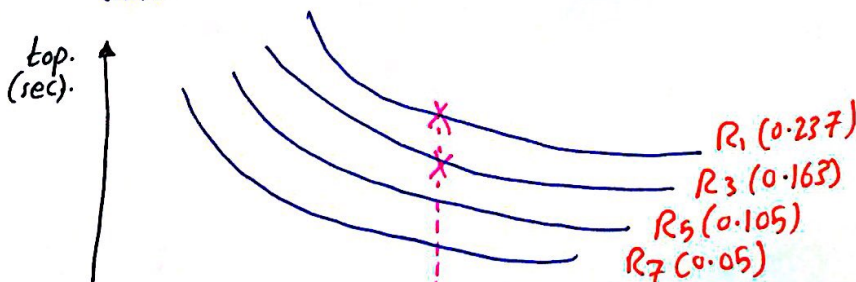
$$0.86 = \frac{0.14}{\left(\frac{7129}{1070}\right)^{0.02} - 1} \times TMS_1 \Rightarrow \boxed{TMS_1 = 0.237} \#$$




↪ If between B & C ⇒ R3 & R1 will work.

\* for the breaker 1 open:

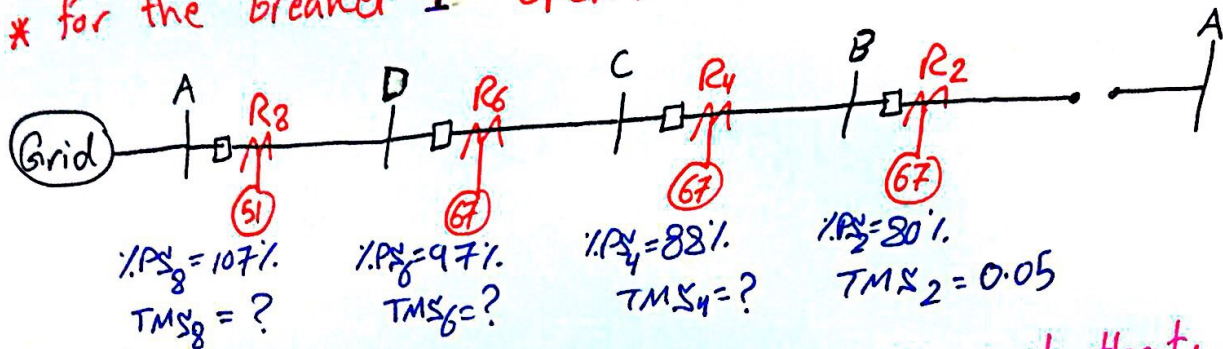

You will obtain the same previous answers such that:

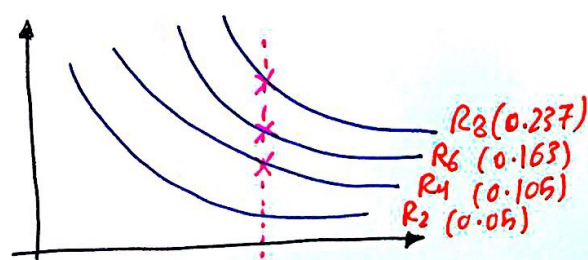$TMS_4 = 0.105$ ,  $TMS_6 = 0.163$ ,  $TMS_8 = 0.237$



$\Rightarrow R_4, R_6, R_8$  will work.

\* \* \*

\* Transformer Protection:

• 87G, 87T  $\Rightarrow$  differential protection, also called unit protection.

\* Why tap changer put on HV side?

- ① Since HV side is accessible.
- ② Since the HV side has lower current (lower sparks).

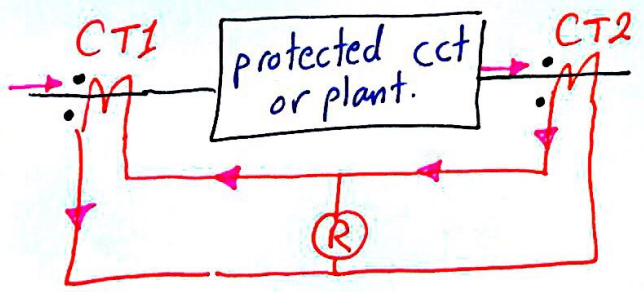


Fig. 1.

\* Some comments on Fig. 1:

- ① The currents in the transformer are NOT equal But we choose CT1 & CT2 such that they give the same current through the secondary i.e Zero Current through the relay.

$\Rightarrow$  Continue.






② at No-load condition,  $I_2 = 0$  so all the current will pass through the relay so we need to have settings for the relay to work for current higher than the rated current.

**\* Balanced Circulating Current:**


- \* External fault case: The contacts will be normally opened  $\Rightarrow$  (No tripping).
- \* Internal fault case:  $\Rightarrow$  tripping will occur.

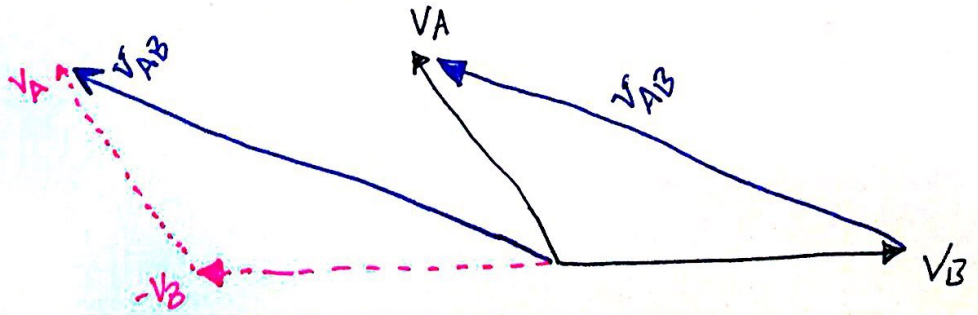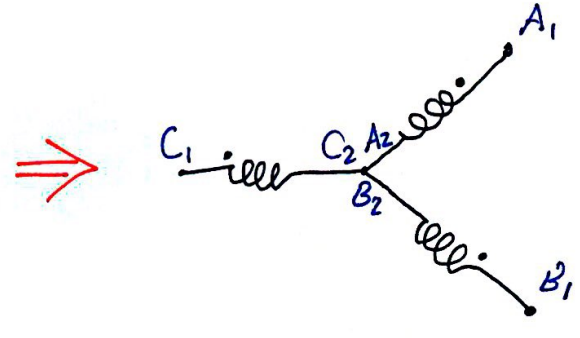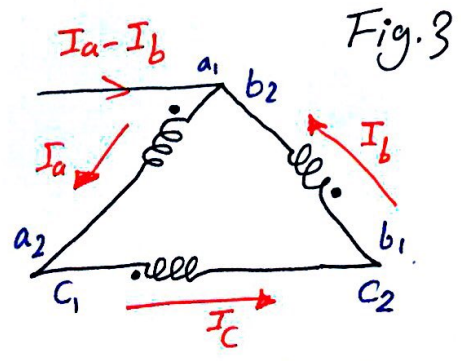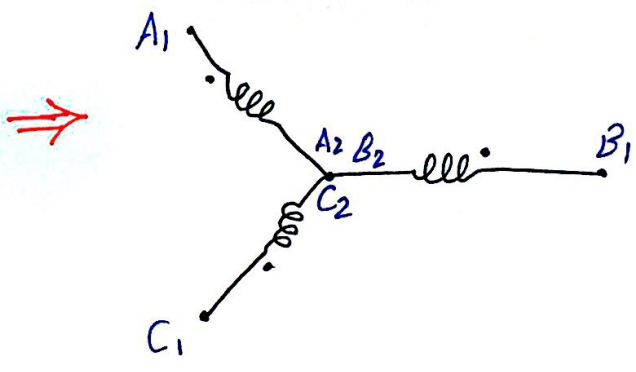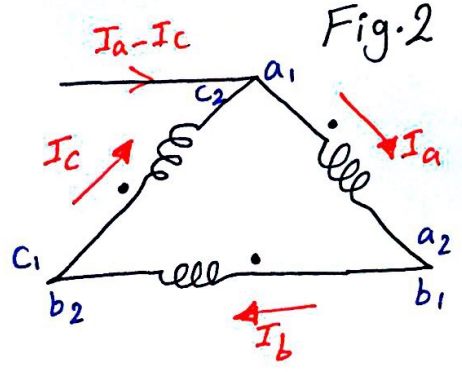**\* Winding Polarity:**


for  $\Delta \lambda$  connection: (phase voltages are in-phase)




\* for Fig. 2:

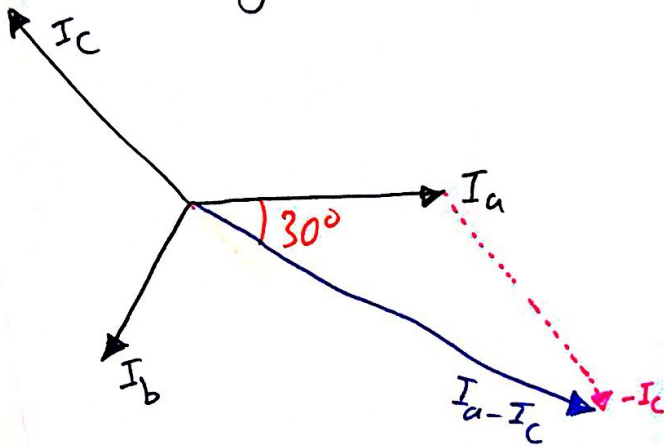


\* for Fig. 3:

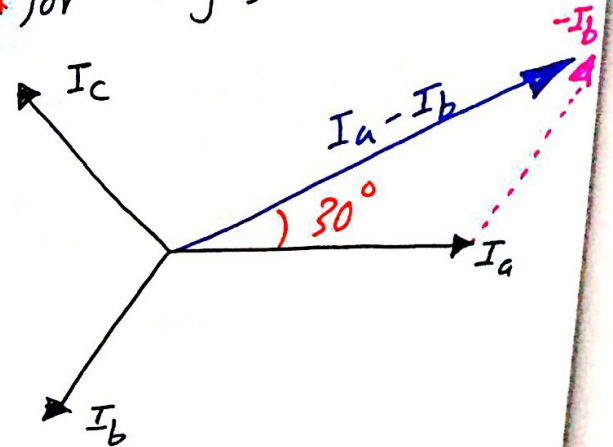

\* for Fig. 2:

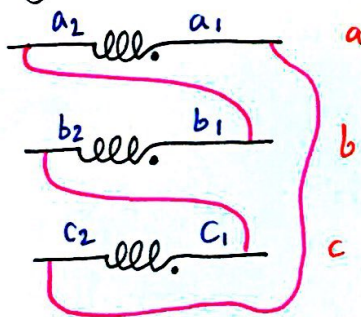

\* for Fig. 3:

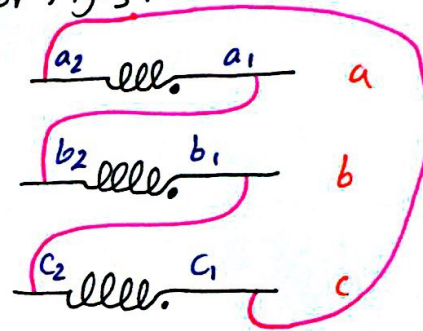

\* Consider  $\Delta$ - $Y$  connected transformer 10 MVA,  $\frac{HV}{LV} = \frac{33}{11}$  KV  
 HV (capital letter), LV (small letter).

$$S_{3\phi} = \sqrt{3} V_H I_H = \sqrt{3} V_L I_L = 10 \text{ M}$$

$$\Rightarrow \sqrt{3} \times 33 \times 10^3 I_H = \sqrt{3} \times 11 \times 10^3 \times I_L = 10 \text{ M}$$

$$I_H = \frac{10 \times 10^6}{\sqrt{3} \times 33 \times 10^3} = 174.9 \approx 175 \text{ A.}$$

$$I_L = \frac{10 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 524.8 \approx 525 \text{ A}$$


$$\left. \begin{array}{l} I_L \\ I_H \end{array} \right\} \frac{I_L}{I_H} = \frac{V_H}{V_L} = \frac{33}{11} = 3$$



• Now choosing a proper CTR for the both sides:

$$CTR_{HV} = 200/5 \quad \& \quad CTR_{LV} = 600/5$$

$$I_{A'} = \frac{I_A}{CTR_{HV}} = \frac{175}{200/5} = 4.38 \text{ A.}$$
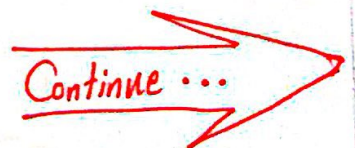
$$I_{a'} = \frac{I_a}{CTR_{LV}} = \frac{525}{600/5} = 4.38 \text{ A.}$$




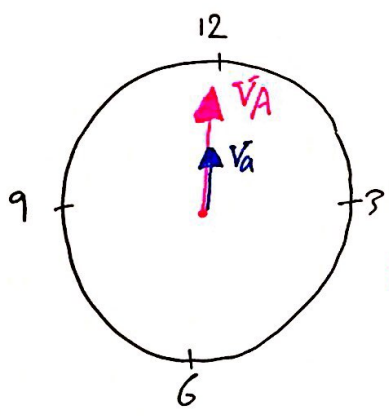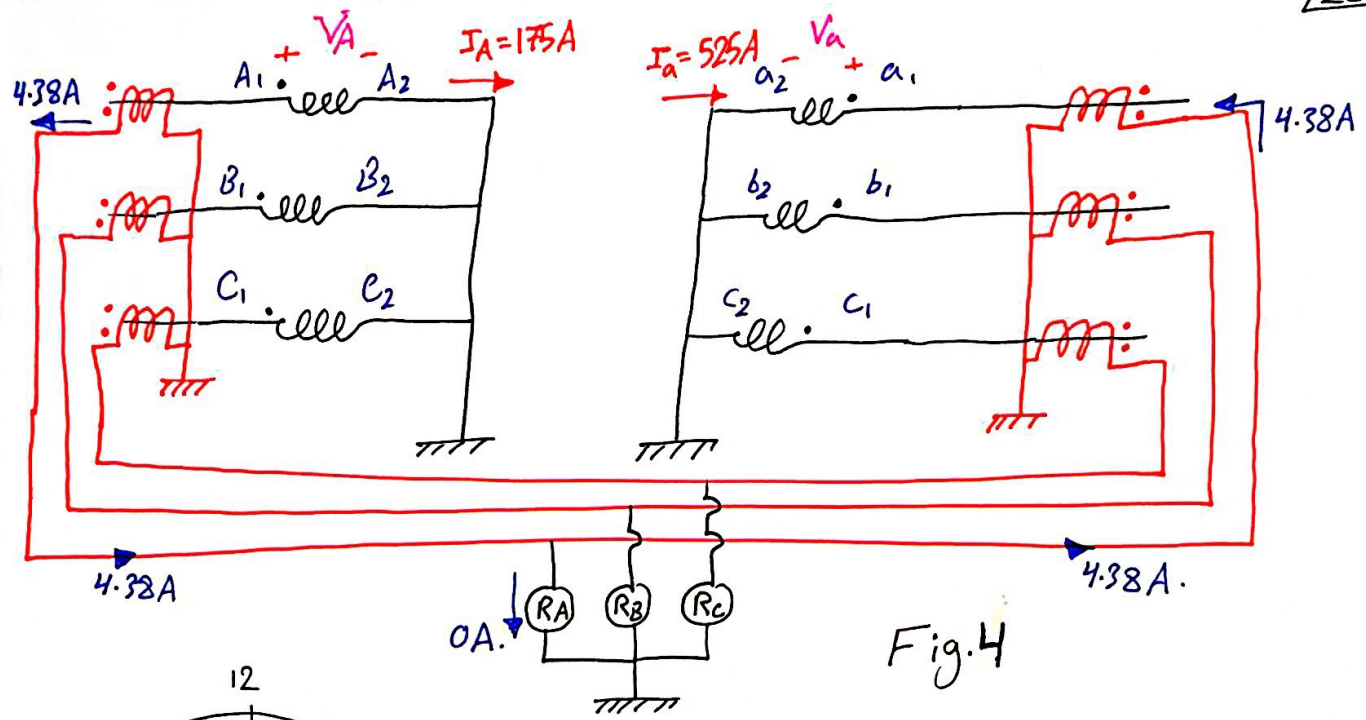


⇒ 0-phase shift

This is represented as:  $Y_N Y_n 0$



for Fig. 4:

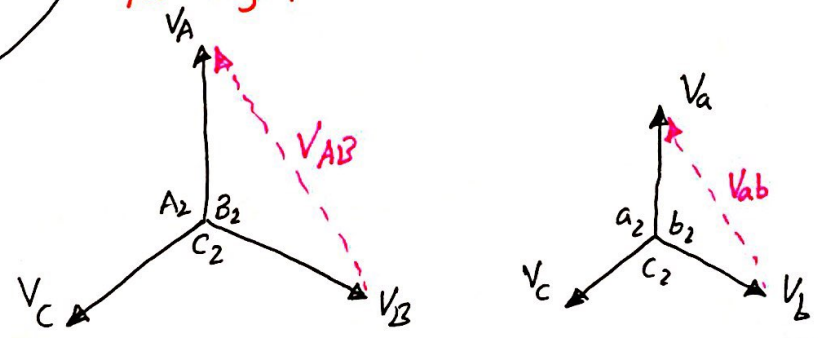

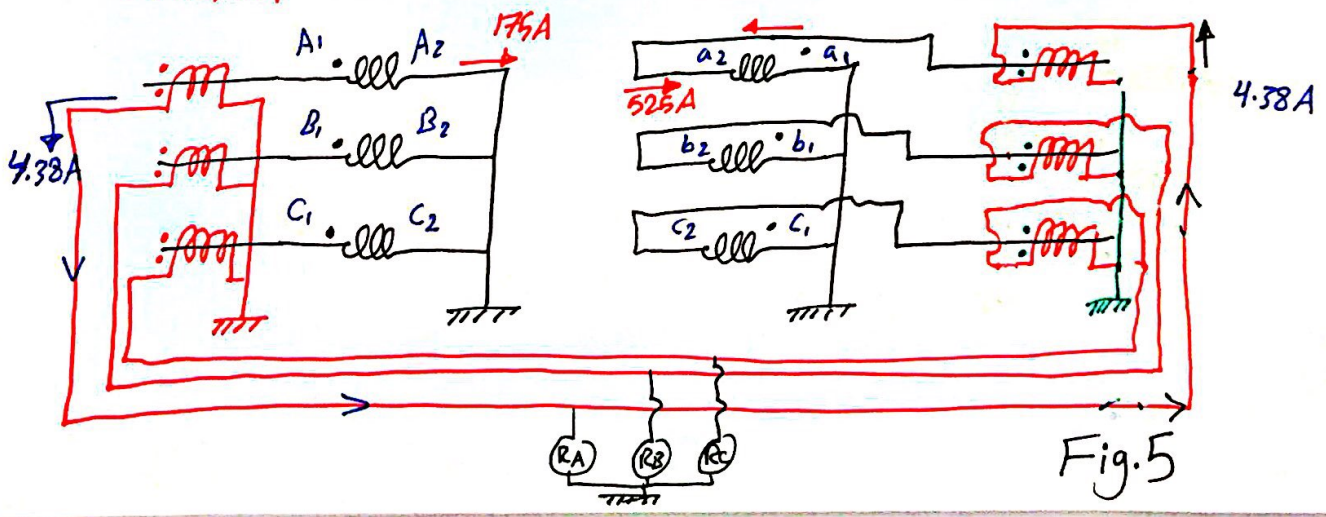\* Now Consider the same previous case But with grounding  $a_1, b_1, c_1$  in the LV side:




for Fig. 5:



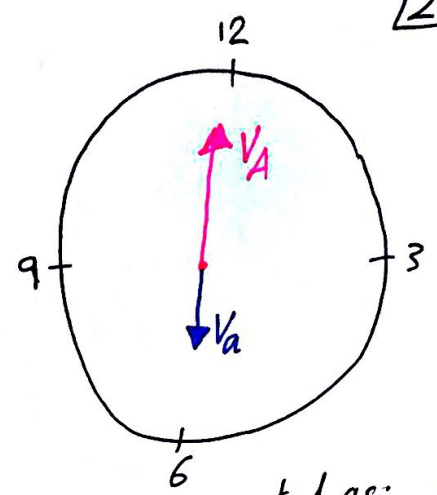
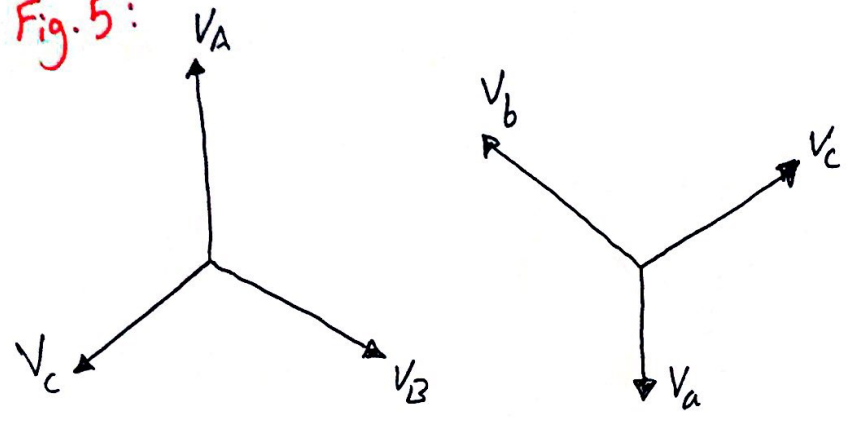


This is represented as:  
 $Y_n Y_n 6$  ( $180^\circ$  phase shift)


\* for  $\Delta-\Delta$ :

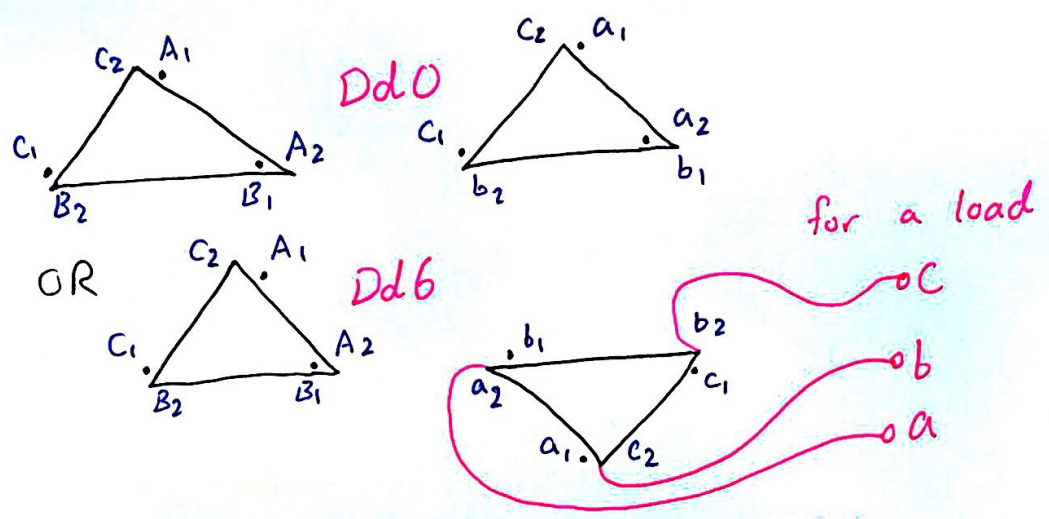

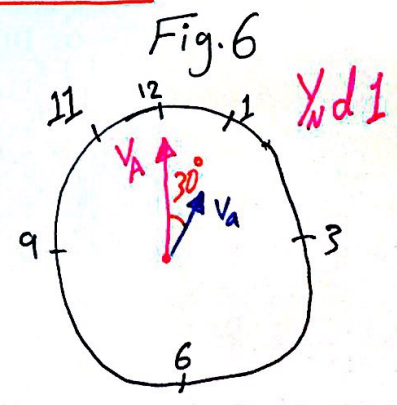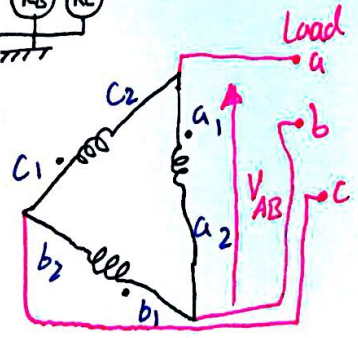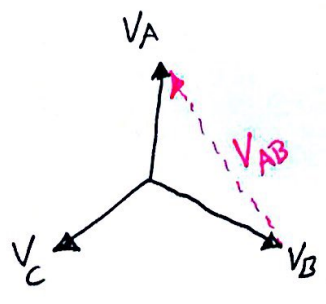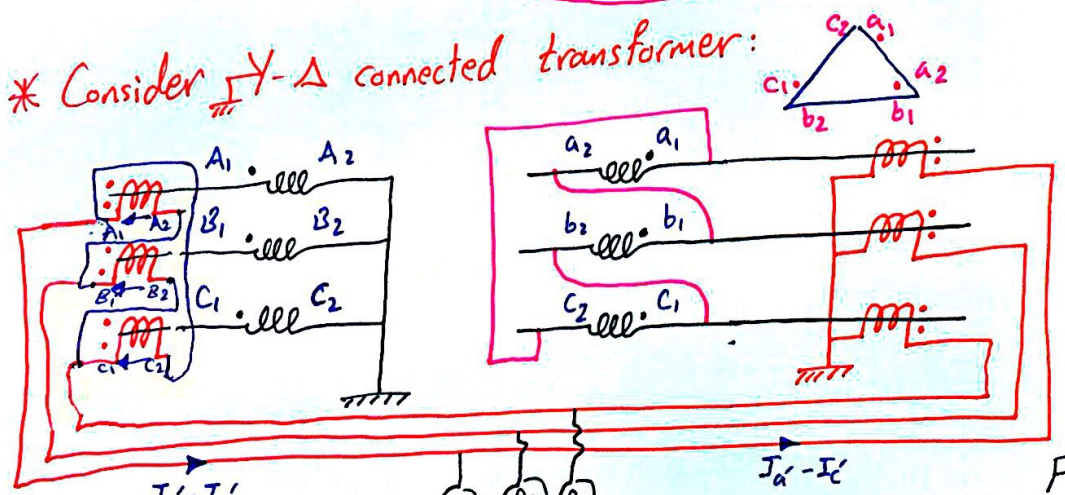
\* Consider  $Y-\Delta$  connected transformer:




for another case:

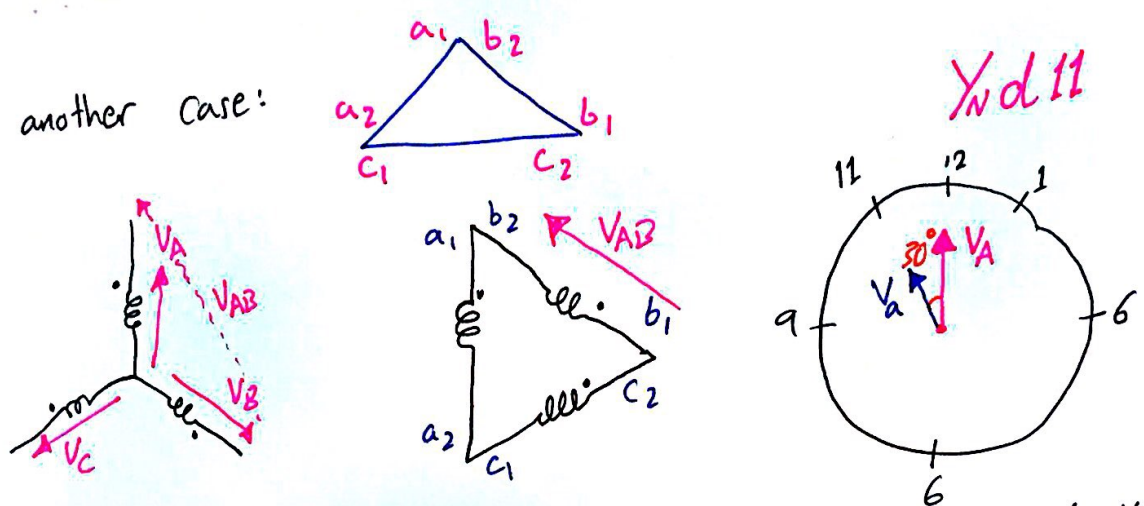

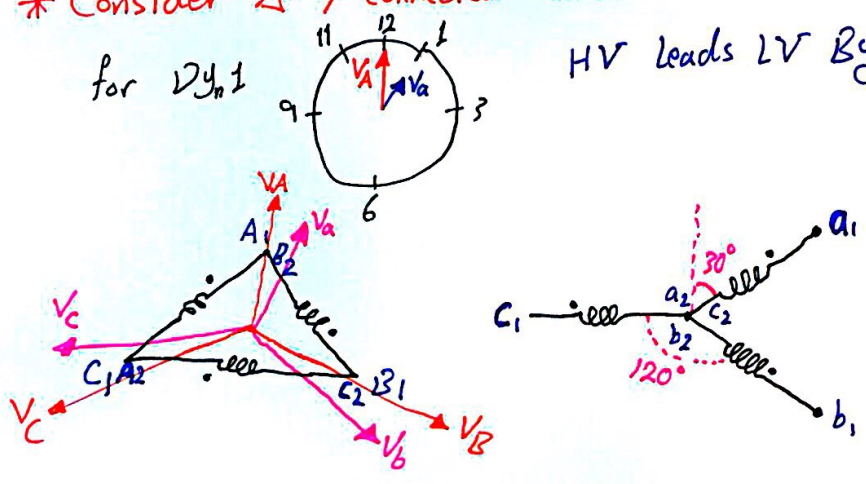\* Consider  $\Delta$ -Y connected Transformer ( $Dy_n 1$ ) with 10 MVA, 132/11 kV.  
 HV leads LV By  $30^\circ$ .



\* CT connection would be  $Y_n d 11$

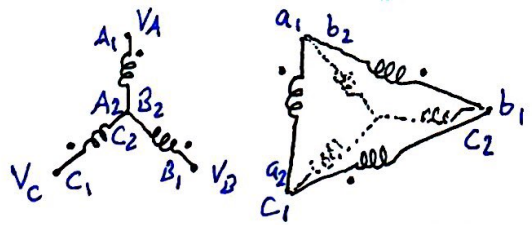

$$I_{HV \text{ rated}} = \frac{10 \times 10^6}{\sqrt{3} \times 132 \times 10^3} = 43.7 \text{ A} \Rightarrow CTR_{HV} = 50/1$$

$$I_{LV \text{ rated}} = \frac{10 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 524.4 \text{ A} \Rightarrow CTR_{LV} = 600/1$$

• Note that: the current through the secondary (CT):

$$I'_{HV} = \frac{43.7}{50} = 0.874 \text{ A.}$$


$$I'_{LV} = \frac{524.4}{600\sqrt{3}} = 0.874 \text{ A.}$$

}  $\Rightarrow$  current passes through the Relay = Zero.



$\rightarrow$  This obtained choosing an appropriate  $CTR_{LV} = 600\sqrt{3}/1$

Continue...



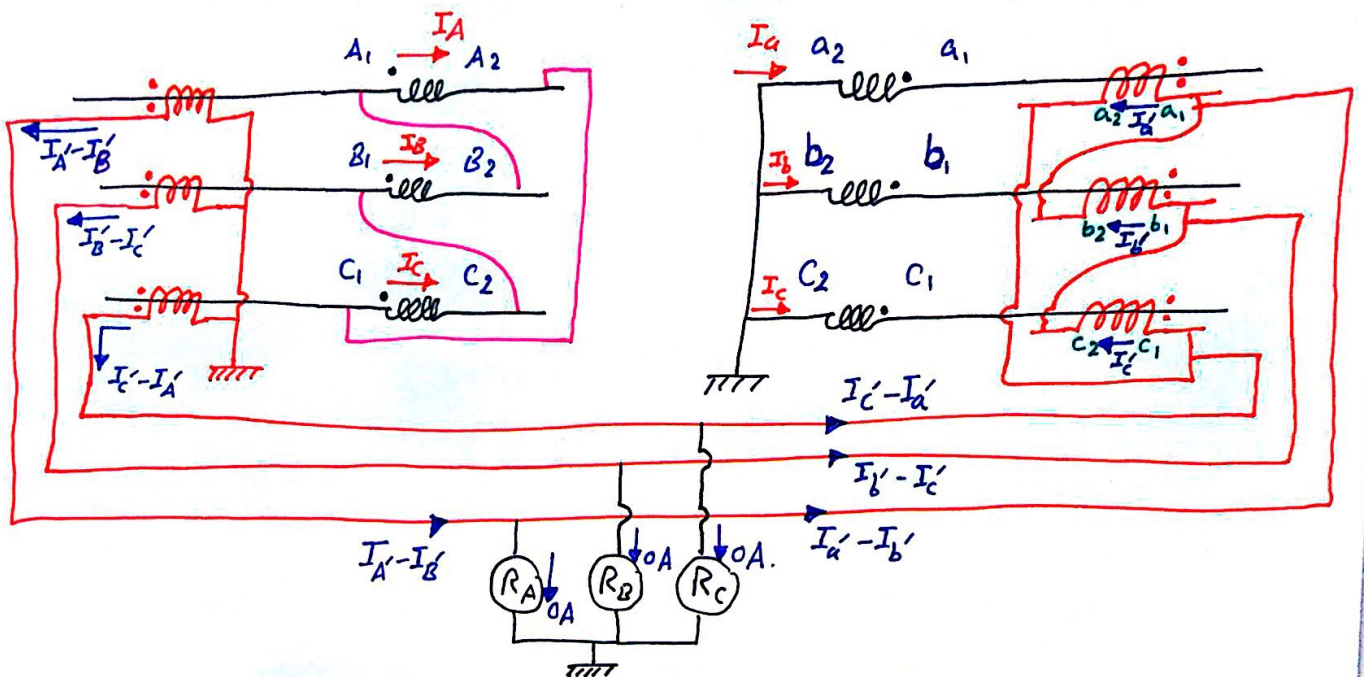

\* for a  $\Delta y7$  connection :

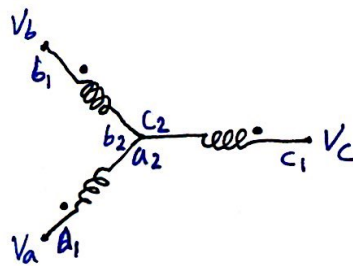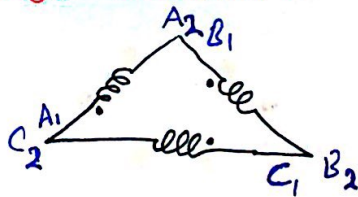

**Problem # 1**

Consider a  $\Delta/Y$ -connected, 20-MVA, 33/11-kV transformer with differential protection applied, for the current transformer ratios shown in Fig. P1. Calculate:

- the relay currents on full load.
- the minimum relay current setting to allow 125 percent overload.

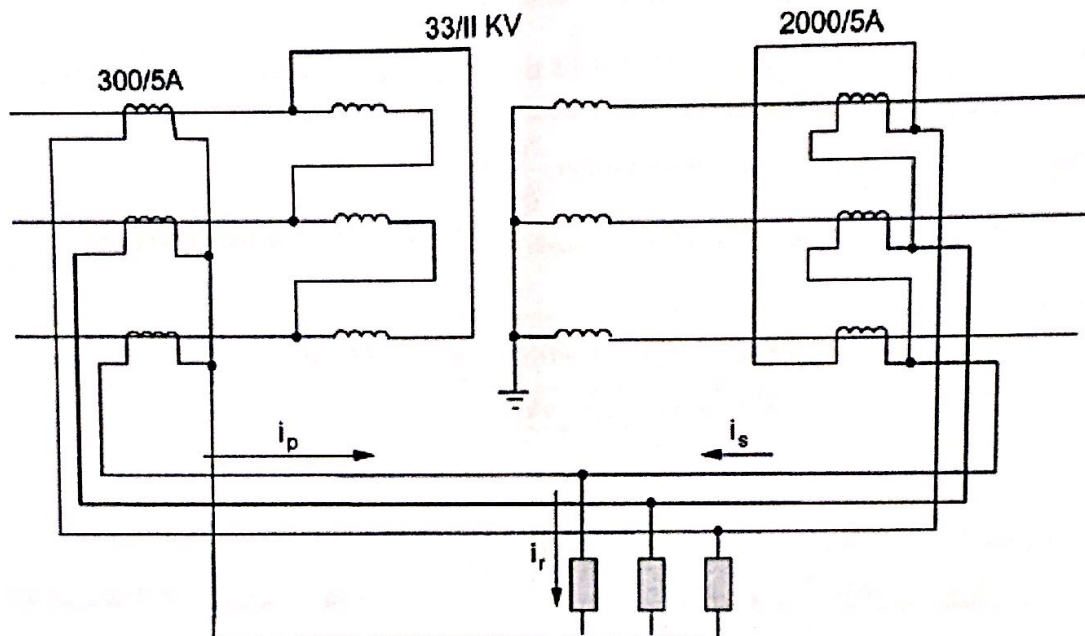


Fig. P1

**Solution:**

The primary line current is given by

$$I_p = \frac{20 \times 10^6}{(\sqrt{3})(33 \times 10^3)} = 349.91 \text{ A}$$

$$i_p = 349.91 \left( \frac{5}{300} \right) = 5.832 \text{ A}$$

The secondary line current is

$$I_s = \frac{20 \times 10^6}{(\sqrt{3})(11 \times 10^3)} = 1049.73 \text{ A}$$

The C.T. current in the secondary side is

$$i_s = 1049.73 \left( \frac{5}{2000} \right) \sqrt{3} = 4.545 \text{ A}$$

Note that we multiply by  $\sqrt{3}$  to obtain the values on the line side of the  $\Delta$ -connected C.T.'s. The relay current on normal load is therefore

$$i_r = i_p - i_s = 5.832 - 4.545 = 1.287 \text{ A}$$

With 1.25 overload ratio, the relay setting should be

$$I_r = (1.25)(1.287) = 1.61 \text{ A}$$

### Problem # 2

For the  $\Delta y11$  transformer shown in Fig. P4, there is a phase angle difference between primary and secondary equal to  $-30^\circ$ . So, an auxiliary current transformer (matching) is installed in the secondary circuit of 11 kV current transformer side to compensate the magnitude and phase. Determine:

- the primary ( $I_{L66P}$ ) and secondary ( $I_{L11S}$ ) currents of the  $\Delta Y$ -connected transformer when the transformer is delivering its rated MVA.
- the currents seen by the CTs on the  $\Delta$ -connected primary ( $I_{CT\Delta-S}$ ,  $I_{CTB\Delta-S}$ , and  $I_{CTC\Delta-S}$ ) side and the currents seen by the Y-connected secondary ( $I_{CTAY-S}$ ,  $I_{CTBY-S}$ , and  $I_{CTCY-S}$ ) side of the transformer.
- the line current of the primary Y-side of the matching transformer ( $I_{P-match-L}$ ) and of the line current of the secondary  $\Delta$ -side of the matching transformer ( $I_{S-match-L}$ ).
- the turns ratio of the matching transformer  $\frac{N_{P-match}}{N_{S-match}}$ .
- the currents seen by each relay ( $I_{relayA}$ ,  $I_{relayB}$ , and  $I_{relayC}$ ) under normal conditions.

### Solution:

$$I_{L66P} = (MVA \times 1000) / (\sqrt{3} \times 66 kV) = (25 \times 1000) / (\sqrt{3} \times 66) = 218.7 \text{ A}$$

$$I_{CT\Delta-S} = \frac{I_{L66P}}{CTR_p} = \frac{218.7}{400/5} = \frac{(25 \times 1000) / (\sqrt{3} \times 66)}{80} = \frac{218.7}{80} = 2.73 \text{ A}$$

$$I_{CT\Delta-S} = I_{CTB\Delta-S} = I_{CTC\Delta-S} = 2.73 \text{ A}$$

$$I_{L11S} = (MVA \times 1000) / (\sqrt{3} \times 11 kV) = (25 \times 1000) / (\sqrt{3} \times 11) = 1312.2 \text{ A}$$

$$I_{CTAY-S} = \frac{I_{L11S}}{CTR_s} = \frac{1312.2}{1500/5} = 4.37 \text{ A}$$

$$I_{CTAY-S} = I_{CTBY-S} = I_{CTCY-S} = 4.37 \text{ A} \text{ -- (Input to the matching transformer)}$$

For equilibrium of differential relay:-

Current of 11 kV of differential relay must be equal to current of 66 kV side of differential relay.

$$\Rightarrow I_{CT\Delta-S} = I_{CTY-S} = 2.73 \text{ A.}$$

But, input current of matching transformer is  $I_{match-P} = 4.37 \text{ A}$ . Therefore, the output current of the matching transformer (input to the differential relay) must be equal  $I_{match-S} = 2.73 \text{ A}$ .

**Note:** the connection of the matching transformer must be Y $\Delta$ 1 to compensate the original angle of the power transformer.

The turns ratio of the matching transformer  $N_{Pmatch} / N_{Smatch} = I_{Smatch-ph} / I_{Pmatch-ph}$ .

$$\frac{N_{P-match}}{N_{S-match}} = \frac{I_{S-match-ph}}{I_{P-match-ph}} = \frac{I_{Smatch-L} / \sqrt{3}}{I_{Pmatch-L}} = \frac{2.73 / \sqrt{3}}{4.37} = \frac{1.58}{4.37} \cong 0.36$$

$$\Rightarrow I_{Smatch-L} = 1.58 \text{ A.}$$

$$I_{relayA} = I_{CT\Delta-S} - I_{Smatch-L} = 2.73 - 2.73 = 0 \text{ A}$$

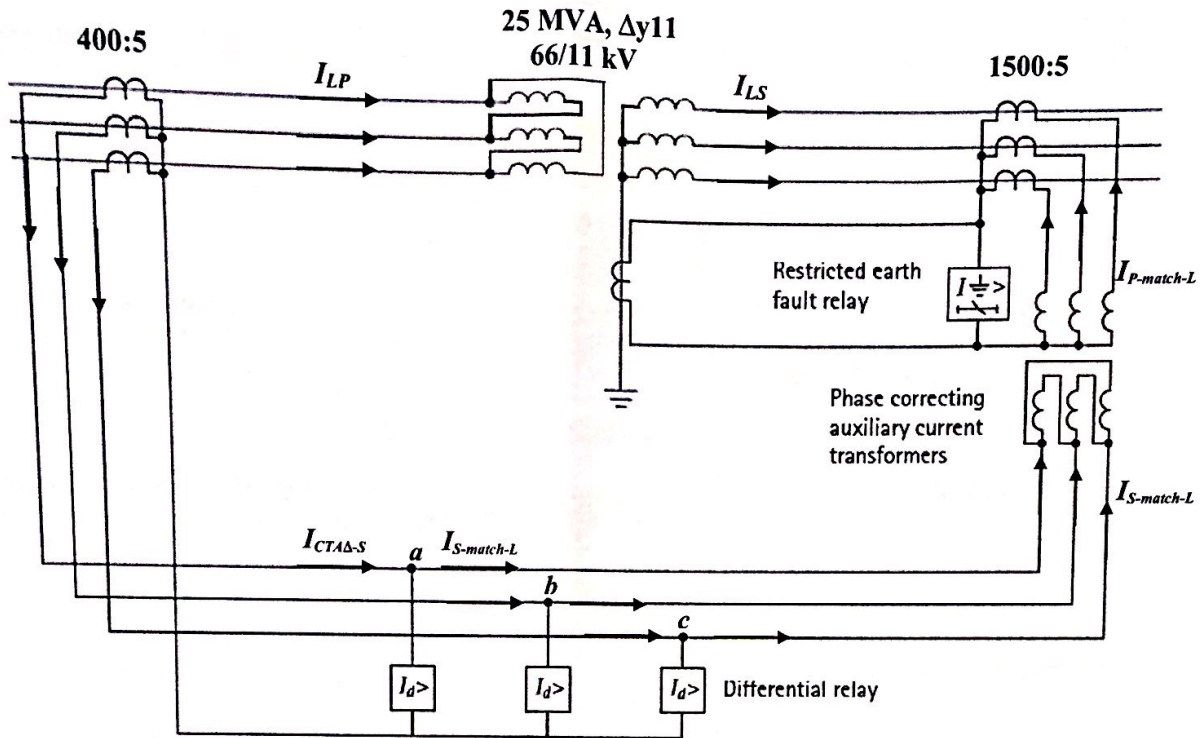


Fig. P4: Transformer Differential Protection

**Problem # 3**

Design the protection of a three-phase, 50-MVA, 230/34.5 kV power transformer, Fig. P3, using available standard CT ratios. The high-voltage side is Y-connected and the low-voltage side is Δ-connected. Specify the CT ratios, and show the three phase wiring diagram indicating the CT polarities. Determine the currents in the transformer and the CTs. Specify the rating of an autotransformer, if one is needed.

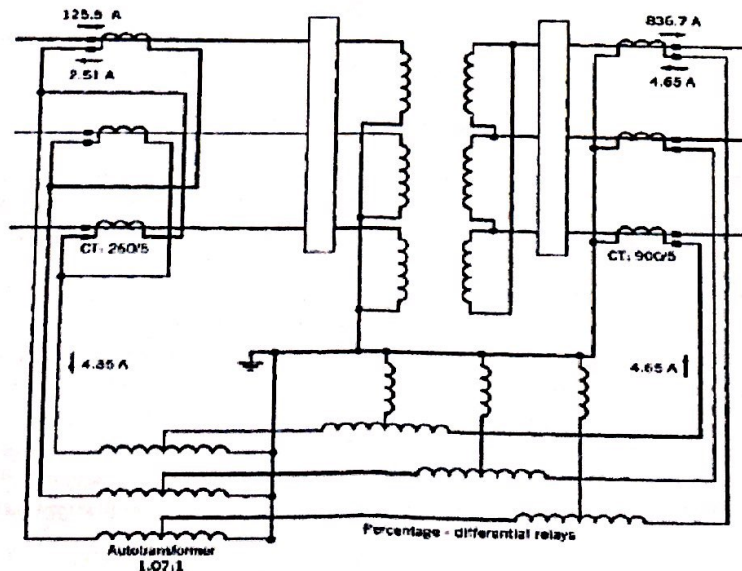


Fig P3: Y- Δ transformer protection

**Solution:**

When the transformer is carrying rated load, the line currents on the high-voltage side and low-voltage side are

$$I_{HV} = \frac{50,000}{\sqrt{3}(230)} = 125.5 \text{ A}$$

$$I_{LV} = \frac{50,000}{\sqrt{3}(34.5)} = 836.7 \text{ A}$$

The CTs on the low-voltage side are Y-connected, and the CT ratio selected for this side is 900/5. The current in the leads flowing to the percentage-differential relay on this side is equal to the CT secondary current and is given by

$$I_{LV\text{lead}} = 836.7 \left( \frac{5}{900} \right) = 4.65 \text{ A}$$

The current in the leads to the relay from the low-voltage side must be balanced by an equal current in the leads connected to the  $\Delta$ -connected CTs on the high-voltage side. This requires a CT secondary current equal to

$$I_{CT\text{sec}} = \frac{4.65}{\sqrt{3}} = 2.68 \text{ A}$$

To obtain a CT secondary current of 2.68 A, the CT ratio of the high-voltage CTs is chosen as

$$\text{CT ratio} = \frac{125.5}{2.68} = 46.8$$

The nearest available standard CT ratio is 250/5. If this CT ratio is selected, the CT secondary currents will actually be

$$I_{CT\text{sec}} = 125.5 \left( \frac{5}{250} \right) = 2.51 \text{ A}$$

Therefore, the currents in the leads to the  $\Delta$ -connected CTs from the percentage-differential relays will be

$$I_{HV\text{lead}} = \sqrt{3}(2.51) = 4.35 \text{ A}$$

It is seen that the currents in the leads on both sides of the percentage-differential relay are not balanced. This condition cannot just be ignored because it could lead to improper tripping of the circuit breaker for an external fault. This problem can be solved by using an autotransformer as shown in Fig. P3. The autotransformer should have a turns ratio of

$$N_{\text{autotransformer}} = \frac{4.65}{4.35} = 1.07$$

In the design of the transformer protection of Problem 3, the magnetizing current of the transformer has been assumed to be negligible. This is a reasonable assumption during normal operating conditions because the magnetizing current is a small percentage of the rated load current. However, when a transformer is being energized, it may draw a large magnetizing inrush current that soon decays with time to its normal value. The inrush current flows only in the primary, causing an unbalance in current, and the differential relay will interpret this an internal fault and will pick up to trip the circuit breakers. To prevent the protection system from operating and tripping the transformer during its energization, percentage-differential relaying with harmonic restraint is recommended. This is based on the fact that the magnetizing inrush current has high harmonic content, whereas the fault current consists mainly of fundamental frequency sinusoid. Thus, the current supplied to the restraining coil consists of the fundamental and harmonic components of the normal restraining current of  $(I_A + I_B)/2$ , plus another signal proportional to the harmonic content of the differential current  $(I_A - I_B)/2$ . Only the fundamental frequency of the differential current is supplied to the operating coil of the relay.

**Problem # 4**

A 3-phase 200 kVA, 11/0.4 kV 3-phase transformer is connected as  $\Delta Y$  as shown in Fig. P4. The CT on the 0.4 kV side has a CTR of 500/5 and the CT on the 11 kV side has a CTR of 10/5.

An earth fault of  $I_f = 750$  A fault current occurred on the blue phase within the protection zone. If the load current is negligible, find the following:

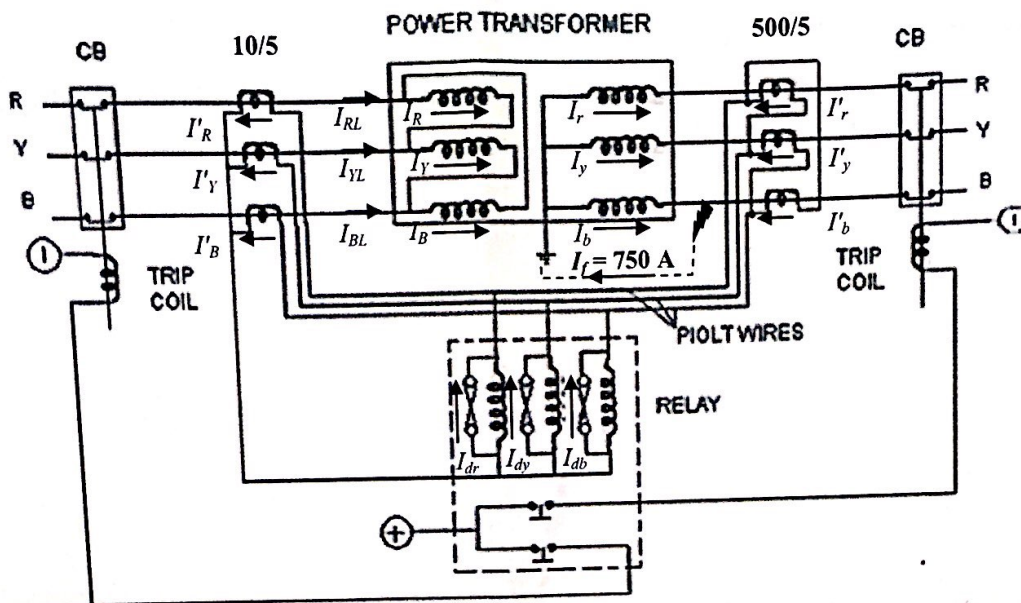


Fig. P4

1.	the LV red phase winding current, $I_r$	0	A
2.	the LV yellow phase winding current, $I_y$	0	A
3.	the LV blue phase winding current, $I_b$	750	A
4.	the HV red phase winding current, $I_R$	0	A
5.	the HV yellow phase winding current, $I_Y$	0	A
6.	the HV blue phase winding current, $I_B$	15.75	A
7.	the HV red phase line current, $I_{RL}$	-15.75	A
8.	the HV yellow phase line current, $I_{YL}$	0	A
9.	the HV blue phase line current, $I_{BL}$	15.75	A
10.	the HV red phase CT current, $I'_R$	-7.87	A
11.	the HV yellow phase CT current, $I'_Y$	0	A
12.	the HV blue phase CT current, $I'_B$	7.87	A
13.	the LV red phase CT current, $I'_r$	0	A
14.	the LV yellow phase CT current, $I'_y$	0	A
15.	the LV blue phase CT current, $I'_b$	0	A
16.	the red phase differential current, $I'_{dr}$	(7.87)	A
17.	the yellow phase differential current, $I'_{dy}$	0	A
18.	the blue phase differential current, $I'_{db}$	(7.87)	A


### **Problem # 5**

A three-phase step-down transformer bank is rated 10 MVA and 69/13.8kV. The high-voltage side is Y-connected, and the low-voltage side is  $\Delta$ -connected. Sketch the developed three-phase wiring diagram for the protection of the transformer bank using differential relays. Show all CT ratings, connections, and polarities. Also show the values of the current in the lines, leads, relay windings, and transformer windings. Indicate the connections and ratings of any autotransformer that may be needed.

### **Problem # 6**

Repeat Problem # 2 for the protection of a three-phase power transformer rated 100 MVA and 230/69kV. Assume that the transformer windings are Y-connected in both the primary and secondary sides.

# # Tutorial #5 :

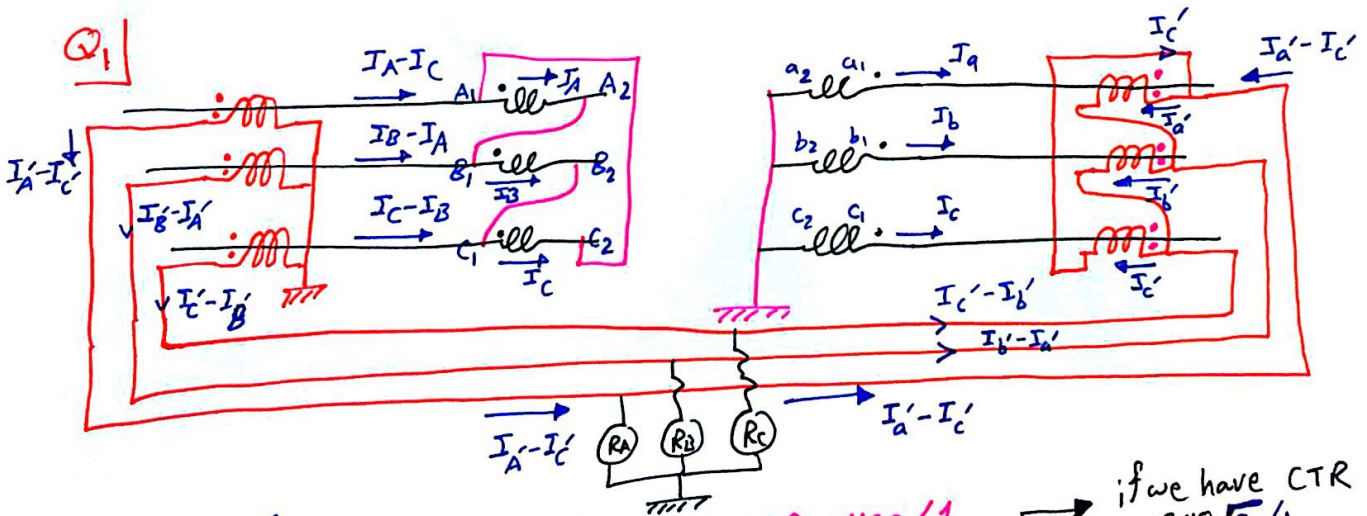

$$I_H = \frac{20 \times 10^6}{\sqrt{3} \times 33 \times 10^3} \approx 350 \text{ A.}$$

$$I_L = \frac{20 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 1050 \text{ A}$$

so choose CTR = 400/1

choose CTR = 1000/1

These CTR's will result  $I_{A'} - I_{C'} = 0.875$ ,  $I_{a'} - I_{c'} = 1.81$

if we have CTR =  $1200\sqrt{3}/1$   
 $\Rightarrow$  this will result  $I_{a'} - I_{c'} = 0.875$

so we need to increase the settings of the relay.






Also choosing  $CTR_{HV} = 300/5$ ,  $CTR_{LV} = 2000/5$

it will result:  $I_{A'} - I_{C'} = 5.83$ ,  $I_{a'} - I_{c'} = 4.5 A$ .



also need to increase the settings of the relay.  
OR manipulate the CTR's so that they would give 0 A through the relay;

$5.8 - 4.5 = 1.3 A$ , consider 25% overload.

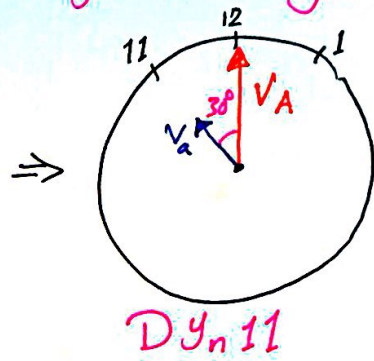
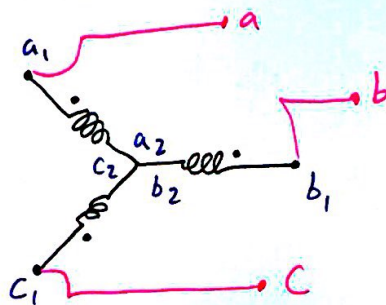
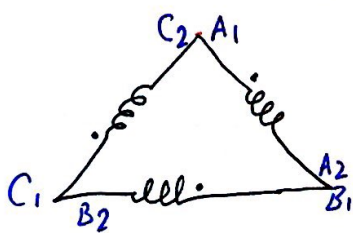
$\Rightarrow I_{relay} = 1.25 \times 1.3 = \underline{1.6 A}$ .  $\Rightarrow$  this is the settings of the Relay.



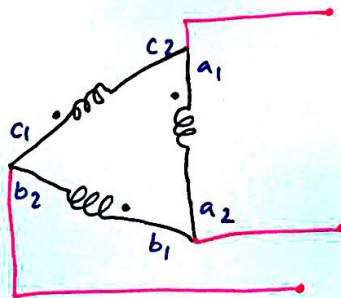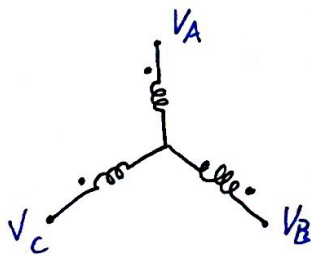$\Rightarrow$  Connection of the CT  $Y_n d 1$




Q2

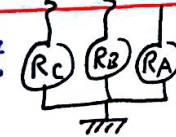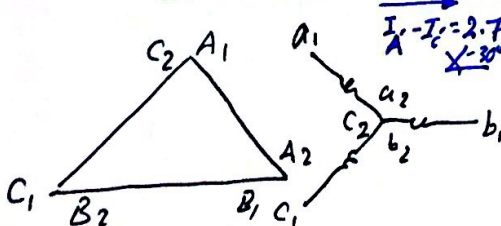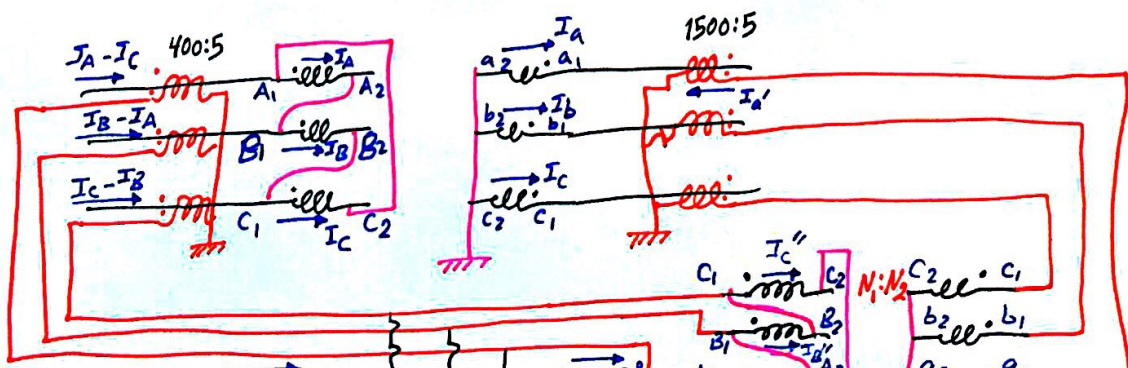

$2.7 \angle 30^\circ$

$I_A'' = \frac{2.7}{\sqrt{3}} = 1.57$

$I_{a'} = 4.37 \angle 0^\circ$

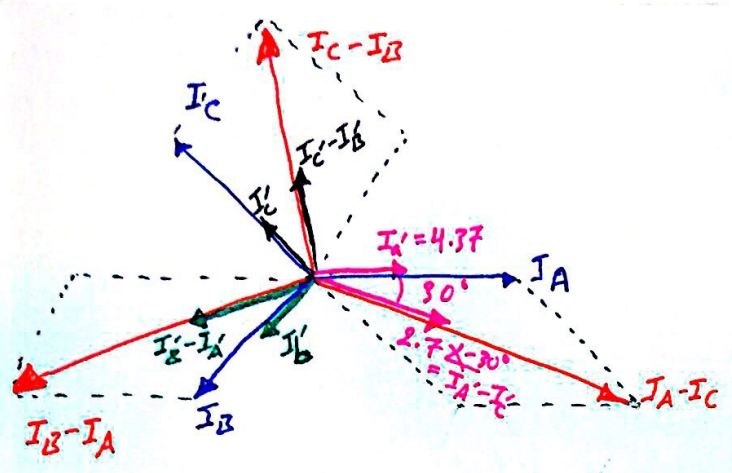


$$* I_{HFL} = \frac{25 \times 10^6}{\sqrt{3} \times 66 \times 10^3} = \underline{218.7} = |I_A - I_C|$$

$$|I_A' - I_C'| = \frac{218.7}{400/5} = \underline{2.73A}$$

$$* I_{LFL} = \frac{25 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = \underline{1312.2A} = |I_a|$$


$$|I_a'| = \frac{1312.2}{1500/5} = \underline{4.37A}$$

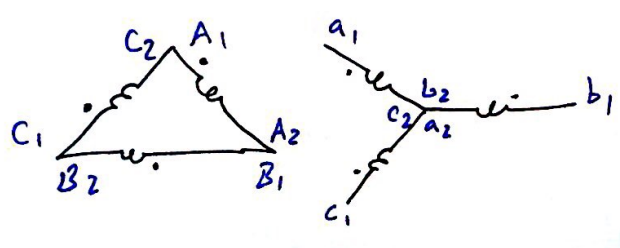for the matching transformer: ( $\Delta Y$ )



$$\Rightarrow \frac{I_a'}{I_a''} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$
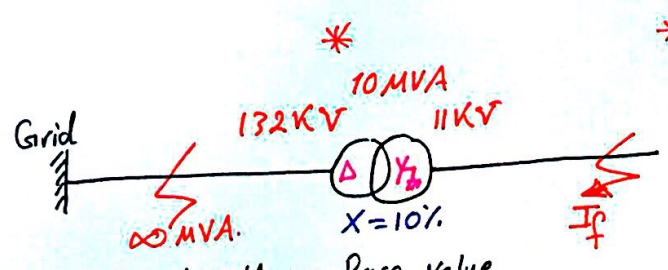
$$\frac{N_1}{N_2} = \frac{4.37}{1.57} = \underline{2.77}$$



Take 10MVA as Base value.


\* for 3-ph. fault:

$$I_b = \frac{10 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 524.86A$$

$$I_{sc} = \frac{1}{0.1} = 10 \text{ PU} = \text{MVA}_{sc} \text{ (PU)}$$

$$\Rightarrow I_{sc} = 10 \times 524.86 = \underline{5248.6A}$$

\* for L-G fault:


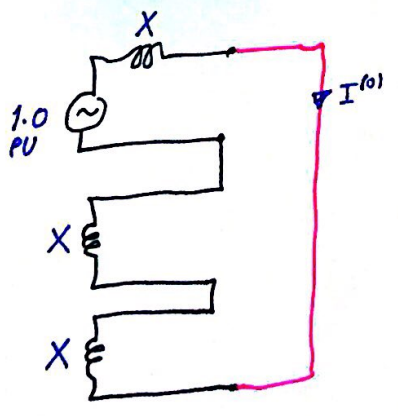


$$I_{LG} = 3I^{(0)} = 3 * \frac{1.0}{3X} = \frac{1}{X} = I_{f \text{ 3-ph.}}$$

$$I_{LG} = \underline{5248.6A}$$

\* If the system is solidly grounded & the fault occur @ the terminal of the transformer then the Line to Ground current approaches to the three phase fault current.

\* Consider 3-ph fault:

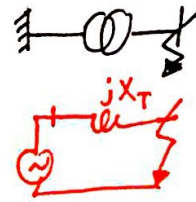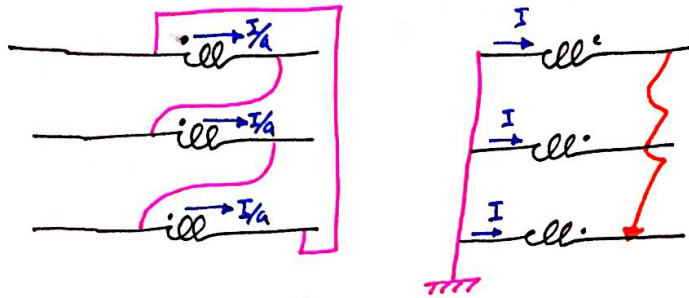


$$I_{3\phi} = \frac{1}{X_T} = I$$

$$I_{LL} = 0.866 I_{3\phi}$$


$$= \frac{\sqrt{3}}{2} I$$

$$I_{LG} = I$$

\* Consider LL fault:

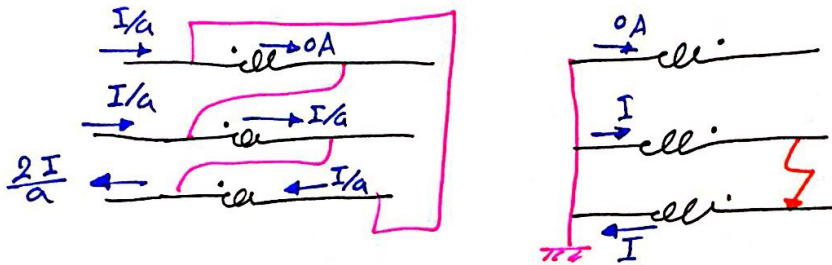

\* Consider LG fault:

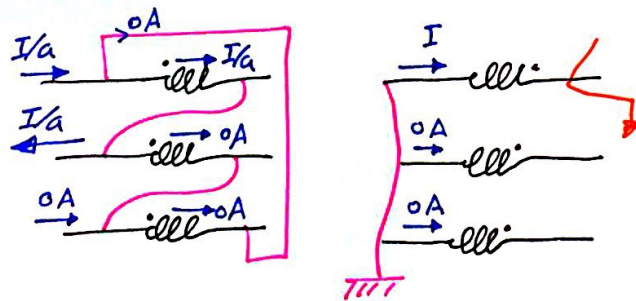

Q4

- $I_{11kV} = \frac{200 \times 10^3}{\sqrt{3} \times 11 \times 10^3} = 10.5 \text{ A}$


- $I_{0.4kV} = \frac{200 \times 10^3}{\sqrt{3} \times 400} = 288.6 \text{ A}$

for the Turns Ratio:


$$\frac{N_1}{N_2} = \frac{I_2}{I_1} = \frac{V_{1ph}}{V_{2ph}} = a = \frac{11000}{400/\sqrt{3}} = \sqrt{3} \frac{V_{LL HV}}{V_{LL LV}}$$

$$\Rightarrow \frac{N_1}{N_2} = \sqrt{3} \times \frac{11000}{400} = 47.6$$

$$I_1 = \frac{I_2}{a}$$

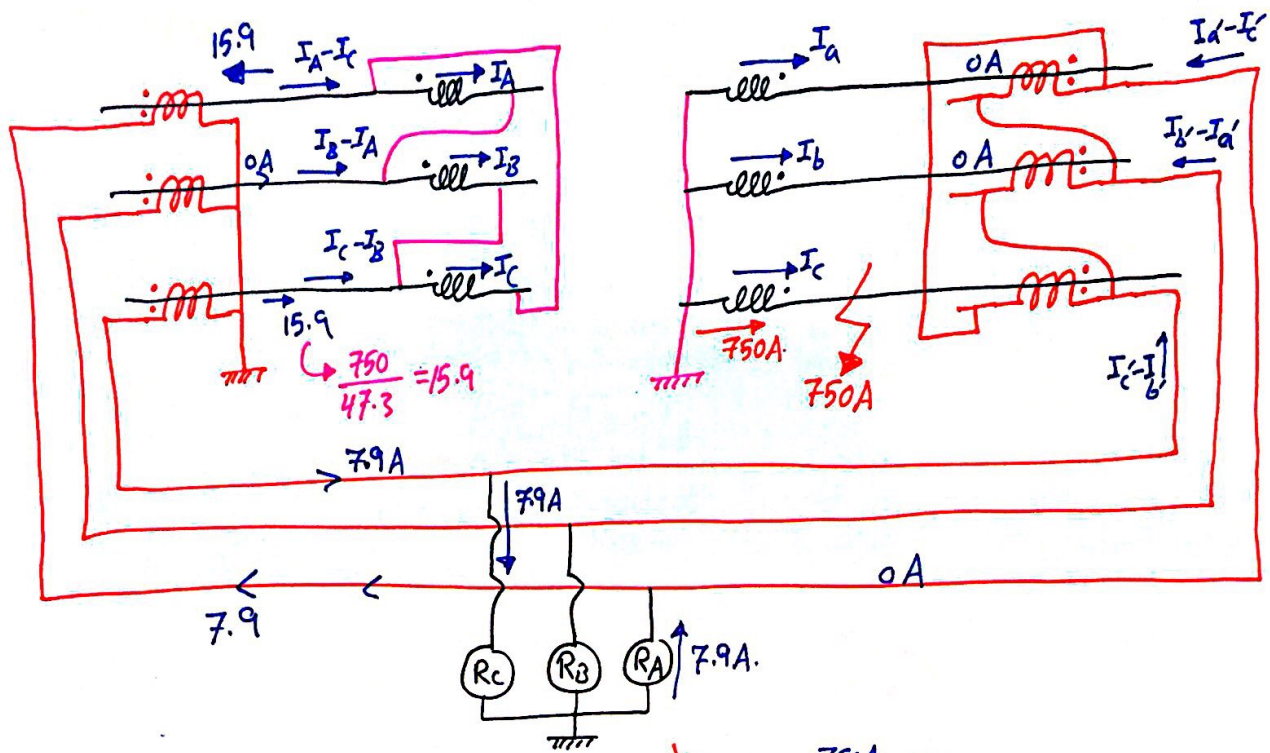


⇒ for External Fault:

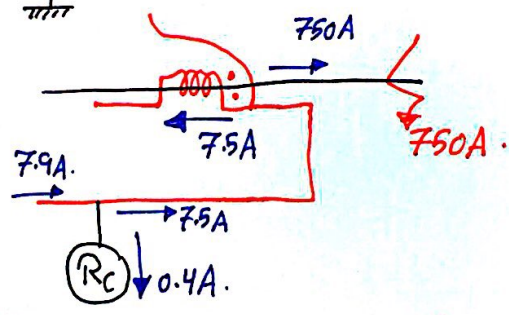

\* \* \*

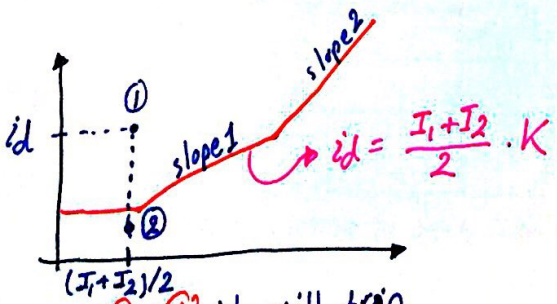**\* Differential Relay:**

• differential relay works only for internal faults, But in certain case of **very high external fault** the CT could have saturation & there would be a current pass through the relay, lead it to work, **But it will give wrong readings.**



@ (1) it will trip.  
 @ (2) No tripping.

\* the second slope to solve the problem of External Fault.

**Problem # 7**

A 115/13.2 kV Dy1 transformer rated at 25MVA has differential protection as indicated below. The transformer is connected to a radial system, with the source on the 115 kV side. The minimum operating current of the relays is 1 A. The transformer 13.2 kV winding is earthed via a resistor which is set so that the current for a single-phase fault on its secondary terminals is equal to the nominal load current. Draw the complete three-phase diagram and indicate on it the current values in all the elements for:

- (i) Find the value of the grounding resistance R.
- (ii) When a fault occurs at the middle of the winding on phase C, on the 13.2 kV side, assuming that the transformer is not loaded. For both cases indicate if there is any relay operation.

**Solution:**

**Full load conditions**

The full load conditions for the maximum load of the transformer are as follows:

$$I_{FL(13.2kV)} = \frac{25 \times 10^6}{\sqrt{3} \times 13.2 \times 10^3} = 1093.5 \text{ A}, \quad R = \frac{13.2 \times 10^3 / \sqrt{3}}{1093.46} = 6.97 \Omega$$

**Fault at the middle of 13.2 kV winding C**

Since the transformer is earthed through a resistor that limits the current for faults at the transformer 13.2 kV bushings to the rating of the winding, and since the fault is at the middle of the winding, the fault current is then equal to half the rated value as follows:


$$I_{fault} = (I_{nom(13.2kV)})/2 = 1093.47/2 = 546.7 \text{ A}$$

The primary current within the delta winding is

$$I_{prim} = I_{fault} \times \frac{(N_2/2)}{N_1}, \quad \frac{N_2}{N_1} = \frac{V_2/\sqrt{3}}{V_1}$$

$$I_{prim} = \frac{1}{\sqrt{3} \times VR} = 546.5 \times \frac{(13.2/\sqrt{3})/2}{115} = 18.1 \text{ A}$$

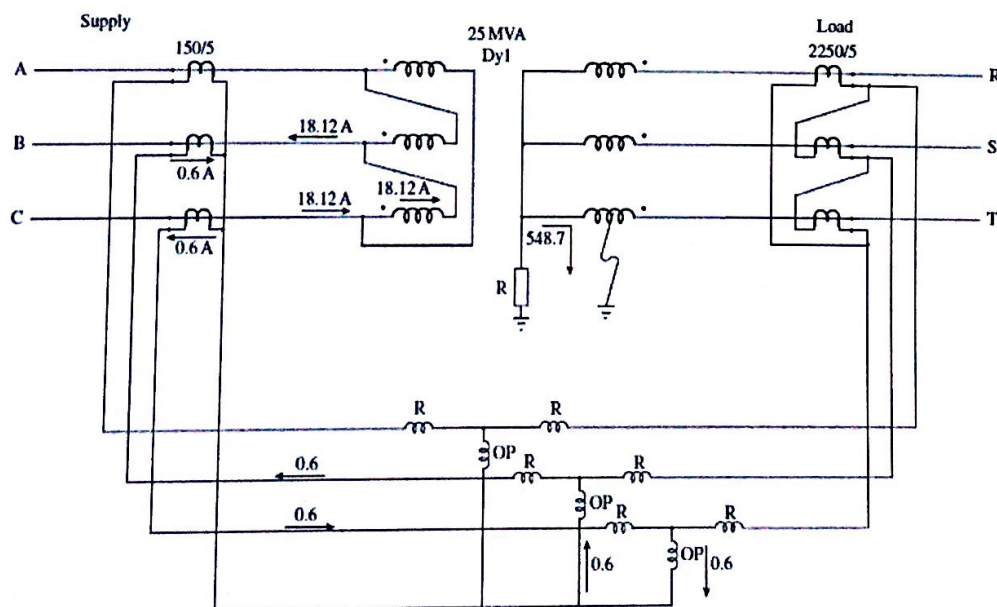The differential relays **do not operate** since the current through their operating coils is only 0.6 A, which is less than the 1A required for relay operation.




Conditions for a fault at the middle of the winding on phase C on the 13.2 kV side

**\* Problem #7:**

25 MVA  
115/13.2 KV  
(2y1)

Fig. 1

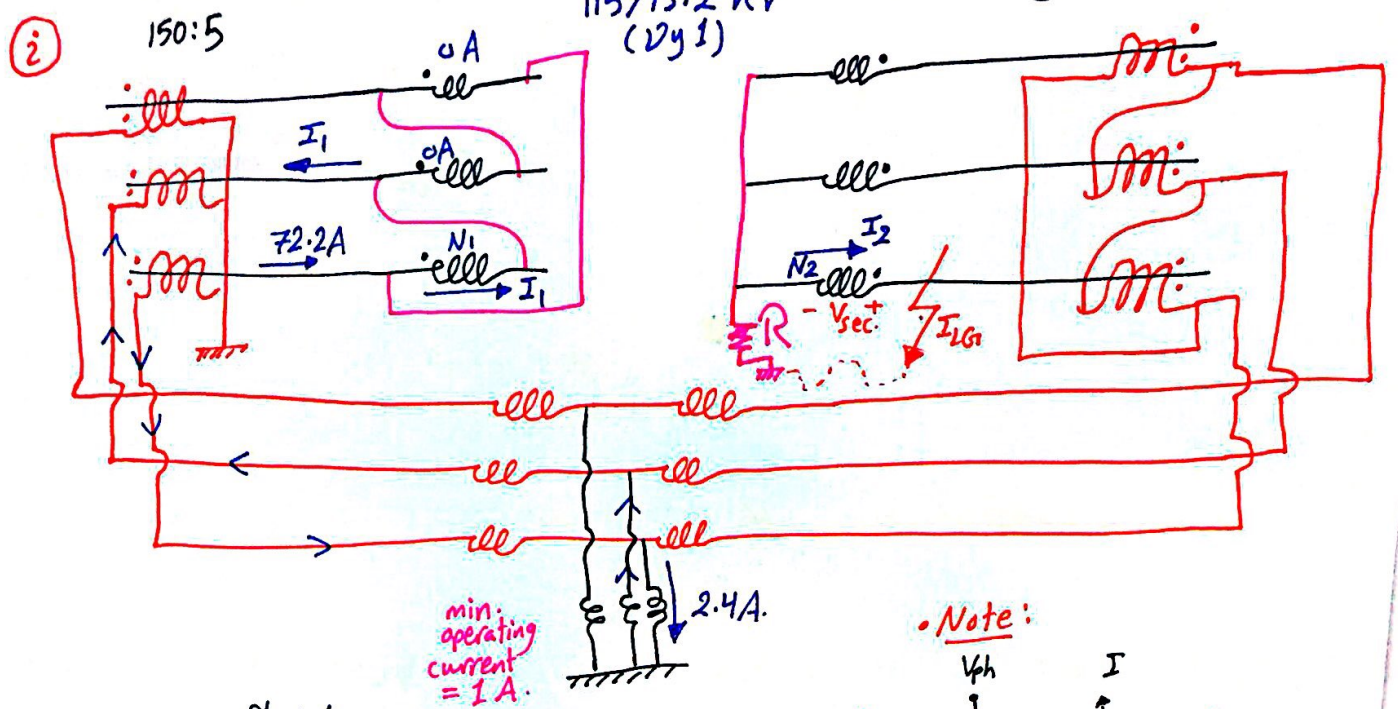


$$I_{LV \text{ rated}} = \frac{S_{\text{rated}}}{\sqrt{3} V_{L \text{ rated}}} = \frac{25 \times 10^6}{\sqrt{3} \times 13.2 \times 10^3} = 1093.5 \text{ A}$$

$$\text{so } R = \frac{V_L / \sqrt{3}}{I_{LV}} = \frac{13.2 \times 10^3 / \sqrt{3}}{1093.5} = 6.97 \approx 7 \Omega$$

\*  $R = 7 \Omega$  \*

**Note:**

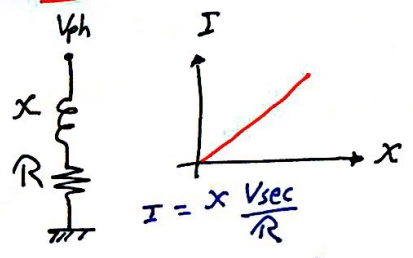

R will limit the fault current ( $R = \frac{V_{\text{sec}}}{I_{\text{rated}}}$ )

**remember:**

$$V = N \frac{dd}{dt}$$

$N \uparrow \Rightarrow V \uparrow$

**(22)** \* Consider the first case for a fault occur as shown in Fig. 1.

$$I_{HV} = \frac{25 \times 10^6}{\sqrt{3} \times 115 \times 10^3} = 125.5 \text{ A}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1} = \frac{V_{\text{ph}}}{V_{\text{ph}}} = \frac{13.2 \times 10^3 / \sqrt{3}}{115 \times 10^3} = 0.066$$

so \*  $\frac{N_1}{N_2} = 15.08$  \*

$$I_1 = 0.066 \times 1093.5 = 72.2 \text{ A}$$


\* The current in the CT:

$$I_{CT} = \frac{72.2}{150/5} = 2.4 \text{ A}$$

**CAUTION:** we used the turns ratio to find  $I_1$ , since the system is not balanced so we can't just divide by  $\sqrt{3}$ .

**Note that  $2.4 \text{ A} > 1 \text{ A}$**   
 $\therefore$  the relay will pick-up.

Continue ...

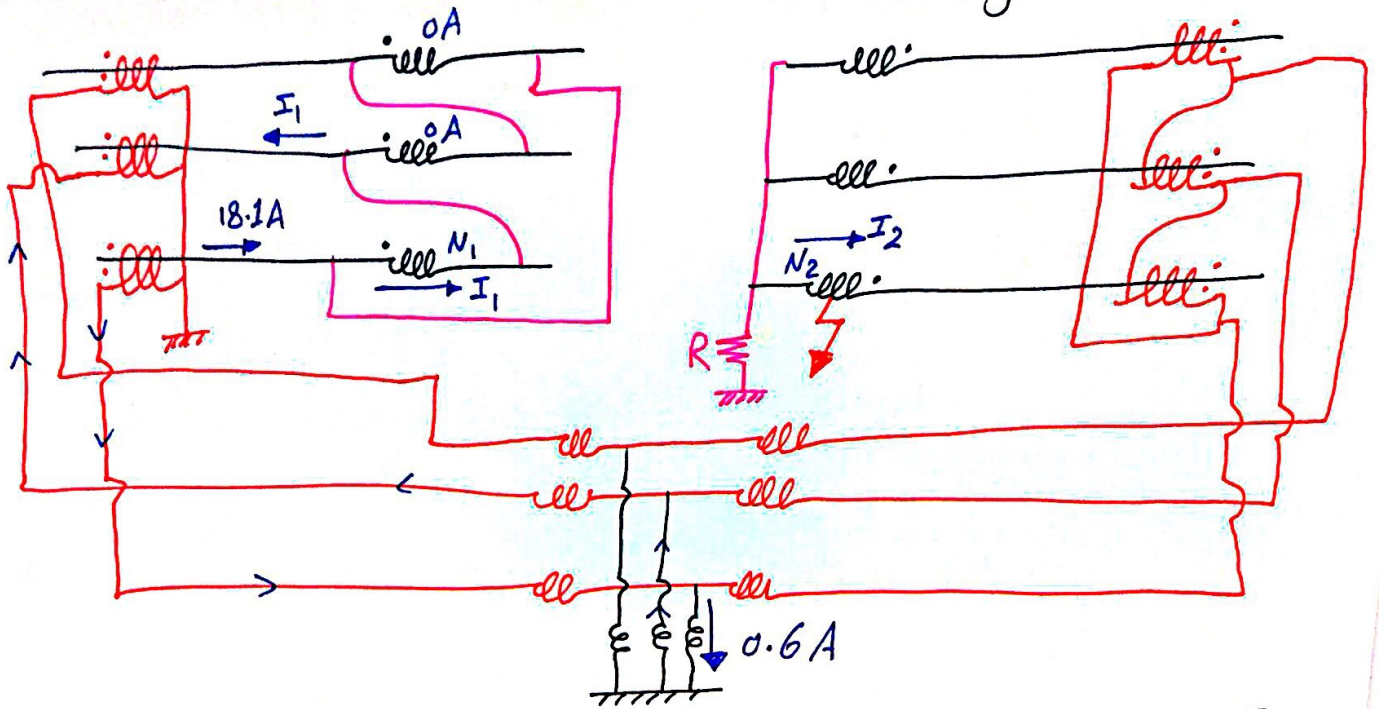

\* Consider the second Case for a fault occur as shown in Fig.2.

$$I_2 = \frac{1093.5}{2} = \underline{546.5A} \Rightarrow I_1 = \frac{N_2}{N_1} \times 546.5 = \frac{0.066}{2} \times 546.5 = \underline{18.1A}$$


\* The current in the CT:  $I_{CT} = \frac{18.1}{150} = \underline{0.6A}$ .

. Note that  $0.6A < 1A$   $\therefore$  the relay won't pick-up.

\* \* \*  
\* Now we want to find a relation between  $I_{pickup}$  & the value of  $x$ :

Consider the same exact connection in the previous figures (Fig.1 & Fig.2).

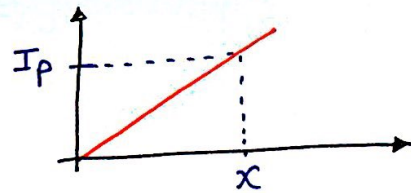$I_1 \equiv I_{sc}'$ ,  $I_2 \equiv I_{sc}''$ , Voltage on the winding  $\equiv xV_{sec}$ .



$$\Rightarrow I_{sc}'' = \frac{xV_{sec}}{R}$$

$$I_{sc}' = x \frac{N_2}{N_1} \cdot \frac{xV_{sec}}{R}$$

$$x^2 = R \frac{N_1}{N_2} \frac{I_{sc}'}{V_{sec}}$$


$$I_{pickup} \text{ (primary)} = I_p \times CTR_{\Delta}$$

$$\Rightarrow x = \sqrt{R \frac{N_1}{N_2} \frac{I_p \cdot CTR_{\Delta}}{V_{sec}}} \quad * 100% *$$

\* Gives the percentage of the unprotected windings.

• you can use this relation to find  $x$  @ 1A pick up for previous problem.
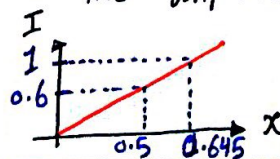
$$1A \Rightarrow (30A)_{primary} \Rightarrow \underline{x = 0.645}$$



# Power Systems Analysis II

---

---

Second Semester  
2018

---

---

Dr. Eyad Feilat  
e. feilat@ju.edu.jo

Notebook:

By. Mohammad  
Abu Hashya.

---

---






\* Consider Inter-Turn Fault in Transformer:

"consider No-load Case"


$$I_f = \frac{5}{1 \times 10^{-3}} = 5000 \text{ A.}$$

$$P_{\text{dissipated}} = I_f^2 R_f = (5000)^2 * 1 \times 10^{-3} = 25 \text{ kW.}$$
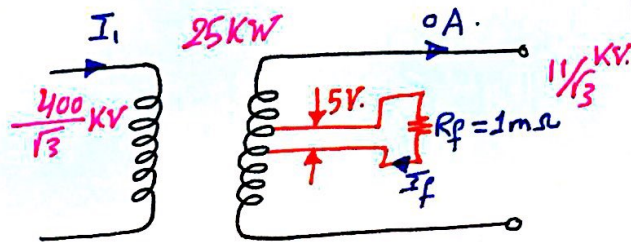
$$V_1 I_1 = 25 \text{ K} \Rightarrow I_1 = \frac{25 \times 10^3}{\frac{400}{\sqrt{3}} \times 10^3} = 0.11 \text{ A.}$$




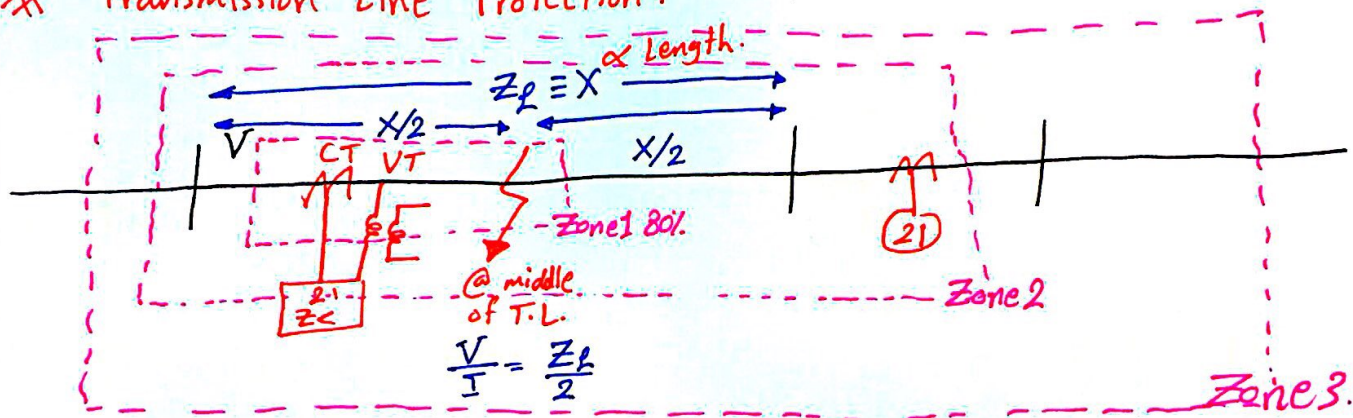\* Transmission Line Protection: "Distance Protection"





\* Communications between Relays could be done using:

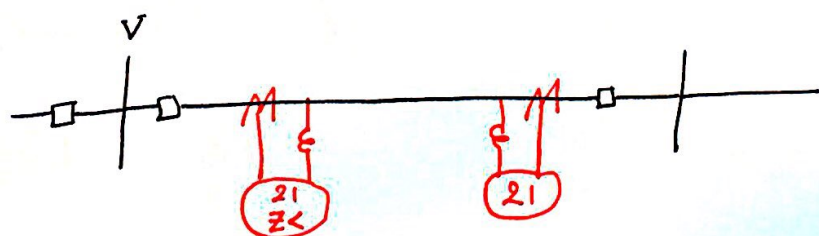- Conductor itself.
- fiber optic.
- Micro waves.




$Z_{\text{seen}} < Z_{\text{setting}}$        $Z = \frac{V}{I}$  ; apparent impedance.



$$Z = R + jX \quad |Z|^2 = R^2 + X^2$$

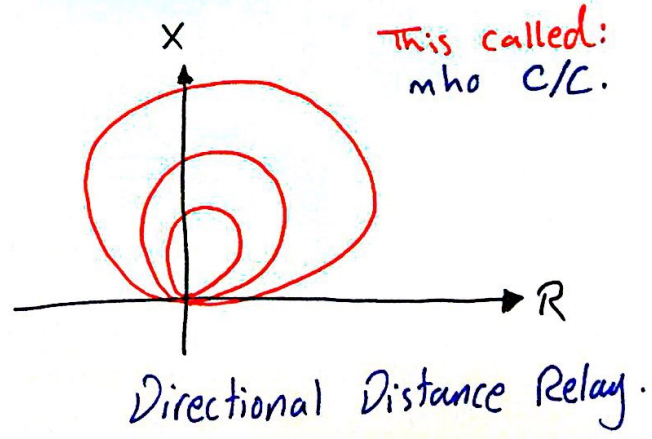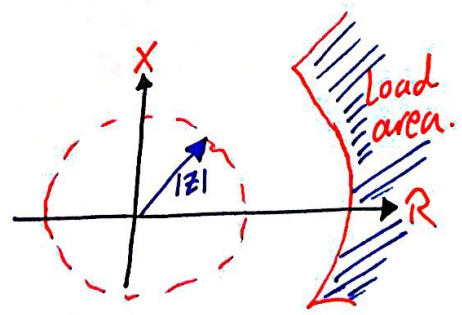

\* Consider the following system:

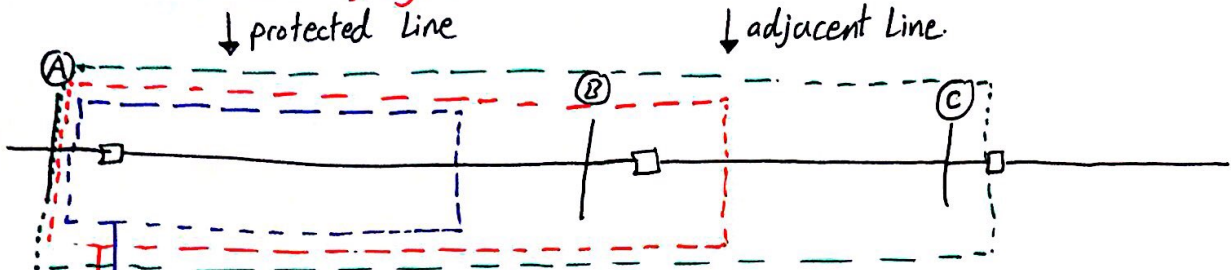

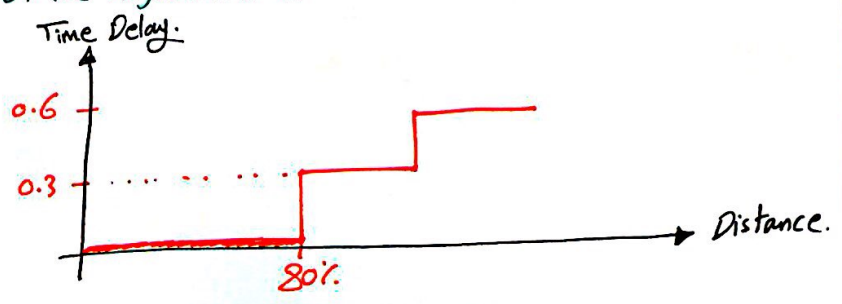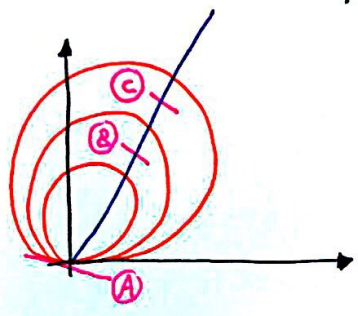
- Zone 1 (80-90)% of the protected line  $\Rightarrow$  "Under reach Zone".
- Zone 2 (120)% of the protected line  $\Rightarrow$  "over reach".
- Zone 3 (100)% of the protected line + (120)% of the adjacent line.  $\Rightarrow$  "over reach".



• Define  $Z_L \equiv$  Line impedance.  $= \frac{V}{I}$


$$Z_{\text{seen by the relay}} = \frac{V/VTR}{I/CTR} = Z_L \times \frac{CTR}{VTR}$$

\* Control Circuit:

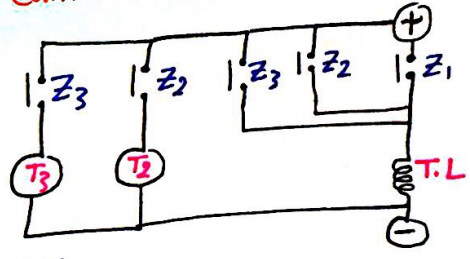


$Z_{r1} = 0.8 Z_{AB}$  ;  $Z_{r2} = 1.2 Z_{AB}$  ;  $Z_{r3} = Z_{AB} + 1.2 Z_{BC}$

Example:

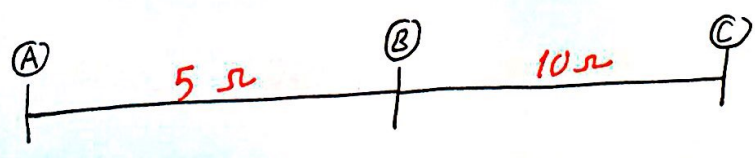

for A:  
 $Z_{r1} = 4 \Omega$   
 $Z_{r2} = 6 \Omega$   
 $Z_{r3} = 17 \Omega$

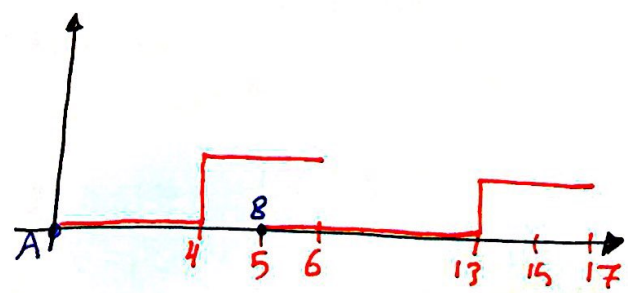for B:  
 $Z_{r1} = 8 \Omega$   
 $Z_{r2} = 12 \Omega$



\*

\*

\*

**Question # 1:**

Consider the system of Fig. Q1 where the values given are impedance in per-unit. Draw the per-phase equivalent circuit and find the impedance as seen by the impedance relay looking into the circuit for the following cases:

- a. normal load conditions,  $Z_n$
- b. 3-phase fault at  $F_1$ ,  $Z_{F1}$
- c. 3-phase fault at  $F_2$ ,  $Z_{F2}$

Plot the impedance as seen by the impedance relay on the R-X diagram.

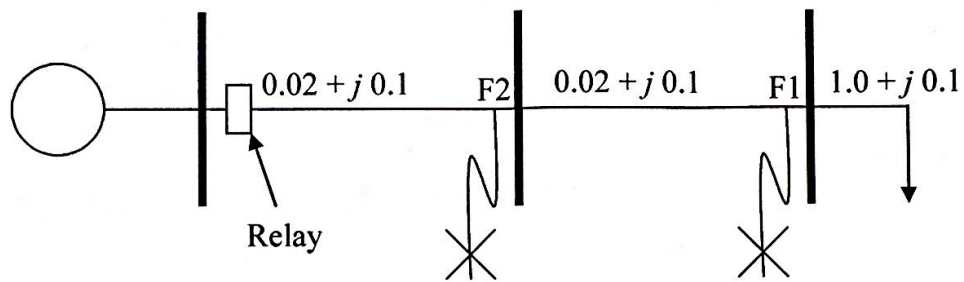


Fig. Q1

**Solution:**



The per-phase circuit is shown.

The desired impedance is  $Z = \frac{V}{I}$

(a) Under normal load,  $Z_n = \frac{V}{I} = 1.04 + j0.3 pu$

(b) For a fault at  $F_1$ ,  $Z_{F1} = \frac{V}{I} = 0.04 + j0.2 pu$

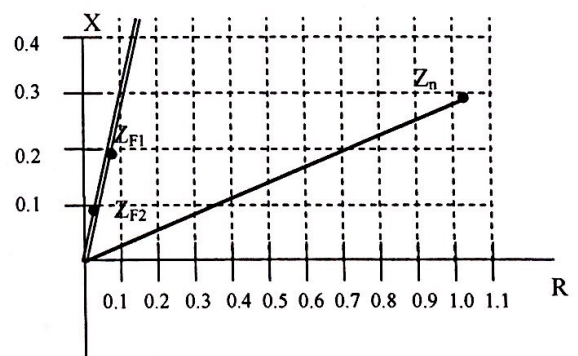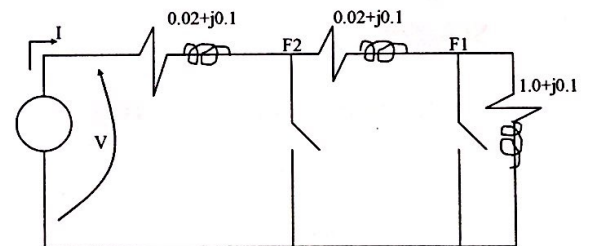(c) For a fault at  $F_2$ ,  $Z_{F2} = \frac{V}{I} = 0.02 + j0.1 pu$



### Question # 2:

Consider a 132 kV transmission system as shown in Fig. Q2. The positive sequence impedances of the lines 1-2 and 2-3 are  $Z_{12} = 3 + j 40 \Omega$  and  $Z_{23} = 7 + j 30 \Omega$  respectively. The maximum peak load supplied by the line 1-2 is 110 MVA with a lagging power factor of 0.8. Assume a L-L fault of  $I_f = 500$  A occurs midway of the line 1-2 and line spacing of 3.5 m is equal to arc length. Design a distance protection system using Mho relays by determining the following:

- Maximum load current
- Suitable CT ratio. Secondary standard 5 A.
- Suitable VT ratio. Secondary standard 67 V.
- Line impedance measured by the relay.
- Load impedance measured by the relay.
- Zones 1, 2, and 3 setting of relay R12.
- Value of arc resistance at fault point in  $\Omega$ .
- Show graphically, whether or not relay will clear the fault instantaneously.

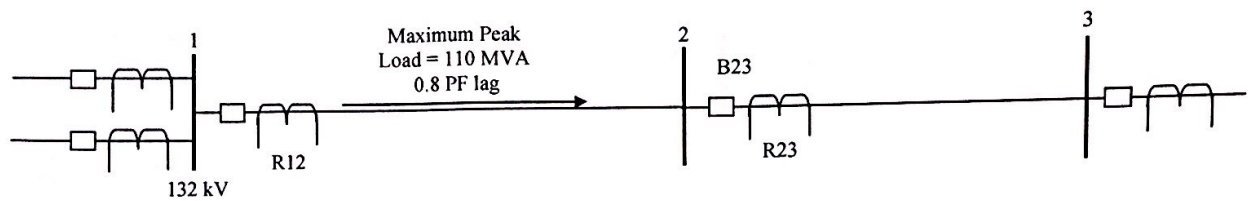


Fig. Q2

### Solution:

- a. Maximum load current

$$I_{L_{\max}} = \frac{S_L}{\sqrt{3}V_{LL}} = \frac{110 \times 10^6}{\sqrt{3}132 \times 10^3} = 481.13 \text{ A}$$

- b. CT ratio

$$\text{Choose } CTR = \frac{500}{5} = 100 : 1$$

- c. VT ratio

$$V_{ph} = \frac{V_{LL}}{\sqrt{3}} = \frac{132 \times 10^3}{\sqrt{3}} = 76210.2 \text{ V} = 76.21 \text{ kV}$$

$$\text{Choose } VTR = \frac{76210}{67} = 1137.46 : 1$$

- d. Line impedance measured by the relay

$$Z_{line-sec\ ondary} = \frac{V_p}{I_p} \times \frac{CTR}{VTR} = Z_{line} \times \frac{CTR}{VTR}$$

$$Z_{line-sec\ ondary} = Z_{line} \times \frac{100}{1137.46} = Z_{line} \times 0.0879$$

Thus the impedances of the two lines as seen by the relay R12 are approximately

$$\text{Line 1-2} \quad Z_{12} = (3 + j40) \times 0.0879 = 0.26 + j3.52 \Omega$$

$$\text{Line 2-3} \quad Z_{23} = (7 + j30) \times 0.0879 = 0.615 + j2.64 \Omega$$

e. Load impedance seen by the relay.  
The maximum load impedance with 0.9 power factor lagging is

$$Z_{load} = \frac{V_{ph}}{I_{L,max}} \angle \cos^{-1}(0.8) = \frac{76.21 \times 10^3}{481.13} \angle 36.9^\circ = \frac{76.21 \times 10^3}{481.13} (0.8 + j0.6)$$

$$= 158.4 \angle 36.9^\circ \Omega = 126.7 + j95.1 \Omega$$

$$Z'_{load} = Z_{load-primary} \times \frac{CTR}{VTR} = Z_{load-primary} \times 0.0879$$

$$Z'_{load} = 158.4 \angle 36.9^\circ \Omega \times 0.0879 = 13.9 \angle 36.9^\circ \Omega$$

$$= 126.7 + j95.1 \Omega \times \frac{40}{1189.1} = 11.1 + j8.4 \Omega$$

$$= 13.9 \angle 37.1^\circ \Omega$$

f. Zones 1, 2, and 3 setting of relay R12.

The zone 1 setting of the relay R12 must **under reach** the line 1-2, so that the setting should be  $Z_{r1} = 0.8 \times Z'_{12} = 0.8 \times (0.26 + j3.52) \Omega = 0.21 + j2.82 \Omega = 2.83 \angle 85.7^\circ \Omega$

The zone 2 setting should reach past terminal 2 of the line 1-2. Zone 2 is usually set at about 1.2x the length of the line being protected.

Zone 2 for R12 is therefore set at

$$Z_{r2} = 1.2 \times Z'_{12} = 1.2 \times (0.26 + j3.52) = 0.31 + j4.22 \Omega = 4.2 \angle 85.8^\circ \Omega$$

The zone 3 setting should reach beyond the longest line connected to bus 2. Thus the zone-3 setting must be

$$Z_{r3} = Z'_{12} + 1.2 \times Z'_{23}$$

$$= (0.26 + j3.52) + 1.2 \times (0.615 + j2.64) = 1.0 + j6.69 \Omega = 6.76 \angle 81.5^\circ \Omega$$

g. Value of arc resistance at fault point in  $\Omega$ .

The empirical fault arc resistance is given by:

$$R_{arc} = \frac{2.9 \times 10^4 L}{I^{1.4}}$$

Where

$L$  is the length of arc (m) in still air

$I$  is the fault current in A.

$$R_{arc} = \frac{2.9 \times 10^4 \times 3.5}{500^{1.4}} = \frac{101500}{6005.6} = 16.9 \Omega$$

$$R'_{arc} = 16.9 \times 0.0879 = 1.486 \Omega$$



Show graphically, whether or not relay will clear the fault instantaneously.

The total impedance seen by the relay up to the fault point is  $Z'_f$

$$Z'_f = 0.5 \times Z'_{12} + R'_{arc} = 0.5 \times (0.26 + j3.52) + 1.486$$

$$Z'_f = 0.13 + 1.486 + j1.76 = 1.62 + j1.76 \Omega = 2.39 \angle 47.4^\circ \Omega$$

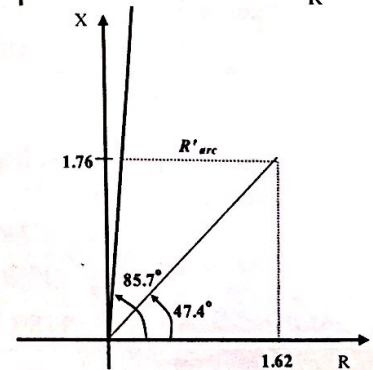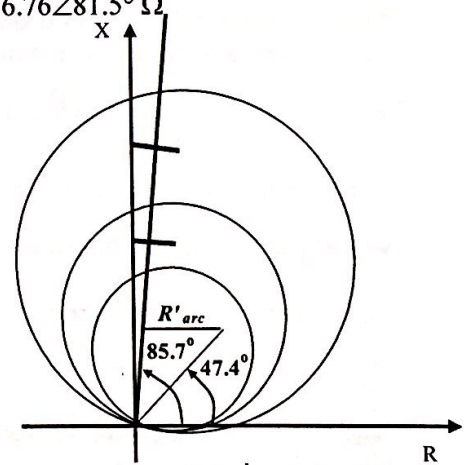
The fault lies in the zone 1, so it will be cleared


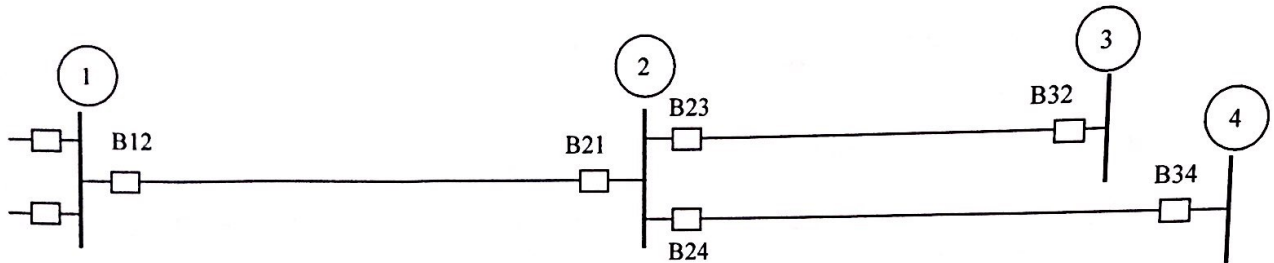
### Question # 3:

Consider the portion of a 138 kV transmission system shown below. Lines 1-2, 2-3 and 2-4 are respectively 64, 64, and 96 km long. The positive sequence impedance of the transmission lines is  $(0.05 + j 0.5) \Omega/\text{km}$ . The maximum load carried by line 1-2 under emergency condition is 50 MVA.

Design a 3-zone step distance relaying system to the extent of determining for R12 the zone setting which are the impedance values in terms of CT and VT secondary quantities. The zone settings give points on the R-X plane through which the zone circles of the relay characteristics must pass.



### Solution:

The positive sequence impedances of the three lines are:

$$\begin{aligned} \text{Line 1-2} \quad Z_{12} &= 3.2 + j 32.0 \Omega \\ \text{Line 2-3} \quad Z_{23} &= 3.2 + j 32.0 \Omega \\ \text{Line 2-4} \quad Z_{24} &= 4.8 + j 48.0 \Omega \end{aligned}$$

Since distance relays depend on the ratio of voltage to current ( $Z=V/I$ ), both a CT and VT are needed for each phase. The maximum load current is

$$I_{L \max} = \frac{50 \times 10^6}{\sqrt{3} \times 138 \times 10^3} = 209.2 \text{ A}$$

Then, select a CT ratio of  $\text{CTR} = \frac{200}{5} = 40$  which will produce about 5 A in the secondary winding under maximum loading conditions ( $209.2/200/5=5.23 \text{ A}$ ).

The system voltage to neutral is:

$$V_{ph} = \frac{138 \times 10^3}{\sqrt{3}} = 79.67 \text{ kV}$$

The industry standard for VT secondary voltage is 67 V for line-to-neutral voltages. Consequently, select a VT ratio (VTR) of

$$VTR = \frac{79.67 \times 10^3}{67} = \frac{1189.1}{1}$$

Denoting primary voltage of VT at bus 1 as  $V_p$  and the primary current of the CT as  $I_p$ , then the impedance measured by the relay is given by

$$Z_{\text{line-secondary}} = \frac{V_p}{I_p} \times \frac{\text{CTR}}{\text{VTR}} = Z_{\text{line}} \times \frac{\text{CTR}}{\text{VTR}}$$

$$Z_{\text{line-secondary}} = \frac{V_p/1189.1}{I_p/40} = \frac{V_p}{I_p} \times \frac{40}{1189.1} = Z_{\text{line}} \times 0.0336$$

Thus the impedances of the three lines as seen by the relay R12 are approximately


$$\begin{aligned} \text{Line 1-2} & \quad Z_{12} = 0.11 + j1.1 \, \Omega \\ \text{Line 2-3} & \quad Z_{23} = 0.11 + j1.1 \, \Omega \\ \text{Line 2-4} & \quad Z_{24} = 0.16 + j1.6 \, \Omega \end{aligned}$$

The maximum load impedance assuming a power factor of 0.8 lagging is

$$\begin{aligned} Z_{load} &= \frac{V_{ph}}{I_{Lmax}} \angle \cos^{-1}(0.8) = \frac{79.67 \times 10^3}{209.2} \angle 36.9^\circ = \frac{79.67 \times 10^3}{209.2} (0.8 + j0.6) \\ &= 380.83 \angle 36.9^\circ \, \Omega = 304.6 + j228.5 \, \Omega \end{aligned}$$

The load impedance seen by the relay is
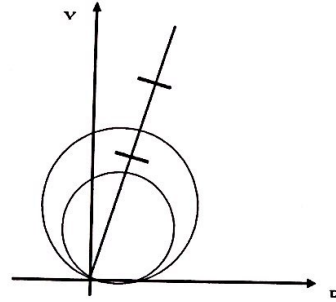
$$\begin{aligned} Z_{load-secondary} &= Z_{load-primary} \times \frac{CTR}{VTR} \\ Z_{load-secondary} &= (304.6 + j228.5) \times \frac{40}{1189.1} = 10.2 + j7.7 \, \Omega \end{aligned}$$



The zone 1 setting of the relay R12 must **under reach** the line 1-2, so that the setting should be

$$Z_{r-setting-zone1} = 0.8 \times Z_{line-secondary} = 0.8 \times (0.11 + j1.1) = 0.088 + j0.88 \, \Omega$$


The zone 2 setting should reach past terminal 2 of the line 1-2. Zone 2 is usually set at about  $1.2 \times$  the length of the line being protected.


Zone 2 for R12 is therefore set at

$$Z_{r-setting-zone2} = 1.2 \times Z_{line-secondary} = 1.2 \times (0.11 + j1.1) = 0.132 + j1.32 \, \Omega$$


The zone 3 setting should reach beyond the longest line connected to bus 2. Thus the zone-3 setting must be
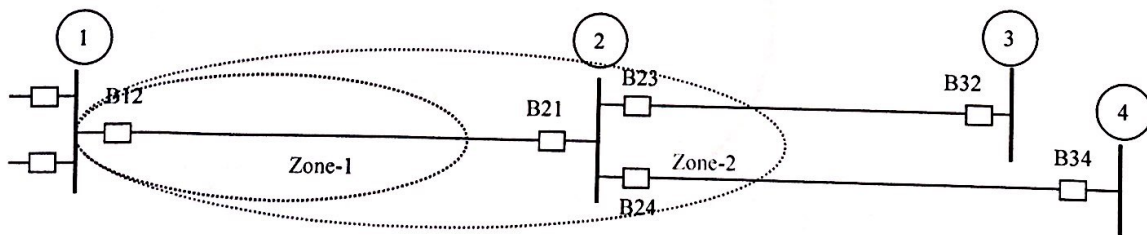
$$\begin{aligned} Z_{r-setting-zone3} &= Z'_{12} + 1.2 \times Z_{longest-line-secondary} \\ &= (0.11 + j1.1) + 1.2 \times (0.16 + j1.6) = 0.302 + j3.02 \, \Omega \end{aligned}$$




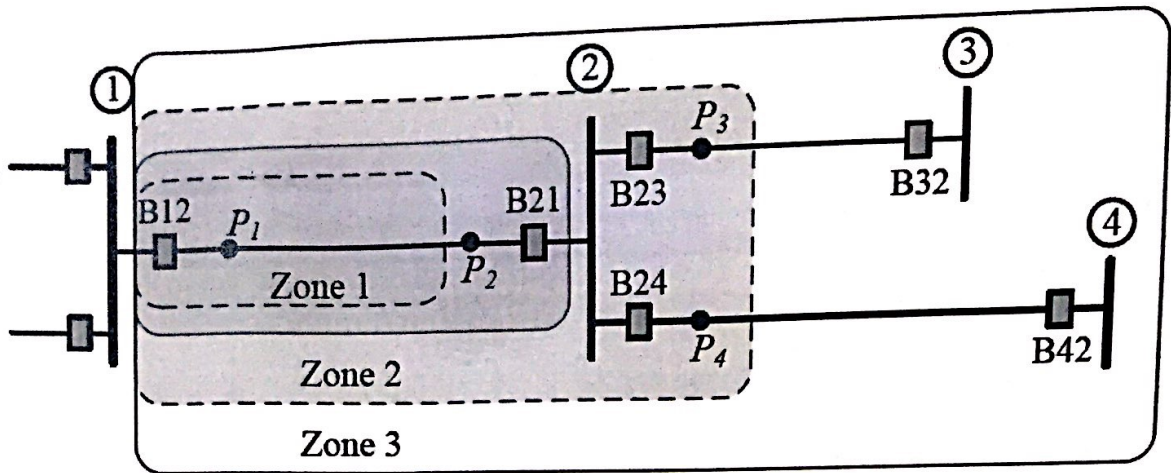

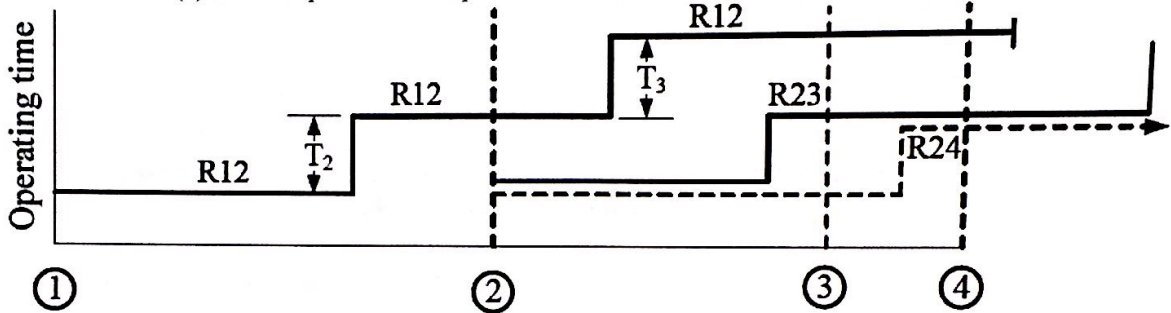(a) Zone of protection of protection of Distance (or impedance) relays.



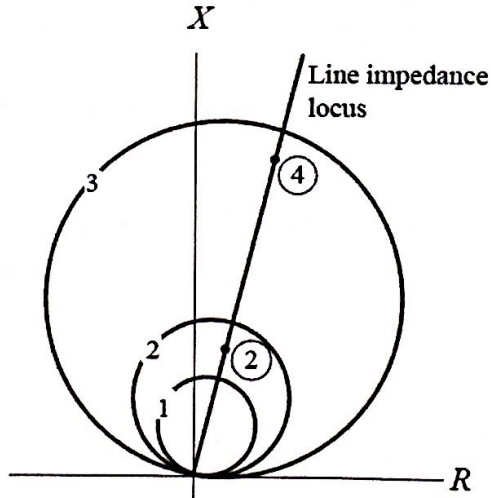(b) Time delay and operating time for R12, R23 and R24





**Question # 4**

A 345 kV transmission network is protected by distance protection with Mho characteristics as shown in Fig. Q4. The CT and VT ratios of B12 are  $CTR=1500:5$  and  $VTR=3000:1$ , respectively. The line data for the system are given below. The maximum load carried by line 1-2 under emergency condition is 1500 A at 0.95 PF lagging.

Line	Positive Sequence Impedance $Z_{ij}$	Line	Positive Sequence Impedance
1-2	$8 + j50 \Omega$	2-4	$5.3 + j33 \Omega$
2-3	$8 + j50 \Omega$	3-1	$3 + j27 \Omega$

Design a a 3-zone step distance protection system using Mho relays to the extent of determining for B12 the zone setting which are the impedance values by determining the following:

a.	impedance measured by the relay $Z'_{ij}$ for lines 1-2, 2-3, 2-4 and 3-1	$Z'_{12} = 0.8 + j5 \Omega$ $Z'_{23} = 0.8 + j5 \Omega$ $Z'_{24} = 0.53 + j3.3 \Omega$ $Z'_{31} = 0.3 + j5 \Omega$
b.	impedance settings of B12 for Zones 1, 2, and 3, $Z_{r1}$ , $Z_{r2}$ and $Z_{r3}$	$Z_{r1} = 0.64 + j4 = 4.05 \angle 80.9^\circ \Omega$ $Z_{r2} = 0.96 + j6 = 6.08 \angle 80.9^\circ \Omega$ $Z_{r3} = 1.55 + j8.96 = 9.07 \angle 80.9^\circ \Omega$
c.	the load equivalent impedance in Ohm	$Z_L = 132.8 \angle 18.2^\circ \Omega$
d.	the load equivalent impedance as seen by the distance relay	$Z_{L-relay} = 13.28 \angle 18.2^\circ \Omega$
e.	Will any of the relays trip during this condition?	Yes / <u>NO</u>

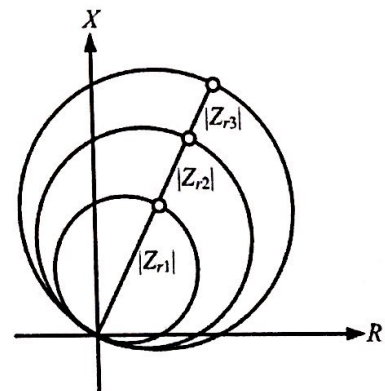
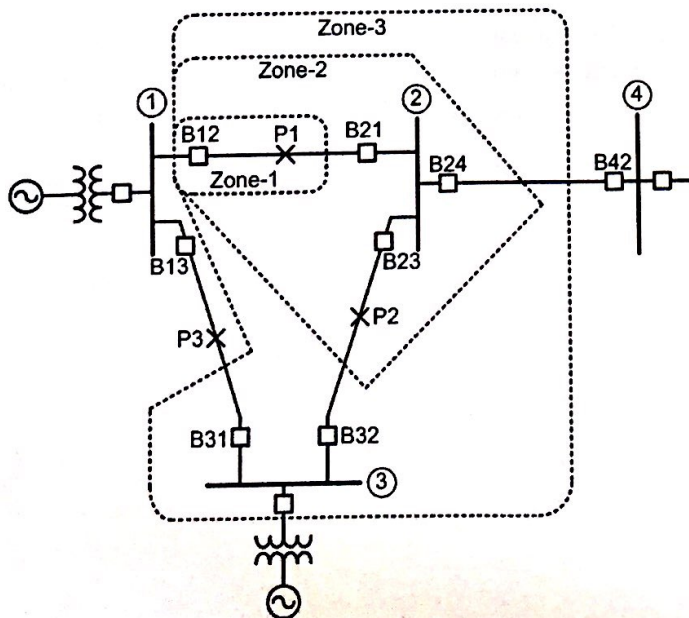


Fig.Q4a. Protection of a loop system using distance protection.

Fig.Q4b. Mho relay characteristics for the three zones

**Solution:**

Using the CT ratio of 1500:5 and PT ratio of 3000:1 at B12, the impedance seen by B12 is:

$$Z = \frac{V_{1(L-N)}}{I_{12}} \Omega$$

Using the CT and PT ratios mentioned above we have

$$Z' = \frac{V_{1(L-N)} / \left( \frac{3000}{1} \right)}{I_{12} / \left( \frac{1500}{5} \right)} = \frac{Z}{10} \Omega$$

Now we set Zone-1 of B12 relay for 80% reach, i.e., 80% of line 1-2 (secondary) impedance. Therefore

$$Z_{r1} = 0.80 \times \frac{8 + j50}{10} = 0.64 + j4 = 4.05 \angle 80.9^\circ \Omega$$

The setting for Zone-2 for B12 relay, with a reach of 120%, is

$$Z_{r2} = 1.2 \times \frac{8 + j50}{10} = 0.96 + j6 = 6.08 \angle 80.9^\circ \Omega$$

From Table Q2, we see that line 2-4 has a larger impedance than line 2-3. Therefore we set B12 for Zone-3 as 100% of line 1-2 and 120% of line 2-4. Therefore

$$Z_{r3} = 1 \times \frac{8 + j50}{10} + 1.2 \times \frac{8 + j50}{10} = 1.55 + j8.96 = 9.07 \angle 80.9^\circ \Omega$$


Suppose now the bus voltage at Bus-1 is 345 kV and the maximum current for an emergency loading condition is 1500 A. Then we have

$$Z' = \frac{Z}{10} = \frac{1}{10} \times \frac{345 \times 10^3 / \sqrt{3}}{1500 \angle -18.2^\circ} = 13.28 \angle 18.2^\circ \Omega$$



Since this impedance exceeds the Zone-3 trip setting, the impedance during the emergency loading condition is outside the trip settings of any of the zones. Therefore none of the relays will trip. Moreover, the impedance during normal loading condition will be even less and hence it will be further away from the trip regions.

# \* Tutorial #6 :

Q1

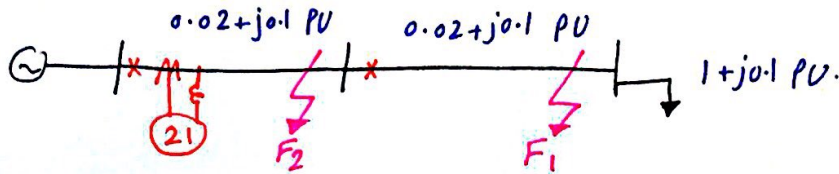


The equivalent circuit:

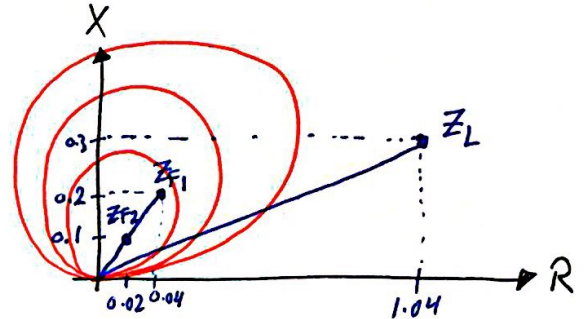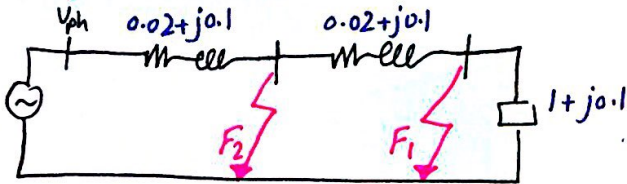

- a)  $Z_{\text{apparent}} = \frac{V}{I} = 0.02 + j0.1 + 0.02 + j0.1 + 1 + j0.1 = 1.04 + j0.3 \text{ pu.}$
- b)  $Z_{F1} = 0.02 + j0.1 + 0.02 + j0.1 = 0.04 + j0.2 \text{ pu.}$
- c)  $Z_{F2} = 0.02 + j0.1 \text{ pu.}$

Q2

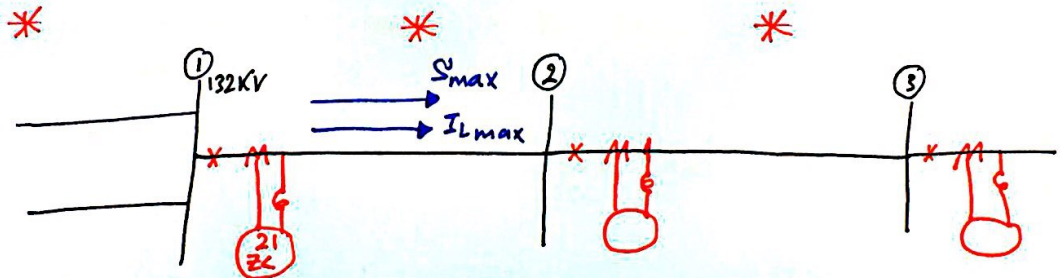

Given:  $Z_{12}^+ = 3 + j40 \Omega$ ,  $Z_{23}^+ = 7 + j30 \Omega$ ,  $S_{L\text{max}} = 110 \text{ MVA}$ ,  $\text{PF} = 0.8 \text{ lag.}$ ,  $I_{F2} = 500 \text{ A.}$

- a)  $|I_{L\text{max}}| = \frac{110 \times 10^6}{\sqrt{3} \times 132 \times 10^3} = 481.1 \text{ A.}$
- b) Choose  $\text{CTR} = 500/5$ .
- c)  $\text{VTR} = \frac{132 \times 10^3 / \sqrt{3}}{5} = 1137.47$
- d)  $Z_{\text{relay}} = \frac{V}{I} \times \frac{\text{CTR}}{\text{VTR}} = Z_{\text{apparent}} \times \frac{\text{CTR}}{\text{VTR}}$   
 $\Rightarrow Z_{\text{relay}} = \frac{500/5}{1137.47} \times Z_2 = 0.0879 \times Z_2$
- $Z_{12}^{\text{sec}} = Z_{12}^{\text{prim}} \times 0.0879 = (3 + j40) \times 0.0879 = 0.26 + j3.52 \Omega$
- $Z_{23}^{\text{sec}} = Z_{23}^{\text{prim}} \times 0.0879 = (7 + j30) \times 0.0879 = 0.615 + j2.64 \Omega$
- e)  $Z_L = \frac{V}{I_{L\text{max}}} = \frac{132 \times 10^3 / \sqrt{3}}{481.1 \angle -26.9^\circ} = 126.7 + j95.1 = 158.4 \angle 36.9^\circ \Omega$



Continue ...

f) For the Zones:

Zone 1: 80% of protected Line ( $Z_{12}$ ) =  $0.8 \times Z_{12}$

Zone 2: 120% of protected Line ( $Z_{12}$ ) =  $1.2 \times Z_{12}$

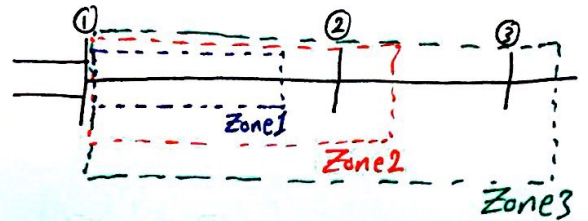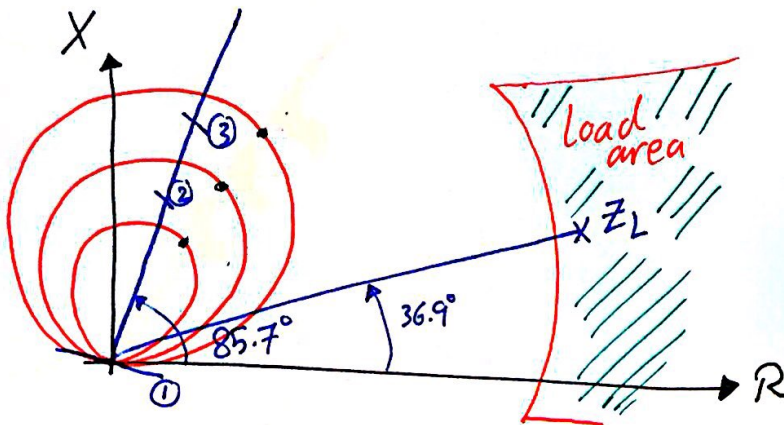Zone 3: 100% of protected line ( $Z_{12}$ ) + 120% of adjacent line ( $Z_{23}$ ) =  $Z_{12} + 1.2 Z_{23}$



Zone 3 should NOT ENCROACH the load area.

$$Z_{r1} = 0.8 Z'_{12} = 0.8 \times (0.26 + j3.52) = 0.21 + j2.82 = 2.83 \angle 85.7^\circ \Omega$$

$$Z_{r2} = 1.2 Z'_{12} = 1.2 \times (0.26 + j3.52) = 4.2 \angle 85.7^\circ \Omega$$


$$Z_{r3} = Z'_{12} + 1.2 Z'_{23} = (0.26 + j3.52) + 1.2 \times (0.615 + j2.64) = 1 + j6.7 = 6.76 \angle 81.5^\circ \Omega$$

g)  $R_{arc} = \frac{2.9 \times 10^4 L}{I_f^{1.4}} \Rightarrow$  would be given in the Exam.  
 @ primary side.

$$R_{arc \text{ prim.}} = \frac{2.9 \times 10^4 \times 3.5}{(500)^{1.4}} = 16.9 \Omega$$


$$\Rightarrow R_{arc \text{ sec.}} = R_{arc} = 16.9 \times 0.0879 = 1.49 \Omega$$
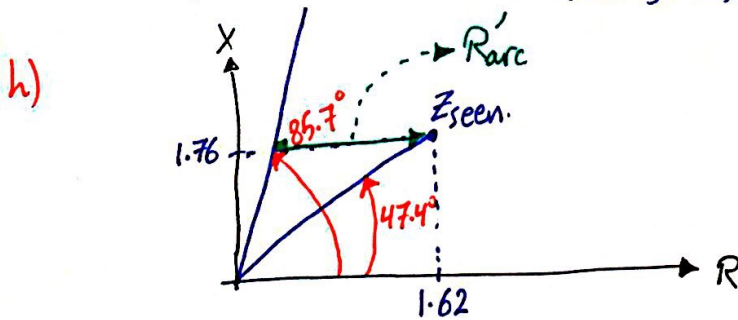
$$Z_{seen} = \frac{1}{2} Z'_{12} + R_{arc} = 0.5 \times (0.26 + j3.52) + 1.49 = 2.4 \angle 47.4^\circ \Omega$$



Since the fault occur in Zone 1, the fault will be cleared.

Q3

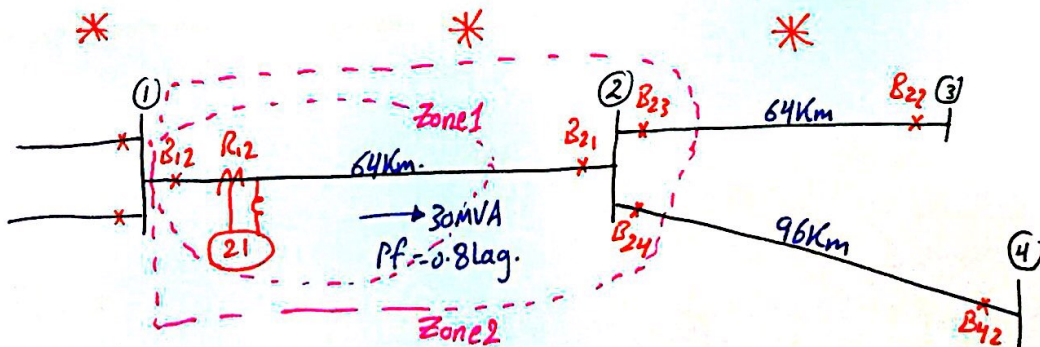

$$Z^+ = 0.05 + j0.5 \Omega/\text{km}$$

\* Before starting to solve this problem there are some required Notes indicated as follows:

- In case we have two adjacent lines, we calculate  $Z_{12}' = 1.2 Z_{12}'$  &  $Z_{12}' + 0.5 Z_{23}$  & we choose the longer reach between both of them.
- for  $Z_{r3}$ :  $Z_{r3} = Z_{12}' + 1.2 Z_{34}'$  here we always take the longest.


Shortest Line

$$Z_{12} = (0.05 + j0.5) \times 64K = 3.2 + j32 \Omega$$

$$Z_{23} = (0.05 + j0.5) \times 64K = 3.2 + j32 \Omega$$

$$Z_{24} = (0.05 + j0.5) \times 96K = 4.8 + j48 \Omega$$

$$|I_L|_{max} = \frac{50 \times 10^6}{\sqrt{3} \times 138 \times 10^3} = 209 \text{ A.}$$

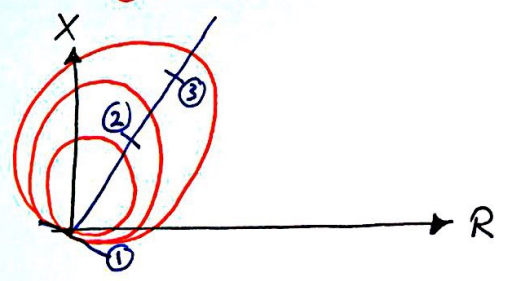

CHOOSE:  $CTR = \frac{200}{5}$ ,  $VTR = \frac{138 \times 10^3 / \sqrt{3}}{67} = \frac{1189.1}{1}$

$$Z_{relay} = Z_L \times \frac{CTR}{VTR} = 0.0336 \times Z_L \Rightarrow Z_{12}' = (3.2 + j32) \times 0.0336 = 0.11 + j1.1 \Omega$$

$$Z_{23}' = (3.2 + j32) \times 0.0336 = 0.11 + j1.1 \Omega$$

$$Z_{24}' = (4.8 + j48) \times 0.0336 = 0.16 + j1.6 \Omega$$


\*  $Z_{r1} = 0.8 \times Z_{12}' = 0.8 \times (0.11 + j1.1) = 0.088 + j0.88 \Omega$

\*  $Z_{r2} = 1.2 Z_{12}' = 1.2 \times (0.11 + j1.1) = 0.13 + j1.32 \Omega$   
 OR  $Z_{r2} = Z_{12}' + 0.5 Z_{23}' = (0.11 + j1.1) + \frac{1}{2} \times (0.11 + j1.1) = 0.16 + j1.6 \Omega$  }  $\Rightarrow$  choose:  $Z_{r2} = 0.16 + j1.6 \Omega$  "longer reach"

\*  $Z_{r3} = Z_{12}' + 1.2 Z_{34}' = (0.11 + j1.1) + 1.2 \times (0.16 + j1.6) = 0.3 + j3 \Omega$

$$|Z_{load}| = \left| \frac{V_{LL}^2}{S_L} \right| = \left| \frac{138^2}{50} \right| = 380 \Rightarrow Z_L = 380 \angle 36.9^\circ \Omega$$
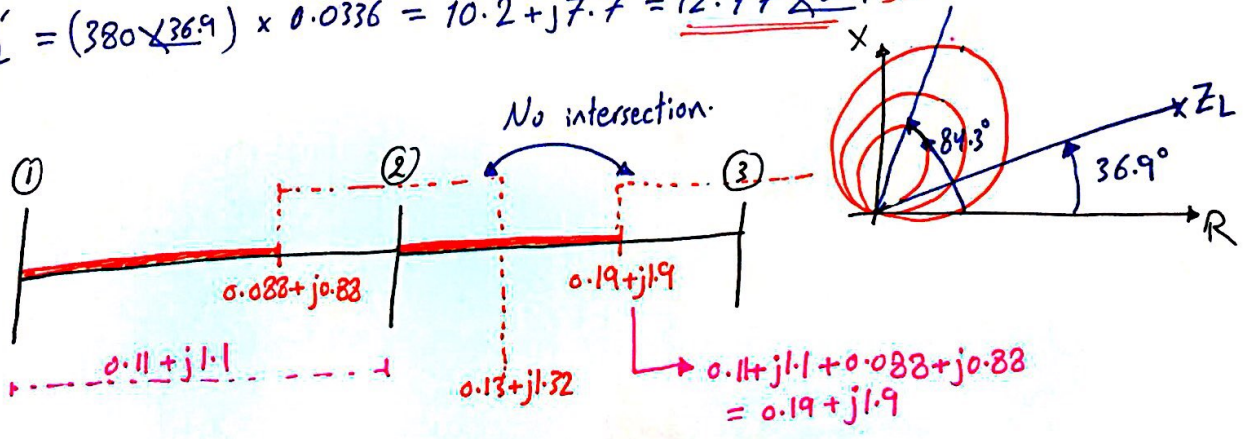
$$Z_L' = (380 \angle 36.9^\circ) \times 0.0336 = 10.2 + j7.7 = 12.77 \angle 36.9^\circ \Omega$$



\* \* \*

Q4 The Given Data as follows:

43

$$V_L = 345 \text{ kV.}$$

$$|I_{L_{\max}}| = 1500 \text{ A.}$$

$$\text{Pf} = 0.95 \text{ Lagging.}$$

$$Z_{12} = 8 + j50 \ \Omega$$

$$Z_{23} = 8 + j50 \ \Omega$$

$$Z_{24} = 5.3 + j33 \ \Omega$$

$$Z_{31} = 3 + j27 \ \Omega$$

$$\text{CTR} = 1500/5$$

$$\text{VTR} = 3000/1$$

$$a) Z_{\text{relay}} = Z_L \times \frac{\text{CTR}}{\text{VTR}} = Z_L \times \frac{1500/5}{3000/1} = \underline{0.1 \times Z_L}$$

$$Z'_{12} = 0.1 \times (8 + j50) = \underline{0.8 + j5 \ \Omega.}$$

$$Z'_{23} = 0.1 \times (8 + j50) = \underline{0.8 + j5 \ \Omega.}$$

$$Z'_{24} = 0.1 \times (5.3 + j33) = \underline{0.53 + j3.3 \ \Omega.}$$

$$Z'_{31} = 0.1 \times (3 + j27) = \underline{0.3 + j2.7 \ \Omega.}$$

$$b) Z_{r1} = 0.8 \times Z'_{12} = 0.8 \times (0.8 + j5) = \underline{0.64 + j4 \ \Omega}$$

$$Z_{r2} = 1.2 \times Z'_{12} = 1.2 \times (0.8 + j5) = 0.96 + j6 \ \Omega$$

OR

$$Z_{r2} = Z'_{12} + 0.5 Z'_{24} = (0.8 + j5) + \frac{1}{2} \times (0.53 + j3.3) = 1.07 + j6.65 \ \Omega$$



}  $\Rightarrow$  choose:  
 $\underline{Z_{r2} = 1.07 + j6.65 \ \Omega}$

$$Z_{r3} = Z'_{12} + 1.2 Z'_{23} = (0.8 + j5) + 1.2 \times (0.8 + j5) = \underline{1.76 + j11 \ \Omega}$$

$$c) Z_L = \frac{V}{I} = \frac{345 \times 10^3 / \sqrt{3}}{1500} = \underline{132.8 \angle 18.2^\circ \ \Omega}$$

$$d) Z'_L = 0.1 \times 132.8 \angle 18.2^\circ = \underline{13.28 \angle 18.2^\circ \ \Omega}$$

e) No tripping.

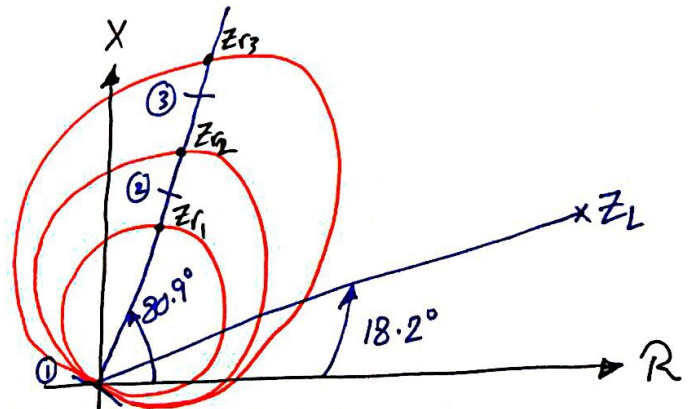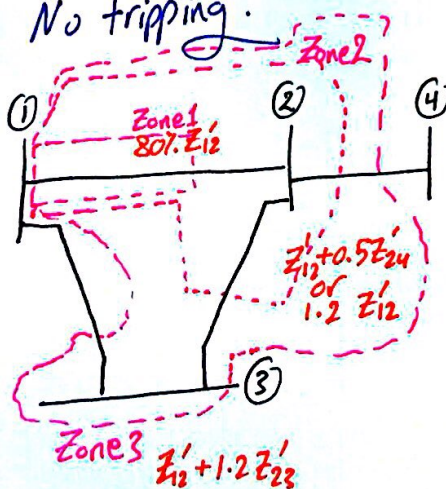


### \* Economic Dispatch:

- every generator has : minimum power limit & maximum power limit.
- Load / Demand  $\Rightarrow$  Both represent real power.

$$C(P_{Gi}) = \alpha_i + \beta_i P_{Gi} + \gamma_i P_{Gi}^2$$


$\downarrow$  Fixed operating cost.

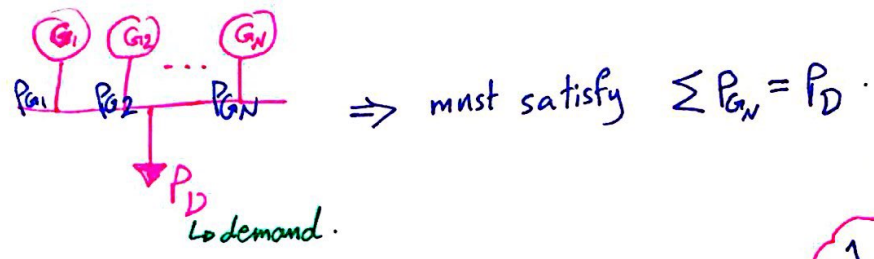$\alpha, \beta$  &  $\gamma$  are known for each machine.



$$\lambda = \frac{P_D + \sum_{i=1}^{n_{gen}} \frac{\beta_i}{2\gamma_i}}{\sum_{i=1}^n \frac{1}{2\gamma_i}}$$
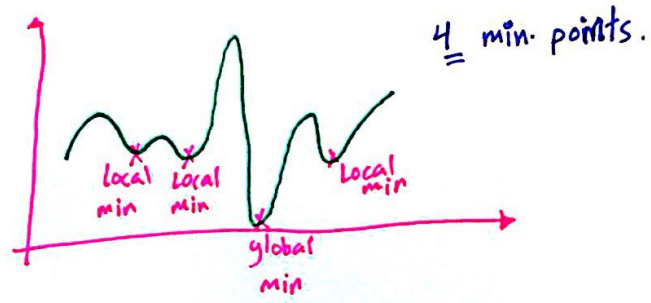
$$P_i = \frac{\lambda - \beta_i}{2\gamma_i}$$



\* for the Example in the Slides:


$$C = \alpha_i + \beta_i P + \gamma_i P^2$$

$$\frac{dC}{dP} = \beta_i + 2\gamma_i P$$



$\downarrow$  slope.

$\downarrow$  intersection with Y-axis

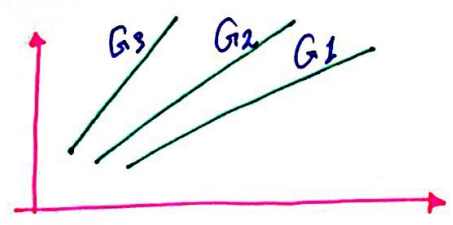we have  $\gamma_3 > \gamma_2 > \gamma_1$



### \* Stability:

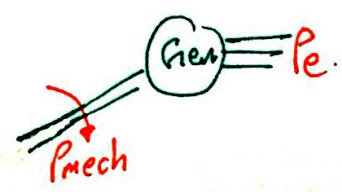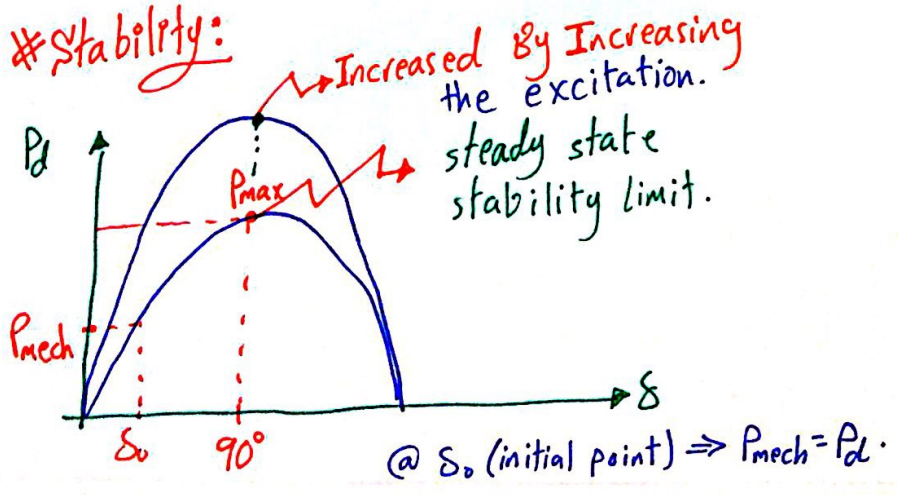

$$P_d = \frac{E \cdot V_t \sin \delta}{X_s}$$

**Question # 1:**

The fuel-cost functions in \$/h for two 800 MW thermal plants are given by

$$C_1 = 400 + 6.0P_1 + 0.004P_1^2$$

$$C_2 = 500 + \beta P_2 + \gamma P_2^2$$

where  $P_1$  and  $P_2$  are in MW.

- The incremental cost of power  $\lambda$  is \$8/MWh when the total power demand is 550 MW. Neglecting losses, determine the optimal generation of each plant.
- The incremental cost of power  $\lambda$  is \$10/MWh when the total power demand is 1300 MW. Neglecting losses, determine the optimal generation of each plant.
- From the results of (a) and (b) find the fuel-cost coefficients  $\beta$  and  $\gamma$  of the second plant.

**Solution:**

$$\frac{dC_1}{dP_1} = 6 + 0.008P_1 = \lambda$$

$$\frac{dC_2}{dP_2} = \beta + 2\gamma P_2 = \lambda$$

(a) For  $\lambda = 8$ , and  $P_D = 550$  MW, we have

$$P_1 = \frac{8 - 6}{0.008} = 250 \text{ MW}$$

$$P_2 = P_D - P_1 = 550 - 250 = 300 \text{ MW}$$

(b) For  $\lambda = 10$ , and  $P_D = 1300$  MW, we have

$$P_1 = \frac{10 - 6}{0.008} = 500 \text{ MW}$$

$$P_2 = P_D - P_1 = 1300 - 500 = 800 \text{ MW}$$

(c) The incremental cost of power for plant 2 are given by

$$\beta + 2\gamma(300) = 8$$

$$\beta + 2\gamma(800) = 10$$

Solving the above equations, we find  $\beta = 6.8$ , and  $\gamma = 0.002$



Question # 2:

The fuel-cost functions in \$/h for three thermal plants are given by

$$\begin{aligned}C_1 &= 350 + 7.20P_1 + 0.0040P_1^2 \\C_2 &= 500 + 7.30P_2 + 0.0025P_2^2 \\C_3 &= 600 + 6.74P_3 + 0.0030P_3^2\end{aligned}$$

where  $P_1$ ,  $P_2$ , and  $P_3$  are in MW. The governors are set such that generators share the load equally. Neglecting line losses and generator limits, find the total cost in \$/h when the total load is

- (i)  $P_D = 450$  MW
- (ii)  $P_D = 745$  MW
- (iii)  $P_D = 1335$  MW

Solution:

- (i) For  $P_D = 450$  MW,  $P_1 = P_2 = P_3 = \frac{450}{3} = 150$  MW. The total fuel cost is

$$\begin{aligned}C_t &= 350 + 7.20(150) + 0.004(150)^2 + 500 + 7.3(150) + 0.0025(150)^2 + \\ &600 + 6.74(150) + 0.003(150)^2 = 4,849.75 \text{ \$/h}\end{aligned}$$

- (ii) For  $P_D = 745$  MW,  $P_1 = P_2 = P_3 = \frac{745}{3}$  MW. The total fuel cost is

$$\begin{aligned}C_t &= 350 + 7.20\left(\frac{745}{3}\right) + 0.004\left(\frac{745}{3}\right)^2 + 500 + 7.3\left(\frac{745}{3}\right) + 0.0025\left(\frac{745}{3}\right)^2 \\ &+ 600 + 6.74\left(\frac{745}{3}\right) + 0.003\left(\frac{745}{3}\right)^2 = 7,310.46 \text{ \$/h}\end{aligned}$$

- (iii) For  $P_D = 1335$  MW,  $P_1 = P_2 = P_3 = 445$  MW. The total fuel cost is

$$\begin{aligned}C_t &= 350 + 7.20(445) + 0.004(445)^2 + 500 + 7.3(445) + 0.0025(445)^2 + \\ &600 + 6.74(445) + 0.003(445)^2 = 12,783.04 \text{ \$/h}\end{aligned}$$

Question # 3:

Neglecting line losses and generator limits, determine the optimal scheduling of generation for each loading condition in Question # 2

- a. by analytical technique.
- b. find the savings in \$/h for each case compared to the costs in Question # 2 when the generators shared load equally.

Solution:

(a) (i) For  $P_D = 450$  MW, from (7.33),  $\lambda$  is found to be

$$\begin{aligned}\lambda &= \frac{450 + \frac{7.2}{0.008} + \frac{7.3}{0.005} + \frac{6.74}{0.006}}{\frac{1}{0.008} + \frac{1}{0.005} + \frac{1}{0.006}} \\ &= \frac{450 + 3483.333}{491.666} = 8.0 \text{ \$/MWh}\end{aligned}$$

Substituting for  $\lambda$  in the coordination equation, the optimal dispatch is

$$\begin{aligned}P_1 &= \frac{8.0 - 7.2}{2(0.004)} = 100 \\ P_2 &= \frac{8.0 - 7.3}{2(0.0025)} = 140 \\ P_3 &= \frac{8.0 - 6.74}{2(0.003)} = 210\end{aligned}$$

(a) (ii) For  $P_D = 745$  MW, from (7.33),  $\lambda$  is found to be

$$\lambda = \frac{745 + 3483.333}{491.666} = 8.6 \text{ \$/MWh}$$

Substituting for  $\lambda$  in the coordination equation, the optimal dispatch is

$$\begin{aligned}P_1 &= \frac{8.6 - 7.2}{2(0.004)} = 175 \\ P_2 &= \frac{8.6 - 7.3}{2(0.0025)} = 260 \\ P_3 &= \frac{8.6 - 6.74}{2(0.003)} = 310\end{aligned}$$

(a) (iii) For  $P_D = 1335$  MW, from (7.33),  $\lambda$  is found to be

$$\lambda = \frac{1335 + 3483.333}{491.666} = 9.8 \text{ \$/MWh}$$

Substituting for  $\lambda$  in the coordination equation, the optimal dispatch is

$$\begin{aligned}P_1 &= \frac{9.8 - 7.2}{2(0.004)} = 325 \\ P_2 &= \frac{9.8 - 7.3}{2(0.0025)} = 500 \\ P_3 &= \frac{9.8 - 6.74}{2(0.003)} = 510\end{aligned}$$

(c)(i) For  $P_1 = 100$  MW,  $P_2 = 140$  MW, and  $P_3 = 210$  MW, the total fuel cost is

$$C_t = 350 + 7.20(100) + 0.004(100)^2 + 500 + 7.3(140) + 0.0025(140)^2 + 600 + 6.74(210) + 0.003(210)^2 = 4,828.70 \text{ \$/h}$$

Compared to Question #2 (i), when the generators shared load equally, the saving is  $4,849.75 - 4,828.70 = 21.05$  \$/h.

(c)(ii) For  $P_1 = 175$  MW,  $P_2 = 260$  MW, and  $P_3 = 310$  MW, the total fuel cost is

$$C_t = 350 + 7.20(175) + 0.004(175)^2 + 500 + 7.3(260) + 0.0025(260)^2 + 600 + 6.74(310) + 0.003(310)^2 = 7,277.20 \text{ \$/h}$$

Compared to Question #2 (ii), when the generators shared load equally, the saving is  $7,310.46 - 7,277.20 = 33.25$  \$/h.

(c)(iii) For  $P_1 = 325$  MW,  $P_2 = 500$  MW, and  $P_3 = 510$  MW, the total fuel cost is

$$C_t = 350 + 7.20(325) + 0.004(325)^2 + 500 + 7.3(500) + 0.0025(500)^2 + 600 + 6.74(510) + 0.003(510)^2 = 12,705.20 \text{ \$/h}$$

Compared to Question #2 (iii), when the generators shared load equally, the saving is  $12,783.04 - 12,705.20 = 77.84$  \$/h.

Question # 4:

Repeat Question # 3 (a), but this time consider the following generator limits (in MW)

$$122 \leq P_1 \leq 400$$

$$260 \leq P_2 \leq 600$$

$$50 \leq P_3 \leq 445$$

Solution:

In Question # 3, in part (a) (i), the optimal dispatch are  $P_1 = 100$  MW,  $P_2 = 140$  MW, and  $P_3 = 210$  MW. Since  $P_1$  and  $P_2$  are less than their lower limit, these plants are pegged at their lower limits. That is,  $P_1 = 122$ , and  $P_2 = 260$  MW. Therefore,  $P_3 = 450 - (122 + 260) = 68$  MW.

In Question # 3, in part (a) (ii), the optimal dispatch are  $P_1 = 175$  MW,  $P_2 = 260$  MW, and  $P_3 = 310$  MW, which are within the plants generation limits.

In Question # 3, in part (a) (iii), the optimal dispatch are  $P_1 = 325$  MW,  $P_2 = 500$  MW, and  $P_3 = 510$  MW. Since  $P_3$  exceed its upper limit, this plant is pegged at  $P_3 = 445$ . Therefore, a load of  $1335 - 445 = 890$  MW must be shared between plants 1 and 2, with equal incremental fuel cost give by

$$\begin{aligned}\lambda &= \frac{890 + \frac{7.2}{0.008} + \frac{7.3}{0.005}}{\frac{1}{0.008} + \frac{1}{0.005}} \\ &= \frac{890 + 2360}{325} = 10 \text{ \$/MWh}\end{aligned}$$

Substituting for  $\lambda$  in the coordination equation, the optimal dispatch is

$$P_1 = \frac{10 - 7.2}{2(0.004)} = 350$$

$$P_2 = \frac{10 - 7.3}{2(0.0025)} = 540$$


Since  $P_1$  and  $P_2$  are within their limits the above result is the optimal dispatch.

\* The subjects that NOT included in the course this semester:

- stability EX1. & EX2.
- Derivation of swing Equation.
- Stability of a synchronous motor connected to  $\infty$ -Bus.
- Steady State Stability.


\* when  $P_m > P_e$  the machine will accelerate &  $\delta$  will increase.

\* Opening of one of the parallel Line:

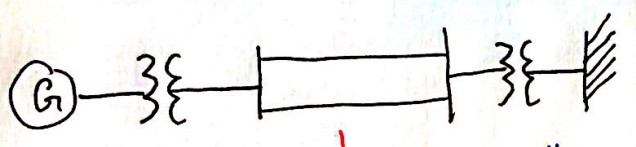



↳ we usually use this double circuit to decrease the value of  $X_s$  which gives more power ( $P = \frac{V_t E \sin \delta}{X_s}$ ).

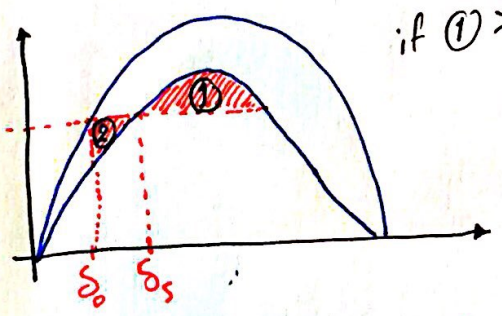- so if one of the lines opened the power will be reduced.



if ① > ② then the system would be stable.

\* Short Circuit Occuring in the System:

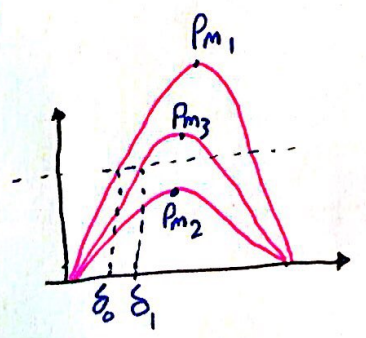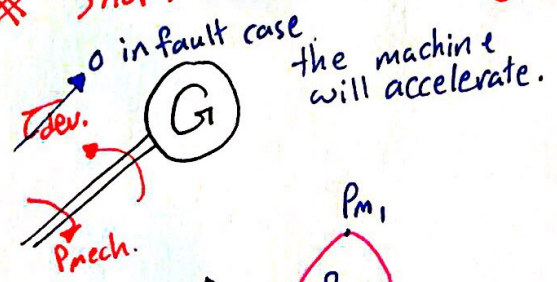

$$\delta_{cc} = \frac{\pi f_0}{H} P_m t_{cc}^2 + \delta_0$$

Critical Clearing Angle.

$$t_{cc} = \sqrt{\frac{2H(\delta_{cc} - \delta_0)}{\pi f_0 P_m}}$$

$$\cos \delta_{cc} = \frac{P_s (\delta_m - \delta_0) + P_m \cos \delta_m - P_m \cos \delta_0}{P_m - P_m}$$

Post fault. during fault.

\*\*\* End of Material. \*\*\*

**Example # 1:**

A transmission line is acting as an interconnector between two constant voltage networks as shown in Fig. E1. Determine graphically or otherwise the maximum additional load which can be suddenly applied to this interconnector already carrying 50 MW if the power angle equation is  $P_e = 100 \sin \delta$ .

**Solution:**

$$P_o = 100 \sin \delta_o = 50 \Rightarrow \delta_o = 30^\circ = 0.5236 \text{ rad}$$

Accelerating Area is  $A_1$  and decelerating area is  $A_2$ .

$$A_1 = \int_{\delta_o}^{\delta_1} (P_1 - 100 \sin \delta) d\delta = P_1(\delta_1 - \delta_o) + 100(\cos \delta_1 - \cos \delta_o)$$

$$A_2 = \int_{\delta_1}^{\delta_2} (100 \sin \delta - P_1) d\delta = -100(\cos \delta_2 - \cos \delta_1) - P_1(\delta_2 - \delta_1)$$

For limiting case  $\delta_2 = \delta_{max} = \pi - \delta_1$ .

Moreover,  $P_1 = 100 \sin \delta_1$ .

Equating areas  $A_1$  and  $A_2$

and substituting these values we get the equation

$$A_1 = A_2$$

$$P_1(\delta_1 - \delta_o) + 100(\cos \delta_1 - \cos \delta_o) = -100(\cos(\pi - \delta_1) - \cos \delta_1) - P_1(\pi - \delta_1 - \delta_1)$$

$$P_1\delta_1 - P_1\delta_o + 100 \cos \delta_1 - 100 \cos \delta_o = -100(\cos(\pi) \cdot \cos(\delta_1) + \sin(\pi) \cdot \sin(\delta_1)) + 100 \cos(\delta_1) - P_1(\pi - \delta_1) + P_1\delta_1$$

$$-P_1\delta_o + 100 \cos \delta_1 - 100 \cos \delta_o = 100 \cos(\delta_1) + 100 \cos(\delta_1) - P_1(\pi - \delta_1)$$

$$-100 \sin(\delta_1)\delta_o - 100 \cos \delta_o = 100 \cos(\delta_1) - 100 \sin(\delta_1)(\pi - \delta_1)$$

$$-\sin(\delta_1)\delta_o - \cos \delta_o = \cos(\delta_1) - \sin(\delta_1)(\pi - \delta_1)$$

$$\sin(\delta_1)(\pi - \delta_1) - \sin(\delta_1)\delta_o + \cos \delta_1 = \cos(\delta_1) + \cos \delta_o$$

$$\cos \delta_o + \cos \delta_1 = (\pi - \delta_1 - \delta_o) \sin \delta_1$$

The angles  $\delta_1$  and  $\delta_o$  in this equation are in radians.

The equation can be solved by hit and trail. The results is  $\delta_1 = 1.054179 = 60.4^\circ$ .

$$\cos \delta_o + \cos \delta_1 = (\pi - \delta_1 - \delta_o) \sin \delta_1 = (\delta_{max} - \delta_o) \sin \delta_1$$


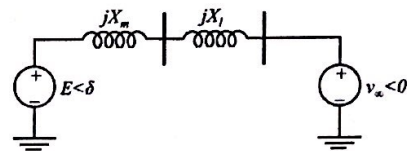
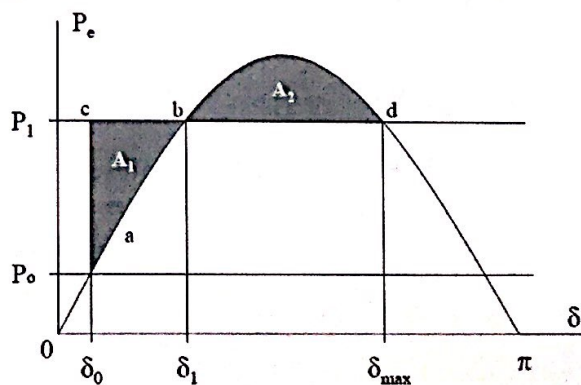
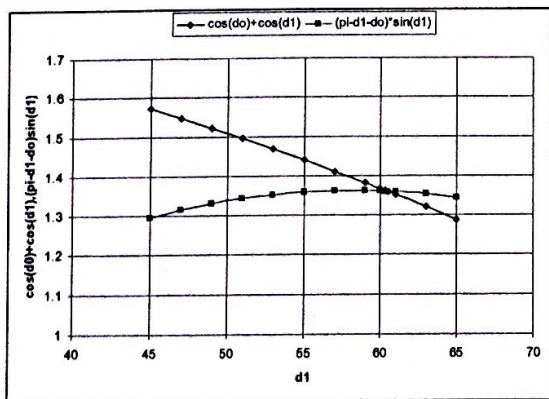


Fig. E1

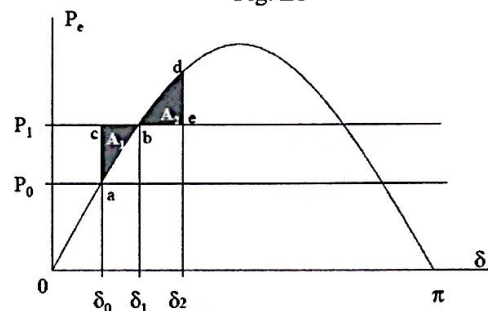

Example # 2:

*transient stability*

For the system shown in Fig. E2, the per unit value of the system are:  $|E| = 1.2$  pu,  $|V_\infty| = 1.0$  pu,  $X'_d = 0.2$  pu,  $X_1 = X_2 = 0.4$  pu. The system is operating in equilibrium with  $P_o = P_{eo} = 1.5$  pu when one of the lines is suddenly switched out. Predict whether the system will be stable or not. If the system is stable find the maximum value of  $\delta$  attains.

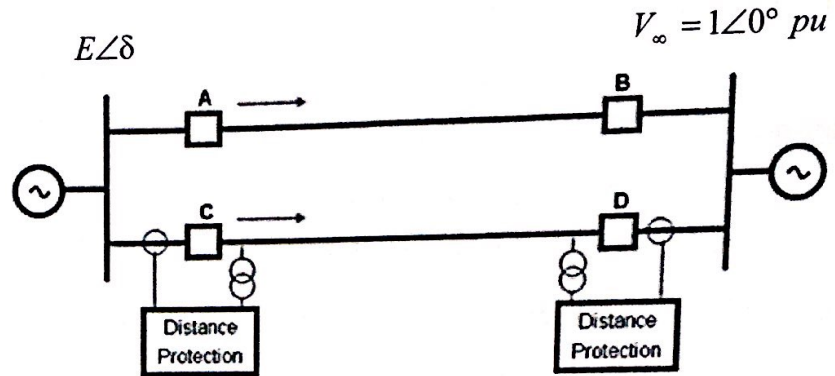


Fig. E2

Solution:

$$P_e = \frac{EV_\infty}{X_{eq}} \sin \delta = \frac{EV_\infty}{X'_d + \frac{X_1 \times X_2}{X_1 + X_2}} \sin \delta = \frac{1.2 \times 1}{0.2 + \frac{0.4 \times 0.4}{0.4 + 0.4}} \sin \delta = \frac{1.2}{0.4} \sin \delta = 3 \sin \delta$$

$$P_e(\delta_o) = 3 \sin \delta_o = 1.5 \Rightarrow \delta_o = 30^\circ \text{ (0.524 radians)}$$

when one line is switched out

$$P'_e = \frac{EV_\infty}{X'_{eq}} \sin \delta = \frac{EV_\infty}{X'_d + X_1} \sin \delta = \frac{1.2 \times 1}{0.2 + 0.4} \sin \delta = \frac{1.2}{0.6} \sin \delta = 2 \sin \delta$$

$$P_e = P'_e(\delta_s) = 2 \sin \delta_s = 1.5 \Rightarrow \delta_s = 48.6^\circ \text{ (0.848 radians)}$$

$$P_e = P'_e(\delta_m) = 2 \sin \delta_m = 1.5 \Rightarrow \delta_m = 131.4^\circ \text{ (0.2.293 radians)}$$

$$A_1 = \int_{\delta_o}^{\delta_s} (P_s - 2 \sin \delta) d\delta = P_s(\delta_s - \delta_o) + 2(\cos \delta_s - \cos \delta_o)$$

$$= 1.5(0.848 - 0.524) + 2(\cos(48.6^\circ) - \cos(30^\circ)) = 0.0773$$

$$A_{2max} = \int_{\delta_s}^{\delta_{max}} (2 \sin \delta - P_s) d\delta = -2(\cos \delta_{max} - \cos \delta_s) - P_s(\delta_{max} - \delta_s)$$

$$= -2(\cos(131.4^\circ) - \cos(48.6^\circ)) - 1.5(2.293 - 0.848) = 0.0478$$

since  $A_{2max}$  (0.478) >  $A_1$  (0.0773), the system is stable.

$$A_2 = \int_{\delta_s}^{\delta_2} (2 \sin \delta - P_s) d\delta = -2(\cos \delta_m - \cos \delta_s) - P_s(\delta_m - \delta_s) = -2(\cos(\delta_m) - \cos(\delta_s)) - 1.5(\delta_m - \delta_s)$$

$$= -2(\cos(\delta_m) - \cos(48.6^\circ)) - 1.5(\delta_m - 0.848)$$

$$A_2 = \int_{\delta_s}^{\delta_m} (2 \sin \delta - P_s) d\delta = -2(\cos \delta_m - \cos \delta_s) - P_s(\delta_m - \delta_s)$$



$$= -2(\cos(\delta_m) - \cos(\delta_s)) - 1.5(\delta_m - \delta_s)$$

$$= -2(\cos(\delta_m) - \cos(48.6^\circ)) - 1.5(\delta_m - 0.848)$$

$$-2(\cos(\delta_m) - \cos(48.6^\circ)) - 1.5(\delta_m - 0.848) = 0.0773$$

$$1.5\delta_m + 2 \cos(\delta_m) = 1.5 \times 0.848 + 2 \cos(48.6^\circ) - 0.0773$$
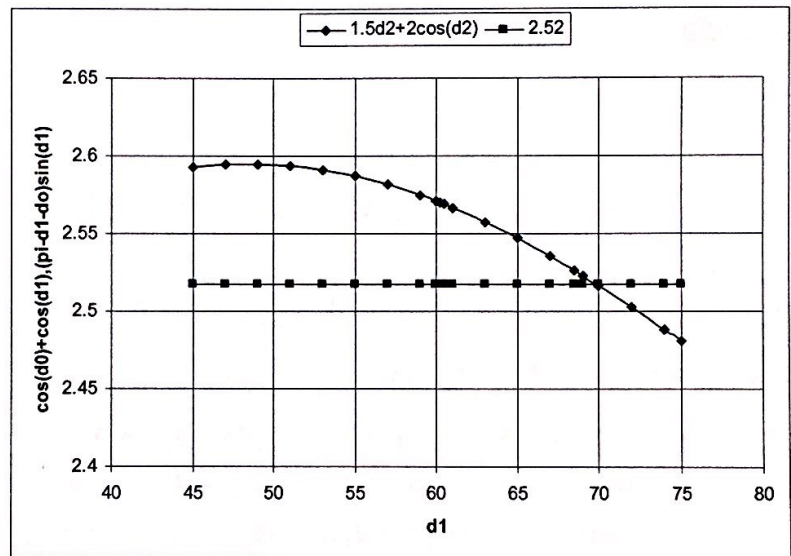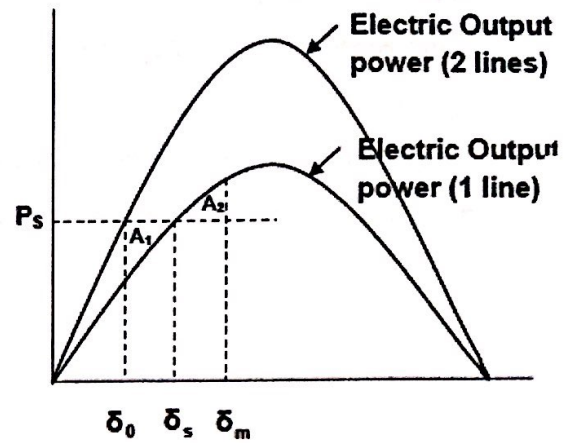
$$1.5\delta_m + 2 \cos(\delta_m) = 2.52$$



$\delta_1$	$\delta_1$		
45	0.785398	2.592311	2.517
47	0.820305	2.594454	2.517
49	0.855211	2.594935	2.517
51	0.890118	2.593818	2.517
53	0.925025	2.591167	2.517
55	0.959931	2.58705	2.517
57	0.994838	2.581535	2.517
59	1.029744	2.574693	2.517
60	1.047198	2.570796	2.517
60.3	1.052434	2.569568	2.517
60.5	1.055924	2.568733	2.517
61	1.064651	2.566596	2.517
63	1.099557	2.557317	2.517
65	1.134464	2.546933	2.517
67	1.169371	2.535518	2.517
68.5	1.195551	2.526328	2.517
69	1.204277	2.523152	2.517
70	1.22173	2.516636	2.517
72	1.256637	2.50299	2.517
74	1.291544	2.48859	2.517
75	1.308997	2.481133	2.517



Example # 3:

A generator is transferring power to a load through a short line as shown in Fig. E3. The power angle equation is  $P_e = P_{max} \sin \delta$ . The initial power is  $P_m$  pu when a 3-phase fault occurs at the terminals of generator.

- Use equal area criterion to find equation for critical clearing angle and the critical clearing time.
- Find the critical clearing time angle  $\delta_{cc}$  if  $P_{max} = 2$  and  $P_m = 1.0$  pu.  $H=6$  MJ/MVA and  $f_o=50$ Hz.

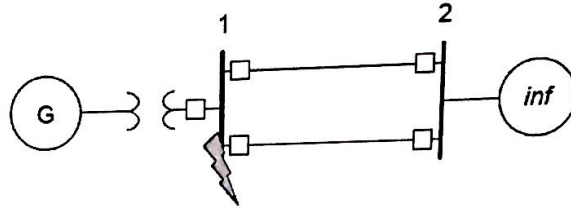


Fig. E3

Solution:

$$A_1 = \int_{\delta_o}^{\delta_c} P_m d\delta = P_m (\delta_c - \delta_o)$$

$$A_2 = \int_{\delta_c}^{\delta_{max}} (P_{max} \sin \delta - P_m) d\delta = -P_{max} (\cos \delta_{max} - \cos \delta_c) - P_m (\delta_{max} - \delta_c)$$

For stability  $A_1 = A_2$ .

$$P_m (\delta_c - \delta_o) = -P_{max} (\cos \delta_{max} - \cos \delta_c) - P_m (\delta_{max} - \delta_c)$$

but  $\delta_{max} = \pi - \delta_o$  and  $P_m = P_{max} \sin \delta_o$

$$P_m (\delta_c - \delta_o) = P_{max} \cos \delta_c - P_{max} \cos \delta_{max} - P_m (\pi - \delta_o - \delta_c)$$


$$P_{max} (\delta_c - \delta_o) \sin \delta_o = P_{max} \cos \delta_c - P_{max} \cos \delta_{max} - P_{max} (\pi - \delta_o - \delta_c) \sin \delta_o$$

$$P_{max} (\delta_c - \delta_o) \sin \delta_o = P_{max} \cos \delta_c + P_{max} \cos \delta_o - P_{max} (\pi - \delta_o - \delta_c) \sin \delta_o$$

$$(\delta_c - \delta_o) \sin \delta_o = \cos \delta_c + \cos \delta_o - (\pi - \delta_o - \delta_c) \sin \delta_o$$

$$\cos \delta_c = (\pi - 2\delta_o) \sin \delta_o - \cos \delta_o$$
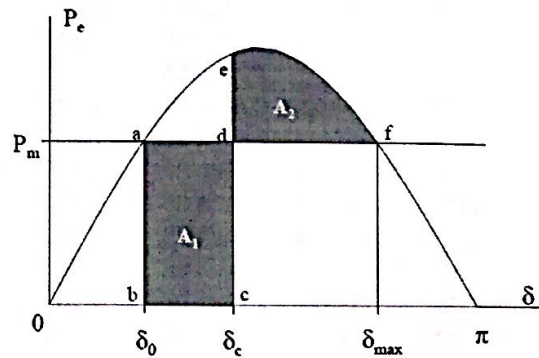
$$\delta_c = \cos^{-1} [(\pi - 2\delta_o) \sin \delta_o - \cos \delta_o]$$



During fault, power transfer is zero.

$$M \frac{d^2\delta}{dt^2} = P_m - 0 = P_{\max} \sin \delta_o$$

$$\frac{d^2\delta}{dt^2} = \frac{P_m - 0}{M} = \frac{P_{\max} \sin \delta_o}{M}$$

$$\frac{d}{dt} \left( \frac{d\delta}{dt} \right) = \frac{P_m}{M} \Rightarrow d \left( \frac{d\delta}{dt} \right) = \frac{P_m}{M} dt$$

$$(d\omega) = \frac{P_m}{M} dt$$

$$\int_{\omega_s}^{\omega} d\omega = \int_0^t \frac{P_m}{M} dt$$

$$\omega - \omega_s = \omega_r = \frac{d\delta}{dt} = \frac{P_m}{M} t \Rightarrow d\delta = \frac{P_m}{M} t dt$$

$$\int_{\delta_o}^{\delta} d\delta = \int_0^t \frac{P_m}{M} t dt$$

$$\delta(t) = \frac{P_m}{2M} t^2 + \delta_o$$

$$\text{at } t = t_c \Rightarrow \delta = \delta_c \Rightarrow \delta_c = \frac{P_m}{2M} t_c^2 + \delta_o$$

$$t_c = \sqrt{\frac{2M}{P_m} (\delta_c - \delta_o)} = \sqrt{\frac{2H}{\pi f_o P_m} (\delta_c - \delta_o)}$$

b.  $P_{\max} = 2$  and  $P_m = 1.0$  pu.  $H = 6$  MJ/MVA and  $f_o = 50$  Hz.

$$\Rightarrow M = \frac{H}{\pi f_o} = \frac{6}{\pi \times 50}, \quad P_m = P_{\max} \sin \delta_o \Rightarrow 1.0 = 2 \sin \delta_o \Rightarrow \delta_o = 30^\circ (0.5236 \text{ rad})$$

$$\delta_c = \cos^{-1} [(\pi - 2\delta_o) \sin \delta_o - \cos \delta_o] = \cos^{-1} [(\pi - 2 \times 0.5236) \sin 30^\circ - \cos 30^\circ]$$

$$\delta_c = 79.6^\circ \text{ } 1.389 \text{ rad}$$

$$t_c = \sqrt{\frac{2H}{\pi f_o P_m} (\delta_c - \delta_o)} = \sqrt{\frac{2 \times 6}{\pi \times 50 \times 1} (1.389 - 0.5236)}$$


$$t_c = 0.257 \text{ s}$$

$$t_c = 12.85 \text{ cycles of } 50 \text{ Hz}$$

**Example # 4:**

A balanced 3-phase fault occurs at middle point of line 2 when the power transfer is 1.5 pu in the system. The system data are  $|E| = 1.2$  pu,  $|V_\infty| = 1.0$  pu,  $X_d' = 0.2$  pu,  $X_1 = X_2 = 0.4$  pu.

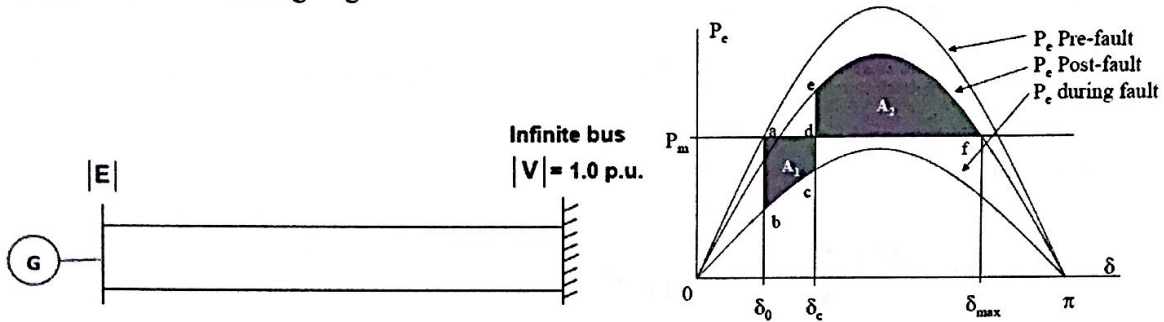- Determine whether the system is stable for a sustained fault.
- The fault is cleared at  $\delta = 60^\circ$ . Is the system stable? If so find the maximum rotor swing.
- Find the critical clearing angle



**Solution:**


**a. Pre-fault condition**

Transfer reactance  $X_{eq} = 0.2 + 0.4 // 0.4 = 0.4$  pu

$$P_e = \frac{EV_\infty}{X_{eq}} \sin \delta = \frac{EV_\infty}{X_d' + \frac{X_1 \times X_2}{X_1 + X_2}} \sin \delta = \frac{1.2 \times 1}{0.2 + \frac{0.4 \times 0.4}{0.4 + 0.4}} \sin \delta = \frac{1.2}{0.4} \sin \delta = 3 \sin \delta$$

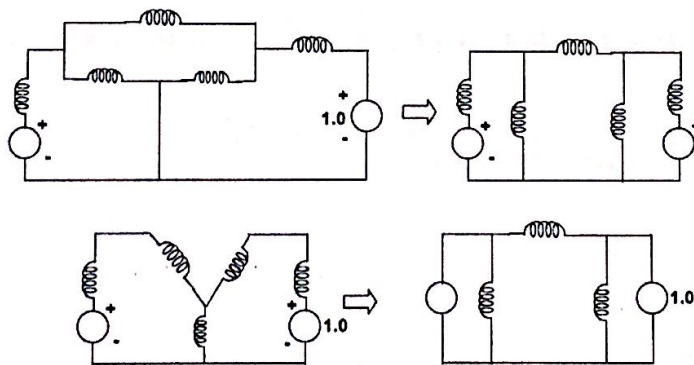**b. During-fault condition**

$$P_e' = \frac{1.2 \times 1}{1.0} \sin \delta = 1.2 \sin \delta$$



Since the initial load is 1.5 pu, and the maximum possible value of power transfer during fault is condition is 1.2 pu, therefore stability is impossible for a sustained fault.

**c. Post-fault condition**

$$P_e'' = \frac{1.2 \times 1}{0.2 + 0.4} \sin \delta = \frac{1.2}{0.6} \sin \delta = 2 \sin \delta$$

$$1.5 \delta_2 + 2 \cos(\delta_2) = 2.225 \Rightarrow \delta_2 = 1.848 \text{ rad } (105.9^\circ)$$

$$\cos \delta_{cc} = \frac{P_m (\delta_{max} - \delta_o) + P_{3max} \cos \delta_{max} - P_{2max} \cos \delta_o}{P_{3max} - P_{2max}} = \frac{1.5(2.293 - 0.524) + 2 \cos(2.293) - 1.2 \cos(0.524)}{2 - 1.2}$$

$$\delta_{cc} = 1.196 \text{ rad } (68.6^\circ)$$