

**Problem 1.** Solve the following short problems.

(6 points)

- a) Complete the following table to show the binary representation of the following number in signed-magnitude and 2's complement, assuming you have 7 bits.

Number	Signed Magnitude	2's Complement
-40		



- b) Given a 6-bit signed 2's complement number system, the maximum positive number that can be represented is \_\_\_\_\_, while the minimum negative number is \_\_\_\_\_.
- c) Consider the following operation of adding the following 5-bit 2's complement numbers:

$$(11100)_2 + (11001)_2 = ( \quad )_{10}$$

1. Fill in the decimal value of the result in the equation above.
2. Does an overflow occur for this operation? Justify your answer.

**Problem 2.** Map the below circuit to an equivalent, optimized circuit using NAND technology. Draw your final circuit in the box.

(3 points)

 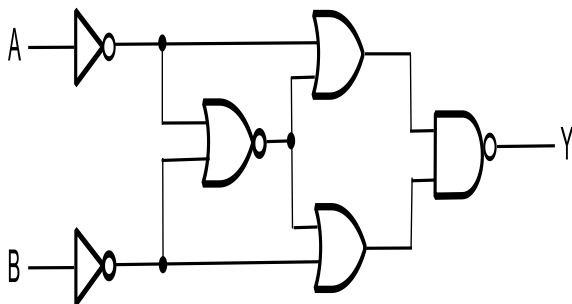


**Problem 3.** Write the truth table of the circuit that computes  $(N \text{ modulo } 3)$ , where  $N$  can be any number in  $\{0,1,5,9,11,12,14,15\}$ . The circuit is required to use the minimum number of bits for representing inputs and outputs. You need not show don't care conditions.

Hint: Remember that modulo operator determines the remainder after division. Example,  $18 \text{ modulo } 5$  is equal to 3. (4 points)

---

**Problem 4:** Study the following circuit. Then fill-in the truth table of the function implemented. Note that in the used encoder,  $I_3$  has the highest priority then  $I_2$ , and so on.

(4 points)

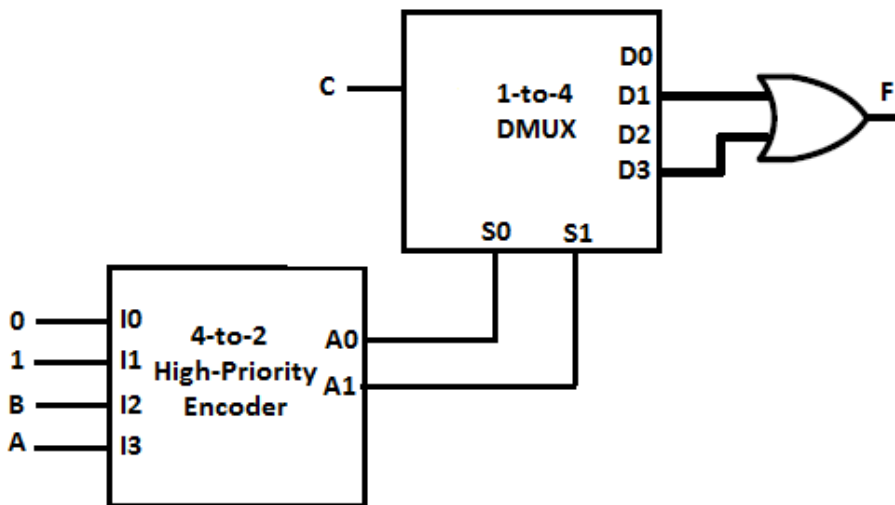

**Problem 5:** Let  $F(x, y, z) = \sum_m(3,5,6,7)$ ,

(4 points)

- a. Draw the logic diagram of F using an 8-to-1 MUX.
- b. Draw the logic diagram of F using a 3-to-8 line decoder and a four-input OR gate.

**Problem 6.** Assume  $x$  is a 4-bit 2's complement signed number. Given the following 4-bit ripple carry adder, design a circuit that outputs a 4 bit 2's complement signed number  $y$ . The circuit has a control bit  $S$ , when  $S=0$  the output  $y=2x$ , when  $S=1$  the output  $y=-x$ .

(Hint: remember that  $2x=x+x$ )

(4 points)

