


* Electropneumatic Control Systems:

E } | N.O "Normally open"


E } / N.C "Normally Close"

• Power supply in the pneumatic system is air signal.

• Valves:

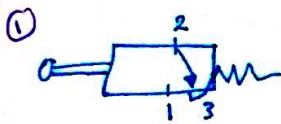

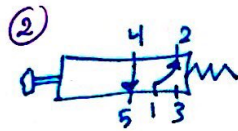
3/2 Directional Push-button with spring centering valve.




5/2 Directional Push-button with spring centering valve.




3/2 directional pedal valve.

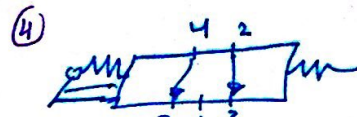

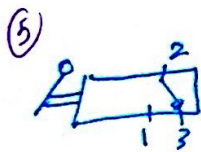
5/3 directional lever with spring centering valve.




3/2 directional lever valve.

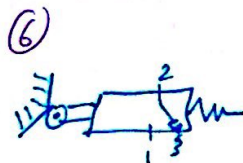


3/2 directional roller valve.

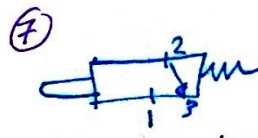


3/2 directional plunger valve.

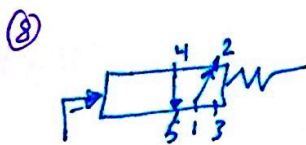

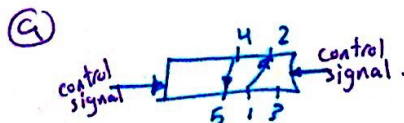5/2 Mono-stable indirect controller valve.





Bistable indirect controller Valve.

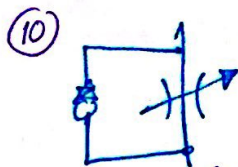


Manual Airflow Regulator Valve.

• Cylinders:

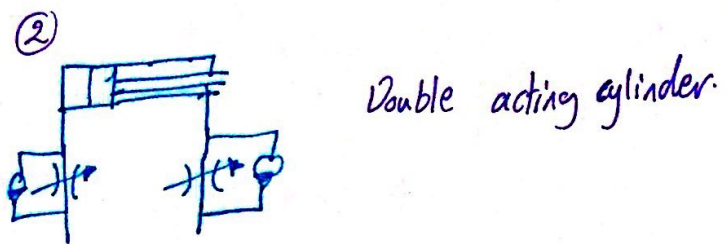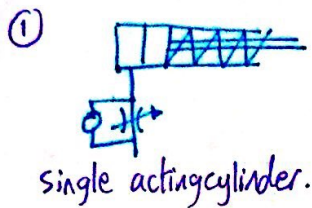


• Timer:

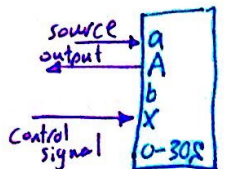

"b Not connected"

① N.C timer.

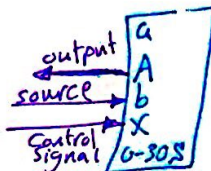

"a Not connected"

② N.O timer.

X ≡ Control signal
A ≡ Output.

• Logic Gates & Memory Cell:

- * performance of
 - AND gate: Logical Product.
 - OR gate: Logical Addition.
 - Not gate: Logical inverse.
 - YES (Buffer) gate: Logical identity.

- SR flip flop:

| | | |
|-----------------------|---|-------------------------|
| $S=0 \& R=1$ (Reset). | ; | $S=1 \& R=1$ (invalid). |
| $S=1 \& R=0$ (Set). | ! | $S=0 \& R=0$ (save). |

• Solenoid Sensors: Translates the mechanical motion to electrical signal.

* * *

* PLC & Ladder Logic:


PLC ≡ Programmable Logic Controllers.

• Name of the used device: "PLC SIEMENS S7-200"

• in Ladder:

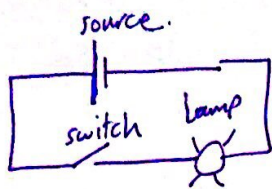
- vertical called Rails.
- Horizontal called Rungs.





Equivalent in ladder \Rightarrow


for NO:

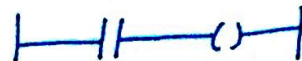

for NC:



* OR Gate:

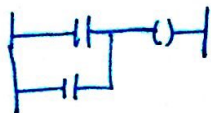

* And Gate:



* Not gate:



* NAND Gate:



* NOR Gate:




* XOR Gate:



* Equivalent cct for the Motor:


* ladder diagram for ON-delay Timer:

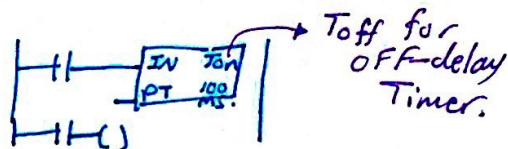

\Rightarrow * Number for ToF & Ton must be different (i.e we can't take ToF & Ton using T52 for Both).




CTU \equiv Count Up.

CTD \equiv Count Down.

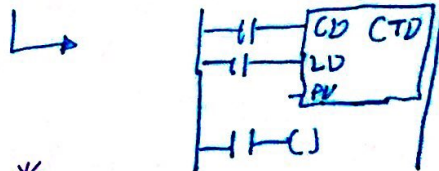

* DC Servo Motor:

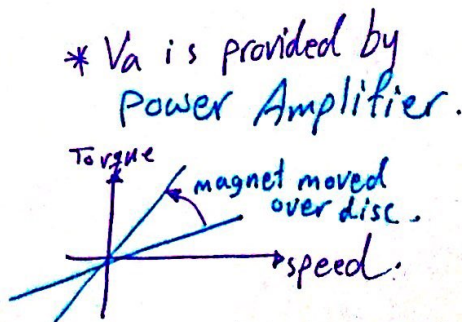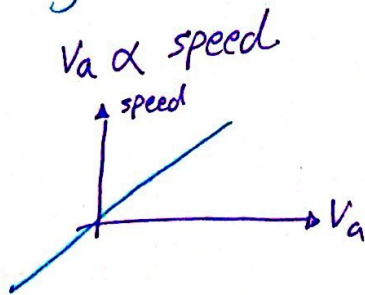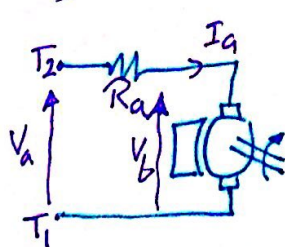- The difference in the comparison called error signal, the part that carries out the comparison called error channel.
- e.g of actuator: geared motor, we use amplifier to drive it.




* Va is provided by Power Amplifier.

* The previous two figures $\left\{ \begin{array}{l} \text{speed} \propto V_a \text{ represents DC Motor charc.} \\ \text{Torque} \propto \text{speed represents charc. of Magnetic Brake.} \end{array} \right.$

* In the experiment, Motor speed = 32 * output shaft speed. (RPM).


* Motor charc. Related to load:

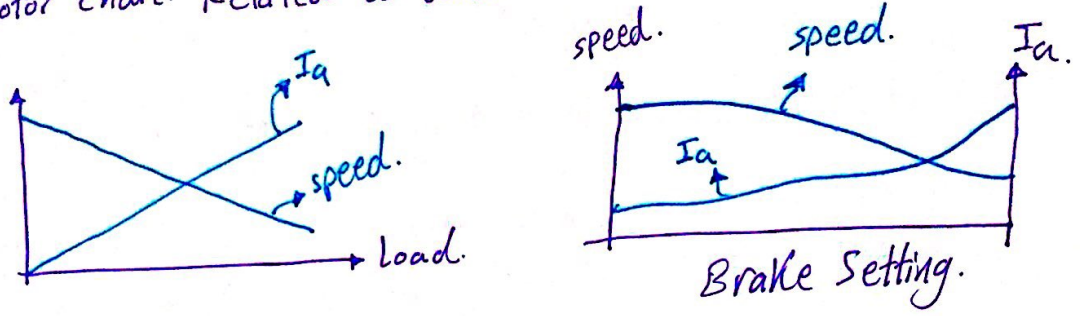

* Overshoot: overshoot = Peak - steady state

* Doubling the gain speeds-up the response.

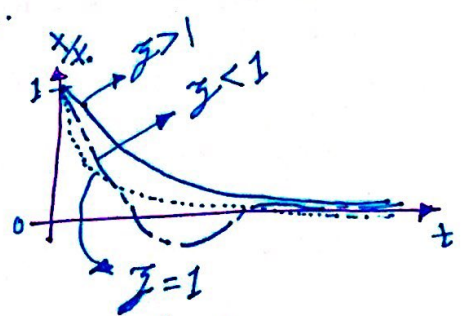* System Behavior: $\left\{ \begin{array}{l} \text{Critical Damping } (\zeta = 1) \\ \text{over Damping } (\zeta > 1) \\ \text{Under Damping } (\zeta < 1) \end{array} \right.$




• Velocity Feedback:

* all practical motor have constant friction called: coulomb friction.
 ↳ also an increased amount of friction force called: striction.
 ↳ the minimum input below which the system won't respond called: Dead-Band. "it is reduced when the gain is high".

* Dead beat response occur just when the motor does NOT reverse.
 * Reversing polarity of Velocity make the system Unstable.

• Speed Control System:

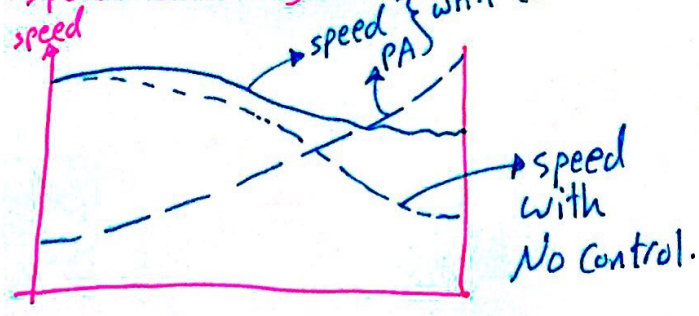

• Digital shaft position sensing:

* Two Types of encoders:
↳ Absolute Encoder. → use Gray Code.
↳ Incremental Encoder.

↳ called incremental because the generation of a pulse indicates an incremental change in position.

* Analogue Unit:


- Fault switches: these enable faults to be introduced. if No fault, all switches should be down.
- Error Amplifier: Combine potentiometer signals to provide the error.
- P_1 & P_2 : provide system gain control & tachogenerator signal adjustment.
- Power Amplifier (PA): Drives the motor.
- Motor: Mech. unit & drives the brake disc & tachogen. directly
- Brake Disc & Magnet: provide an adjustable load for the motor.
- Tachogen.: provide voltage proportional to motor speed.
- P_3 : Can be linked to any input to provide an adjustable input to the error amplifier.
- Controller: Contain OP-amps with associated networks to enable various compensating & control ccts.

* * *

* Fuzzy Logic Control:

- Fuzzy logic controllers are widely used to operate the automatic functions of washing machines, video recorders, CD's, air conditioning systems, cameras.
- Main Purpose of fuzzy: Power Saving.

* Fuzzy controller:

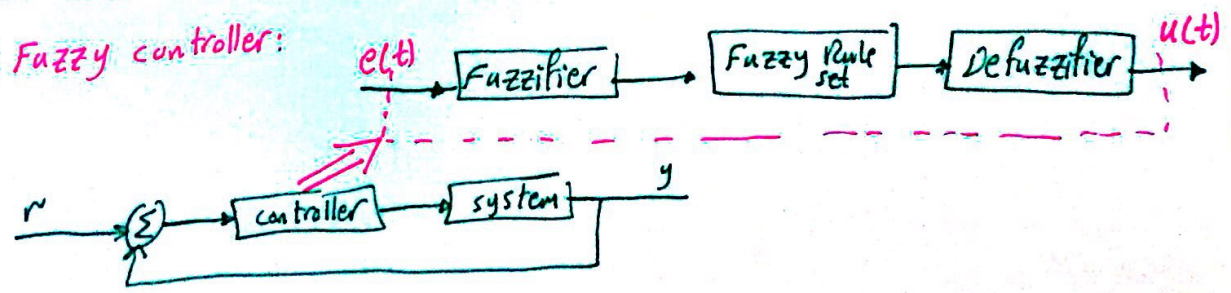

• Fuzzy Logic Operators:
 → AND gives Minimum.
 → OR gives Maximum.
 → NOT gives Complement.

• Classification of the fuzzy Control Law:


- 1) Large -ve control (-10V).
- 2) Medium -ve Control (-5V).
- 3) Small control (Zero).
- 4) Medium +ve Control (5V).
- 5) Large +ve control (10V).

• Some Abbreviations: LN ≡ Large Negative, LP ≡ Large Positive, S ≡ Small, MN ≡ Medium Negative, MP ≡ Medium Positive.

• Voltage Range is $0 \leq V \leq 10$ why?!

$V \geq 0$ since the pump can't suck water out of the tanks so it shouldn't be less than 0.
 $V \leq 10$ since the pump max. speed is achieved with 10 volt, so it shouldn't be greater.

* Fuzzy Membership :

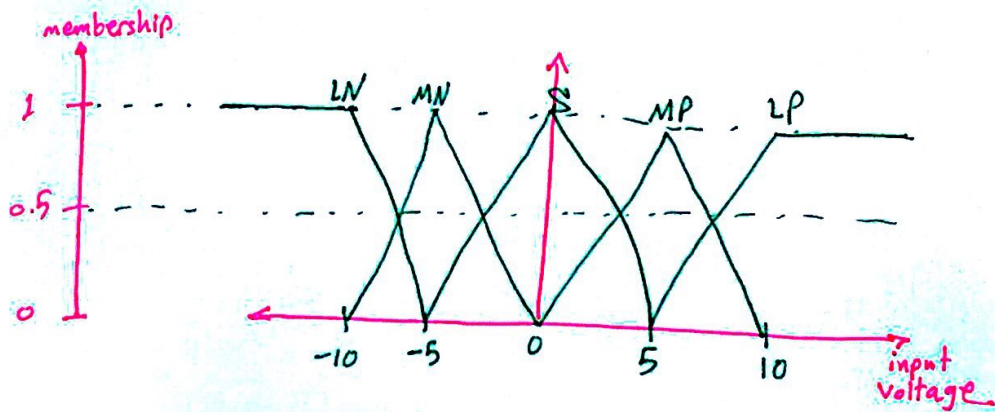

Best of Luck.