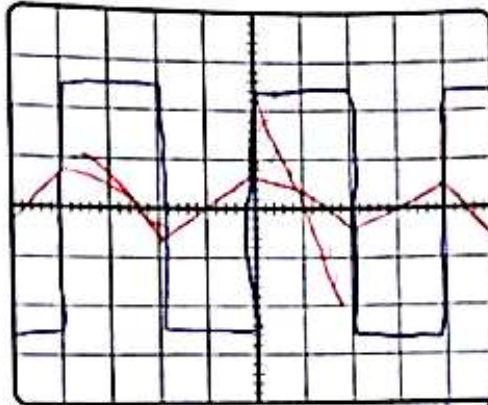


Operational Amplifier Applications (2)

Part A: The Inverting Integrator circuit




5- Comment on the output signal and its relation to the input signal.


..... the output signal is the ^{inverted} integral of the input signal
.....

Part B: The Inverting Differentiator circuit


Sine wave input signal

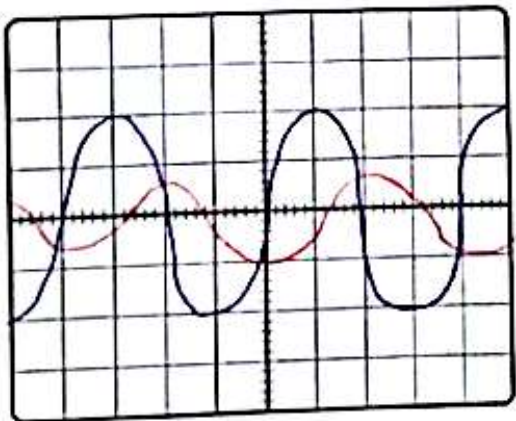

Triangle wave input signal

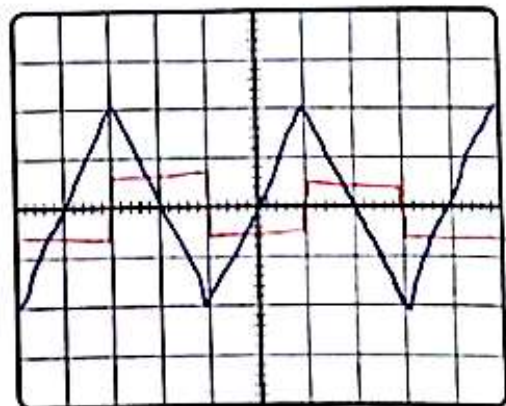


Square wave input signal

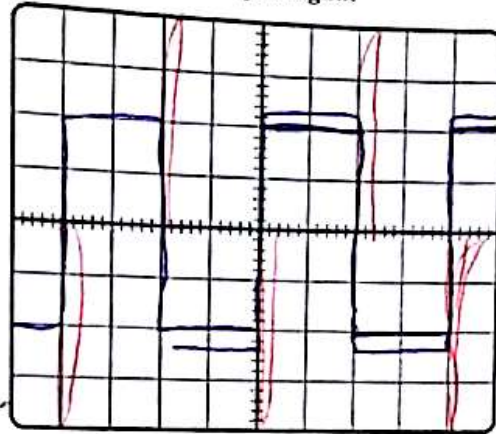

5- Comment on the output signal and its relation to the input signal.

The output signal is the inverted differential of the input signal.

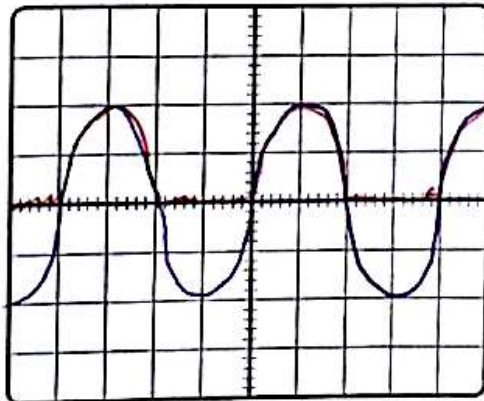
Part C: The Half wave Precision Rectifier circuit



5- What is the main difference between the rectified signals if we use Op-amp instead of using diode only as in Exp2?

In the diode experiment, there is a difference of V_D between output and input and in the op-amp, they are exactly the same.

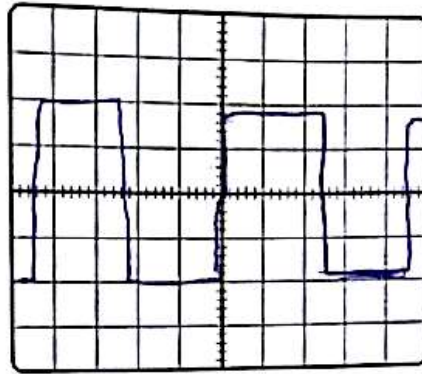Part D: The Square Wave generator circuit




3- Measure the frequency of the output signal from the scope screen and compare it with the calculated frequency.

$(4.5 \times 500 \mu s) = 2.25 \text{ ms}$ ^{measured} $\left\{ \begin{array}{l} T = 2RC \ln\left(\frac{2R_2}{R_1} + 1\right) \\ = 2 \cdot 10K \cdot 0.1 \mu \ln\left(\frac{2 \cdot 15K}{15K} + 1\right) \\ T = 4.55 \text{ ms} \end{array} \right.$

4- Explain how can we change the frequency of the output signal?

... by changing the resistors and capacitance

Part E: The Sine Wave Oscillator circuit

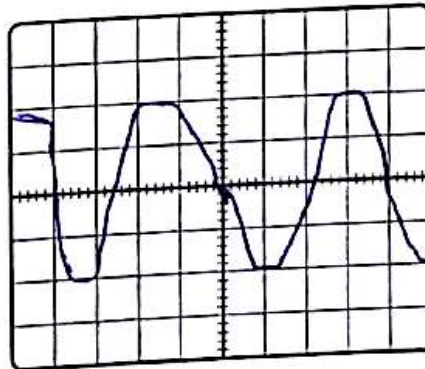

3- Measure the frequency of the output signal from the scope screen and compare it with the calculated frequency.

$f = 1538.46$ ^{measure} $\left\{ \begin{array}{l} \text{calculated} \\ f = \frac{1}{2\pi RC} = \frac{1}{2 \cdot \pi \cdot (10K) \cdot (0.1 \mu)} \\ = 1591.54 \end{array} \right.$

4- Explain how can we change the frequency of the output signal?

... by changing R_1 & C_1