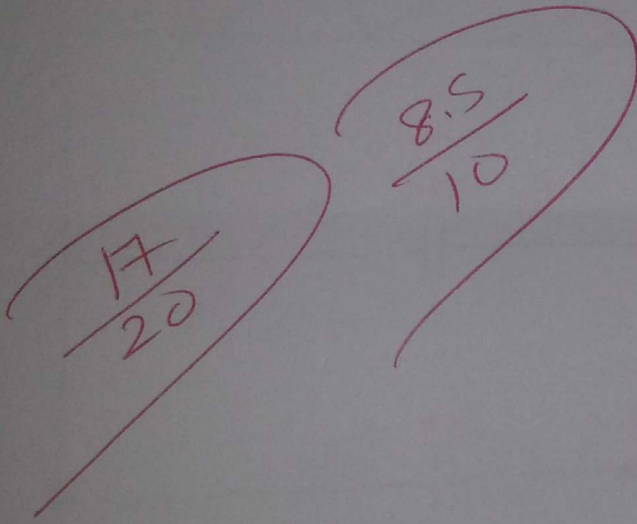


University of Jordan

Electrical Engineering Department

Power lab

Experiment No. 1



Done by Mohammed Zaidme

0136600 - 1. محمد زياد العجيل قوسه

0134757

- 2. يوسف نزال القريع

0134546

- 3. كريمة عيسى

0134069

- 4. احسان داود العبادي

0134062

- 5. محمد هادي

البياس 110 C

(A) : Voltage Distribution Over a String of Suspension Insulators

* Objectives :-

- to study the voltage distribution over a string of suspension insulators.
- to determine the string efficiency.
- to find out how the voltages distribution can be equalized.

* Theory :

Introduction
-3-

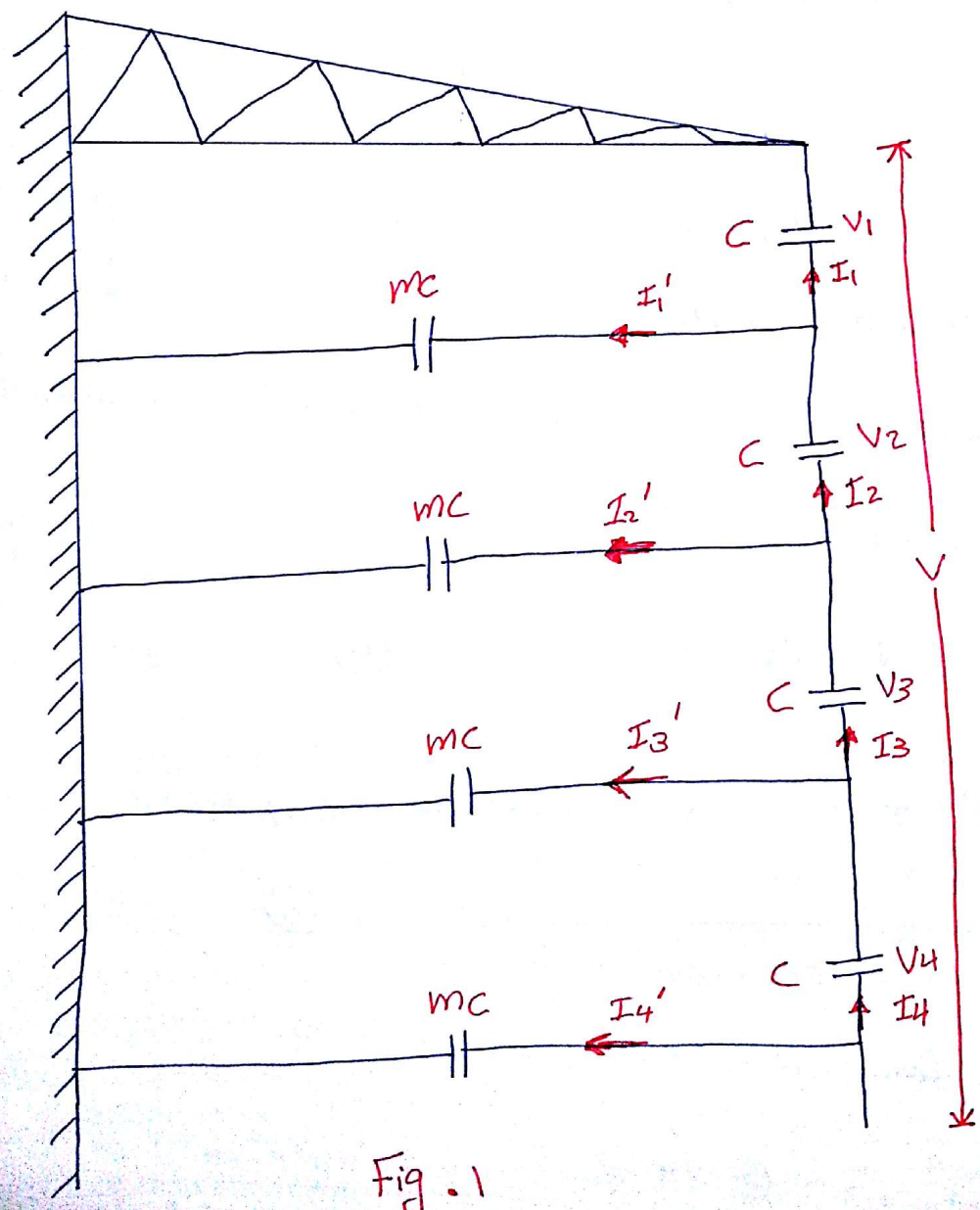


Fig. 1

* the relations between voltages in Fig. 1 are as follows :

$$* I_2 = I_1 + I_1'$$

$$j\omega C V_2 = j\omega C V_1 + j\omega C m V_1$$

$$V_2 = V_1 (1+m) \text{ ———— (1)}$$

$$* I_3 = I_2 + I_2'$$

$$j\omega C V_3 = j\omega C V_2 + j\omega C m (V_1 + V_2)$$

$$V_3 = V_1 (1+m) + m V_1 + m(m+1) V_1$$

$$V_3 = V_1 (1+3m+m^2) \text{ ———— (2)}$$

$$* I_4 = I_3 + I_3'$$

$$j\omega C V_4 = j\omega C V_3 + j\omega C m (V_1 + V_2 + V_3)$$

$$V_4 = V_3 + m V_1 + m V_2 + m V_3$$

$$V_4 = V_1 (1+3m+m^2) + m V_1 + m V_1 (1+m) + m (V_1) (1+3m+m^2)$$

$$V_4 = V_1 (1+6m+5m^2+m^3) \text{ ———— (3)}$$

$$* \text{Knowing that : } V = V_1 + V_2 + V_3 + V_4 \text{ ———— (4)}$$

$$\text{Then } V = V_1 + (m+1) V_1 + (m^2+3m+1) V_1 + (m^3+5m^2+6m+1) V_1$$

$$* \underline{\text{So}} : V_1 = \frac{V}{4 + 10m + 6m^2 + m^3} \text{ ———— (5)}$$

* in the same way we can find V_2 & V_3 & V_4 :

$$\textcircled{6} V_2 = \frac{V(1+m)}{4 + 10m + 6m^2 + m^3}$$

$$\textcircled{8} V_4 = \frac{V(1+6m+5m^2+m^3)}{4 + 10m + 6m^2 + m^3}$$

$$\textcircled{7} V_3 = \frac{V(1+3m+m^2)}{4 + 10m + 6m^2 + m^3}$$

$$\eta \text{ efficiency} = \frac{\text{Voltage across the string}}{N * \text{Voltage across the unit adjacent the live}}$$

$$\eta = \frac{V_1 + V_2 + V_3 + V_4}{4 * V_4} = \frac{4 + 6m + 6m^2 + m^3}{4(1 + 6m + 6m^2 + m^3)} \quad (9)$$

* the voltages are distributed in not uniform way, but there's two way to control the voltage distribution :

1] Grading of the units :

- in this method we take different values of capacitors, $C_4 > C_3 > C_2 > C_1$

- The voltage across lower units will be reduced while the voltage on the top units will be increased.

- For perfect grading $V_1 = V_2 = V_3 = V_4$

* Find the value of the capacitor to satisfy the perfect grading :

$$* V_1 = V_2$$

$$\frac{I_1}{j\omega C_1} = \frac{I_2}{j\omega C_2} = \frac{I_1 + I_1'}{j\omega C_2} = \frac{I_1}{j\omega C_2} + \frac{j\omega C_m V_1}{j\omega C_2}$$

$$\text{- but: } V_1 = \frac{I_1}{j\omega C_1} \text{ then: } \frac{I_1}{j\omega C_1} = \frac{I_1}{j\omega C_2} + \frac{m C_1 I_1}{j\omega C_1 C_2}$$

$$\text{- So: } \boxed{C_2 = C_1 + m C_1}$$

* $V_2 = V_3$

$$\frac{I_2}{j\omega C_2} = \frac{I_3}{j\omega C_3} = \frac{I_2 + I_2'}{j\omega C_2} = \frac{I_3}{j\omega C_3} + \frac{j\omega C_m (V_1 + V_2)}{j\omega C_3}$$

- but: $V_2 = \frac{I_2}{j\omega C_2}$ then: $\frac{I_2}{j\omega C_2} = \frac{I_2}{j\omega C_3} + \frac{2mC I_2}{j\omega C_3 C_2}$

- So: $C_3 = C_2 + 2mC$

* $V_3 = V_4$

$$\frac{I_3}{j\omega C_3} = \frac{I_4}{j\omega C_4} = \frac{I_3 + I_3'}{j\omega C_4} = \frac{I_3}{j\omega C_4} + \frac{j\omega C_m (V_1 + V_2 + V_3)}{j\omega C_4}$$

- but $V_3 = \frac{I_3}{j\omega C_3}$ then $\frac{I_3}{j\omega C_3} = \frac{I_3}{j\omega C_4} + \frac{3mC I_3}{j\omega C_3 C_4}$

- So: $C_4 = C_3 + 3mC$

* From all this we find that:

$$C_n = C_{n-1} + (n-1)mC \quad (10)$$

where: $C_n \equiv$ the capacitance of the n^{th} unit

$C_{n-1} \equiv$ the capacitance of the lower unit

$mC \equiv$ capacitance of the ground

* Using different type of capacitor is complex and hard to maintain so we need another method.

AC Shielding :

Here we control the voltages by employing a guard ring which usually takes the form of large metal ring surrounding the bottom unit & connected to the line as shown in Fig. 2

- this ring increases the capacitance between the ^{line} ~~work~~ & the metal work .

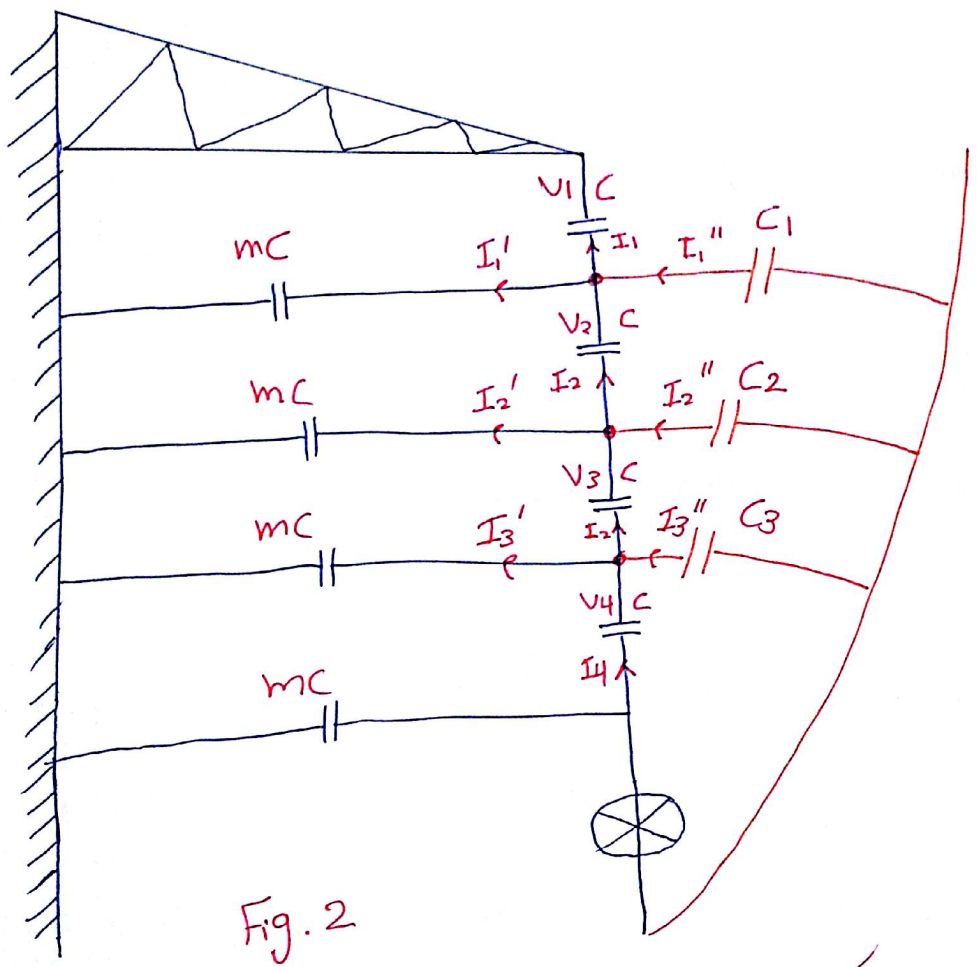


Fig. 2

* Finding the value of the capacitor to satisfy $V_1 = V_2 = V_3 = V_4$

* $I_2 = I_1 + I_1' + -I_1''$

$j\omega C V_2 = j\omega C V_1 + j\omega m C V_1 - j\omega C_1 V$

$V = V_1 + V_2 + V_3 + V_4$, then: $C = C + mC - 3C_1$

$C_1 = \frac{mC}{3}$ (a)

* $I_3 = I_2 + I_2' + -I_2''$

$j\omega C V_3 = j\omega C V_2 + j\omega m C (V_1 + V_2) - j\omega C_2 V$

$V = V_2 + V_3$, then: $C = C + 2mC - 2C_2$

$C_2 = 2mC/2$ (b)

* $I_4 = I_3 + I_3' + -I_3''$

$j\omega C V_4 = j\omega C V_3 + j\omega m C (V_1 + V_2 + V_3) - j\omega C_3 V$

$V = V_3$, then: $C = C + 3mC - C_3$

$C_3 = 3mC$ (c)

* From all above we can find that:

where $N \equiv$ number of units

$$\left. \begin{aligned} C_1 &= mC / (N-1) \\ C_2 &= 2mC / (N-2) \\ C_3 &= 3mC / (N-3) \end{aligned} \right\} \text{(ii)}$$

Table (1) : Determination of Voltage Distribution :

V / mC	0	0.22 μF	0.47 μF	0.69 μF
V_1	25.61V	20.32V	16.13V	14.55V
V_2	25.35V	22.8V	19.31V	18.8V
V_3	25.29V	26V	26.5V	28.8V
V_4	25.6V	33V	39.5V	48.1V

Table.1 measured value

* using equations number 5, 6, 7 & 8 to calculate the voltage Distribution theoretically :

For $mC = 0$	For $mC = 0.22 \mu F$	For $mC = 0.47 \mu F$	For $mC = 0.69 \mu F$
$V_1 = 27.5$	$V_1 = 21.72$	$V_1 = 17.12$	$V_1 = 14.14$
$V_2 = 27.5$	$V_2 = 23.81$	$V_2 = 20.4$	$V_2 = 18.63$
$V_3 = 27.5$	$V_3 = 28.46$	$V_3 = 28.8$	$V_3 = 28.91$
$V_4 = 27.6$	$V_4 = 35.87$	$V_4 = 43.17$	$V_4 = 48.27$

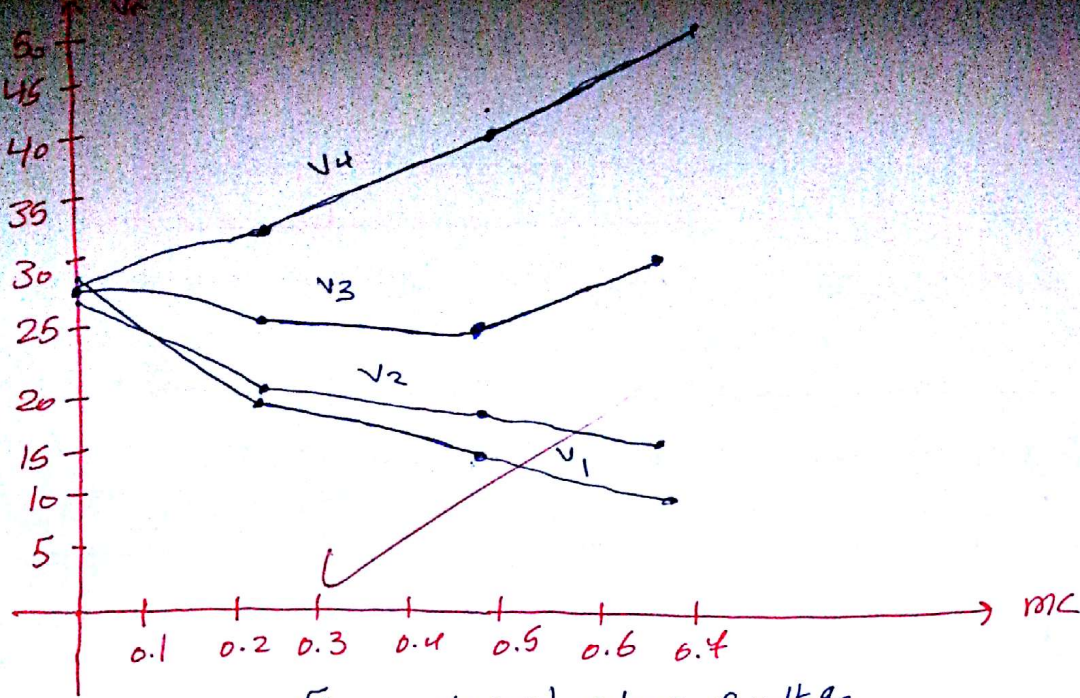


Fig. 3 Measured values of voltage due to different MC value

* String efficiency : using equation number (9)

For $mc = 0$	For $mc = 0.22 \mu F$	For $mc = 0.47 \mu F$	For $mc = 0.69 \mu F$
$\eta = 100\%$	$\eta = 76.63\%$	$\eta = 58.95\%$	$\eta = 55.95\%$

* Procedure (2) :- Voltage control using static shielding

- taking $mc = 0.47 \mu F$ & $N = 4$

- calculating C_1, C_2 & C_3 by equation (11)

$$C_1 = 0.154 \mu F$$

$$C_2 = 0.47 \mu F$$

$$C_3 = 1.41 \mu F$$

- then we connect the capacitors C_1 & C_2 & C_3 as guard ring

ring the Voltage Distribution we get :

$$\begin{aligned} V_1 &= 27.86 \text{ V} \\ V_2 &= 27.7 \text{ V} \\ V_3 &= 27.7 \text{ V} \\ V_4 &= 27.7 \text{ V} \end{aligned}$$

that show that the static shielding helps the voltage distribution to be almost uniform

* trying the grading method :

- take $mc = 0.22$ & $C_1 = 2.2 \mu\text{F}$

- $C_1 = 2.2 \mu\text{F}$

$C_2 = C_1 + mc = 2.42 \mu\text{F}$

$C_3 = C_2 + 2mc = 2.86 \mu\text{F}$

$C_4 = C_3 + 3mc = 3.52 \mu\text{F}$

- $V_1 = 27.92 \text{ V}$

$V_2 = 27.23 \text{ V}$

$V_3 = 26.83 \text{ V}$

$V_4 = 28.79 \text{ V}$

* It's show that grading method give an un-uniform Distribution because of the imperfection deviations.

* PART (B) : I-t characteristics of wire Fuse in the over current zone

* objectives :

-to find the relationship between current in the Fuse and the time needed by the Fuse

* Procedure :

Measurement No	Input voltage (V)	Primary current Fuse 1/25 (A)	Time (Sec)
1	130	0.28	> 200
2	135	0.3	> 200
3	140	0.31	> 160
4	150	0.33	67.12
5	160	0.36	2.24
6	170	0.4	2.06
7	180	0.42	1.96
8	190	0.46	1.46
9	200	0.46	1.26
10	210	0.49	1.06

Table .3

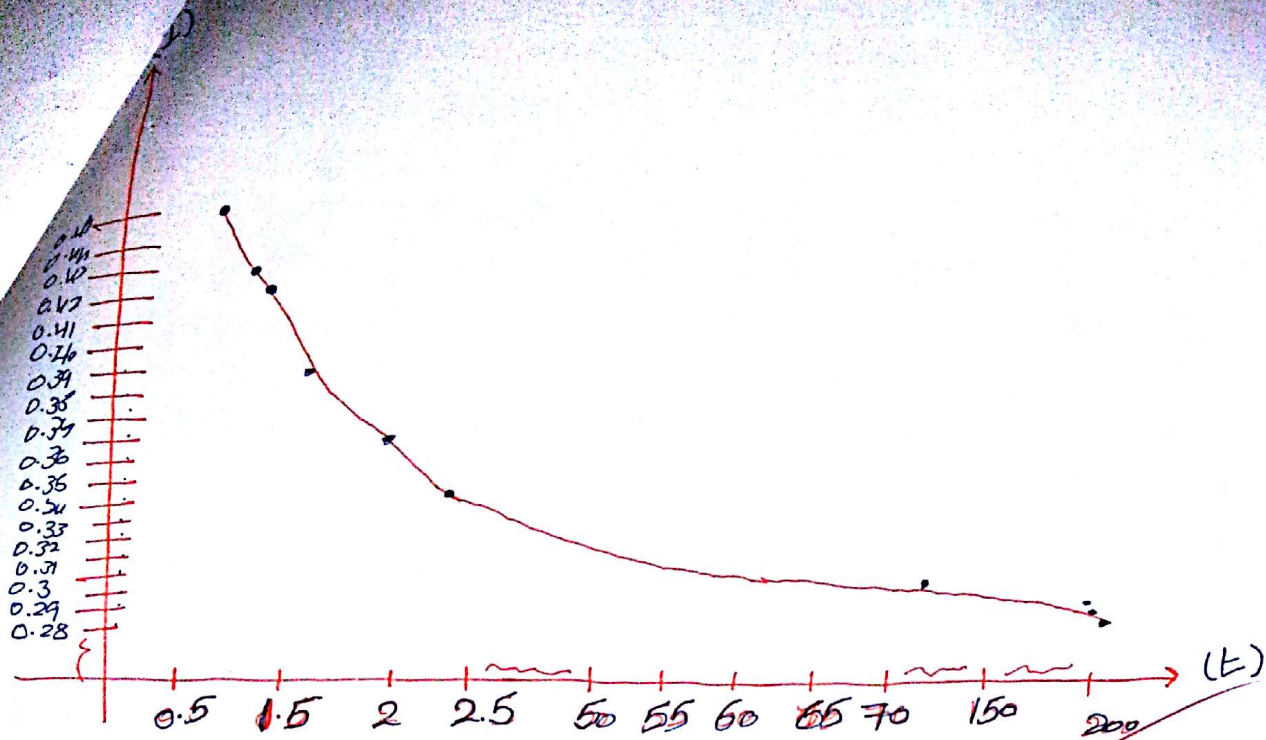


Fig No. 4

* From the table.3 and Fig No.4 we find that the time needed by the Fuse to interrupt the circuit is Inversely proportional that is as the fault increase the operating time decreases, which is the fundamental property in the fuse which lead to its use in protection the circuit from the fault.

* rating current is the maximum current the Fuse can stand & still work for it, in our procedure rating current calculated as follow :

$$I_{\text{rating}} = I_{\text{sec}} * I_{\text{rel}} = 0.3 * 25 = 7.5 \text{ A}$$

- The END -

Exp (i)

Measure of the & -ve and zero seq cont

- 1- محمد رضا اعين
- 2- يزن عوف
- 3- محمد هوريه
- 4- احمد عياض

done by the group

6/10


Exp(2)

Measurement of symmetrical component of current in unbalanced system.

Objective

To measure the zero, positive and negative current for 3-phase unbalanced system.

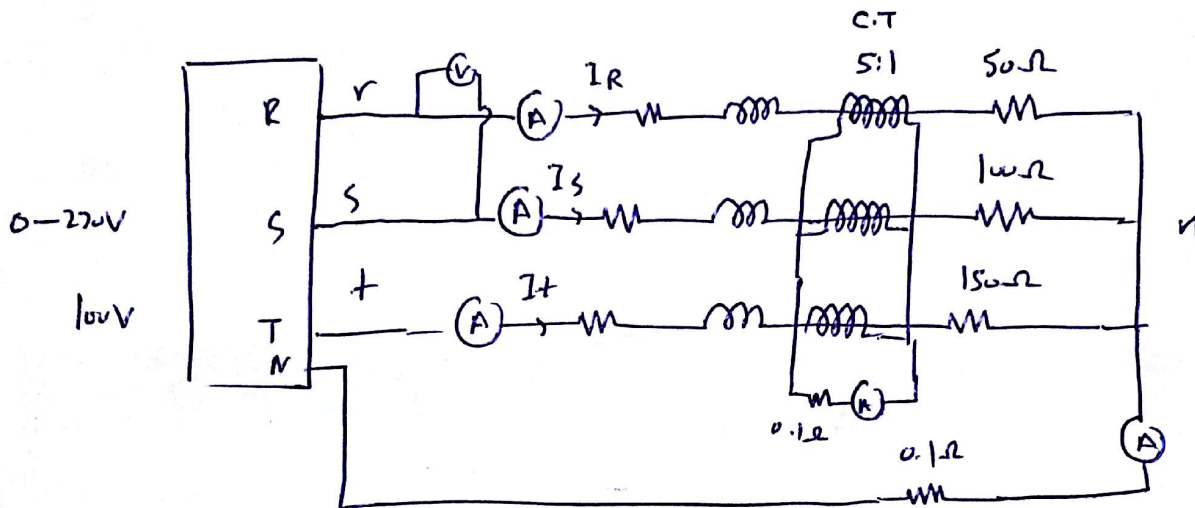PART (A) : Measurement of zero sequence current :



$$I_R = 1.05 \angle \theta \text{ In phase with } V_{RN}$$

$$I_{CT} = 0.11$$

$$I_S = 0.55 \angle 120^\circ \text{ with } V_{RN}$$

$$I_T = 0.4 \angle 240^\circ \text{ with } V_{RN}$$

$$I_N = 0.62$$

\Rightarrow Now disconnect R_N ;

$$V_{RN} = 0.1 \times I_N = 0.062V = 37^{(2)} R_N$$

$$I_{CT} = \frac{1}{5} I_N = \frac{0.62}{5} = 0.11$$

$$I^{(0)} = \frac{I_N}{3} = \frac{0.62}{3} = 0.2$$

$$I^{(0)} = 2 \times I_{CT} = 0.2$$

$\Rightarrow I_N$

* Now disconnect V_n ;

$$I_R = 0.7 \angle 0^\circ$$

$$I_S = 0.59 \angle 135^\circ$$

$$I_T = 0.4 \angle 225^\circ$$

$$I_n = 0$$

$$I_{CT} = 0$$

$$V_{Nn} = V^{(0)} = ~~0.533~~ 18V$$

* Conclusion from first part:

[1] we find the The Relation between I_{CT} & I_{Nn} & $I^{(0)}$ is:

$$[1] I^{(0)} = \frac{I_{Nn}}{3} = 0.11$$

$$[2] I_{CT} = \frac{1}{5} I_{Nn} = 0.11$$

$$[3] I^{(0)} = 2 \times I_{CT} = 0.22$$

$$\Rightarrow I^{(0)} = \frac{1}{3} I_{Nn} = \frac{1}{3} (I_R + I_S + I_T)$$



[2] when we disconnect V_n

$V_{Nn} = V^{(0)} = 18$ The V_{Nn} equal to zero seq voltage.

$$[3] V^{(0)} = \frac{1}{3} (V_a + V_b + V_c)$$

$$[V_{012}] = [A]^{-1} [V_{abc}]$$

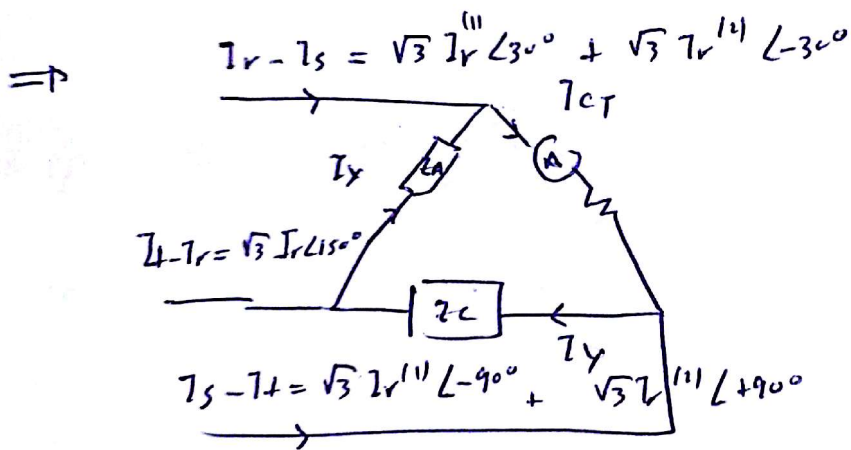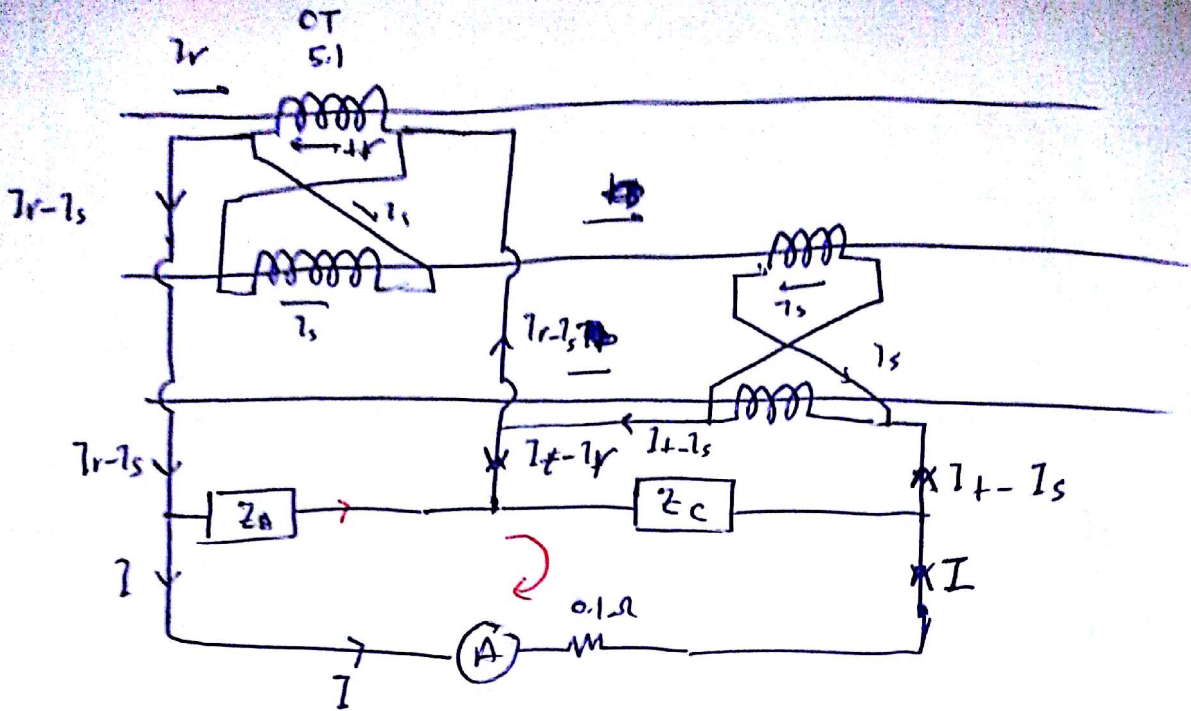* Prob B: Measure of positive & negative seq current



$$I_x Z \angle 30^\circ + I_y Z \angle -90^\circ + 0.1 I_{CT} = 0$$

$$(-\sqrt{3} I_r^{(1)} \angle 30^\circ + I_{CT}) Z \angle 30^\circ + (I_{CT} + \sqrt{3} I_r^{(1)} \angle 90^\circ) Z \angle 90^\circ + 0.1 I_{CT} = 0$$

$$\Rightarrow -\sqrt{3} Z I_r^{(1)} \angle 60^\circ + Z I_{CT} \angle 30^\circ + Z I_{CT} \angle -90^\circ + \sqrt{3} Z I_r^{(1)} \angle -180^\circ + 0.1 I_{CT} = 0$$

$$\Rightarrow -\sqrt{3} Z I_r^{(1)} \angle 60^\circ + \sqrt{3} Z I_r^{(1)} \angle -180^\circ = (-Z \angle 30^\circ - Z \angle 90^\circ) I_{CT}$$

$$\Rightarrow 3 Z I_r^{(1)} \angle 210^\circ = -Z \angle -30^\circ I_{CT} = +Z \angle +150^\circ I_{CT}$$

$$\Rightarrow I_{CT} = 3 I_r^{(1)} \angle 60^\circ \quad \# \text{ Final ans}$$

The second prove if we interchange Z_A & Z_C

$$I_x Z \angle -90 + I_y Z \angle 30 + 0.1 I_{CT} = 0$$

$$(-\sqrt{3} I_r^{(2)} \angle -30^\circ) (Z \angle -90) + (I_{CT} + \sqrt{3} I_r^{(2)} \angle 90) Z \angle 30 + 0.1 I_{CT} = 0$$

$$-\sqrt{3} Z I_r^{(2)} \angle -120 + Z I_{CT} \angle -90 + Z I_{CT} \angle 30 + \sqrt{3} Z I_r^{(2)} \angle 120 + 0.1 I_{CT} = 0$$

$$-\sqrt{3} Z I_r^{(2)} \angle -120 + \sqrt{3} Z I_r^{(2)} \angle +120 = (-Z \angle -90 - Z \angle 30) I_{CT}$$

$$3 Z I_r^{(2)} Z \angle 90 = Z \angle 150 I_{CT}$$

$$I_{CT} =$$

$$I_{CT} = 3 I_r^{(2)} Z \angle -60^\circ$$

* Some conclusion :

(i) The value of I_{CT} before and after interchange Z_A & Z_C and phase by 180°

(ii) If N-n is removed then the value of zero ^{seq.} current will be zero

⇒ The CT on R will measure the value of the seq current

⇒ The CT on T will measure the -ve seq

⇒ The CT on S phase is not required to measure the & -ve seq.

$$(iii) I_{CT} = 0.28 Z \angle 30^\circ$$

After Interchng

$$I_{CT} = 0.28 Z \angle -172^\circ$$

After Interchng

Experiment 3

Current Voltage and Power Relations

Across A Transmission Line



0158725
0125516
0120387
0129573
0091734

محمد الحكيم
خلاد محمد
اسراء الشرد
المولود
ابراهيم عايد

Discussion:- To determine The parameters. of the short and medium length Lines
And to investig voltage, current and Power relations at Both ends
Under no load and Load conditions.

Procedure :-

1:- open circuit test

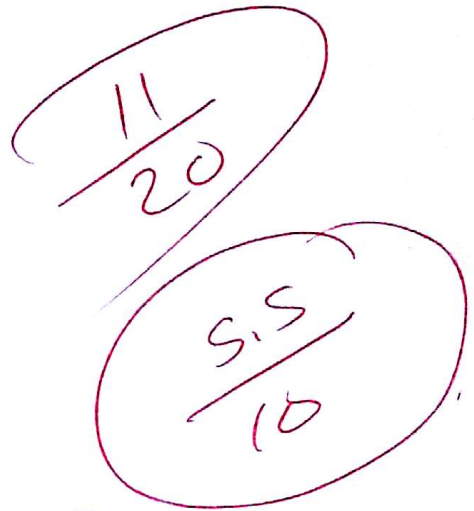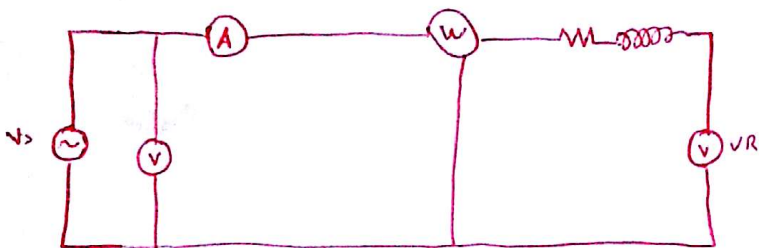

1) set V_s To 25, 50, 75, 100

2) take The readings of V_s and V_R and I_s, W and find the phase shift

3) Find A, C constants.

$$V_s = AV_R + BI_R$$

$$I_s = C V_R + DI_R$$

$$A = \frac{V_s}{V_R} \dots \text{①}$$

$$C = \frac{I_s}{V_R} \dots \text{②}$$

V_s	25	50	75	100
V_s	25.92	50.61	75.38	99.77
I_s	0	0	0	0
Power	0	0	0	0
V_R	25.92	50.62	75.37	99.76
Phase shift	0	0	0	0
A	1.0003	1.001	1.0001	1.0001
C	0	0	0	0

*since I am working on an open circuit Then The current will be zero



Circuit test :-

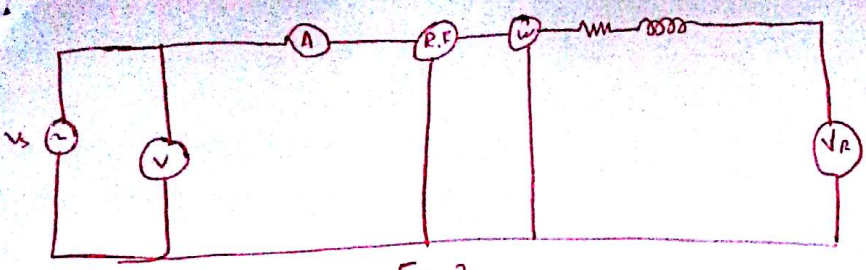


Fig. 2.

- 1) increase V_s very slowly Adjusting I_R to 1A And take the readings V_s, I_s, W, I_R , Phase shift and $I_R(I_s)$
- 2) Repeat For $I_R = 2, 3, 4$
- 3) calculate B, D

$V_s = AV_R + BI_R$

$I_s = CI_R + DI_R$

$V_R = 0$

$B = \frac{V_s}{I_R}$

$D = \frac{I_s}{I_R}$

I_R	0.5	1	1.5	2
V_s	13.3	28.2	41	60.9
I_s	0.479	0.99	1.443	1.96
W	0.463	1.03	3.58	6.273
I_e	0.479	1.09	1.463	1.96
Phase shift	62.5	54.7	51.5	51.8
B	27.76	27.38	28.07	31.07
D	1	0.961	1.02	1



B.1 ~~Circuit~~ ^{open} circuit test For medium Transmission Line.

1) Adjust V_s to 25, 50, 75, 100V and measure $V_s, I_s, W, I_{c1}, I_{c2}, V_R$ and the phase shift

$A = (\frac{Y}{2}Z + 1)$

$B = Z\alpha$

$C = Y(\frac{Y}{4}Z + 1)$


$D = (\frac{Y}{2}Z + 1)$

* Calculate A, C Parameters.

at the open ckt test

$A = \frac{V_s}{V_R}$

$C = \frac{I_s}{V_R}$

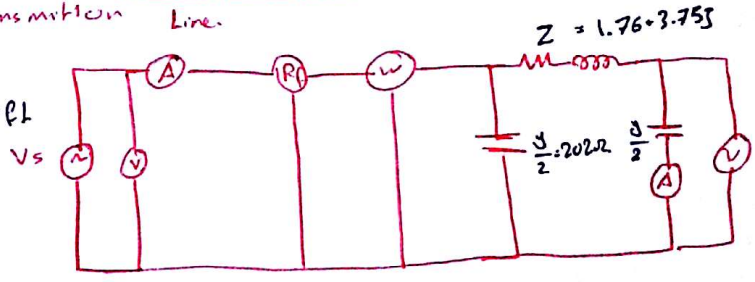

V_s	25	50	75	100
V_s	24.77	50.7	74.6	100.4
I_s	0.196	0.325	0.478	0.644
W	7.161	7.204	7.075	7
V_R	26.37	54.17	79.8	107.4
I_{c1}	0.07	0.15	0.22	0.29
I_{c2}	0.07	0.15	0.22	0.29
A	0.94	0.936	0.934	0.935
C	7.471mA	6×10^{-3}	6×10^{-3}	6×10^{-3}

as we see here V_R is larger than V_s
This is due to the capacitor C_1 .

At test for medium transmission line:-


increase V_s slowly to set I_R to

1, 1.5, 2 A

2) take the readings of $V_s, I_s, W, V_R, I_{c1}, I_{c2}$

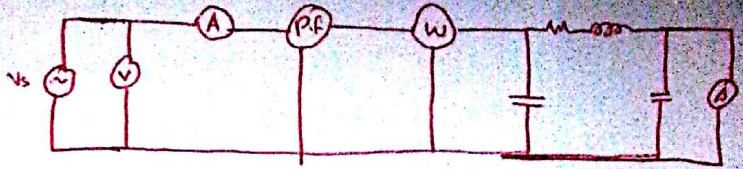
3) calculate B, D constants

$$B = \frac{V_s}{I_R} \quad / \quad D = \frac{I_s}{I_R}$$



I_s	0.5	1	1.5	2
V_s	15.4	33	46.1	64.3
I_s	0.505	1.08	1.508	1.9
W	0.715	2	4.8	6.9
I_R	0.541	1.17	1.639	2.134
I_{c1}	0.03	0.04	0.13	0.17
I_{c2}	0.01	0.01	0.01	0.02
B	28.46	28.2	28.1	28
D	0.933	0.923	0.92	0.89

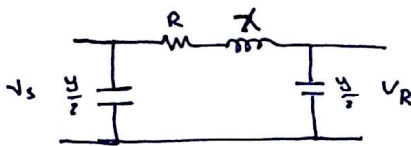The equivalent ckt of the medium transmission line is:-



$$B = Z = 28.2 \Omega$$

$$D = \left(\frac{Y}{2} Z + 1 \right) \Rightarrow \frac{Y}{2} = 2.836 \times 10^{-3}$$

Operating at No Load:-

1) adjust V_s to 100 V (L-N)

2) Take the readings of V_s, I_s, V_R


3) adjust X_L to the max

4) keep V_s const and Adjust X_L until

$$V_L = V_s = 100 \text{ V}$$

5) take I_L and calculate X_L

6) comment on I_L value

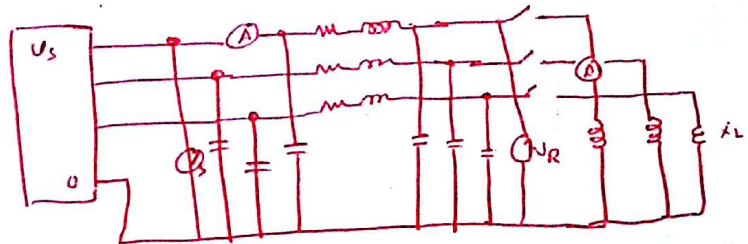

	V_s	I_s	V_R	I_L	X_L
(1)	100	0.668	107	0.26	166.6

(1)


* note that I_L Here (0.26) is the current value that flows through the inductor, because

the SEADA can't measure the current in the inductor. This current exists due to the line resistance and inductance.

I to 2A and the pf to 0.8 by adjusting I_s, I_2 while V_R is 100v

Continuously Adjusting v_s

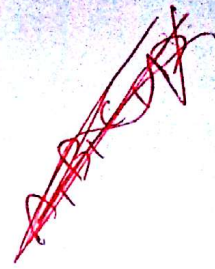- 1) Take the readings of $v_s, I_R, P_R, I_s, V_R, PF$.
- 2) Draw The circle diagram
- 3) Ensure x_c is kept at max and close the switch
- 4) increase I_c to Achieve $v_s, V_R = 100v$
- 5) calculate the VAR injected by x_c
- 6) Explain why I_s increases after shunt compensation.



VAR injected By $x_c = 100 \text{ VAR}$

?

Before compensating						after			
v_s	I_R	P_R	I_s	V_R	PF	x_c	I_c	PF	I_L
99.5	0.442	20.5	0.5	94%	0.813	100 VAR	0.37	0.98	0.43

(2)

Conclusion of this part:- we performed compensating with and without load

We are doing the compensation because at no load or light loads the out volt is smaller than the input and to maintain it we use compensating

* in the no load The load is capacitive so we use an inductive compensating
 ... as it's shown in the first and second table V_R was bigger than v_s at no load and after the compensating it's closer to each other


* we can use capacitors to compensate if the power factor isn't high enough
 * also we can use compensation to increase V_R when it isn't equal to V_R

* I_s increases after the shunt compensation Because we are aiming to achieve the resonance, at the resonance I_s is max.

circle diagrams -4
 Conclusion -1
 RILIC -2

EXP 4

Done by : إيمان العبدى 034069

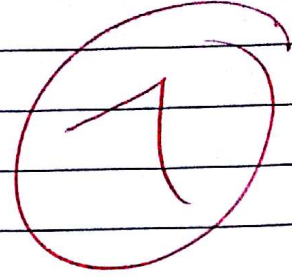

- 034069 إيمان العبدى (1)
- 036600 عبد الرحمن (2)
- 034757 يوسف نفال (3)
- 034062 محمد (4)
- 034540 محمد (5)

5.10/8
0.14/2/17

Reading $S_1 = S_2 = 0, S_3 = 1$

- $V_{st} = 225, -V_{rs} = 225, V_{rt} = 223$
- $V_s = 220, -V_o = 122.7, V_f = 95.9$
- $V_f = 95.5, I_r = 0.72, I_s = 1.15$
- $I_t = 1.62, I_j = 0, I_j = 1.64$

3- with $R_j = 50, S_2 = 2, S_3 = 0$

- $V_{st} = 225, V_{rs} = 225, V_{rt} = 223$
- $V_o = 126.2, V_f = 99, V_f = 0.15$
- $I_r = 1.1, I_s = 1.12, I_t = 0.42$
- $I_{cj} = 1.98, I_{rj} = 2.25, I_j = 0.37$

2- Reading at $S_2 = S_3 = 1, S_1 = 0$

- $V_{st} = 225, V_{rs} = 225, V_{rt} = 223$
- $V_o = 127, V_f = 99.6, V_f = 0.13$
- $I_r = 1.1, I_s = 1.14, I_t = 0.25$
- $I_{cj} = 2, I_{rj} = 2, I_j = 0.29$

Part B Reading : Power system with neutral earthed through a resistance

1- $S_1 = 1, S_2 = S_3 = 1$

- $V_{rs} = 225, V_{rt} = 225, V_{st} = 223$
- $V_i = 99.8, I_t = 2.8, I_s = 1.14$
- $I_r = 1.08, I_{rj} = 2.53, I_{cj} = 1.87$
- $I_j = 2.75$

2- $S_1 = 1, S_2 = 2, S_3 = 1$

- $V_{st} = 225, V_{rt} = 225, V_{rs} = 223$
- $V_o = 122.8, V_f = 96.1, V_f = 95.5$
- $I_r = 0.83, I_s = 1.17, I_t = 1.65$
- $I_{cj} = 1.66, I_j = 1.65$

Part (C) Power system with neutral earthed through a reactor:-

1. $S_1 = 2, S_2 = S_3 = 1, L_o \text{ max}$

- $V_{st} = 225, -V_{rt} = 225, V_{rs} = 223$
- $V_o = 122.8, -V_f = 96.1, V_f = 45.5$
- $I_r = 0.73, I_s = 1.17, I_f = 1.65$
- $I_{cj} = 1.66, -I_j = 1.65$

2. $L_o \text{ min}, I_{L_{min}} = 0.35$

- $V_{st} = 225, V_{rs} = 225, V_{rt} = 223$
- $V_o = 126.2, V_f = 99, V_f = 0.15$
- $I_r = 1.1, I_s = 1.12, I_t = 0.42$
- $I_{cj} = 1.98, I_{rj} = 2.25, I_j = 0.37$

Discussion and Conclusion:-

the relation between I_{Cj} for all position of S_2 :-

① when $S_2 = 0, S_1 = 0, S_3 = 1$ $I_{Cj} = 0$; No current will flow because a sum of currents equal = 0.

② when $S_3 = 1, S_2 = 1 \rightarrow I_{Cj} = 2.26$, In this while $S_1 = 0$
 $I_{Cj} = I_j = 2.6$

③ when $S_3 = 1, S_2 = 2, S_1 = 1$
 $I_{Cj} = 0.99$ A while $I_j = 1.42$ A there are almost equal

④ when $S_3 = 1, S_2 = 1, S_1 = 1$
 $I_j = 2.72, I_{Cj} = 1.87, I_{rj} = 2.53$
So $I_j = I_{Cj} = I_{rj}$

⑤ $V_r = 1.4$ in $S_1 = 0, S_2 = 0, S_3 = 1$ with Isolated neutral.
- $V_r = 50$ with $R_3 = 50, S_1 = 0, S_2 = 1, S_3 = 1$
- $V_r = 105.5$ $S_1 = 1, S_2 = 1, S_3 = 1$ with reactor.

- From all number above we can say that the voltage with neutral is small too because $\Sigma = 0$


- for Resistance + Inductance - Grounding V_r is bigger because summation of voltages not equal to ZERO

⑥ when we add maximum L we reduce the fault current


$I_{rj} =$ Pure Inductive + $I_{Cj} =$ is Pure capacitive

; because they are subtract each other + they not equal exactly



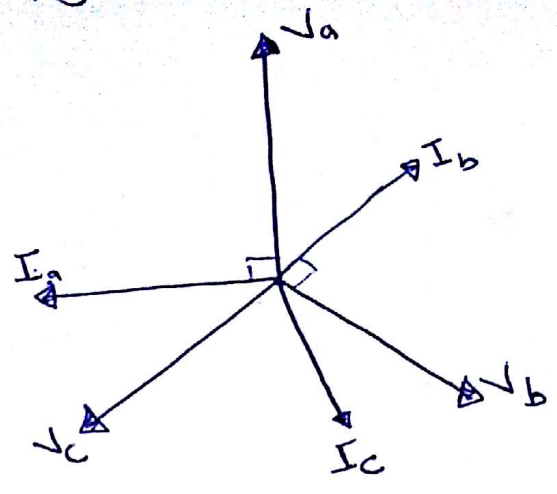
balance load conditions the currents and voltages shown in Fig 1-b & $V_n = V_E$ n: neutral E: earth



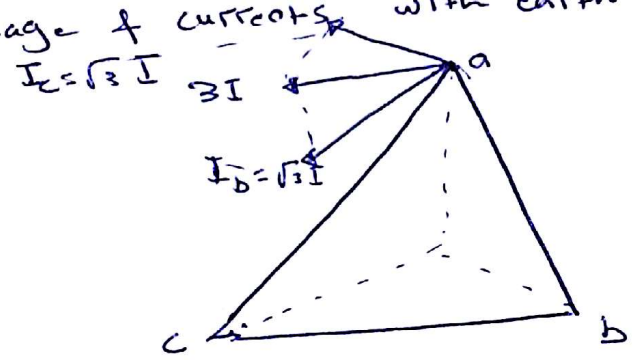* The voltage & currents with earth fault on phase a




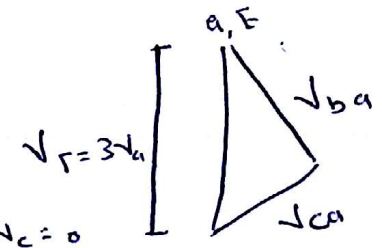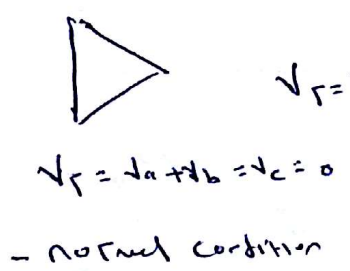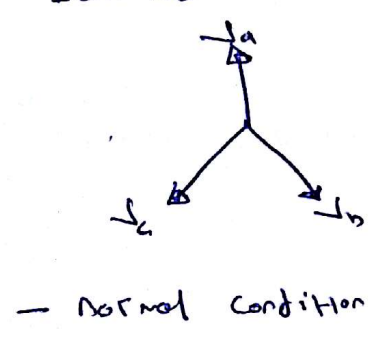* Figures during healthy and faulted conditions for an isolated earthed system




Voltage during fault condition
 $V_f = V_a + V_b + V_c = 3V_a$


solidly earthed system.

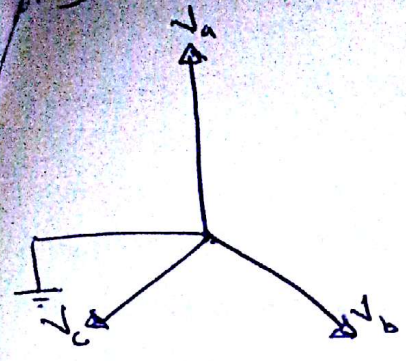

- Voltage during healthy condition

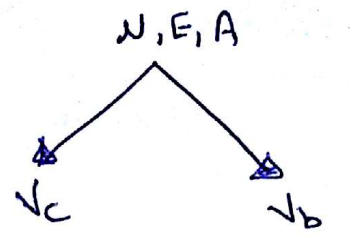


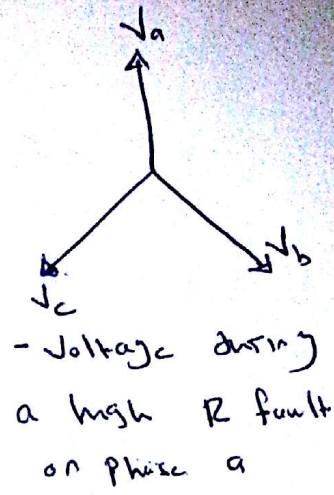+ Voltage during a zero resistance fault on phase 'a'




- Voltage during a high R fault on phase 'a'

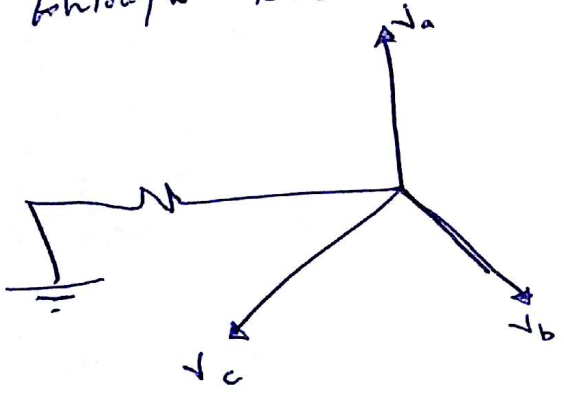* Voltage during healthy & fault condition on a system earthed through resistance




* Voltage during healthy condition

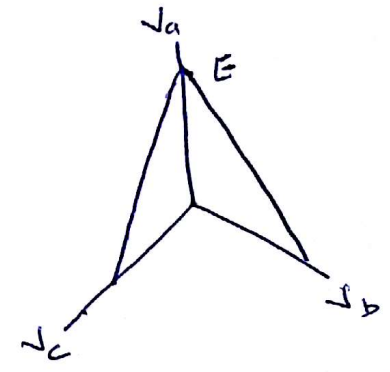

+ during a high R fault in phase 'a'

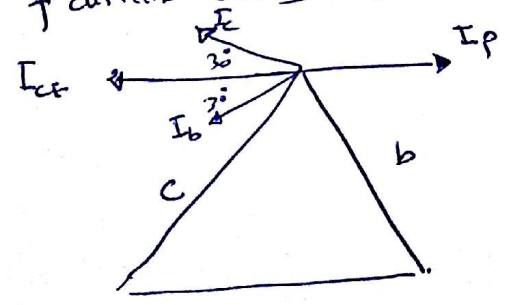voltage & current during fault in phase 'a'



$$I_f + I_{CG} + I_p = 0$$

$$\text{Since } I_{CG} + I_p = 0$$

$$\text{then } I_f = 0$$

+ Conclusion 1.

Following things during exp 2.


- ① is connected to an open delta Transformer to get rid of an residual voltages
- ② when a switches is set to zero position it's means that point left is unconnected.
- ③ In the first part when we have a minimum fault current, this mean that the cct will act as reasonable circuit
- ④ when a fault occurs in part II we notice that the values of the currents, are no longer balanced but instead value will rise however, the increased current is small enough for the system to work satisfactorily and so the fault does not have to be clear immediately
- ⑤ In the 2nd part we first ground the neutral through a reactance X so it's value excessive, this lead to high value of fault current
- ⑥ In the last part, the value of L_0 is adjusted until we obtain a minimum fault current that is the cct becomes a reasonable cct.

Experiment no. 5

Instantaneous Measuring Relays
for ac type RXIG, RXEG

1. Esra' Adel Al-shrouf. 0120387
2. Anwar Salim Awamlah 0129973
3. Muath Ayman 0138725
4. Ala' Awwad 0125516
5. Ibrahim Ayesk 091734

* Prepared by Esra', Anwar, Muath, Ala'

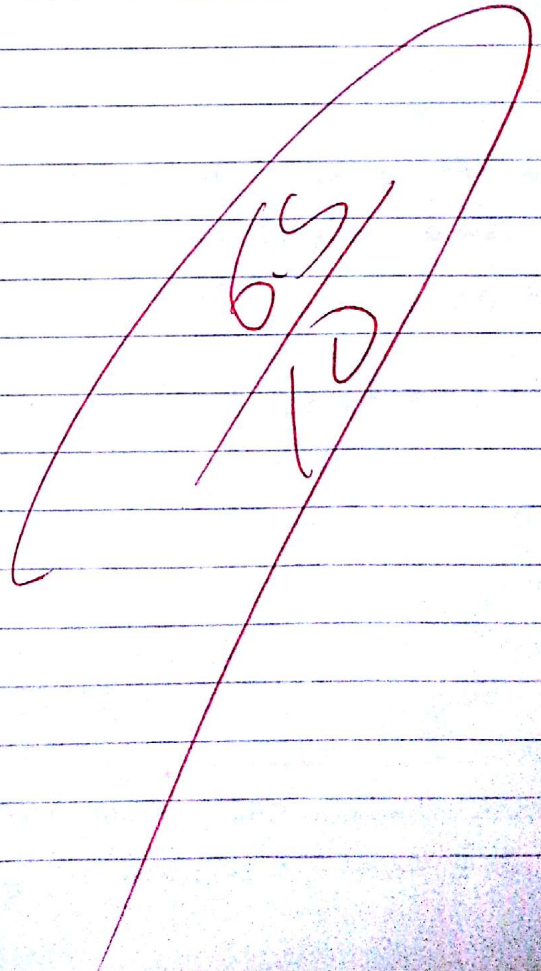

OBJECTIVES

- Recording the operating and resetting values for RXEG 2, RXIG 2 relays.
- Determining the power consumption of the measuring circuit.
- Recording the pick up times of RXEG 2 relay.

THEORY

Description of The Relays :

An auxiliary dc supply is needed because both relays are designed to work for both 50-60 Hz alternating current supply. They are also calibrated for operation at both max & min values. The output is an auxiliary electromagnetic relay.

Current Relay RXIG2:

It can be used as a short-circuit protection for direct-on-line-started induction motor since it's insensitive to the dc component of the short-circuit current.

Providing an air gap in the input transformer achieve the above mentioned characteristic, and also makes the relay suitable for measuring ac current superimposed on dc current.

There's another type of this relay that is sensitive to the dc component. It could have a higher operating value at frequencies above the rated one, high overload capacity and a very high resetting ratio.

Voltage Relay RXEG2:

It can be used at frequencies up to 400 Hz with no variation in the operating value. It's useful for monitoring ac voltage levels because of the high resetting ratio.

PROCEDURE

a) Operating Characteristics of The Current Relay RXIG2

- a.1) Use a screwdriver to put the max marking to 1.
- a.2) Connect the ckt and ~~change~~ ^{increase} the voltage until the indicator flag drops. [ckt in Fig 1]
- a.3) Enter the ammeter reading in Table 1
- a.4) Repeat for relay settings to 1.5 & 2.
- a.5) The indicator flag must be reset by hand

TABLE 1

Scale Factor X 2.5 A	operating Value (A)	
	Measured	Relay Data
1.0	2.48	2.5
1.5	3.78	3.75
2	4.98	5.0

b) Operating & Resetting Values of The Voltage Relay RXEG2

It's recommended to use a digital voltmeter since a voltmeter of extremely high quality should be used for a measurement to be worthwhile.


The signaling ckt RXSF is supplied with dc auxiliary voltage from suitable terminals of the front panel of the relay unit.

- b.1.) set up the ckt in Fig 2.
- b.2) Set scale factor to 1 on relay RXEG2.
- b.3) Increase the voltage (using the rotary transformer) until signal relay RXSF indicates
- b.4) Enter the operating value in Table 2.
- b.5) Reduce the voltage until the signal relay resets.
- b.6) Enter the resetting value in the table.
- b.7) Repeat steps 1.3 to 1.6 twice.
- b.8) change the scale factor to 1.25 and perform all subsequent measurements as shown in the table.

Measurement no.	Set Value (V)	operating Value (V)	Resetting Value (V)	resetting ratio
1	1.0 X 80	80.1	70.3	0.878
2	1.25 X 80	100.2	98	0.978
3	1.5 X 80	120.1	117.1	0.975
4	1.75 X 80	140.2	136.1	0.971
5	2.0 X 80	163.6	157.2	0.961
6	2.25 X 80	184.9	177.6	0.961
7	2.5 X 80	203.4	196.4	0.966
8	2.75 X 80	227.5	218.4	0.96

* where Resetting Ratio = $\frac{\text{Resetting Value}}{\text{operating Value}}$

○ Resetting Values
 x Operating Values

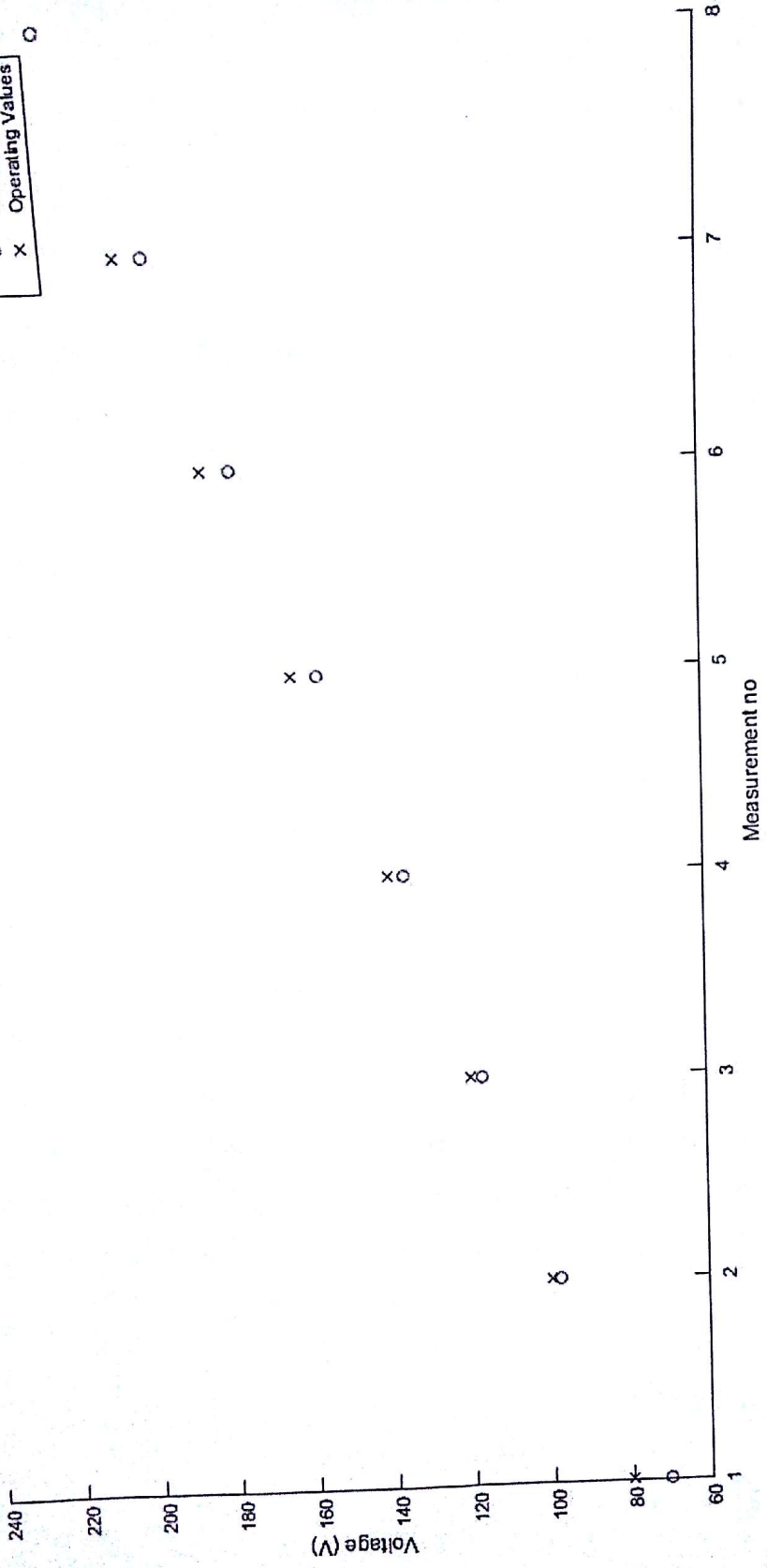

Copy?

• Power Consumption ∞∞

Use the same set up as for step b1.A
digital voltmeter must be used connected directly
across the relay input

In this part we repeated steps b.2 & b.3 then
measured current and voltage when scale factor
(1 & 2 & 2.75)

Scale Factor	V	I	S
1.0	78.9	0.08	6.312
2.0	161.6	0.16	25.856
2.75	227.2	0.22	49.98

TABLE (3)

d. Pick-up times

The pick-up-time of RXEG is the time from
the instant when the measuring input detects
a voltage until completion of the contact
movement of the output relay.

To measure pick-up time it is necessary to
include an intermediate relay (RXME)

operating times for RXME

Two contacts one make and one break contact are connected in parallel and to the input of the timer as shown in Fig (3)

RXME is energized with switch 's' and the operating time on the timer is recorded

After repeated the measurement twice and read the value of time (ms) we calculated the mean value

Measurement	Time (ms)
1	9
2	7
3	11
Mean value	9

TABLE (4)

- ~~1.1~~
- d.1 set up the circuit shown in Fig (4)
- d.2 Ensure that the rotary transformer in the power supply unit is set to zero and close the main switch
- d.3 set the scale factor (1)
- d.4 Increase the voltage from the rotary transformer to 88V
- d.5 open the main switch, and reset the timer to zero

d.7 Repeat points (d.5) and (d.6) twice

d.8 Increase the voltage to 120 and 200 V repeating the measurements

Measurement	Set Voltage	Test Voltage	time (ms)		MCU Value (ms)
			read	collected	
1	1.00 X 86	88	44 41	32	32
2	1.00 X 86	120	39	30	30
3	1.00 X 86	200	32	23	23

Discussion & Conclusion

Part a)

Our measured & the actual relay data are very close with only a small error. Increasing the scale factor increases the current that the relay is set to, and hence the relay trips at higher currents.

Part b)

Looking at the resetting ratios, we notice that they are very close to 1 (around 0.97 or so), which means that the relay operating & resetting value are close which leads to a sensitive relay. Also it's noticed that the resetting value is less than the operating value.

Part c)

We investigated the power consumed by the relay, this ~~depends~~^{increases} as the scale factor increases.

Part d)

The operating times of both RXME & RXEG2 is studied. The measured time is the operating time of both RXEG & RXME, ~~there~~ therefore, to measure RXEG time we must include RXME and measure the time for both relays, and measure the operating time of RXME, then we can subtract the two values to find the operating time of RXEG.

The operating time of RXME is measured 3 times to reduce errors.

The operating time of the relay is in the order of 30 ms or less, and this number decreases as the test voltage increases (fault current increases). However, this is an instantaneous

Voltage relay, so this delay is not intended, and is due to mechanical issues.

Sources of Errors.

We notice a slight deviation between our measured and actual readings, and this is due to the following:

1. Human errors in performing the procedure and in reading the data.
2. Resistances of wires and other components, which causes voltage drops.
3. Errors in the measuring devices themselves
4. Wear in moving mechanical parts (like switches)

University of Jordan
Electrical Engineering Department
Power Lab experiment # 6

* Done by : محمد تاد قروس

8
10
18/10/25

* اشعة يوم الأربعاء :

- 1) محمد تاد قروس 0136600
- 2) يوسف نضال الرفيع
- 3) حمزة عيسى
- 4) احسان داود العبادي
- 5) مهند حيدر

Introduction :

- our goal is to compare between electromechanical relay & Static Relay.
- operation of electro mechanical relay based on Force between electro magnet & armature parts to open & close the circuit as shown in Fig. 1

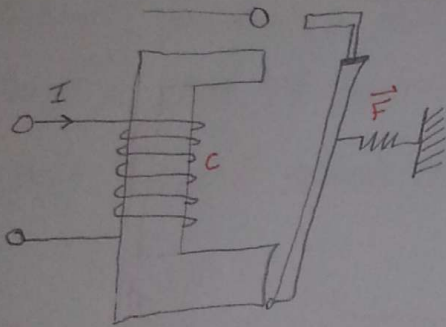


Fig. 1

- we have 2 forces the spring force \vec{F} & the electro magnetic force & the electro magnetic force depend on the amount of current I in the winding C , if the electro magnetic force exceeds the spring force then the contacts will open.
- electro mechanical relay have setting knob which adjust the tension of armature spring the scale is graduated for operation with slowly increasing current
- the operating value depends on the rate of change of the current or voltage or whatever the relay designed to work with, if the short circuit current have a dc component the relay pick-up at the value of the a.c component which is 50% approximately.

* RXIG1 : The static Relay which block the dc component of short circuit current.

* RXIC : The electro Mechanical Relay.

* First we test the operating & Reseting value for both Relay without any d.c component.

* RXIG12 :
Static

No	Set value (A)	operating value (A)	Reseting Value (A)	Reseting Ratio
1	1.0 * 2.5	2.66	2.56	1.039 / 0.962
2	2.0 * 2.5	5.2	5.11	1.017 / 0.982

* RXIC1 :
electro Mechanical

No	Set Value (A)	operating value (A)	Reseting value (A)	Reseting Ratio
1	1.25 * 2	2.2	1.2	1.83 / 0.546
2	2.5 * 2	4.8	1.63	2.94 / 0.339

In this part we notice that the resetting ratio of the static relay is larger than the electro mechanical relay.

* that means that the static relay will be ready faster than the electro mechanical relay if another fault is happened.

* The reason why the electro mechanical have a huge difference between the operating & Resetting values that we need the spring to go back to its normal position & that mean we have to remove the force that going against its tension so we need lower current so that the spring force F exceeds the electro magnetic force.

* 2. power Consumption :

set value	operating value	voltage before operating	voltage after operating	before (VA)	After (VA)
1.0x2.0	1.81	0.36	0.54	0.652	0.9774

Table.2 for RXIC1


set value	operating value	voltage before operating	voltage after operating	before (VA)	after (VA)
1.0x2.5	2.69	0.56	0.6	1.5064	1.614

Table.3 for RXIG2

* electro mechanical relay need (consume) power more than static relay because we need large current to generate force to exceed the spring force.

* The effect of Dc component :

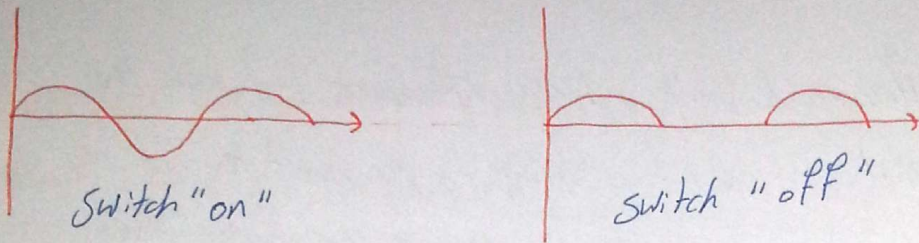* We introduce the Dc component by other source connected in series with a switch so that



* we use 3 Ammeter (Ac, Dc & Rms) to get better indication of what the different between the two Relays.

Set	Ac operating	Dc operating	Rms operating	Ac Reseting	Dc Reseting	RMS Reseting
1.25x2	1.09	0.93	1.5	0.12	0.06	0.02

Table.4 the RXIG1 "electroMagnetic".

Set	Ac operating	Dc operating	Rms operating	Ac Reseting	Dc Reseting	RMS Reseting
10x25	2.6	236	55	2.6	22	3.4

Table.5 the RXIG2 "static".

$$I_{eRMS} = \sqrt{\frac{I_{AC}^2}{RMS} + \frac{I_d^2}{RMS}}$$

* For RXIC2 :

$$\text{AC Reseting ratio} = \frac{0.12}{1.093} = 0.109$$

$$\text{DC Reseting ratio} = \frac{0.06}{0.93} = 0.064$$

* For RXIG1 :

$$\text{AC Reseting ratio} = \frac{2.59}{2.62} = 0.98$$

$$\text{DC Reseting ratio} = \frac{2.2}{2.36} = 0.932$$

* So the static Relay effected by the DC component but the electroMechanical Relay see the fault & the DC component so it's Not effected by the DC.

Conclusion
Intravalue

Experiment No# 7

Time-lag Over-Current Relay

RXIDE-41

students:

-Esra' Adel Al-shrouf 0120387

-Anwar Awamleh

-Maath

-Ala' Awwad

-Ibrahim Ayesh

6/10

المشرف

Objective

to explore the inverse & instantaneous operation of a relay, and its current & time settings.

Procedure

1) Operating and Resetting Values for starting function without tripping function.

Measurement no.	set Value (A)	operating value(A)	Resetting value(A)	resetting Ratio(%)
1	0.5X4	1.95	1.82	93.3
2	0.75X4	2.93	2.75	93.86
3	1.25X4	4.82	4.56	93.25

where Resetting Ratio = Resetting Value / operating Value

The resetting ratio is about 93.3%.

→ Inverse Time Curves

TABLE 2: set current $0.5 \times 4 = 2A$ set time Factor $K=1.$

Measurement No.	Measuring current(A)		I/I_s	Measured Time (mSec)
	I	I_R		
1	4	0.4	2	14.68
2	8	0.8	4	4.88
3	12	0.8	6	2.73
4	16	0.8	8	1.92
5	20	1	10	1.49

TABLE 4: Set current $0.5 \times 4 = 2A$, set time factor $K=0.5$
when K was reduced, the measured time decreased.

So K is directly proportional to k

Measurement No.	Measuring current(A)		I/I_s	Measured Time (mSec)
	I	I_R		
1	4	0.4	2	6.3
2	8	0.8	4	2.18
3	12	0.8	6	1.34
4	16	0.8	8	0.97
5	20	1	10	0.75

The following operating times were calculated from

$$t = \frac{13.5}{\frac{I}{I_s} - 1}$$

I/I_s

T (calculated time)

2

13.5

4

4.5

6

2.7

8


1.93

10

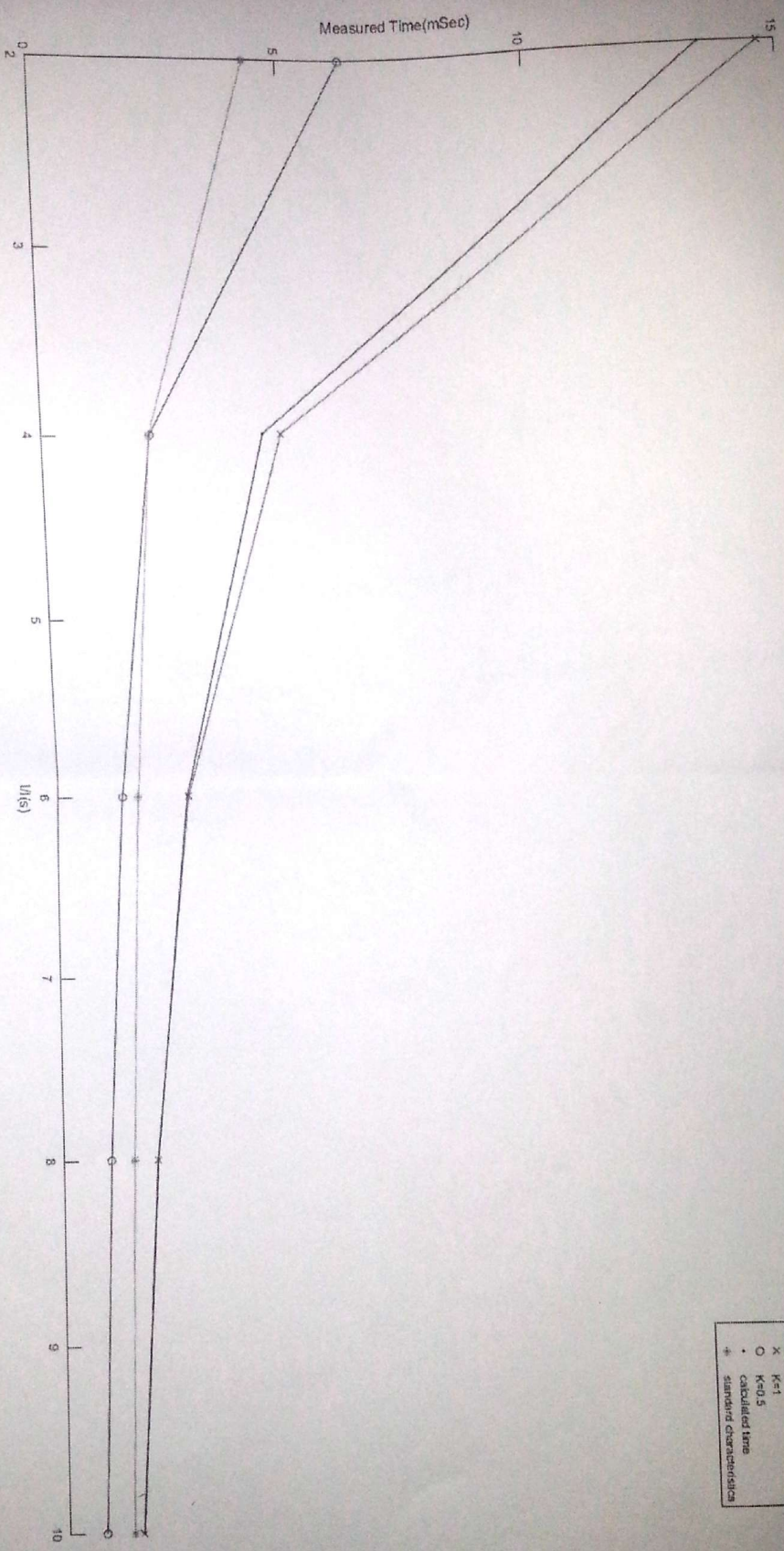1.5

Time calculated from the above equation and the standard characteristics ($t = \frac{3}{\log psm}$) are plotted as well as the measured data.

from the graph we can see that the time calculated using standard characteristics is less than that of $t = \frac{13.5}{\frac{I}{I_s} - 1}$.



instantaneous operation.

Instantaneous setting B

$$2 \times I_s$$

~~3~~
 $3 \times I_s$

$$4 \times I_s$$

$$8 \times I_s$$



current instantaneous operation (A)

$$(2) (0.5)(1.1) = 1.1$$

$$3 (0.5)(1.1) = 1.65$$

$$4 (0.5)(1.1) = 2.2$$

$$8 (0.5)(1.1) = 4.4$$

we noticed that both flags operated together, which means that increasing the current setting increase the instantaneous operation current.

Conclusion?