

39
40

FACULTY OF ENGINEERING & TECHNOLOGY
MEASUREMENTS AND CONTROL LAB.0908448
MID-TERM EXAM


Eng. Nazmi Abu Ashour, Eng. Nisreen Amayreh

Second Semester

Name: _____
Reg. No: 0076375
Section No: 2

PART ONE: (42)


Resistance measuring using Voltmeter & Ammeter method
1. One of the experiments in the measurements lab was to measure the value of resistances using two PMMCs, there were two cases in that experiment name identify and draw them.

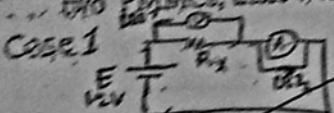

CASE 1

$$R_x = \frac{V}{I_x} \approx 100 \%$$

$$R_x = \frac{R_x R_v}{R_x + R_v}$$

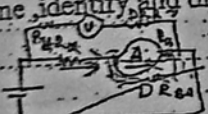

CASE 2

$$R_x = R_x + R_a$$

$$E = \frac{R_x I_x}{R_x}$$

$$D.R.B.A = \frac{R_a I_x D}{I_x D}$$

$$I_x - I_a$$

CASE 1: Voltmeter Galvanometer: in this case the voltmeter parallel to Rx only D.R.B.A = $\frac{V - R_v I_x}{I_x D}$

CASE 2: Ammeter Galvanometer: in this case the Ammeter will be in series with Rx and the voltmeter parallel with them

After doing this experiment the results were as follows

Rx(kΩ)	7	20
Expected Ix (mA)	1.714	0.5
Measured Ix' (mA)	1.95	0.65
Measured voltage across resistance Vx (V)	12	12
Measured value of Rx (Rx')(kΩ)	6.154	18.462
Measured percentage Error (e%)	12.08 %	7.69 %

Handwritten: Rx + Ra = Ix D

Table 1.

2. Fill in Table 1 the *expected current* I_x in mA, and the *measured value of R_x* in ohms, show one sample of your calculations for both I_x and measured R_x .

5)
$$I_x = \frac{V}{R_x} = \frac{12}{7 \text{ k}\Omega} = 1.714 \text{ mA}$$

$$R_{x \text{ meas}} = \frac{V_{\text{meas}}}{I_{\text{meas}}} = \frac{12}{1.915} = 6.154$$

3. If you were given:

Galvanometer with *internal resistance* = 600 ohms, *max current* = 0.5 mA.

Decade resistance box:


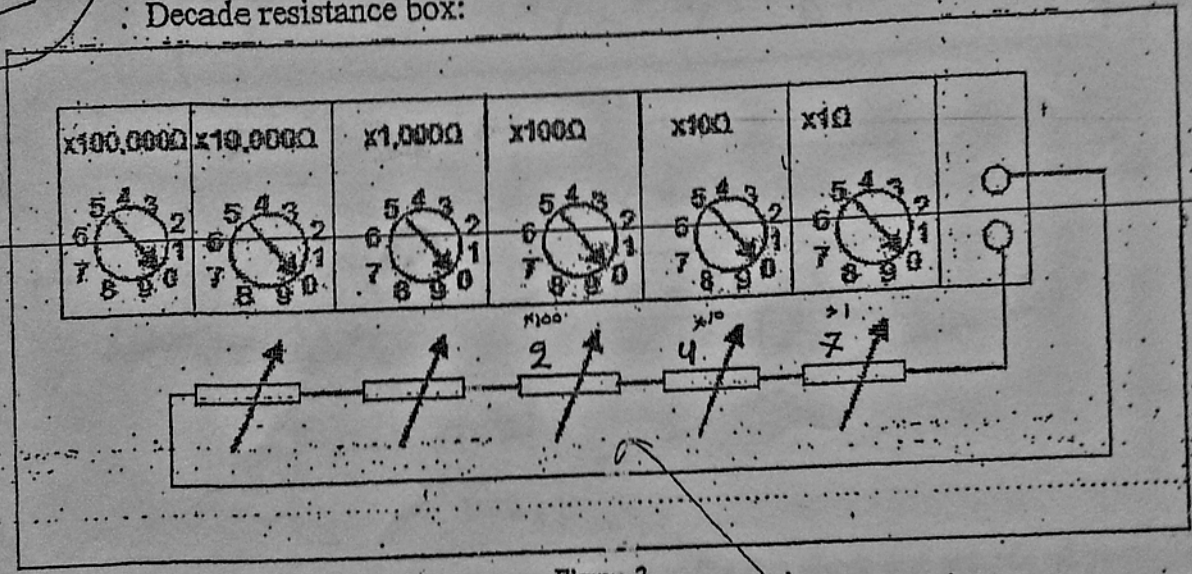


Figure 2.

Considering your results in 2 above, design ammeter to measure the current I_x show your calculations, the circuit and the settings of DRB on Figure 2.
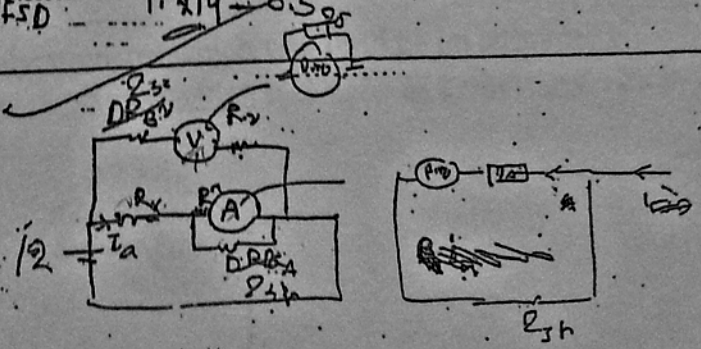
$$DRB_A = \frac{R_g I_{fsd}}{I_x} = \frac{600 \times 0.5}{1.714} = 175 \Omega$$



4. If you were given:

Galvanometer with internal resistance = 2000 ohms, max current = 0.4 mA

Decade resistance box:


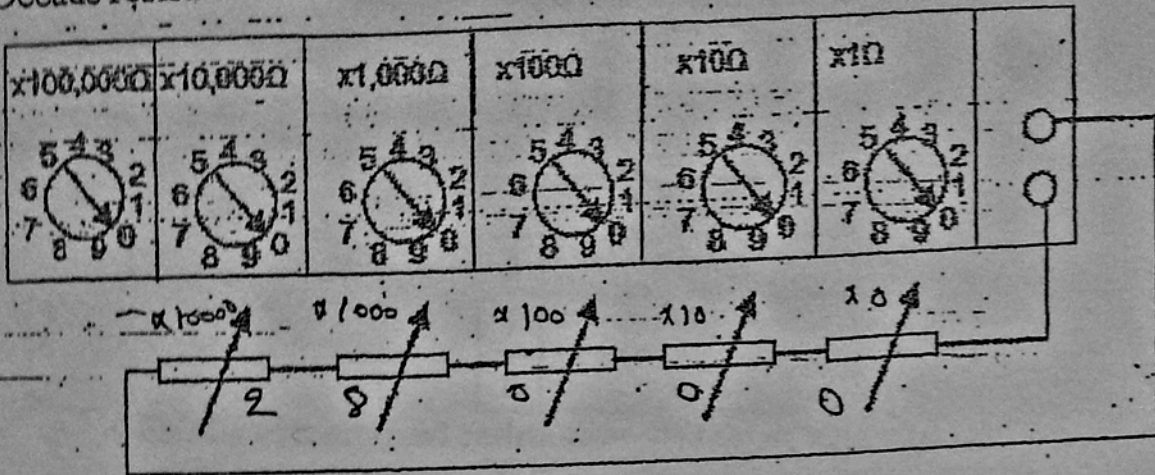


Figure 3.

Design voltmeter to measure the voltage across R_x , show your calculations, the circuit and the setting of DRB on figure 3.

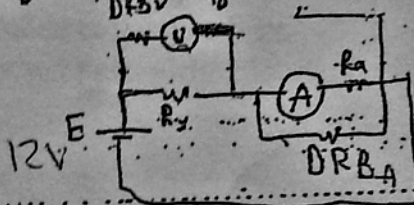
$$DRB_v = \frac{V - R_v I_{fsd}}{I_{fsd}} = \frac{12 - 2000 \times 0.4 \text{ mA}}{0.4 \text{ mA}} = 28000 \Omega$$



5. Fill in table 1 the measured percentage error for R_x , show one sample of your calculations.

$$e = \frac{R_x - R_{x,m}}{R_x} \times 100\% = \frac{7 - 6.154}{7} \times 100\% = 12.08\%$$

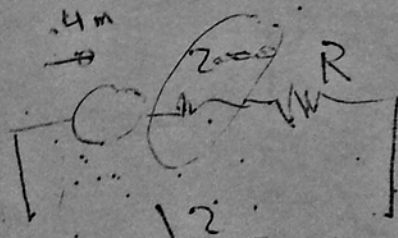6. The sensitivity of the galvanometer which was used as an ammeter is: $\frac{2000}{0.4 \text{ mA}} = 5000 \text{ ohm/volt}$
 The sensitivity of the galvanometer which was used as a voltmeter is: $\frac{28000}{0.4 \text{ mA}} = 70000 \text{ ohm/volt}$



$$\frac{12}{0.4 \text{ mA}} - 2000 = R$$


PART TWO: (12)

To design a DC milli-voltmeter, you will use:

- Operational Amplifier LM741, and here is the pin connection for this OP-AMP:

1	Offset Null
2	Inverting Input
3	Non-inverting Input
4	Vs-
5	Offset Null
6	Output
7	Vs+
8	N/C

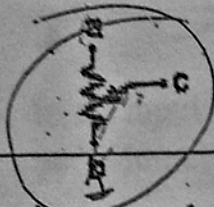- A PMMC with internal resistance = 700 Ohms, max current = 0.1 mA.
- ... 20kΩ Potentiometers.. 15k Ω potentiometer



When rotated fully clockwise, a is connected to c.

When rotated fully counter-clockwise, b is connected to c.

- A power supply with +10 V, -10 V and +6 V.
- Resistors of any values that you might need.
- Decade resistance box.

Here is shown part of the electrical circuit that measure milli-voltages:

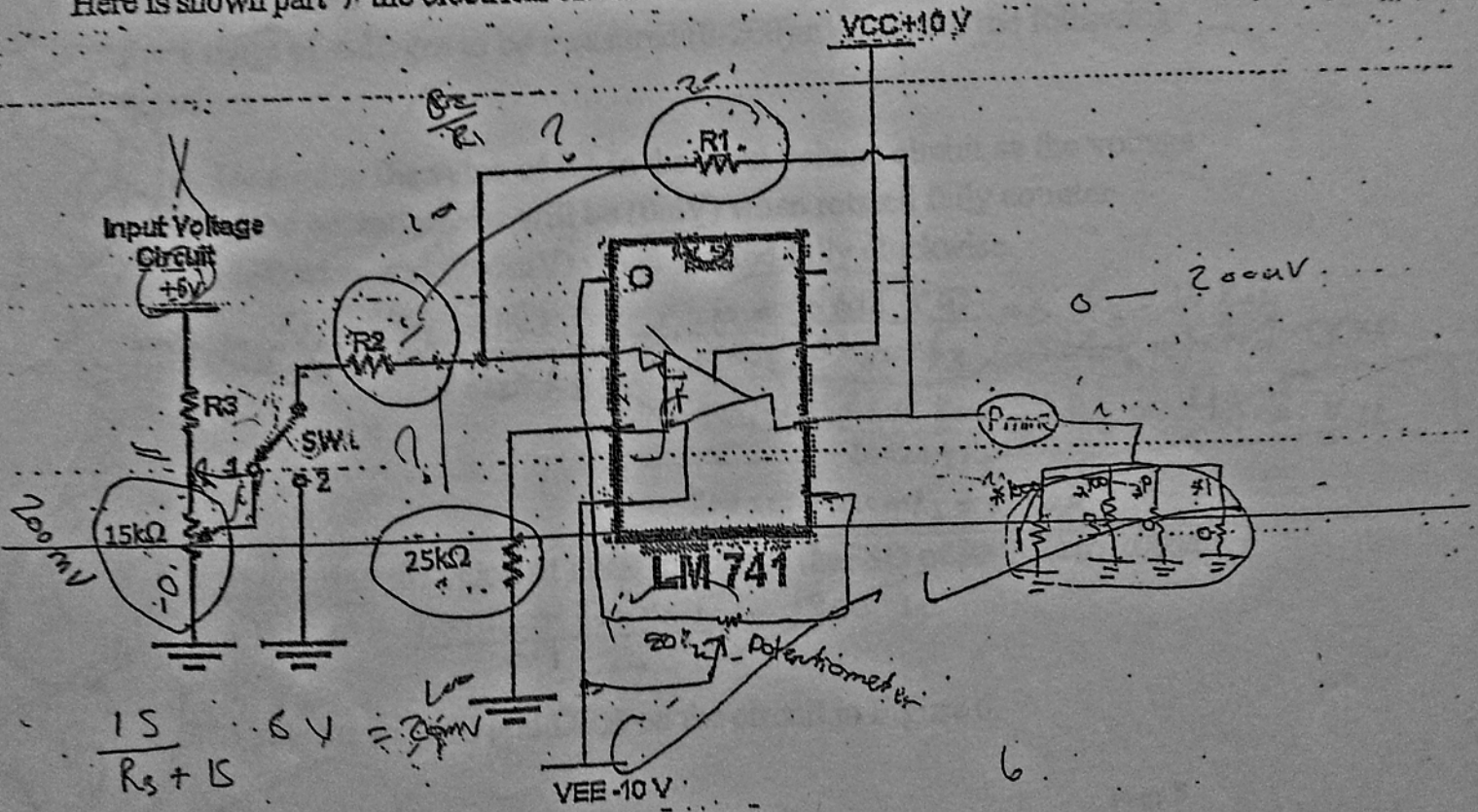


Figure 6.

1. In order to perform the offset null adjustment, the switch SW1 should be connected to terminal 2.

2. Draw the connection of the 20kΩ potentiometer on the circuit in Figure 6, in order to do the offset null adjustment.

3. What is the importance of the Offset Null Adjustment for the OP-AMP?

to remove any drift from the output, and to ensure that the output will be zero when we apply zero input

4. What are the values of:

+ R1: 50 kΩ

+ R2: 50 kΩ

$$25 \text{ k}\Omega = \frac{R_1 \times R_2}{R_1 + R_2} \quad , \quad \frac{R_1}{R_2} = 1 \Rightarrow R_1 = R_2$$

$$\frac{R_1^2}{2R_1} = 25 \text{ k}\Omega$$

$$R_1 = 2 \times 25 \text{ k}\Omega = 50 \text{ k}\Omega, \quad R_2 = 50 \text{ k}\Omega$$

5. In the input voltage circuit, why R3 is connected in series with the potentiometer?

to increase sensitivity & accuracy, and to prevent a short circuit when we apply zero input, and to safe the op-amp when we apply high voltage, so there will be voltage division on it

For a range of voltages to be measured: (0-200)mV, answer the following questions:

6. Determine the value of R3 in the input voltage circuit, so the voltage of the potentiometer will be (0mV) when rotated fully counter-clockwise, and (200mV) when rotated fully clockwise.

$$\Rightarrow V_o = \frac{V_{in} \times 15 \text{ k}\Omega}{15 \text{ k}\Omega + R_3} \Rightarrow 0 = \frac{6 \times 15 \text{ k}\Omega}{15 \text{ k}\Omega + R_3} \Rightarrow R_3 = 15 \text{ k}\Omega \text{ when rotated CCW}$$

$$\frac{200 \text{ mV}}{200} = \frac{6 \times 15 \text{ k}\Omega}{15 \text{ k}\Omega + R_3} \Rightarrow R_3 = 435 \text{ k}\Omega$$

$$200 \times 15 + 200 \text{ m}R_3 = 6 \times 15 \text{ k}\Omega$$

7. Determine the value of DRB to change the FSD of PMMC to 200mV.

$$\text{DRB} = \frac{200 \text{ mV} - 100 \times 0.1}{0.1} = 1300 \Omega$$


8. Draw the PMMC and DRB on the circuit in Figure 6.

Digital earth Tester

Digital earth Resistance

PART THREE: (8)

*The circuit shown in figure 7 is the circuit that you have used to measure the earth resistance; three earthing rods X, Y and Z were used, there resistances are R_X , R_Y and R_Z .

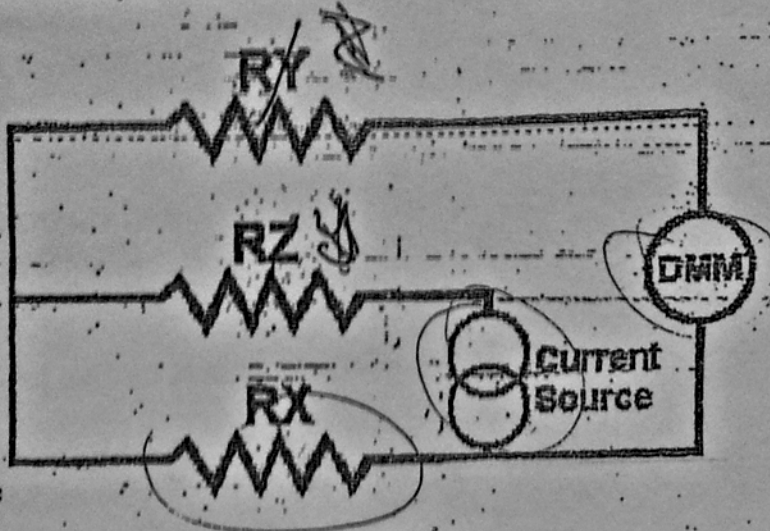

(Figure 7)

1.5
1.5
1
1
1
1.5

- The name of the method which was used to measure the earth resistance in the circuit above is Potential method.
- Which resistance performs the earth resistance R_X , R_Y , or R_Z ? R_X .
- The sitting for the DMM in figure 7 is voltmeter.
Choose one (voltmeter, Ammeter, or Ohmmeter)
- What is the equation that shows the relationship between the diameter of the earth rod and the resistance of it? $R = \frac{\rho L}{A}$ $A = \frac{\pi D^2}{4}$ when we increased D R will decrease.
- Soil conductivity and resistivity depend on: fertilize and wet soil.
- What is the maximum allowable value of earth resistance according to the Jordanian Engineers Association specifications?

5 Ω



fertilize

PART FOUR: (8)

A. Choose the correct answer:

1. LabVIEW is a programming language that uses:
 - a) Ladder diagram
 - b) Icons
 - c) Lines of text
 - d) nodes
2. In LabVIEW, you build a user interface that known as:
 - a) block diagram
 - b) Front panel
 - c) functions palletete
 - d) Controls palletete
3. The following palletete should be visible when the front panel window is active:
 - a) Controls palletete only
 - b) Tools palletete and Controls palletete
 - c) Tools palletete only
 - d) Tools palletete and Functions palletete
4. The following palletete should be visible when the block diagram window is active:
 - a) Controls palletete only
 - b) Tools palletete and Controls palletete
 - c) Tools palletete and Functions palletete
 - d) Tools palletete only
5. When you need to build a function generator you will assign DAQ as:
 - a) Input
 - b) Output

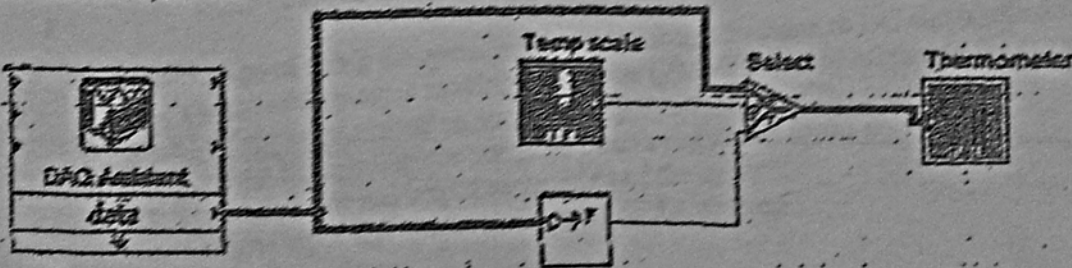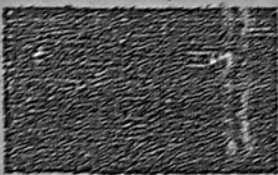B. Give a brief description for the following code.



In the front panel we put a vertical slide switch & thermometer (0-125)
 In the block diagram we add a DAQ Assistant to get the signal from the thermometer
 on the Board and move it to the PC → it will separate in 2 lines
 First line when the vertical slide switch up → will display the temperature in celsius
 the second line will pass through the converter and convert the celsius Temp.
 into a Fahrenheit, Now to chosg. one of the 2 lines we put a comparator
 and select one of them and move it to the Thermometer.