

Some useful Constants:		
$B(\text{Si}) = 5.23 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$	$E_g(\text{Si}) = 1.1 \text{ eV}$	$k = 86 \times 10^{-6} \text{ eV/K}$
$e = 1.6 \times 10^{-19} \text{ C}$		
$\mu_n(\text{Si}) = 1350 \text{ cm}^2/\text{V-s}$	$\mu_p(\text{Si}) = 480 \text{ cm}^2/\text{V-s}$	

Question 1: [20-points] 15

A Silicon semiconductor material is to be designed at temperature 330K, such that the majority carrier hole concentration is $4.5 \times 10^{16} \text{ cm}^{-3}$. Answer the following questions clearly:

a) What is the intrinsic carrier concentration for this sample?

2) $T = 330 \text{ K}$ $p_0 = 4.5 \times 10^{16}$

$$n_i = B T^{3/2} e^{-\frac{E_g}{2kT}} = 5.23 \times 10^{15} \times (330)^{3/2} e^{-\frac{1.1}{2 \times 86 \times 10^{-6} \times 330}}$$

$$= 1.2 \times 10^{11} \text{ cm}^{-3}$$

b) Should donor or acceptor impurity atoms be used to achieve this concentration?

3) acceptor impurity should be used

c) Determine the minority carrier concentration.

5) $n_0 = \frac{n_i^2}{p_0} = \frac{(1.2 \times 10^{11})^2}{4.5 \times 10^{16}} = 3.2 \times 10^5 \text{ cm}^{-3}$

d) An applied electric field $E = 15 \text{ V/cm}$ is applied to the designed sample, determine the drift current if you know that the cross sectional area for it is $2 \times 10^{-4} \text{ cm}^2$.

2) $A = 2 \times 10^{-4} \text{ cm}^2$

$$J = \sigma E = q n \mu_n E + q p \mu_p E$$

μ_n too small

$$J = (2 \times 10^{-4}) (15) (-3.456)$$

$$J = -0.01 \text{ A/cm}^2$$

$$J = -e \mu_p p_0 E = -(1.6 \times 10^{-19}) (480) (4.5 \times 10^{16}) (15)$$

$$= -3.456$$

$$= -3.456$$

e) True or False: As impurity concentration increase, the electron mobility decrease. False

6)

20
Question 2: [20-points]

For a Silicon pn junction, let $N_a = 5 \times 10^{15}$ and $N_d = 8 \times 10^{17}$ answer the following questions:

- a) Determine the built-in potential barrier of the generated pn junction at room temperature.

16
$$V_{bi} = V_T \ln \left(\frac{N_a N_d}{N_i^2} \right)$$

$$n_i(\text{Si}) = 1.5 \times 10^{10}$$

$$= 0.026 \ln \left(\frac{5 \times 10^{15} \times 8 \times 10^{17}}{(1.5 \times 10^{10})^2} \right)$$

n_i

$$V_{bi} = 0.79323 \text{ V}$$

$$V_{bi} = 0.79323 \text{ V}$$

- b) If this pn junction diode is operating in forward-bias region, determine the increase in forward bias voltage that will cause a factor of 22 increase in current.

10
$$\frac{I_{D2}}{I_{D1}} = e^{\left(\frac{V_{D2} - V_{D1}}{V_T} \right)}$$

$$\frac{e^{\left(\frac{V_{D2}}{V_T} \right)}}{e^{\left(\frac{V_{D1}}{V_T} \right)}}$$

$$\Delta V = V_T \ln \left(\frac{I_{D2}}{I_{D1}} \right)$$

$$= 0.026 \ln(22)$$

$$\Delta V = 0.08 \text{ V} \rightarrow \text{increase in forward bias voltage}$$

Question 3: [20-points]

Part 3.1: For the diode circuit shown in Figure Q.3.Part 1, it has a reverse-saturation current of $I_s = 5 \times 10^{-13}$, assume $T = 300K$, answer the following questions:

a) What is the input voltage V_{PS} that will produce $V_D = 0.5V$.

10 $V_D = V_{PS} \left(\frac{R_2}{R_1 + R_2} \right)$

$0.5 = V_{PS} \left(\frac{20K\Omega}{40K\Omega + 20K\Omega} \right)$

$V_{PS} = 1.5V$

$R_{th} = 13.33$

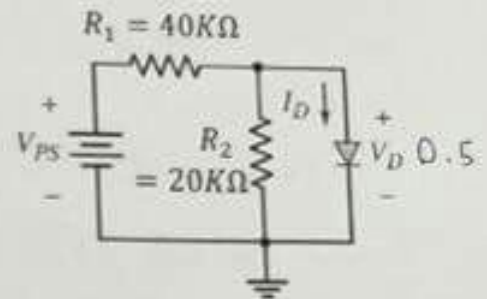


Figure Q.3.Part 1

5 b) Determine the I_D value

$I_D = I_s \left(e^{\frac{V_D}{V_T}} - 1 \right)$

$= 5 \times 10^{-13} \left(e^{\frac{0.5}{0.026}} - 1 \right)$

$I_D = 1.12 \times 10^{-4}$

Part 3.2: For the circuit shown in Q.3.Part 2, assume $V_f = 0.6V$, find I and V_o .

10 $I = \frac{12 - 0.6}{22 K\Omega} = 0.518 mA$

$V = 0.6 + (0.518 \times 12) mA \cdot K - 3 = 3.816 V$


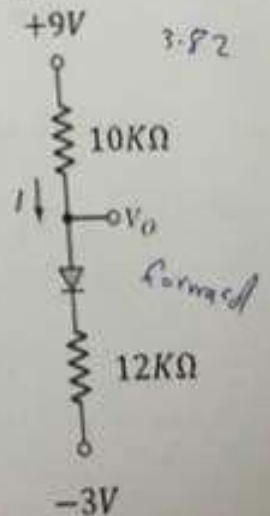
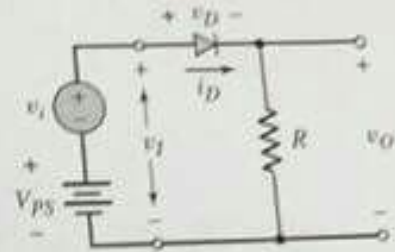


Figure Q.3.Part 2

17
Question 4: [20-points]

For the circuit shown in Figure Q.4, at room temperature, assume circuit parameters: $V_{PS} = 6V$, and $R = 1k\Omega$. The diode $V_f = 0.6V$. A sinusoidal voltage is superimposed on V_{PS} such that $v_i = 0.2 \sin(\omega t)$. As you learned in the class, do the following:

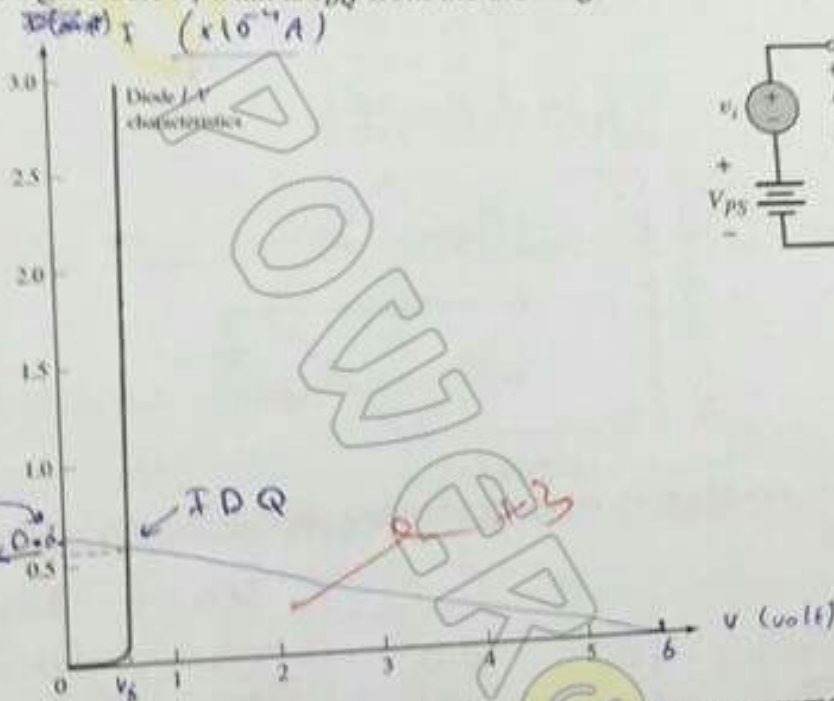- a) For this circuit, draw the related load line over the diode characteristic curve given in the figure below, what is I_{DQ} from the drawing?



$$\frac{6}{1k} = 6 \times 10^{-4}$$

- b) Calculate the small-signal diode diffusion resistance, assume $T = 300K$.

$$r_d = \frac{V_T}{I_{DQ}} = \frac{0.026}{5.4 \times 10^{-4}} = 4.814 \Omega$$

$$I_{DQ} = \frac{V_{PS} - V_f}{R} = \frac{6 - 0.6}{1k\Omega} = 5.4 \text{ mA}$$

- c) What is the "only" ac component of the output voltage v_o ?

$$v_d = \frac{v_i \times R}{r_d + R} = \frac{0.2 \sin(\omega t) \times R}{(4.8 + 1k)} = 1.99 \times 10^{-4} \sin(\omega t) \times R$$

$$v_o = 0.199 \sin(\omega t) \text{ V}$$

Question 5: [20-points]

For the full-bridge rectifier circuit shown in Figure Q.5, if the turns ratio of the attached transformer is 22, the input voltage v_1 was $220V_{RMS}$, each diode has the following cut-in voltages shown in the table, answer the following questions:

D1	$V_Y = 0.5$
D2	$V_Y = 0.6$
D3	$V_Y = 0.7$
D4	$V_Y = 0.8$

$$V_S = \frac{220 \times \sqrt{2}}{22} = \frac{10\sqrt{2}}{1} = 14.14 \text{ V}$$

$$\frac{N_1}{N_2} = 22$$


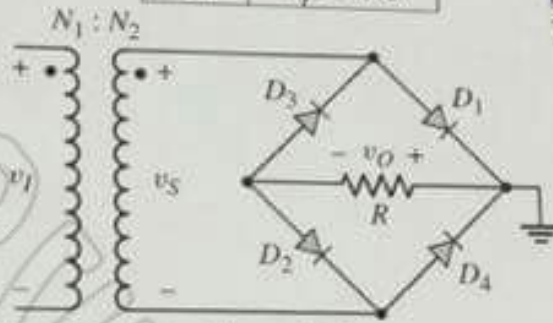


Figure Q.5

$$V_S = 14.14 \text{ V}$$

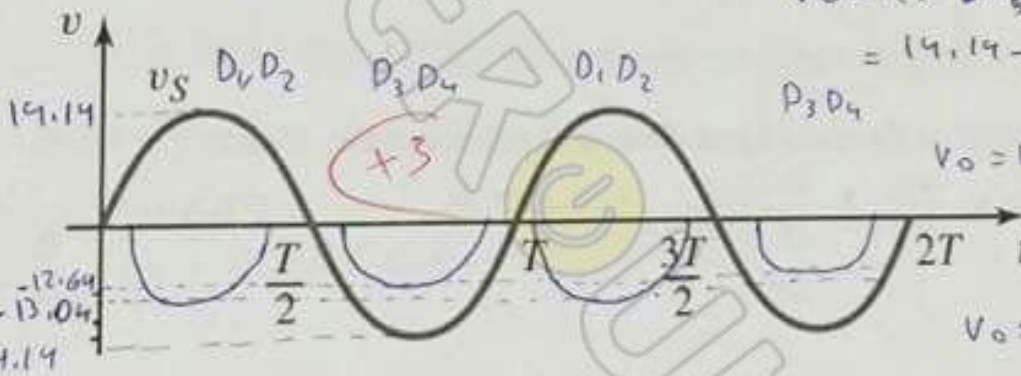- a) Draw the output voltage v_o on the graph below showing the real values of v_s and v_o voltages.



$$V_o = -(V_s - 2V_Y)$$

$$= 14.14 - (0.5 + 0.6)$$

$$V_o = 14.14 - (0.7 + 0.8)$$

-12.64
 -13.04

-12.64
 -13.04
 -14.14

- b) Determine the peak inverse voltage rating for each diode in the circuit.

$PIV = V_s - V_Y$

$D_1 : 14.14 - 0.5 = 13.64$

$D_2 : 14.14 - 0.6 = 13.54$

$D_3 : 14.14 - 0.7 = 13.44$

$D_4 : 14.14 - 0.8 = 13.34$

PIV