

16

Question 1: [10-points]

The cut-in voltage of each diode in the circuit shown in Figure Q1 is $V_f = 0.7V$. Determine I_{D1} , I_{D2} , I_{D3} , and V_A for the following:

- $V_1 = 25V$, $V_2 = -10V$, and $V_3 = -8V$
- $R_1 = 4.9k\Omega$, $R_2 = 1.5k\Omega$, $R_3 = 15k\Omega$, and $R_4 = 24k\Omega$;

○ Hint: Assume All Diodes are ON

@ Node A

$$\frac{25 - V_A}{4.9k} = \frac{V_A + 9.3}{24k} + \frac{V_A + 7.3}{15k} + \frac{V_A - 0.7}{1.5k}$$

$$\frac{25}{4.9} - \frac{V_A}{4.9} = \frac{V_A}{24} + \frac{9.3}{24} + \frac{V_A}{15} + \frac{7.3}{15} + \frac{V_A}{1.5} - \frac{0.7}{1.5}$$

$$\frac{25}{4.9} - \frac{9.3}{24} - \frac{7.3}{15} + \frac{0.7}{1.5} = V_A \left(\frac{1}{4.9} + \frac{1}{24} + \frac{1}{15} + \frac{1}{1.5} \right)$$

$$4.49 = V_A (0.979)$$

$$V_A = 4.5863$$


$$V_o = 4.5863 - 0.7 = 3.886$$

$$I_{D1} = \frac{4.586 - 0.7}{1.5} = 2.59 \text{ mA}$$

$$I_{D2} = \frac{4.586 + 8 - 0.7}{15} = 0.7924 \text{ mA}$$

$$I_{D3} = \frac{4.586 + 9.3}{24} = 0.5785 \text{ mA}$$

Power Unit

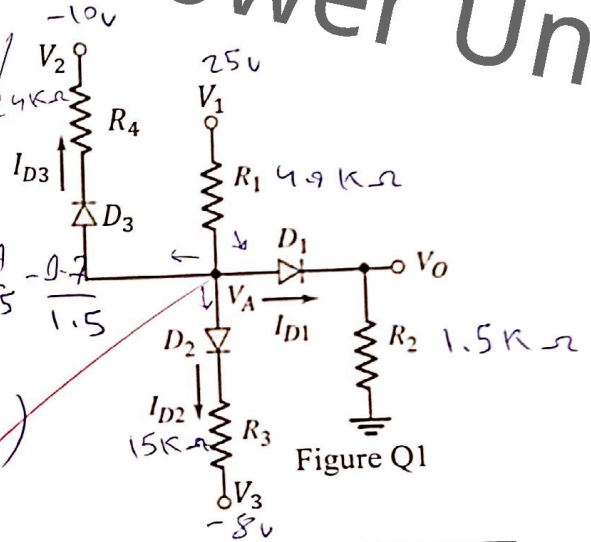

Your Final Answer	
I_{D1}	2.59 mA
I_{D2}	0.792 mA
I_{D3}	0.5785 mA
V_A	4.5863
V_o	3.886

Question 2 [10-points] Consider the circuit in Figure Q2. Each diode cut-in voltage is $V_V = 0.7 V$. Determine I_{D1} , I_{D2} , and V_A for $R_2 = 1.1 k\Omega$.

~~$I_{D1} = 5.06 mA$~~

Power Unit

Assume D_1, D_2 on

$$\frac{5 - 0.7 - V_A}{2k\Omega} + 5mA = \frac{V_A - 0.7 + 5}{1.1}$$

$$\frac{4.3}{2k} - \frac{V_A}{2k} + 5mA = \frac{V_A}{1.1} + \frac{4.3}{1.1}$$

$$3.241 = 1.41 V_A$$

$$V_A = 2.2985$$

$$I_{D1} = \frac{5 - 0.7 - 2.2985}{2k\Omega} = 1mA$$

$$I_{D2} = \frac{2.2985 + 4.3}{1.1k} = 5.99mA$$

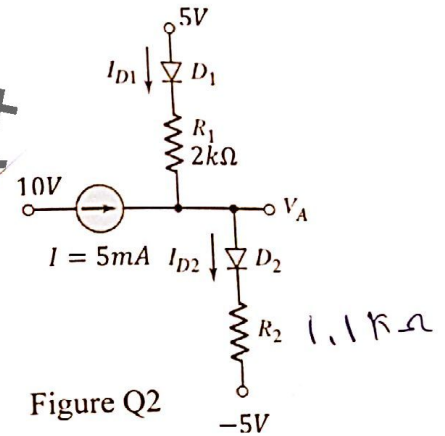


Figure Q2

Your Final Answer	
I_{D1}	5 mA 1 mA
I_{D2}	5 mA 6 mA
V_A	2.2985 V

5.99

Question 3: [20-points]

The pnp transistor shown in Figure Q3 has a common-base current gain $\alpha = 0.9860$.
 (a) Determine the emitter current such that $V_C = -1.2$ V.
 (b) What is the base current?
 (c) Using the results of part (a) and assuming $I_{E0} = 2 \times 10^{-15}$ A, determine V_{EB} .

$$V_C = -1.2 = I_C R_C - 10$$

$$8.8 = I_C 5k$$

$$I_C = 1.76 \text{ mA}$$

$$I_E = \frac{I_C}{\alpha}$$

$$I_E = 1.785 \text{ mA}$$

$$I_B = I_E - I_C$$

$$= (1.785 - 1.76) \text{ mA}$$

$$= 25 \mu\text{A}$$

$$I_E = 1.785 \text{ mA}$$

$$I_E = I_{E0} e^{\frac{V_{EB}}{V_T}}$$

$$1.785 \times 10^{-3} = 2 \times 10^{-15} e^{\frac{V_{EB}}{V_T}}$$

$$0.926 \ln \left(\frac{1.785 \times 10^{-3}}{2 \times 10^{-15}} \right) = V_{EB} = 0.7154$$

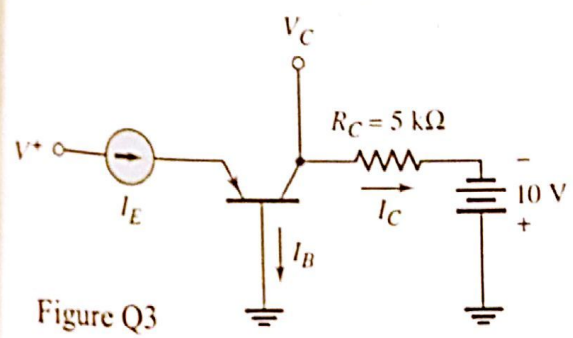


Figure Q3

Your Final Answer	
emitter current	1.785 mA
base current	25 μA
V_{EB}	0.7154 V

Power Unit

16

Question 4: [20-points]

(a) For the circuit in Figure Q4, determine V_{B1} and I_E such that $V_B = V_C$.
 Assume $\beta = 90$.

(b) What value of V_{B2} results in $V_{CE} = 2V$?

$\alpha = 0.989$

$10 - 5 = I_C R_C + I_E R_E + V_{CE}$

$15 = I_C (2k\Omega) + I_E (1k\Omega) + 0.7$

$14.3 = \alpha I_E (2k\Omega) + I_E (1k\Omega)$

$14.3 = (0.989 \times 2 + 1) I_E$

$14.3 = 2.978 I_E$

$I_E = 4.802 \text{ mA}$

$I_C = 4.75 \text{ mA}$


$V_{B1} = 10 - 4.75 \times 2$

$15 = I_C R_C + I_E R_E + 2$

$13 = 2.978 I_E$

$I_C = 4.317$

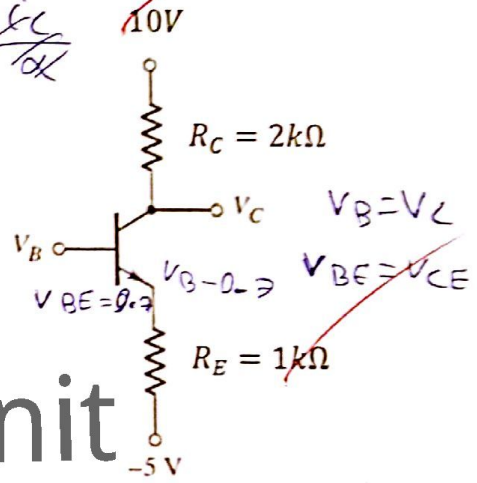$\frac{I_C}{I_E} = \alpha$
 $I_C = \alpha I_E$
 $\frac{I_C}{I_E} = \frac{I_C}{10k}$



Power Unit


Figure Q4

Your Final Answer	
v_{B1}	0.5 V ✓
I_E	4.802 mA ✓
v_{B2}	0.06534 V ✓

(c) Write the load line equation for part (a) and then plot it over the figure below, show me the Q point, is the Q point closer to saturation or cutoff?

4

Q point is closer to the saturation

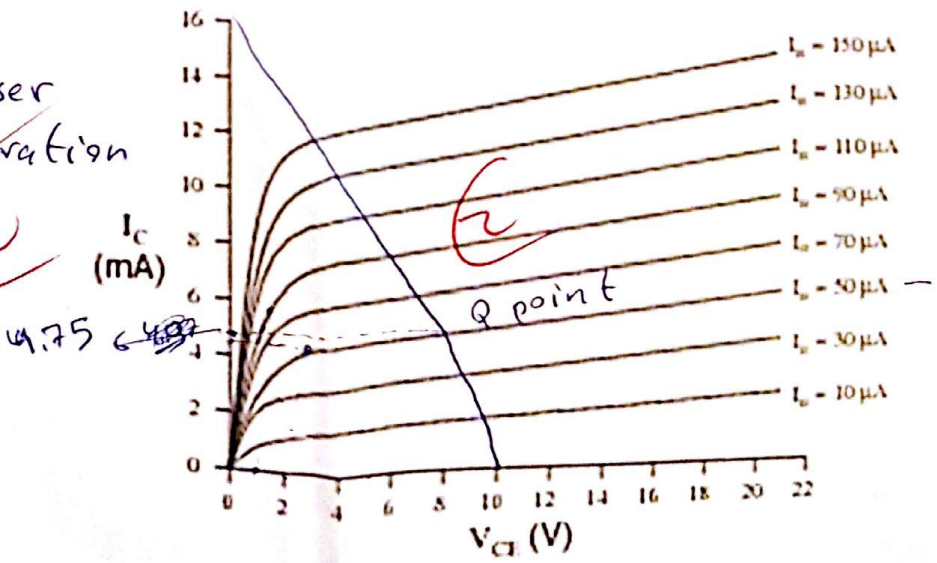

Some useful Equations:

$$I_Z(\max) = \frac{I_L(\max) \cdot [V_{PS}(\max) - V_Z] - I_L(\min) \cdot [V_{PS}(\min) - V_Z]}{V_{PS}(\min) - 0.9V_Z - 0.1V_{PS}(\max)} \text{ for } I_Z(\min) = 0.1I_Z(\max)$$

$$R_i = \frac{V_{PS}(\max) - V_Z}{I_Z(\max) + I_L(\min)}$$

Power Unit

17

Question 5: [20-points]
 A Zener diode is connected in a voltage regulator circuit as shown in Figure Q5. The Zener voltage is $V_Z = 10V$ and the Zener resistance is assumed to be $r_z = 0$.

(a) Determine the value of R_i such that the Zener diode remains in breakdown if the load current varies from $I_L = 50$ to 500 mA and if the input voltage varies from $V_i = 15$ to 20 V.

➤ Assume: $I_Z(\min) = 0.4I_Z(\max)$.

(b) Determine the power rating required for the Zener diode and the load resistor.

V_i ^{min} ^{max} I_L (50 to 500) mA

$I_Z(\min) = 0.4 I_Z(\max)$

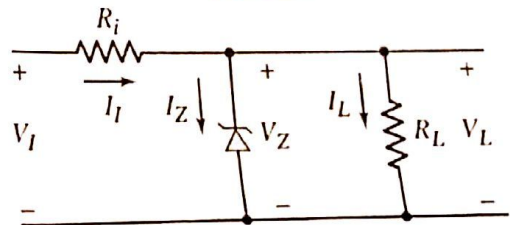


Figure Q5

$I_Z(\max)$

① $R_i = \frac{V_{PS}(\max) - V_Z}{I_Z(\max) + I_L(\min)}$

② $R_i = \frac{V_{PS}(\min) - V_Z}{I_Z(\min) + I_L(\max)}$

① $R_i = \frac{20 - 10}{I_Z(\max) + 50 \text{ mA}}$

② $R_i = \frac{15 - 10}{I_Z(\min) + 500 \text{ mA}}$

$\frac{20 - 10}{I_Z(\max) + 50 \text{ mA}} = \frac{15 - 10}{I_Z(\min) + 500 \text{ mA}}$

4750 1900

Your Final Answer	
R_i	30 kΩ 2.0833 Ω
Power ratings	47.5 W ✓ $P_L(\max) = ?$

$10 I_Z(\min) + 500 \text{ mA} = 5 I_Z(\max) + 250 \text{ mA}$

$4 I_Z(\max) + 500 \text{ mA} = 5 I_Z(\max) + 250 \text{ mA}$

$I_Z(\max) = 250 \text{ mA} \rightarrow 4750 \text{ mA}$

$I_Z(\min) = 0.4 \times 250 \text{ mA} = 100 \text{ mA}$

$R_i = \frac{20 - 10}{250 + 50} = \frac{10}{300} \text{ k}\Omega$

$R_i = \frac{20 - 10}{1.75 + 500 \text{ mA}} = 42.1$

+ 0.05

$P_Z = I_Z(\max) \times V_Z$

=

480

Question 6: [10-points]

For the circuit in Figure Q6:

- Plot v_o versus v_i for $0 \leq v_i \leq 15V$.
 Assume $V_y = 0.7V$.
- Indicate all breakpoints.

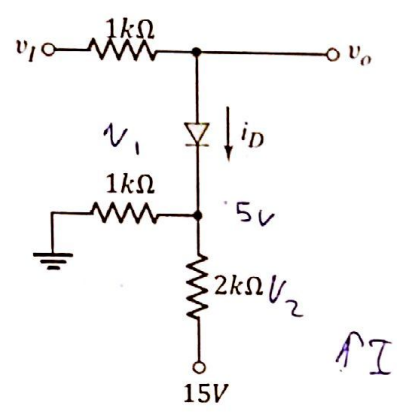


Figure Q6

$$v_i - v_1 = 0 \Rightarrow v_i = v_1$$

$$v_i - 0.7 + \frac{15 - v_1}{2} = 0$$

$$v_i - 0.7 + \frac{15 - v_i}{2} = 0$$

$$2v_i - 1.4 + 15 - v_i = 0$$

$$v_i = 5.7$$

$$v_i = 0.44$$

~~$v_i < 0.7$ diode is off~~
 $v_i = 0 \rightarrow$ diode is off
 $v_i = 15 \times \frac{1}{3} = 5V$

$0 < v_i < 5.7 \quad v_o = v_i$
 $v_i > 5.7$ diode is on $\rightarrow v_o = 5.7$
 $v_o = v_i - 1k\Omega(i_D)$

$$v_o(v_i = 15) = 15 - 1k \times 9.3mA$$


$$= 15 - 9.3 = 5.7V$$

$$i_D = \frac{v_i - 5.7}{1k\Omega}$$


$$v_i = 15 \quad 9.3mA$$

$$i_D = \frac{15 - 5.7}{1k} = 9.3mA$$

$$v_i = 15 \quad v_o = 5.7$$

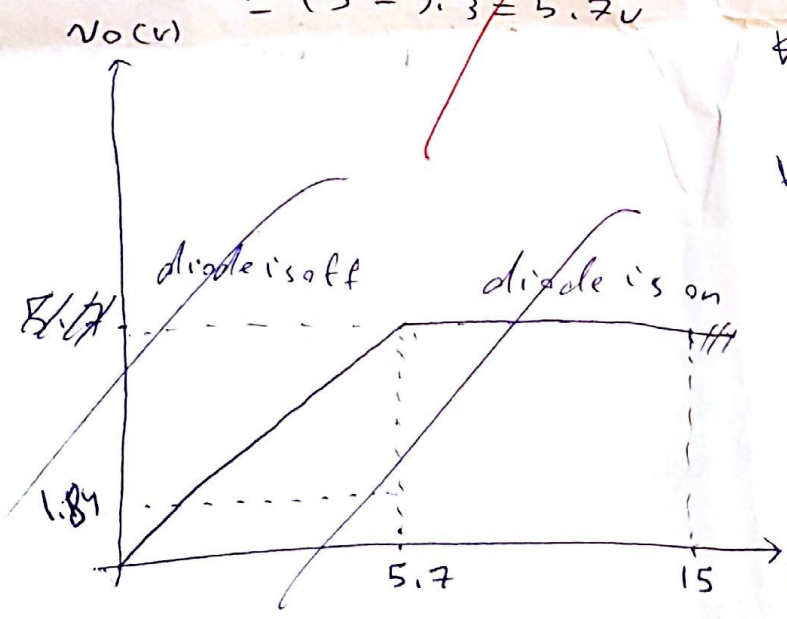

Power Unit

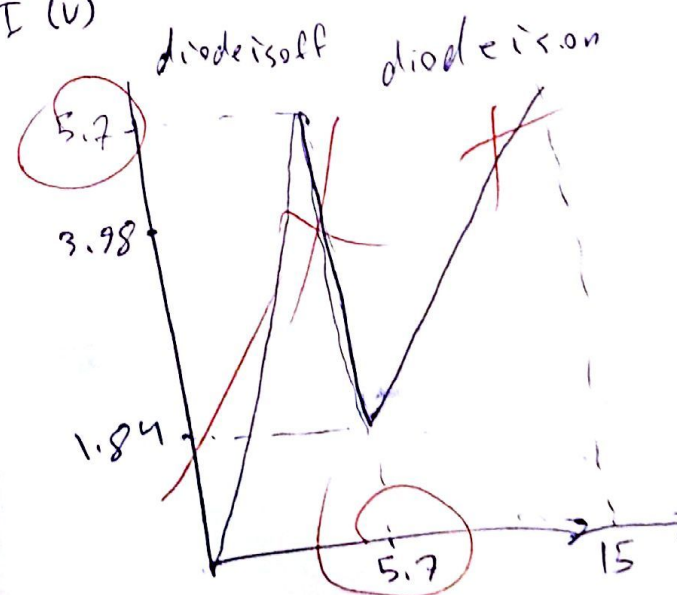

Question 7. [10-points] Design a diode clamper to generate a steady-state output voltage v_o from the input voltage v_i shown in Figure Q7

➤ Assume $V_f = 0.7V$.

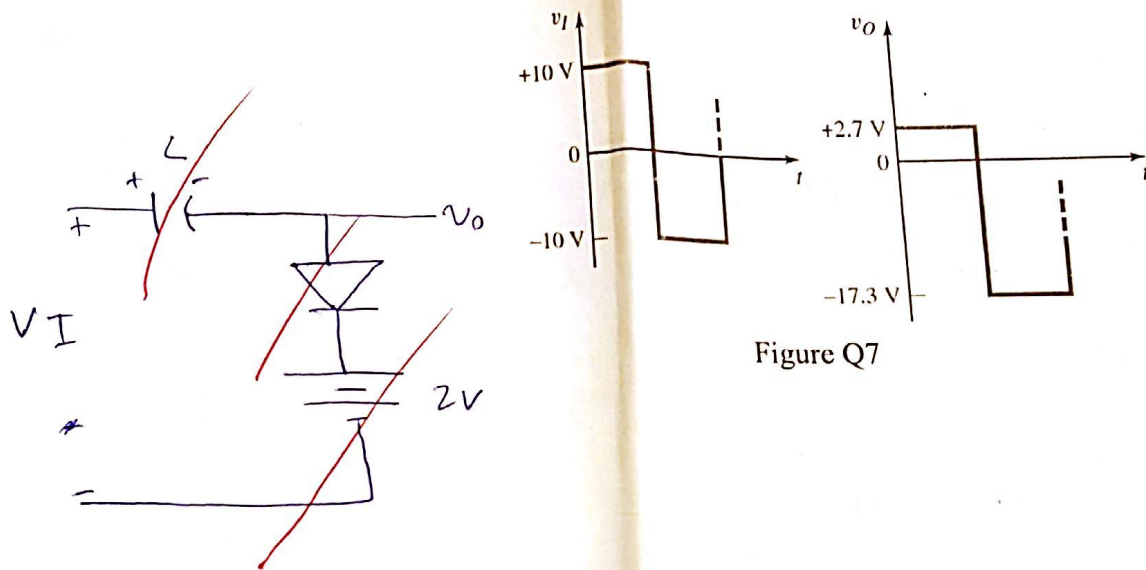


Figure Q7

Power Unit

➤ What happens if $V_f = 0V$?

