

بسم الله الرحمن الرحيم

اللهم لا سهل الا ما جعلته سهلا وانك تجعل العزيم اذا استعدت سهلا

The University of Jordan
Department of Electrical Engineering
Circuit I, EE-211
Fall 2014
First Exam


13/20
Date: Oct. 23, 2014

أ.م.د. م.ع. الدبس
أثنين (8 و 9:30)
Time: 60 Min.

Name (Arabic): [Redacted] Student # [Redacted] Section #: 1

Problem #1 (1 pt)
Find the absorbed power for each element of the following:


1. $i=3\text{ A}$ and $v=8\text{ V}$

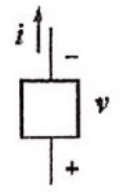

$P = IV = (3)(8) = 24\text{ W}$

(1)


2. $i=3\text{ A}$ and $v=-8\text{ V}$

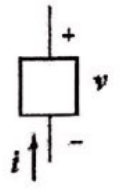

$P = IV = (-3)(+8) = (-3)(-8) = 24\text{ W}$


Problem #2 (1.5 pts)
Find R_{eq} of the following connection:

~~$R_{eq} = 3.124\ \Omega$~~

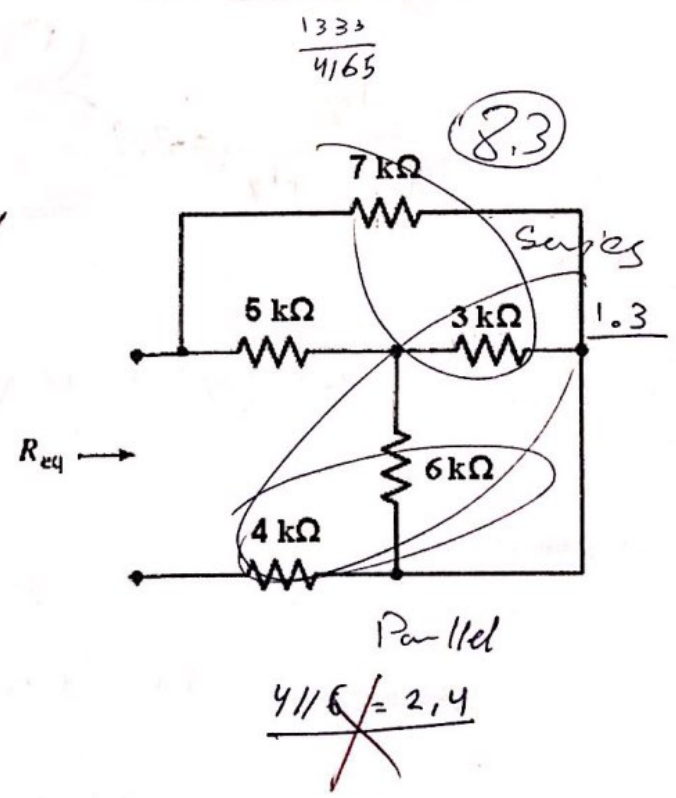

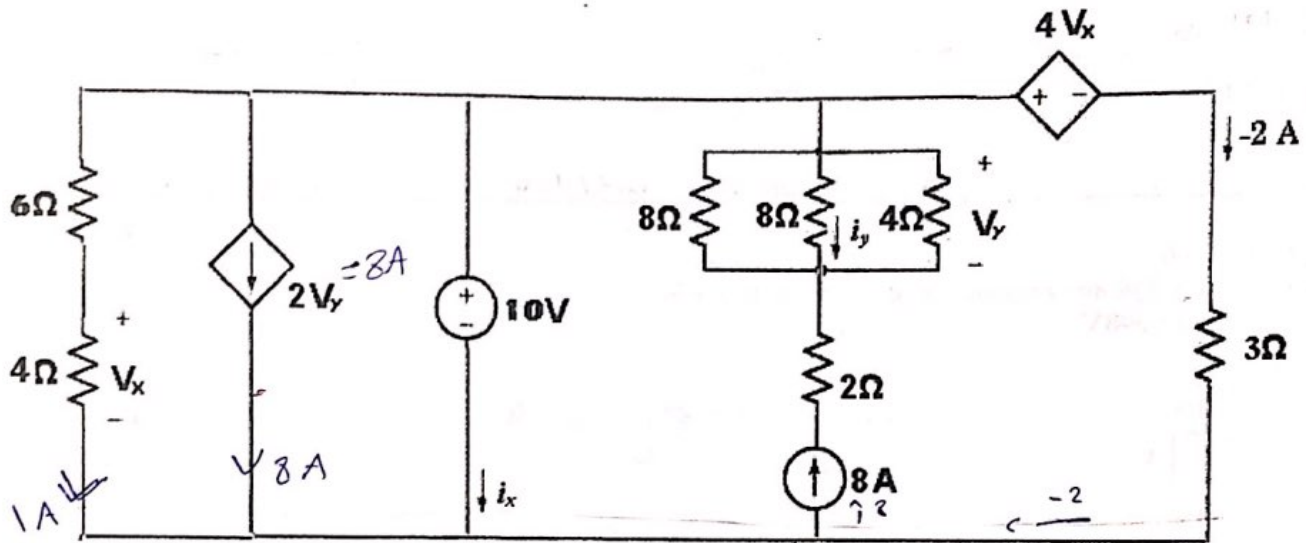Problem #3 (4.5 pts)

Don't use MESH, NODAL or SUPERPOSITION to solve the following circuit:



1. find V_x by voltage division rule only.

Node 5,5

~~$V_x = 10V$~~

$V_x = V_T \frac{4}{10} = 4V$ (1)

2. find i_y by current division rule only.

$i_y = 8 \frac{1/8}{1/8 + 1/8 + 1/4} = -2A$

$4A = 4 \cdot 2 \mu$

3. find V_y

$V_y = iR = (-4)(4) = -16V$ (1)

4. find i_x using KCL.

~~$1A + 8A$~~

$1 + 8 + i_x = 2 + 8$

$9 + i_x = 10$

$i_x = 1A$ (1)

Problem #4 (4 pts)

The Mesh Equations of the following Circuit are given by:


$$20 I_1 - 40 I_2 - 5 I_3 = V_1$$

$$-15 I_1 + 65 I_2 - 25 I_3 = -V_2$$

$$-5 I_1 - 25 I_2 + 35 I_3 = 0$$

(2)

Find R_1, R_2, R_3 and R_4 .

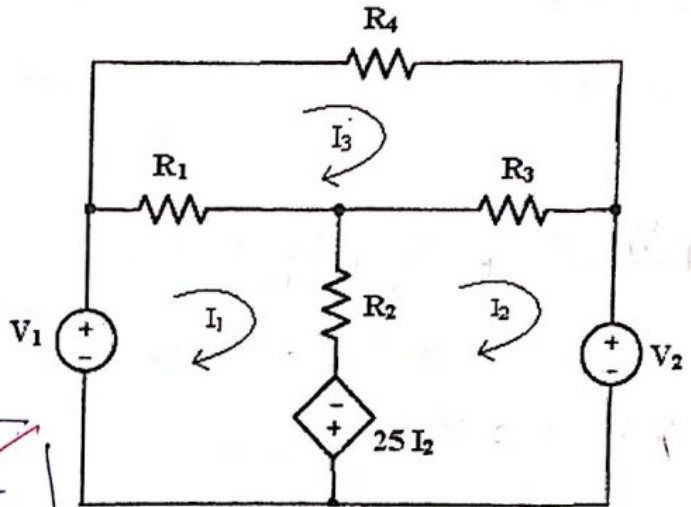

~~$R_2 = 15 \Omega$~~

$R_2 = 15 \Omega$

$R_1 = 5 \Omega$

~~$R_3 = 5 \Omega$~~

- $R_1 = 5 \Omega$
- $R_2 = 15 \Omega$
- ~~$R_3 = 5 \Omega$~~
- ~~$R_4 = 25 \Omega$~~

$$+V_1 = R_1(I_1 - I_3) + R_2(I_1 - I_2) + 25I_2$$

$$(R_1 I_1) - R_1 I_3 + R_2 I_1 - R_2 I_2 - 25 I_2$$

$$-R_2 I_2 - 25 I_2 = -40 I_2$$

(15)

$$20 I_1 = R_1 I_1 + 15 I_2$$

$$R_1(I_3 - I_1) + R_4 I_3 + R_3(I_3 - I_2)$$

$$R_1 I_3 - R_1 I_1 + R_4 I_3 + R_3 I_3 - R_3 I_2 = 0$$

~~$$5 I_3 + R_4 I_3 = 35 I_3$$~~

$$R_1 I_3 + R_4 I_3 + R_3 I_3 = 35 I_3$$

$$\downarrow \quad \quad \quad \downarrow$$

$$5 + R_4 + 15 = 35$$

~~$R_4 = 25 \Omega$~~

4



Problem #5 (5 pts)

Write the NODAL voltage equations for the following circuit (Don't solve them; just arrange them to fill the blanks below.

(KCL)

$$5 + \frac{V_1 - V_2}{12.5} + \frac{V_3}{20} + \frac{V_3 - V_4}{10} = 0 \dots$$

$$V_1 - V_3 = 100 \text{ V}$$

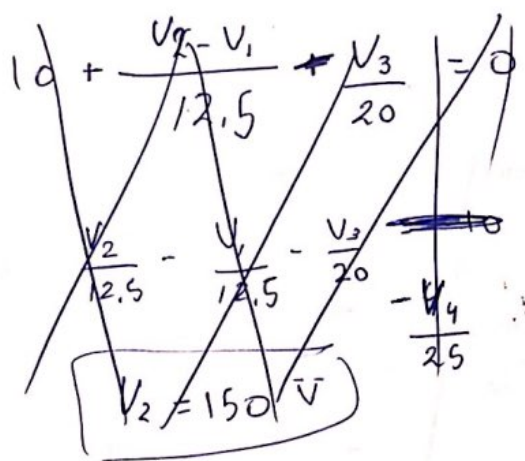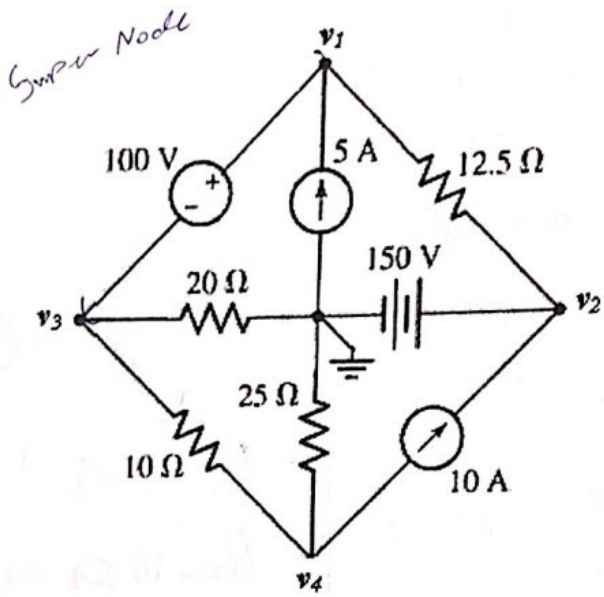

$$10 + \frac{v_2 - v_1}{12.5} = 0$$

$$10 + 0.08v_2 - 0.08v_1 = 0$$

$$\frac{v_4}{25} + \frac{v_4 - v_3}{10} = 10$$

$$0.04v_4 + 0.1v_4 - 0.1v_3 = 10$$

$$0.14v_4 - 0.1v_3 = 10$$

$$\boxed{0.08} v_1 + \boxed{-0.08} v_2 + \boxed{0.15} v_3 + \boxed{-0.1} v_4 = \boxed{-5}$$

$$-0.08 \cancel{v_1} + \cancel{0.08} v_2 + \cancel{0} v_3 + \cancel{0} v_4 = \cancel{-10}$$


$$\boxed{0} v_1 + \boxed{0} v_2 + \boxed{-0.1} v_3 + \boxed{0.14} v_4 = \boxed{10}$$

$$\boxed{1} v_1 + \boxed{0} v_2 + \boxed{-1} v_3 + \boxed{0} v_4 = \boxed{100}$$

Problem #6 (4 pts)

Use Superposition Principle to find i_x and i_y in the following circuit.

3

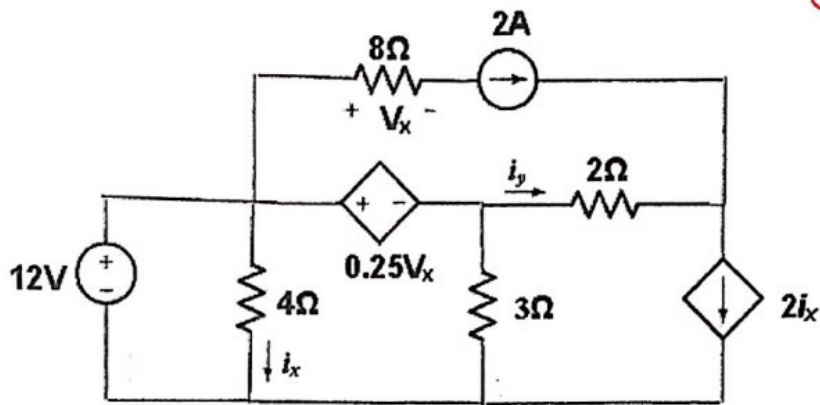

12V

$$i_x' = \frac{U}{R} = \frac{12}{4} = 3A$$

circ $V_x = 0$

$$i_y' = 2i_x = 2(3) = 6A$$

Circuits?

2A

$$i_x'' = 0$$

cuz the S.C

$$V_x = 16V$$

Volt Division

$$i_y'' = 0.8$$

$$0.25 \times 16 = 4$$

$$i_x = i_x' + i_x'' = 3A$$

$$i_y = i_y' + i_y'' = 6.8A$$