

* اللهم صل على ابي عبد الله وآلته تجعل العزرا ازا جنت *
 * اللهم رب العالمين انا كنا ظالمين *

The University of Jordan
 Department of Electrical Engineering
 Circuit I, EE-211

Fall 2014

Second Exam

بسم الله الرحمن الرحيم
 Student #: 0132436

12/30
 Dr Raed al-Zubi
 Eng. Reem Al-Debes
 Eng. Noor Awad


Date: Nov. 20, 2014

Time: 90 Min.

Name (Arabic):

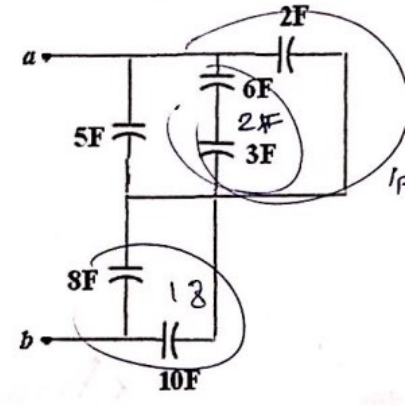Problem #1 (2 pt): Find C_{eq} between a and b



① $\frac{1}{6} + \frac{1}{3} = 2F$ ~~+~~ ~~4F~~ = $4F$
~~8 + 10 = 18F~~
 $\frac{1}{18} + \frac{1}{4} = 3.27$ + 5 =
 $C_{eq} = 8.27$



Problem #2 (2 pt): For the following circuit, find:

1) The value of the load resistor (R_L) for maximum power transfer.

② Maximum when $R_L = R_{Th}$

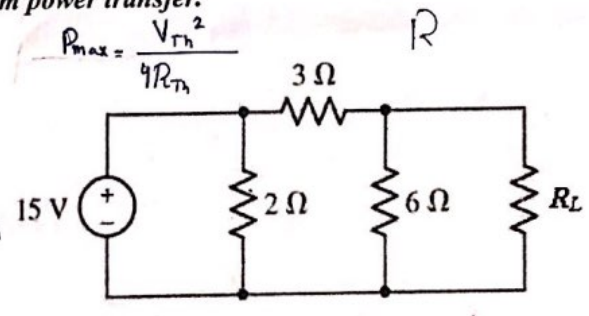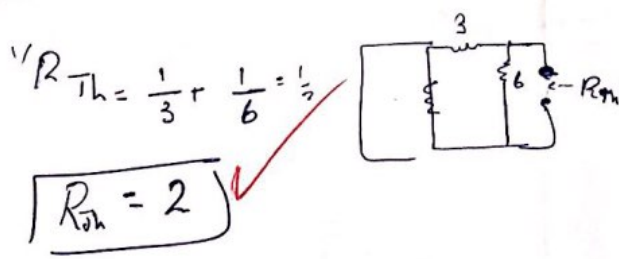


2) Calculate the value of the maximum power (P_{max}).

$V_{Th} = 10V$

$P_{max} = \frac{(10)^2}{4 \times 2} = \frac{100}{8}$


$P_{max} = 12.5 W$

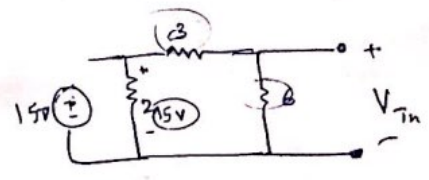

$V \neq$
 i_c



(2)

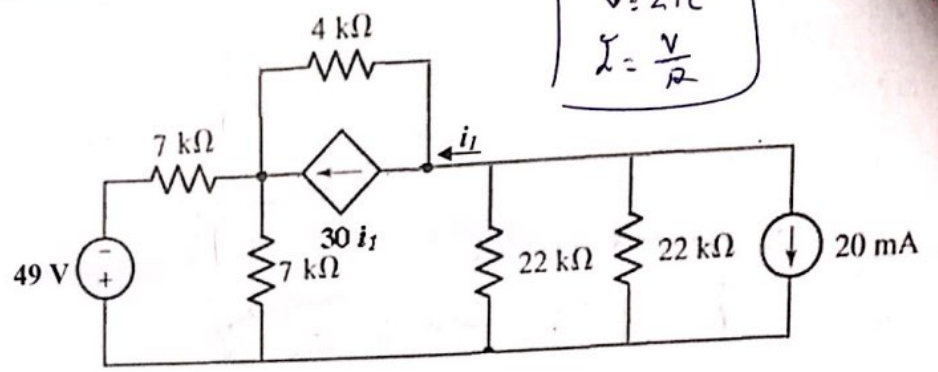Problem #3 (3 pt): Simplify the following circuit to one single loop circuit consists of: one dependent voltage source, one independent voltage source and one resistor.



$$V = IR$$

$$I = \frac{V}{R}$$

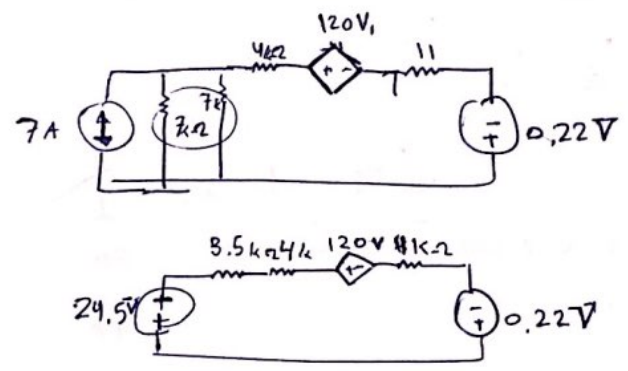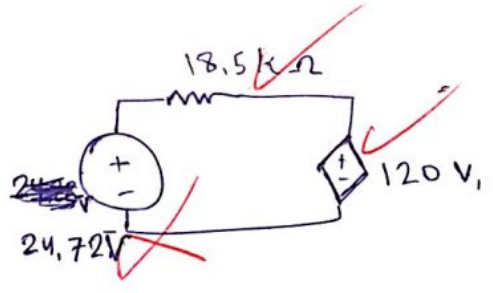

Complete


(3)

Problem #4 (3 pt): Find R_{eq} between a and b.


$$R_A = \frac{6.125}{12.25} = 0.5 \Omega$$

$$R_B = \frac{24.5}{12.25} = 2 \Omega$$

$$R_C = \frac{12.25}{12.25} = 1 \Omega$$


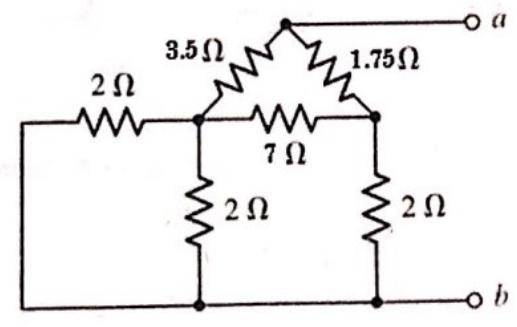


$$R_{eq} = 2 \Omega$$

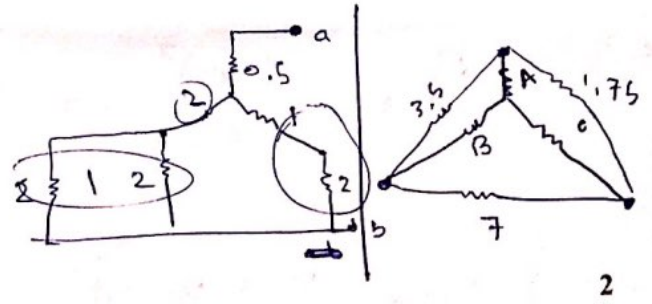


$$R_{eq} = \left(3 \parallel (3 + 0.5) \right) + 2 =$$

Problem #5 (4 pt): Given the following:

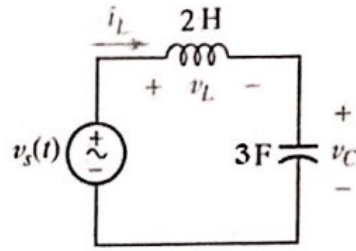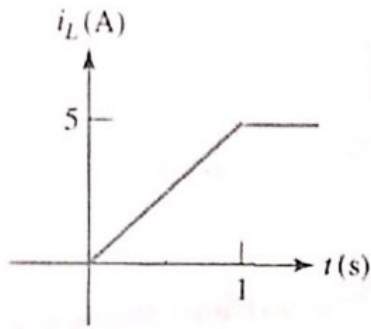

1) Draw $v_L(t)$

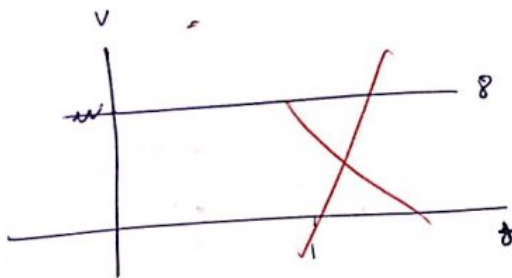

$$V_L = L \frac{di}{dt}$$

$$L = 2 \text{ H}$$

$$i = 5t$$

$$2 \times 4$$

$$V_L = 8$$

2) Find $v_C(t)$ for $t \geq 0$, if $v_C(0) = 0$

$$V_C = \frac{1}{3} \int_{t_0}^t 5 \, dt + 0$$

$$V_C = \frac{1}{C} \int_{t_0}^t di \, dt + V_C(t_0)$$

0.5


3) Find the energy stored in the inductor $w_L(t)$ for $0 < t < 1$ if $w_L(0) = 0 \text{ J}$

$$E = \frac{1}{2} L i_C^2$$

0.5



0.5

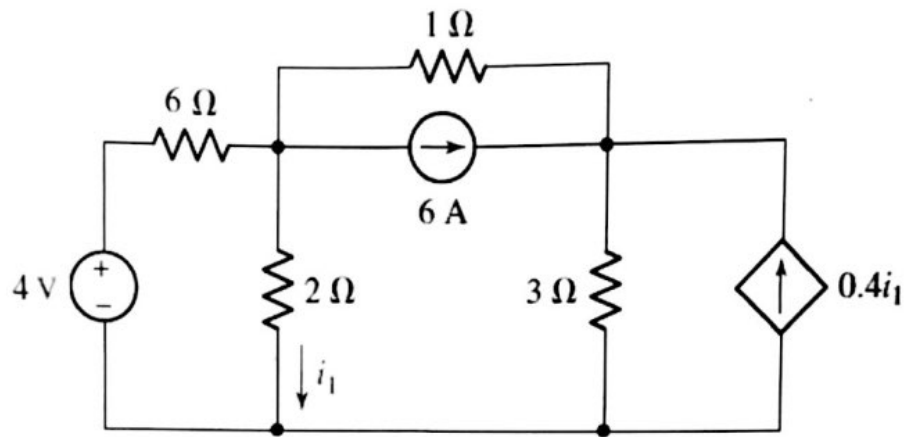Problem #6 (5 pt): For the circuit shown below, find the values of V_{th} and I_N seen by the $(2\ \Omega)$ resistor.




$V_{Th} = 4V$

$I_{s.c} = 0.6A$

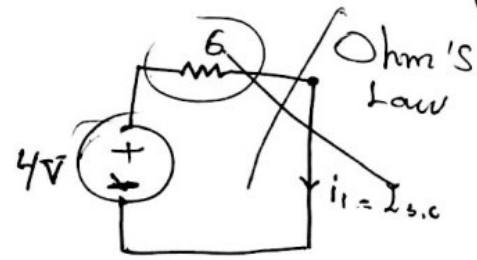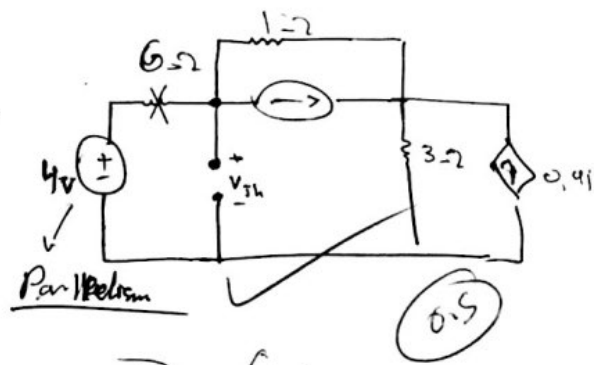

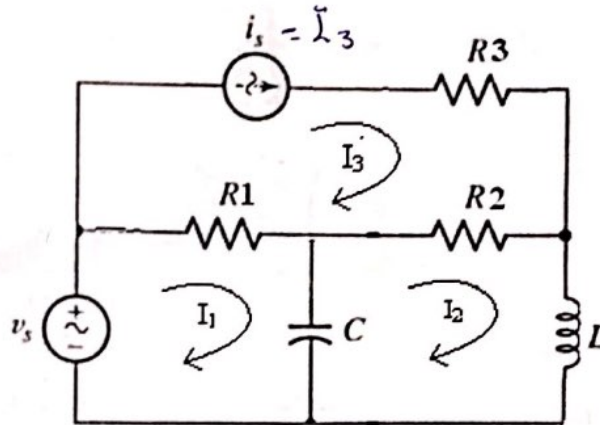Problem #7 (3 pt): Write the Mesh equations for the following circuit for $t \geq 0$ (no need to solve them):



For Mesh1:

$$-V_s(t) + R_1(I_1 - I_3) + \frac{1}{C} \int_{t_0}^t d(I_1 - I_2) + V(t_0) = 0$$

For Mesh2:

$$-\frac{1}{C} \int_{t_0}^t d(I_2 - I_1) + V(t_0) + R_2(I_2 - I_3) + L \frac{d(I_2)}{dt} = 0$$


For Mesh3:

~~$$I_3 R_3 + R_1(I_3 - I_2) = I_3 R_3 + R_1(I_3 - I_2) + R_1(I_3 - I_1)$$

$$I_3 R_3 + R_1(I_3 - I_2)$$~~


0.5

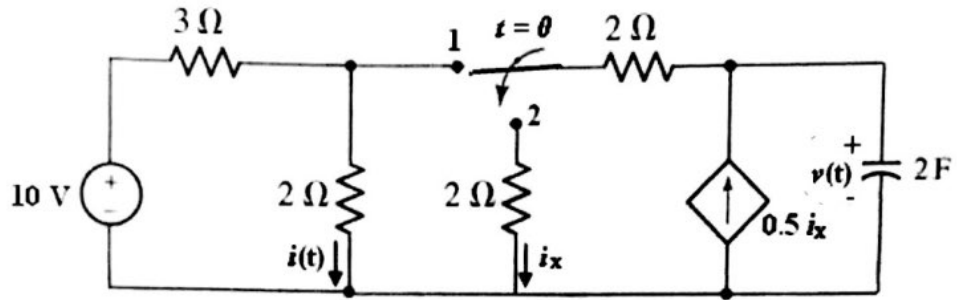Problem #8 (8 pt): For the following circuit, the switch is moved from position 1 to position 2 at $t=0$. Find:




1) The time constant τ

$\tau = RC$ (0.5)
 R_{eq}

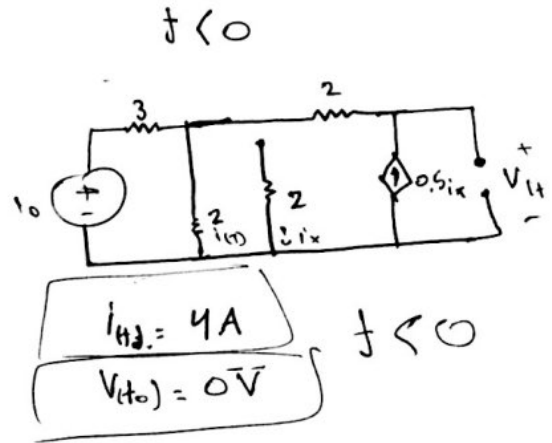

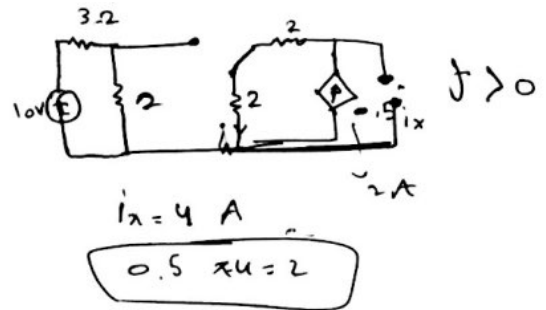2) $v(t)$ for all t

$v(t) \begin{cases} 0 & , t < 0 \\ 0 & , t > 0 \end{cases}$



3) $i(t)$ for all t

$i(t) \begin{cases} 4A & , t < 0 \\ 4A & , t > 0 \end{cases}$