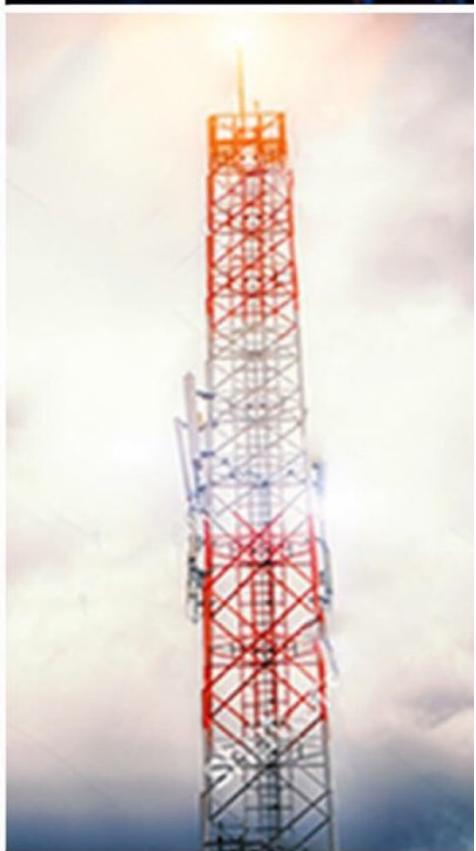


# PROTECTION

DR.EYAD A.FILAT  
BY: ANOUD AL-HALLAQ




POWERUNIT-JU.COM





# Protection

6/2 TUE

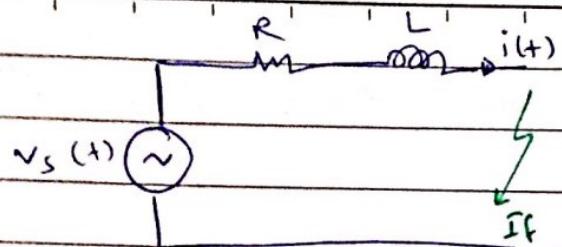

$$v_s(t) = R i + L \frac{di}{dt}$$

$$i(t) = i_{ss} + i_{tr}$$

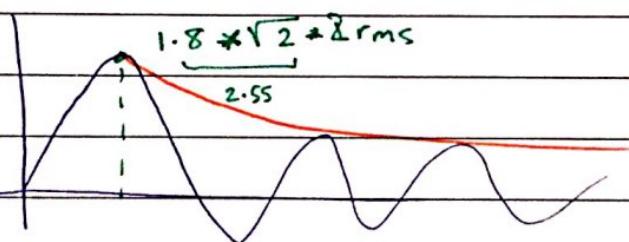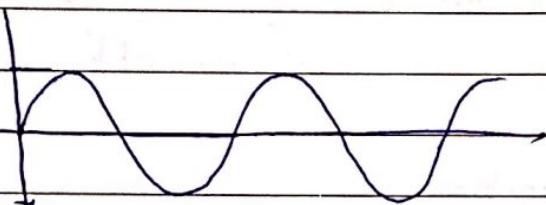

II

8/2 Thur

Fuses : over current device


contactor ←



\* ↑ current → arc → open

\* TCC :-

\* current = zero → arc





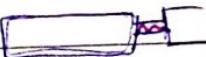


(Zero = current) → arc → arc is broken due to current &  
Switch OFF ←

\* Recloser → circuit breaker

2)

20/12 TUE

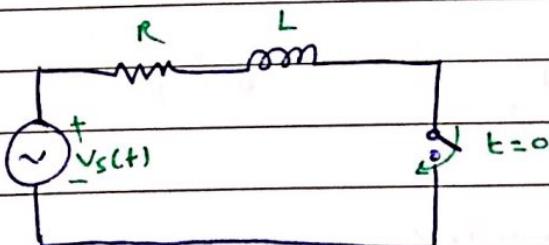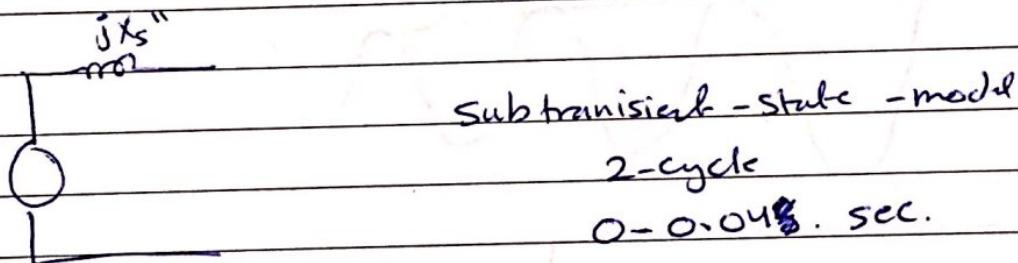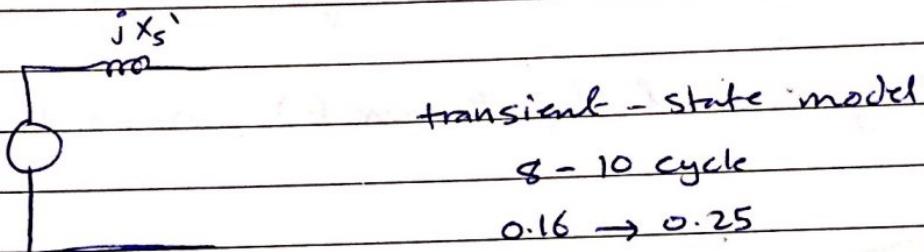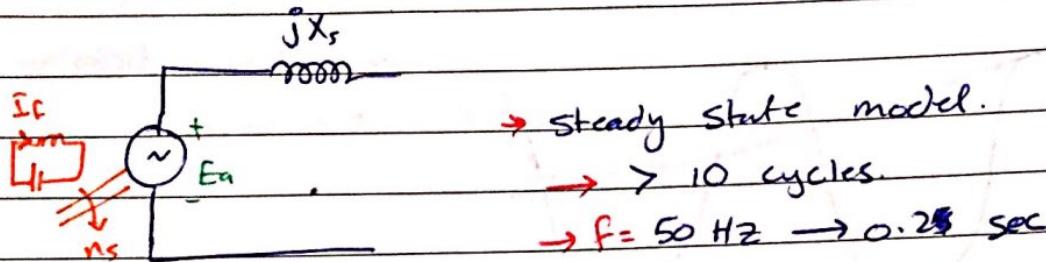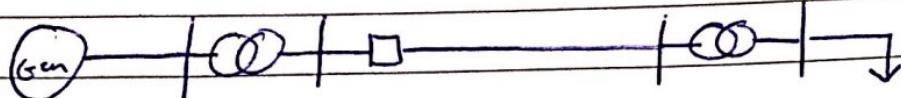

$$V_s(t) = V_m \sin(\omega t + \alpha)$$

$$i(t) = i_{ss} + i_{tr}$$

$$= \frac{\sqrt{2} V_m}{|Z|} \sin(\omega t + \alpha + \Theta) + \frac{\sqrt{2} V_m \sin(\alpha - \Theta)}{|Z|} e^{-\frac{t}{T}}$$

Steady state ↪


transient

$$|Z| = \sqrt{R^2 + (\omega L)^2}$$


$$\Theta = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

③

$$\Rightarrow T = \frac{L}{R}$$

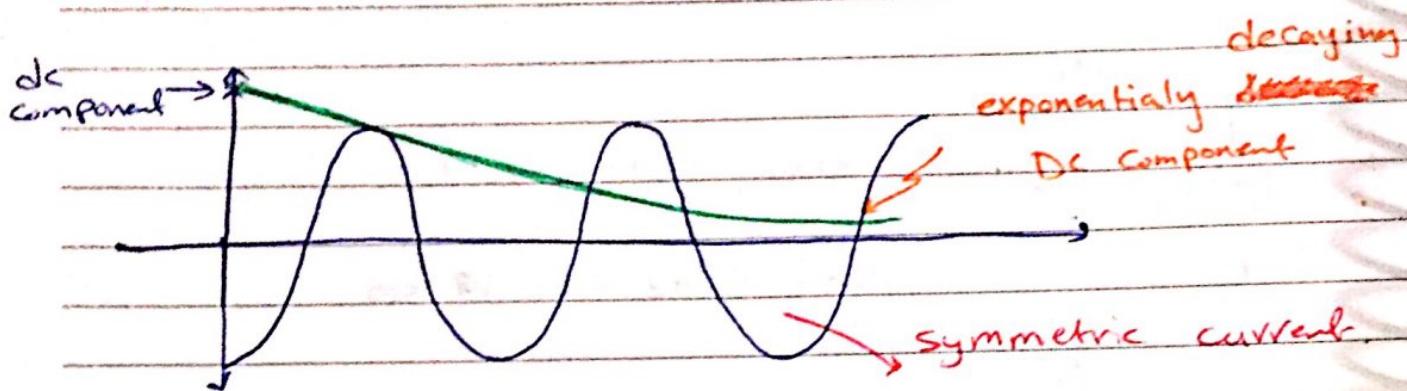

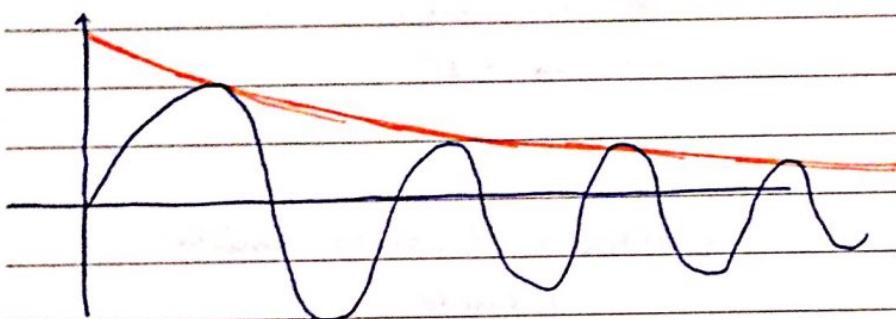$I_m$  = making current (peak current), momentary current



$$I_m = 2.55 \times I_{\text{breaking}} \\ \hookrightarrow 1.8 \times \sqrt{2}$$

where  $I_{\text{breaking}}$  in peak value

$$I = 1.6 \times I_{\text{breaking}} \Rightarrow I_{\text{breaking}} = \frac{X}{\sqrt{2}} \text{ (RMS current)}$$

$$I_{\text{breaking}} = K \times I_{\text{symmetric}}$$

$$① K = 1.4 \rightarrow 2 \text{ cycle C.B}$$

$$② K = 1.2 \rightarrow 3 \text{ cycle C.B}$$

$$③ K = 1.1 \rightarrow 5 \text{ cycle C.B}$$

$$④ K = 1.0 \rightarrow 8 \text{ cycle C.B}$$


④

Five Apple

Refer to Stevenson p. 402 (C.B selection).

### Tutorial \*1] 8

Q1

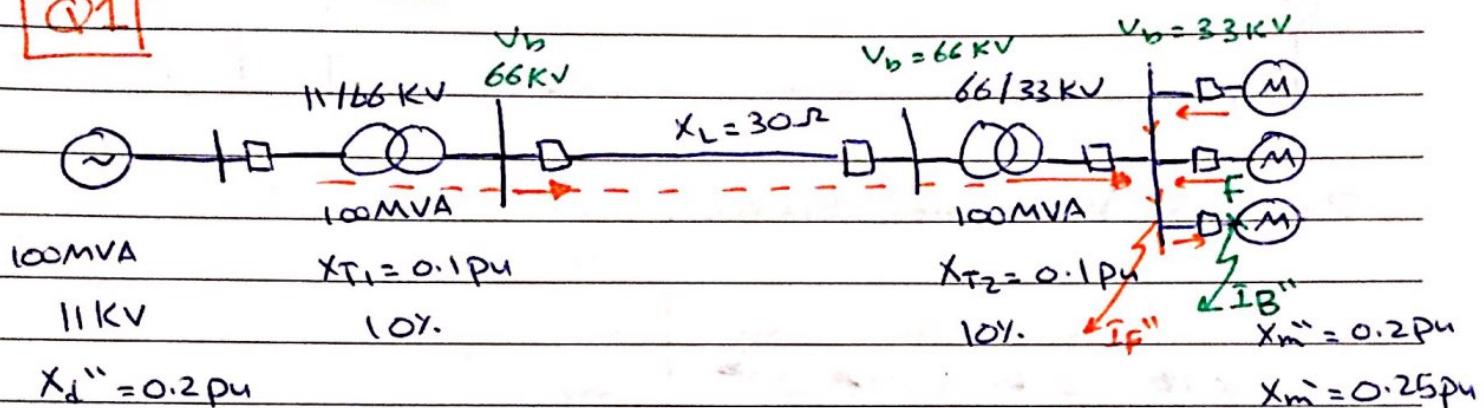


Find  $I_F''$  ?!

$I_{SC''} = \frac{E}{X_d''}$

$I_{SC'} = \frac{E}{X_d'}$


$I_{SC} = \frac{E}{X_s}$

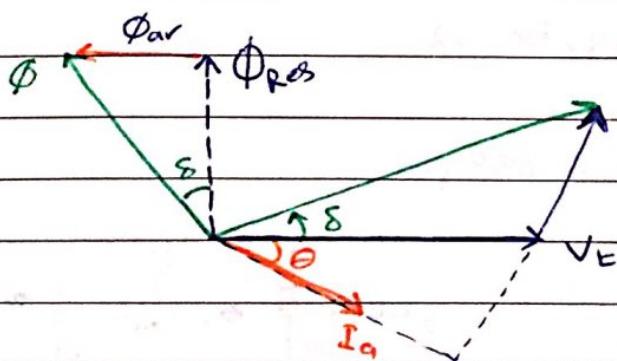


~~Breaker~~  $I_{breaker} = I_{\text{steady state}}$ .

5

## Subtransient fault:-

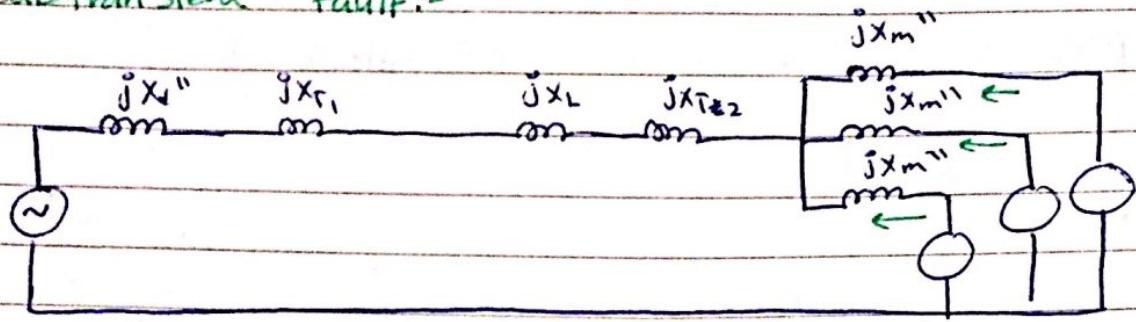

$Z_{th} \rightarrow$  Kill the Source.

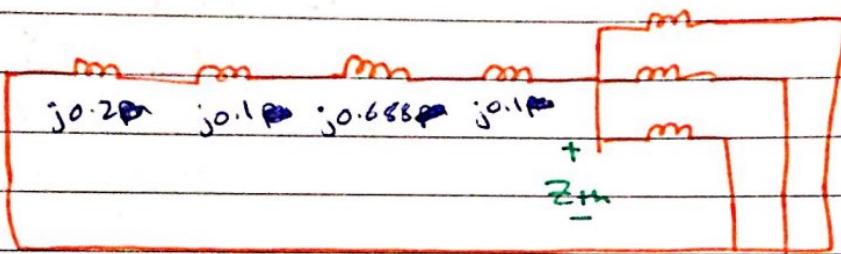

$$Z_{th} = (X_d'' + X_{T1} + X_L + X_{T2}) // \frac{X_m''}{3}$$

$$X_d'' = 0.2 \text{ pu}$$

$$X_{T1} = 0.1 = X_{T2}$$

$$X_L = 30 \Omega$$


$$\hookrightarrow X_L \text{ pu} = \frac{(66)^2}{100} = 43.56 \Omega$$

$$X_L \text{ pu} = \frac{30}{43.56} = 0.688 \text{ pu.}$$

$$X_m'' = \frac{S_{new}}{S_{old}} * X_m'' \text{ old}$$

$$= \frac{100}{20} \approx 0.2 = 1 \text{ pu}$$
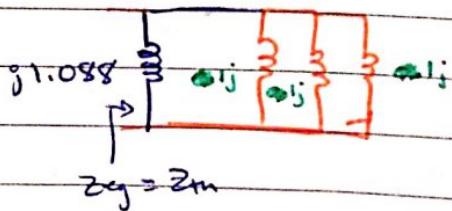
$$\frac{1}{Z_{eq}} = \frac{1}{1.088} + \frac{1}{1.0} + \frac{1}{1.0} + \frac{1}{1.0}$$



6

$$\frac{1}{Z_{eq}} = 3.92 = \hat{I}_F''$$

$$Z_{eq} = j0.255 \text{ pu}$$

$$V_{th} = 1.0 \text{ pu.}$$

$$\hat{I}_F'' = \frac{1 \text{ V}}{Z_{eq}} = \frac{1}{j0.255} = -j3.92 \text{ pu}$$

$$I_b = \frac{S_b}{\sqrt{3} V_b} = \frac{100 \times 10^3}{\sqrt{3} \times 33 \times 10^3} = 1.75 \text{ kA}$$

$$| \hat{I}_F'' | = 3.92 \text{ pu.}$$


$$\hat{I}_F'' = 3.92 \times 1.75 \text{ k} = 6.85 \text{ kA}$$

symmetry current (RMS)


$$\hat{I}_B'' = \hat{I}_F'' \times [1.088 / 0.5] \xrightarrow{0.34} 0.34$$

0.34 + 1.0

$$\hat{I}_B'' =$$

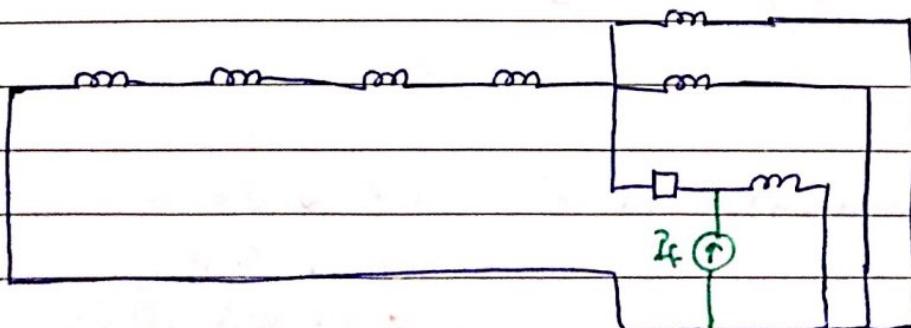

[7]

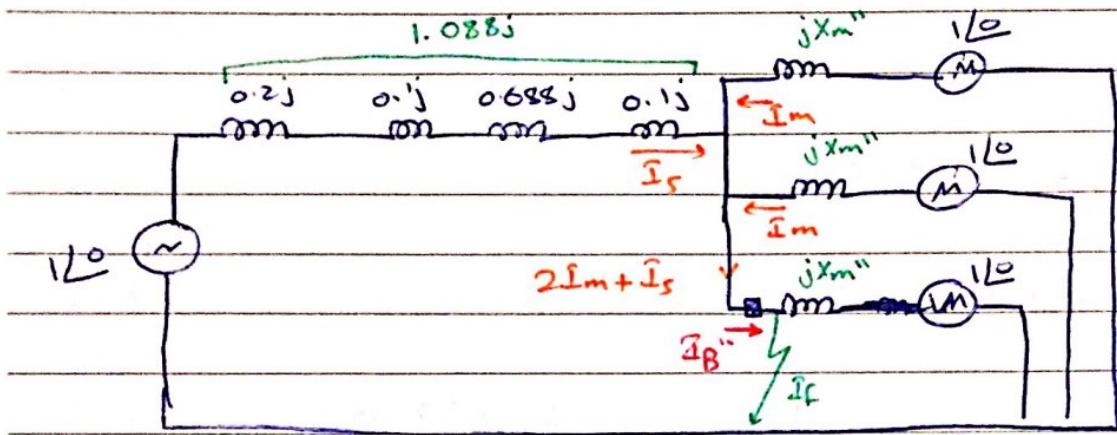


$$I_B'' = \frac{1}{j0.1088} + \frac{1}{j1} + \frac{1}{j1}$$

$$= -j0.92 + j2$$

$$= -j2.92 \text{ pu}$$

$$|I_B''| = 2.92 \times 1.75 \text{ kA}$$

$$= 5.11 \text{ kA}$$

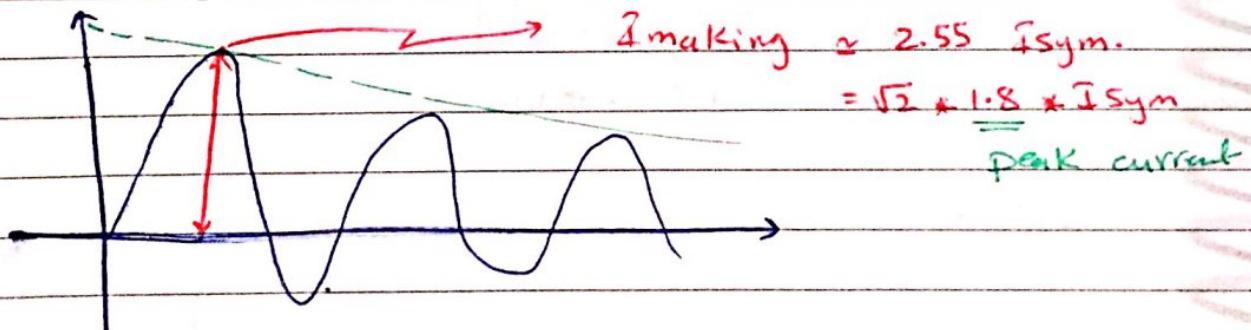

$$I_{mm} (momentary) = I_{B''}^{rms} = 1.6 \times I_{sym}$$

$$= 1.6 \times 5.11$$

$$= 8.17 \text{ kA (RMS value)}$$

8

$I_{\text{interrupting}} = K \cdot I_{\text{symm}}$

CB

$\hookrightarrow I_{\text{breaking}}$

for 2-cycle CB  $\rightarrow K = 1.4$

3-cycle CB  $\rightarrow K = 1.3$

5 cycle CB  $\rightarrow K = 1.1$

8 cycle CB  $\rightarrow K = 1.0$

Use transient reactance :-

$x_m' = 0.25 \Rightarrow$  at (20MVA, 33KV base.)

$$x_m'_{\text{new}} = 0.25 \times \frac{100}{5} = 1.25 \text{ pu} \quad (100 \text{ kVA}, 33 \text{ KV base})$$

$$I_f'_{\text{bus}} = \frac{1}{j1.088} + \frac{3}{j1.25} = 0.42 + 2.4j$$

$$I_f'_{\text{bus}} = 3.32 \text{ pu}$$

$$I_f'_{\text{bus}} = 3.32 \times 1.75 \text{ K}$$

$$I_f'_{\text{bus}} = 5.81 \text{ KA}$$

$$I_f'_{\text{Break}} = \frac{1}{j1.088} + \frac{1}{j1.25} + \frac{1}{j1.25}$$

9

$$I_f^{\text{break}} = 0.92 + 2 \times 0.8 \\ = 2.52 \text{ pu}$$



$$I_f^{\text{breaker}} = K * 2.52 * 1.75K \\ = K * 4.41 \text{ KA}$$

① 2 cycle  $\Rightarrow I_f^{\text{breaker}} = 1.4 * 4.41 \text{ KA} = 6.17 \text{ KA}$

② 3-cycle  $\Rightarrow I_f^{\text{breaker}} = 1.3 * 4.41 \text{ KA} = 5.6 \text{ KA}$

③ 5-cycle  $\Rightarrow I_f^{\text{breaker}} = 1.1 * 4.41 \text{ KA} = 4.85 \text{ KA}$

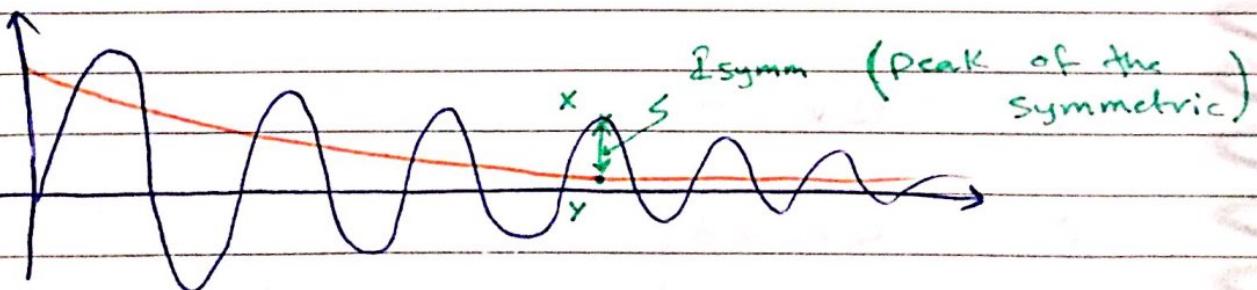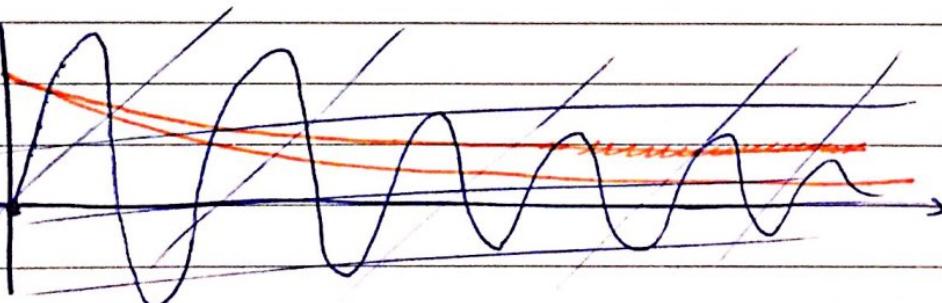
④ 8-cycle  $\Rightarrow I_f^{\text{breaker}} = 1.0 * 4.41 \text{ KA} = 4.41 \text{ KA}$




\*  $I_{\text{int, interrupting}} = \sqrt{\left(\frac{x}{\sqrt{2}}\right)^2 + y^2}$  in Americ. (USA)

\*  $I_{\text{int}} = \frac{x}{\sqrt{2}}$  in Europe.

10

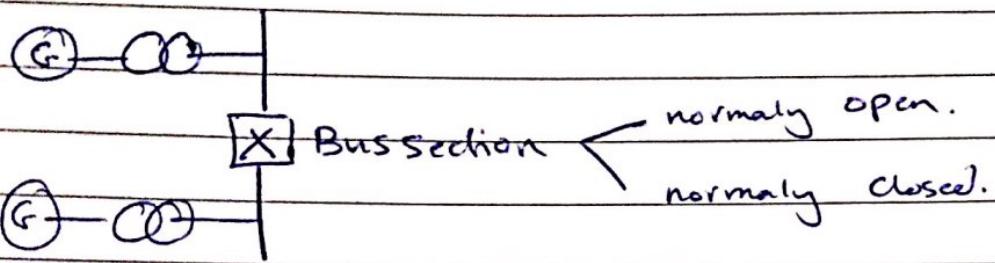

if normally open.  $\rightarrow$

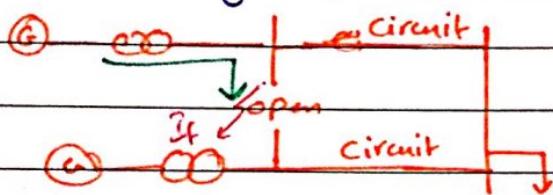

$b_1 s_1 = b_2 s_2$  ... اذ اذ

no short  $\leftarrow$  fault  $\rightarrow$   
no contribution.


open  $\rightarrow$  volt level.  $v_{bus} \approx 1^*$

... اذ اذ if CB close  $\rightarrow$  bus 1 is \*

**Question # 1**

A 100 MVA, 11 kV generator with  $X_d'' = 0.2 \text{ pu}$  is connected through a transformer, and line to a busbar that supplies three identical motor as shown below and each motor has  $X_m'' = 0.2 \text{ pu}$  and  $X_m' = 0.25 \text{ pu}$  on a base of 20 MVA, 33 kV. The bus voltage at the motors is 33 kV when a three-phase fault occurs at the point  $F$ . Choose 100 MVA base and 11 kV base at the generator and calculate:

- the subtransient current in the fault,  $I_f''$ .
- the subtransient current in the circuit breaker  $B$ ,  $I_B''$ .
- the momentary current in the circuit breaker  $B$ ,  $I_{Bmom}$ .
- the current to be interrupted by circuit breaker  $B$ ,  $I_{Bint}$  in
  - 2 cycles ( $K=1.4$ ), (i) 3 cycles ( $K=1.2$ ), (iii) 5 cycles ( $K=1.1$ ), (iv) 8 cycles ( $K=1.0$ ),

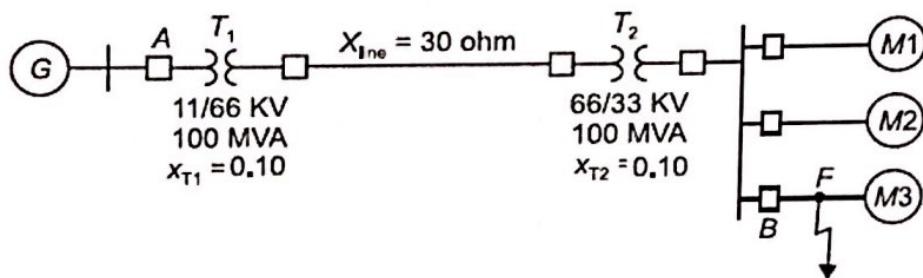**Solution:**



$$x_g'' = j0.20 \text{ pu.}$$

$$x_m'' = x_{m1}'' = x_{m2}'' = x_{m3}'' = j0.2 \times \frac{100}{20} = j1.0 \text{ pu.}$$

$$x_m' = x_{m1}' = x_{m2}' = x_{m3}' = j0.25 \times \frac{100}{20} = j1.25 \text{ pu.}$$

$$x_{T1} = x_{T2} = j0.10 \text{ pu}$$
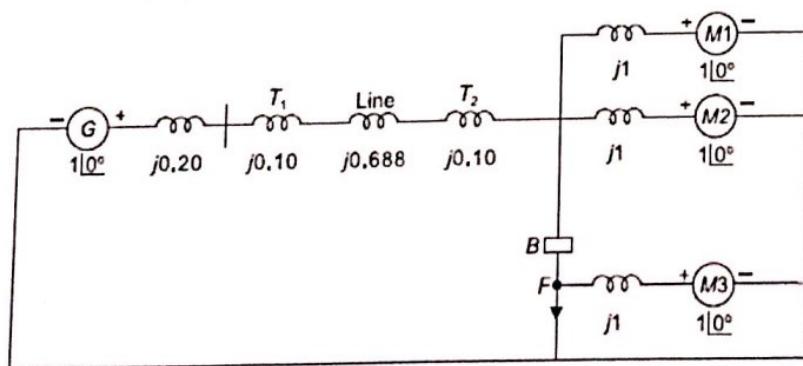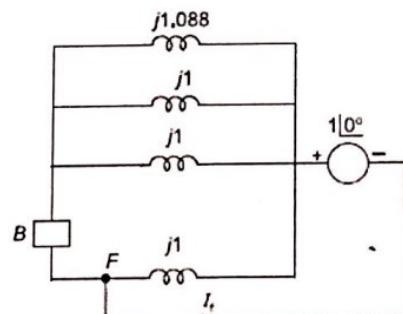
$$x_{line} = 30 \times \frac{100}{(66)^2} = j0.688 \text{ pu.}$$



$$\therefore x_{eq} = \frac{j}{3.919} = j0.255$$

$$\therefore I_f = \frac{1|0^\circ}{j0.255} = -j3.919 \text{ pu.}$$

Base current for 33 KV circuit

$$I_B = \frac{100 \times 1000}{\sqrt{3} \times 33} = 1.75 \text{ KA.}$$

$$\therefore |I_f| = 3.919 \times 1.75 = 6.85 \text{ KA.}$$

(b) Current through circuit breaker *B* is,

$$I_{fb} = \frac{2}{j1} + \frac{1}{j1088} = -j2.919 \text{ pu}$$

$$\therefore |I_{fb}| = 2.919 \times 1.75 = 5.108 \text{ KA.}$$

(c) Momentary current can be calculated by multiplying the symmetrical momentary current by a factor of 1.6 to account for the presence of DC off-set current.

$\therefore$  Momentary current through breaker *B*

$$= 1.6 \times 5.108 \text{ KA} = 8.17 \text{ KA.}$$

(d) For computing the current to be interrupted by the breaker, motor  $x_m''$  ( $x_m'' = j1.0$ ) is now

replaced by  $x_m'$  ( $x_m' = j1.25$  pu). The equivalent circuit is shown in Fig. 8.13(c).

$$x_{eq} = j0.3012$$

Current to be interrupted by the breaker

$$I_f' = \frac{1}{j0.3012} = -j3.32 \text{ pu}$$

Allowance is made for the DC off-set value by multiplying with a factor of (i) 1.4 for 2 cycles (ii) 1.2 for 3 cycles (iii) 1.1 for 5 cycles (iv) 1.0 for 8 cycles.


Therefore, current to be interrupted as:

$$(i) 1.4 \times 3.32 \times 1.75 = 8.134 \text{ KA}$$

$$(ii) 1.2 \times 3.32 \times 1.75 = 6.972 \text{ KA}$$

$$(iii) 1.1 \times 3.32 \times 1.75 = 6.391 \text{ KA}$$
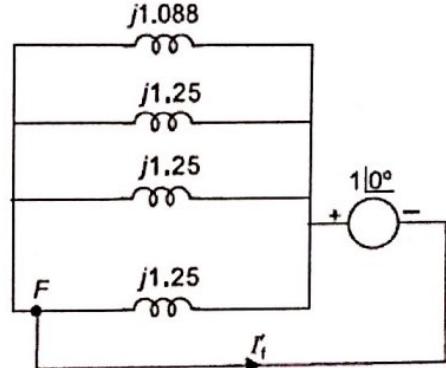
$$(iv) 1.0 \times 3.32 \times 1.75 = 5.81 \text{ KA.}$$



## Question # 2


A generating station feeding a 220 KV system is shown below. Determine the total fault current, fault level and fault current supplied by each generator for a three phase fault at the receiving end of the line.

$G_1 : 11 \text{ KV, } 100 \text{ MVA, } x'_{g1} = j0.15$

$G_2 : 11 \text{ KV, } 75 \text{ MVA, } x'_{g2} = j0.125$

$T_1 : 100 \text{ MVA, } x_{T1} = j0.10, 11/220 \text{ KV}$

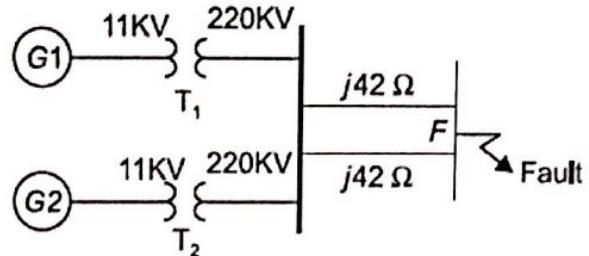$T_2 : 75 \text{ MVA, } x_{T2} = j0.08, 11/220 \text{ KV}$



### Solution:

Let base MVA = 100, Base voltage = 11 KV.

$$x'_{g1} = j0.15, \quad x_{T1} = j0.10$$


$$x'_{g2} = j0.125 \times \frac{100}{75} = j0.166$$

$$x_{T2} = j0.08 \times \frac{100}{75} = j0.106$$

$$= j42 \times \frac{100}{(220)^2} = j0.0867 \text{ pu.}$$

Per unit reactance of each line

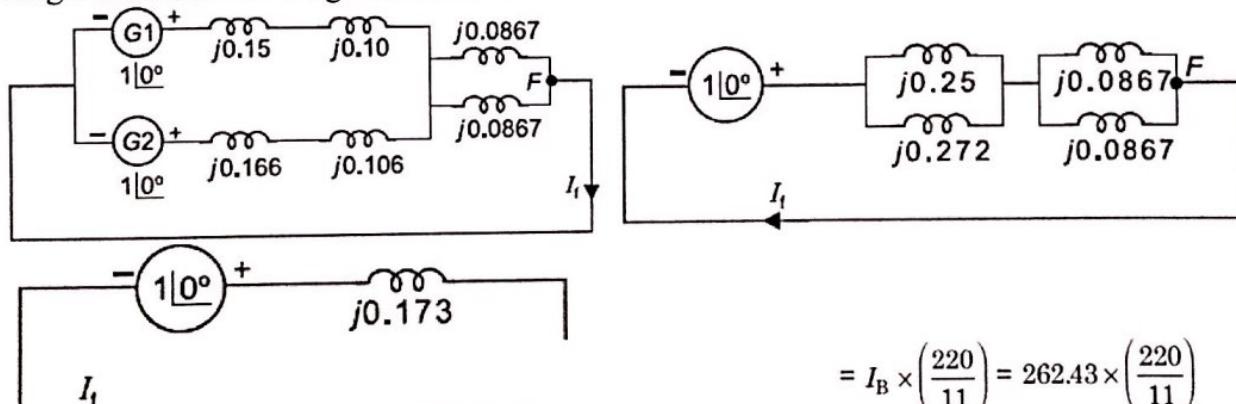Single line reactance diagram is shown below



$$I_f = \frac{1}{j0.173} = -j5.78 \text{ pu}$$

Base current for 220 KV side

$$= I_B \times \left( \frac{220}{11} \right) = 262.43 \times \left( \frac{220}{11} \right)$$

$$= 5248.6 \text{ Amp.}$$

Fault current supplied by the two generators

$$= 5248.6 \times (-j5.78) = 30.34 \angle -90^\circ \text{ KA}$$

$$\therefore I_{fg1} = \frac{0.272}{0.522} \times 30.34 \angle -90^\circ \text{ KA}$$

$$\therefore I_{fg1} = 15.8 \angle -90^\circ \text{ KA}$$

$$I_{fg2} = \frac{0.25}{0.522} \times 30.34 \angle -90^\circ \text{ KA}$$

$$\therefore I_{fg2} = 14.53 \angle -90^\circ \text{ KA}$$

### Question # 3

Two generating stations are connected together through transformers and a transmission line as shown below. If a three phase fault occurs as shown below, calculate the fault current.

$G_1$  : 11 KV, 40 MVA, 15%

$G_2$  : 11 KV, 20 MVA, 10%


$G_3$  : 11 KV, 20 MVA, 10%

$T_1$  : 40 MVA, 11/66 KV, 15%

$T_2$  : 40 MVA, 66/11 KV, 15%

$T_3$  : 5 MVA, 11/6.6 KV, 8%

Line reactance = 40 ohm.

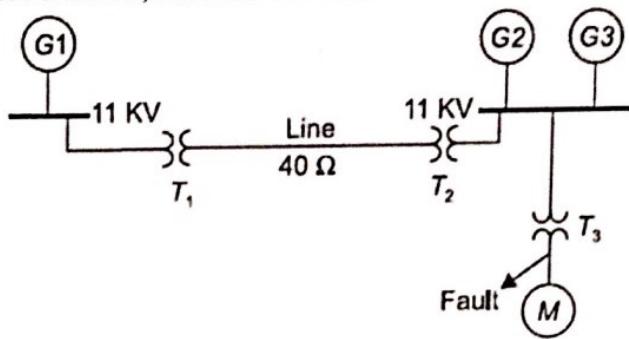

### Solution:

Set Base MVA = 40, Base Voltage = 11 KV

$$\therefore x_{g1} = j0.15 \text{ pu},$$

$$x_{g2} = j \frac{40}{20} \times 0.10 = j0.20 \text{ pu}$$

$$x_{g3} = j0.10 \times \frac{40}{20} = j0.20 \text{ pu}$$

$$x_{T1} = j0.15 \text{ pu}$$

$$x_{T2} = j0.15 \text{ pu}$$

$$x_{T3} = j0.08 \times \frac{40}{5} = j0.64 \text{ pu}$$


$$x_{\text{line}} = j40 \times \frac{40}{(66)^2} = j0.367 \text{ pu.}$$

Circuit model for fault calculation is shown below.


$$I_f = \frac{1|0^\circ}{j0.729} = -j1.37 \text{ pu}$$

$$\begin{aligned} \text{Base current } I_B &= \frac{40 \times 1000}{\sqrt{3} \times 11} \\ &= 2099.45 \text{ Amp} \end{aligned}$$

$$\begin{aligned} |I_f| &= 1.37 \times 2099.45 \\ &= 2.876 \text{ KA} \end{aligned}$$

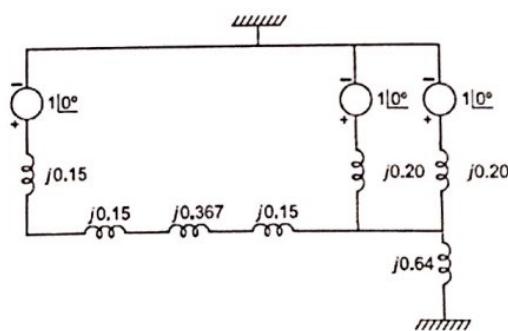



11KV

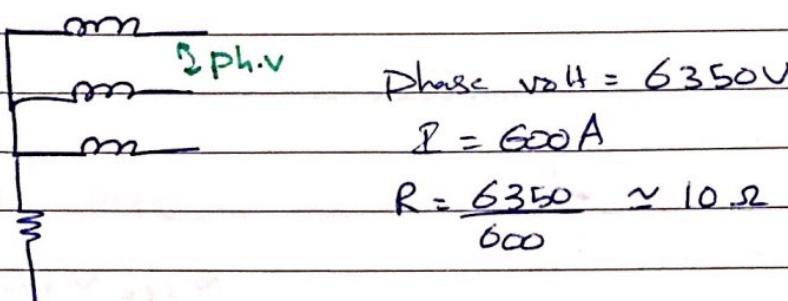



slide 22:-

$\Rightarrow$  In H.V side  $\rightarrow$  current  $I \downarrow$   
59G  $\rightarrow$  over voltage relay.

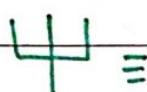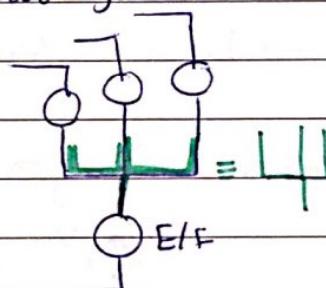 = earthing between neutral and ground.  
 $\rightarrow$  residual connection



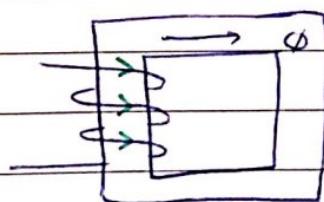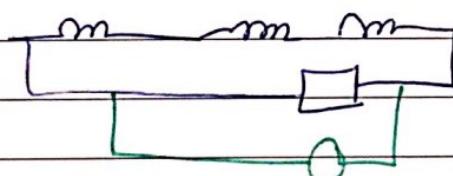$\Rightarrow$  1 delta broken  
unbalance, L-G fault



$L = \text{flux leakage per unit current}$

$$NI = \Phi R$$

$$R = \frac{L}{MA}$$


$$L = \frac{N^2}{R}$$

Inductance  $\downarrow \rightarrow$   $\uparrow$  airgap.


12

Five Apple
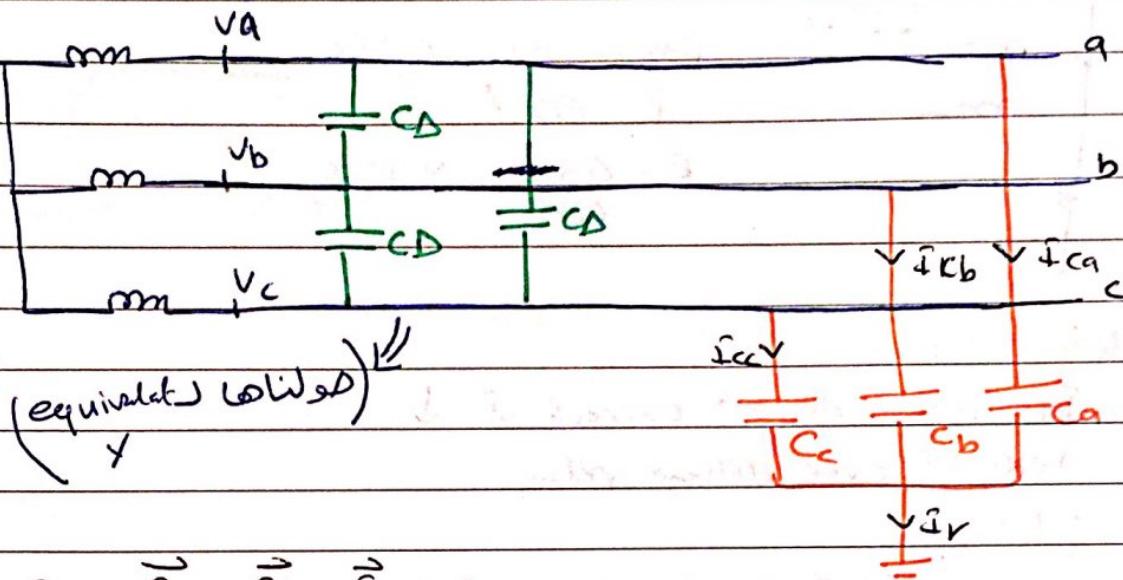
## Ungrounded neutral (2 isolated) $\Delta$



Phasor diagram:-

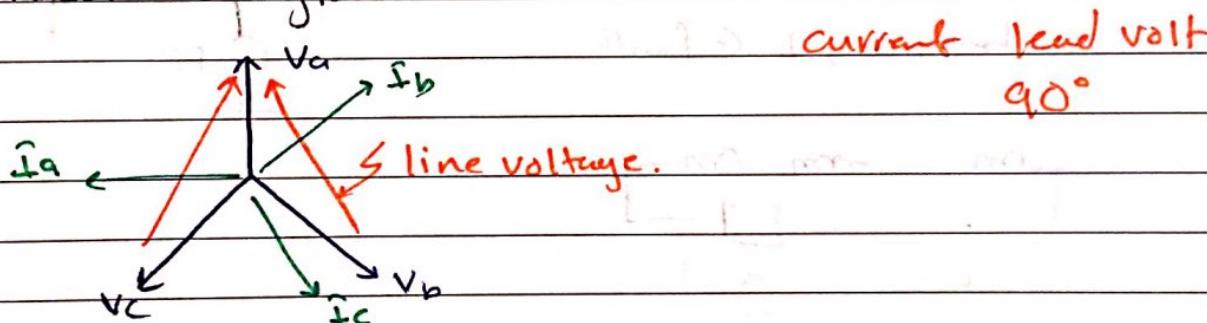

at balance:


$$\vec{I}_{ca} = \frac{\vec{V}_a}{-jX_{ca}} \Rightarrow |I_{ca}| = \frac{V_{ph}}{X_c}$$

$$|I_{ca}| = |I_{cb}| = |I_{cc}| = \frac{V_{ph}}{X_c} = \omega_c V_{ph}$$

$$\vec{I}_{cb} = j \frac{V_{ph}}{X_c}$$

13

At fault:-

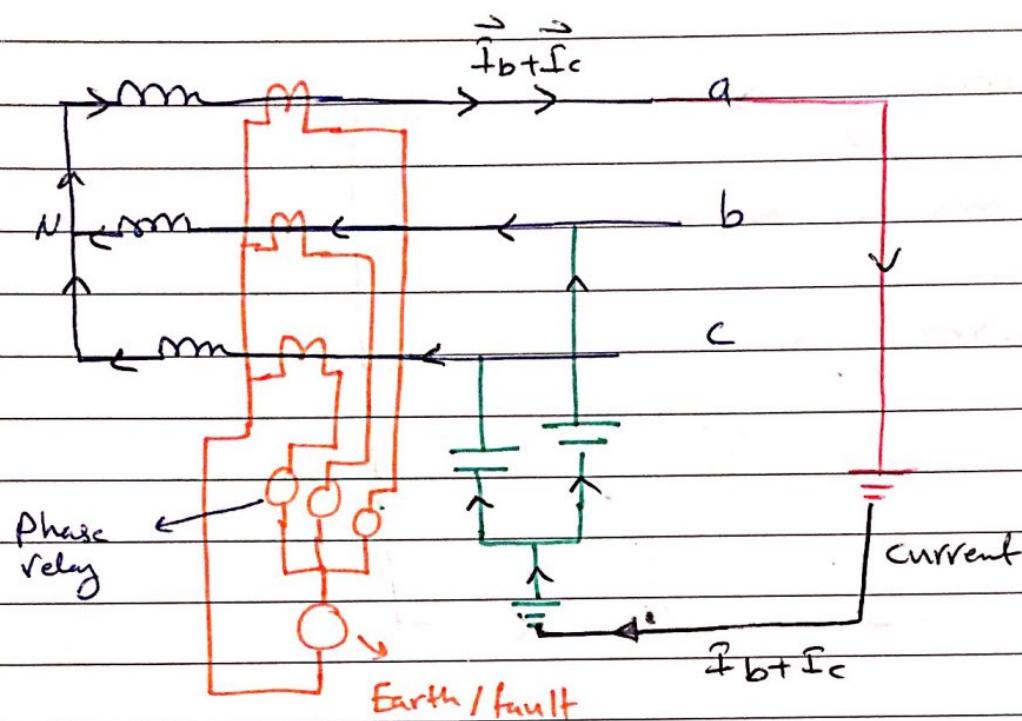


line to ground.

↳ Line  $\rightarrow$  Medium voltage.

↳ Current

$$|I_b| = \frac{\sqrt{3} V_{ph}}{X_c}$$

$$|I_c| = \frac{\sqrt{3} V_{ph}}{X_c}$$

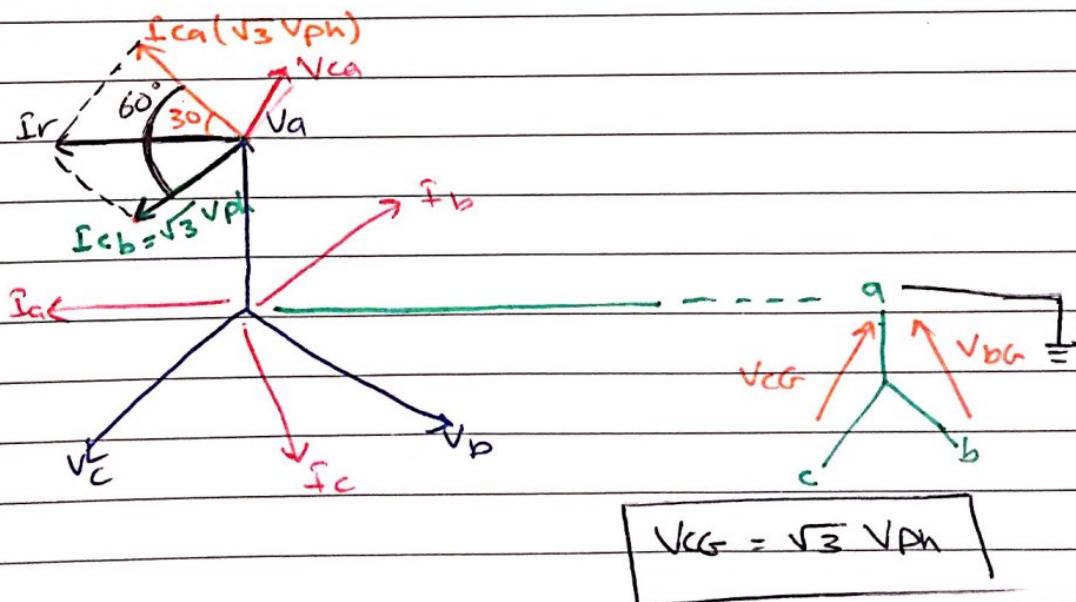


$$V_{GG} = \sqrt{3} V_{ph}$$

14


Five Apple

## 2] Solidly grounded system:-

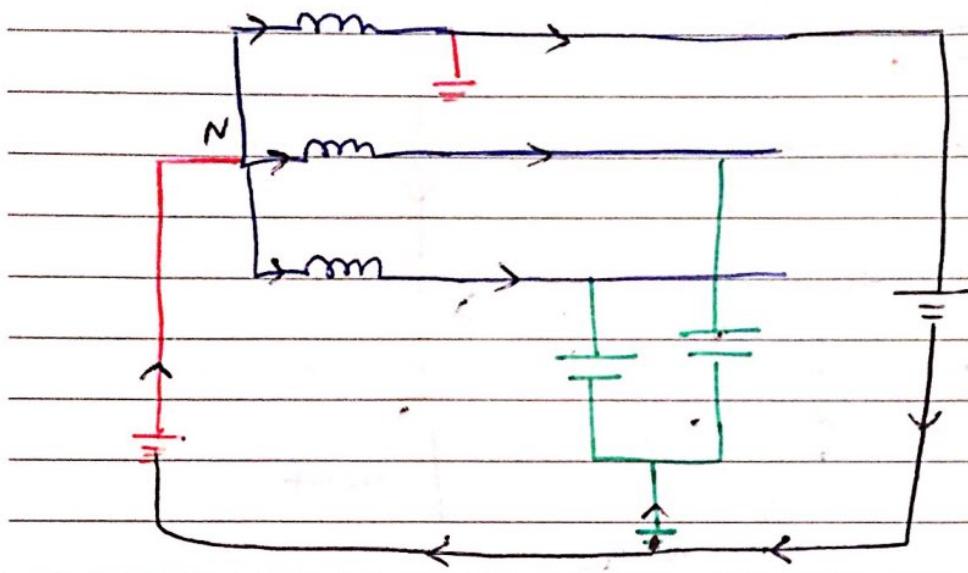
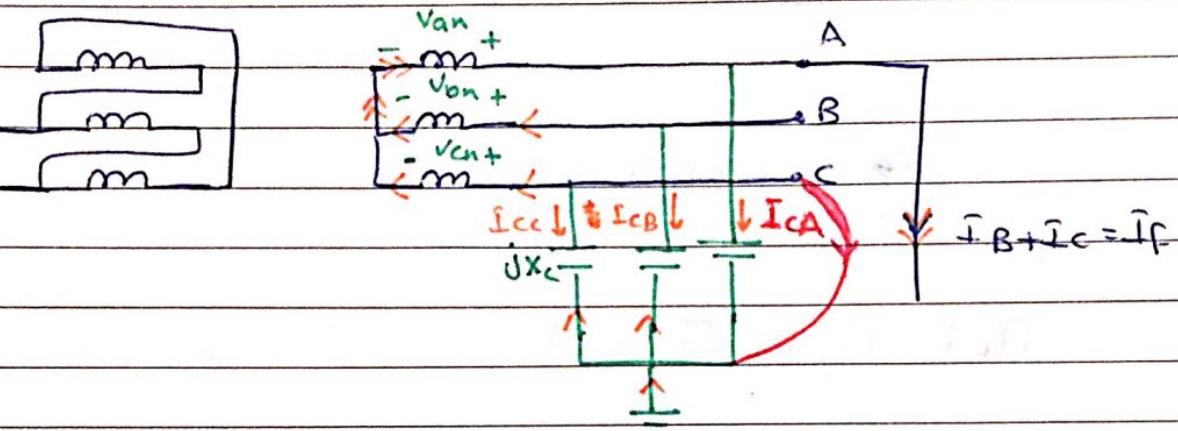
## Natural Grounding :-

II Isolated natural (Ungrounded) system).





I under normal condition :-

$$\vec{I}_{CA} = \frac{\vec{V}_A}{-jX_C} \quad \vec{I}_{CB} = \frac{\vec{V}_B}{-jX_C} \quad \vec{I}_{CA} = \frac{\vec{V}_C}{-jX_C}$$

$$|I_{AC}| = |I_{BC}| = |I_{CA}| = \frac{V_{ph}}{\sqrt{3}/X_C} = \omega_C V_{ph}$$

$$\frac{N_1}{N_2} = \frac{V_{1ph}}{V_{2ph}} = \frac{V_{L1}}{V_{L2}/\sqrt{3}} = \sqrt{3} \frac{V_{L1}}{V_{L2}}$$
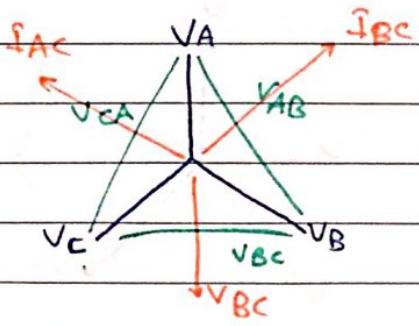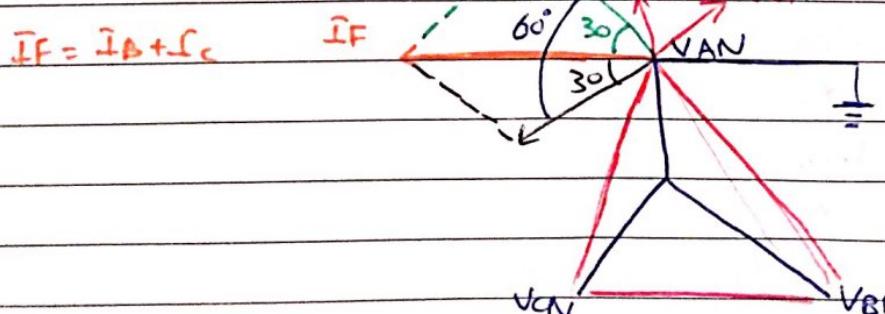
$$I_A = \frac{N_2}{N_1} I_A = \frac{V_{L2}}{V_{L1}} \sqrt{3}$$



16

## 2) LG-fault :-


$$\dot{I}_F = \dot{I}_B + \dot{I}_C$$

$$|I_F| = \frac{3V_{ph}}{X_C} = 3W_C V_{ph}$$

$$V_{NG} = -V_{AN}$$

$$|I_B| = |I_C| = \frac{\sqrt{3}V_{ph}}{X_C}$$

## 2) Solidly grounded systems

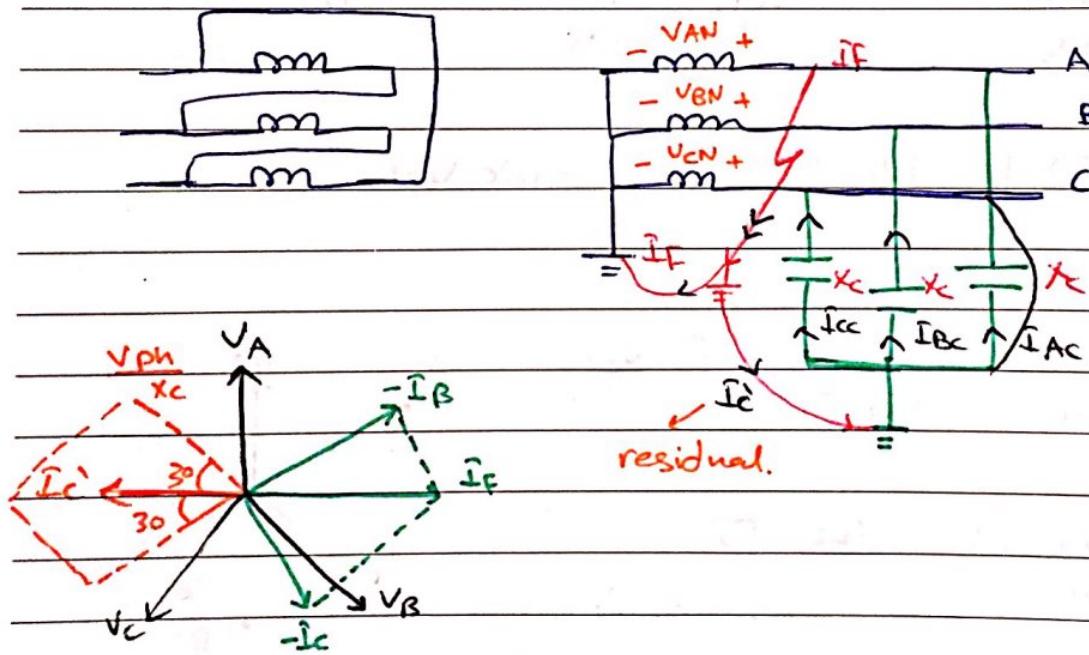


$$|I_B| = \frac{V_{ph}}{X_C}$$

$$|I_F| = \frac{V_{ph}}{X_C}$$

$$I_c' (\text{residual}) = I_B + I_F$$



17

### ③ Grounding through $R_{\text{G}}$

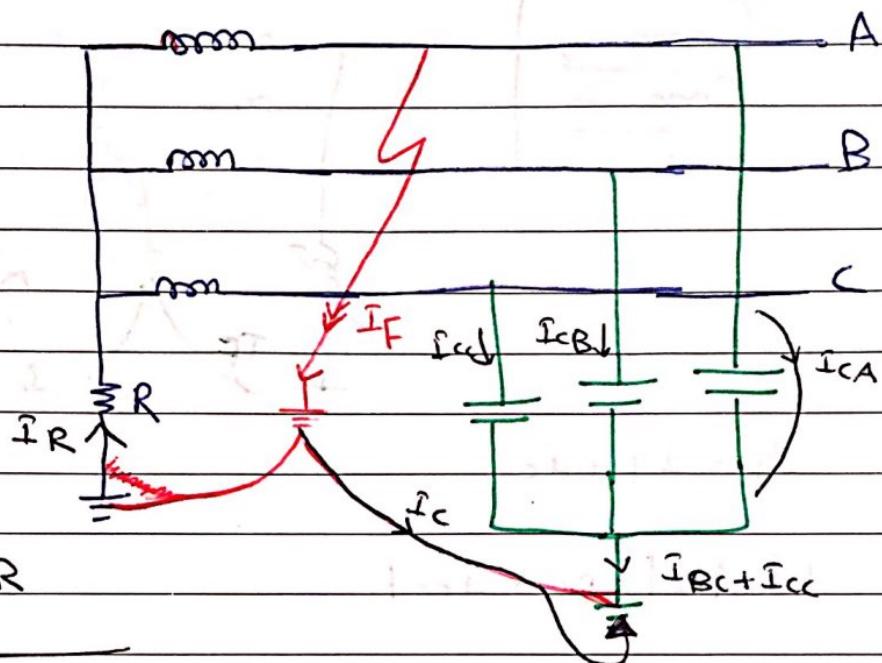

$$V_{NG} = I_R \cdot R$$

$$|I_F| = \sqrt{I_R^2 + I_c^2}$$

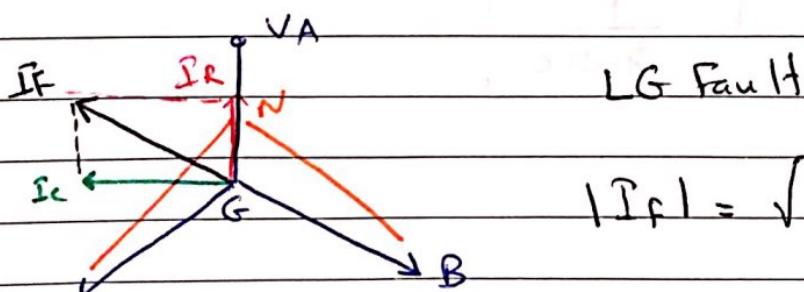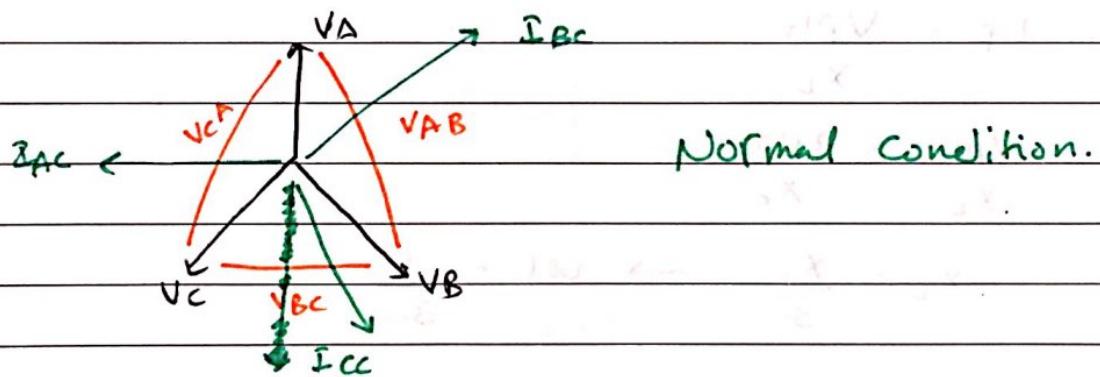


$$|I_F| = \sqrt{I_R^2 + I_c^2}$$

18

Five Apple

## 4 Person coil grounding :-

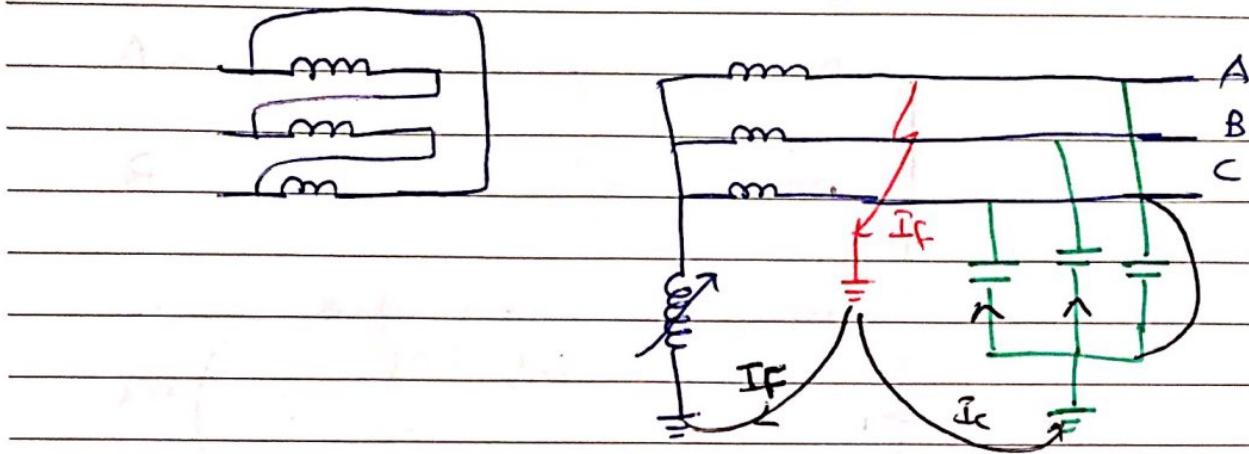

$$I_f = I_f + I_c$$

$$|I_c| = |I_{BC} + I_{CC}|$$

$$|I_c| = \frac{3V_{ph}}{X_C}$$

$$I_f = \frac{V_{ph}}{X_L}$$


$$\frac{V_{ph}}{X_L} = \frac{3V_{ph}}{X_C}$$

$$X_L = \frac{X_C}{3} \rightarrow \omega L = \frac{1}{3\omega C}$$

$$L = \frac{1}{3\omega^2 C}$$

**[Q1]**

25 MVA

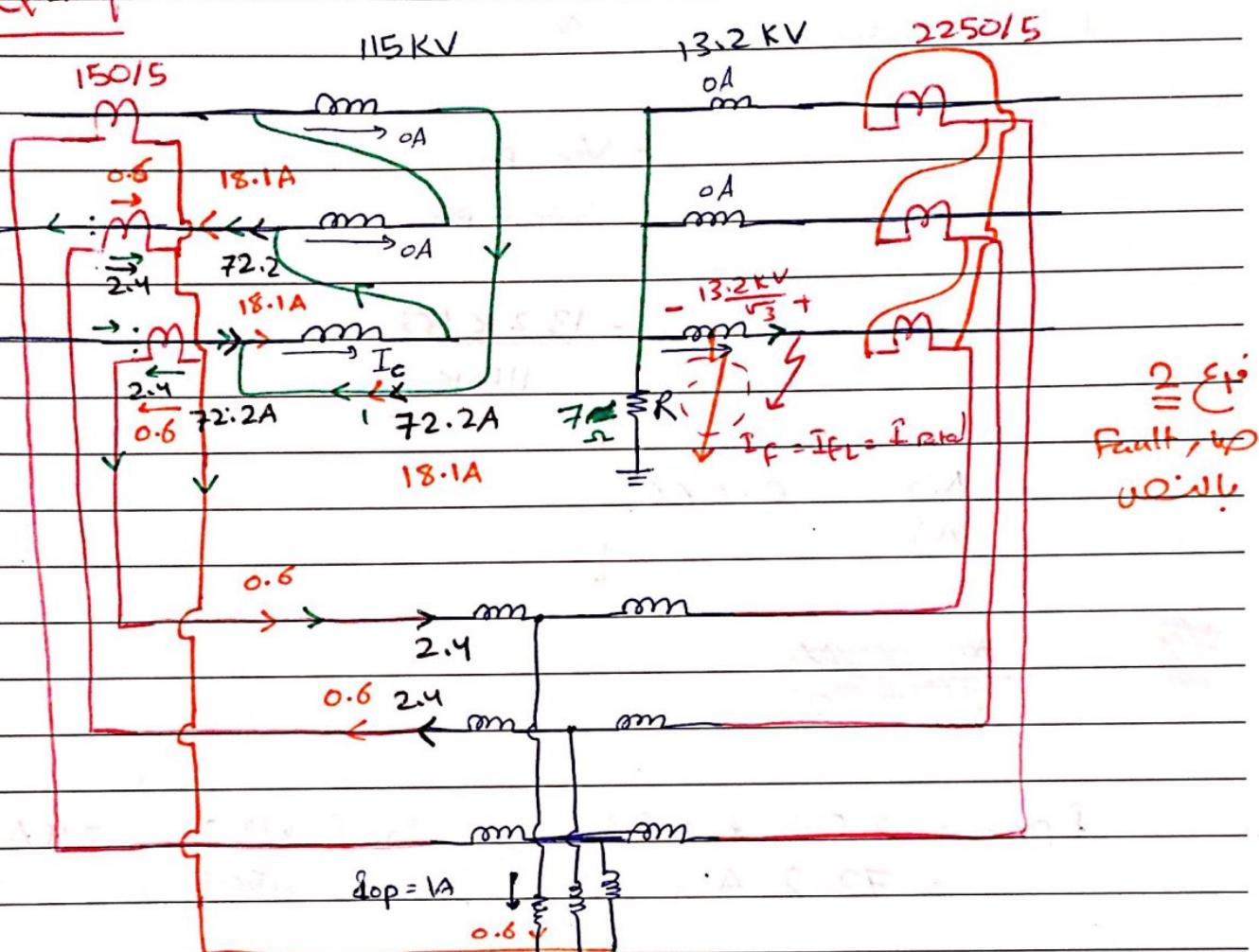

$\approx \epsilon_1$   
Fault,  $\rightarrow$   
 $0.6 \text{ A}$

$$\bar{I}_{FL} = \bar{I}_{\text{rated}} = \frac{25 \times 10^6}{\sqrt{3} \times 13.2 \times 10^3} = 1093.5 \text{ A}$$

$$V_{ph\ sec} = \frac{13.2 \text{ KV}}{\sqrt{3}} = 7.62 \text{ KV}$$

$$I_F = I_{\text{rated}} = 1093.5 = \frac{V_{ph\ sec}}{R}$$

$$R = \frac{7.62 \text{ KV}}{1093.5} = 6.97 \Omega$$

**$R = 7 \Omega$**

**[20]**

Five Annele

$$\frac{I_c}{I_c} = \frac{I_{\text{primary}}}{I_{\text{secondary}}} = \frac{N_2}{N_1}$$

$$= \frac{V_{\text{sec ph}}}{V_{\text{prim ph}}}$$

$$= \frac{13.2 \text{ kV}/\sqrt{3}}{115 \text{ kV}}$$

$$\frac{N_2}{N_1} = 0.066$$

~~1~~



$$I_{\text{prim}} = 0.066 * 1093.5 \Rightarrow \frac{\text{in CT} \rightarrow 72.2}{150/5} = 2.4 \text{ A}$$

$$= 72.2 \text{ A}$$

② Fault in the middle.

$$I_c = \left( \frac{N_2/2}{N_1} \right) * 546.7$$

$$= \frac{0.066}{2} * 546.7$$

$$I_c = 18.1 \text{ A} \rightarrow \frac{\text{in CT} \rightarrow 18.1}{150/5} = 0.6 \text{ A}$$

differential 3 ratio  $\rightarrow$  winding 11 no. coil's  $\approx$   
= 2018 ~~2010~~



~~1~~ relay 11  $\rightarrow$  110 winding no. 50% \*

Line to Line  $\rightarrow$  80% winding 11 15 V  $\rightarrow$  \*

[2]

Q2

Summation law.

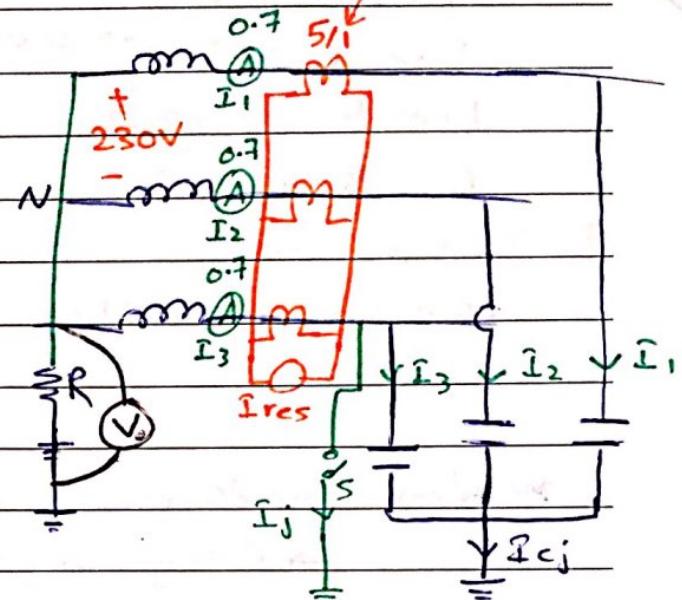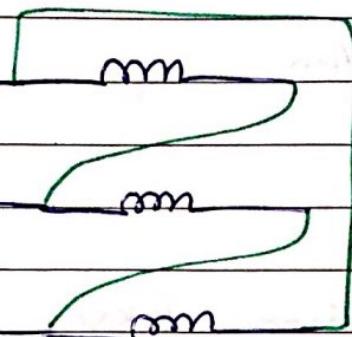

1] Isolated balanced  $\Rightarrow$

$$I_{res} = 0 \text{ A}$$

$$I_{cj} = 0 \text{ A}$$


$$V_o = 0 \text{ V} \quad (0 \neq R)$$

2] Isolated having fault  $\Rightarrow$  Switch close.

$$I_1 = 1.15 \text{ A}$$

$$I_2 = 1.1 \text{ A}$$

Capacitor 3  $\rightarrow$  shorted.

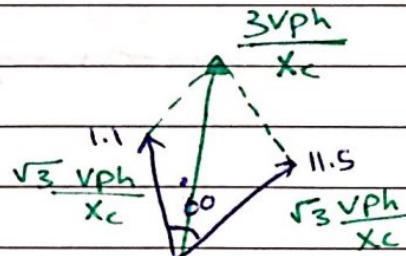

$$I_{cj} = \underline{\text{sum of } I_1 \text{ and } I_2}$$

$$I_{cj} = 1.95 \text{ A} = \sqrt{3} \left( \frac{1.15 + 1.1}{2} \right) \text{ A}$$

$$V_o = V_{ph} = \frac{230}{\sqrt{3}}$$

$$|I_{cj}| = |I_{cl}| = I_3$$

22

$$G = 2 \text{ MVA}, 10\%$$

$$\text{MVA}_b = 20 \text{ MVA}$$

$$T_1 = 2 \text{ MVA}, 7\%$$

Line 1, 2, 3  $\rightarrow 0.02 \Omega/\text{ph.}$

$$\text{Line } 5 = 0.02 \Omega$$

$$\text{Line } 8 = 0.2 \Omega$$

$\Rightarrow$  IE Sys. no

Icon - Grid  $\rightarrow$  Click rating 11 KV. (nominal)

Short cir impedance 10%.




Winding impedance

$\rightarrow$  Rating  $\rightarrow 3.3 \text{ seconds.}$



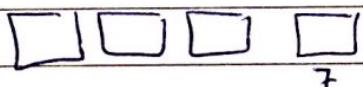winding impedance  $\rightarrow$  impedance. 3.7 7%  $\leftrightarrow$  base  $\approx 10^6$




~~Grid rating  $\rightarrow$~~

Grid.

BUS  $\rightarrow$  line



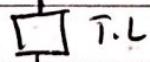T.L  $\rightarrow$  impedance  $\approx 10^6$  KV



click Rating

3.3

Balanced.

~~Base~~

R X Y

$\square$  0.02  $\square$

person

~~excuse me help~~

base.  $\rightarrow 1 \text{ kV}$

23

Five Apple

\* add bus. and CT's

Ratio

Prim      Sec

CT  $\rightarrow$

200A

1A

class


De  $\Rightarrow$

10P5

standard

error 5%.

2.5VA

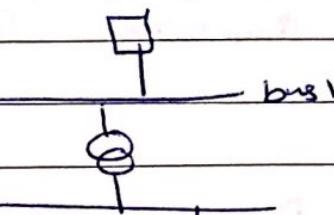

CT impedance.

add Relay

Overcurrent relay

OCR

library

Model - REJ 525

Function

overcurrent.

curve type normal impedance.

Lumped load.



Nameplate  $\rightarrow$

kVA

PF%

2000

85

Project standard  $\rightarrow$  50 Hz.

Power Grid

Rating

9.1V

Operating

100

2-winding

Grounding

Transformer primary

Y

Solid

Sec

Y

Solid

241

impedance Rating Base KV

~~WB~~

### Display option


→ AC display on diagram

R → Unit  KV power

o Amp graph

# Differential Protection Schemes of synchronous Generator

- Consider Y-connected Generator.

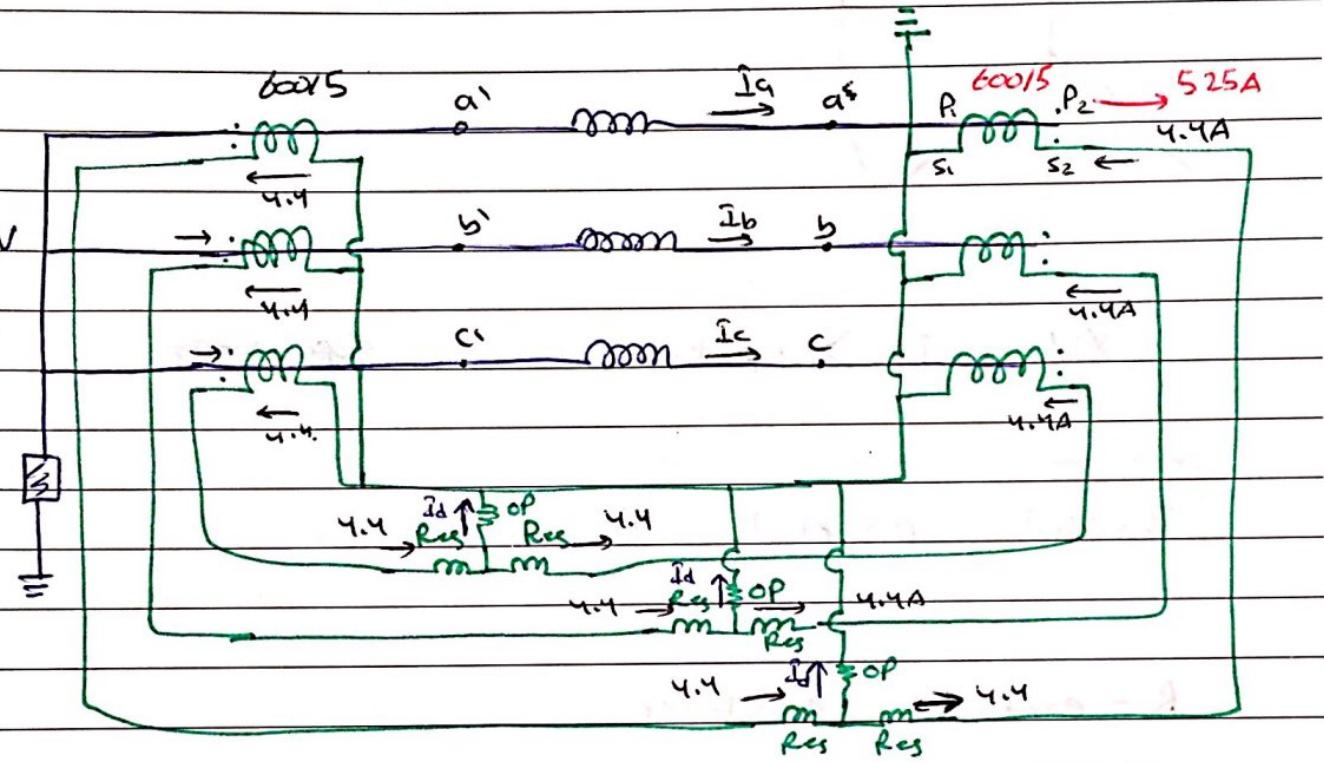


10MVA, 11 KV Gen. pf=0.8

$$I_{FL} = \frac{10 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 525 \text{ A.}$$

$$I_d = I_1 - I_2$$


$$I_{res} = \frac{I_1 + I_2}{2}$$

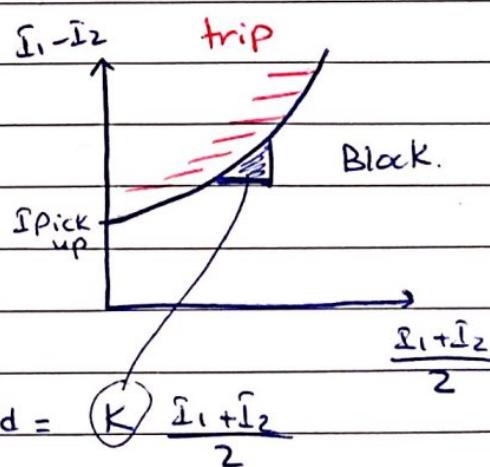

$$\text{trip } I_d > K \cdot I_{res}$$

[26]

Five Apple

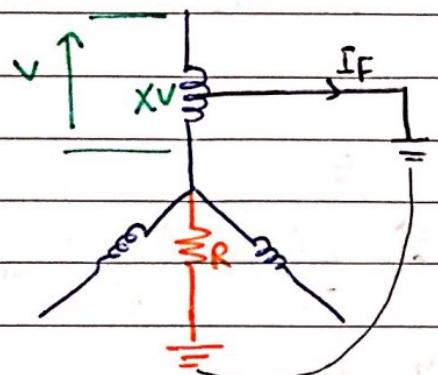

$$\frac{Xv}{R} = If \geq I_{\text{pickup}}$$

~~if~~

$$\% \text{ winding protected} = \frac{R \cdot I_0}{V} \times 100\%$$

$R$  = earthing resistance.

$V$  = full-line - neutral voltage.

$I$  = full-load current of the Gen.

$I_0$  = minimum operating current in the primary of the CT

**Q 1**

10MVA, 13.2 kV

% winding protected against LG = 85%  
% winding protected = 15%.

Q pick up  $\geq 20\%$  I<sub>rated</sub>.


**Sol:-**

$$I_{\text{rated}} = \frac{10 \times 10^6}{\sqrt{3} \times 13.2 \text{ kV}} = 437 \text{ A}$$

$$Q \text{ pick up} = 0.2 \times 437 = 87.5 \text{ A}$$

$$V_{\text{ph}} = \frac{13.2 \text{ kV}}{\sqrt{3}}$$

$$V_{\text{ph}} = 7.6 \text{ kV}$$

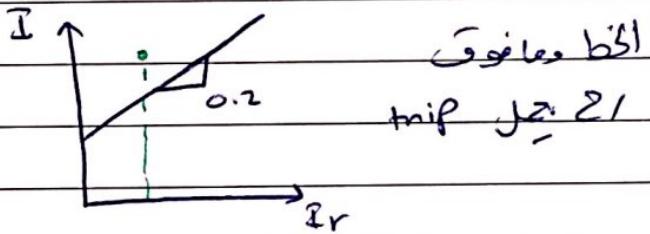


$$V_{\text{ph}} = 7621 \text{ V}$$

$$15 = \frac{R \times 87.5}{7621} \times 100$$

$$R = 13.07 \Omega$$

If trip middle

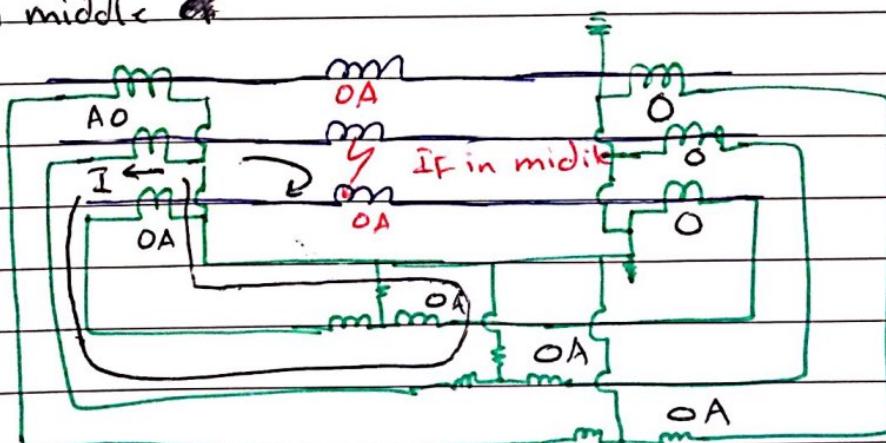

28)

Five Apple

A 115/13.2 kV Dy1 transformer rated at 25MVA has differential protection as indicated below. The transformer is connected to a radial system, with the source on the 115 kV side. The minimum operating current of the relays is 1 A. The transformer 13.2 kV winding is earthed via a resistor which is set so that the current for a single-phase fault on its secondary terminals is equal to the nominal load current. Draw the complete three-phase diagram and indicate on it the current values in all the elements for:

- Find the value of the grounding resistance R.
- When a fault occurs at the middle of the winding on phase C, on the 13.2 kV side, assuming that the transformer is not loaded. For both cases indicate if there is any relay operation.

### Solution:

#### Full load conditions

The full load conditions for the maximum load of the transformer are as follows:

$$I_{FL(13.2kV)} = \frac{25 \times 10^6}{\sqrt{3} \times 13 \times 10^3} = 1093.5 A, \quad R = \frac{13.2 \times 10^3 / \sqrt{3}}{1093.46} = 6.97 \Omega$$

#### Fault at the middle of 13.2 kV winding C

Since the transformer is earthed through a resistor that limits the current for faults at the transformer 13.2 kV bushings to the rating of the winding, and since the fault is at the middle of the winding, the fault current is then equal to half the rated value as follows:


$$I_{fault} = (I_{nom(13.2kV)})/2 = 1093.47/2 = 546.7 A$$

The primary current within the delta winding is

$$I_{prim} = I_{fault} \times \frac{(N_2 / 2)}{N_1}, \quad \frac{N_2}{N_1} = \frac{V_2 / \sqrt{3}}{V_1}$$

$$I_{prim} = \frac{1}{\sqrt{3} \times VR} = 546.5 \times \frac{(13.2 / \sqrt{3})/2}{115} = 18.1 A$$

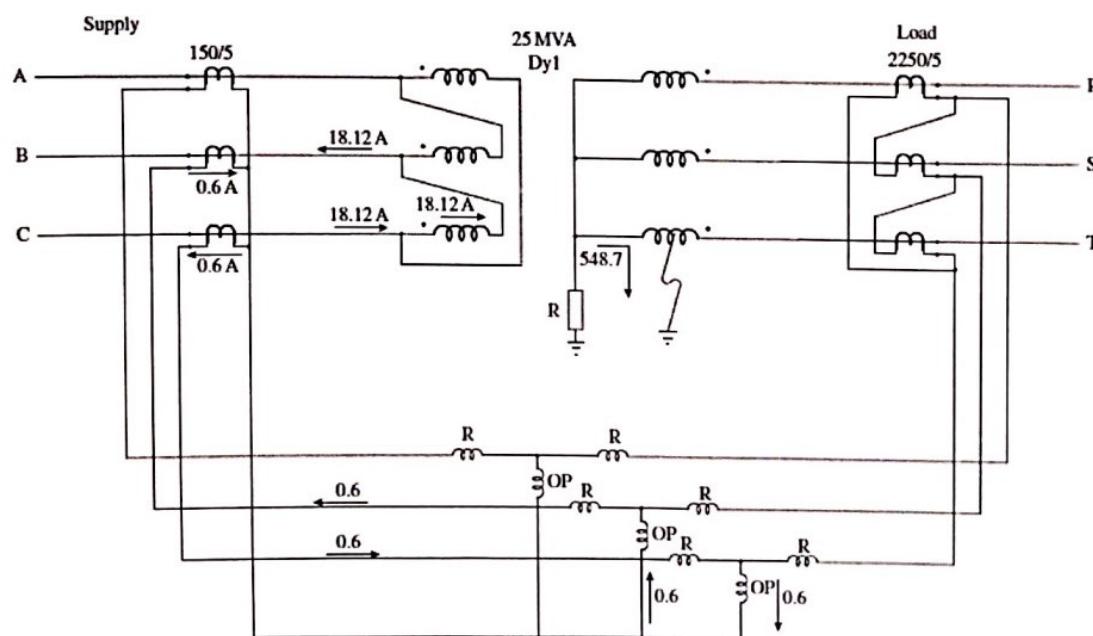The differential relays **do not operate** since the current through their operating coils is only 0.6 A, which is less than the 1A required for relay operation.



Conditions for a fault at the middle of the winding on phase C on the 13.2 kV side

**Question #2**

- I. For the circuit shown in below, with an input voltage  $U_2 = 230$  V together with  $R_o = \infty$  (infinite), and the switch S is open. The currents  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_{res}$  are measured. For  $I_1$ ,  $I_2$ , and  $I_3$  are as given in Table 1-a, what will be the readings of  $I_{res}$ ,  $I_{cj}$  and  $U_o$ ?

Table 1-a

$I_1$ (A)	$I_2$ (A)	$I_3$ (A)	$I_{res}$ (A)	$I_{cj}$ (A)	$U_o$ (V)
0.7	0.7	0.7	0.0	0.0	0.0

- II. For the circuit shown below, with an input voltage  $U_2 = 230$  V together with  $R_o = \infty$  (infinite), and the switch S is closed. The currents  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_{res}$ , and  $I_j$  are measured. For  $I_1$  and  $I_2$  are as given in Table 1-b, what will be the readings of  $I_3$ ,  $I_{res}$ ,  $I_j$  and  $I_{cj}$  and  $U_o$ ?


Table 1-b

$I_1$ (A)	$I_2$ (A)	$I_3$ (A)	$I_{res}$ (A)	$I_j$ (A)	$I_{cj}$ (A)	$U_o$ (V)
1.15	1.1	2.25	0.0	2.25	2.25	133

- III. For the circuit shown below, with an input voltage  $U_2 = 230$  V together with  $R_o = 50 \Omega$  (infinite), and the switch S is closed. The currents  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_{res}$ , and  $I_j$  are measured. For  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_{res}$  and  $I_{cj}$  are as given in Table 1-c, what will be the readings of  $I_j$ ,  $I_{Ro}$  and  $U_o$ ?

Table 1-c

$I_1$ (A)	$I_2$ (A)	$I_3$ (A)	$I_{res}$ (A)	$I_{cj}$ (A)	$I_j$ (A)	$I_{Ro}$ (A)	$U_o$ (V)
1.25	0.45	3.3	0.52	2.1	3.3	2.6	130

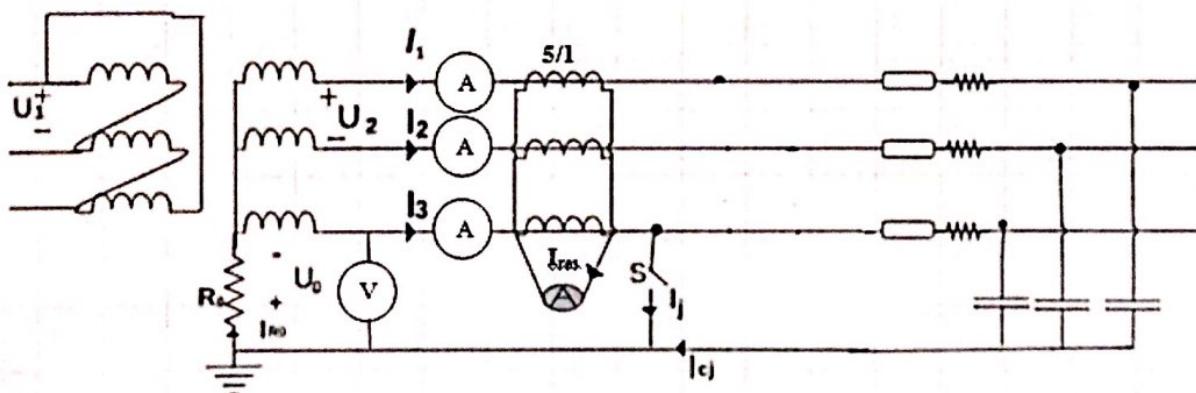

## Term Project-I

### EE483-Project-OC Coordination-ETAP

#### **LOYALTY OATH:**


I signify by my signature below that all of the attached work on the Term Project for the course EE483 for the 2<sup>nd</sup> Semester is that entirely of our own, and We did NOT seek assistance from any other classmate or other personnel, or provide any assistance to any other classmate in the completion of this term project.

---

Name \_\_\_\_\_ S.N. \_\_\_\_\_ Signature \_\_\_\_\_

Name \_\_\_\_\_ S.N. \_\_\_\_\_ Signature \_\_\_\_\_

<b>Objective:</b>	Design the protective scheme of the power system shown below. It is required to size all the CTs, define type of protection and relay setting.
<b>Procedure:</b>	You can use ETAP software programs.
<b>Steps:</b>	<ol style="list-style-type: none"><li>1. Draw the network with all the data as provided.</li><li>2. Run a load flow to determine your steady state conditions.</li><li>3. Perform short circuit analysis at different buses.</li><li>4. Select and size all CT.</li><li>5. Connect relays where appropriate.</li><li>6. Carry out coordinating studies to adjust relay settings.</li><li>7. Check for relay operation for selected fault locations.</li></ol>
<b>Report:</b>	Prepare a detailed report of your work.
<b>Team Work:</b>	You may work in a group of two but no more.
<b>Report Submission:</b>	March 22, 2018

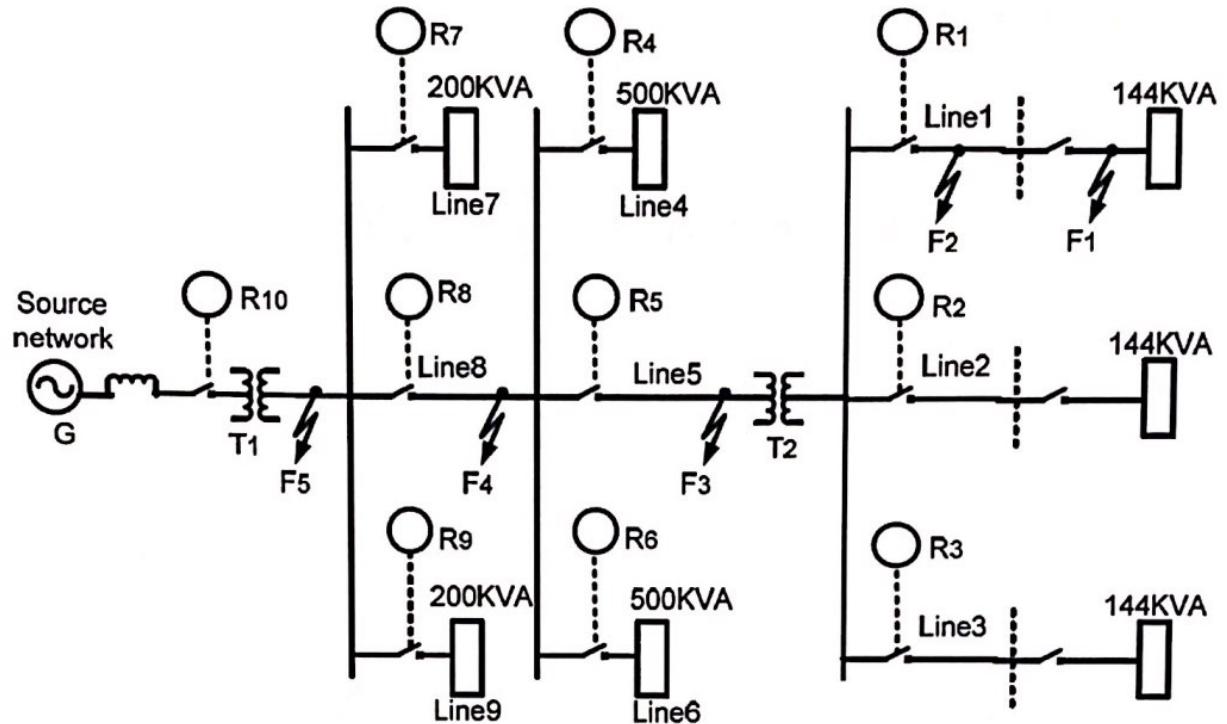

Protection of radially-connected network

Apply inverse definite minimum-time (IDMT) relay with normal inverse characteristic given as

$$t = \frac{0.14}{\left(\frac{I}{I_s}\right)^{0.02} - 1} T_p$$

Where  $t$  = tripping time of relay,  $T_p$  = time

Network parameters:  $G$ : 2MVA, 10%;  
 $T_1$ : 2MVA, 11/3.3KV, 7%;  $T_2$ : 500KVA,  
3.3/0.415KV, 6%; Lines 1, 2, 3: 0.02  $\Omega$ /ph;  
Line 5: 0.2 $\Omega$ /ph; Line 8: 0.2 $\Omega$ /ph; System MVA  
base = 20MVA; Positive and negative sequence  
impedances are assumed equal.


In this network, for a fault at the point  $F_1$ ,  
relays  $R_1$ ,  $R_2$  and  $R_3$  must not operate in less  
than 0.5s.

Reactance of  $G$  = 1p.u; Reactance of  $T_1$  =  
0.7p.u; Reactance of Line 8 = 0.367p.u; Reac-  
tance of Line 5 = 0.367p.u; Reactance of  $T_2$  =  
2.4p.u; Reactance of Line 1 = 2.323p.u;



For example, the feeder relay and breaker, which  
are downstream, should clear a feeder fault be-  
fore the supply-side relay and breaker (upstream)  
could trip. Generally, CTI of about 0.4 seconds

## Generator Differential Protection

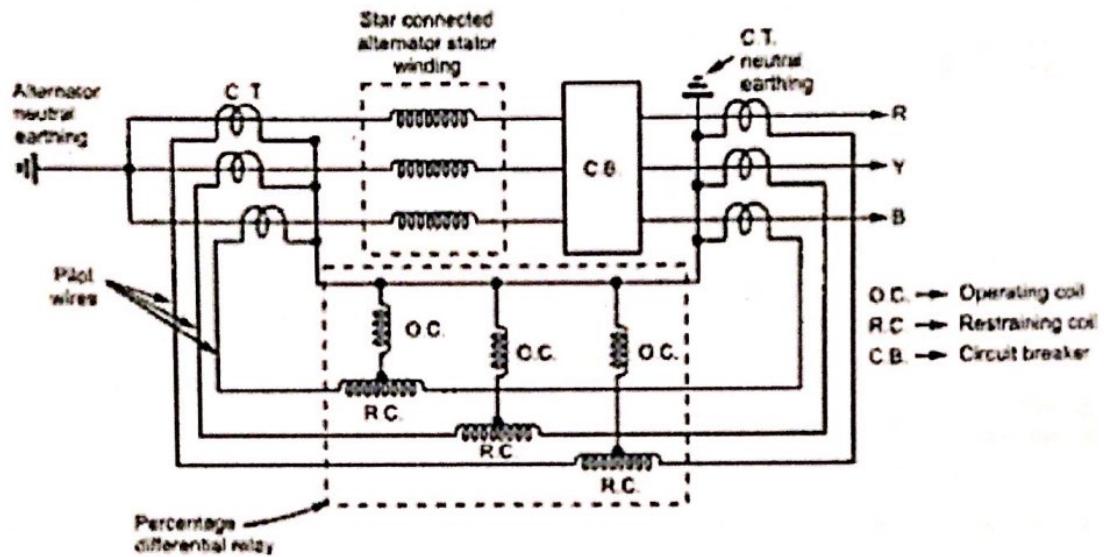
### Differential Protection for Y-Connected Generator



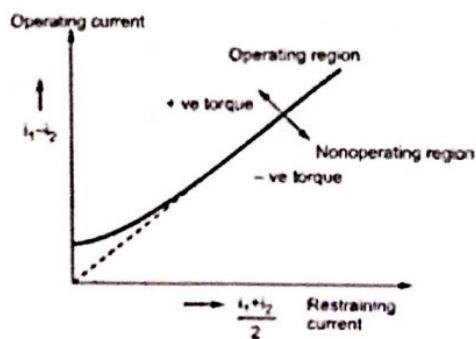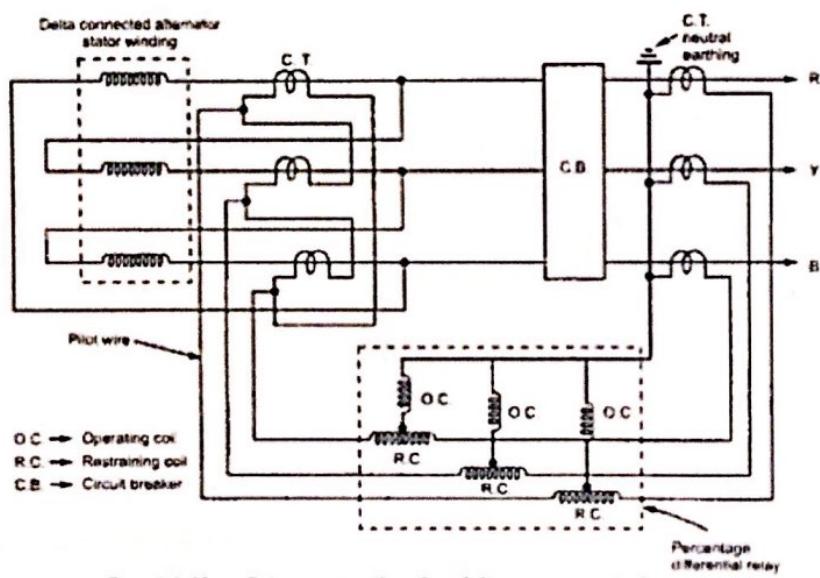
### Differential Protection for Delta Connected Generator


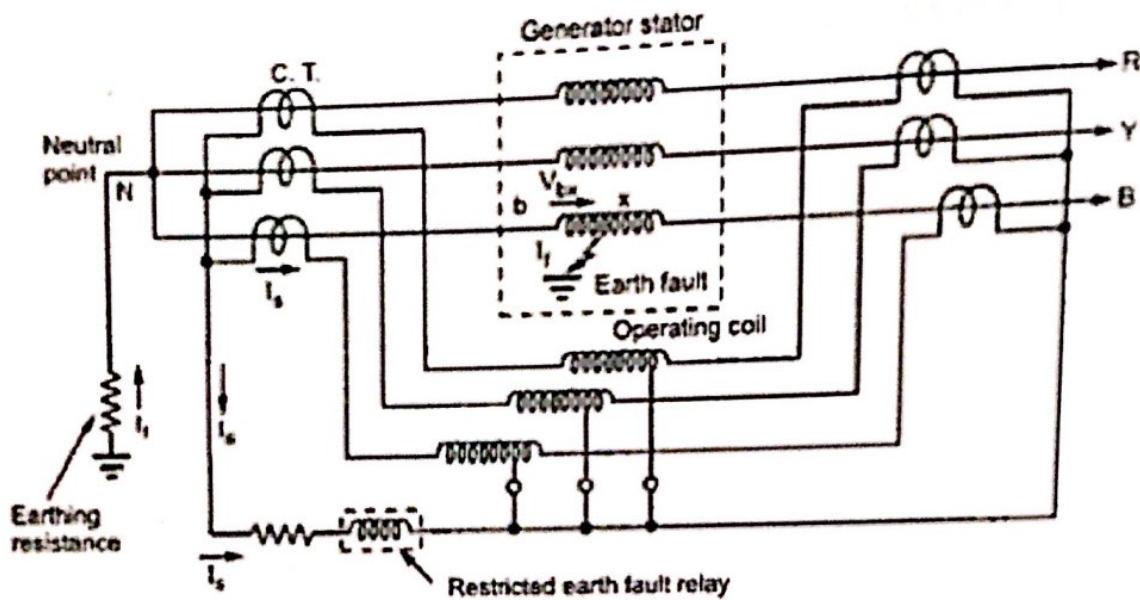
## Restricted Earth Fault Protection of a Generator



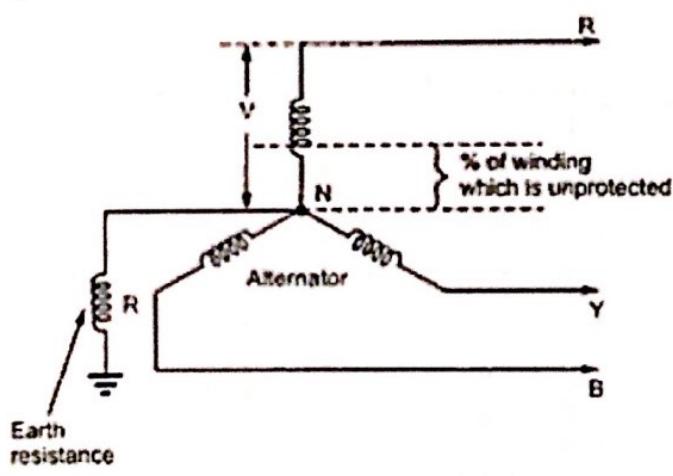Let us see the effect of earth resistance on the % of the winding which remains unprotected.



Consider the earth resistance  $R$  used to limit earth fault current as shown

The value of the resistance  $R$  limits the earth fault current.

If the resistance  $R$  is very small i.e. the neutral is almost solidly grounded, then the fault current is very high. But high fault currents are not desirable hence small  $R$  is not preferred for the large machines.

For low resistance  $R$ , the value of  $R$  is selected such that full load current passes through the neutral, for a full line to neutral voltage  $V$ .

In medium resistance  $R$ , the earth fault current is limited to about 200A for full line to neutral voltage  $V$ , for a 60 MW machine.

In high resistance  $R$ , the earth fault current is limited to about 10 A. This is used for distribution transformers and generator-transformer units.

Now higher the value of earth resistance R, less is the earth fault current and less percentage of winding gets protected. Large percentage of winding remains unprotected.

Let

$V$  = Full line to neutral voltage

$I$  = Full load current of largest capacity generator

$R$  = Earth resistance

Then the value of the resistance R is,

$$R = \frac{V}{I}$$


And the percentage of winding unprotected is given by,

$$\% \text{ of winding unprotected} = \frac{RI_o}{V} \times 100$$


where  $I_o$  = Minimum operating current in the primary of C.T.

If relay setting used is 15% then  $I_o$  is 15% of the full load current of the largest machine and so on.
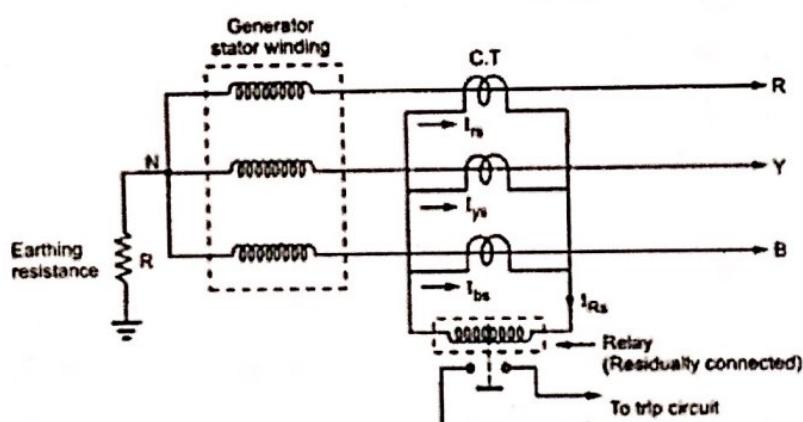
### Unrestricted Earth Fault Protection Scheme



### Balanced Earth Fault Protection

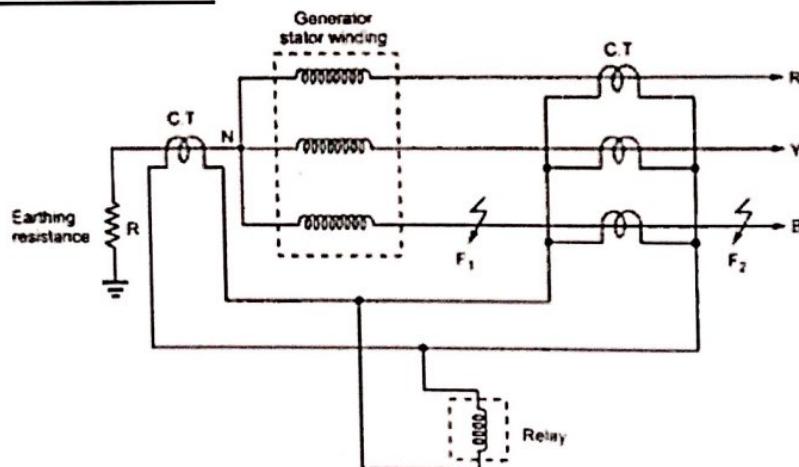

**Question # 1**

A generator is protected by restricted earth fault protection. The generator ratings are 13.2 kV, 10 MVA. The percentage of winding protected against phase to ground fault is 85%. The relay setting is such that it trips for 20% out of balance. Calculate the resistance to be added in the neutral to ground connection.

**Solution:**

$$I = \frac{\text{Rating in VA}}{\sqrt{3} V_L} = \frac{10 \times 10^6}{\sqrt{3} \times 13.2 \times 10^3} = 437.386 \text{ A}$$

$$V = \text{Line to neutral voltage} = \frac{V_L}{\sqrt{3}} = \frac{13.2 \times 10^3}{\sqrt{3}} = 7621.02 \text{ V}$$

Relay setting is 20% out of balance i.e. 20% of the rated current activates the relay.

$$I_o = 4387.386 \times \frac{20}{100} = 87.477 \text{ A} = \text{Minimum operating current}$$

% of winding unprotected = 15% as 85% is protected

$$15 = \frac{R I_o}{V} \times 100 = \frac{R \times 87.477}{7621.02} \times 100 \Rightarrow R = 13.068 \Omega$$

### Question # 2

A star connected 3-phase, 12 MVA, 11 kV alternator has a phase reactance of 10%. It is protected by differential circulating scheme which is set to operate for fault current not less than 200 A. Calculate the value of earthing resistance to be provided in order to ensure that only 15% of the alternator winding remains unprotected.

Solution:

$$12 \times 10^6 = \sqrt{3} \times 11 \times 10^3 \times I_L \Rightarrow I_L = \frac{12 \times 10^6}{\sqrt{3} \times 11 \times 10^3} = 629.8366 \text{ A}$$

$$V = \frac{V_L}{\sqrt{3}} = \frac{11 \times 10^3}{\sqrt{3}} = 6350.8529 \text{ V}$$

$$\% \text{ Reactance} = \frac{IX}{V} \times 100$$

$$10 = \frac{629.8366 X}{6350.8529} \times 100 \Rightarrow X = 1.0083 \Omega$$

$\therefore$  Reactance of unprotected winding = (% of unprotected winding)  $\times$  (X)

$$= \frac{15}{100} \times 1.0083 = 0.1512 \Omega$$

v = voltage induced in unprotected winding

$$= \frac{15}{100} \times V = 0.15 \times 6350.8529 = 952.6279 \text{ V}$$

i = Fault current = 200 A

$$Z = \text{Impedance offered to the fault} = \frac{v}{i} = \frac{952.6279}{200} = 4.7631 \Omega$$

Z = r + j (reactance of unprotected winding)

$$Z = r + j (0.1512) \Omega \Rightarrow |Z| = \sqrt{r^2 + (0.1512)^2} = 4.7631 \Omega$$

$\Rightarrow r = 4.7607 \Omega$  This is the earthing resistance required.

### Question # 3

The neutral point of a 11 kV alternator is earthed through a resistance of  $12 \Omega$ , the relay is set to operate when there is out of balance current of 0.8 A. The CTs have a ratio of 2000/5. What percentage of the winding is protected against earth faults? What must be the minimum value of earthing resistance required to give 90% of protection to each phase?

#### Solution:

$$V_L = 11 \text{ kV} \quad R = 12 \Omega \quad \text{CTR} = 2000/5 \quad i_o = 0.8 \text{ A} = \text{relay current}$$

$$I_o = \text{minimum operating line current (C.T. primary)} = i_o \times \frac{2000}{5} = \frac{0.8 \times 2000}{5} = 320 \text{ A}$$

$$V = \text{line to neutral voltage} = \frac{V_L}{\sqrt{3}} = \frac{11 \times 10^3}{\sqrt{3}} = 6350.8529 \text{ V}$$

$$\% \text{ Winding unprotected} = \frac{R I_o}{V} \times 100 = \frac{12 \times 320}{6350.8529} \times 100 = 60.46 \%$$

$$\therefore \% \text{ Winding protected} = 100 - 60.46 = 39.53 \%$$

Thus with  $R = 12 \Omega$  only 39.53 % winding is protected.

It is necessary to give 90% protection.

$$\therefore \% \text{ Winding unprotected} = 100 - 90 = 10\% \Rightarrow 10\% = \frac{R \times I_o}{V} \times 100$$

$$10 = \frac{R \times 320}{6350.8529} \times 100 \Rightarrow R = 1.9846 \Omega$$

This is the minimum value of resistance to give 90% protection to the largest machine.

### Question # 4

A 50 MVA, 33 kV, 3-phase synchronous generator is protected by differential protection scheme using 1000/5 CTR. It is provided with restricted earth fault protection with the earthing resistance of  $7.5 \Omega$ . Calculate the percentage of winding unprotected in each phase against earth faults if the minimum operating current of the relay is 0.5 A.

#### Solution:

$$V_L = 33 \text{ kV} \quad R = 7.5 \quad \text{CTR} = 1000/5 \quad i_o = 0.5 \text{ A} = \text{relay current} \quad V = \frac{V_L}{\sqrt{3}} = \frac{33 \times 10^3}{\sqrt{3}} = 19052.55 \text{ V}$$


$$I_o = \text{minimum operating line current (C.T. primary)} = i_o \times \frac{1000}{5} = \frac{0.5 \times 1000}{5} = 100 \text{ A}$$

$$\% \text{ Winding unprotected} = \frac{R I_o}{V} \times 100 = \frac{7.5 \times 100}{19052.55} \times 100 = 3.936\%$$


### Question # 5

An alternator stator winding protected by a percentage differential relay is shown below. The relay has 15% slope of characteristics  $(I_1 - I_2)$  against  $(I_1 + I_2)/2$ . The high resistance ground fault has occurred near the grounded neutral end of the generator winding while the generator is carrying load. The currents flowing at each end of the generator winding are also shown. Assuming CTR = 500/5, will the relay operate to trip the circuit breaker?

Solution:

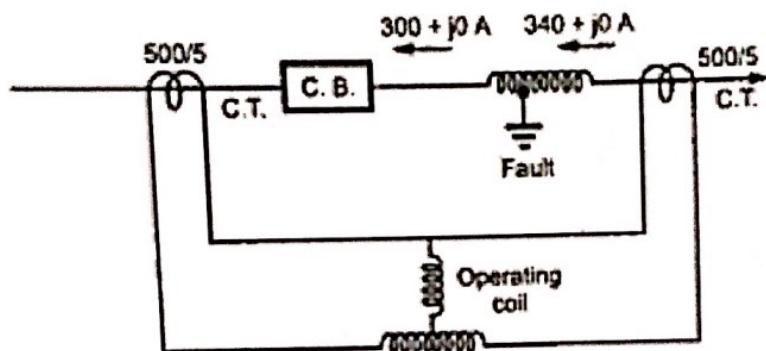

(a)

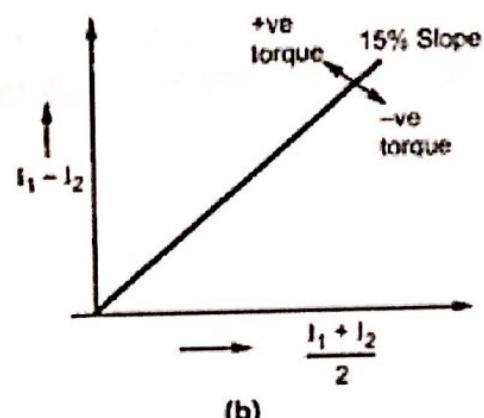


(b)

From the given current at two ends, let us calculate C.T. secondary currents at two ends,

$$i_1 = (300 + j 0) \times \frac{5}{500} = 3 \text{ A} \quad i_2 = (340 + j 0) \times \frac{5}{500} = 3.4 \text{ A}$$

The directions of currents are shown

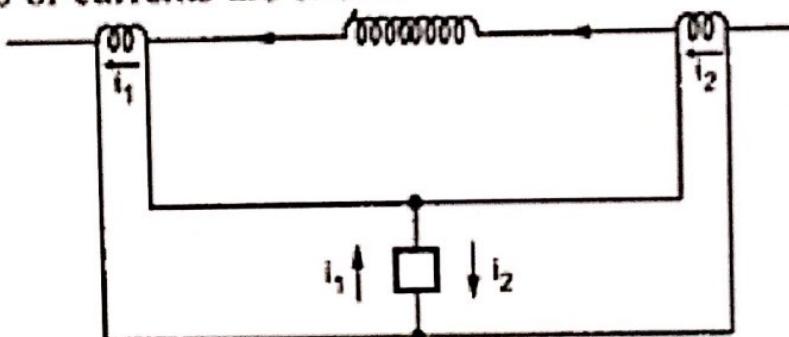


The current flowing through the relay coil is  $i_1 - i_2$ .

$$i_1 - i_2 = 3 - 3.4 = -0.4 \text{ A} \quad \frac{i_1 + i_2}{2} = \frac{3+3.4}{2} = 3.2 \text{ A}$$

From the characteristics of 15 % slope, corresponding to  $\frac{i_1 + i_2}{2}$  the out of balance current required is,
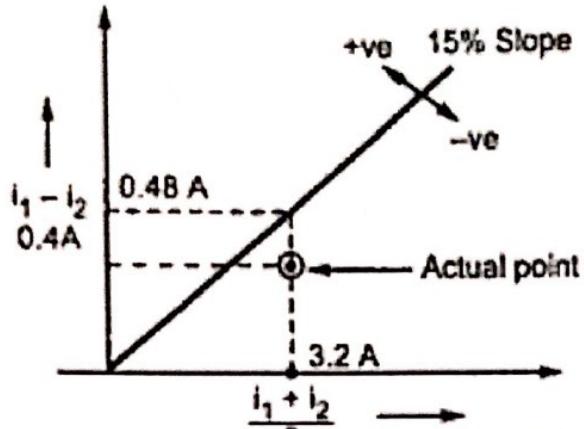
$$i_1 - i_2 = \text{Slope} \times \left( \frac{i_1 + i_2}{2} \right) = 0.15 \times 3.2 = 0.48 \text{ A}$$



Hence the relay will not operate.

Thus  $i_1 - i_2$  must be more than 0.48 A i.e. above the line to operate the relay but actual point is located below the line in negative torque region.