

6/5


Name: محمد مبروك ابو حياينة Stu. ID: 0144235

EE 529: Selected Topics in Communications
Second Exam (Spring 2018) April 10th, 2018

Question 1 (6 pts)

Design a three-port resistive divider for an equal power split and a 100 Ω system impedance.
a) If port 3 is matched, calculate the change in output power at port 3 (in dB) when port 2 is connected first to a matched load, and then to a load having a mismatch of $\Gamma = 0.3$. Assume the incident voltage from port 1 is 1 V.

$R = \frac{100}{3} = 33.3 \Omega$
 $P_3 = \frac{1}{2} \frac{|V_3|^2}{Z_3}$
 $Z_3 = R + Z_0 = 133.3 \Omega$
 $V_3^- = V_3^+ + V_3^-$
 $P_2 = P_3 = \frac{1}{4} P_1$
 3dB will be lost in the resistors.

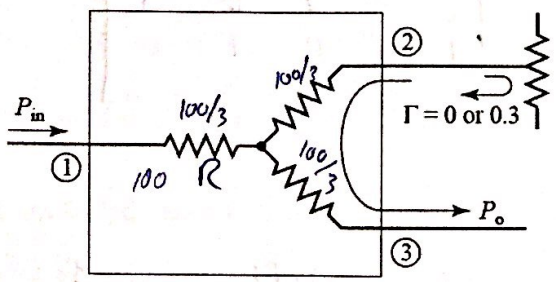

*case (1): port is matched.

$V_2^+ = V_3^+ = 0$
 $V_3 = V_3^- \Rightarrow V_2 = V_2^+ + V_2^-$
 $V_1 = 1 \text{ volt}$
 $V_2 = \frac{1}{2} V_1 = 0.5$

$$\begin{bmatrix} V_1^- \\ V_2^- \\ V_3^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ V_3^+ \end{bmatrix}$$

$V_2 = V_3 = \frac{1}{2} V_1 = 0.5 \text{ volt}$
 so $P_3 = \frac{1}{2} \times \frac{(0.5)^2}{100 + 33.3} = 9.38 \times 10^{-4} \text{ W}$

$P_3 = -30.3 \text{ dB}$

$V_2^- = V_2^+ + V_2^-$
 $V_2^- = P | V_2^+ |$
 $V_2^- = 1 \times 0$
 $V_3^- =$

* Case (2):

$V_3 = V_3^- \Rightarrow V_2 = V_2^+ + V_2^- \Rightarrow V_2 = 1.3 V_2^+$

$V_1^- = S_{12} V_2^+$
 $V_2^- = (0.3) V_2^+$

$P_3 = \frac{1}{2} \frac{|V_3^-|^2}{133.3} = \frac{|0.35|^2}{2 \times 133.3} = 4.6 \times 10^{-4} \text{ W}$

$P_3 = -33.4 \text{ dB}$

5.5


Question 2 (7 pts)

For the symmetric hybrid shown below. If port 1 is fed with an incident wave of $1 \angle 0$ V. Assume that the outputs are matched.

a) Construct the scattering matrix.

$$[S] = \begin{bmatrix} 0 & 1 & 0 & 0 & 1 \\ 1 & 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & 1 \\ 1 & 0 & 0 & 1 & 0 \end{bmatrix}$$

L
 $\sqrt{2}$
2-5

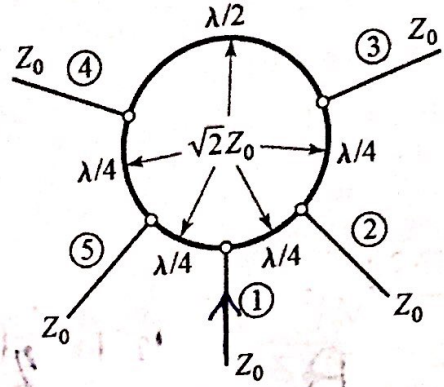

b) Calculate the phase between ports 3 and 4.


phase shift₍₃₂₄₎ = $\lambda/2 = \underline{\underline{180^\circ}}$

0.5

c) What are the coupler properties?

- ① Matched for all ports.
 - ② The Power is divided equally.
- 0.5

d) Draw the signal flow graph.

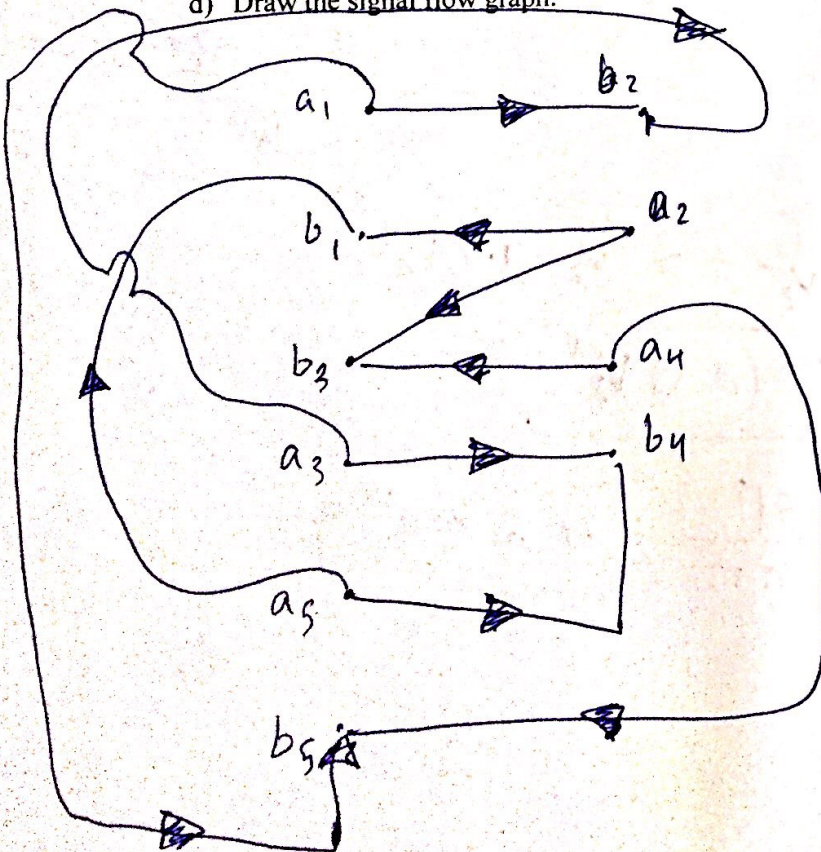

Question 3 (7 pts)

R_0

$$\frac{2\text{GHz} - 1.9\text{GHz}}{2} = \underline{\underline{0.05\text{GHz} = f_c}}$$


To suppress noise in a $50\ \Omega$ digital communication system a bandpass RF filter is required with a passband from 1.9 GHz to 2 GHz. The minimum attenuation of the filter at 6 GHz and 0.475 GHz should be 25 dB. Assuming that a 0.5 dB ripple in the passband can be tolerated.

- Design a filter that will use a minimum number of components.
- Draw the circuit and label all the components.
- Plot the attenuation as a function of frequency.
- Determine the frequency in which the attenuation equal to 10 dB.

(a) $\left| \frac{\omega}{\omega_c} \right| - 1 = \left| \frac{0.475\text{GHz}}{0.05\text{GHz}} \right| - 1 = 8.5$

so $N=1$

(b) consider the element is Capacitor

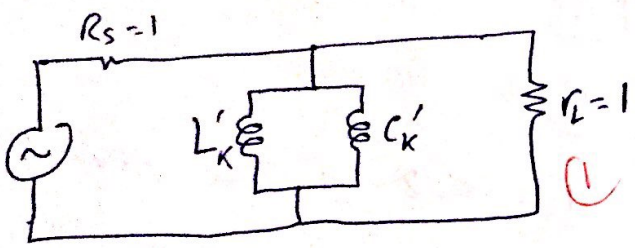


$g_1 = 0.6986$

$$L'_K = \frac{\Delta R_0}{\omega_c C_K}$$

$\Delta = 0.1$

$$L'_K = \frac{0.1 \times 50}{2\pi \times 50 \times 10^6 \times 0.6986} = \underline{\underline{22.78\text{ nH}}}$$
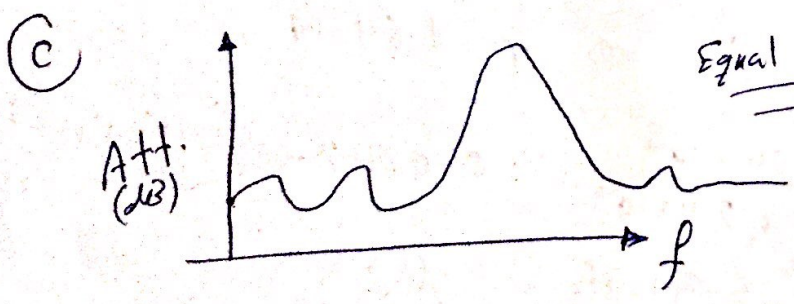
$$C'_K = \frac{C_K}{\Delta \omega_c R_0} = \frac{0.6986}{0.1 \times 2\pi \times 50 \times 10^6 \times 50} = \underline{\underline{0.445\text{ nF}}}$$



Equal ripple 0.5 dB.

(d) @ 10 dB $\Rightarrow \left| \frac{\omega}{\omega_c} \right| - 1 \approx 7.2$

$$\left| \frac{\omega}{\omega_c} \right| = 8.2 \Rightarrow \omega = 8.2 \omega_c = 8.2 \times 2\pi \times 50 \times 10^6$$

$$\Rightarrow \omega = 2\pi \times 410 \times 10^6 \text{ rad/s}$$

so $f = \underline{\underline{410\text{ MHz}}}$

Q4 Question 4 (5 pts)

Consider a microstrip resonator constructed from a $\lambda/2$ length of 50Ω open-circuited microstrip line. The substrate is FR-4 ($\epsilon_r = 4.4$, $\tan\delta = 0.02$), with a thickness of 0.78 mm , and the conductors are copper ($\sigma = 5.813 \times 10^7 \text{ S/m}$).

- Compute the required length of the line for resonance at 2.4 GHz , and the unloaded Q of the resonator. Ignore fringing fields at the end of the line.
- Sketch its equivalent RLC lumped circuit and determine their values.

(a) $Q_0 = \frac{\beta}{2\alpha} \dots (1)$

for μstrip : $A = \frac{Z_0}{60} \sqrt{\frac{\epsilon_r + 1}{2}} + \frac{\epsilon_r - 1}{\epsilon_r + 1} (0.23 + \frac{0.11}{\epsilon_r})$
 $= 1.53$

$B = \frac{377 \text{ A}}{2 Z_0 \sqrt{\epsilon_r}} = 5.65$

Assume $\frac{W}{d} < 2$: $\frac{W}{d} = 1.9 < 2$ True Assumption.

so $W = 0.78 \text{ mm} \times 1.9 \Rightarrow W = 1.482 \text{ mm}$

$\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} * \frac{1}{1 + \frac{12}{W/d}} = 3.329$

so $V_p = \frac{c}{\sqrt{\epsilon_e}} = \frac{3 \times 10^8}{\sqrt{3.329}} \Rightarrow V_p = 1.64 \times 10^8$

$l = \frac{\lambda}{2} = \frac{V_p}{2f} = \frac{1.64 \times 10^8}{2 \times 2.4 \times 10^9} = 0.0342 \text{ m} = 3.42 \text{ cm}$

$\beta = \frac{2\pi f}{V_p} = \frac{2\pi \times 2.4 \times 10^9}{1.64 \times 10^8} = 91.95 \dots (2)$

$\alpha_c = \frac{R_s}{Z_0 W} \Rightarrow R_s = \sqrt{\frac{\omega \mu_0}{2\sigma}} = \sqrt{\frac{2\pi \times 2.4 \times 10^9 \times 4\pi \times 10^{-7}}{2 \times 5.813 \times 10^7}} = 0.0128 \text{ Np/m}$


$\alpha_d = \frac{K_0 \epsilon_r (\epsilon_e - 1) \tan\delta}{2 \sqrt{\epsilon_e} (\epsilon_r - 1)} = \frac{50.3 \times 4.4 (3.329 - 1) (0.02)}{2 \sqrt{3.329} (4.4 - 1)} = 0.8309 \text{ Np/m}$

$K_0 = 50.3$

so $\alpha_{\text{Total}} = \alpha_c + \alpha_d = 0.8309 + 0.0128 = 0.8437 \text{ Np/m} \dots (3)$

Substitute (2) & (3) into (1)

$\Rightarrow Q_0 = 108.98$

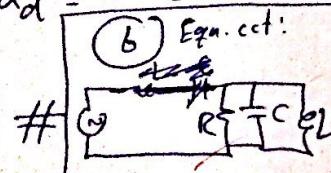

$R = \frac{Z_0}{\alpha l} = 1732.83 \Omega$

$C = \frac{\pi}{2\omega_0 Z_0} = 2.083 \text{ pF}$

$L = \frac{1}{\omega_0^2 C} = 2.111 \text{ nH}$