

Lecture 01

Operational Amplifiers

Op-Amps

Introduction

Chapter 9



Ideal Operational Amplifiers and Op-Amp Circuits

*Donald A. Neamen (2009). **Microelectronics: Circuit Analysis and Design**,
4th Edition, Mc-Graw-Hill*


Prepared by: Dr. Hani Jamleh, *School of Engineering, The University of Jordan*

Integrated Circuit

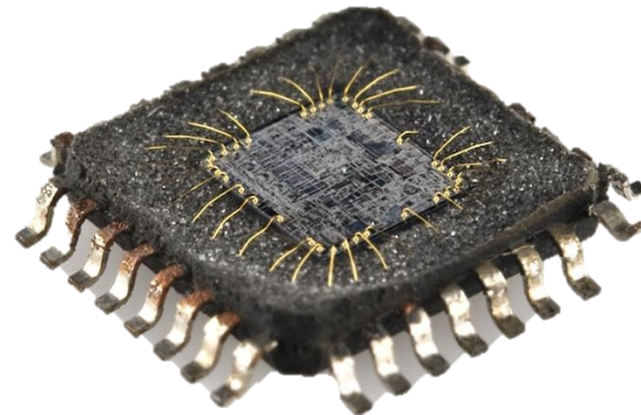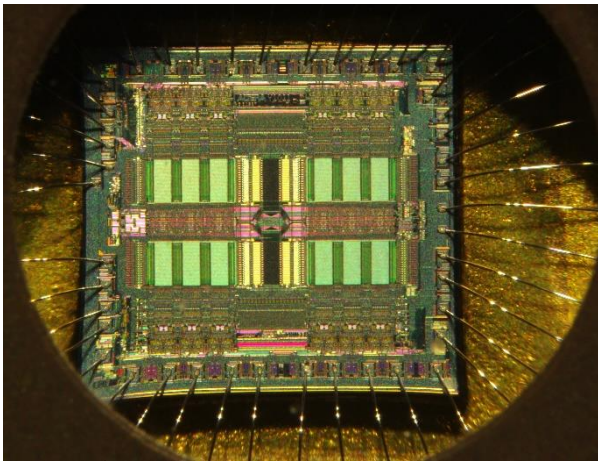- An **integrated circuit** (more often called an **IC**, microchip, silicon chip, computer chip, or chip) is a piece of specially prepared silicon (or another semiconductor) into which a very complex electronic **circuit** is etched using photographic techniques.



Integrated Circuit (IC Chip)

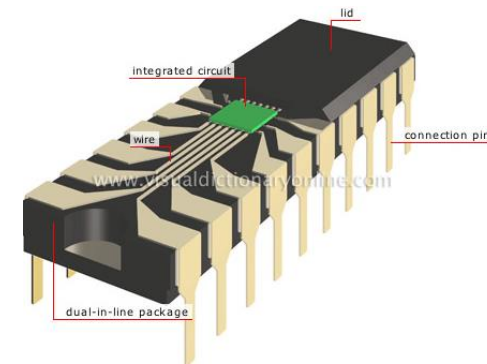


Introduction

- An **operational amplifier** (op-amp) is an integrated circuit that:
 - Amplifies the difference between two input voltages and
 - Produces a single output.
- The op-amp is dominant in analog electronics, and can be thought of as another electronic device, in much the same way as the BJT or MOSFET.


Introduction

- The term **operational amplifier** comes from the original applications of the device in the early 1960s.
 - Op-amps, in conjunction with resistors and capacitors, were used in analog computers **to perform mathematical operations** to solve:
 - Differential equations and
 - Integral equations.
 - The applications of op-amps have expanded significantly since those early days.

Op Amp

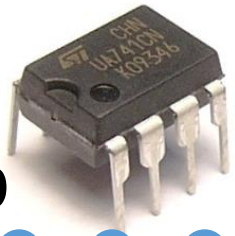

Resistors

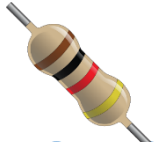



Capacitors



Inductors




Diodes

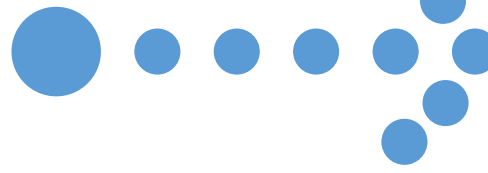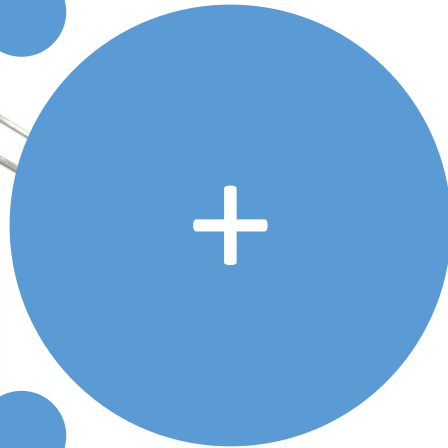

Arithmetic Operations:

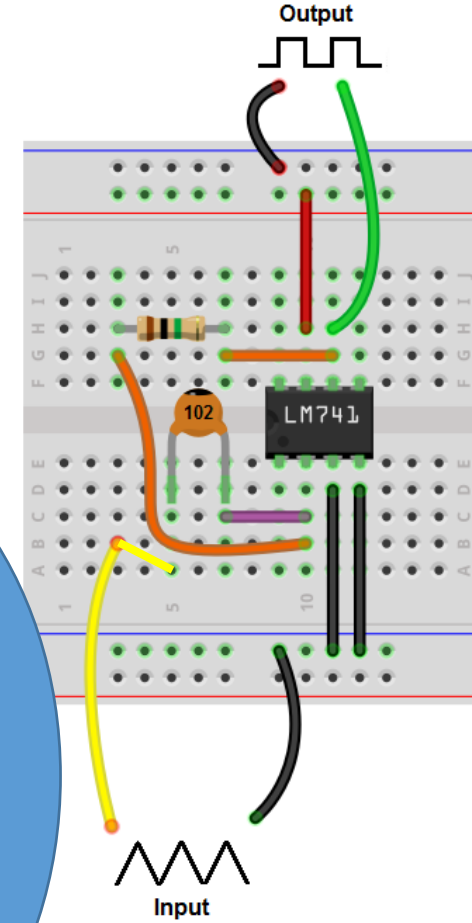- Addition
- Subtraction
- Integration
- Differentiation
- etc.




Introduction

- Our aim is to develop the **ideal characteristics of the op-amps**.
- You can then be more comfortable applying these ideal characteristics in the design of op-amp circuits.
- We will develop a basic op-amp equivalent circuit with:
 - A **dependent source** that represents the device gain that can be used to determine some of the nonideal properties of op-amp circuits.

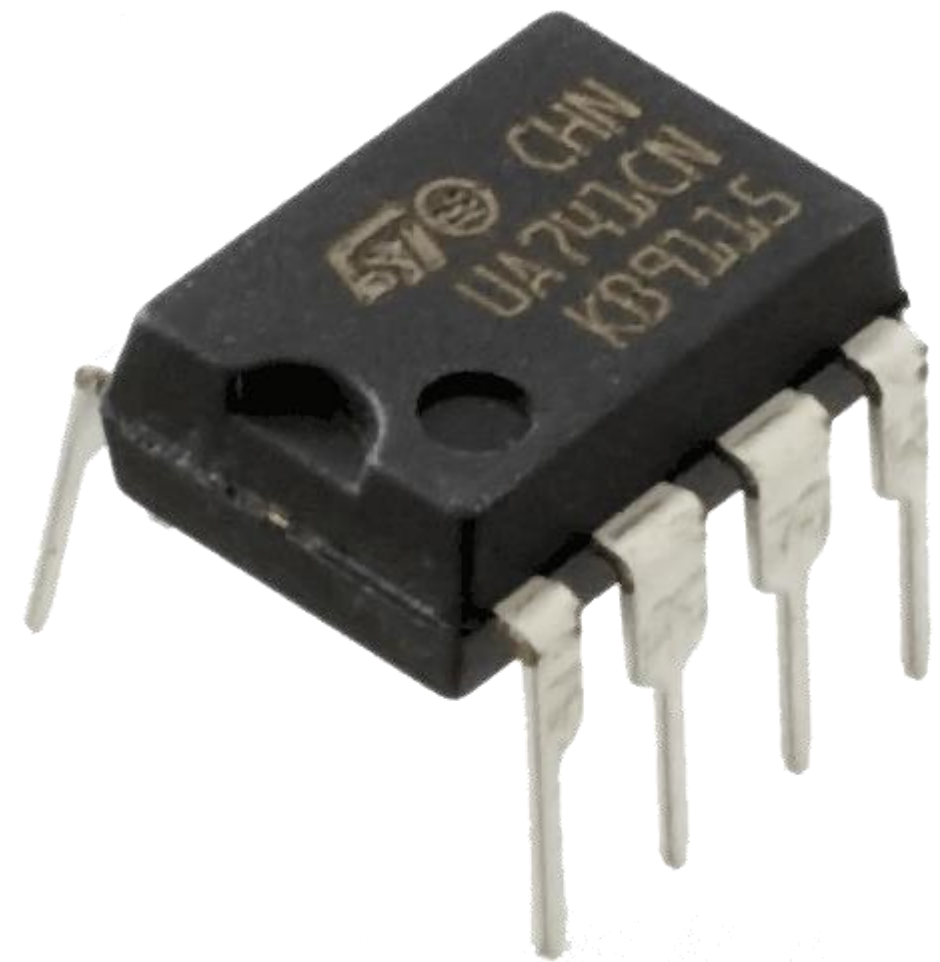
9.1 The Operational Amplifier

- The classic $\mu\text{A}-741$, by Fairchild, was introduced in the late 1960s.
- Since then, a vast array of op-amps with improved characteristics, using both bipolar and MOS technologies, have been designed.
- Most op-amps are very inexpensive (less than a \$dollar\$).






FAIRCHILD
SEMICONDUCTOR®

9.1 The Operational Amplifier

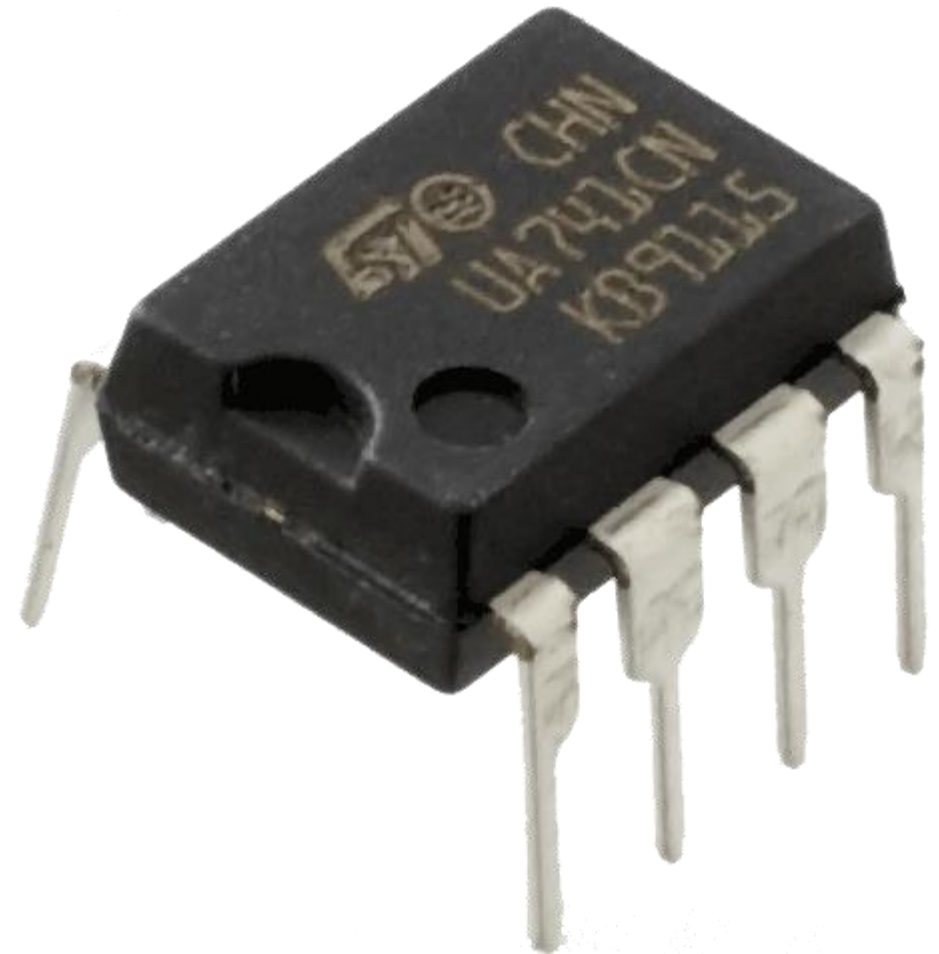

9.1 The Operational Amplifier

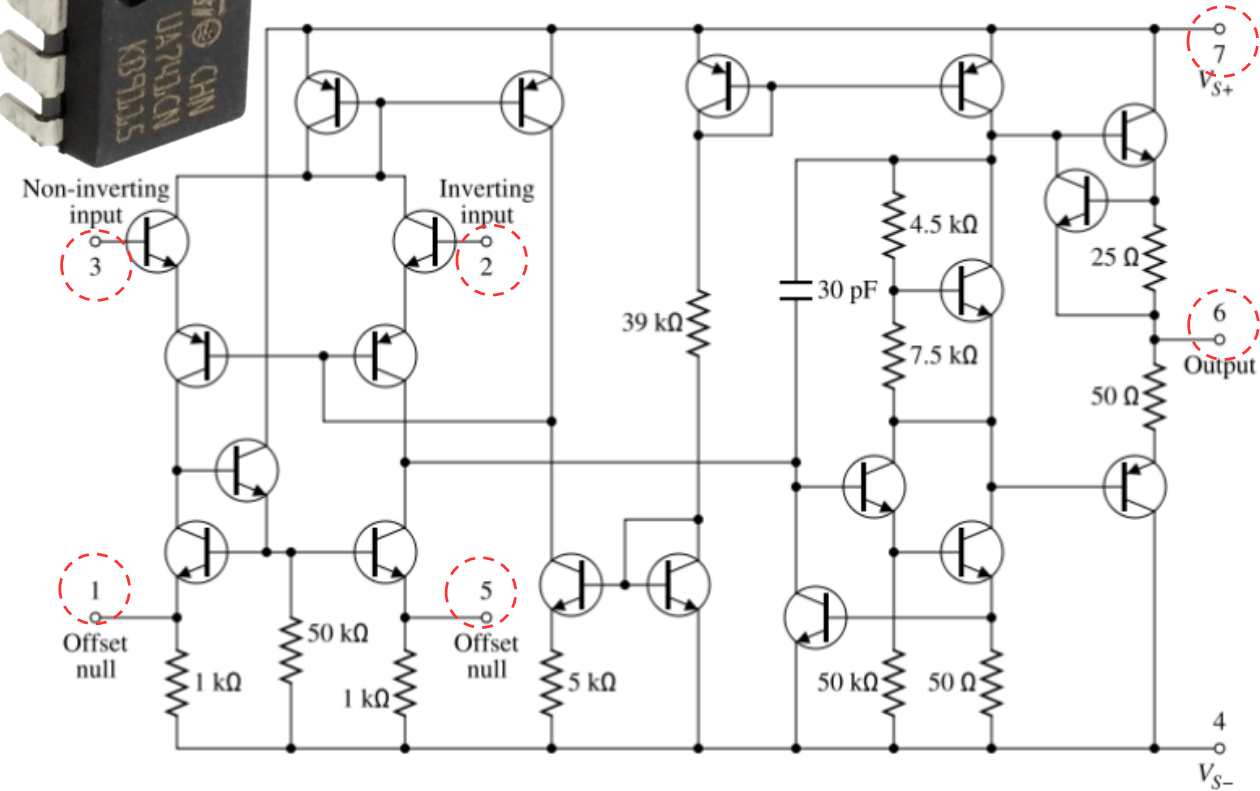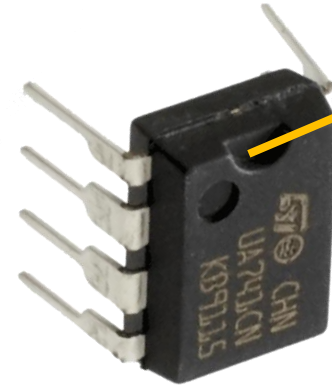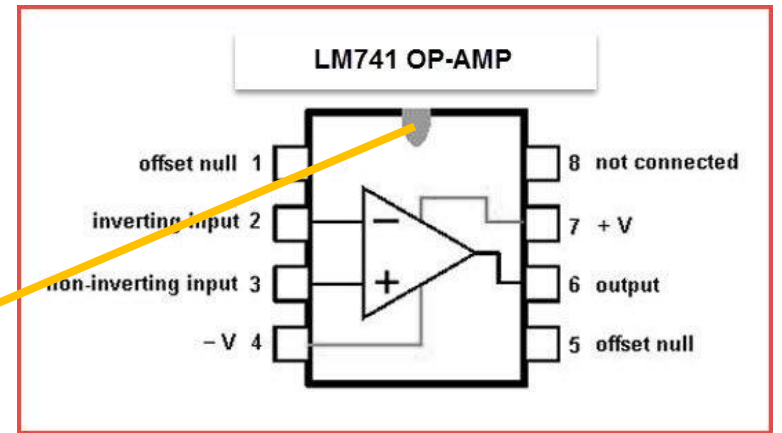

9.1 The Operational Amplifier

- From a signal point of view, the op-amp has:
 - Two input terminals and
 - One output terminal.

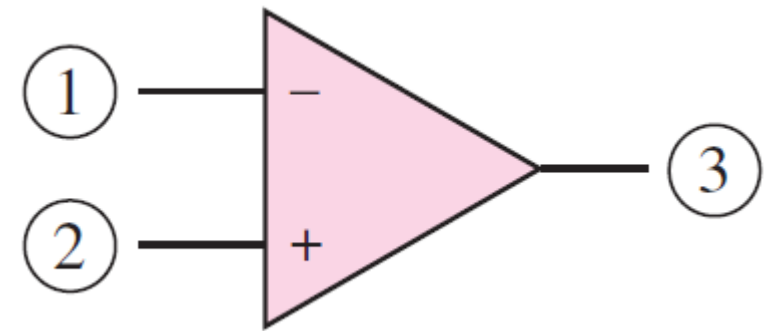


Figure 9.1(a)

9.1 The Operational Amplifier

- The op-amp also **requires** DC power so that the transistors are biased in the active region.
 - Op-amp is an **active device**.
- Most op-amps are **biased** with both:
 - A positive voltage supply V^+ and
 - A negative voltage supply V^- .


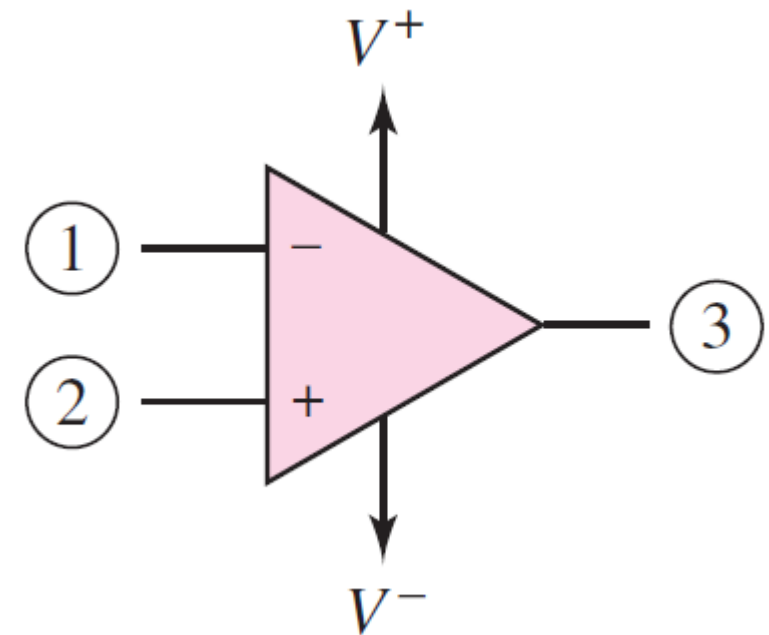


Figure 9.1(b)


9.1 The Operational Amplifier

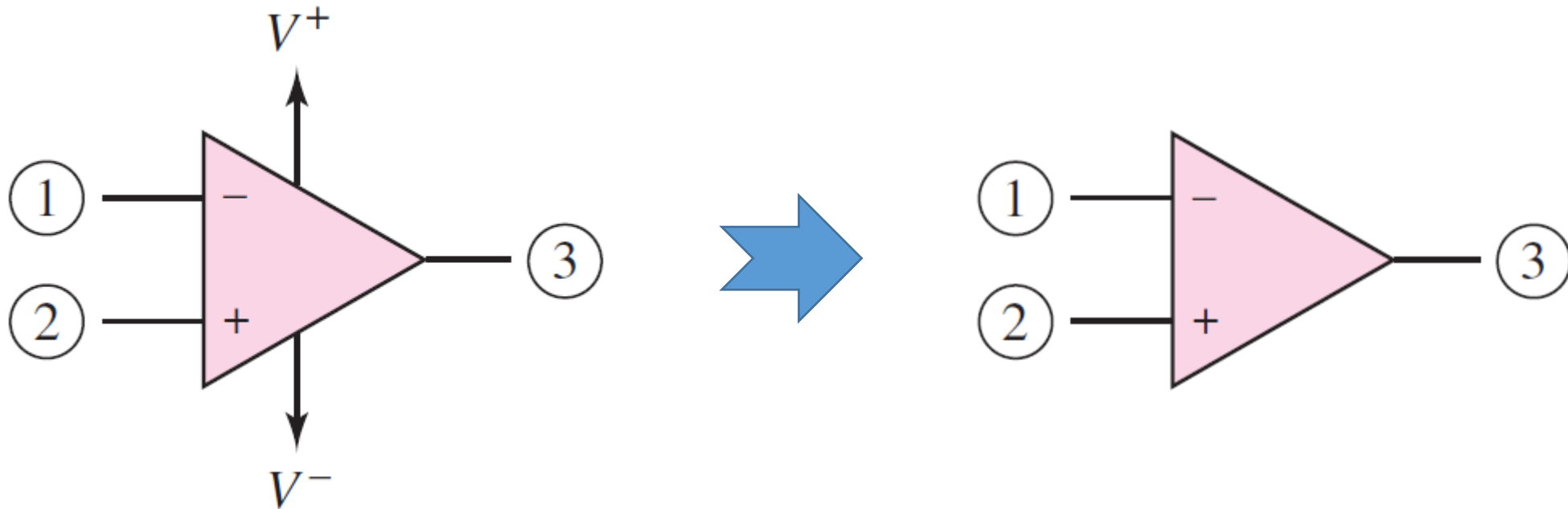

- No need to draw the voltage supplies: V^+ and V^-

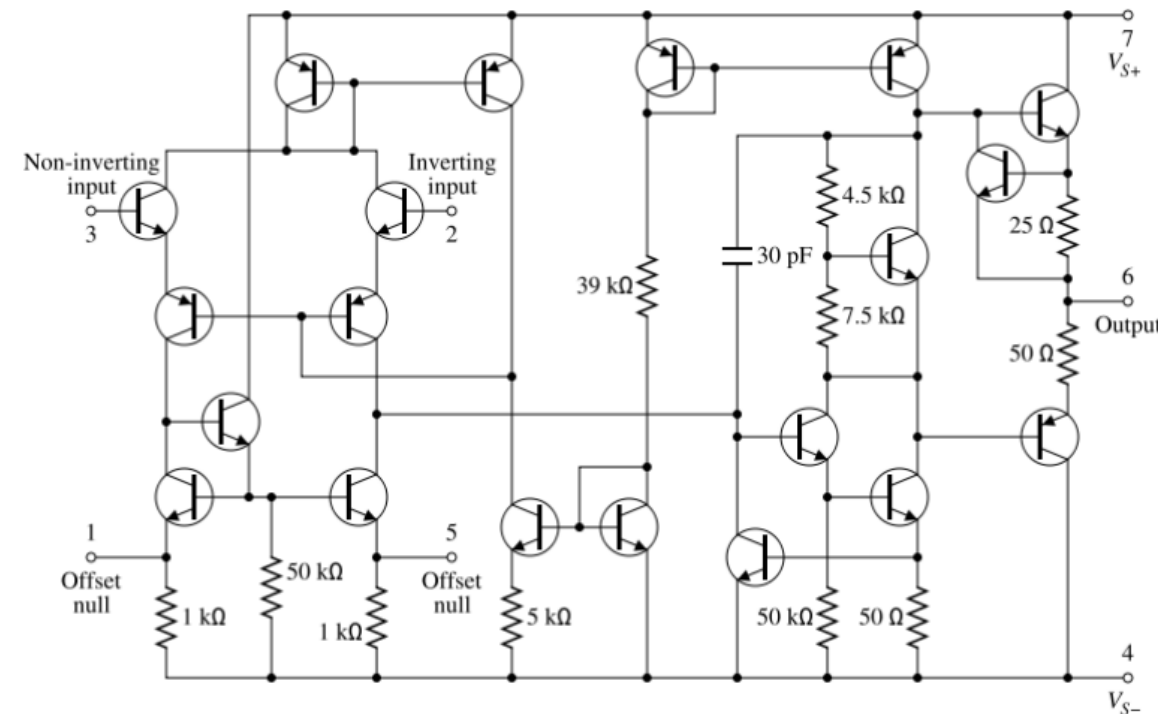
9.1 The Operational Amplifier

- There are normally 20 to 30 transistors that **make up** an op-amp circuit.
- The typical IC op-amp has **parameters** that **approach** the “ideal characteristics.”
 - For this reason, we can treat the op-amp as a “simple” electronic device.
 - It is **quite easy to design a wide range of circuits** using the IC op-amp.



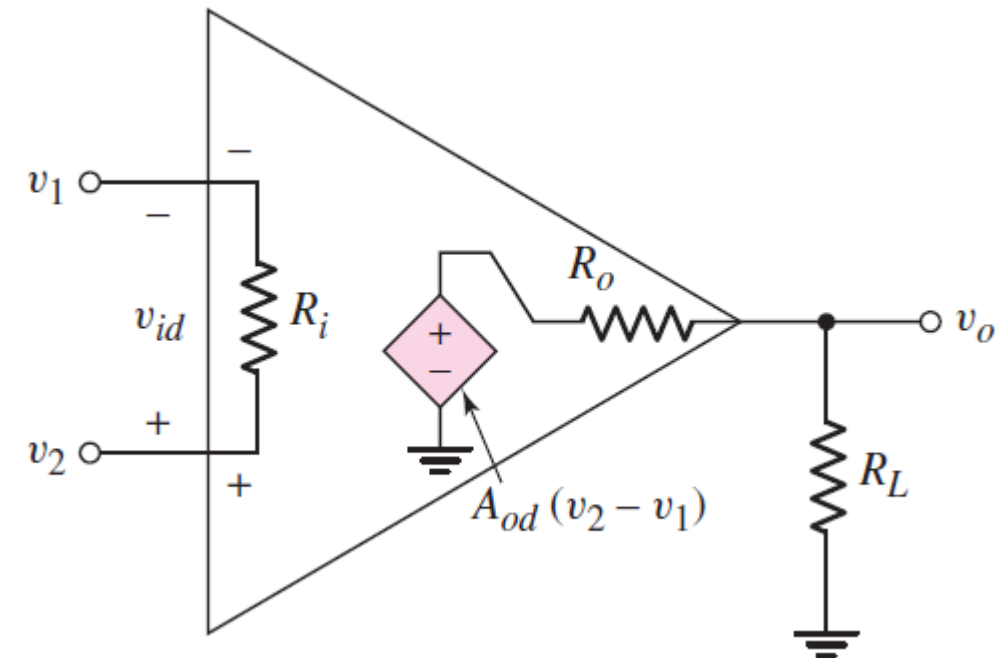9.1 The Operational Amplifier

- In this chapter:
 - We **develop** the ideal set of **op-amp parameters**.
 - We **consider** the analysis and design of a wide variety of op-amp circuits.
 - In this Chapter, we generally **assume**, that the op-amp is **ideal**.



9.1.1 Ideal Parameters

- What is the basic operation principle of op-amp?
 - The ideal op-amp **senses** the difference between two input signals, i.e. v_1 and v_2 , and **amplifies** this difference to **produce** an output signal v_o .
- What is the “terminal voltage”?
 - It is the voltage at a terminal measured **with respect to ground**.
- The ideal op-amp equivalent circuit is shown in Figure 9.2.

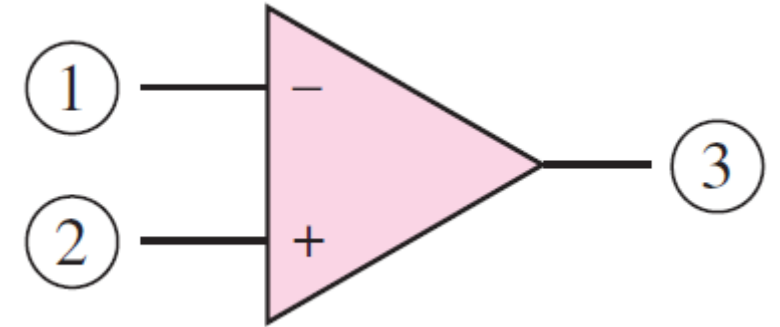


Figure 9.1(a)

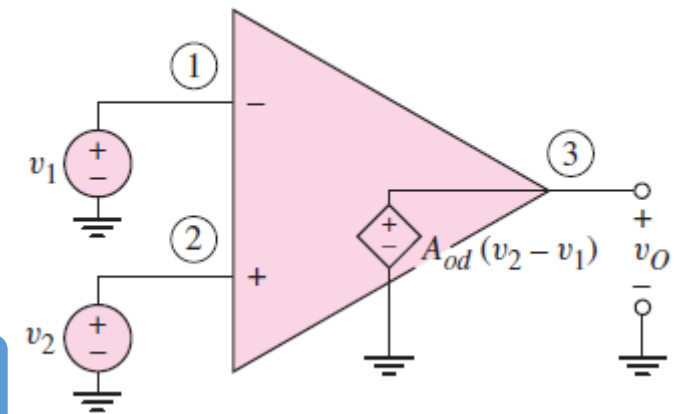


Figure 9.2

9.1.1 Ideal Parameters

Input Resistance R_i

- Ideally, the **input resistance R_i** between terminals 1 and 2 is infinite

$$R_i \rightarrow \infty:$$

- Which means that the **input current** at each terminal is **zero**.

$$i_1 = i_2 = 0$$

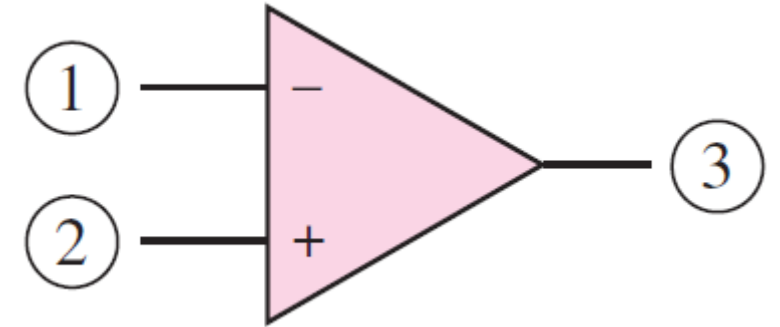


Figure 9.1(a)

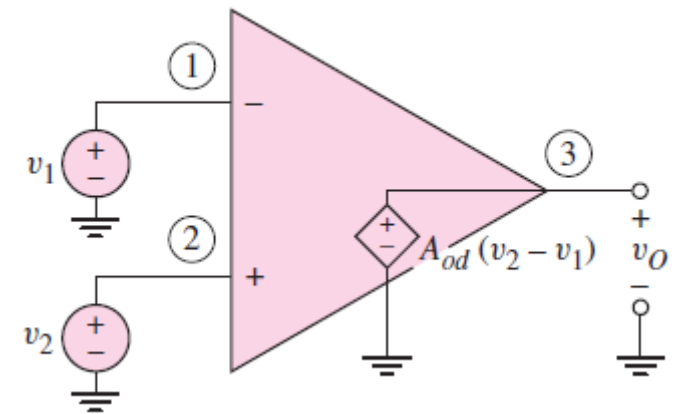


Figure 9.2

9.1.1 Ideal Parameters

Output Resistance R_o

- The **output terminal** of the ideal op-amp **acts** as the output of an ideal voltage source:
 - Meaning that the small-signal **output resistance R_o** is **zero**.

$$R_o \rightarrow 0$$

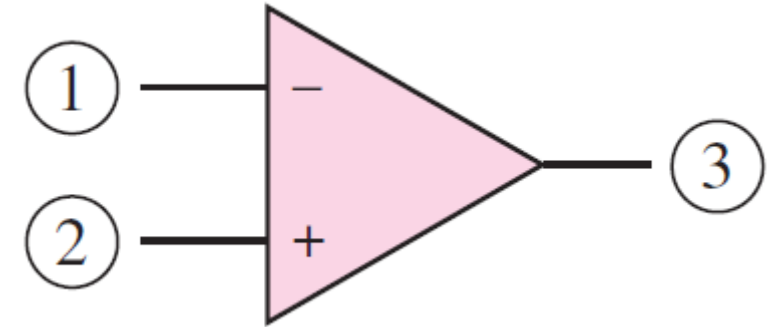


Figure 9.1(a)

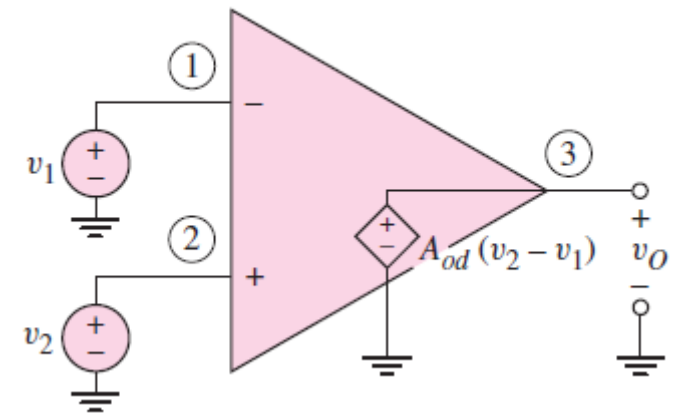


Figure 9.2

9.1.1 Ideal Parameters

Differential Voltage Gain A_{od}

- The parameter A_{od} shown in the equivalent circuit is the open-loop **differential voltage gain** of the op-amp.
- In the ideal op-amp, the **open-loop gain** A_{od} is **very large** and approaches infinity.

$$A_{od} \rightarrow \infty$$

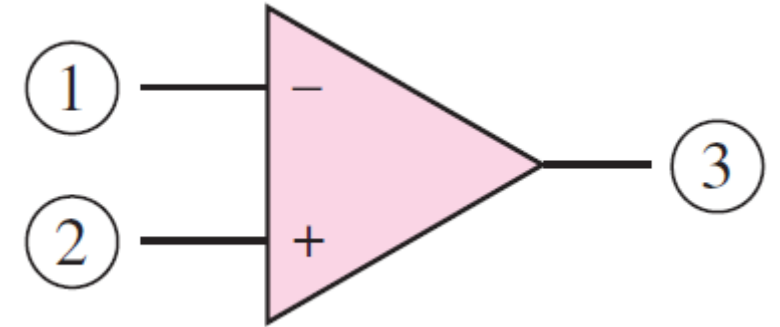


Figure 9.1(a)

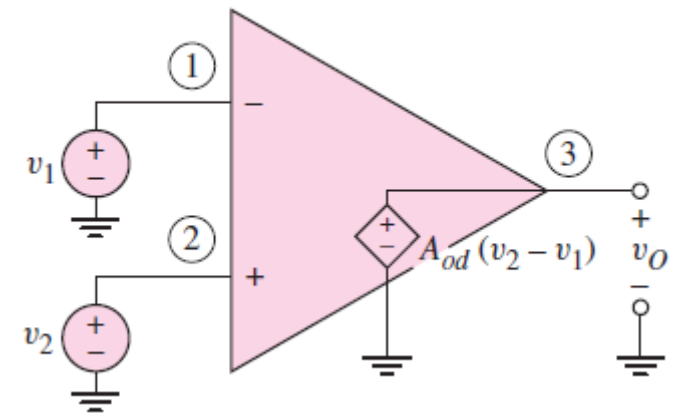


Figure 9.2

9.1.1 Ideal Parameters

Inverting/Noninverting Input Terminal v_1 & v_2

- Terminal (1):
 - Is the **inverting** input terminal, designated by the “-” notation.
- Terminal (2):
 - Is the **noninverting** input terminal, designated by the “+” notation.
- The output is:
 - **Out of phase** with respect to v_1 and
 - **In phase** with respect to v_2 .
 - **Why?**

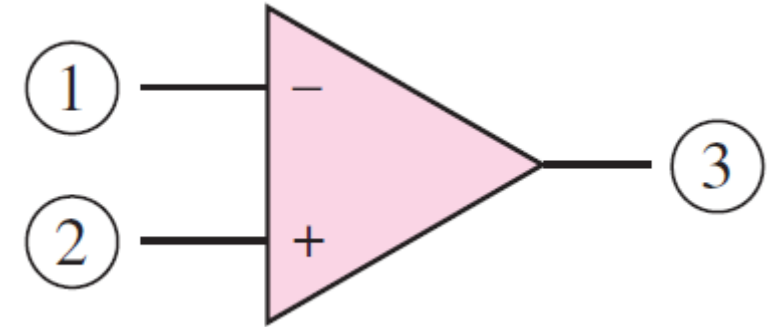


Figure 9.1(a)

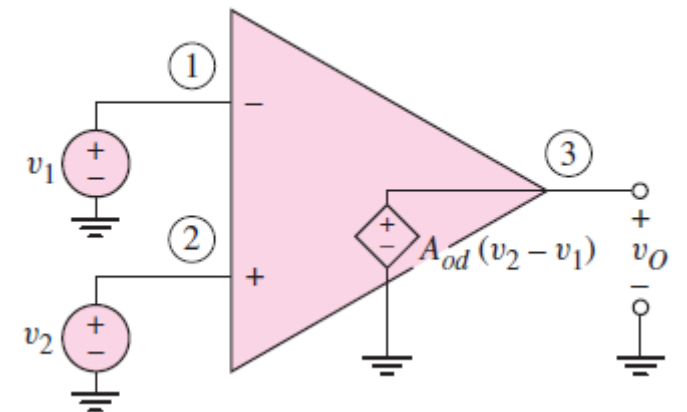


Figure 9.2

9.1.1 Ideal Parameters

Inverting/Noninverting Input Terminal v_1 & v_2

- The ideal op-amp **responds** only to the difference between the two input signals v_1 and v_2 :
 - The ideal op-amp **maintains** a zero output signal for $v_1 = v_2$.
- When $v_1 = v_2 = 0$:
 - It is called a **common-mode input signal**.
 - For the **ideal** op-amp, the common-mode output signal is $v_o = \text{zero}$.
 - This characteristic is referred to as **common-mode rejection**.

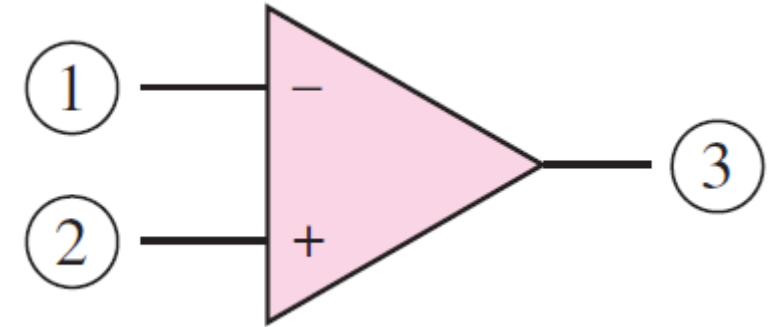


Figure 9.1(a)

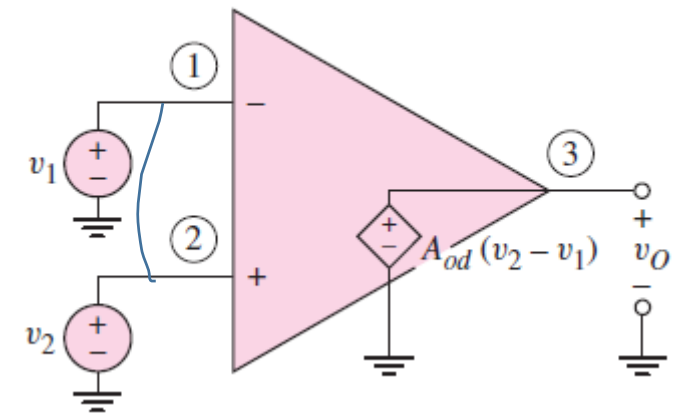


Figure 9.2

9.1.1 Ideal Parameters

Inverting/Noninverting Input Terminal v_1 & v_2

- Because the device is **biased** with both positive and negative power supplies, most op-amps are **direct-coupled devices**.
 - No coupling capacitors are used on the input.
 - Therefore, the input voltages v_1 and v_2 shown in Figure 9.2 can be DC voltages, which will **produce** a DC output voltage v_o .

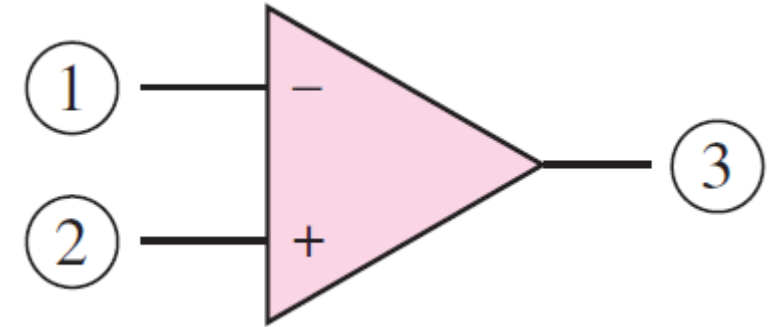


Figure 9.1(a)

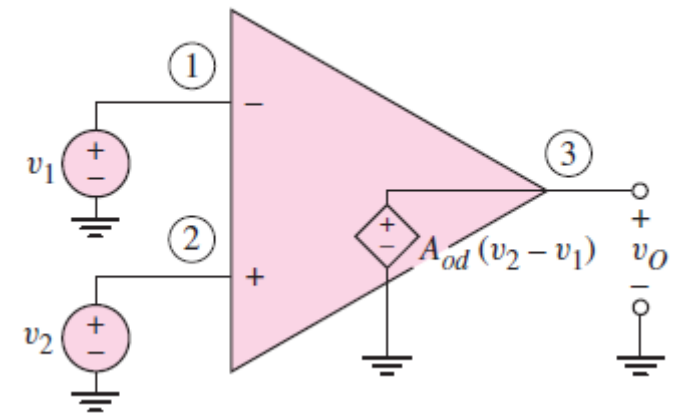


Figure 9.2

9.1.1 Ideal Parameters

Bandwidth

- Another characteristic of the op-amp that must be considered in any design is:
 - the **bandwidth** or **frequency response**.
- In the ideal op-amp, this parameter is **neglected**, *i. e.* $BW \rightarrow \infty$.

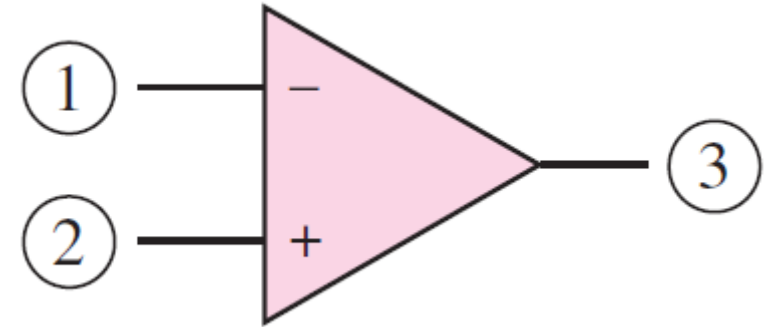


Figure 9.1(a)

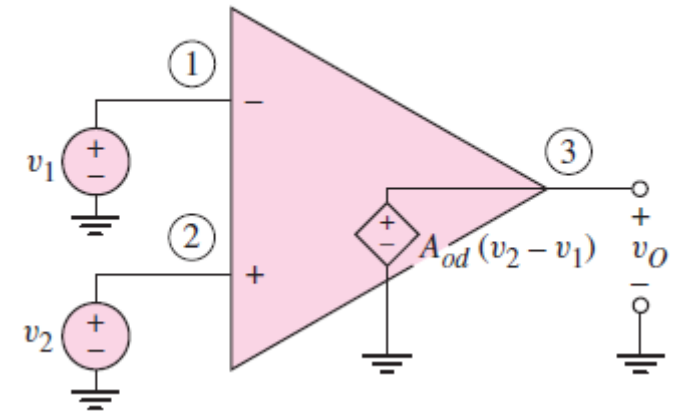


Figure 9.2