

L02

Operational Amplifiers

Applications 1

Chapter 9

Ideal Operational Amplifiers and Op-Amp Circuits

Donald A. Neamen (2009). **Microelectronics**: Circuit Analysis and Design,
4th Edition, Mc-Graw-Hill

Prepared by: Dr. Hani Jamleh, *Electrical Engineering Department, The University of Jordan*

9.1.3 Analysis Method

Feedback

- Usually, an op-amp is not used in the **open-loop configuration** shown in Figure 9.2.
 - **Feedback** is added to **close the loop** between the output and the input.
 - **Negative feedback:**
 - The output is connected to the **inverting terminal**.
 - This configuration **produces stable circuits**.
 - **Positive feedback:**
 - The output is connected to the **noninverting terminal**.
 - This configuration can be used to **produce oscillators**.

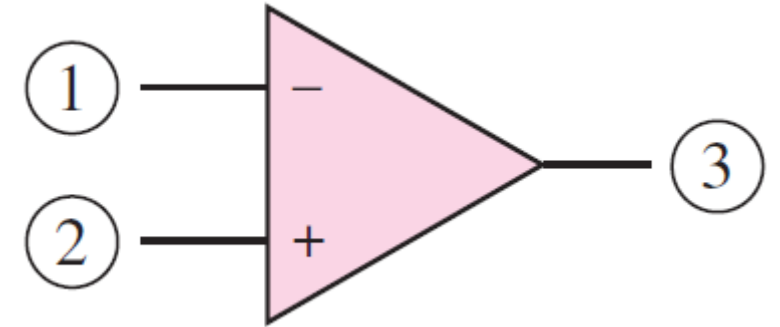


Figure 9.1(a)

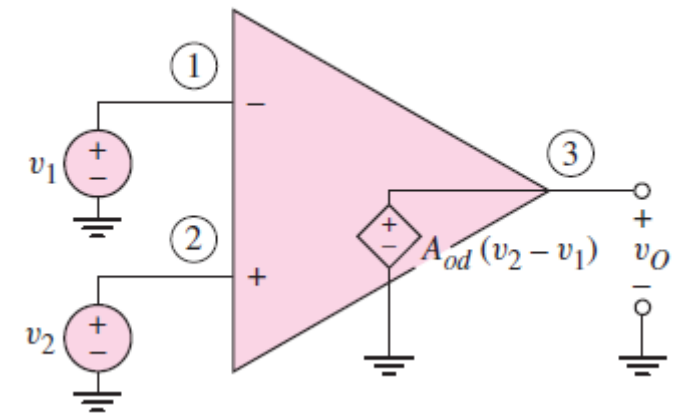


Figure 9.2

9.1.3 Analysis Method

Two Port Network Voltage Amplifier


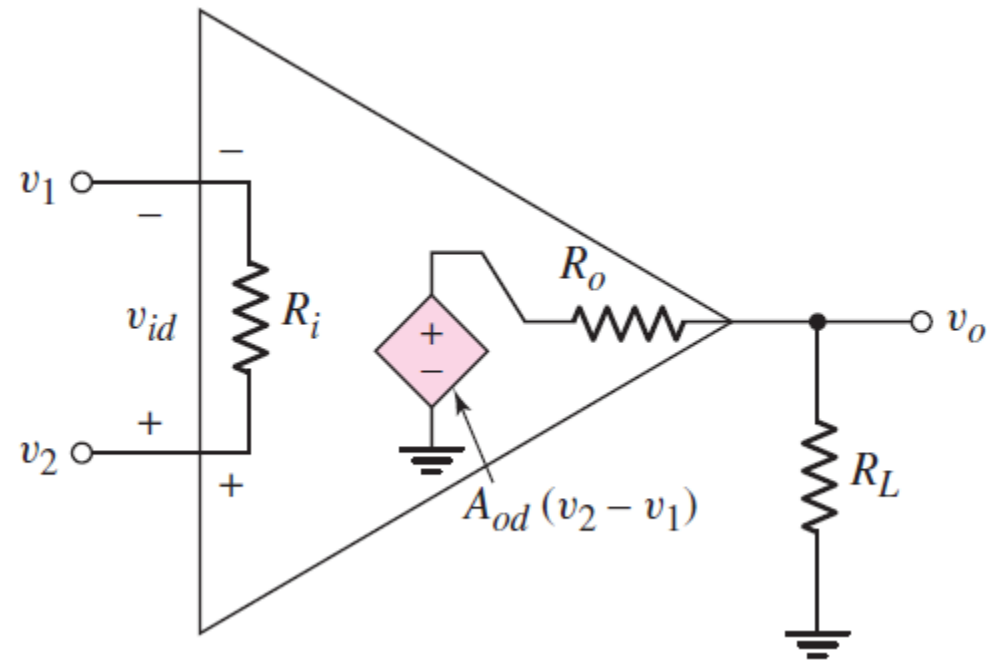


Figure 9.7(a)

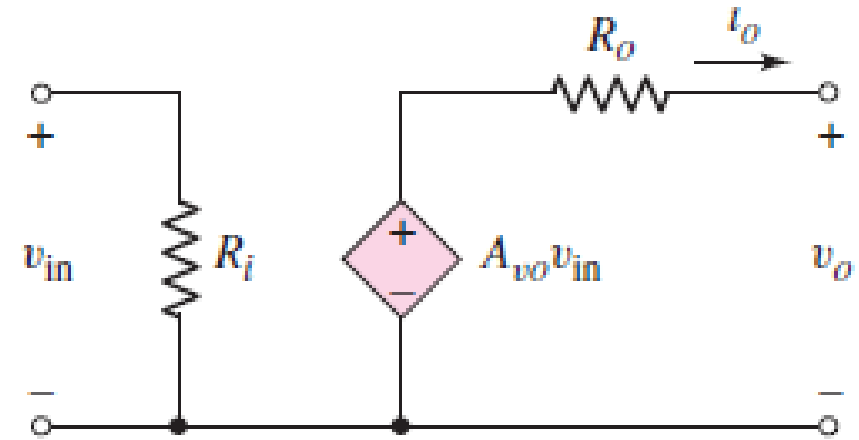

9.1.3 Analysis Method

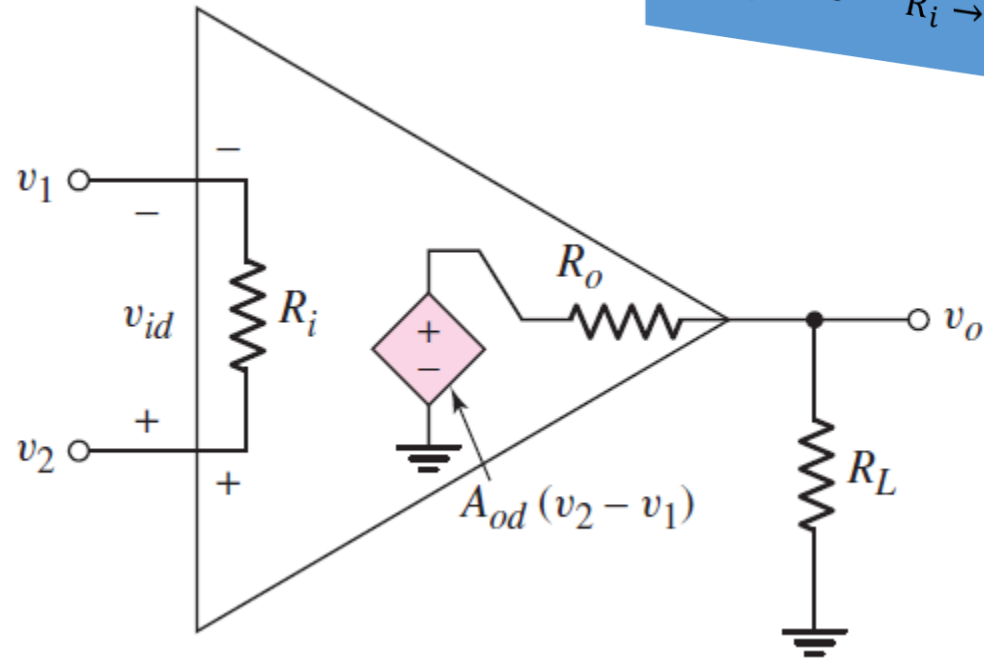
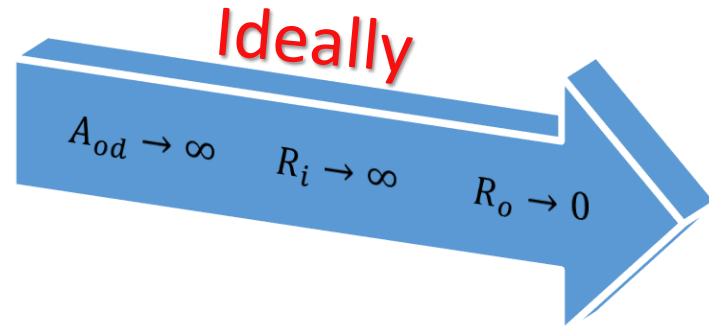


Figure 9.7(a)

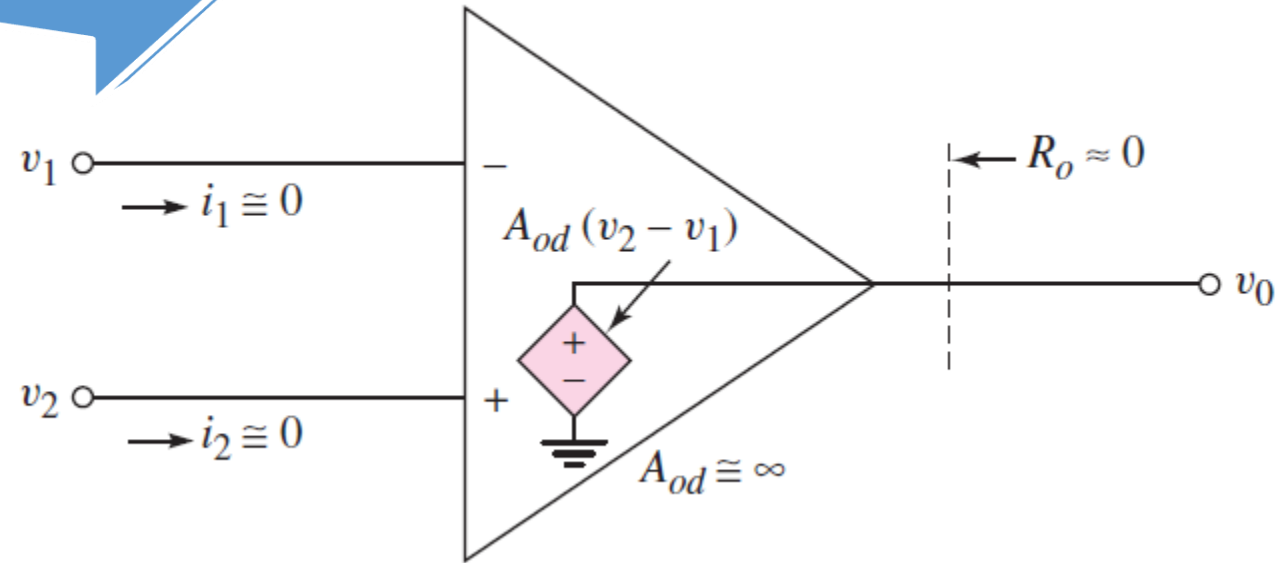


Figure 9.6

9.1.3 Analysis Method

Ideal op-amp characteristics

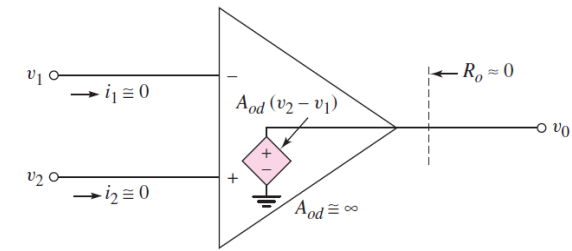


Figure 9.6

- The **ideal op-amp** characteristics resulting from our negative feedback analysis are shown in Figure 9.6 and summarized below.

- The **internal differential gain** A_{od} is considered to be *infinite*.

- The **differential input voltage** $(v_2 - v_1)$ is assumed to be *zero*.

- If A_{od} is very large and if the output voltage v_o is finite, then the two input voltages must be nearly equal.

$$v_o = A_v(v_2 - v_1) \rightarrow (v_2 - v_1) = \frac{v_o}{A_v} \rightarrow (v_2 - v_1) = \frac{v_o}{\infty} = 0 \rightarrow \boxed{v_2 = v_1}$$

- The **effective input resistance** R_i to the op-amp is assumed to be *infinite*, so the two input currents, $\boxed{i_1 = i_2 = 0}$.

- The **output resistance** R_o is assumed to be *zero*, so the output voltage:

- is connected directly to the dependent voltage source, and
- is independent of any load connected to the output.

9.1.4 Practical Specifications

- **Practical** op-amps are **not ideal**.
 - Although their characteristics **approach** those of an ideal op-amp.
- Figure 9.7(a) is a **more accurate equivalent circuit** of an op-amp.
- A load resistance R_L is connected to the output terminal.
 - R_L may actually **represent** another op-amp circuit.

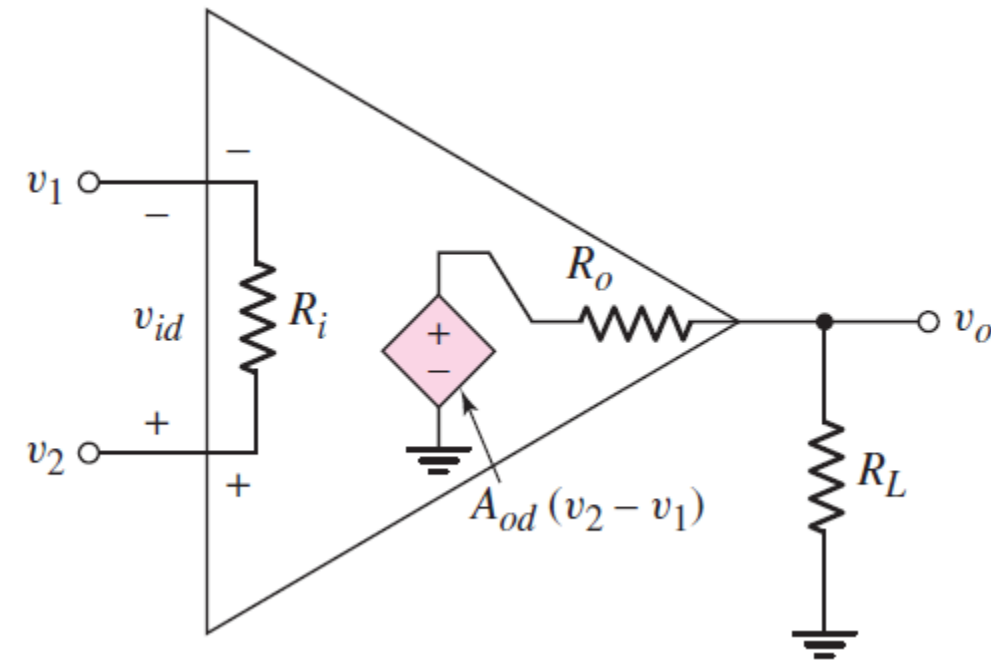


Figure 9.7(a)

9.1.4 Practical Specifications

Output Voltage Swing

- Since the op-amp is composed of transistors **biased** in the **active region** by the DC input voltages V^+ and V^- , the **output voltage is limited**.
 - When $v_o \rightarrow V^+$, it **will saturate** at a value nearly equal to V^+ .
 - When $v_o \rightarrow V^-$, it **will saturate** at a value nearly equal to V^- .
 - v_o **cannot go** above the V^+ or below the V^- .
- The output voltage is limited to:

$$V^- + \Delta V < v_o < V^+ - \Delta V$$

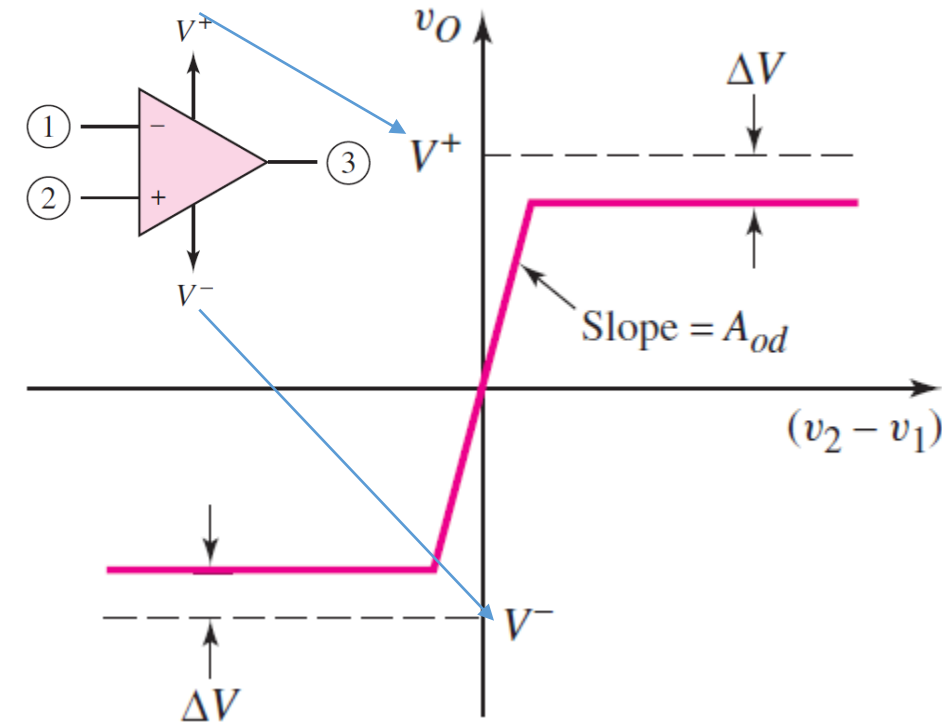


Figure 9.7(b)

9.1.4 Practical Specifications

Output Voltage Swing

- Figure 9.7(b) is a simplified voltage transfer characteristic for the op-amp, showing the saturation effect.
- In older op-amp designs, such as the 741, the **value of ΔV** is between 1 and 2V.
 - Example: If $V^+ = 15V$ and $V^- = -15V$, let $\Delta V = 2V$ then:
$$-13 < v_o < 13$$

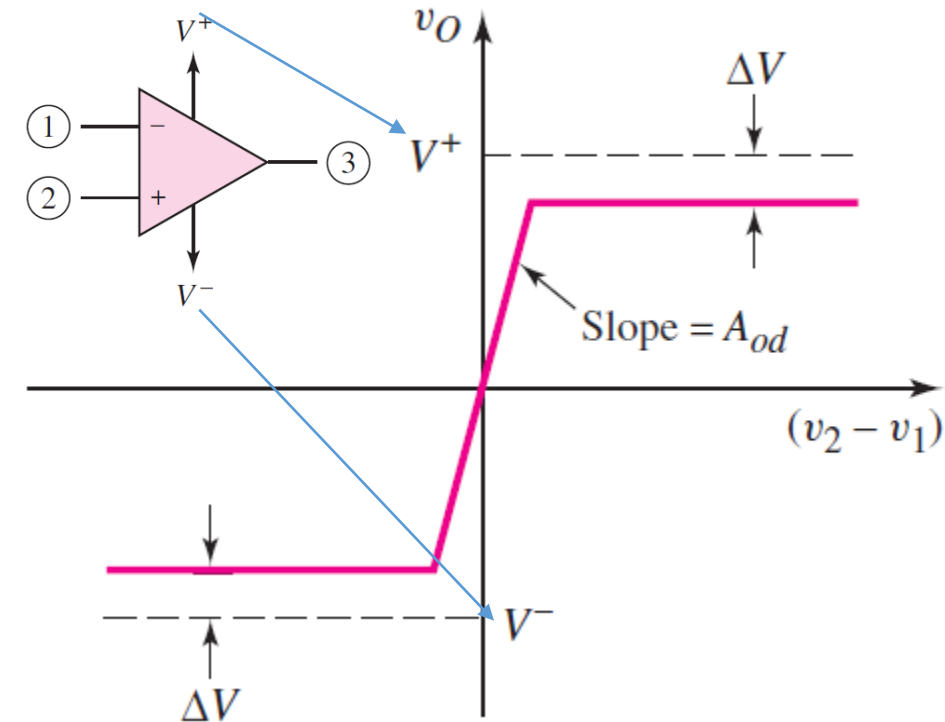


Figure 9.7(b)

9.1.4 Practical Specifications

Output Currents

- As we can see from Figure 9.7(a):
 - If the output voltage is positive, the load current is **supplied** by the output of the op-amp.
 - If the output voltage is negative, then the output of the op-amp **sinks** the load current.
- A limitation of practical op-amps is the **maximum current** that an op-amp can **supply or sink**.
- A typical value of **the maximum current** is on the order of $\pm 20mA$ for a general-purpose op-amp.


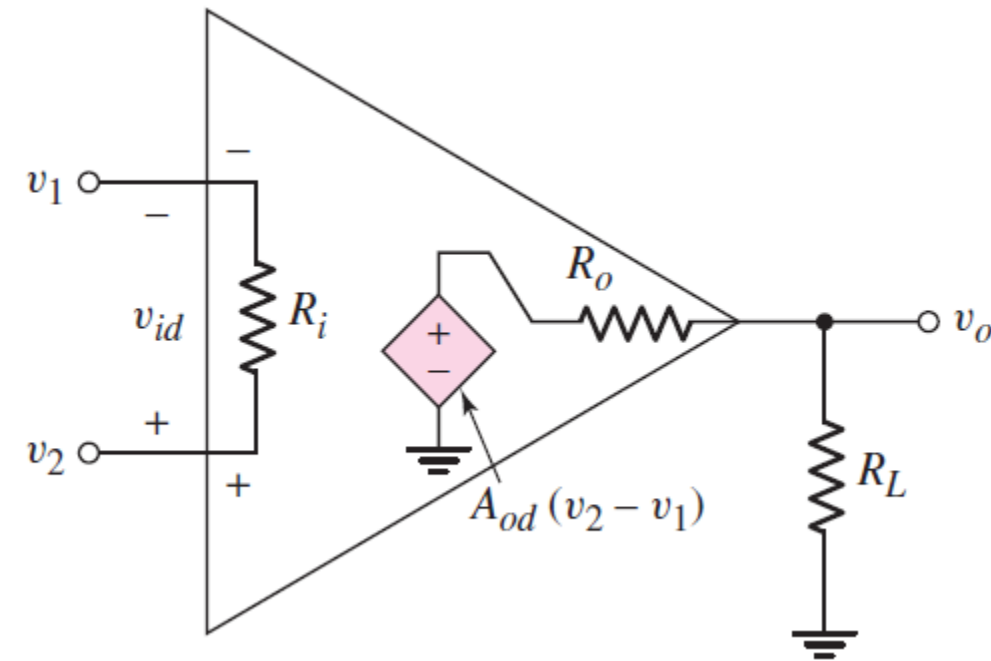


Figure 9.7(a)


Op-Amp Applications

1. Inverting Amplifier
2. Amplifier with T-Network
3. Non-Inverting Amplifier
4. Voltage Follower (Buffer)
5. Summing Amplifier
6. Current to Voltage Converter


1

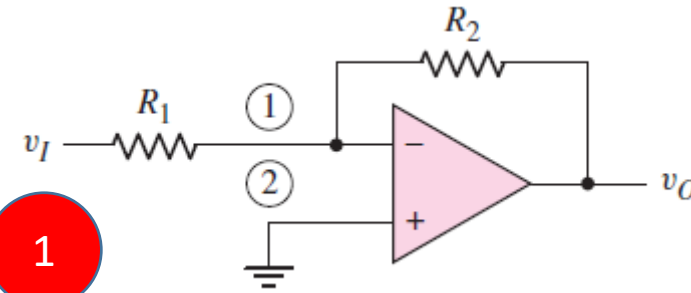


3

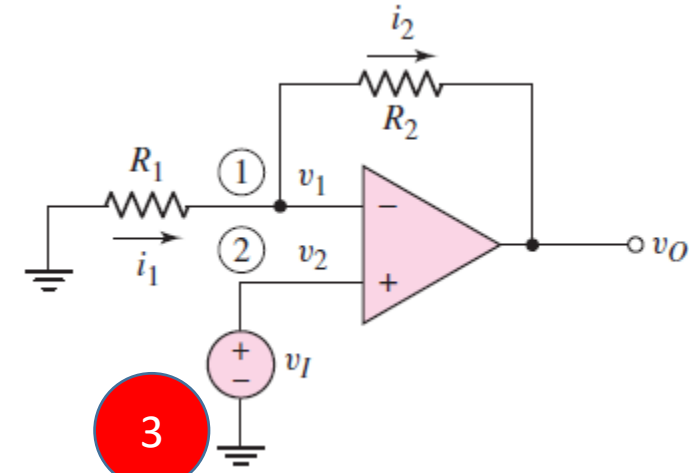


2

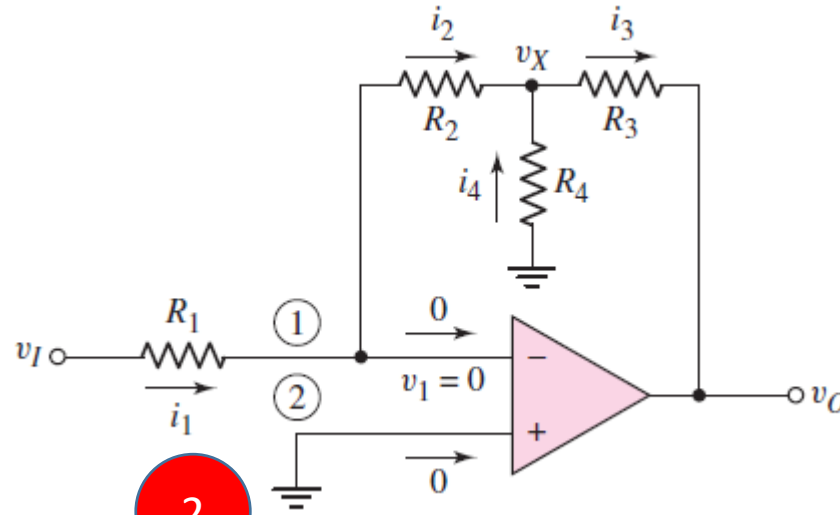


4

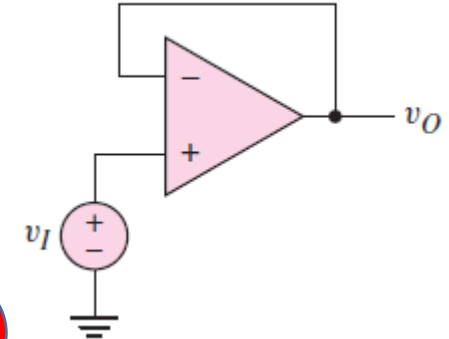

5

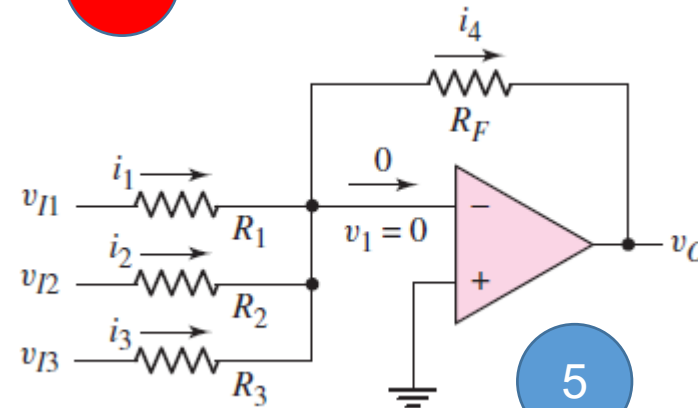

6

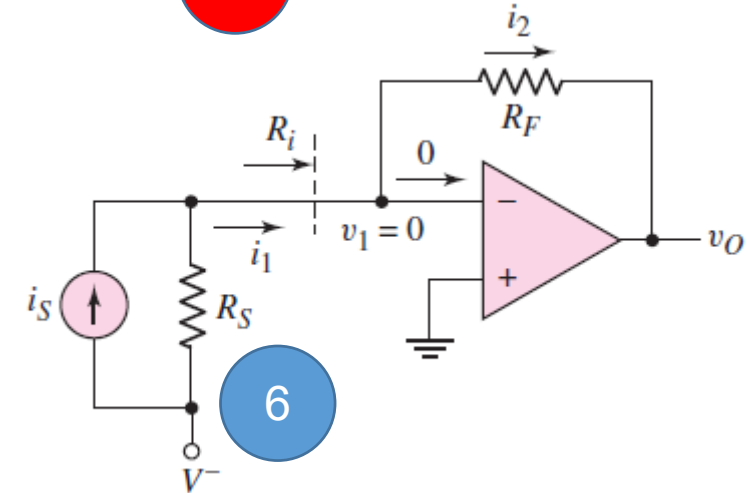

Op-Amp Applications

7. Difference Amplifier


8. Instrumentation Amplifier

9. Integrator


10. Differentiator

11. Reference Voltage Source Design


12. Precision Half-wave Rectifier

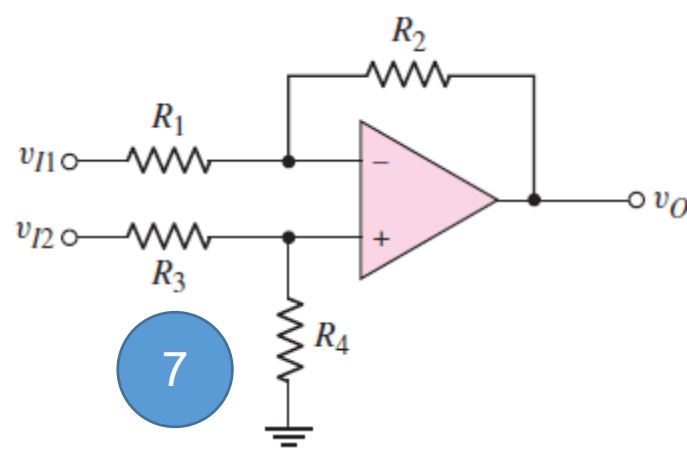


7

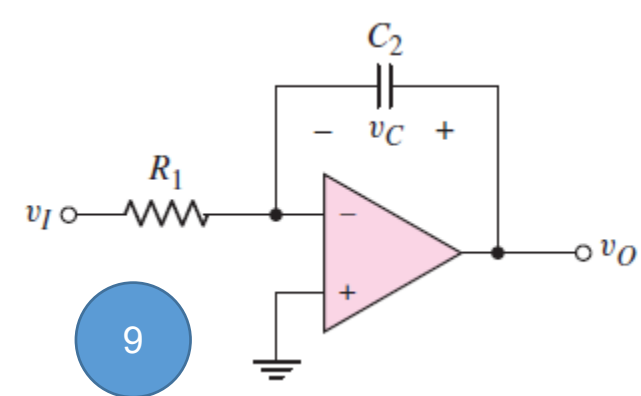


9

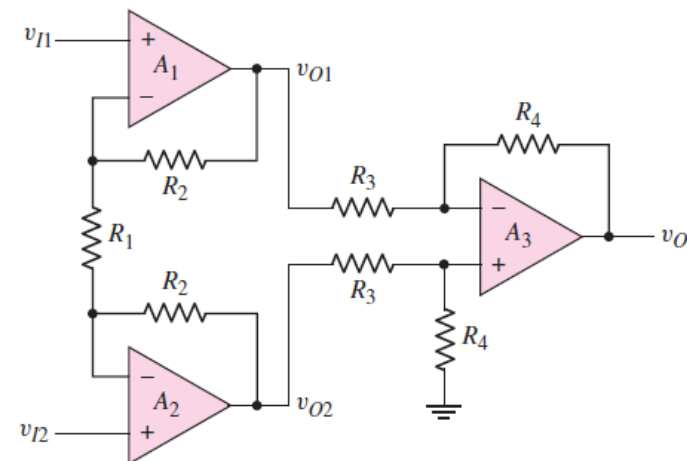


8

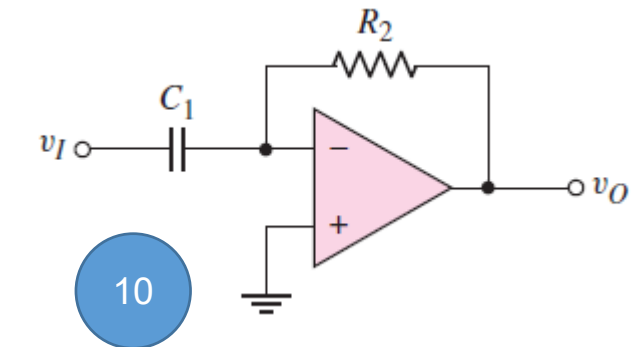

10

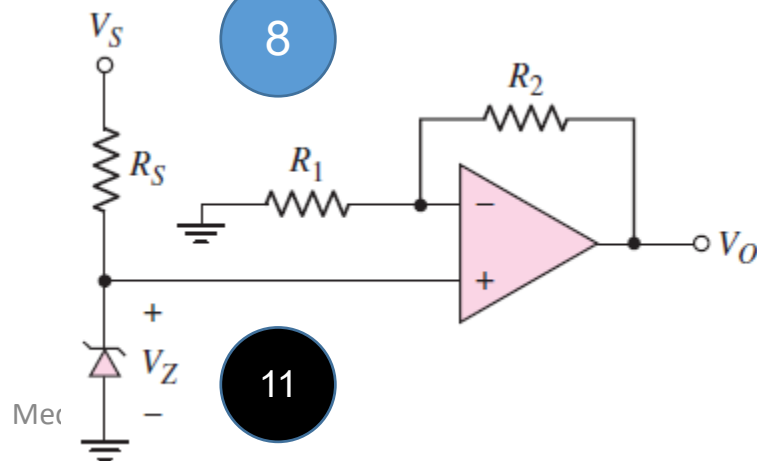

11

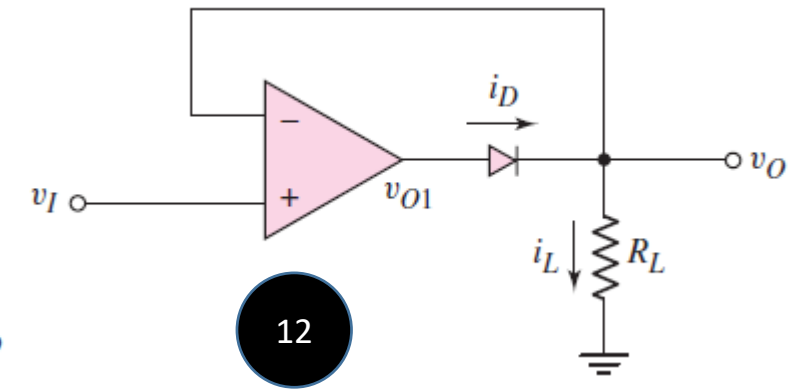

12

9.2 Inverting Amplifier

- One of the most widely used op-amp circuits is the **inverting amplifier**.
- Figure 9.8 shows the **closed-loop configuration** of this circuit.
- **Note**, we must **keep in mind** that:
 - The op-amp is **biased with DC voltages** as an active device.

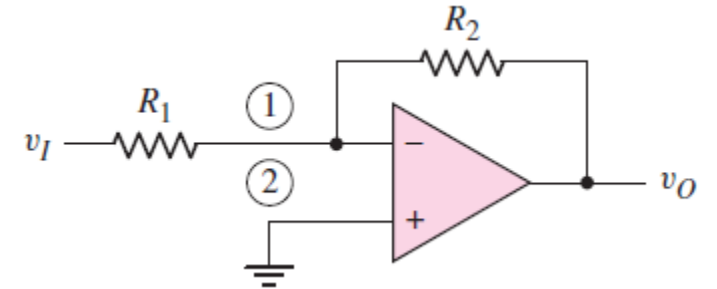


Figure 9.8

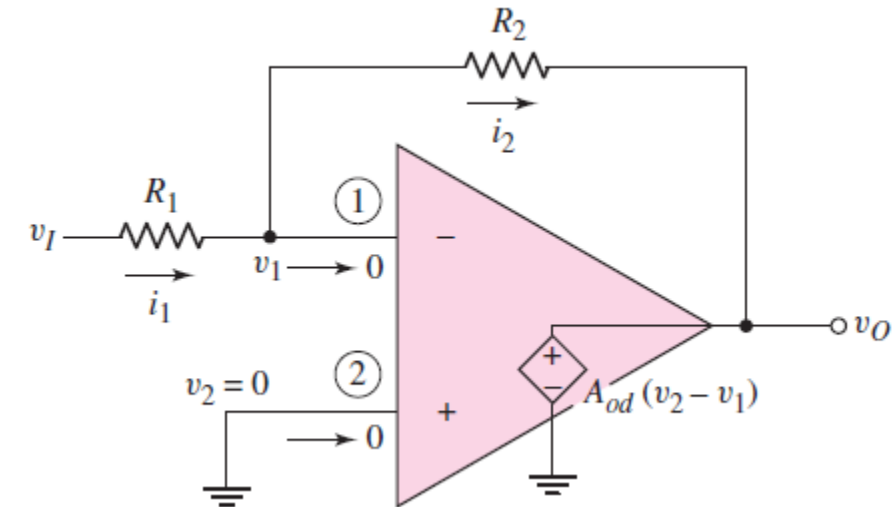


Figure 9.9

9.2.1 Basic Amplifier-Inverting Amplifier

- We **analyze** the circuit in Figure 9.8 by considering the ideal equivalent circuit shown in Figure 9.9.
- The **closed-loop voltage gain**, or simply the **voltage gain**, is defined as:

$$A_v = \frac{v_O}{v_I}$$

- We stated that if the open-loop gain A_{od} is very large, then the two inputs v_1 and v_2 must be nearly equal.
- **Proof:**

$$v_O = A_{od}(v_2 - v_1)$$

$$\frac{v_O}{A_{od}} = (v_2 - v_1)$$

$$A_{od} \rightarrow \infty$$

$$v_2 = v_1$$

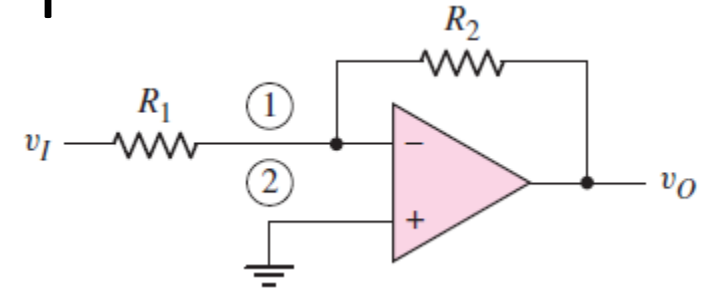


Figure 9.8

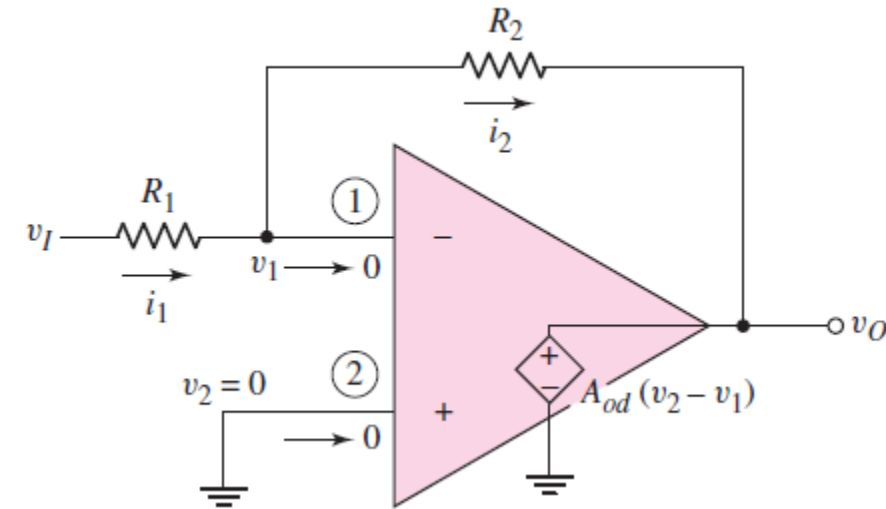


Figure 9.9

9.2.1 Basic Amplifier-Inverting Amplifier

$$v_2 = v_1$$

- Since v_2 is at ground potential, voltage v_1 must also be approximately *zero* volts.
 - Having v_1 be essentially **at ground potential** **does not imply** that terminal (1) is grounded.
 - Terminal (1) is said to be at **virtual ground**:
 - It is essentially *zero* volts, but **it does not provide a current path to ground** → **means** that terminal 1 is essentially at *zero* volts, but is not connected to ground potential.

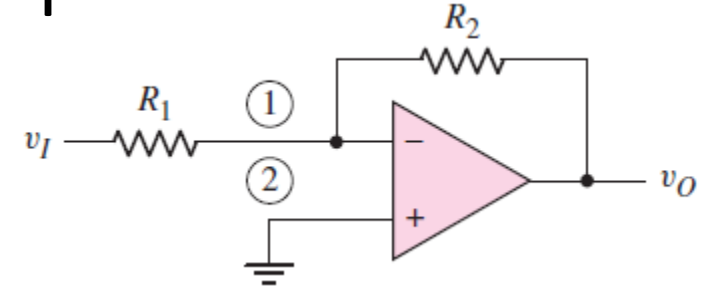


Figure 9.8

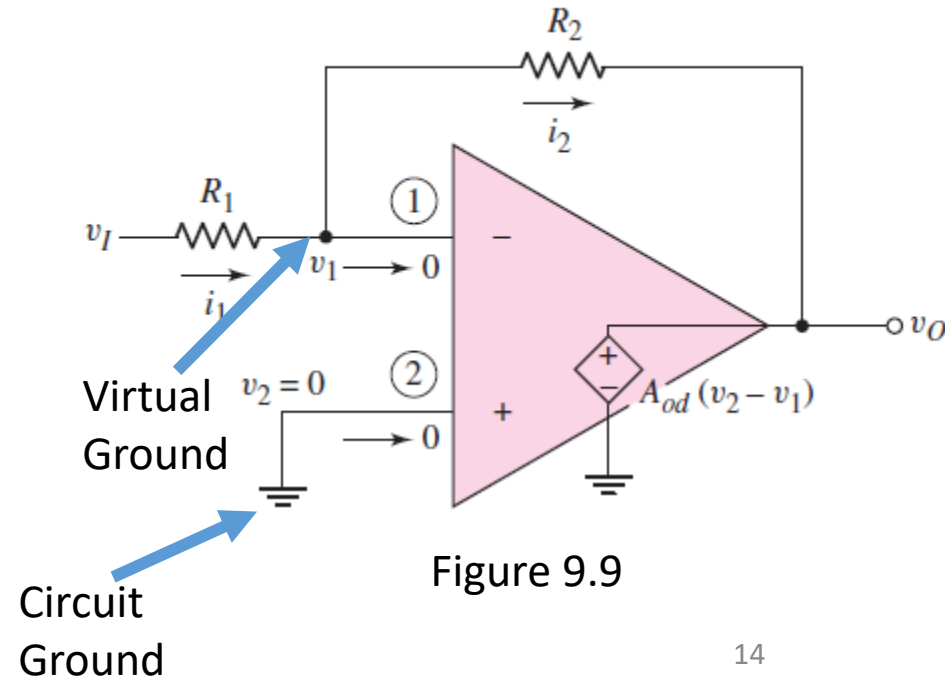


Figure 9.9

9.2.1 Basic Amplifier-Inverting Amplifier

- From Figure 9.9, we can write:

$$i_1 = \frac{v_I - v_1}{R_1} = \frac{v_I - 0}{R_1} = \frac{v_I}{R_1}$$

- Since the current into the op-amp is assumed to be *zero*, current i_1 must flow through resistor R_2 to the output terminal, which means that $i_2 = i_1$.

- The output voltage is given by (KVL):

$$v_O = v_1 - i_2 R_2 = 0 - \left(\frac{v_I}{R_1} \right) R_2$$

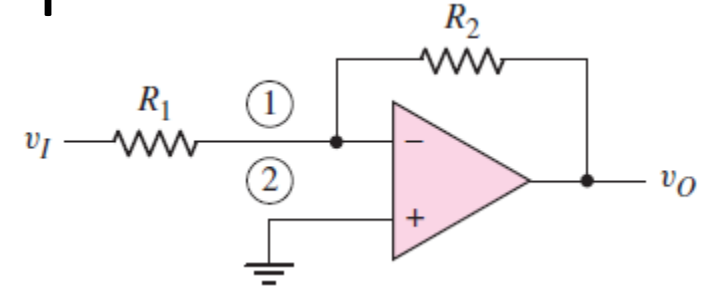


Figure 9.8

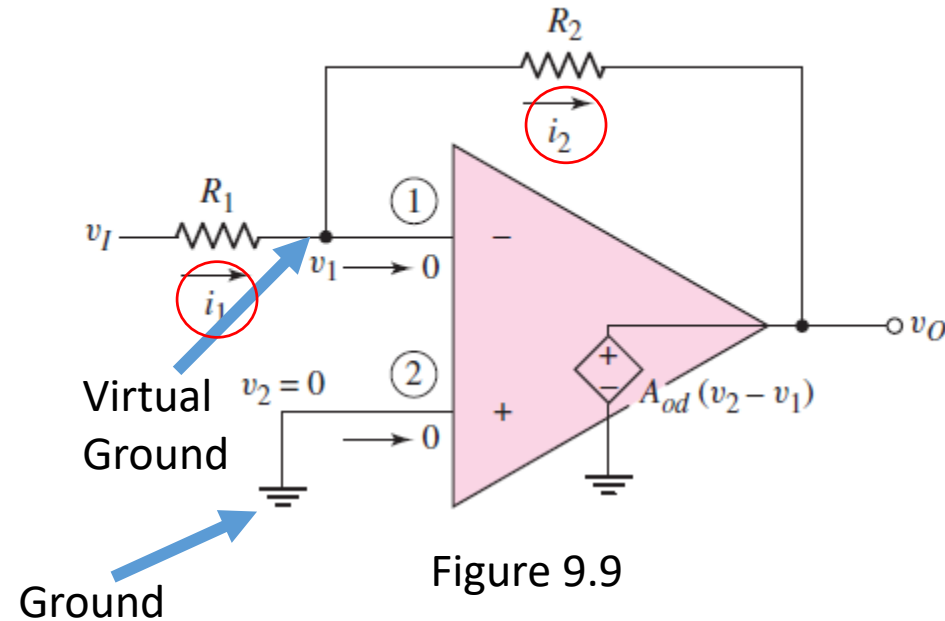


Figure 9.9

9.2.1 Basic Amplifier-Inverting Amplifier

$$v_O = v_1 - i_2 R_2 = 0 - \left(\frac{v_I}{R_1} \right) R_2$$

- Therefore, the closed-loop voltage gain is:

$$A_v = \frac{v_O}{v_I} = -\frac{R_2}{R_1}$$

- For the ideal op-amp, the closed-loop voltage gain A_v is a **function of the ratio of two resistors**;
 - **Note:** It is not a function of the transistor parameters within the op-amp circuit.
- The minus sign **implies** a phase reversal \rightarrow **180° phase shift.**

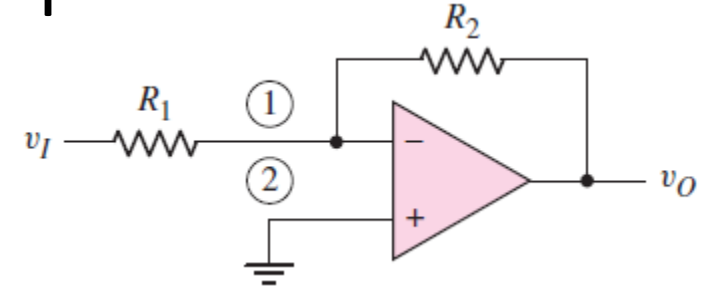


Figure 9.8

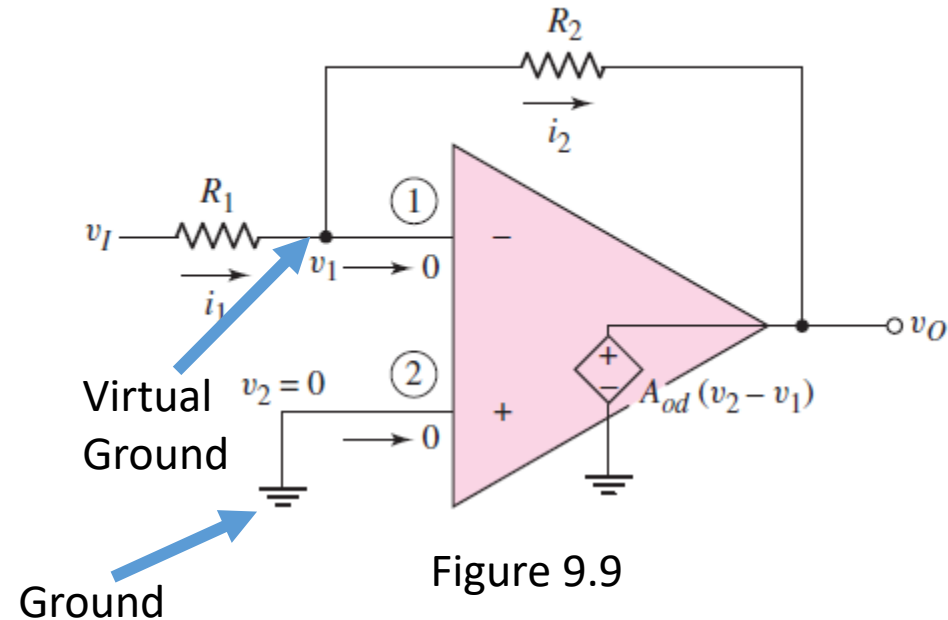


Figure 9.9

9.2.1 Basic Amplifier-Inverting Amplifier

- We can also determine the **input resistance** seen by the voltage source v_I .
- Because of the virtual ground, we have:

$$i_1 = \frac{v_I - v_1}{R_1} = \frac{v_I - 0}{R_1} = \frac{v_I}{R_1}$$

$$i_1 = \frac{v_I}{R_1}$$

- The **input resistance** is then defined as:

$$R_i = \frac{v_I}{i_1} = R_1$$

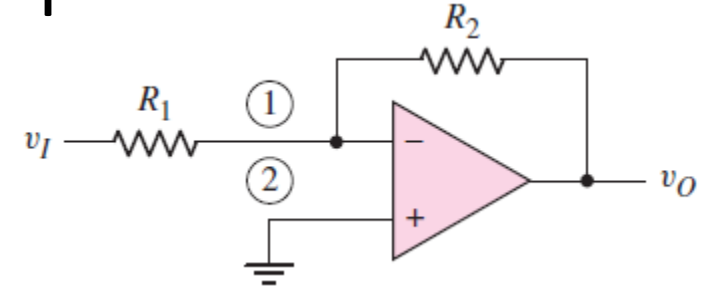


Figure 9.8

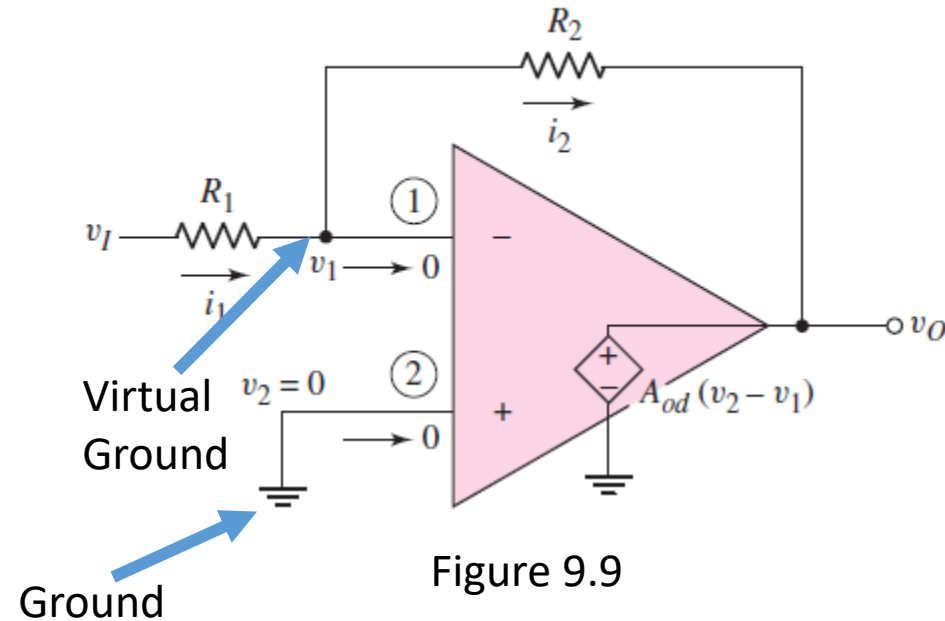


Figure 9.9

9.2.1 Basic Amplifier-Inverting Amplifier

$$R_i = \frac{v_I}{i_1} = R_1$$

- This shows that:
 - The input resistance seen by the source is a **function of R_1 only**, and is a result of the “virtual ground” concept.
- Figure 9.10 summarizes our analysis of the inverting amplifier circuit.
- Since there are **no coupling capacitors** in the op-amp circuit, the input and output voltages, as well as the currents in the resistors, can be DC signals.
 - The inverting op-amp can then **amplify DC voltages**.

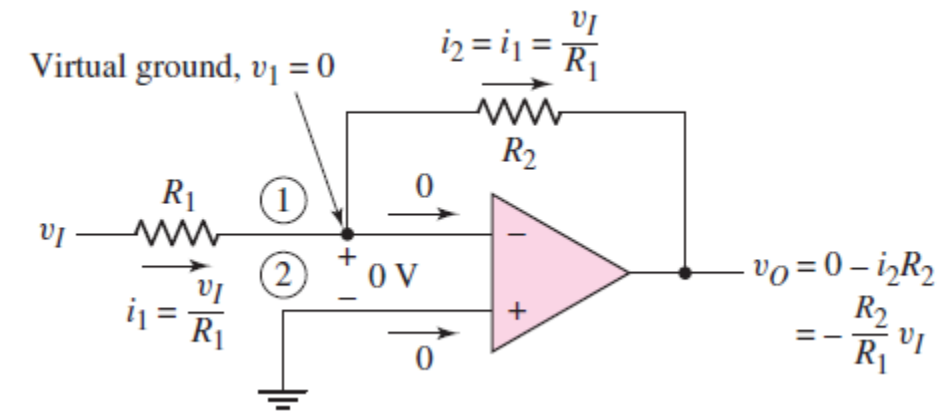


Figure 9.10

DESIGN EXAMPLE 9.1

- **Specifications:** The circuit configuration to be designed is shown in Figure 9.10.
- **Design** the circuit such that the voltage gain is $A_v = -5$.
- **Assume** the op-amp is driven by an ideal sinusoidal source:

$$v_s = 0.1\sin\omega t \text{ (V)}$$

that can supply a maximum current of $5\mu\text{A}$.

- Note: **Assume** that frequency ω is low so that any **frequency effects** can be neglected.
- **Design Pointer:** If the **sinusoidal input signal source has a nonzero output resistance**, the op-amp must be redesigned to provide the specified voltage gain.

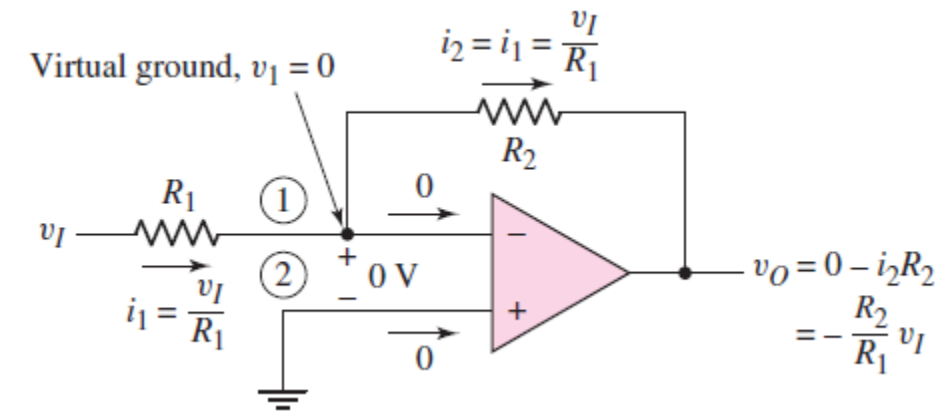


Figure 9.10

DESIGN EXAMPLE 9.1

- **Initial Solution:** The input current is given by:

$$i_1 = \frac{v_I}{R_1} = \frac{v_s}{R_1}$$

- If $i_1(\text{max}) = 5 \mu\text{A}$, then we can write:

$$R_1 = \frac{v_s(\text{max})}{i_1(\text{max})} = \frac{0.1}{5 \times 10^{-6}} \Rightarrow 20 \text{ k}\Omega$$

- The closed-loop gain is given by:

$$A_v = -\frac{R_2}{R_1} = -5$$

- We then have:

$$R_2 = 5R_1 = 5(20\text{k}\Omega) = 100 \text{ k}\Omega$$

- **Comment:** The output resistance of the signal source R_s must be included in the design of the op-amp to provide a specified voltage gain.

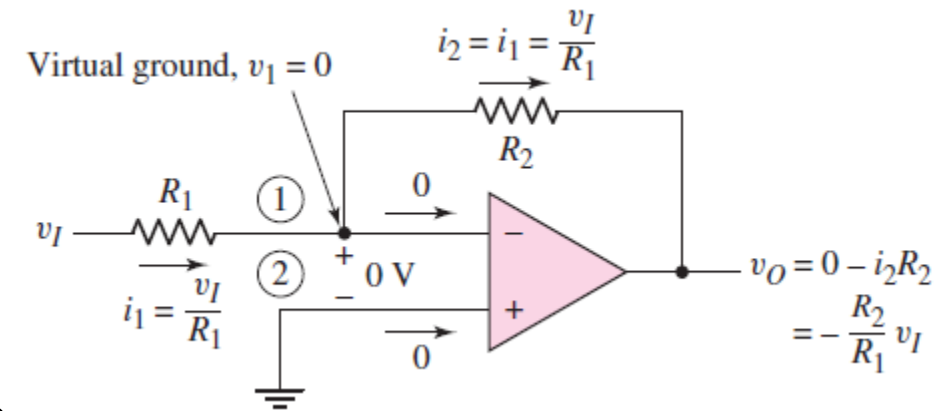


Figure 9.10

Problem-Solving Technique: Ideal Op-Amp Circuits

1. If the **noninverting terminal** of the op-amp **is at ground potential**, then the inverting terminal v_1 is at virtual ground.
 - Sum currents at this node, assuming *zero* current enters the op-amp itself.
2. If the **noninverting terminal** of the op-amp **is not at ground potential**, then the inverting terminal voltage v_1 is equal to that at the noninverting terminal voltage v_2 .
 - Sum currents at the inverting terminal node, assuming *zero* current enters the op-amp itself.
3. For the ideal op-amp circuit, the output voltage is determined from either step 1 or step 2 above and is **independent of any load connected to the output terminal**.

9.2.2 Amplifier with a T-Network

- Assume that an inverting amplifier is to be designed having a closed-loop voltage gain of $A_v = -100$ and an input resistance of $R_i = R_1 = 50\text{ k}\Omega$.
- The feedback resistor R_2 would then have to be $R_2 = |A_v| \cdot R_1 = 100 \cdot 50\text{ k}\Omega = 5\text{ M}\Omega$!
 - However this resistance value is too large for most practical circuits.
 - **Practically, for IC design, always avoid resistance values larger than $50\text{ k}\Omega$!**
- **What is the solution?**

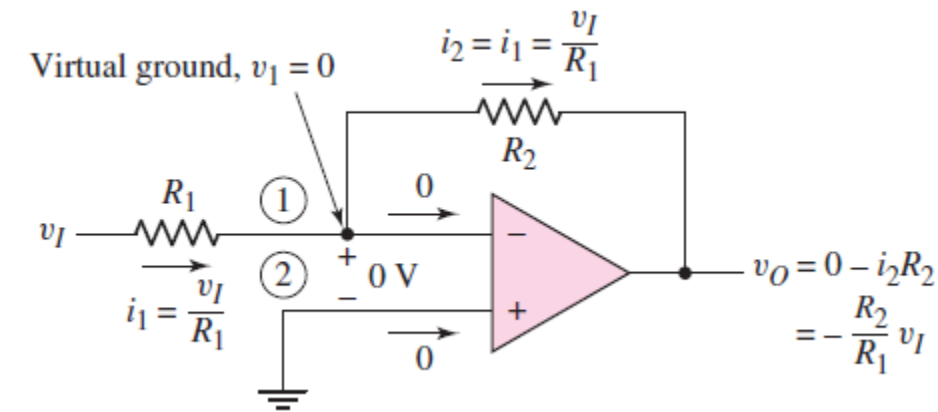


Figure 9.10

9.2.2 Amplifier with a T-Network

- Consider the op-amp circuit shown in Figure 9.12 with a T-network in the feedback loop.
- The analysis of this circuit is similar to that of the inverting op-amp circuit of Figure 9.10. At the input, we have:

$$i_1 = \frac{v_I}{R_1} = i_2$$

- We can also write that:

$$v_X = 0 - i_2 R_2 = -v_I \left(\frac{R_2}{R_1} \right)$$

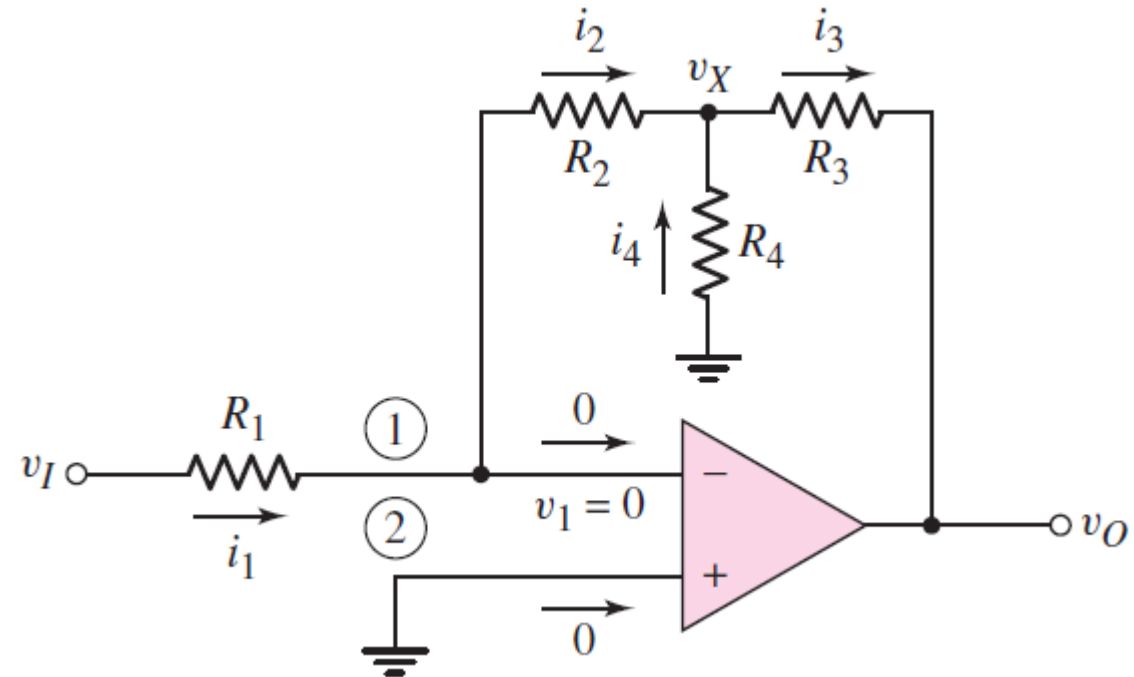


Figure 9.12

9.2.2 Amplifier with a T-Network

$$v_X = 0 - i_2 R_2 = -v_I \left(\frac{R_2}{R_1} \right)$$

- If we sum the currents at the node v_X , we have (i.e. KCL at node v_X):

$$i_2 + i_4 = i_3$$

- which can be written:

$$-\frac{v_X}{R_2} - \frac{v_X}{R_4} = \frac{v_X - v_O}{R_3}$$

$$v_X \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_3} \right) = \frac{v_O}{R_3}$$

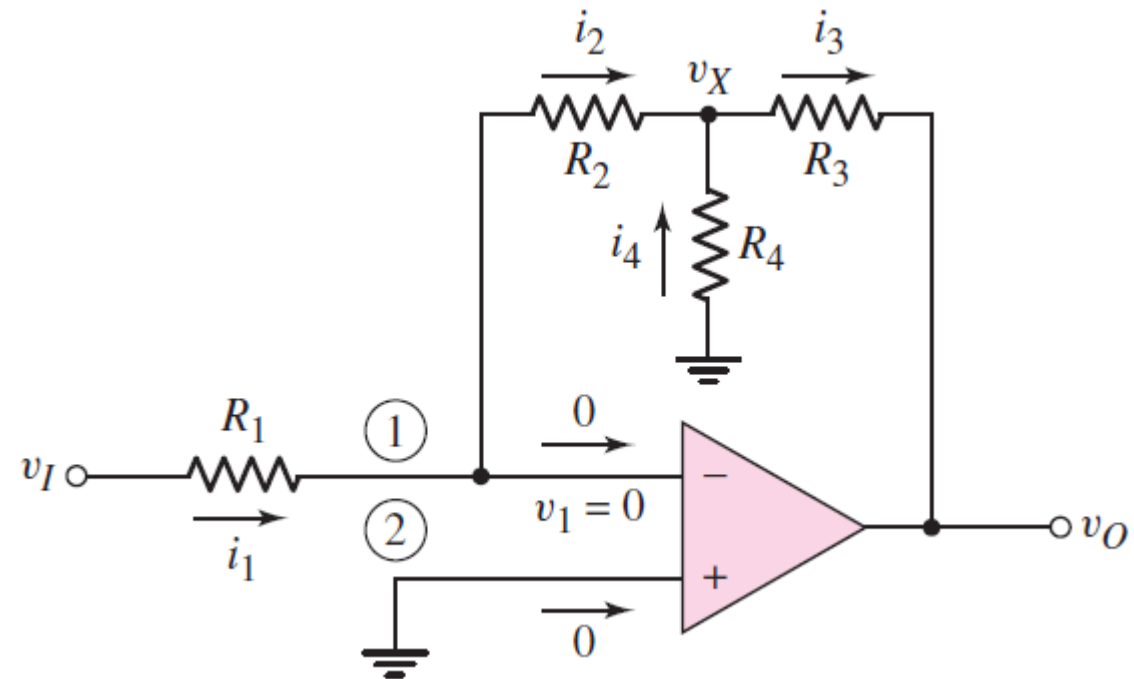


Figure 9.12

9.2.2 Amplifier with a T-Network

$$v_X = 0 - i_2 R_2 = -v_I \left(\frac{R_2}{R_1} \right)$$

$$v_X \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_3} \right) = \frac{v_O}{R_3}$$

- Substituting the expression for v_X we obtain:

$$-v_I \left(\frac{R_2}{R_1} \right) \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_3} \right) = \frac{v_O}{R_3}$$

- The closed-loop voltage gain is therefore:

$$A_v = \frac{v_O}{v_I} = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2} \right)$$

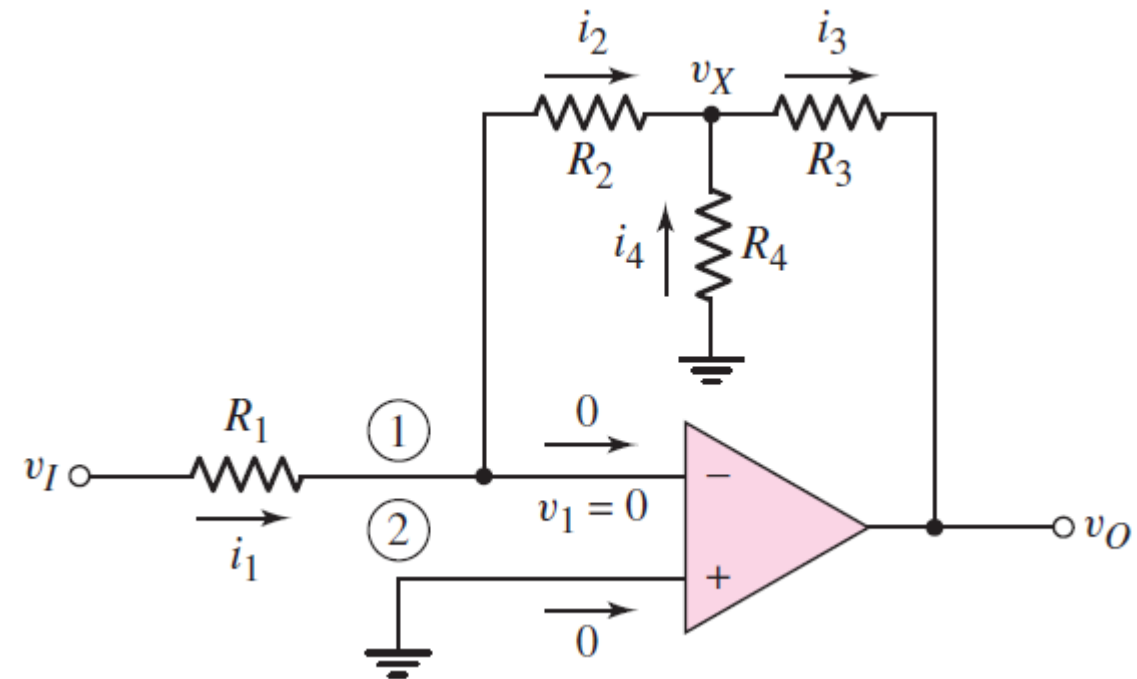


Figure 9.12

DESIGN EXAMPLE 9.2

- **Objective:** An op-amp with a T-network is to be designed as a **microphone preamplifier**.
- **Specifications:** The circuit configuration to be designed is shown in Figure 9.12.
- The **maximum microphone output voltage** is 12mV (*rms*) and the microphone has an output resistance of $R_S = 1\text{k}\Omega$.
- The op-amp circuit is to be designed such that the **maximum output voltage** is 1.2V (*rms*).
- The **input amplifier resistance** should be fairly large, but all resistance values should be less than $500\text{k}\Omega$.

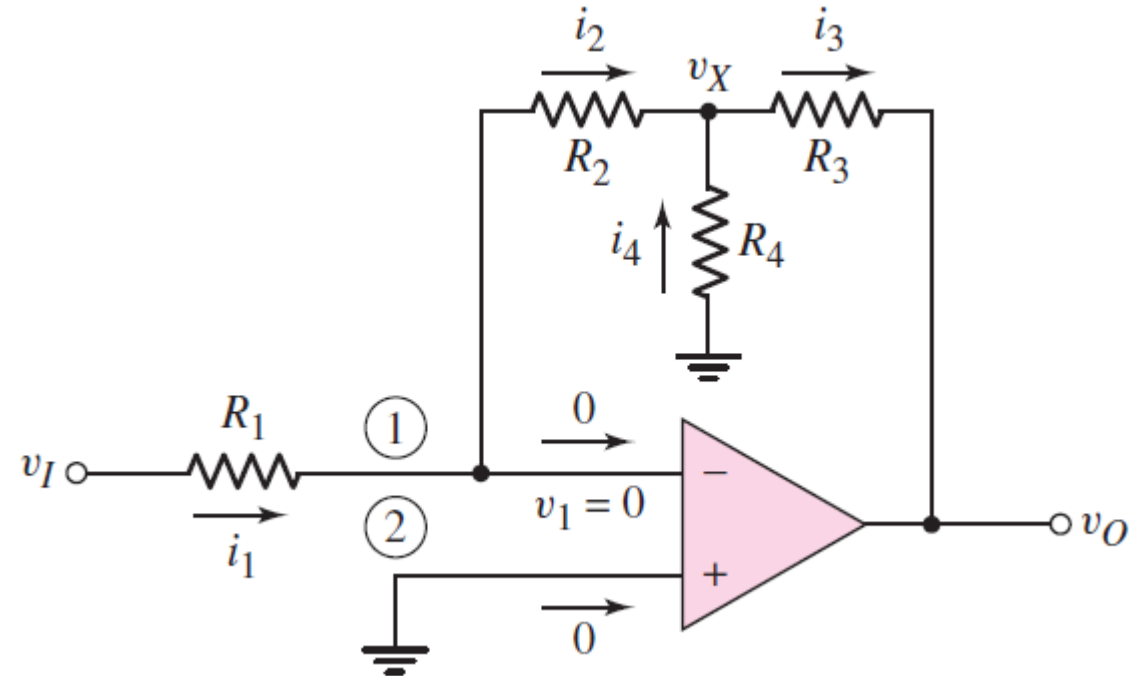


Figure 9.12

DESIGN EXAMPLE 9.2

- **Choices:**
 - The final design should use **standard resistor values**.
 - Standard resistors with **tolerances** of ± 2 percent are to be considered.
- **Solution:** We need a voltage gain of $|A_v| = 1.2/0.012 = 100$
- The gain Equation for such a circuit can be written in the form:

$$A_v = \frac{v_O}{v_I} = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} + \frac{R_3}{R_2} \right)$$

$$= -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} \right) - \frac{R_3}{R_1}$$

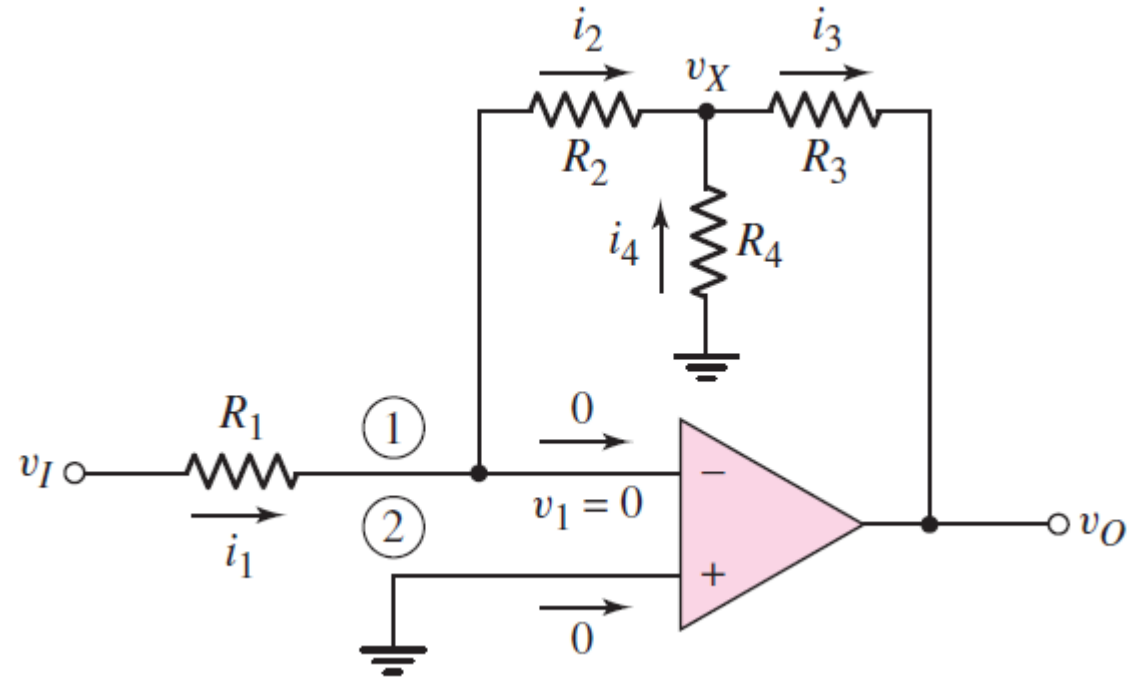


Figure 9.12

DESIGN EXAMPLE 9.2

$$A_v = \frac{v_O}{v_I} = -\frac{R_2}{R_1} \left(1 + \frac{R_3}{R_4} \right) - \frac{R_3}{R_1}$$

- As a designer, we arbitrarily choose:

$$R_2/R_1 = R_3/R_1 = 8$$

- Then:

$$-100 = -8 \left(1 + \frac{R_3}{R_4} \right) - 8$$

- Which yields:

$$\frac{R_3}{R_4} = 10.5$$

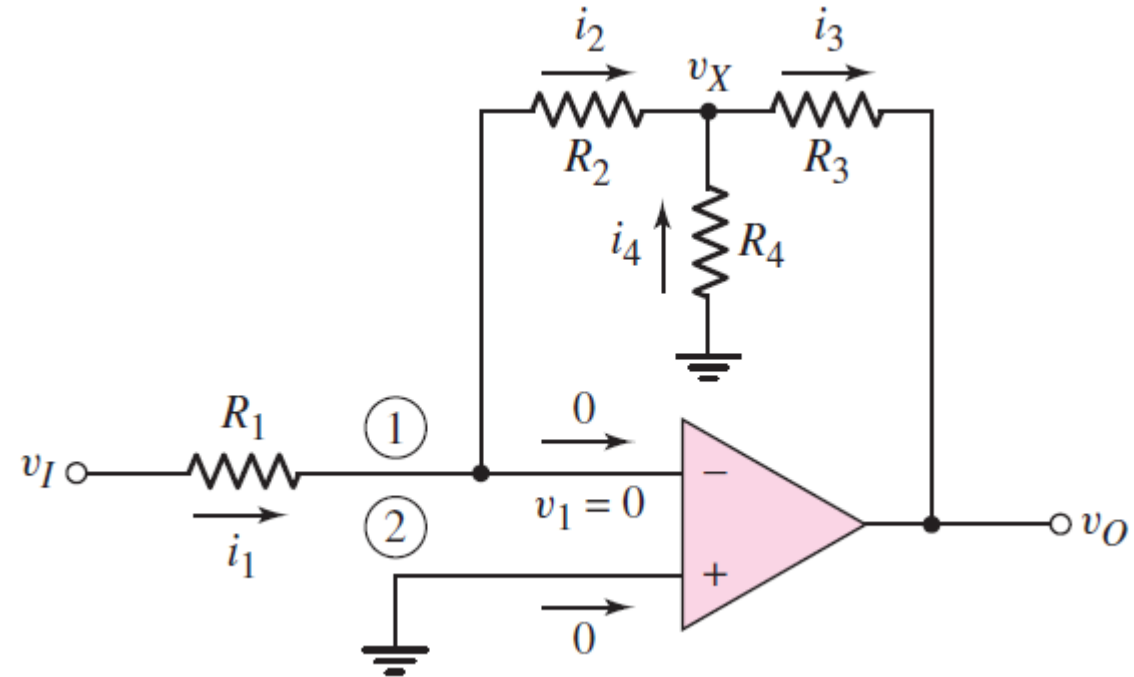


Figure 9.12

DESIGN EXAMPLE 9.2

- The effective R'_1 must include the R_S resistance of the microphone.
- If we set $R_1 = 49\text{ k}\Omega$ so that $R'_1 = 50\text{ k}\Omega$, then:

$$R_2 = R_3 = 400\text{ k}\Omega$$

and:

$$R_4 = \frac{R_3}{10.5} = \frac{400\text{ k}}{10.5} = 38.1\text{ k}\Omega$$

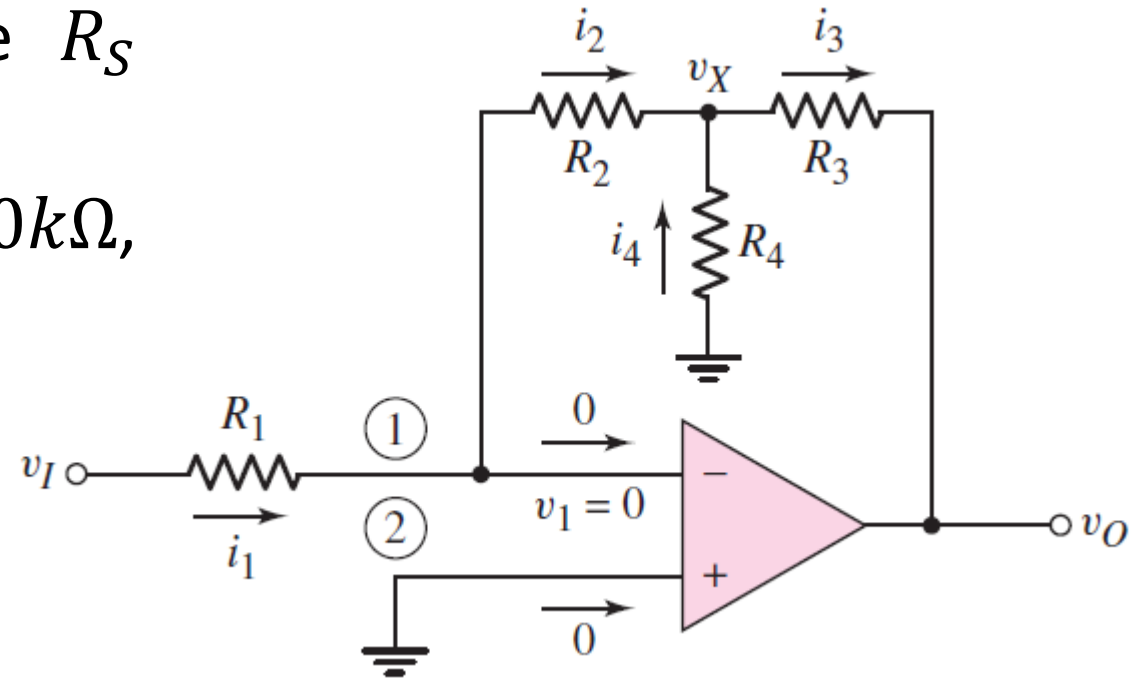


Figure 9.12

Choosing Standard Resistor Values (Appendix C)

| Resistor | Calculated Value | Nearest Standard Value |
|----------|------------------|------------------------|
| R_1 | 49 k Ω | 51 k Ω |
| R_2 | 400 k Ω | 390 k Ω |
| R_3 | 400 k Ω | 390 k Ω |
| R_4 | 38.1 k Ω | ? |

Table C.1

Standard resistance values ($\times 10^n$)

| | | | | |
|-----------|-----------|-----------|-----------|------------|
| 10 | 16 | 27 | 43 | 68 |
| 11 | 18 | 30 | 47 | 75 |
| 12 | 20 | 33 | 51 | 82 |
| 13 | 22 | 36 | 56 | 91 |
| 15 | 24 | 39 | 62 | 100 |

DESIGN EXAMPLE 9.2

- **Design Pointer:** If we need to use standard resistance values in our design, then, using Appendix C, we can choose $R_1 = 51 \text{ k}\Omega$ so that $R'_1 = 52 \text{ k}\Omega$, and we can choose $R_2 = R_3 = 390 \text{ k}\Omega$. Then, after recalculating for R_4 we have:

$$\begin{aligned} -100 &= -\frac{R_2}{R'_1} \left(1 + \frac{R_3}{R_4} \right) - \frac{R_3}{R'_1} \\ -100 &= -\frac{390k}{52k} \left(1 + \frac{390k}{R_4} \right) - \frac{390k}{52k} \end{aligned}$$

- which yields $R_4 = 34.4 \text{ k}\Omega$. We may use a standard resistor of $R_4 = 33 \text{ k}\Omega$.
- This resistance value then produces a voltage gain of:

$$A_v = -\frac{R_2}{R'_1} \left(1 + \frac{R_3}{R_4} \right) - \frac{R_3}{R'_1} = -\frac{390}{52} \left(1 + \frac{390}{33} \right) - \frac{390}{52} = -103.6$$

DESIGN EXAMPLE 9.2

- **Trade-offs:** If we **consider** ± 2 percent tolerances in the standard resistor values, the A_v can be written as:

$$A_v = -\frac{R_2(1 \pm 0.02)}{1k + R_1(1 \pm 0.02)} \left[1 + \frac{R_3(1 \pm 0.02)}{R_4(1 \pm 0.02)} \right] - \frac{R_3(1 \pm 0.02)}{1k + R_1(1 \pm 0.02)}$$
$$= -\frac{390k(1 \pm 0.02)}{1k + 51k(1 \pm 0.02)} \left[1 + \frac{390k(1 \pm 0.02)}{33k(1 \pm 0.02)} \right] - \frac{390k(1 \pm 0.02)}{1k + 51k(1 \pm 0.02)}$$

- Analyzing this equation, we find:
 - The **maximum** magnitude as $|A_v|_{\max} = 111.6$ or $+7.72$ percent, and
 - The **minimum** magnitude as $|A_v|_{\min} = 96.3$ or -7.05 percent.

DESIGN EXAMPLE 9.2

- **Comments:**
 1. All resistor values are less than $500\text{ k}\Omega$.
 2. The resistance ratios in the voltage gain expression are approximately equal.
- As with most design problems, **there is no unique solution**.
- We must **keep in mind** that:
 - Because of resistor value tolerances, the **actual gain** of the amplifier will have a **range of values**.
- The amplifier with a T-network **allows** us to **obtain** a large gain using reasonably sized resistors.

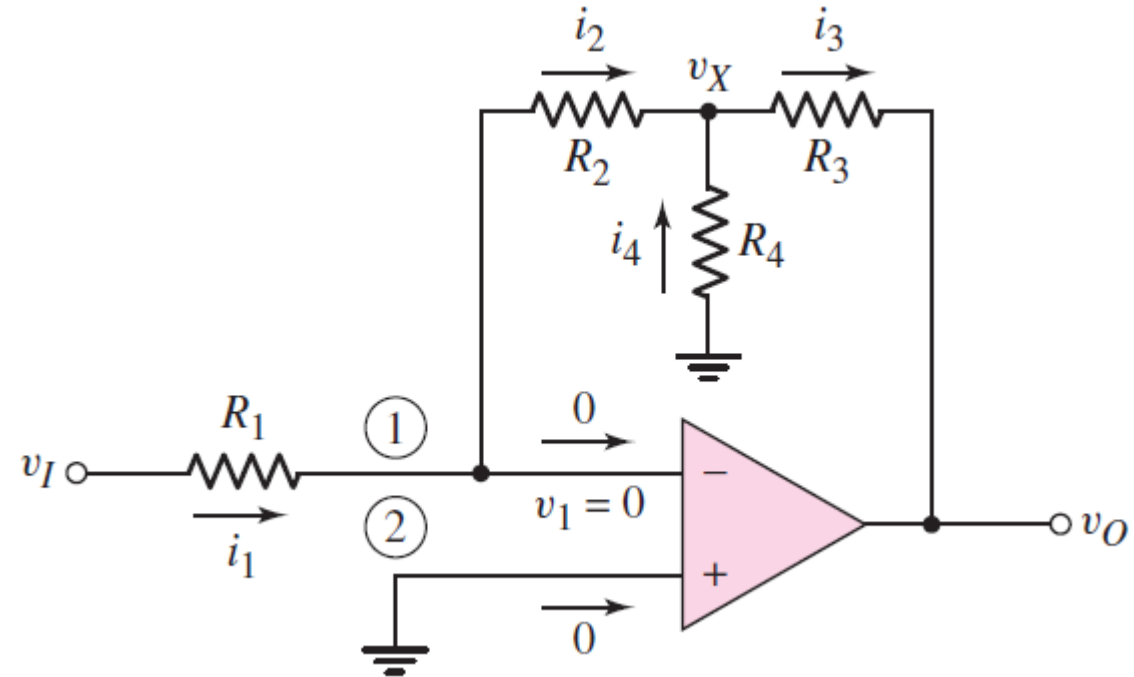


Figure 9.12

9.4.1 Basic Amplifier-Noninverting Amplifier

- Figure 9.15 shows the basic **noninverting amplifier**.
- The input signal v_I is **applied** directly to the noninverting terminal, while:
 - One side of resistor R_1 is connected to the inverting terminal and
 - The other side is at ground.

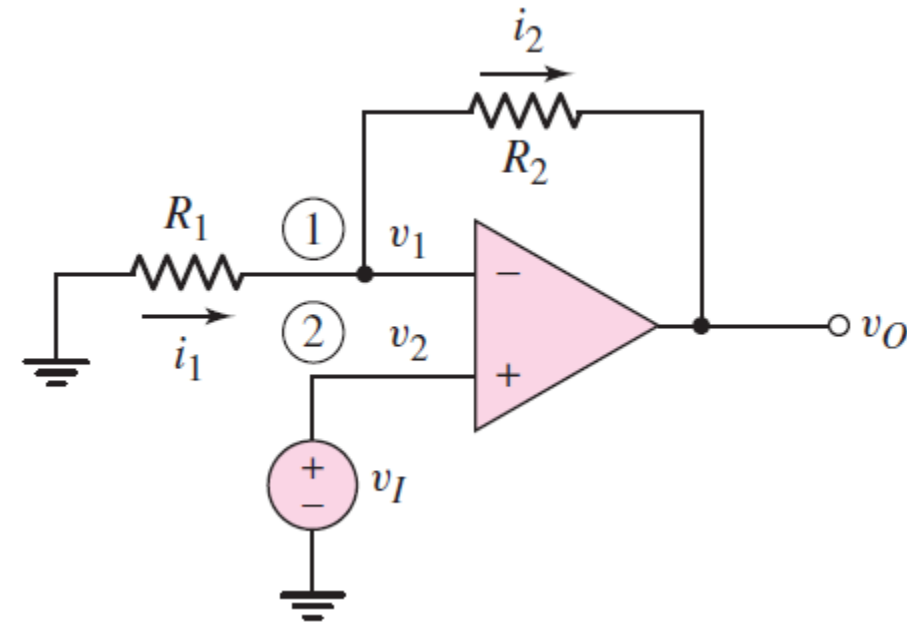


Figure 9.15

9.4.1 Basic Amplifier-Noninverting Amplifier

- The analysis of the noninverting amplifier is essentially the same as for the inverting amplifier.
- We **assume** that no current enters the input terminals.
- Since $v_1 = v_2$, then $v_1 = v_I$, and current i_1 is given by:

$$i_1 = -\frac{v_1}{R_1} = -\frac{v_I}{R_1}$$

- Current i_2 is given by:

$$i_2 = \frac{v_1 - v_O}{R_2} = \frac{v_2 - v_O}{R_2} = \frac{v_I - v_O}{R_2}$$

- As before, $i_1 = i_2$, so that:

$$-\frac{v_I}{R_1} = \frac{v_I - v_O}{R_2}$$

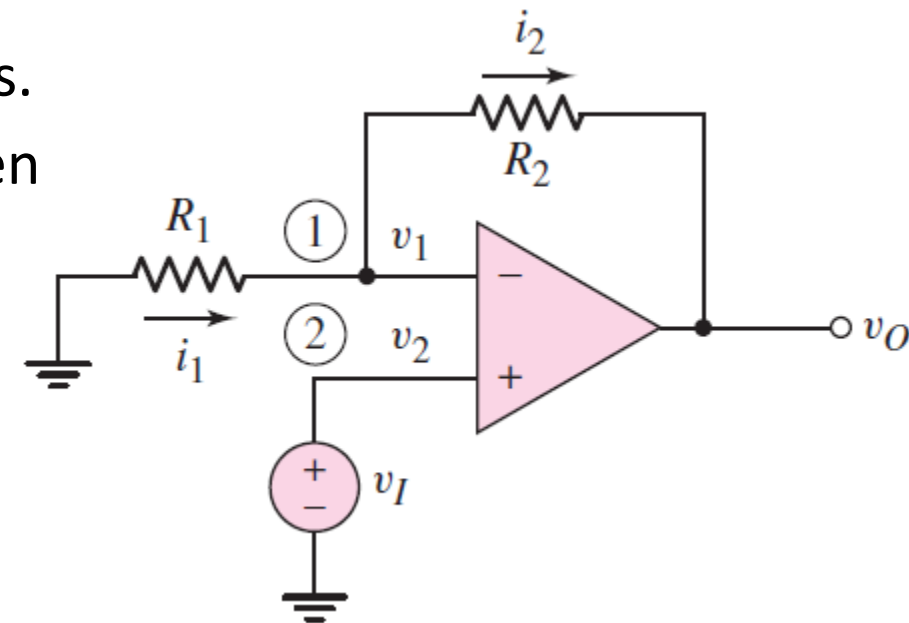


Figure 9.15

9.4.1 Basic Amplifier-Noninverting Amplifier

$$-\frac{v_I}{R_1} = \frac{v_I - v_O}{R_2}$$

- Solving for the closed-loop voltage gain, we find:

$$A_v = \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$

- From this equation, note that:

1. The output is **in phase** with the input, as expected (i.e. it is a non-inverting amplifier).
2. The gain is always greater than unity (i.e $A_v > 1$).

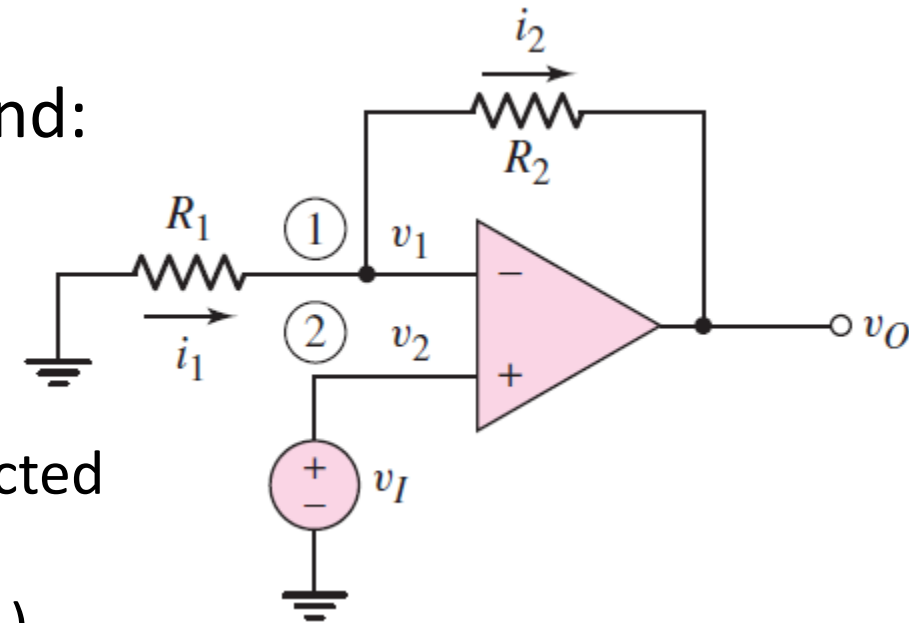


Figure 9.15

9.4.1 Basic Amplifier-Noninverting Amplifier

- The input signal v_I is connected **directly** to the noninverting terminal; therefore, since the input current is essentially *zero*, the **input impedance** R_i seen by the source is very large, **ideally infinite**.
- The ideal equivalent circuit of the noninverting op-amp is shown in Figure 9.16.

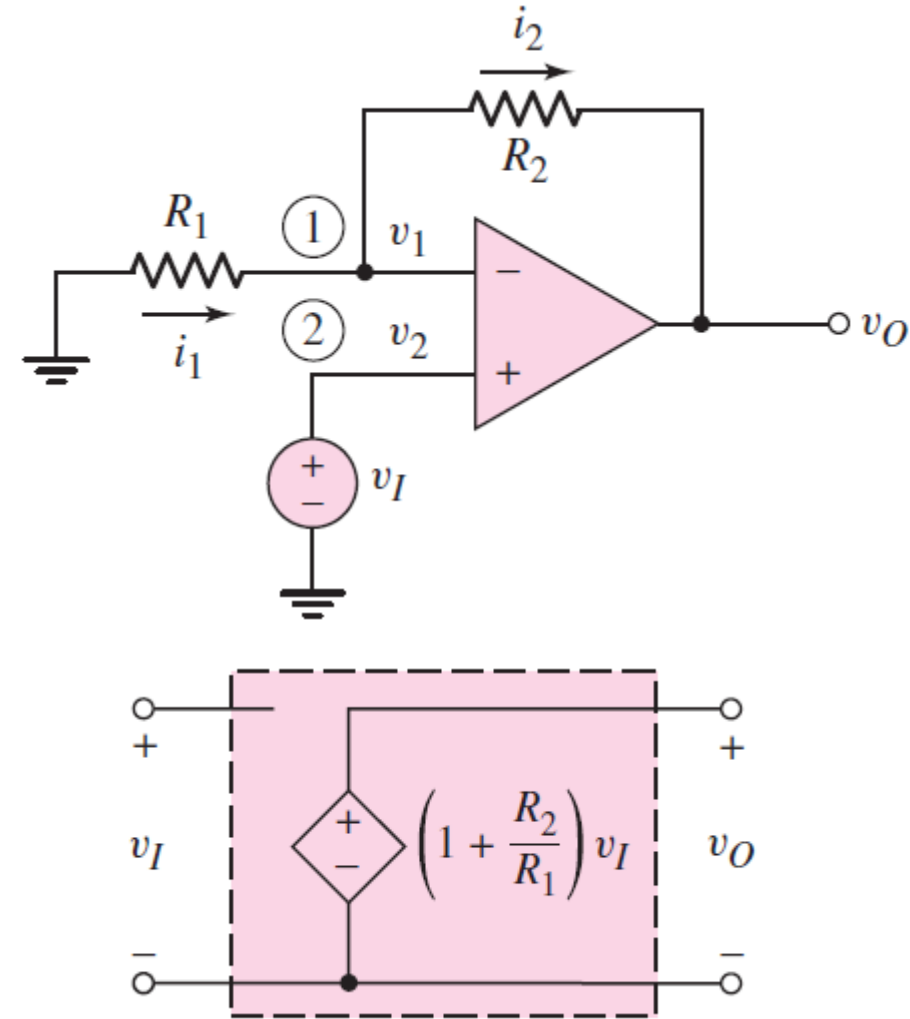




Figure 9.16

9.4.2 Voltage Follower-Noninverting Amplifier

$$A_v = \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$

- An interesting property of the noninverting op-amp occurs when:
 - $R_1 = \infty$, an open circuit, and
 - $R_2 = 0$, a short circuit.
- The closed-loop gain then becomes:

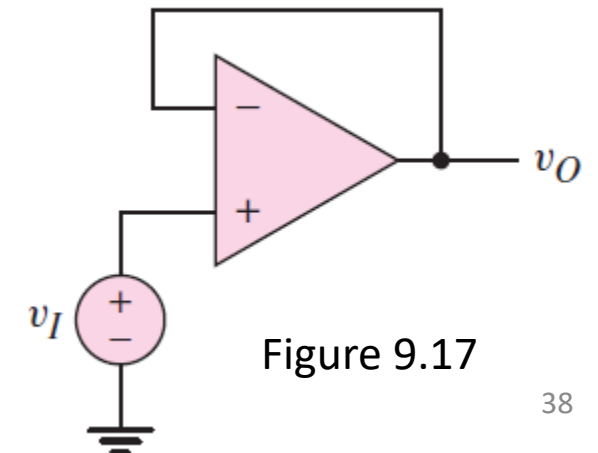
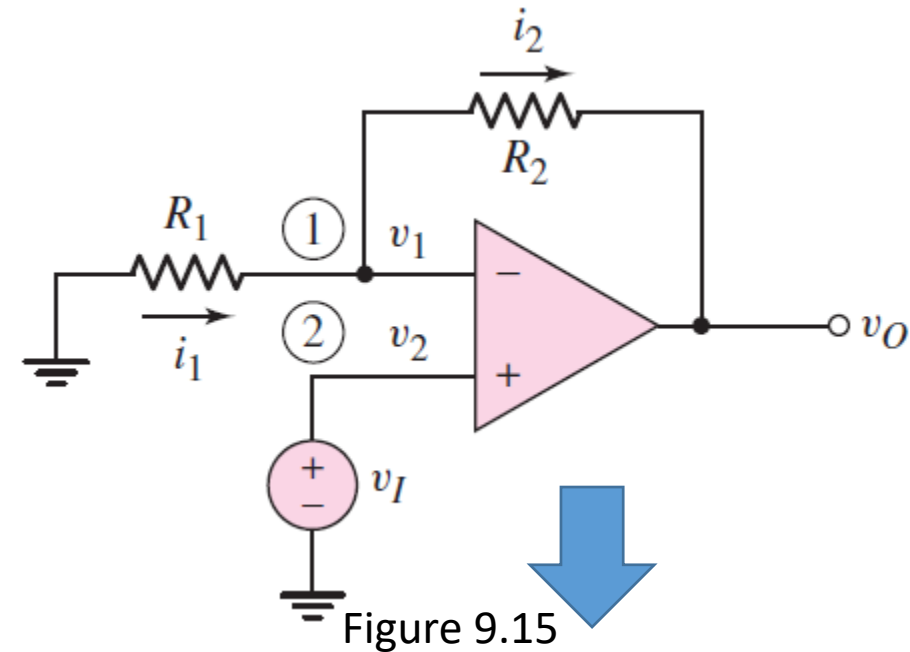
$$A_v = \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1} = 1 + \frac{0}{\infty} = 1$$



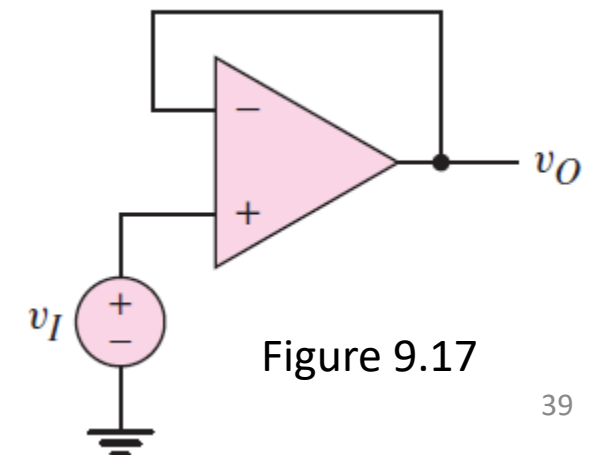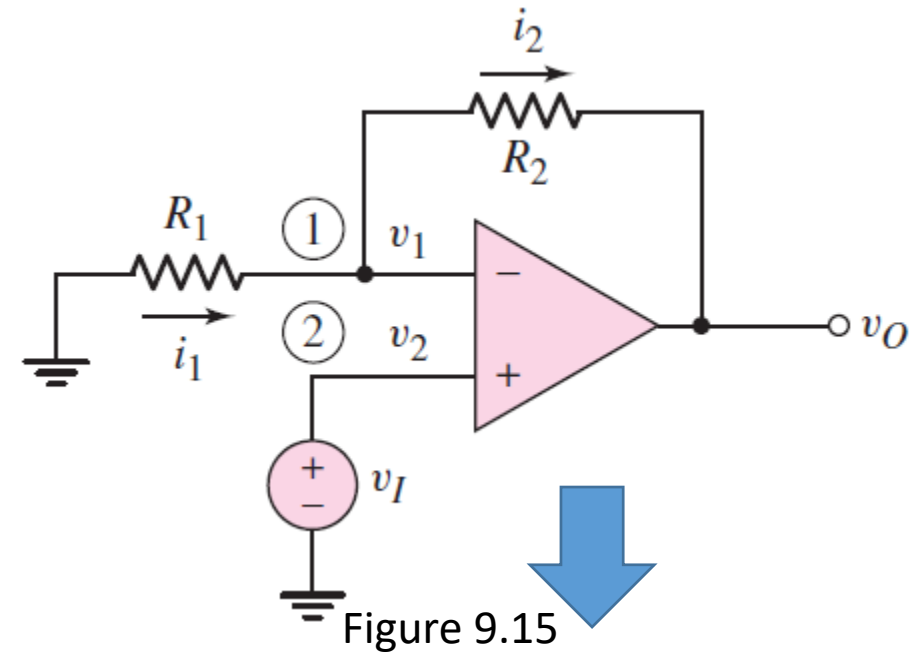9.4.2 Voltage Follower-Noninverting Amplifier



$$A_v = \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1} = 1 + \frac{0}{\infty} = 1$$
$$v_O = v_I$$

- Since the output voltage follows the input, this op-amp circuit is called a **voltage follower**.
- The closed-loop gain is independent of resistor R_2 (except when $R_2 = \infty$),
- So we can set $R_2 = 0\Omega$ to **create** a short circuit.



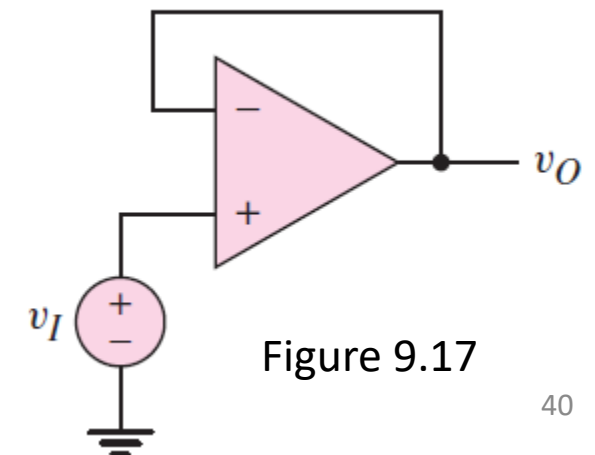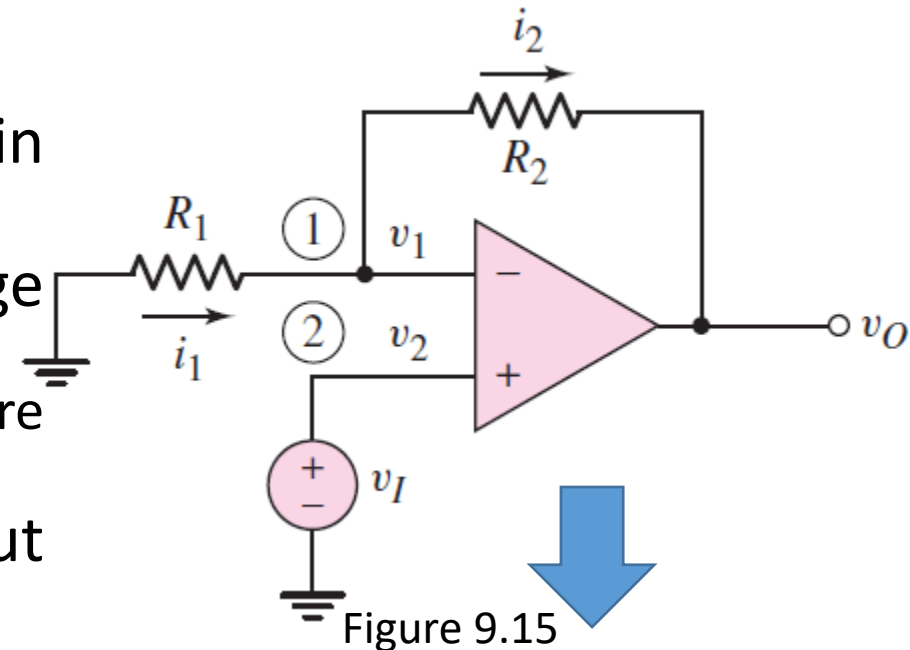9.4.2 Voltage Follower-Noninverting Amplifier

- The **voltage-follower op-amp** circuit is shown in Figure 9.17.
- It might seem that this circuit, with unity voltage gain, would be of little value.
 - However, other terms used for the voltage follower are **impedance transformer** or **buffer**.
- The input impedance $R_i \rightarrow \infty$, and the output impedance $R_o \rightarrow 0$.
- If, for example, the output impedance of a signal source is large, a **voltage follower inserted between the source and a load will prevent loading effects**.
 - It **will act** as a **buffer** between the source and the load.



9.4.2 Voltage Follower-Noninverting Amplifier

- Compare between the following two circuits!

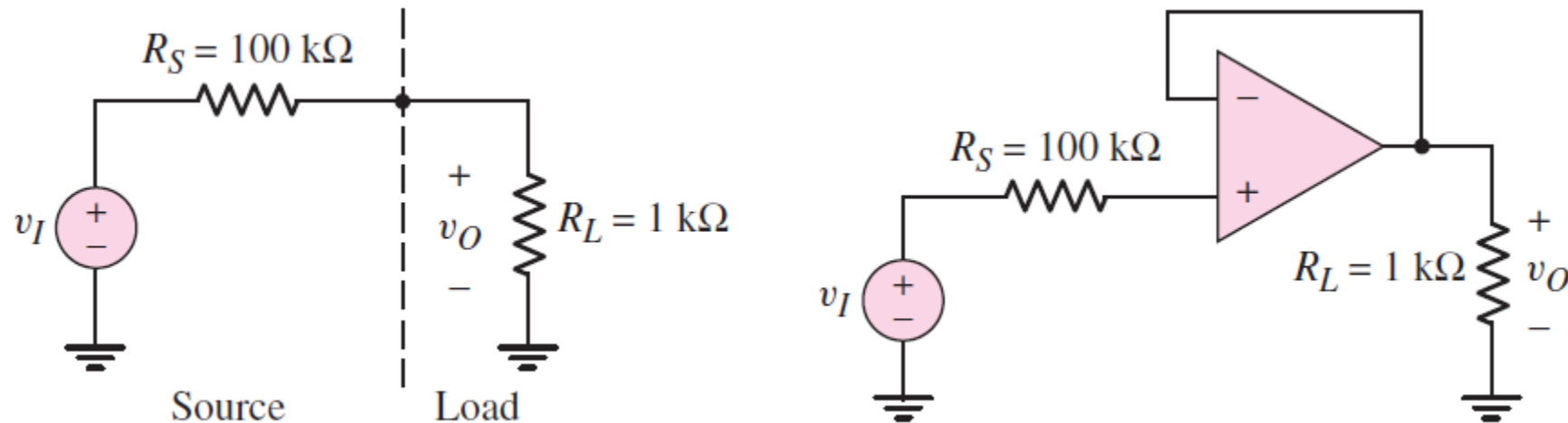


Figure 9.18