

L03

Operational Amplifiers Applications 2

Chapter 9

Ideal Operational Amplifiers and Op-Amp Circuits


Donald A. Neamen (2009). **Microelectronics**: Circuit Analysis and Design,
4th Edition, Mc-Graw-Hill

Prepared by: Dr. Hani Jamleh, *Electrical Engineering Department, The University of Jordan*


Op-Amp Applications

1. Inverting Amplifier
2. Amplifier with T-Network
3. Non-Inverting Amplifier
4. Voltage Follower (Buffer)
5. Summing Amplifier
6. Current to Voltage Converter


1

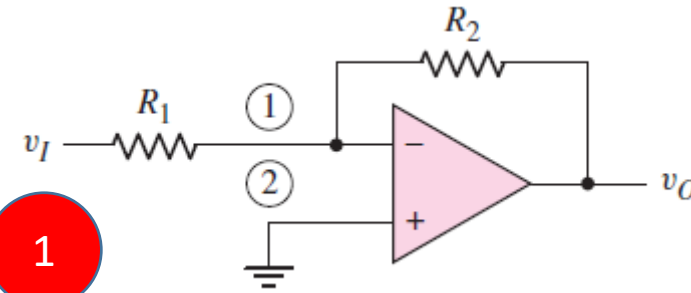


3

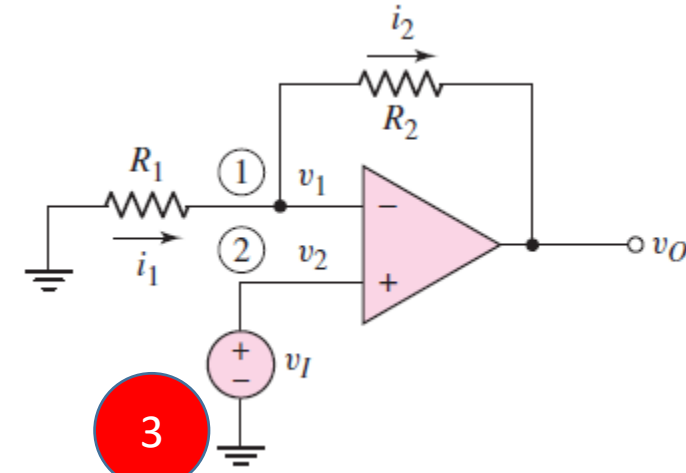


2

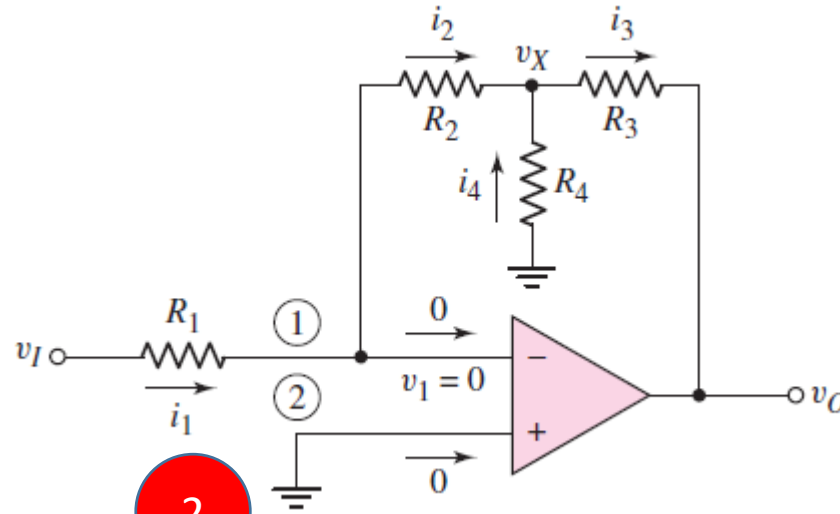


4

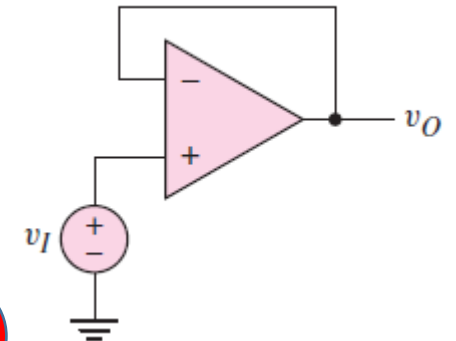

5

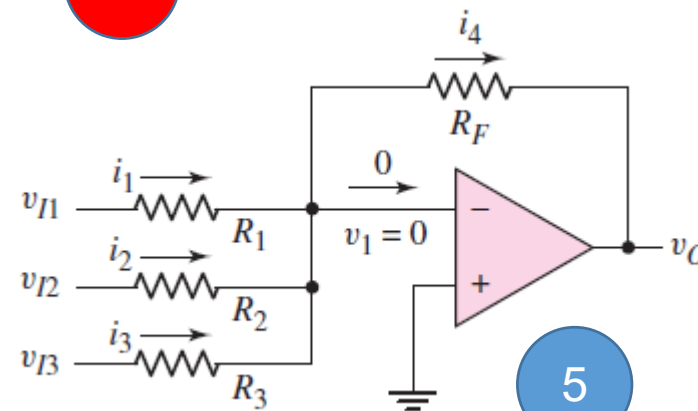

6

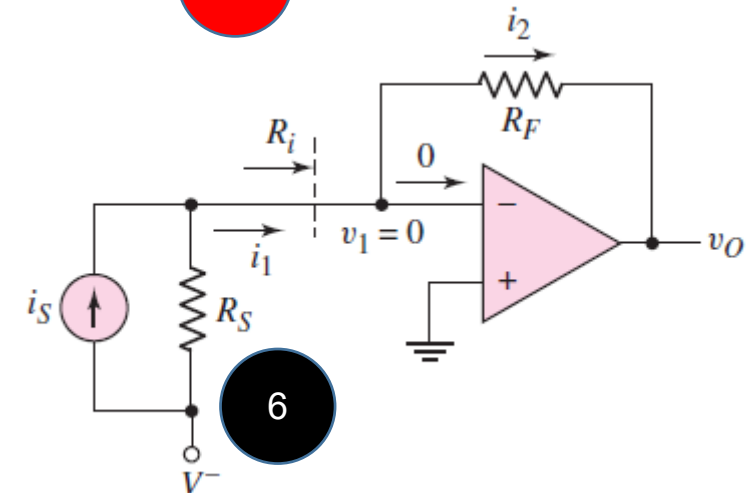

Op-Amp Applications

7. Difference Amplifier


8. Instrumentation Amplifier

9. Integrator


10. Differentiator

11. Reference Voltage Source Design


12. Precision Half-wave Rectifier

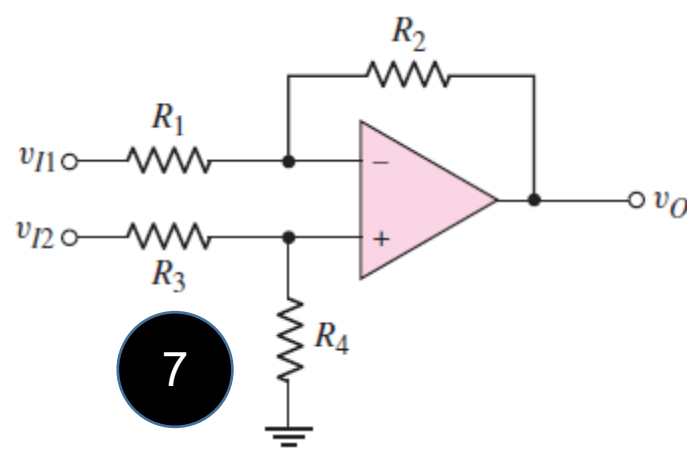


7

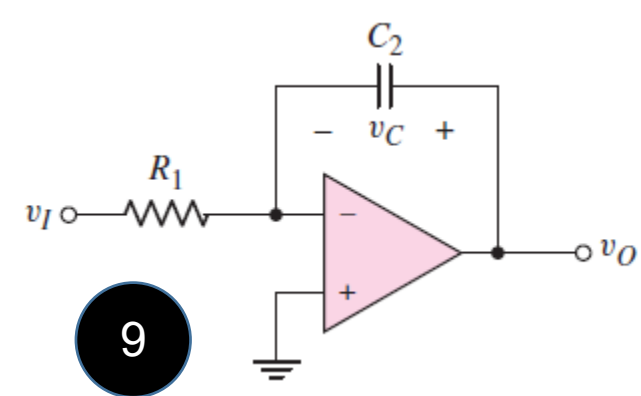


9

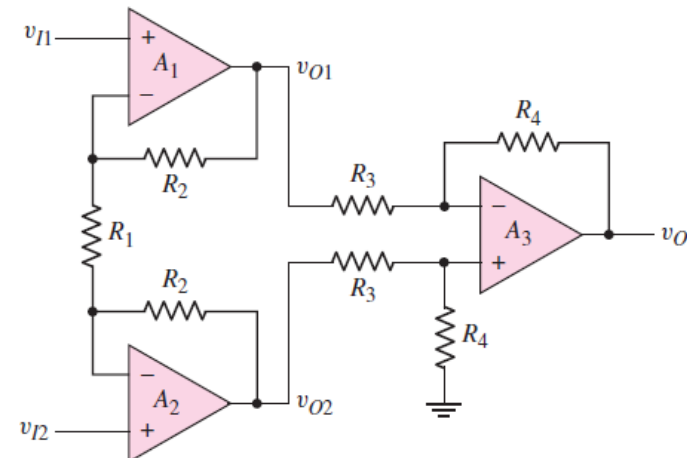


8

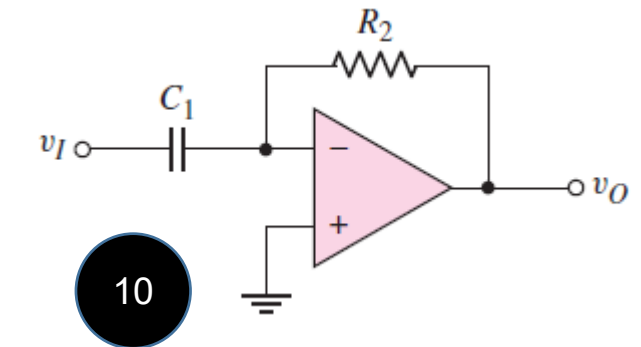

10

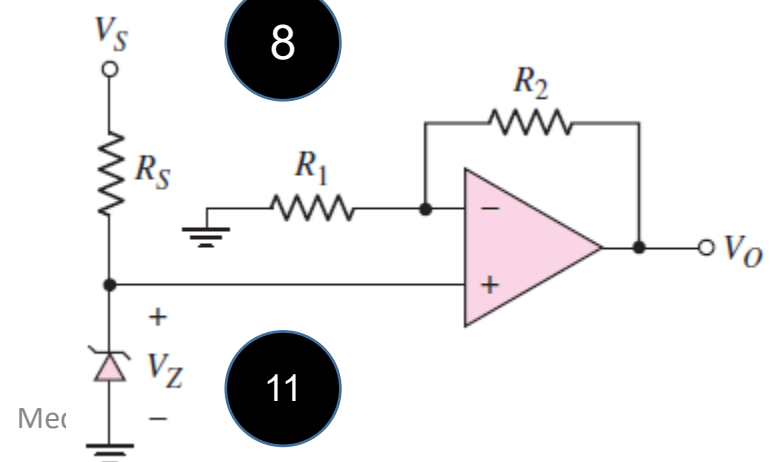

11

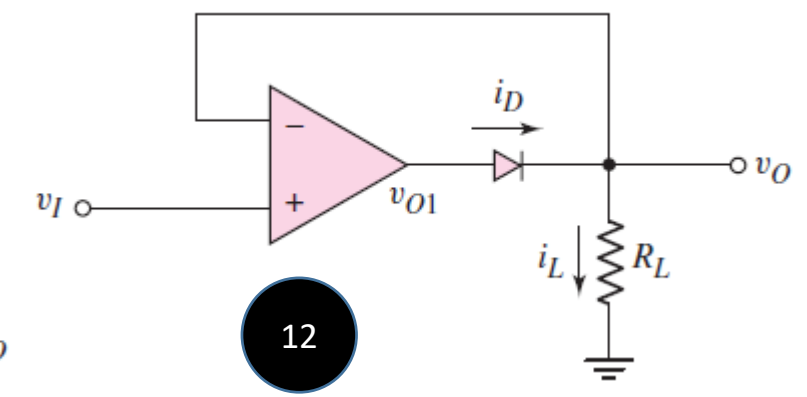

12

9.3 Summing Amplifier

- To analyze the op-amp circuit shown in Figure 9.14(a), we will use:
 1. The **superposition theorem** and
 2. The concept of **virtual ground**.
- Using the **superposition theorem**, we will:
 1. Determine the output voltage due to each input acting alone, then
 2. Algebraically sum these terms to determine the total output.

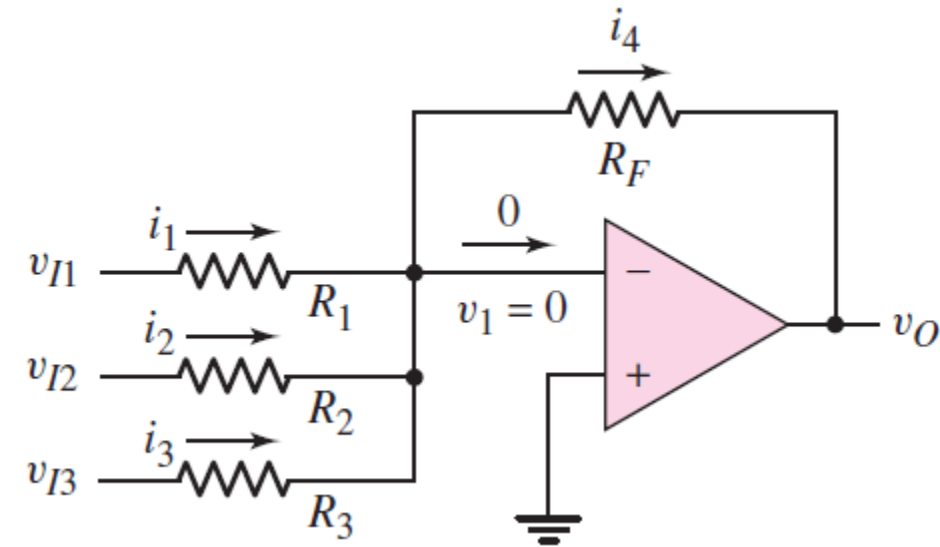


Figure 9.14(a)

9.3 Summing Amplifier

- If we set $v_{I2} = v_{I3} = 0$, the current i_1 is:

$$i_1 = \frac{v_{I1}}{R_1}$$

- Since $v_{I2} = v_{I3} = 0$ and the inverting terminal is at virtual ground, the currents i_2 and i_3 must both be zero.
 - Current i_1 does not flow through either R_2 or R_3 , but the entire current must flow through the feedback resistor R_F , as indicated in Figure 9.14(b).

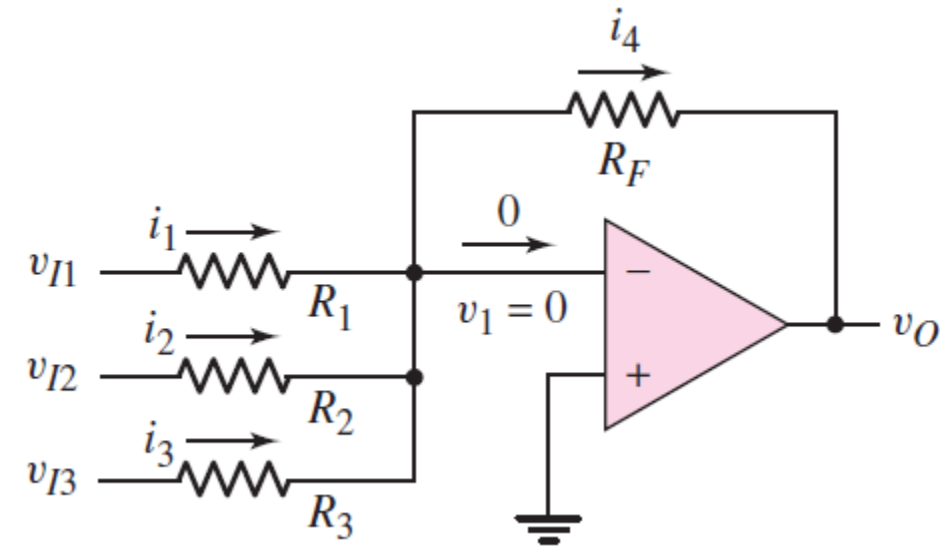


Figure 9.14(a)

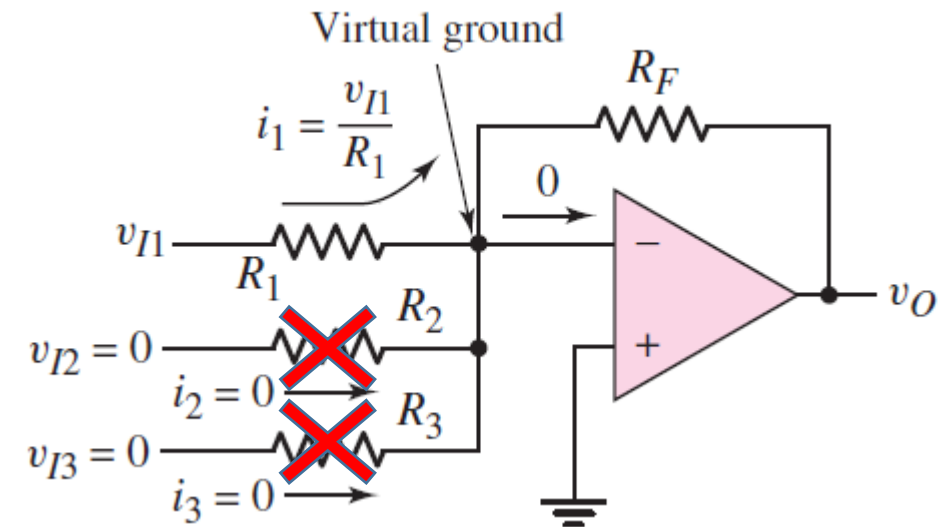


Figure 9.14(b)

9.3 Summing Amplifier

$$i_1 = \frac{v_{I1}}{R_1}$$

- The output voltage due to v_{I1} acting alone is:

$$v_O(v_{I1}) = -i_1 R_F = -\left(\frac{R_F}{R_1}\right) v_{I1}$$

- Similarly, the output voltages due to v_{I2} and v_{I3} acting individually are:

$$v_O(v_{I2}) = -i_2 R_F = -\left(\frac{R_F}{R_2}\right) v_{I2}$$

$$v_O(v_{I3}) = -i_3 R_F = -\left(\frac{R_F}{R_3}\right) v_{I3}$$

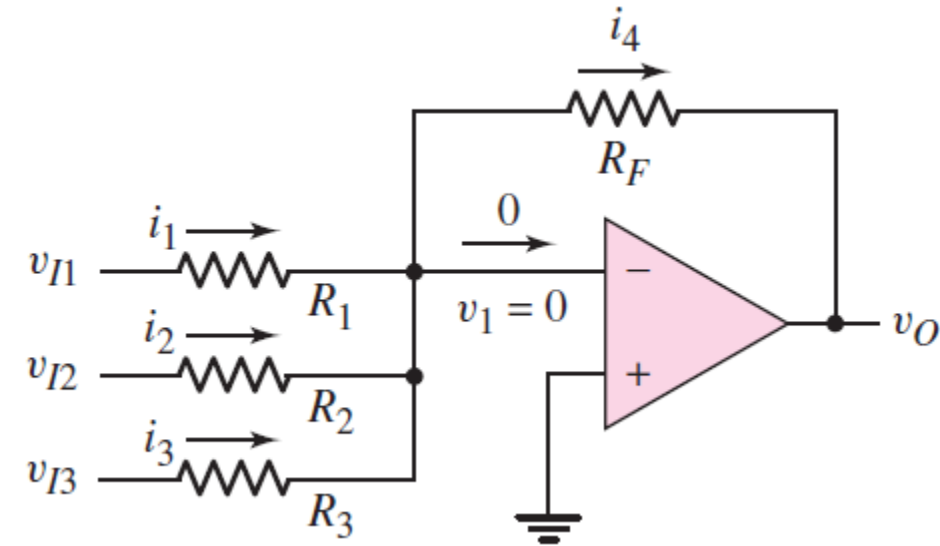


Figure 9.14(a)

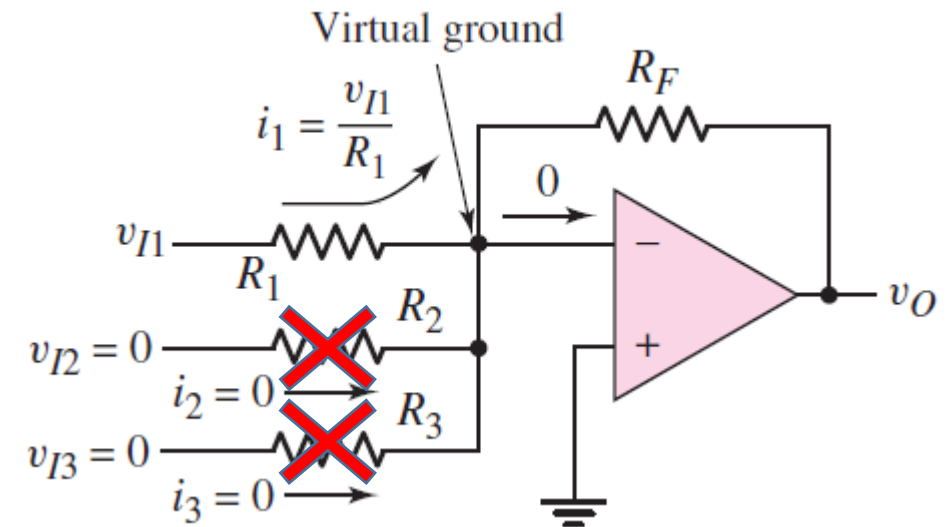


Figure 9.14(b)

9.3 Summing Amplifier

- Now we have:

$$v_O(v_{I_1}) = -i_1 R_F = -\left(\frac{R_F}{R_1}\right) v_{I_1}$$

$$v_O(v_{I_2}) = -i_2 R_F = -\left(\frac{R_F}{R_2}\right) v_{I_2}$$

$$v_O(v_{I_3}) = -i_3 R_F = -\left(\frac{R_F}{R_3}\right) v_{I_3}$$

- The **total output voltage** is the algebraic sum of the individual output voltages:

$$v_O = v_O(v_{I_1}) + v_O(v_{I_2}) + v_O(v_{I_3})$$
$$v_O = -\left(\frac{R_F}{R_1} v_{I_1} + \frac{R_F}{R_2} v_{I_2} + \frac{R_F}{R_3} v_{I_3}\right)$$

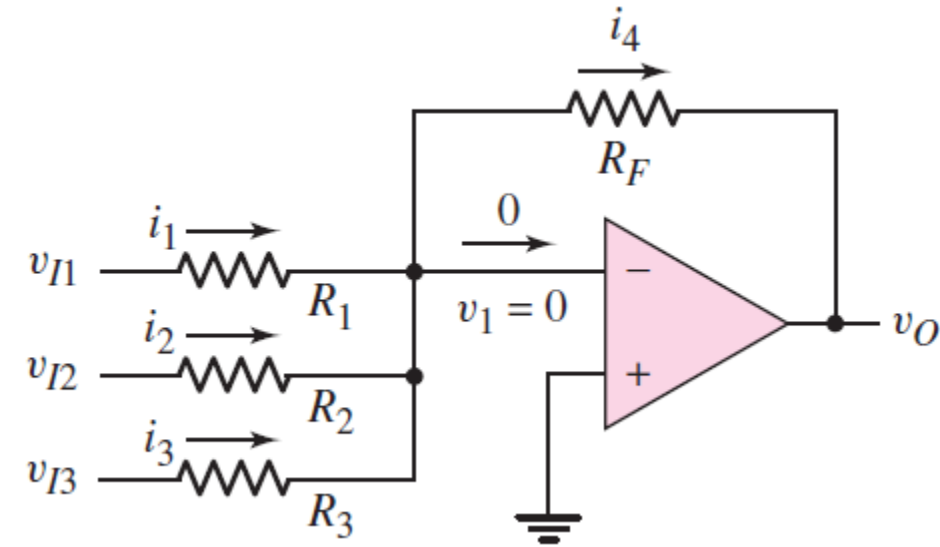


Figure 9.14(a)

9.3 Summing Amplifier

$$v_O = - \left(\frac{R_F}{R_1} v_{I1} + \frac{R_F}{R_2} v_{I2} + \frac{R_F}{R_3} v_{I3} \right)$$

- The output voltage is the sum of the three input voltages, with different **weighting factors**.
- This circuit is therefore called the **inverting summing amplifier**.
- The number of input terminals and input resistors can be changed to add more or fewer voltages.
- A special case occurs when the three input resistances are equal. When $R_1 = R_2 = R_3 \equiv R$, then

$$v_O = - \frac{R_F}{R_1} (v_{I1} + v_{I2} + v_{I3})$$

- This means that the output voltage is the sum of the input voltages, with a **single amplification factor**.

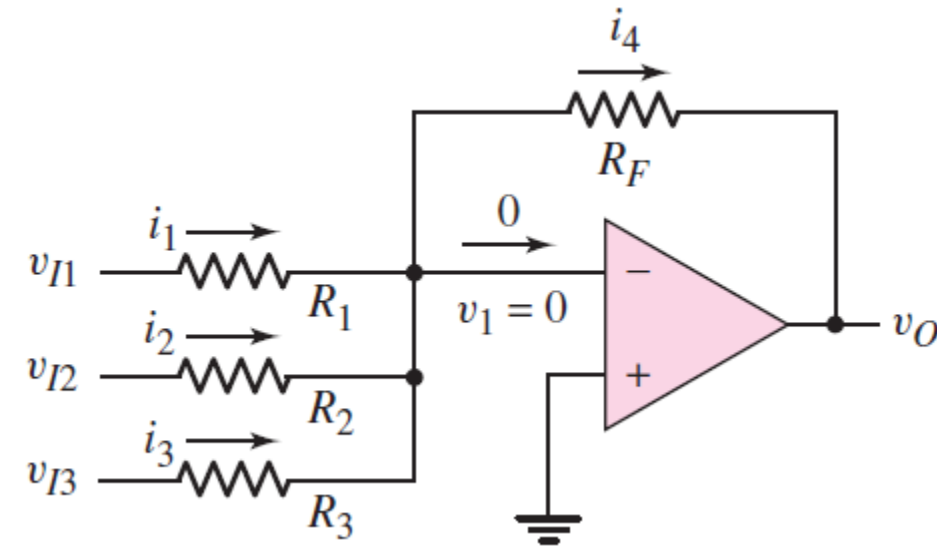


Figure 9.14(a)

Discussion

- Up to this point, we have seen that op-amps can be used to:
 - Multiply a signal by a constant (e.g. $\frac{R_F}{R_1}$)
 - Sum a number of signals with prescribed weights.
 - These are mathematical operations.
- Later in the chapter, we will see that op-amps can also be used to integrate and differentiate.
 - These circuits are the building blocks needed to **perform analog computations**—hence the original name of **operational amplifier**.

Discussion

- Opamps, however, are versatile and can do much **more than just perform mathematical operations**, as we will continue to observe through the remainder of this course.

DESIGN EXAMPLE 9.4

- **Objective:** Design a summing amplifier to produce a specified output signal.
- **Specifications:** The output signal generated from an ideal amplifier circuit is:

$$v_{O1} = 1.2 - 0.5 \sin \omega t \text{ (V)}$$

- Design a summing amplifier to be connected to the amplifier circuit such that the output signal is:

$$v_o = 2 \cdot \sin \omega t \text{ (V)}$$

DESIGN EXAMPLE 9.4

$$v_{O1} = 1.2 - 0.5 \sin\omega t \text{ (V)} \rightarrow v_O = 2 \cdot \sin\omega t \text{ (V)}$$

- **Choices:**

1. Standard precision resistors with tolerances of ± 1 percent are to be used in the final design.
2. Assume an ideal op-amp is available.

- **Solution:** In this case, we need only two inputs to the summing amplifier, as shown in Figure 9.14.

- One input to the summing amplifier is the output of the ideal amplifier circuit and
- The second input should be a DC voltage to cancel the $+ 1.2V$ signal from the amplifier circuit.

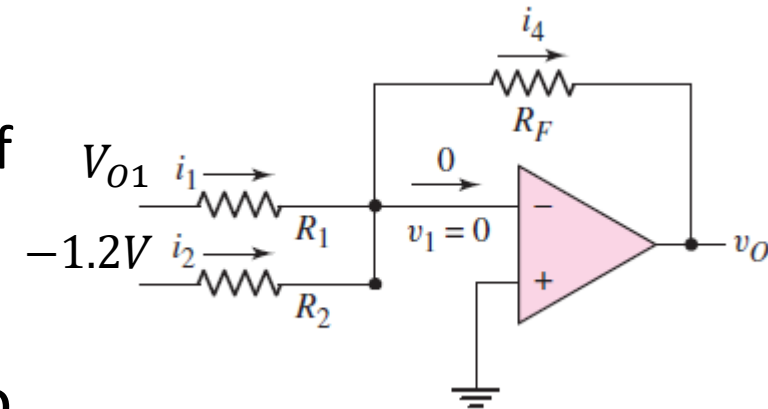


Figure 9.14

DESIGN EXAMPLE 9.4

$$v_{O1} = 1.2 - 0.5 \sin \omega t \text{ (V)} \rightarrow v_o = 2 \cdot \sin \omega t \text{ (V)}$$

- If the voltage gains of each input to the summing amplifier are equal, then an input of $-1.2V$ at the second input will cancel the $+1.2V$ from the amplifier circuit.
- For a $-0.5V$ sinusoidal input signal and a desired $2V$ sinusoidal output signal, the summing amplifier gain must be:

$$A_v = -\frac{R_F}{R_1} = \frac{2}{-0.5} = -4$$

- If we choose the input resistances to be:

$$R_1 = R_2 = 30k\Omega$$

- Then the feedback resistance must be:

$$R_F = 4 \times 30k\Omega = 120k\Omega$$

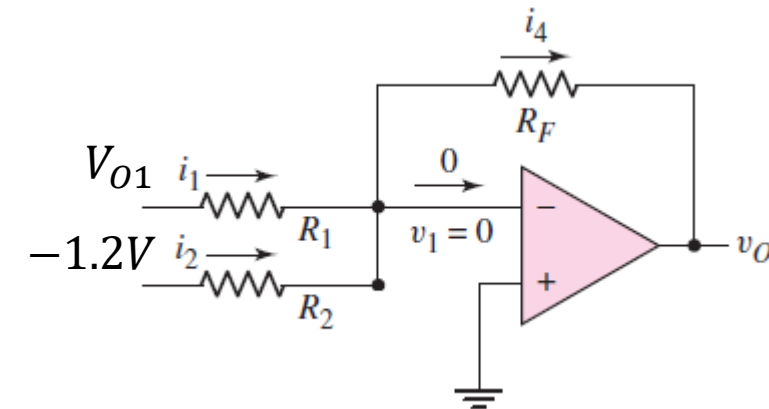


Figure 9.14

DESIGN EXAMPLE 9.4

$$v_{O1} = 1.2 - 0.5 \sin \omega t \text{ (V)} \rightarrow v_o = 2 \cdot \sin \omega t \text{ (V)}$$

$$R_1 = R_2 = 30 \text{ k}\Omega$$

$$R_F = 4 \times 30 \text{ k}\Omega = 120 \text{ k}\Omega$$

- **Trade-offs:** From **Appendix C**, we can choose precision resistor values of $R_F = 124 \text{ k}\Omega$ and $R_1 = R_2 = 30 \text{ k}\Omega$. The ratio of the ideal resistors is 4.13.
- Considering the ± 1 percent tolerance values, the output of the summing amplifier is:

$$v_o = -\frac{R_F(1 \pm 0.01)}{R_1(1 \pm 0.01)} \cdot (1.2 - 0.5 \sin \omega t) - \frac{R_F(1 \pm 0.01)}{R_2(1 \pm 0.01)} \cdot (-1.2)$$

- The DC output voltage is in the range:
 $-0.1926 \leq v_o(\text{DC}) \leq 0.1926 \text{ V}$
- The peak ac output voltage is in the range:
 $1.967 \leq v_o(\text{ac}) \leq 2.047 \text{ V}$

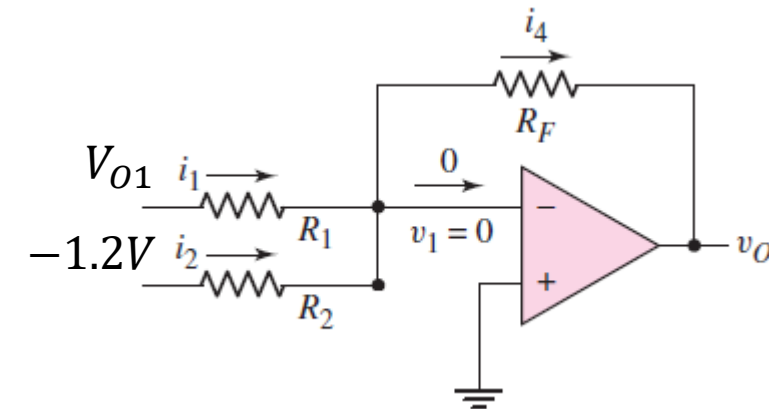


Table C.1 Standard resistance values ($\times 10^n$)

10	16	27	43	68
11	18	30	47	75
12	20	33	51	82
13	22	36	56	91
15	24	39	62	100

EXERCISE PROBLEM Ex. 9.4

- **Design** an inverting summing amplifier that will produce an output voltage of:

$$v_O = -3(v_{I_1} + 2v_{I_2} + 0.3v_{I_3} + 4v_{I_4})$$

- The maximum resistance is to be **limited** to:

$$R_{max} = 400 \text{ k}\Omega$$


- **Answer:** Recall the summing amplifier output for three inputs:

$$v_O = -\left(\frac{R_F}{R_1}v_{I_1} + \frac{R_F}{R_2}v_{I_2} + \frac{R_F}{R_3}v_{I_3}\right)$$

- We expand it for Four inputs as:

$$v_O = -\left(\frac{R_F}{R_1}v_{I_1} + \frac{R_F}{R_2}v_{I_2} + \frac{R_F}{R_3}v_{I_3} + \frac{R_F}{R_4}v_{I_4}\right)$$

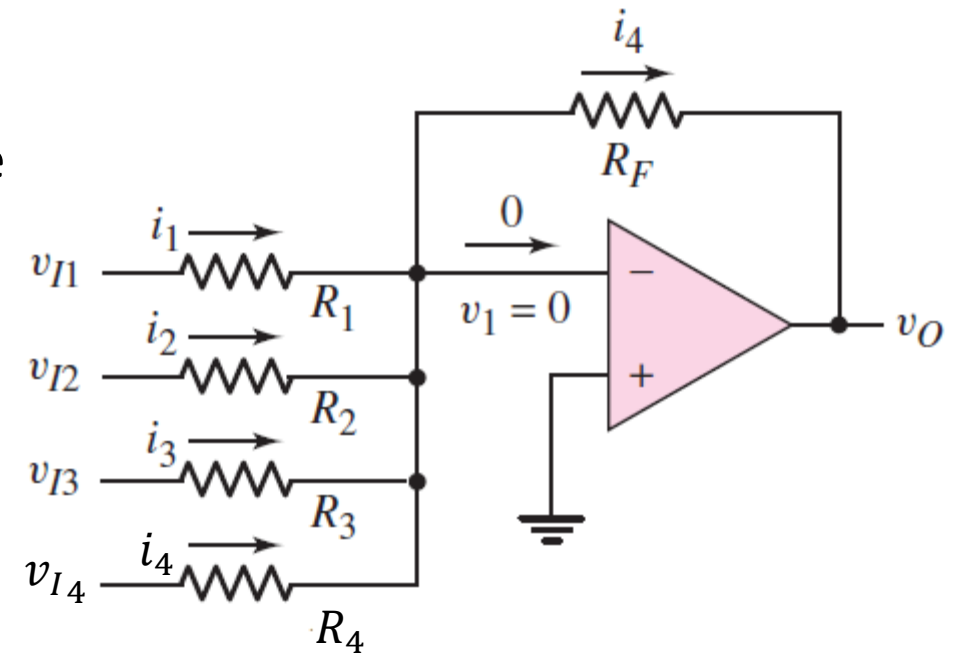- Let $R_3 = R_{max} = 400 \text{ k}\Omega$. **Why R_3 ?**



EXERCISE PROBLEM Ex. 9.4

$$v_o = -3(v_{I_1} + 2v_{I_2} + 0.3v_{I_3} + 4v_{I_4})$$
$$v_o = -\left(\frac{R_F}{R_1}v_{I_1} + \frac{R_F}{R_2}v_{I_2} + \frac{R_F}{R_3}v_{I_3} + \frac{R_F}{R_4}v_{I_4}\right)$$

- Let $R_3 = R_{max} = 400k\Omega \rightarrow 390k\Omega + 10k\Omega$
- $R_F = 3 \times 0.3 \cdot 400k\Omega = 360k\Omega$
- $R_1 = \frac{360k}{3} = 120k\Omega$
- $R_2 = \frac{360k}{3 \times 2} = 60k\Omega \rightarrow 47k\Omega + 13k\Omega$
- $R_4 = \frac{360k}{3 \times 4} = 30k\Omega$

Table C.1

Standard resistance values ($\times 10^n$)

10	16	27	43	68
11	18	30	47	75
12	20	33	51	82
13	22	36	56	91
15	24	39	62	100

EXERCISE PROBLEM Ex. 9.4

• Using the results of previous part for R 's values. Determine v_o for:

a) $v_{I_1} = 0.1V, v_{I_2} = -0.2V, v_{I_3} = -1V, v_{I_4} = 0.05V;$

• **Answer:** $v_o = +1.2V$

b) $v_{I_1} = -0.2V, v_{I_2} = 0.3V, v_{I_3} = 1.5V, v_{I_4} = -0.1V;$

• **Answer:** $v_o = -1.35V$

9.4 Noninverting Amplifier

- In our previous discussions, the feedback element R_2 or R_F was connected between the output and the **inverting terminal** creating a **negative feedback loop**.
- However, a signal can be applied to the **noninverting terminal** while **still maintaining negative feedback**.

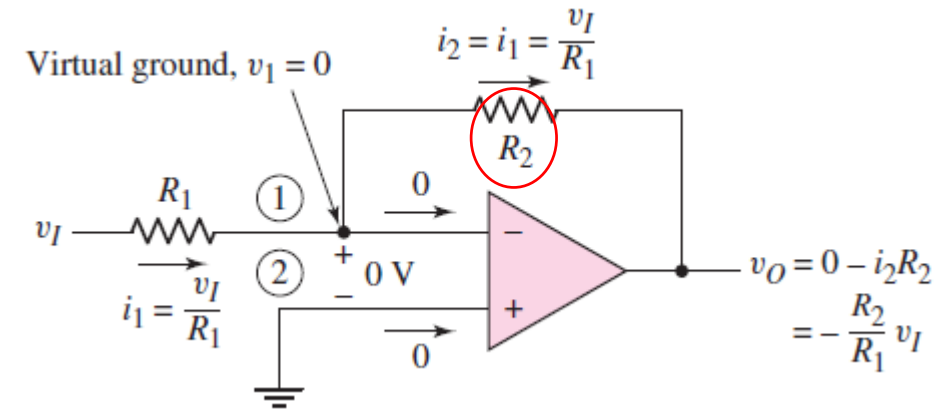


Figure 9.10

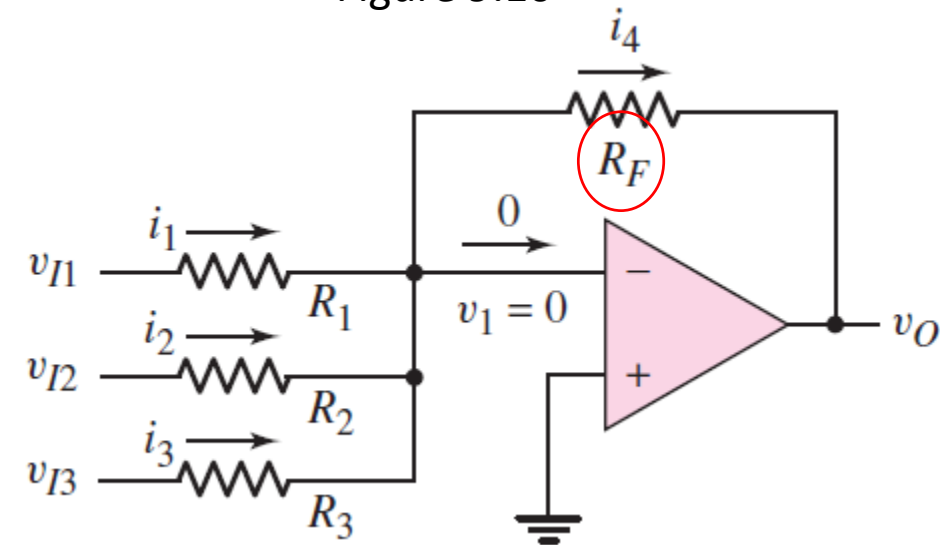


Figure 9.14(a)