

L04

Operational Amplifiers Applications 3

Chapter 9

Ideal Operational Amplifiers and Op-Amp Circuits


Donald A. Neamen (2009). **Microelectronics**: Circuit Analysis and Design,
4th Edition, Mc-Graw-Hill

Prepared by: Dr. Hani Jamleh, *Electrical Engineering Department, The University of Jordan*


Op-Amp Applications

1. Inverting Amplifier
2. Amplifier with T-Network
3. Non-Inverting Amplifier
4. Voltage Follower (Buffer)
5. Summing Amplifier
6. Current to Voltage Converter


1

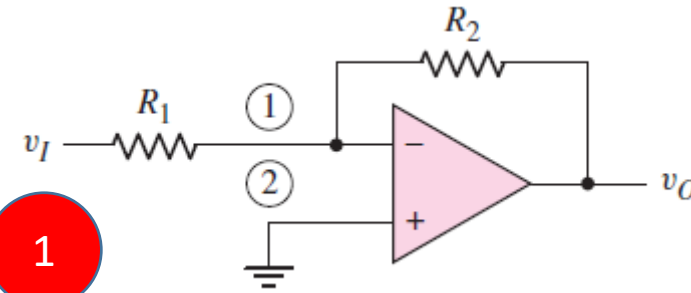


3

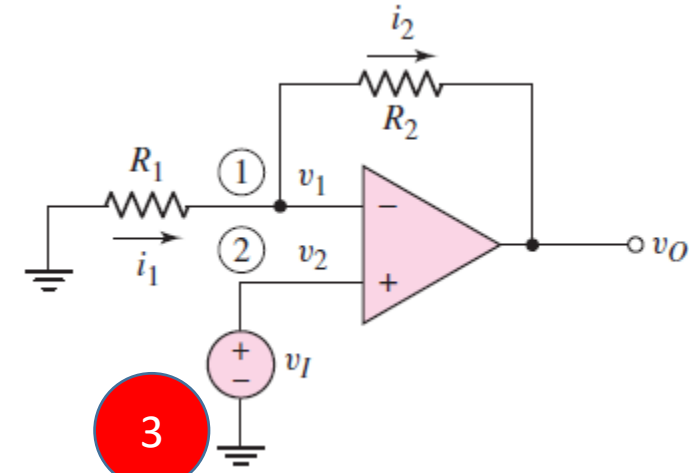


2

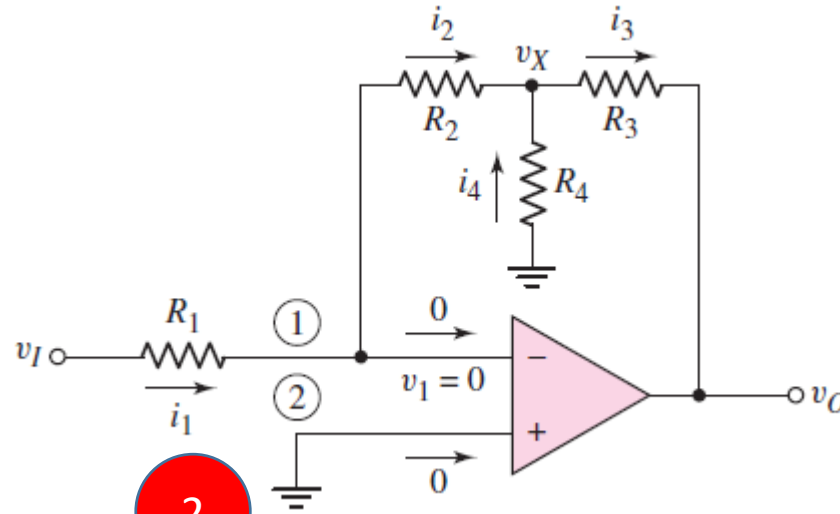


4

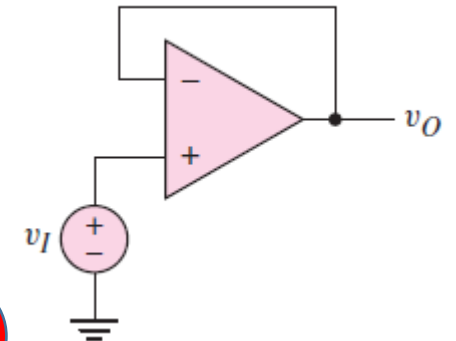

5

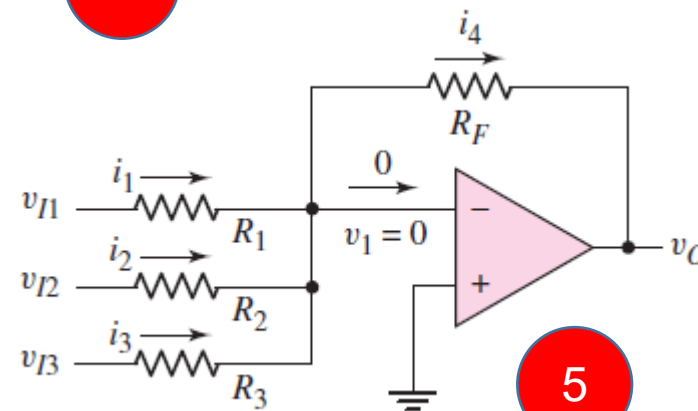

6

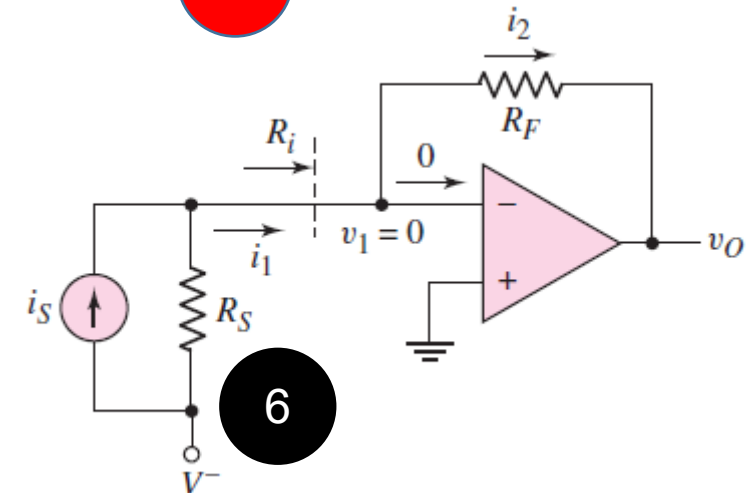

Op-Amp Applications

7. Difference Amplifier


8. Instrumentation Amplifier

9. Integrator


10. Differentiator

11. Reference Voltage Source Design


12. Precision Half-wave Rectifier

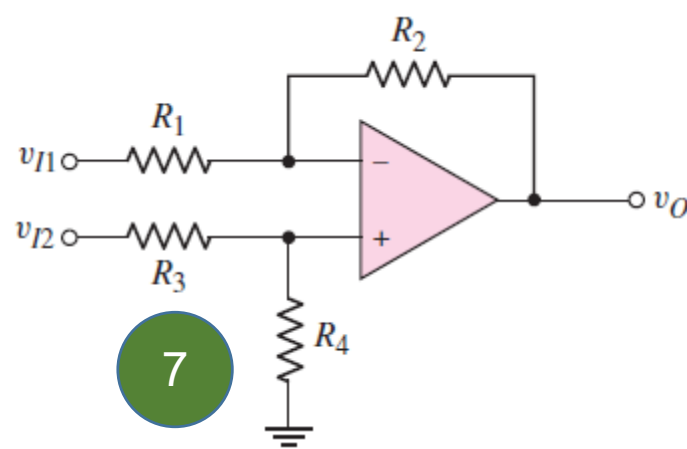


7

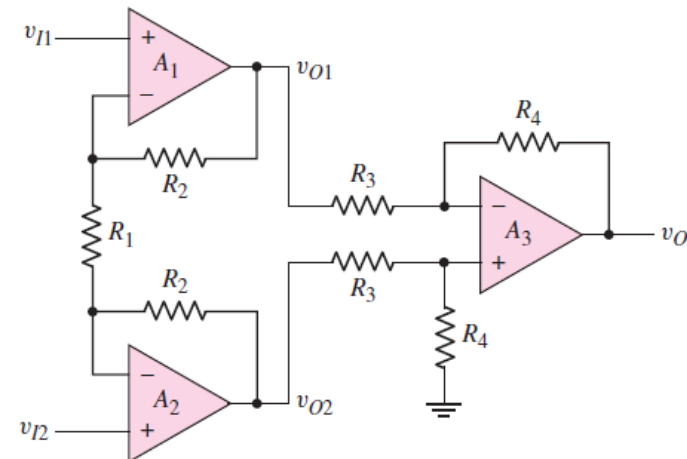


8

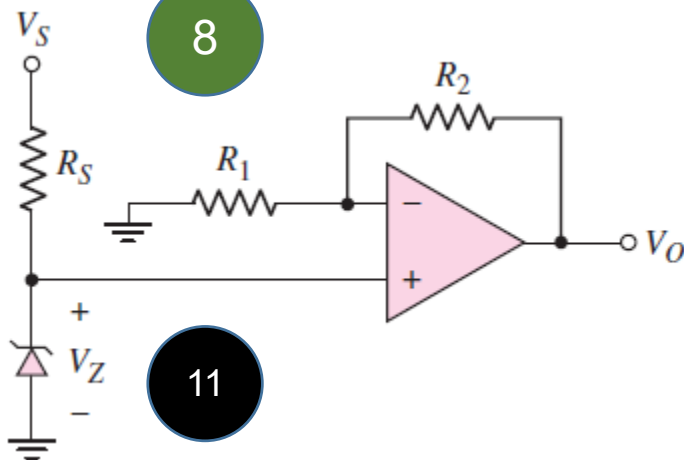


11

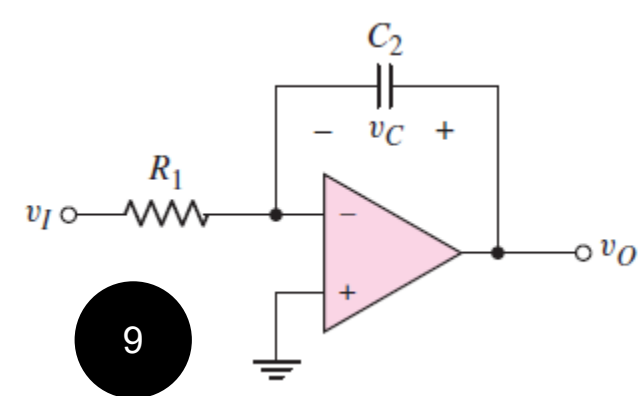

9

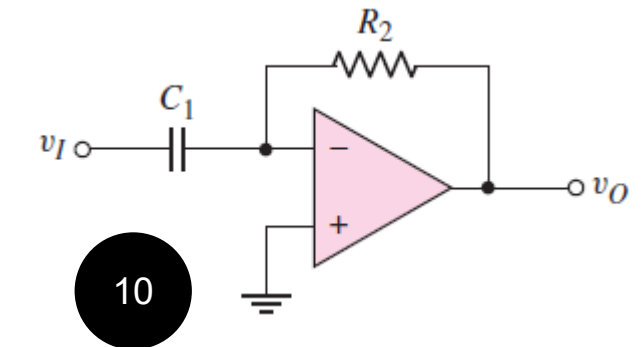

10

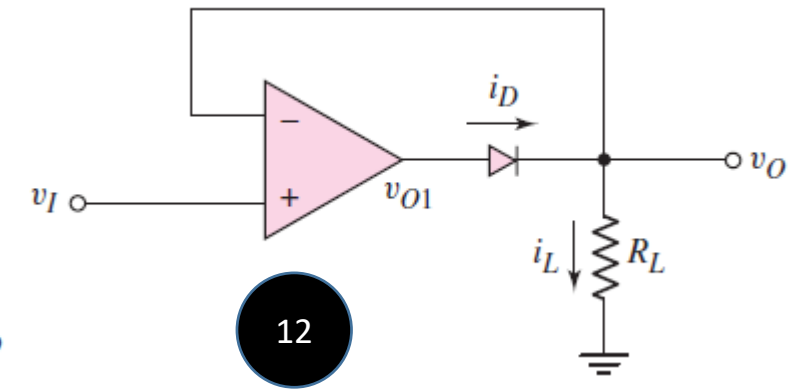

12

9.5.3 Difference Amplifier

- An ideal **difference amplifier** **amplifies** only the difference between two signals
 - It **rejects** any common signals to the two input terminals.
 - For example, a microphone system **amplifies** an audio signal applied to one terminal of a difference amplifier, and **rejects** any 60 Hz noise signal or “hum” existing on both terminals.
- We would like to make a difference amplifier, in which:
 - The output is a function of the **ratio of resistors**, as we had for the inverting and noninverting amplifiers.

9.5.3 Difference Amplifier

- Consider the circuit shown in Figure 9.24(a), with inputs v_{I1} and v_{I2} .
- To analyze the circuit, we will use:
 1. Superposition and
 2. The virtual short concept.
- Figure 9.24(b) shows the circuit with input $v_{I2} = 0$.
 - There are no currents in R_3 and R_4 ; therefore, $v_{2a} = 0$.
- The resulting circuit is the inverting amplifier previously considered, for which:

$$v_{O1} = -\frac{R_2}{R_1} v_{I1}$$

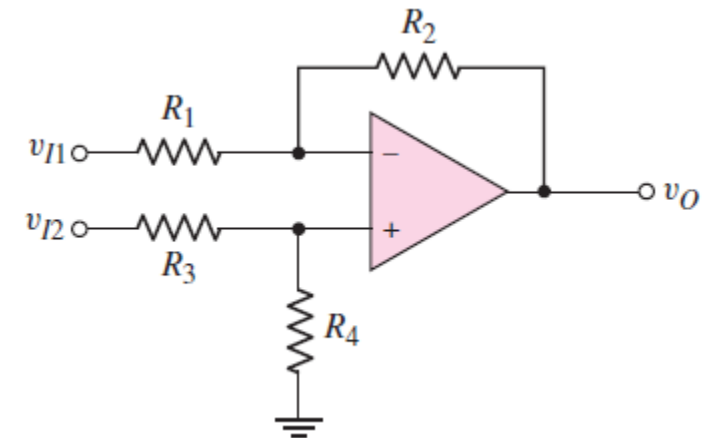


Figure 9.24(a)

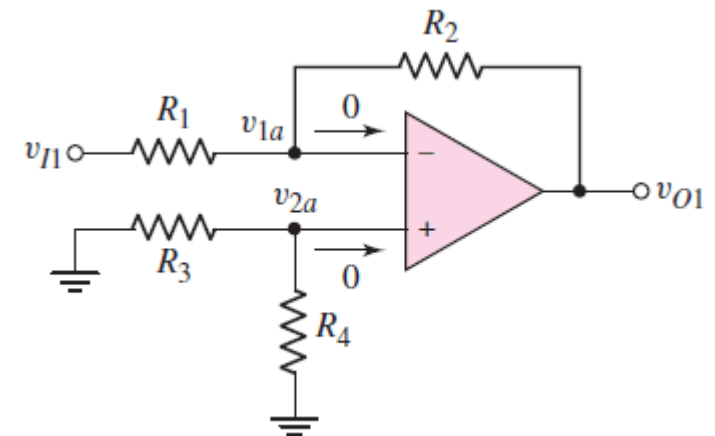


Figure 9.24(b)

9.5.3 Difference Amplifier

- Figure 9.24(c) shows the circuit with $v_{I1} = 0$.
- Since the current into the op-amp is *zero*, R_3 and R_4 form a **voltage divider**.

$$v_{2b} = \frac{R_4}{(R_3 + R_4)} v_{I2}$$

- From the **virtual short concept**, $v_{1b} = v_{2b}$ and the circuit **becomes** a noninverting amplifier:

$$v_{O2} = \left(1 + \frac{R_2}{R_1}\right) v_{1b} = \left(1 + \frac{R_2}{R_1}\right) v_{2b}$$

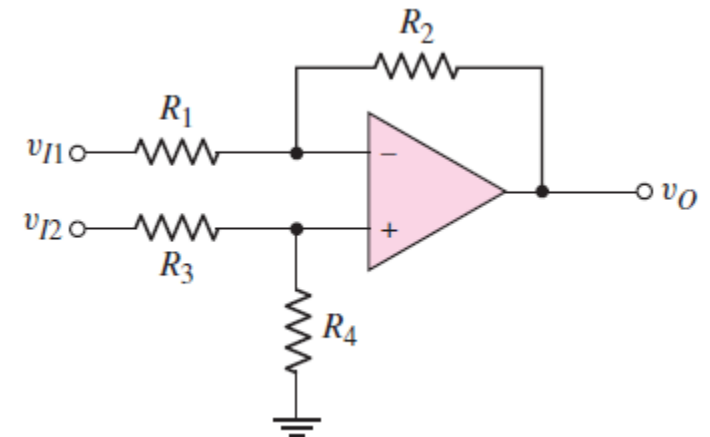


Figure 9.24(a)

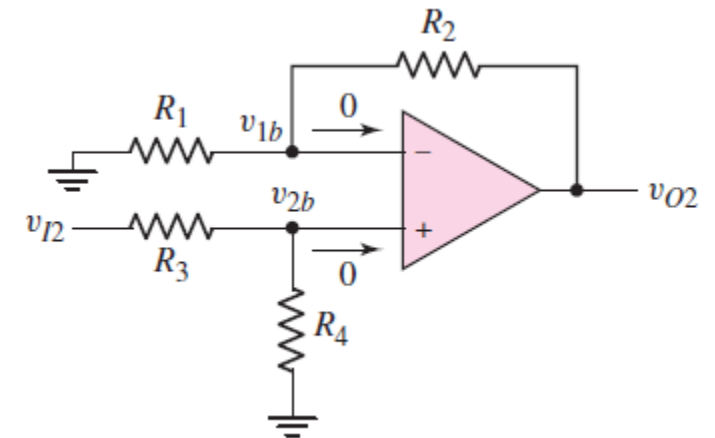


Figure 9.24(c)

9.5.3 Difference Amplifier

- Substituting:

$$v_{2b} = \frac{R_4}{(R_3 + R_4)} v_{I2}$$

- Into:

$$v_{O2} = \left(1 + \frac{R_2}{R_1}\right) v_{2b}$$

- we obtain:

$$v_{O2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) v_{I2}$$

which can be rearranged as follows:

$$v_{O2} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4/R_3}{1 + R_4/R_3}\right) v_{I2}$$

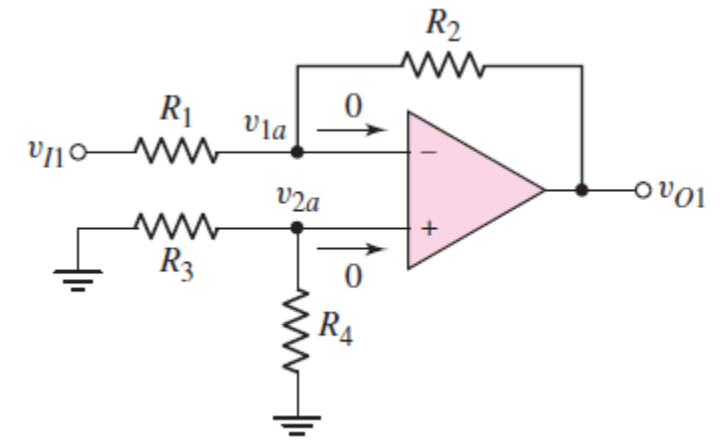


Figure 9.24(b)

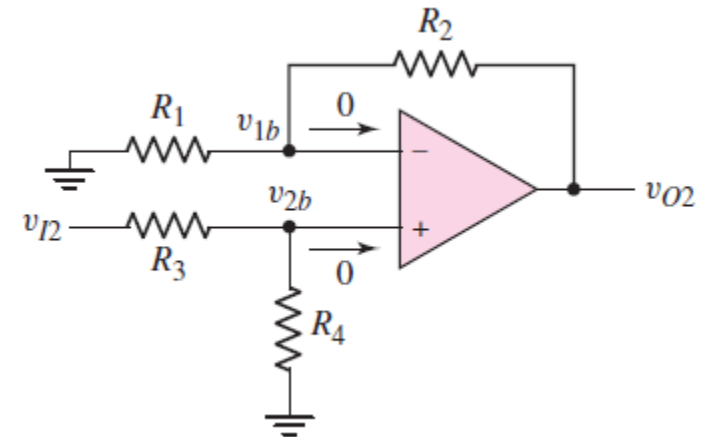


Figure 9.24(c)

9.5.3 Difference Amplifier

$$v_{O1} = -\left(\frac{R_2}{R_1}\right)v_{I1}$$

$$v_{O2} = \left(1 + \frac{R_2}{R_1}\right)\left(\frac{R_4/R_3}{1 + R_4/R_3}\right)v_{I2}$$

- By **superposition**, the net output voltage is the sum of the individual terms, we have:

$$v_O = -\left(\frac{R_2}{R_1}\right)v_{I1} + \left(1 + \frac{R_2}{R_1}\right)\left(\frac{R_4/R_3}{1 + R_4/R_3}\right)v_{I2}$$

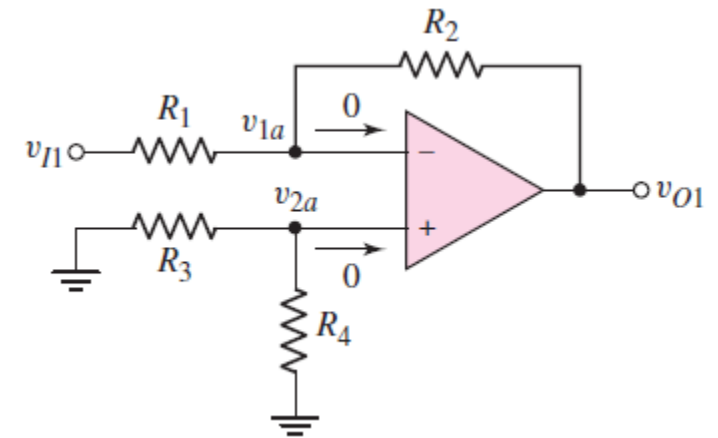


Figure 9.24(b)

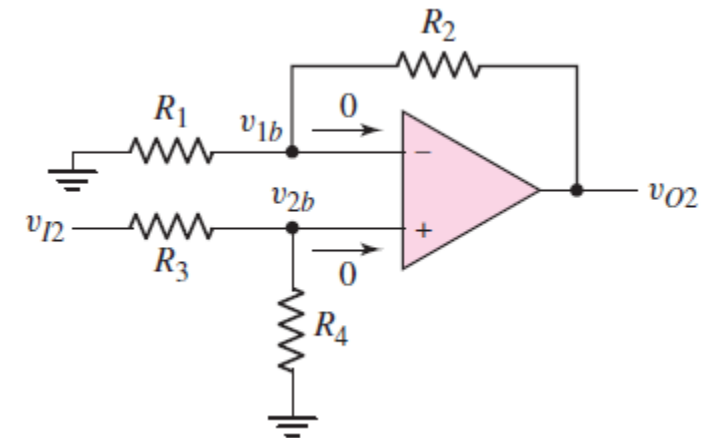


Figure 9.24(c)

9.5.3 Difference Amplifier

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4/R_3}{1 + R_4/R_3}\right) v_{I2} - \left(\frac{R_2}{R_1}\right) v_{I1}$$

- A property of the **ideal difference amplifier** is that:
 - The output voltage is *zero* when $v_{I1} = v_{I2}$.
- An inspection of Equation above shows that this condition is met if:

$$\frac{R_4}{R_3} = \frac{R_2}{R_1}$$

- The output voltage is then:

$$v_O = \frac{R_2}{R_1} (v_{I2} - v_{I1})$$

- Which **indicates** that this amplifier has a differential gain of:

$$A_d = R_2/R_1$$

- This factor is a closed-loop differential gain, rather than the open-loop differential gain A_{od} of the op-amp itself.

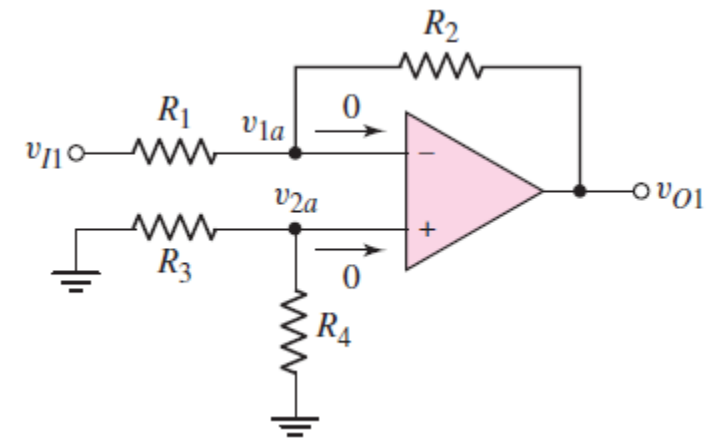


Figure 9.24(b)

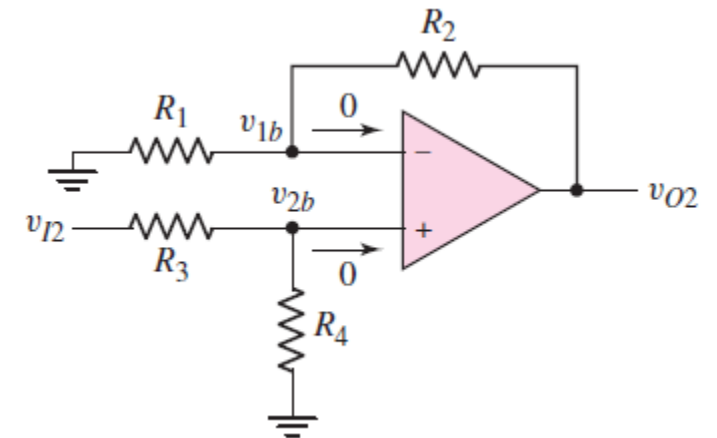


Figure 9.24(c)

9.5.3 Difference Amplifier

- Another important characteristic of electronic circuits is the **input resistance**.
- The **differential input resistance** can be determined by using the circuit shown in Figure 9.25.
- In the figure, we have imposed the condition given in Equation:

$$\frac{R_4}{R_3} = \frac{R_2}{R_1}$$

- Set $R_1 = R_3$ and $R_2 = R_4$.

- The input resistance is then defined as:

$$R_i = \frac{v_I}{i}$$

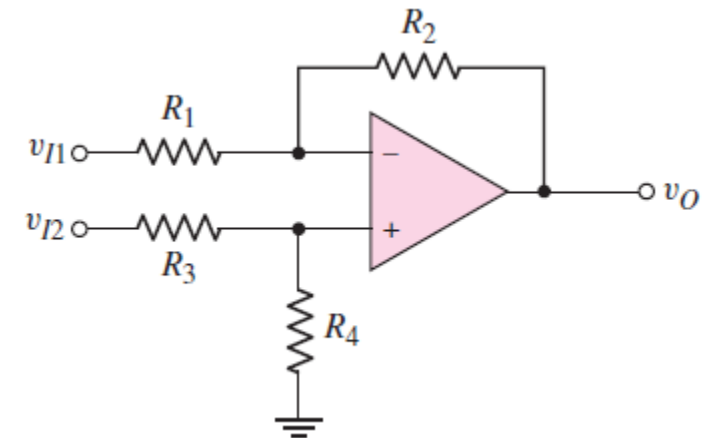


Figure 9.24(a)

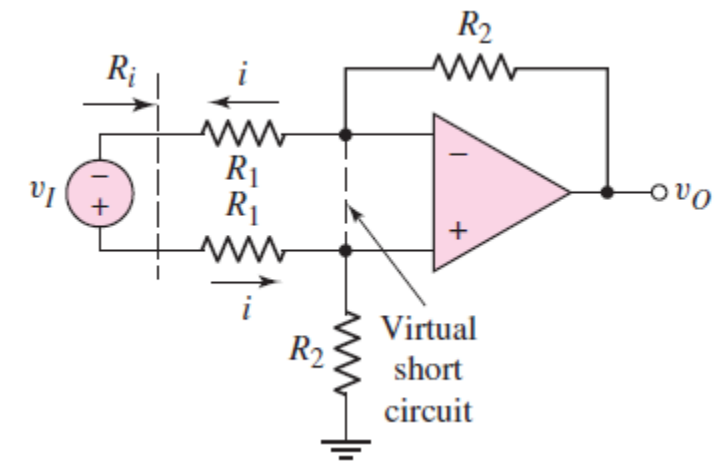


Figure 9.25

9.5.3 Difference Amplifier

$$R_i = \frac{v_I}{i}$$

- Taking into account the **virtual short concept**, we can write a loop equation, as follows:

$$v_I = i \cdot R_1 + i \cdot R_1 = i(2 \cdot R_1)$$

- The input resistance is:

$$R_i = 2R_1$$

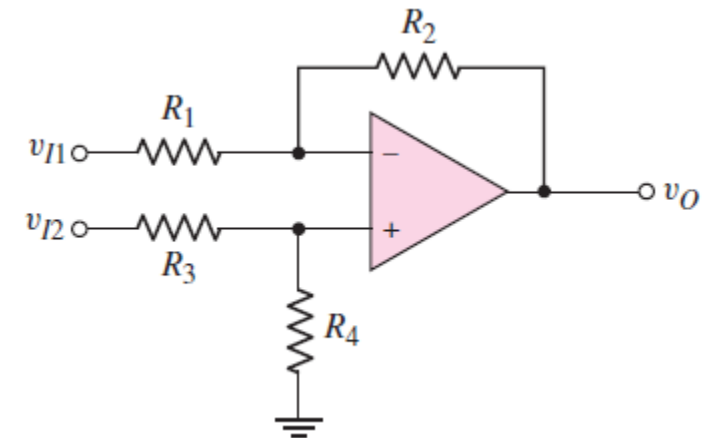


Figure 9.24(a)

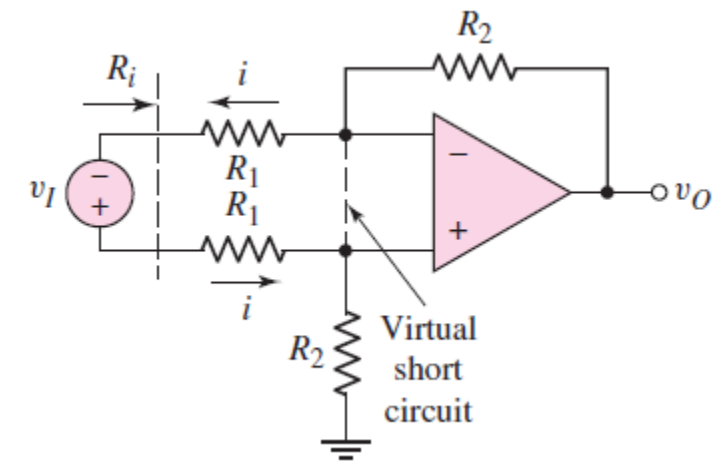


Figure 9.25

9.5.3 Difference Amplifier common-mode input signal

- In the **ideal difference amplifier**, the output v_O is zero when $v_{I1} = v_{I2}$.
- However, an inspection of Equation:

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4/R_3}{1 + R_4/R_3}\right) v_{I2} - \left(\frac{R_2}{R_1}\right) v_{I1}$$

shows that this condition is not satisfied if:

$$R_4/R_3 \neq R_2/R_1$$

- When $v_{I1} = v_{I2}$, the input is called a **common-mode input signal**.
- The **common-mode input voltage** is defined as:

$$v_{cm} = (v_{I1} + v_{I2})/2$$

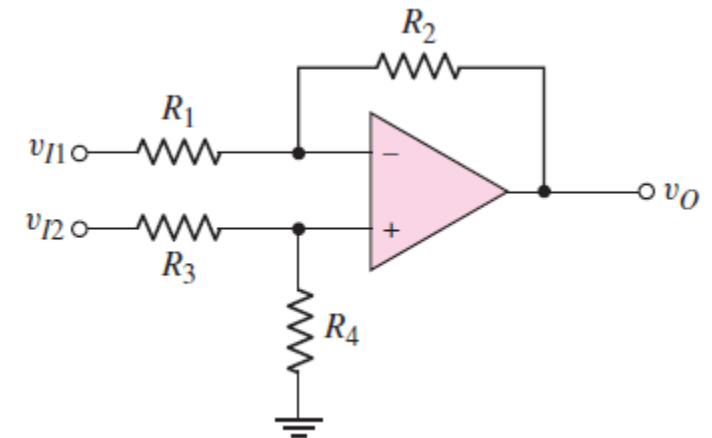


Figure 9.24(a)

9.5.3 Difference Amplifier common-mode rejection ratio

$$v_{cm} = (v_{I1} + v_{I2})/2$$

- The **common-mode gain** is then defined as:

$$A_{cm} = \frac{v_O}{v_{cm}}$$

- Ideally**, when a common-mode signal is applied, $v_O = 0$ and $A_{cm} = 0$.
- A *nonzero* common-mode gain **may be generated** in actual op-amp circuits.
- A **figure of merit** for a difference amplifier is the **common-mode rejection ratio (CMRR)**, which is defined as:
 - The magnitude of the ratio of differential gain to common-mode gain:

$$CMRR = \left| \frac{A_d}{A_{cm}} \right|$$

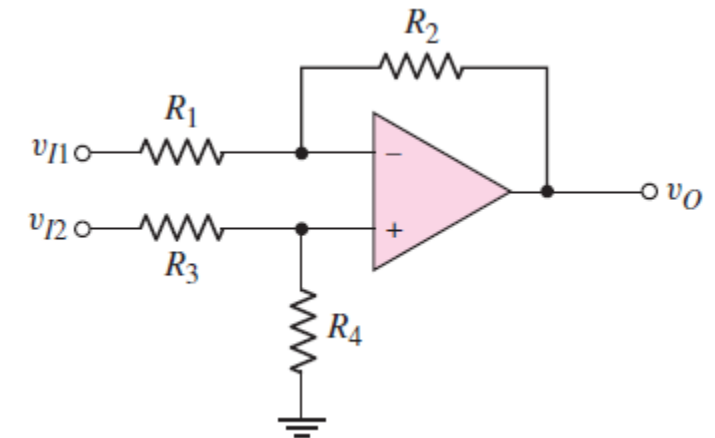


Figure 9.24(a)

9.5.3 Difference Amplifier

$$CMRR = \left| \frac{A_d}{A_{cm}} \right|$$

- Usually, the $CMRR$ is expressed in decibels:

$$CMRR(dB) = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right|$$

- **Ideally**, the common-mode rejection ratio is *infinite*.
- In an **actual** differential amplifier, we would like the common-mode rejection ratio to be **as large as possible**.

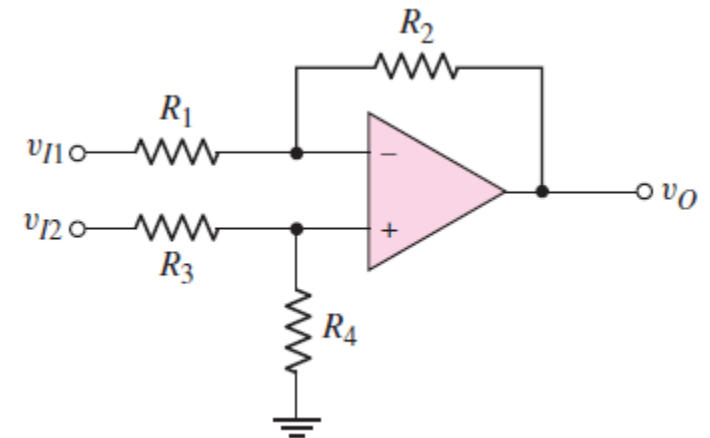


Figure 9.24(a)

EXAMPLE 9.7

- **Objective:** Calculate the common-mode rejection ratio of a difference amplifier.
- Consider the difference amplifier shown in Figure 9.24(a). Let $R_2/R_1 = 10$ and $R_4/R_3 = 11$.
- Determine $CMRR(dB)$.
- **Solution:** From Equation:

$$v_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4/R_3}{1 + R_4/R_3}\right) v_{I2} - \left(\frac{R_2}{R_1}\right) v_{I1}$$

- we have:

$$v_o = (1 + 10) \left(\frac{11}{1 + 11}\right) v_{I2} - (10)v_{I1}$$
$$v_o = 10.0833v_{I2} - 10v_{I1}$$

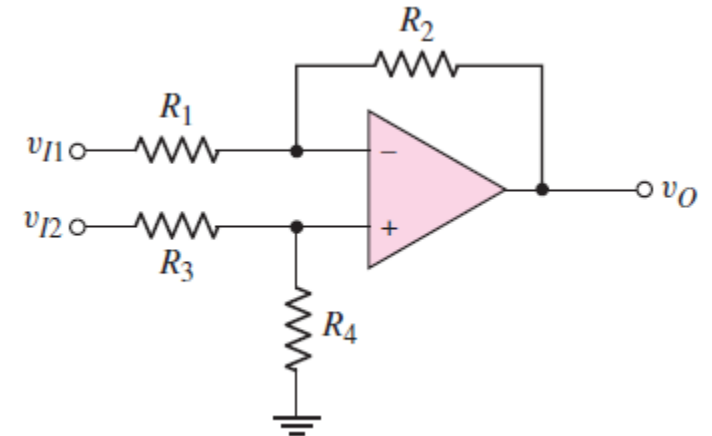


Figure 9.24(a)

EXAMPLE 9.7

$$v_O = 10.0833v_{I2} - 10v_{I1}$$

- The **differential-mode input voltage** is defined as:

$$v_d = v_{I2} - v_{I1}$$

- and the **common-mode input voltage** is defined as:

$$v_{cm} = (v_{I1} + v_{I2})/2$$

- **Combining** these two equations **produces**:

$$v_{I1} = v_{cm} - \frac{v_d}{2}$$

$$v_{I2} = v_{cm} + \frac{v_d}{2}$$

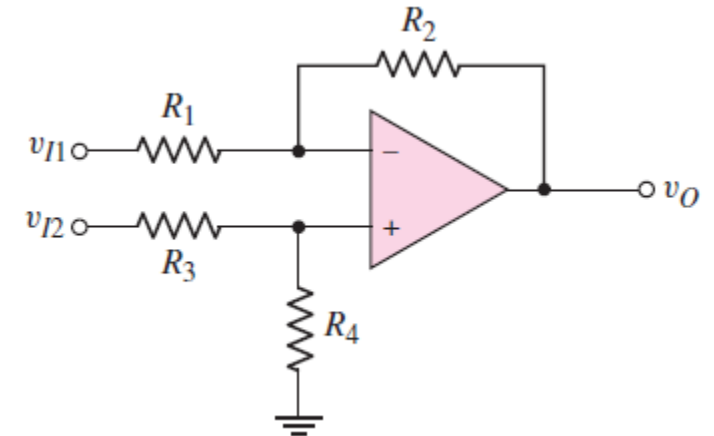


Figure 9.24(a)

EXAMPLE 9.7

- If we substitute Equations:

$$v_{I1} = v_{cm} - \frac{v_d}{2}$$

and

$$v_{I2} = v_{cm} + \frac{v_d}{2}$$

in Equation:

$$v_o = 10.0833v_{I2} - 10v_{I1}$$

we obtain:

$$v_o = (10.0833) \left(v_{cm} + \frac{v_d}{2} \right) - (10) \left(v_{cm} - \frac{v_d}{2} \right)$$

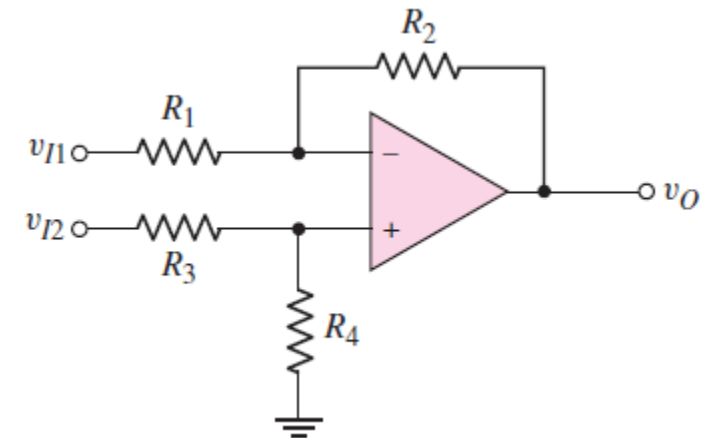


Figure 9.24(a)

EXAMPLE 9.7

$$v_o = (10.0833) \left(v_{cm} + \frac{v_d}{2} \right) - (10) \left(v_{cm} - \frac{v_d}{2} \right)$$
$$v_o = 10.042v_d + 0.0833v_{cm}$$

- The output voltage is also:

$$v_o = A_d v_d + A_{cm} v_{cm}$$

- If we compare the two Equations above, we get:

$$A_d = 10.042 \text{ and } A_{cm} = 0.0833$$

- Therefore the common-mode rejection ratio, is:

$$CMRR(dB) = 20 \log_{10} \left| \frac{A_d}{A_{cm}} \right| = 20 \log_{10} \left(\frac{10.042}{0.0833} \right) = 41.6dB$$

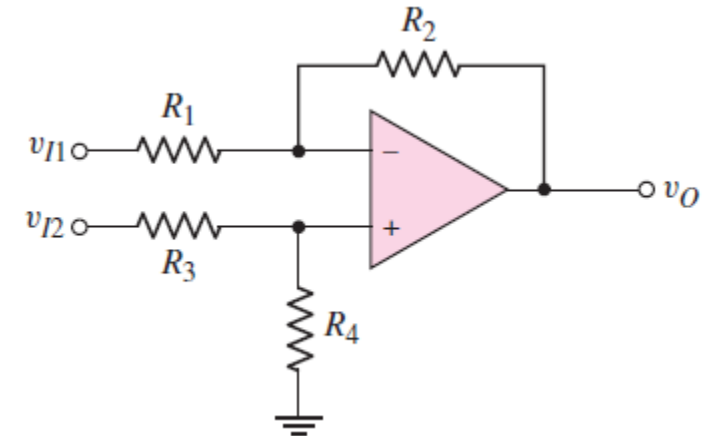


Figure 9.24(a)

EXAMPLE 9.7

$$CMRR(dB) = 20\log_{10} \left(\frac{10.042}{0.0833} \right) = 41.6dB$$

- **Comment:** For good differential amplifiers, **typical** $CMRR$ values are in the range of 80~100 dB.
- This example **shows** how close the ratios R_2/R_1 and R_4/R_3 must be in order to achieve a $CMRR$ value in that range.


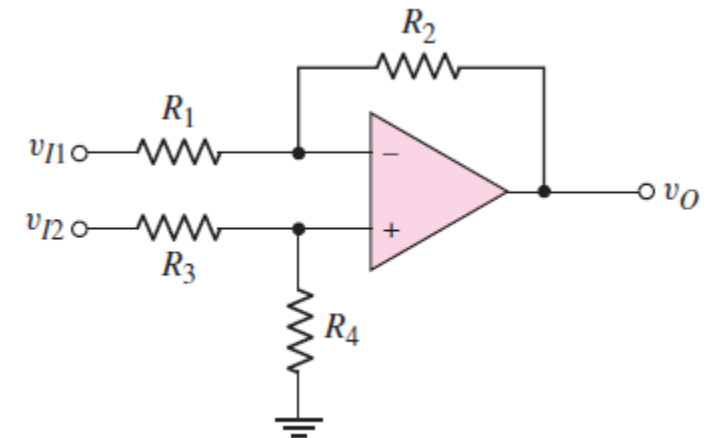
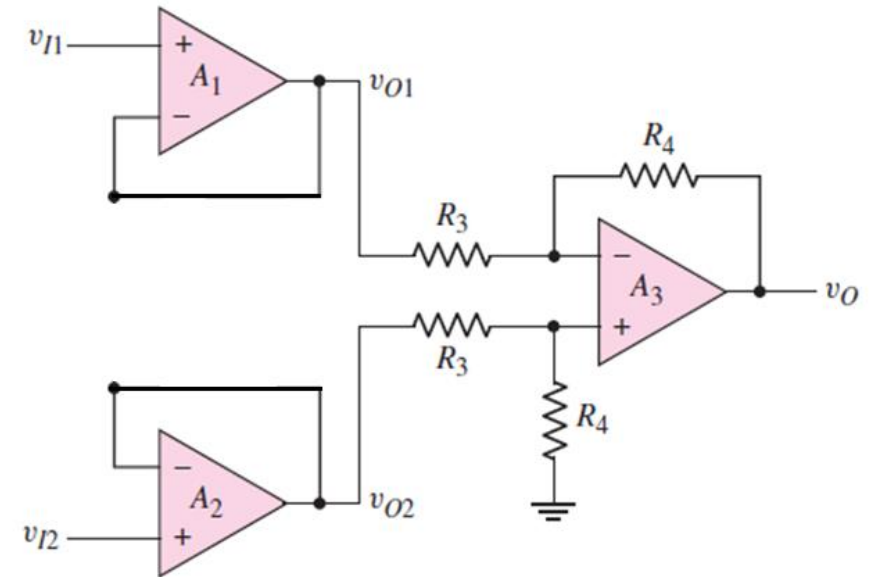


Figure 9.24(a)

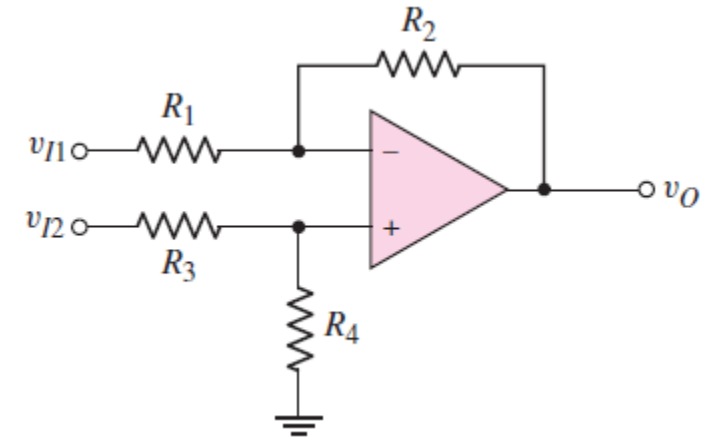9.5.4 Instrumentation Amplifier

- We saw that it is difficult to obtain:
 1. A **high input impedance R_i** and
 2. A **high gain A_d** in a difference amplifier
 - with **reasonable** resistor values.
- One solution is:
 - **To insert** a voltage follower between each source and the corresponding input.
- A **disadvantage of this design** is that:
 - The **gain** of the amplifier cannot easily be **changed**. In which we would **need to change** two resistance values and still maintain equal ratios between R_2/R_1 and R_4/R_3 .



9.5.4 Instrumentation Amplifier

- Optimally, we would like to be able to **change the gain by changing only a single resistance value**.
- The circuit in Figure 9.26, called an instrumentation amplifier, allows this flexibility.
 - Two noninverting amplifiers, A_1 and A_2 , are used as the **input stage**, and
 - A difference amplifier, A_3 is the **amplifying stage**.

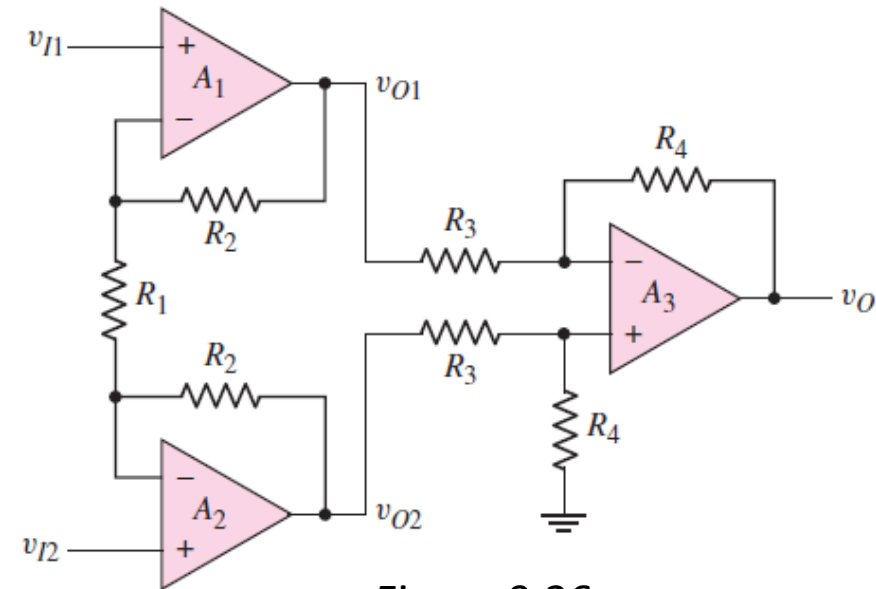


Figure 9.26

9.5.4 Instrumentation Amplifier

- We **begin** the analysis using the **virtual short concept** for the input stages.
- The currents and voltages in the amplifier are shown in Figure 9.27. The current in resistor R_1 is then:

$$i_1 = \frac{(v_{I1} - v_{I2})}{R_1}$$

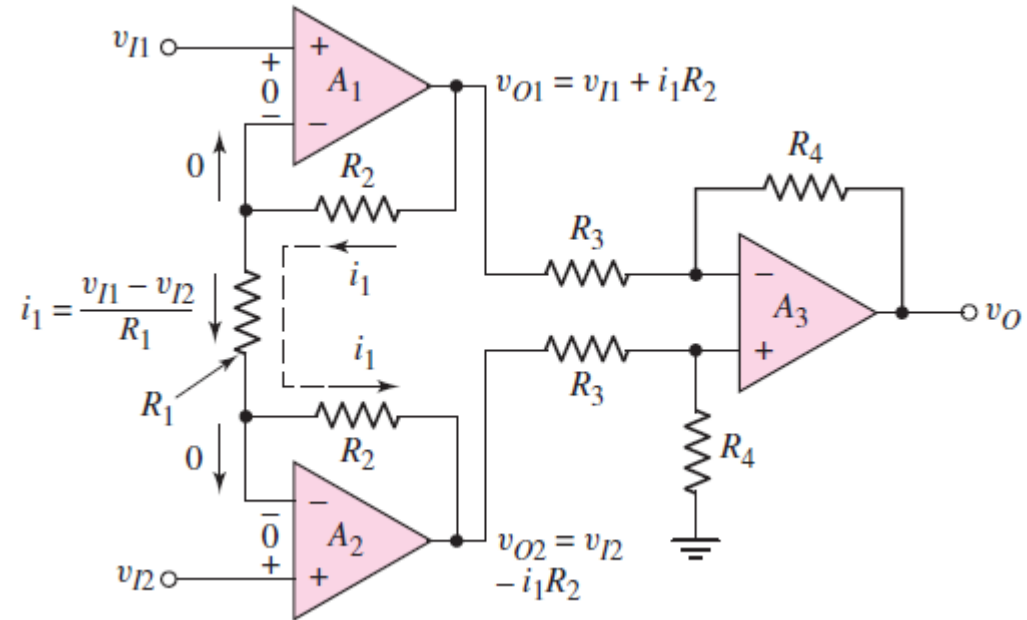


Figure 9.27

9.5.4 Instrumentation Amplifier

- The current in resistors R_2 is also i_1 , and the output voltages of op-amps A_1 and A_2 are, respectively:

$$v_{O1} = v_{I1} + i_1 R_2 = \left(1 + \frac{R_2}{R_1}\right) v_{I1} - \frac{R_2}{R_1} v_{I2}$$

$$v_{O2} = v_{I2} - i_1 R_2 = \left(1 + \frac{R_2}{R_1}\right) v_{I2} - \frac{R_2}{R_1} v_{I1}$$

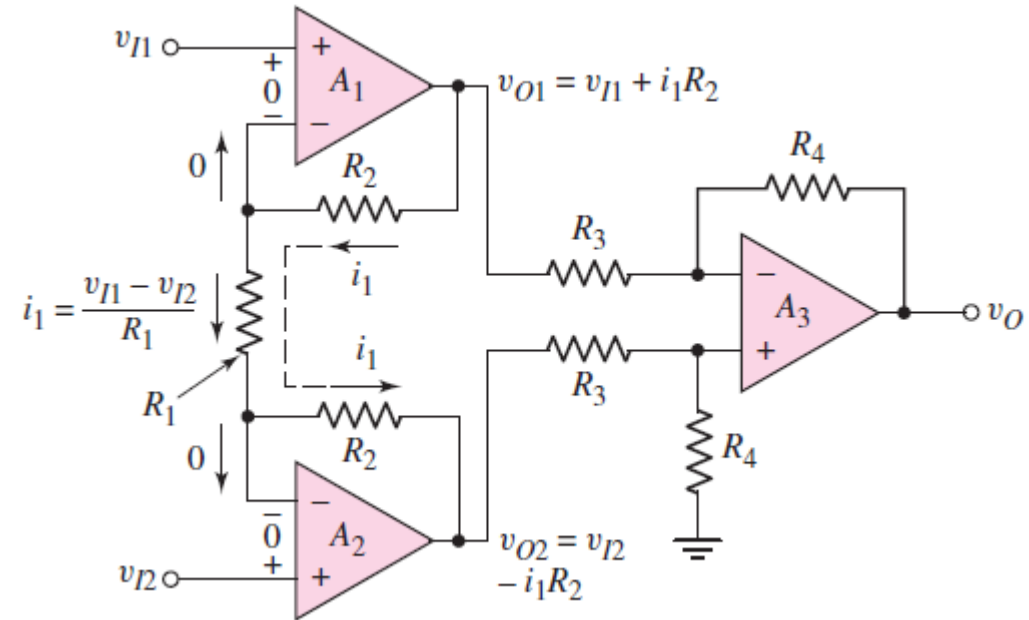


Figure 9.27

9.5.4 Instrumentation Amplifier

- From previous results, the output of the difference amplifier is given as:

$$v_O = \frac{R_4}{R_3} (v_{O2} - v_{O1})$$

- Substituting Equations of v_{O1} and v_{O2} into the Equation above:

$$v_O = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (v_{I2} - v_{I1})$$

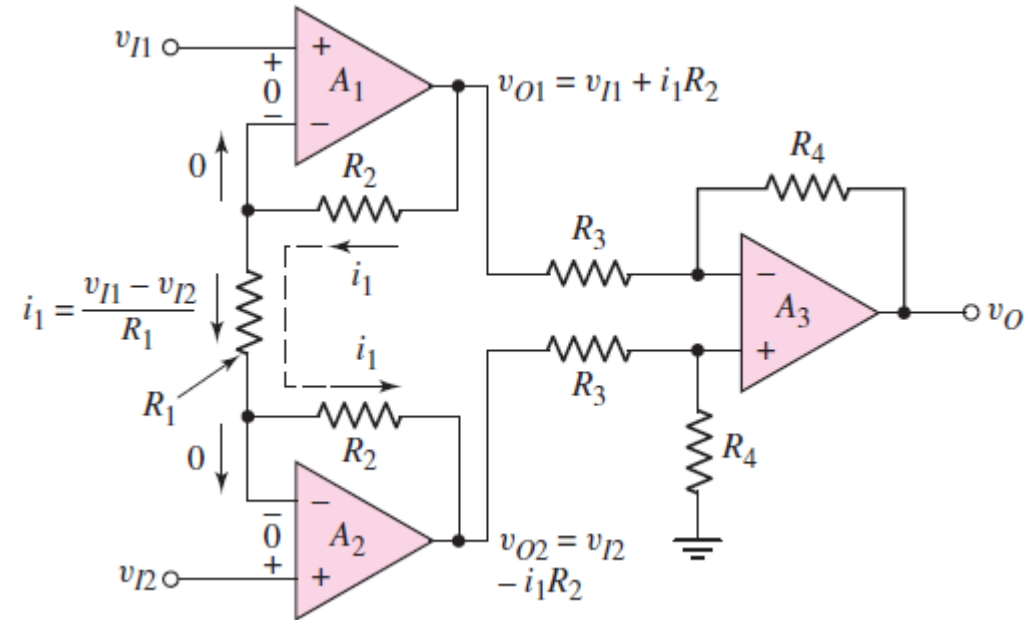


Figure 9.27

9.5.4 Instrumentation Amplifier

$$v_O = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (v_{I2} - v_{I1})$$

- Two advantages:
 1. Since the input signal voltages are applied directly to the noninverting terminals of A_1 and A_2 , **the input impedance is very large, ideally infinite.**
 - It is one desirable characteristic of the instrumentation amplifier.
 2. The **differential gain is a function of resistor R_1** , which can easily **be varied** by using a potentiometer, thus **providing** a variable amplifier gain.

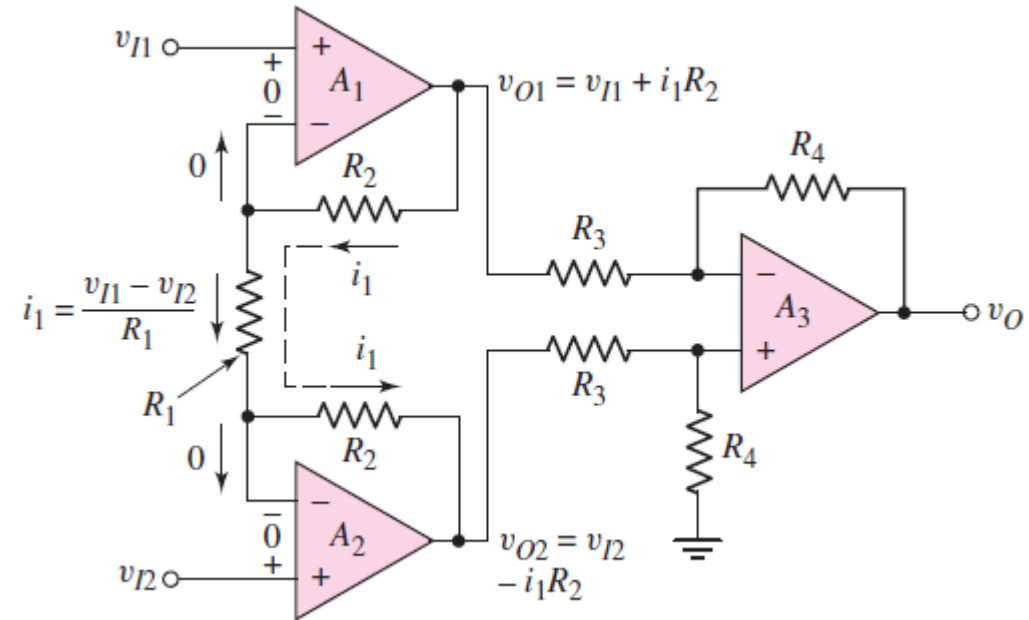


Figure 9.27



EXAMPLE 9.8

- **Objective:** Determine the range required for resistor R_1 , to realize a differential gain adjustable from 5 to 500.
- For the instrumentation amplifier circuit shown in Figure 9.26.
- Assume that $R_4 = 2R_3$, so that the difference amplifier gain is 2.

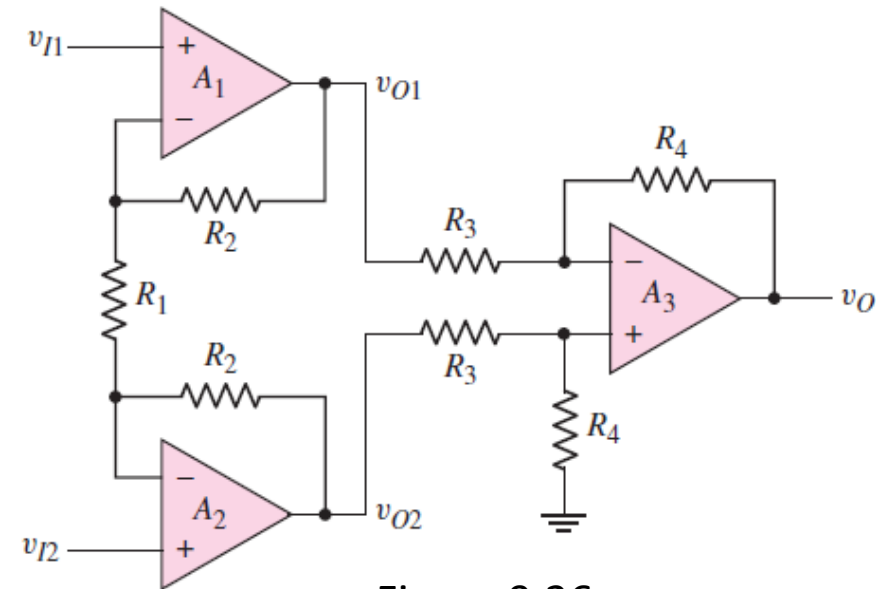


Figure 9.26

EXAMPLE 9.8

- **Solution:** Assume that resistance R_1 is a combination of a fixed resistance R_{1f} and a variable resistance R_{1v} , as shown in Figure 9.28.
- The fixed resistance ensures that:
 - The gain is limited to a maximum value, even if the variable resistance is set equal to zero.
- Assume the variable resistance is a potentiometer:

$$R_{1v} = 100 \text{ k}\Omega$$

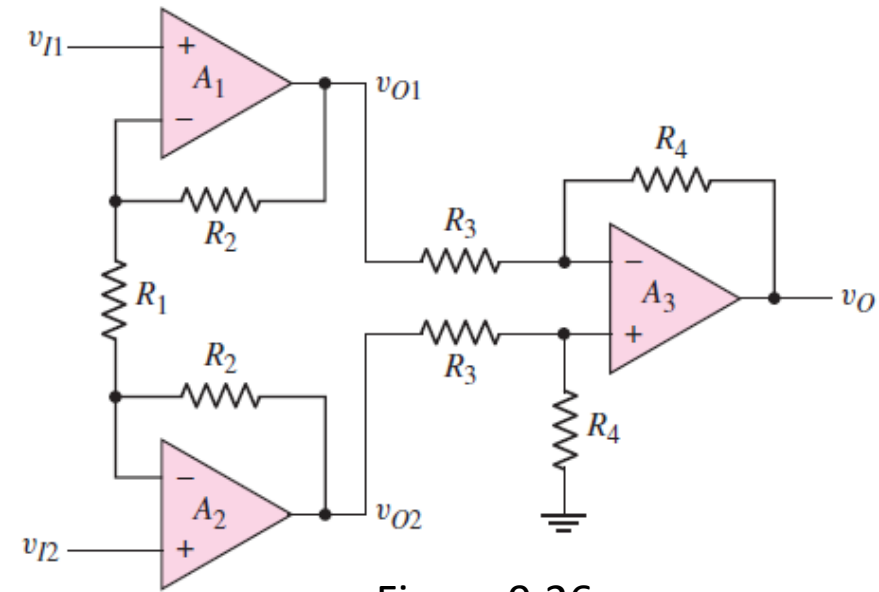


Figure 9.26

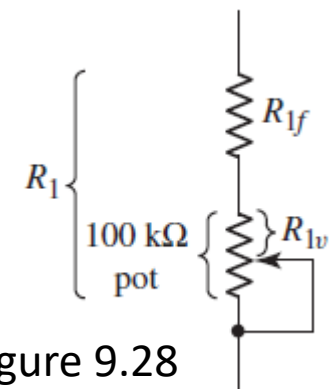


Figure 9.28

EXAMPLE 9.8

- From the Equation:

$$v_O = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (v_{I2} - v_{I1})$$


- The maximum differential gain is:

$$500 = 2 \left(1 + \frac{2R_2}{R_{1f}} \right)$$

$$2R_2 = 249R_{1f}$$

- The minimum differential gain is:

$$5 = 2 \left(1 + \frac{2R_2}{R_{1f} + 100k} \right)$$

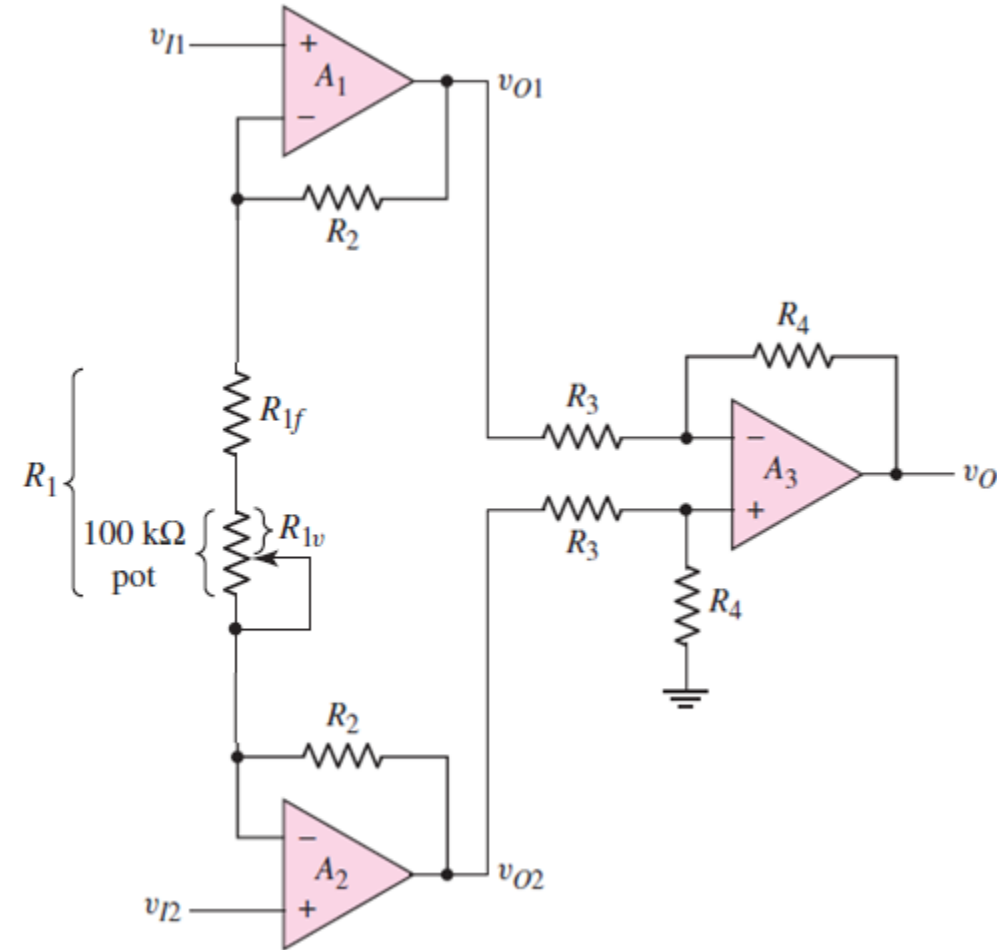

EXAMPLE 9.8

- Let:

$$2R_2 = 249R_{1f}$$

- Into:

$$5 = 2 \left(1 + \frac{2R_2}{R_{1f} + 100k} \right)$$

- We get:


$$1.5 = \frac{249R_{1f}}{R_{1f} + 100}$$

- The resulting value of R_{1f} is:

$$R_{1f} = 0.606k\Omega = 606\Omega$$

- which yields:

$$R_2 = 75.5k\Omega$$

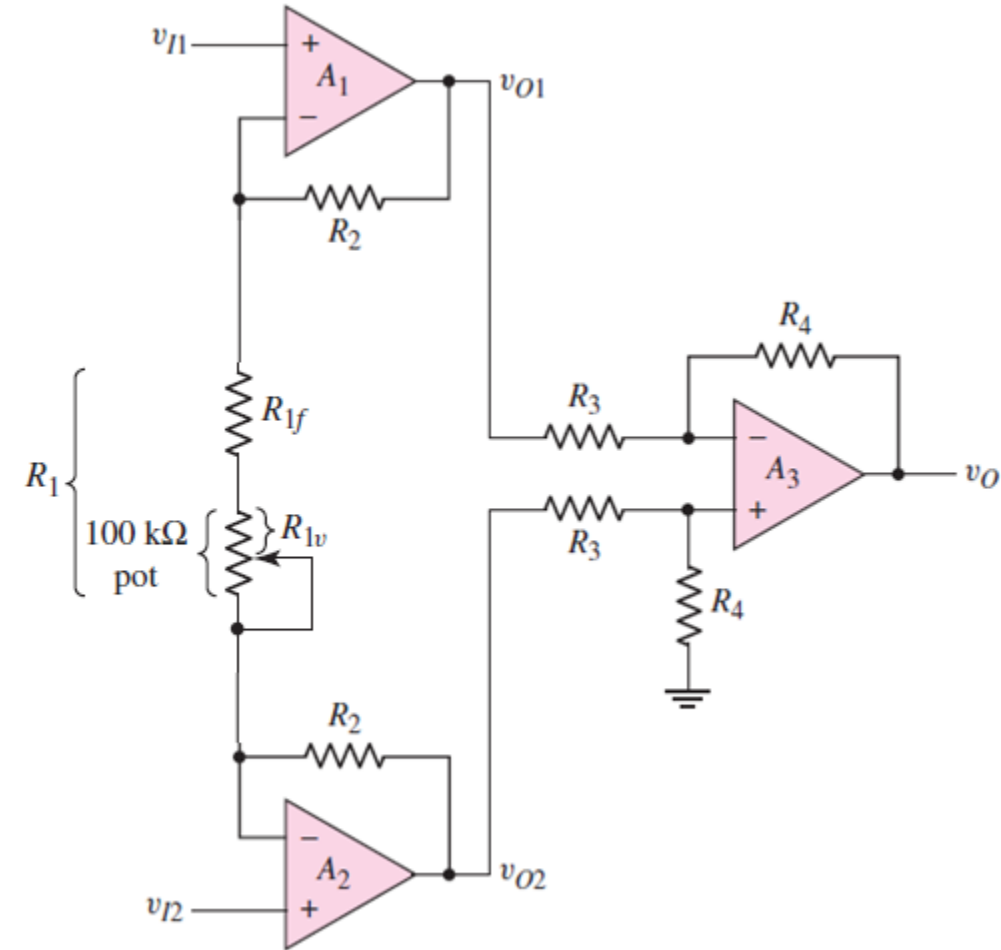


EXAMPLE 9.8

$$R_{1f} = 606\Omega, \text{ and } R_2 = 75.5k\Omega$$

- **Comment:** We can select **standard resistance values** that are close to the values calculated, and the range of the gain will be approximately in the desired range.


Table C.1		Standard resistance values ($\times 10^n$)		
10	16	27	43	68
11	18	30	47	75
12	20	33	51	82
13	22	36	56	91
15	24	39	62	100

- $R_{1f} = 606 \rightarrow 470 + 130 = 600\Omega$, and
- $R_2 = 75.5k\Omega \rightarrow 75k\Omega + 510\Omega = 75.51 k\Omega$

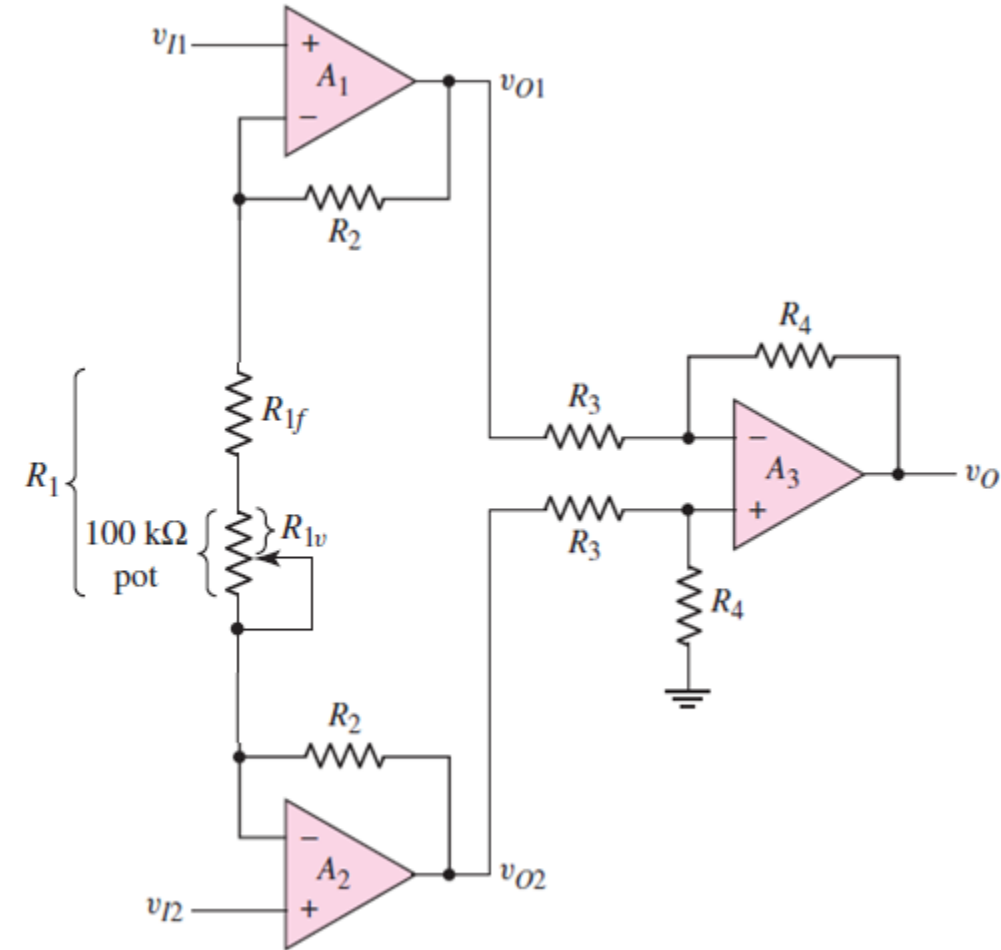

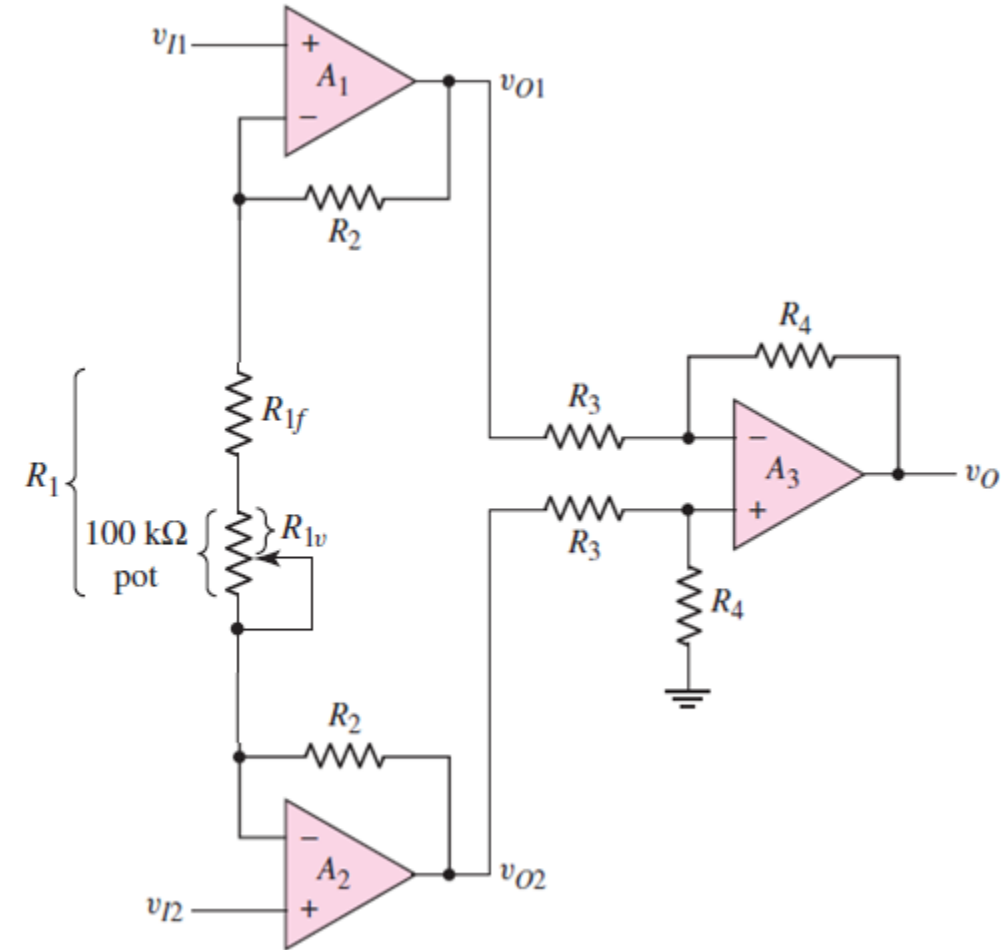EXAMPLE 9.8

- **Design Pointer:** An amplifier with a wide range of gain and designed with a potentiometer would normally not be used with standard integrated circuits in electronic systems.
- However, such a circuit might be very useful in specialized test equipment.



9.7.3 Difference Amplifier and **Bridge Circuit** Design

- A **transducer** is:
 - A device that **transforms** one form of energy into another form.
- One type of transducer **uses** nonelectrical inputs **to produce** electrical outputs.
- For example:
 - A **microphone** **converts** acoustical energy into electrical energy.
 - A **pressure transducer** is a device in which a **resistance is a function of pressure**, so that pressure **can be converted** to an electrical signal.
- Often, the **output characteristics** of these transducers are **measured with a bridge circuit**.

Wheatstone bridge [[Wikipedia](#)]

- A Wheatstone bridge is an **electrical circuit** used to **measure** an **unknown electrical resistance** by **balancing two legs** of a bridge circuit, **one leg** of which **includes** the **unknown component**.
- The primary benefit of a Wheatstone bridge is:
 - Its ability **to provide** extremely accurate measurements (in contrast with something like a **simple voltage divider**).
- Its operation is similar to the original potentiometer.

9.7.3 Difference Amplifier and Bridge Circuit Design

- Figure 9.44 shows a bridge circuit.
 - Resistance R_3 represents the transducer, and
 - Parameter δ is the deviation of R_3 from R_2 due to the input response of the transducer.
 - The output voltage v_{O1} is now a measure of δ .
- Applying voltage divider concept:

$$v_{O1}^+ = \frac{R_3}{R_3 + R_1} V^+$$
$$v_{O1}^- = \frac{R_2}{R_1 + R_2} V^+$$

- Therefore:

$$v_{O1} = v_{O1}^+ - v_{O1}^-$$

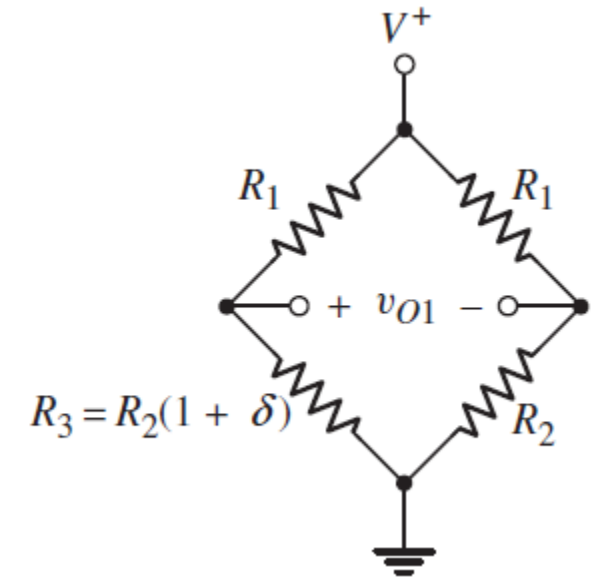


Figure 9.44

9.7.3 Difference Amplifier and Bridge Circuit Design

- If v_{O1} is an open-circuit voltage, then:

$$v_{O1} = v_{O1}^+ - v_{O1}^-$$

$$v_{O1} = \left[\frac{R_2(1 + \delta)}{R_2(1 + \delta) + R_1} - \frac{R_2}{R_1 + R_2} \right] V^+$$

$$v_{O1} = \frac{R_1R_2 + R_2^2 + \delta R_1R_2 + \delta R_2^2 - R_2^2 - \delta R_2^2 - R_1R_2}{\delta R_2(R_1 + R_2) + (R_1 + R_2)^2} V^+$$

$$v_{O1} = \frac{\delta R_1R_2}{\delta R_2(R_1 + R_2) + (R_1 + R_2)^2} V^+$$

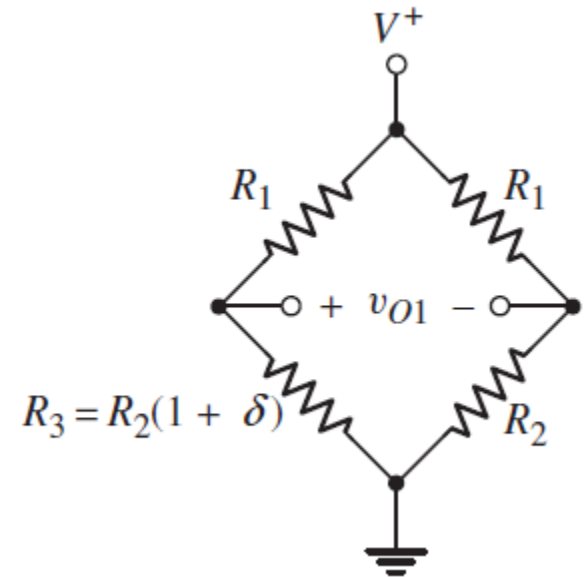


Figure 9.44

9.7.3 Difference Amplifier and Bridge Circuit Design

$$v_{O1} = \frac{\delta R_1 R_2}{\delta R_2 (R_1 + R_2) + (R_1 + R_2)^2} V^+$$

Reduces to:

$$v_{O1} = \delta \left(\frac{R_1 \parallel R_2}{R_1 + R_2} \right) V^+$$

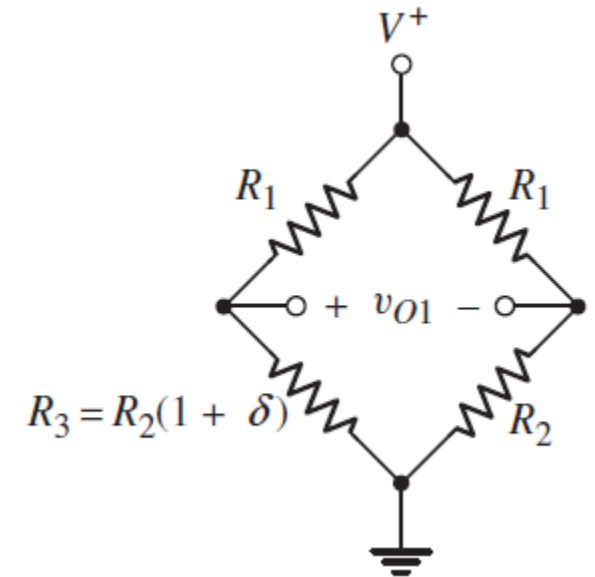


Figure 9.44

9.7.3 Difference Amplifier and Bridge Circuit Design

$$v_{O1} = \delta \left(\frac{R_1 \parallel R_2}{R_1 + R_2} \right) V^+$$

- Since neither side of voltage v_{O1} is at ground potential, we must connect v_{O1} to an **instrumentation amplifier**.
- In addition, v_{O1} is directly proportional to supply voltage V^+ ; therefore, **this bias should be a well-defined voltage reference**.

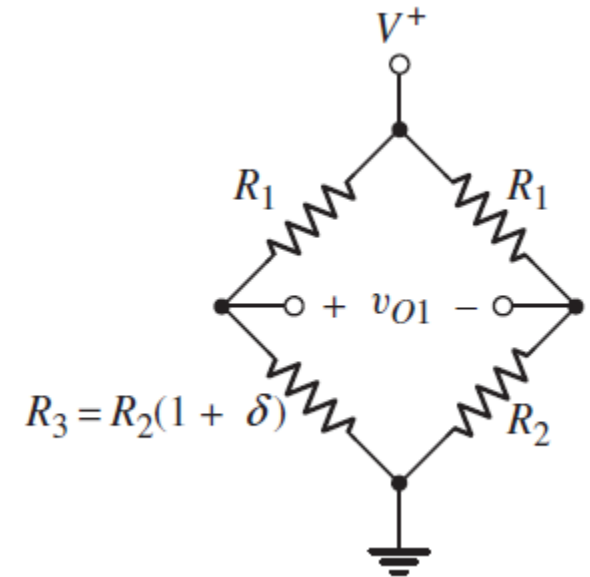


Figure 9.44

DESIGN EXAMPLE 9.12

- **Objective:** Design an amplifier system that will produce an output voltage of $\pm 5V$ when the resistance R_3 deviates by $\pm 1\%$ from the value of R_2 .
- This would occur, for example, in a system where R_3 is a thermistor whose resistance is given by:


$$R_3 = 200 \left[1 + \frac{(0.040)(T - 300)}{300} \right] k\Omega$$

- Where T is the absolute temperature.
- For R_3 to vary by $\pm 1\%$ means the temperature is in the range:
 $225 \leq T \leq 375K \rightarrow -48 \leq T \leq 102^\circ C$
- Consider biasing the bridge circuit at $V^+ = 7.5V$ using a $5.6V$ Zener diode.
- Assume $\pm 10V$ is available for biasing the op-amp and reference voltage source, and that $R_1 = R_2 = 200 k\Omega$.



Home Work #1

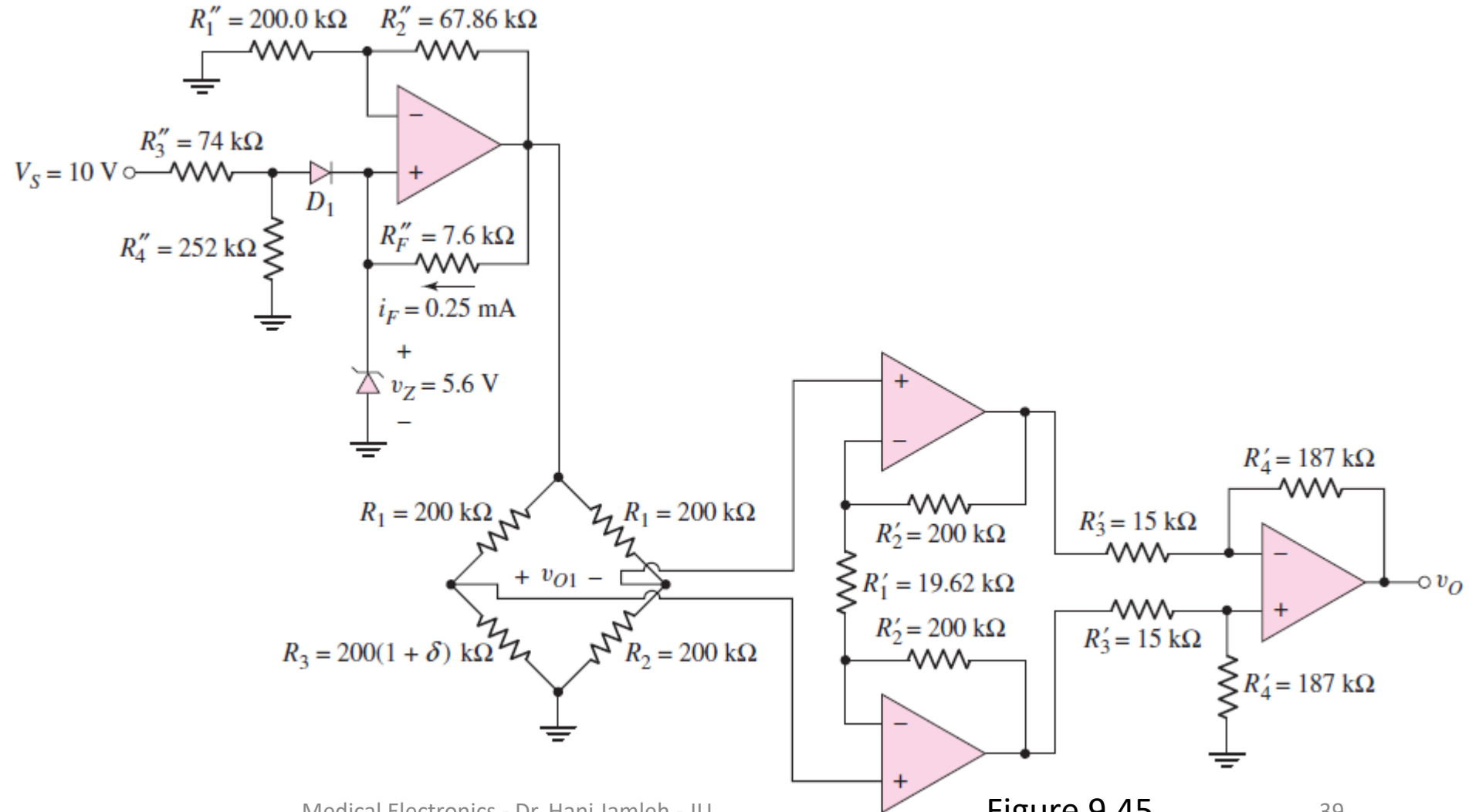- Simulate the circuit shown in Figure 9.45 using **Multisim**.
- See DESIGN EXAMPLE 9.12 in Microelectronics Book by Neamen 4th ed.



9.5.5 Integrator and Differentiator

- In the op-amp circuits previously considered, the elements exterior to the op-amp have been **resistors**.
 - Other elements can be used, with differing results.
- Figure 9.29 shows a **generalized inverting amplifier** for which the voltage transfer function has the same general form as before:

$$\frac{v_O}{v_I} = -\frac{Z_2}{Z_1}$$

- where Z_1 and Z_2 are **generalized impedances**.
- Two special circuits can be developed from this generalized inverting amplifier :
 - Integrator and
 - Differentiator.

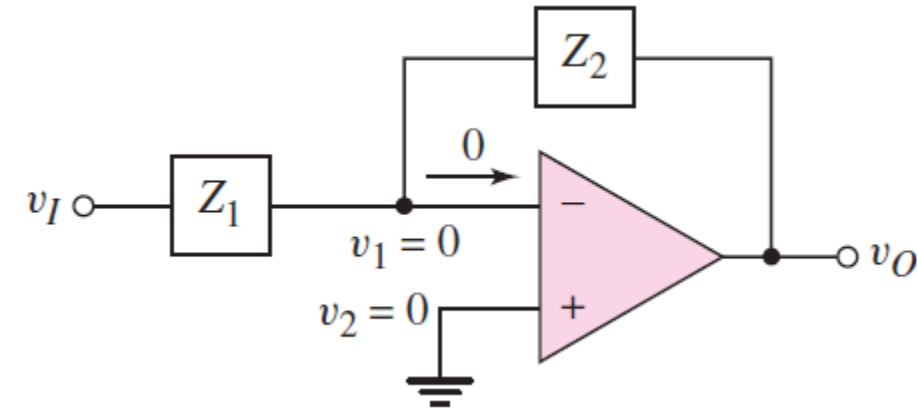


Figure 9.29

Op-amp integrator

- Low Pass Filter


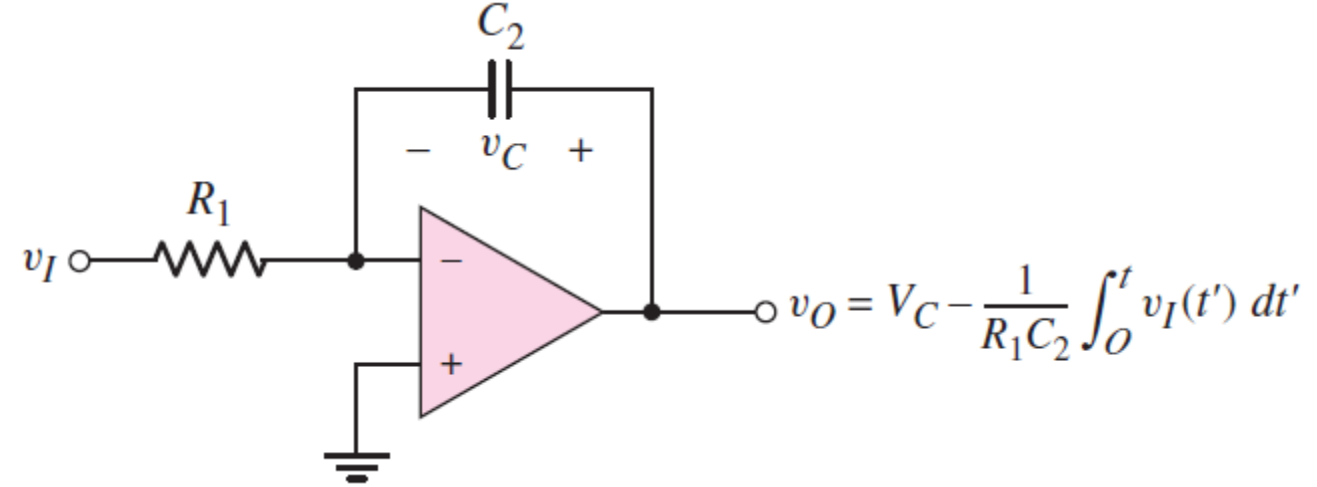


Figure 9.30

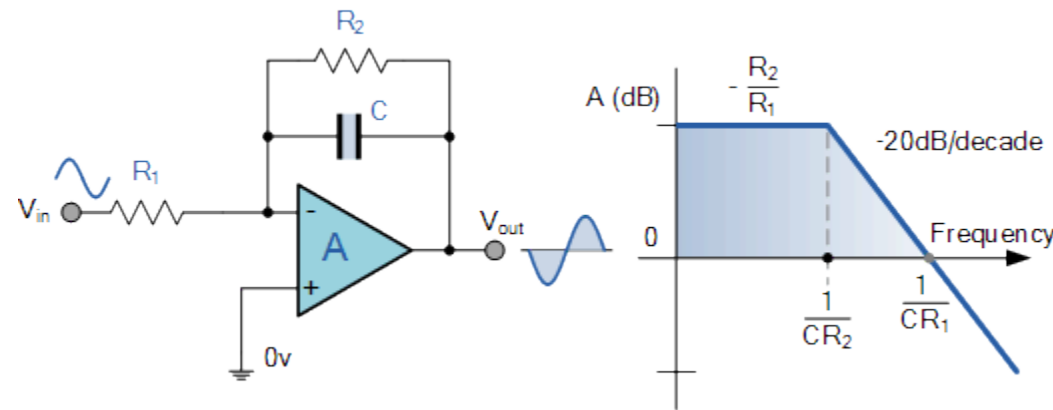

Op-amp differentiator

- High Pass Filter

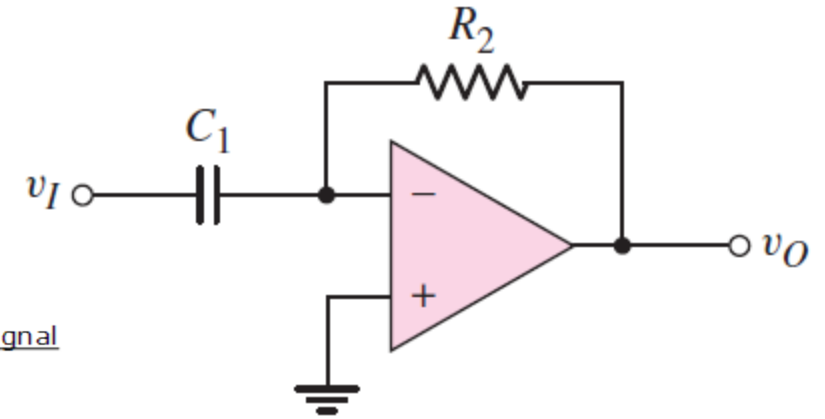


Figure 9.31

