

# L05

## Practical *Operational Amplifiers*

### *Op-Amps 1*

Chapter 14

Nonideal Effects in Operational Amplifier

Circuits *Donald A. Neamen (2009). **Microelectronics: Circuit Analysis and Design**,  
4th Edition, Mc-Graw-Hill*

**Prepared by:** Dr. Hani Jamleh, *School of Engineering, The University of Jordan*

# 14.1.1 Practical Op-Amp Parameter Definitions: *Input voltage limits*

- Two **input voltage limitations** must be considered:
  - A DC input voltage limit and
  - A differential signal input voltage.
- All transistors in the input diff-amp stage **must be properly biased**
  - So there is a **limit** in the range of **common-mode input voltage** that can be applied and still maintain the proper transistor biasing.
- The **maximum differential input signal voltage** that can be **applied** and still **maintain linear circuit operation**.
  - Is limited primarily by the **maximum allowed output signal voltage**.

# 14.1.1 Practical Op-Amp Parameter Definitions: Output voltage limits

- The output voltage of the op-amp can **never exceed** the **limits** of the DC supply voltages.
- In **practice**, the difference between the bias voltage and the maximum output voltage depends on the design of the output stage.
  - In **older designs**, this difference was on the order of **1 to 2 volts**.
    - In **newer designs**, this difference can be on the order of **millivolts**.
- If  $V_{out} = A_v \cdot V_{in}$  (where  $A_v$  is the overall voltage gain) is greater than the bias voltage, then:
  1. The **output voltage** **would saturate** and
  2.  $V_{out}$  is **no longer a linear function** of the input voltage.

# 14.1.1 Practical Op-Amp Parameter Definitions: Output current limitation

- The **maximum current** out of or into the op-amp is **determined** by the **current ratings** of the output transistors.
  - **Practical** op-amp circuits cannot source or sink an infinite amount of current.

## 14.1.1 Practical Op-Amp Parameter Definitions: *Finite open-loop voltage gain*

- The **open-loop gain**,  $A_{od}$ , of the **ideal** op-amp is assumed to be **infinite**.
- In **practice**, the open-loop gain of any op-amp circuit is **always finite**.
  - This nonideal parameter value will **affect** circuit performance.

# 14.1.1 Practical Op-Amp Parameter Definitions: *Input resistance*

- The **input resistance**.
  - Is the small-signal resistance between the inverting and noninverting terminals when a differential voltage is applied.
- **Ideally**, this parameter is infinite.
- **Practically** and **especially for BJT circuits**, this parameter is **finite**.

# 14.1.1 Practical Op-Amp Parameter Definitions: *Output resistance*

- The **output resistance** is the Thevenin equivalent small-signal resistance looking back into the output terminal of the op-amp measured with respect to ground.
- The **ideal** output resistance is *zero*, which **means** there is **no loading effect** at the output.
- In **practice**, this value is *not zero*.

# 14.1.1 Practical Op-Amp Parameter Definitions: *Finite bandwidth*

- In the **ideal** op-amp, the bandwidth is **infinite**.
- In **practical** op-amps, the bandwidth is **finite**.
  - Because of **capacitances** within the op-amp circuit.






# 14.1.1 Practical Op-Amp Parameter Definitions: *Slew rate*

- The slew rate is defined as:
  - The maximum rate of change in output voltage per unit of time, due to limited current sink or source.

$$SR = \max \left( \left| \frac{\partial V_o(t)}{\partial t} \right| \right)$$

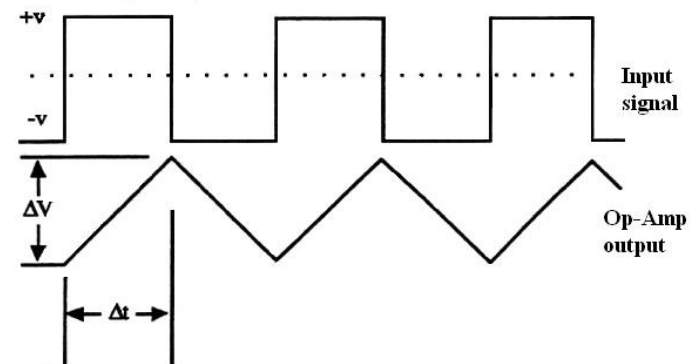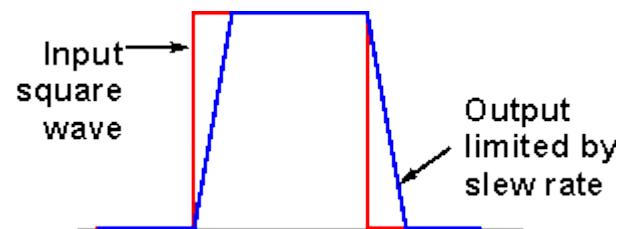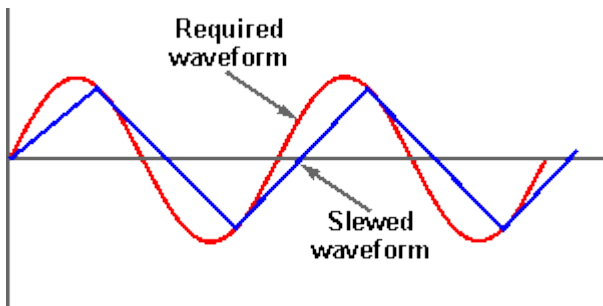- The maximum rate at which the output voltage can change.
  - It is also a function of capacitances within the op-amp circuit.




# 14.1.1 Practical Op-Amp Parameter Definitions: *Slew rate*

- If a node in a circuit where the load is capacitive-dominant, i.e., the load is mostly made of a capacitance  $C$  (although there is always some very large parallel resistance  $R$ ).
- So that all current  $I$  entering the load will flow to the capacitor and none to the resistance.
  - Then, the rate of voltage change across the capacitor is defined by:

$$\frac{dV_o}{dt} = \frac{I}{C}$$

- If the current being sourced to this load is limited at  $I_{max}$ , the maximum voltage change per unit time is:

$$SR = \max \left( \left| \frac{\partial V_o}{\partial t} \right| \right) = \frac{I_{max}}{C}$$

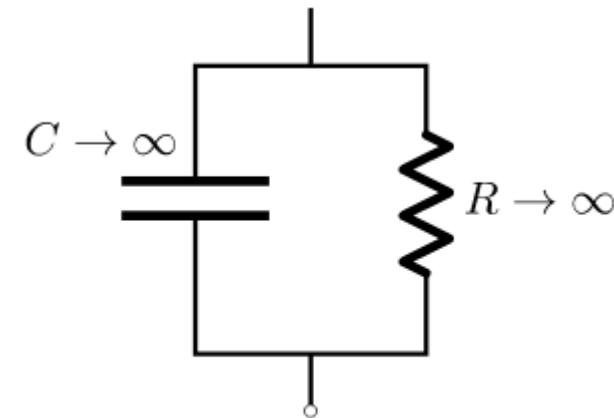

C-dominant load

## 14.1.1 Practical Op-Amp Parameter Definitions: *Slew rate of a Sinusoidal waveform*


$$SR = \max \left( \left| \frac{\partial V_o}{\partial t} \right| \right) = \frac{I_{max}}{C}$$

- To avoid distortion of an output signal.
  - The circuit must be designed so that output node has a **Slew-Rate** higher than the highest slope of the output signal.
- Let the output has the highest sinusoidal as a function of frequency  $f$ :

$$V_o(t) = V_p \cdot \sin(2\pi ft)$$
$$\frac{\partial V_o}{\partial t} = V_p \cdot 2\pi f \cdot \cos(2\pi ft)$$

- The highest slope is when the cosine is 1, therefore:

$$SR \geq 2\pi f V_p$$

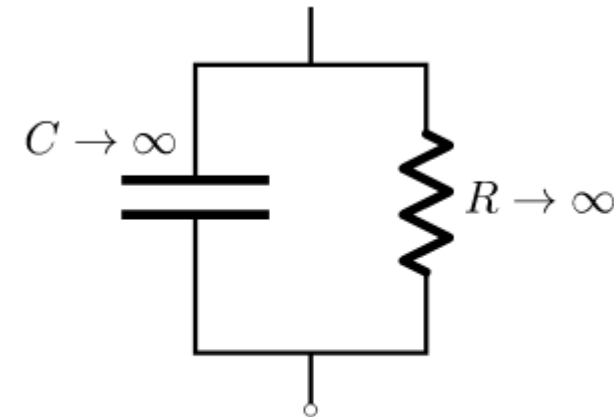

C-dominant load

Source: <http://www.onmyphd.com/?p=slew.rate>

# 14.1.1 Practical Op-Amp Parameter Definitions: *Slew rate*

- In amplifiers, limitations in slew rate capability, can give rise to **non-linear effects**.
- For a sinusoidal waveform not to be **subject to** slew rate limitation, the **slew rate capability** (in volts per second) at all points in an amplifier **must satisfy** the following **condition**:

$$SR \geq 2\pi f V_p$$

- Where:
  - $f$  is the operating frequency, and
  - $V_p$  is the peak amplitude of the waveform.

# 14.1.1 Practical Op-Amp Parameter Definitions: *Slew rate*

- Slew rate **helps** us identify:
  - The maximum **input frequency** and
  - The maximum **input amplitude**

applicable to the amplifier such that the **output** is **not significantly distorted**.

- Thus it **becomes** imperative to **check** the **datasheet** for the device's slew rate before using it **for high-frequency applications**.

Part of LM741 Datasheet


Electrical Characteristics (Note 5) (Continued)											
Parameter	Conditions	LM741A			LM741			LM741C			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Slew Rate	T <sub>A</sub> = 25°C, Unity Gain	0.3	0.7			0.5			0.5		V/μs

LM741


# 14.1.1 Practical Op-Amp Parameter

## *Slew rate*

**Circuit with  $SR = 15V/s$**

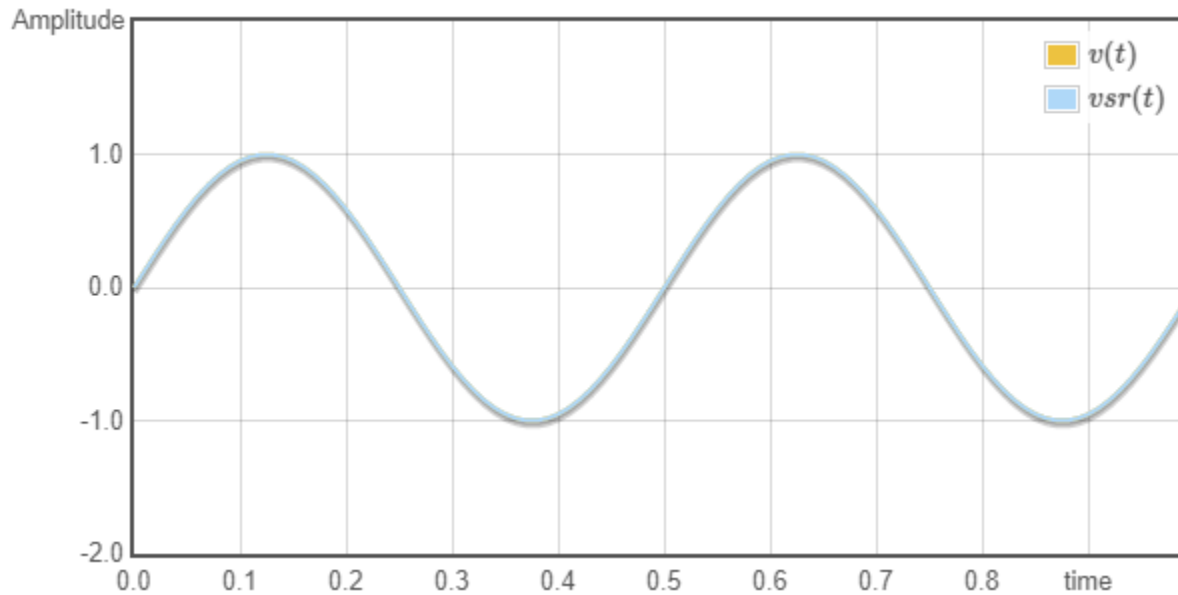

**Circuit with  $SR = 5V/s$**

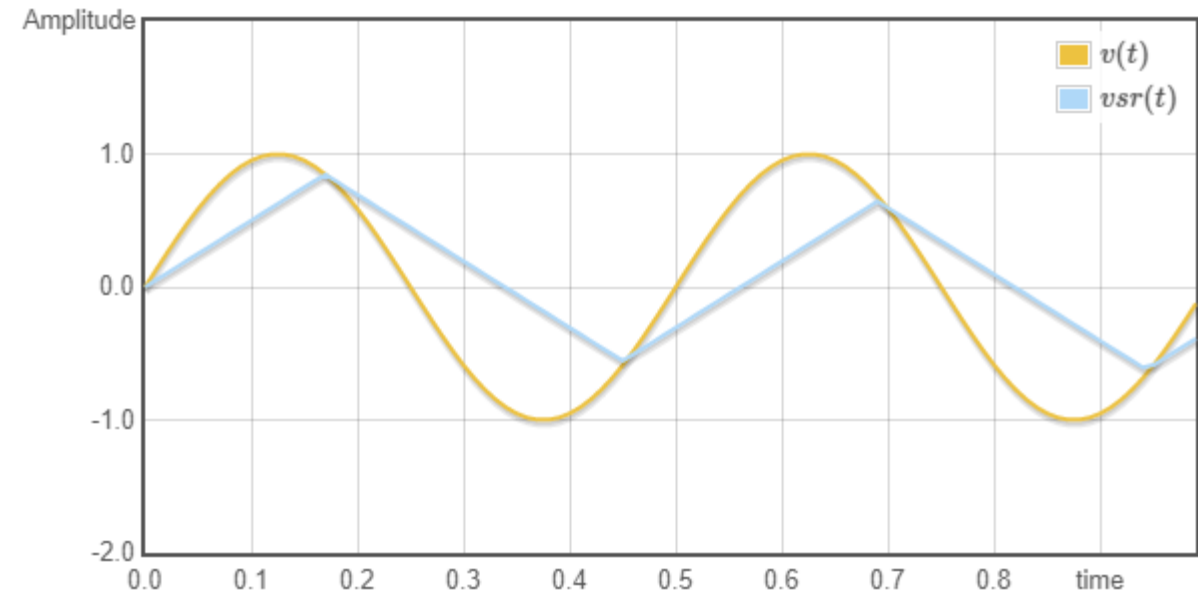

Source: <http://www.onmyphd.com/?p=slew.rate>

# Slew Rate Testing Conditions for 741

operating conditions,  $V_{CC} = \pm 15 \text{ V}$ ,  $T_A = 25^\circ\text{C}$

PARAMETER		TEST CONDITIONS	TYP	UNIT
SR	Slew rate at unity gain	$R_L = 1 \text{ M}\Omega$ , $C_L = 30 \text{ pF}$ , $V_I = \pm 10 \text{ V}$ (see Figure 1)	0.5	$\text{V}/\mu\text{s}$
$B_1$	Unity-gain bandwidth	$R_L = 1 \text{ M}\Omega$ , $C_L = 20 \text{ pF}$ (see Figure 1)	1.2	MHz
$V_n$	Equivalent input noise voltage	$R_S = 100 \Omega$ , $V_I = 0 \text{ V}$ , $f = 1 \text{ kHz}$ (see Figure 2)	35	$\text{nV}/\sqrt{\text{Hz}}$


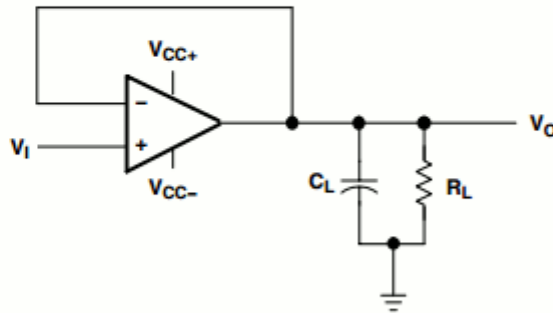


Figure 1. Unity-Gain Amplifier
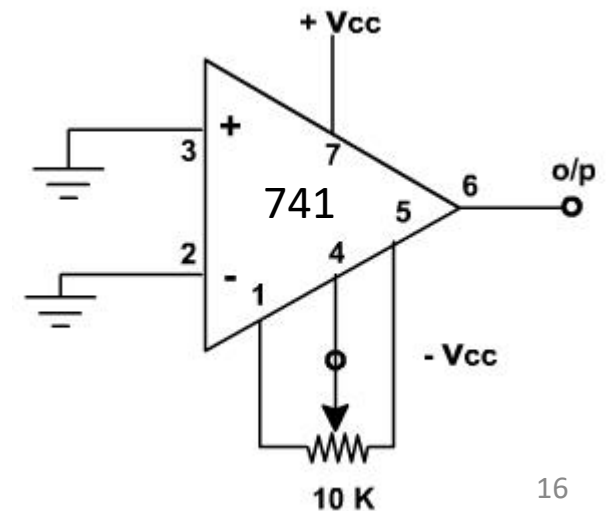
# 14.1.1 Practical Op-Amp Parameter Definitions: *Input offset voltage*

- In an **ideal** op-amp, the output voltage is *zero* for *zero* differential input signal voltage.
- However, **mismatches** between input devices, **may create** a nonzero output voltage with *zero* input.
- The **input offset voltage** is the **applied** differential input voltage **required to induce a zero output voltage**.





# 14.1.1 Practical Op-Amp Parameter Definitions: *Input bias currents*

- In an **ideal** op-amp, the input bias DC current to the op-amp circuit is assumed to be *zero*.
- In **practical** op-amps, especially with BJT input devices, the **input bias currents** are *not zero*.

## 14.6.2 Common-Mode Rejection Ratio

- The ability of a differential amplifier to **reject** a **common-mode signal** is **described** in terms of the common-mode rejection ratio (CMRR).
  - The CMRR is a figure of merit for the diff-amp.
- Figure 14.30(a) shows the open-loop op-amp with a pure differential-mode input signal.
- The differential-mode gain  $A_d$  is the same as the open-loop gain  $A_{OL}$ .
- Figure 14.30(b) shows the open-loop op-amp with a pure common-mode input signal.

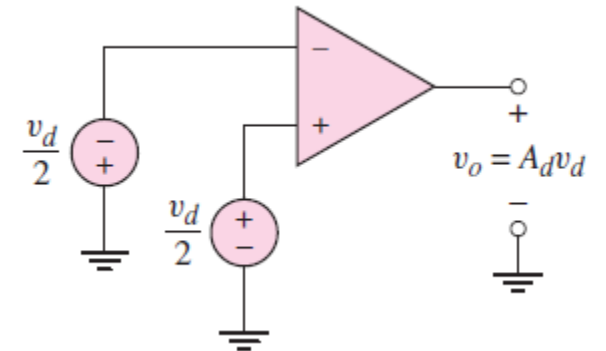


Figure 14.30(a)

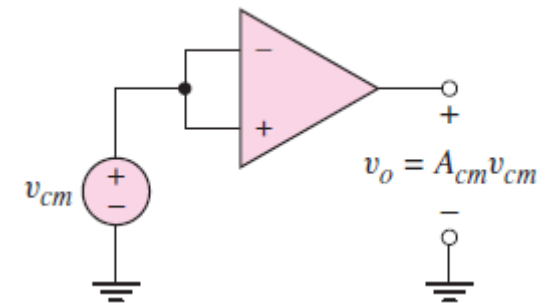


Figure 14.30(b)

## 14.6.2 Common-Mode Rejection Ratio

- The common-mode rejection ratio, in dB, is:

$$CMRR_{dB} = 20 \cdot \log_{10} \left| \frac{A_d}{A_{cm}} \right|$$

- For an ideal diff-amp,  $A_{cm} = 0$  and  $CMRR = \infty$ .
- Typical values of  $CMRR_{dB}$  range from 80 to 100 dB.
- The common-mode gain decreases as  $R_o$  increases and vice versa.

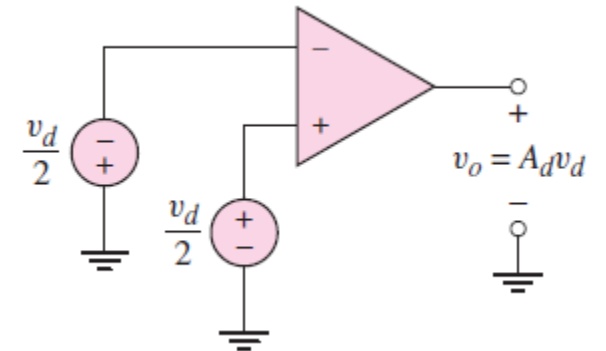


Figure 14.30(a)

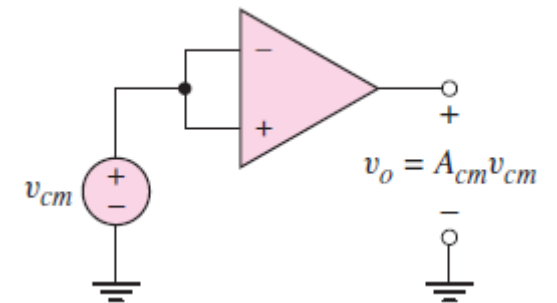


Figure 14.30(b)

# 14.1.1 Practical Op-Amp Parameter Definitions


- We will **discuss** the effects of these nonideal parameters on **op-amp circuit performance**.
- Table 14.1 **lists** a few of the **nonideal parameter values** for three of the op-amps i.e. 741E, CA3140, and LH0042C.
- The output resistance for **741E** is about  $75\Omega$ .

Table 14.1 Nonideal parameter values for three op-amp circuits

	741E			CA3140			LH0042C		
	Typ.	Max.	Unit	Typ.	Max.	Unit	Typ.	Max.	Unit
Input offset voltage	0.8	3	mV	5	15	mV	6	20	mV
Average input offset voltage drift		15	$\mu\text{V}/^\circ\text{C}$				10		$\mu\text{V}/^\circ\text{C}$
Input offset current	3.0	30	nA	0.5	30	pA	2		pA
Average input offset current drift		0.5	$\text{nA}/^\circ\text{C}$						
Input bias current	30	80	nA	10	50	pA	2	10	pA
Slew rate	0.7		$\text{V}/\mu\text{s}$	9		$\text{V}/\mu\text{s}$	3		$\text{V}/\mu\text{s}$
CMRR	95		dB	90		dB	80		dB


# CA3140, CA3140A

## Block Diagram

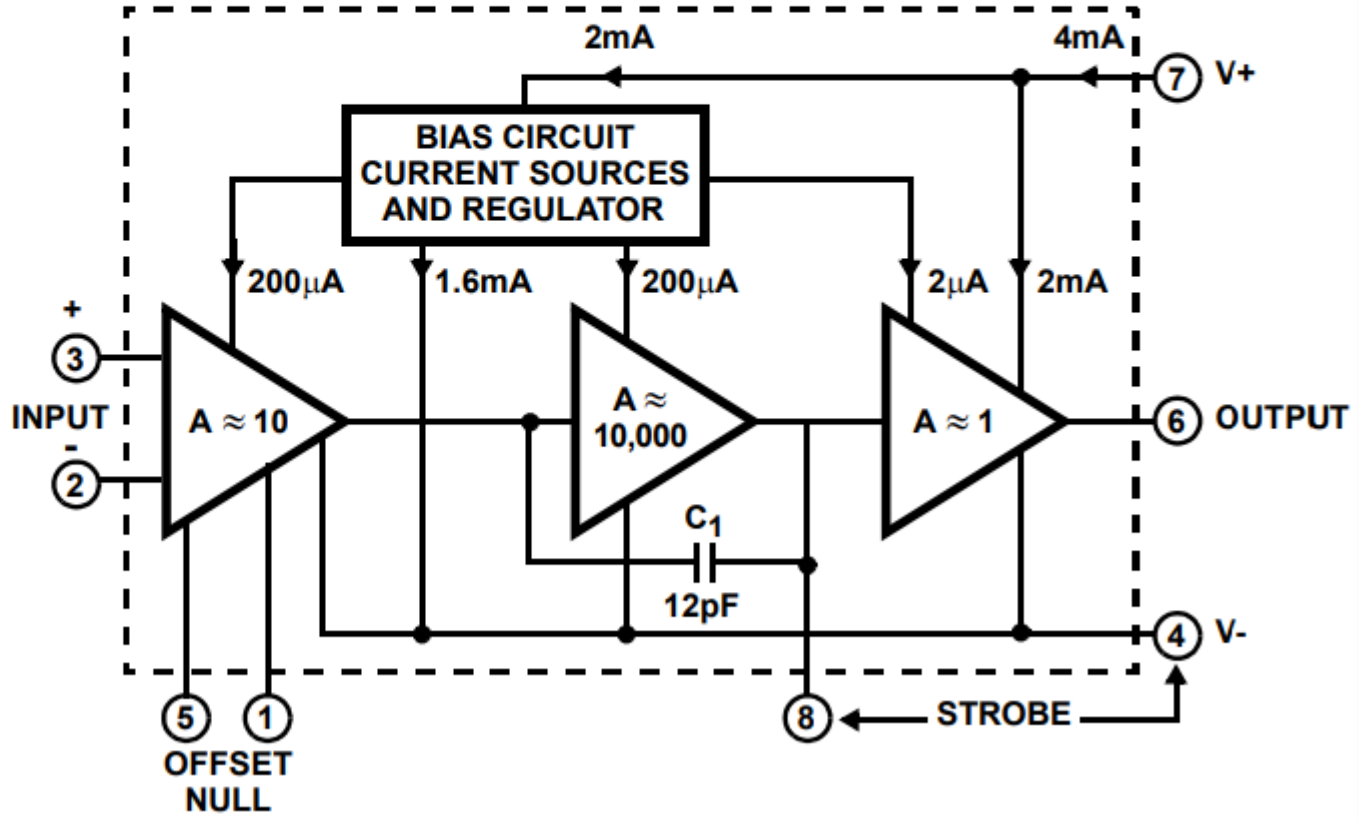

# Schematic Diagram

## CA3140, CA3140A

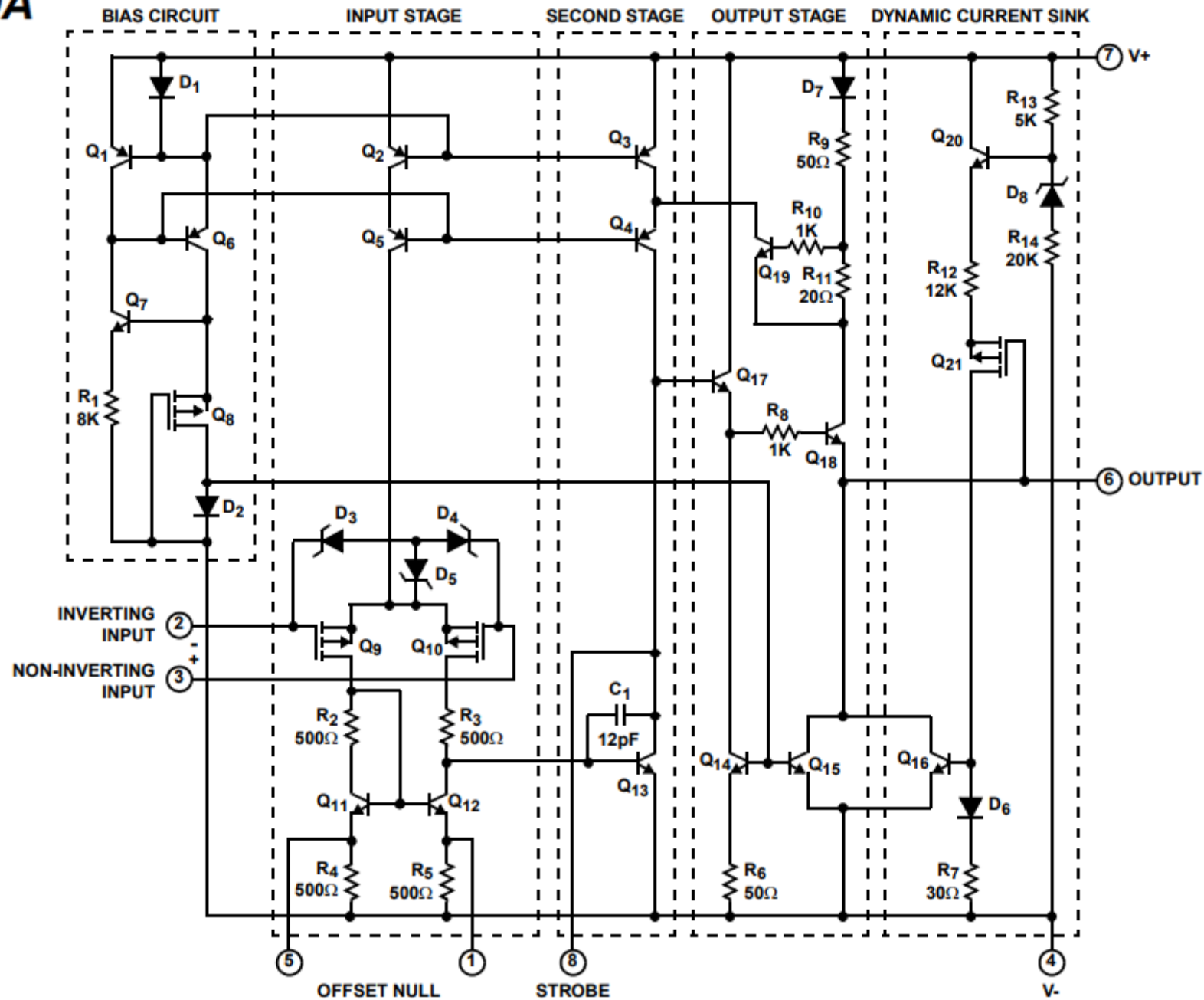

## 14.2 Finite Open-loop Gain $A_{od} \neq \infty$

- **Objective:**

- Analyze the effect of finite open-loop gain.

- In the **ideal** op-amp:

1. The open-loop gain  $A_{od}$  is infinite,
2. The input differential resistance  $R_i$  is infinite, and
3. The output resistance  $R_o$  is *zero*.

- *None of these conditions exists in actual operational amplifiers.*

- But we determined that:

1. The **open-loop gain** may be large but **finite** and
2. The **input differential resistance** may be large but **finite**, and
3. The **output resistance** may be small but ***non – zero***.

## 14.2 Finite Open-loop Gain $A_{od} \neq \infty$

- We will:
  - **Determine** the effect of a finite open-loop gain and input resistance on both the inverting and noninverting amplifier **characteristics**.
  - **Calculate** the output resistance.
  - **Limit** our discussion of the finite open-loop gain to **low frequency**.
  - **Consider** the effect of finite gain, and the frequency response of the amplifier.



# 14.2.1 Inverting Amplifier Closed-Loop Gain

- The equivalent circuit of the inverting amplifier with a finite open-loop gain is shown in Figure 14.2.
- If the **open-loop input resistance is assumed to be infinite**, then:

$$\frac{v_I - v_1}{R_1} = \frac{v_1 - v_O}{R_2}$$
$$\frac{v_I}{R_1} = v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{v_O}{R_2}$$

- Since  $v_2 = 0$ , the output voltage is:
  - $v_O = A_{OL}(v_2 - v_1) = -A_{OL}v_1$
  - where  $A_{OL}$  is the low-frequency open-loop gain.

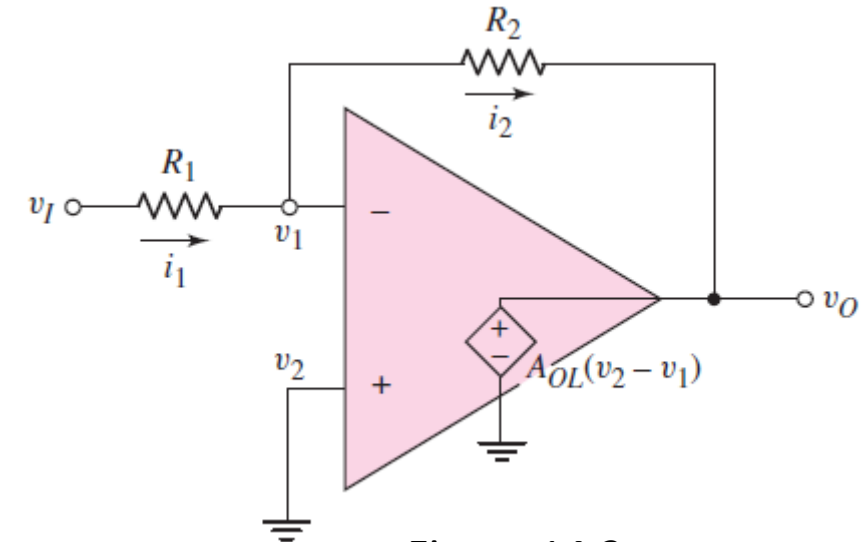


Figure 14.2

# 14.2.1 Inverting Amplifier Closed-Loop Gain

- Solving for  $v_1$  from Equation  $v_O = -A_{OL}v_1$  and substituting the result into Equation:

$$\frac{v_I}{R_1} = v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{v_O}{R_2}$$

- We get:

$$\frac{v_I}{R_1} = - \left( \frac{v_O}{A_{OL}} \right) \left( \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{v_O}{R_2}$$

- The closed-loop voltage gain is then:

$$A_{CL} = \frac{v_O}{v_I} = - \frac{\left( \frac{R_2}{R_1} \right)}{1 + \frac{1}{A_{OL}} \left( 1 + \frac{R_2}{R_1} \right)}$$

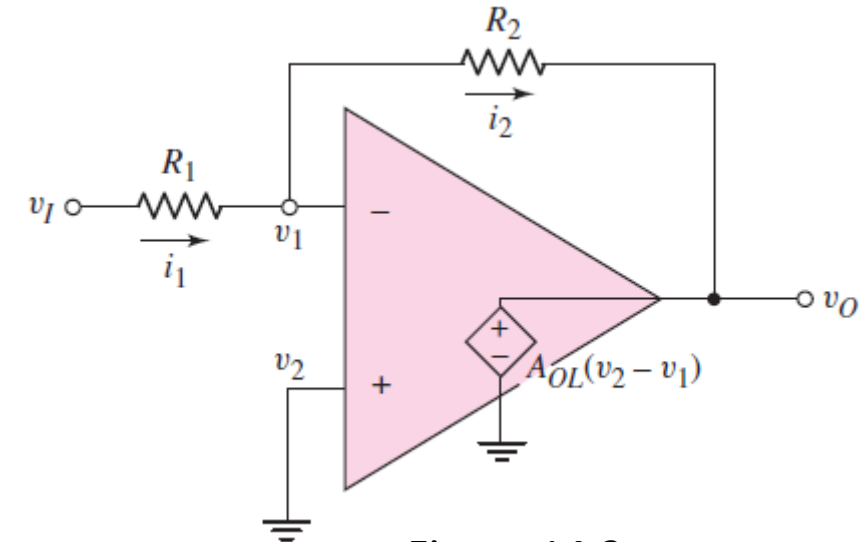


Figure 14.2

## EXAMPLE 9.3

- Consider an inverting op-amp with  $R_1 = 10 \text{ k}\Omega$  and  $R_2 = 100 \text{ k}\Omega$ .
- Determine the closed-loop gain for:  $A_{od} = 10^2, 10^3, 10^4, 10^5$ , and  $10^6$ .
- Calculate the percent deviation from the ideal gain (i.e.  $\infty$ ).

- **Solution:** The ideal closed-loop gain is:

$$A_v = -\frac{R_2}{R_1} = -\frac{100}{10} = -10$$

- If  $A_{od} = 10^2$ , we have, from Equation:

$$A_{CL} = \frac{v_O}{v_I} = -\frac{\left(\frac{R_2}{R_1}\right)}{\left(1 + \frac{1}{A_{OL}} \left(1 + \frac{R_2}{R_1}\right)\right)} = -\frac{\left(\frac{100}{10}\right)}{\left(1 + \frac{1}{10^2} \left(1 + \frac{100}{10}\right)\right)} = -9.01$$

- which is a  $\frac{10-9.01}{10} \times 100 = 9.9\%$  deviation from the ideal.


# EXAMPLE 9.3

- For the other differential gain values we have the following results:

$A_{od}$	$A_v$	Deviation (%)
$10^2$	-9.01	9.9
$10^3$	-9.89	1.1
$10^4$	-9.989	0.11
$10^5$	-9.999	0.01
$10^6$	-9.9999	0.001

- **Comment:**

- For this case, the **open-loop gain** must be on the order of at least  $10^3$  in order to be within **1 percent** of the ideal gain.
- If the ideal closed-loop gain **changes**, a new value of open-loop gain must be **determined** in order to **meet** the specified requirements.
- Usually, **at low frequencies**, most op-amp circuits have **gains on the order of  $A_{od} = 10^5$** , so **achieving** the required accuracy is not difficult.

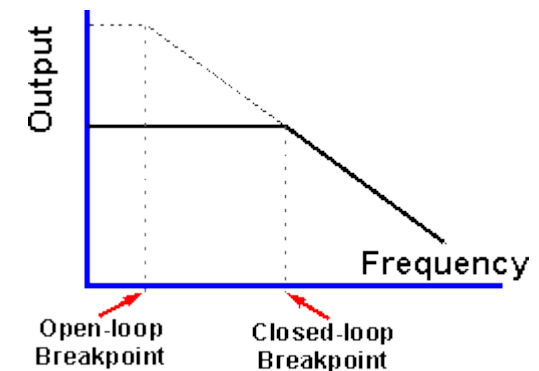

# EXAMPLE 14.1

- **Objective:** Determine the minimum open-loop voltage gain ( $A_{OL}$ ) to achieve a particular accuracy.
- A **pressure transducer:**
  - Produces a maximum DC voltage signal of  $2mV$  and
  - Has an output resistance of  $R_S = 2k\Omega$ .
  - The maximum DC current is to be limited to  $0.2 \mu A$ .
- An **inverting amplifier** is to be used in conjunction with the transducer:
  - To produce an output voltage of  $-0.10V$  for a  $2 mV$  transducer signal.
  - The error in the output voltage cannot be greater than  $0.1 percent$ .
- Determine the minimum open-loop gain of the amplifier to meet this specification.

# EXAMPLE 14.1

- **Solution:** We must first determine the resistor values to be used in the inverting amplifier.
- The source resistor is in series with  $R_1$ , so let:

$$R'_1 = R_1 + R_S$$

- The minimum input resistance is found from the maximum input current as:

$$R'_1(\text{min}) = \frac{v_i}{i_i(\text{max})} = \frac{2 \times 10^{-3}}{0.2 \times 10^{-6}} = 10 \times 10^3 = 10 \text{ k}\Omega$$

- The resistor  $R_1$  then:

$$R_1 = R'_1 - R_S = 10\text{k}\Omega - 2\text{k}\Omega = 8\text{k}\Omega$$

# EXAMPLE 14.1

- The closed-loop voltage gain **required** is:

$$A_{CL} = \frac{v_O}{v_i} = -\frac{0.10}{2 \times 10^{-3}} = -50 = -\frac{R_F}{R'_1}$$

- The **required** value of the feedback resistor is:

$$R_F = A_{CL} \times R'_1 = 50 \times 10k = 500k\Omega$$

- For the voltage gain to be within 0.1 percent, the **minimum gain** is:

$$A_{CL} = 50 - (50 * 0.001) = 49.95$$

- We can **determine** the minimum value of the **open-loop gain** from:

$$A_{CL} = \frac{v_O}{v_I} = -\frac{\left(\frac{R_F}{R'_1}\right)}{\left(1 + \frac{1}{A_{OL}} \left(1 + \frac{R_F}{R'_1}\right)\right)} = -49.95 = -\frac{\left(\frac{500k}{10k}\right)}{\left(1 + \frac{1}{A_{OL}} \left(1 + \frac{500k}{10k}\right)\right)}$$

- Which **yields**  $A_{OL}(\text{min}) = 50,949$ .

# EXAMPLE 14.1

- **Comment:**

- If the  $A_{OL}$  is **greater** than the value of  $A_{OL}(\text{min}) = 50,949$ , then the error in the voltage gain will be less than 0.1%.



# Exercise: Ex 14.1

- Consider an **inverting amplifier** in which the op-amp open-loop gain is  $A_{OL} = 2 \times 10^5$  and the ideal closed-loop amplifier gain is  $A_{CL}(\infty) = -40$ .
  - a) Determine the actual closed-loop gain.
  - b) Repeat part (a) if the open-loop gain is  $A_{OL} = 5 \times 10^4$ .
  - c) What is the **percent change** between the magnitudes of the actual gains from part (a) to part (b)?

# Exercise: Ex 14.1

$$a) A_{CL} = \frac{v_O}{v_I} = - \frac{\left(\frac{R_F}{R_1}\right)}{\left(1 + \frac{1}{A_{OL}} \left(1 + \frac{R_F}{R_1}\right)\right)} = \frac{A_{CL}(\infty)}{\left(1 + \frac{1}{A_{OL}} (1 - A_{CL}(\infty))\right)} = \frac{-40}{1 + \frac{1}{2 \times 10^5} (1 + 40)} = -39.9918$$

$$b) A_{CL} = \frac{v_O}{v_I} = - \frac{\left(\frac{R_F}{R_1}\right)}{\left(1 + \frac{1}{A_{OL}} \left(1 + \frac{R_F}{R_1}\right)\right)} = \frac{A_{CL}(\infty)}{\left(1 + \frac{1}{A_{OL}} (1 - A_{CL}(\infty))\right)} = \frac{-40}{1 + \frac{1}{5 \times 10^4} (1 + 40)} = -39.9672$$

$$c) \text{ Present Change} = \frac{39.9672 - 39.9918}{39.9916} = -0.0615\%$$

## 14.2.1 Inverting Amplifier Closed-Loop Gain

$$A_{CL} = \frac{v_O}{v_I} = - \frac{\left(\frac{R_F}{R_1'}\right)}{\left(1 + \frac{1}{A_{OL}} \left(1 + \frac{R_F}{R_1'}\right)\right)}$$

- In the limit as  $A_{OL} \rightarrow \infty$ , the closed-loop gain is equal to the ideal value, designated  $A_{CL}(\infty)$ , which for the inverting amplifier is:

$$A_{CL}(\infty) = - \frac{R_2}{R_1}$$

- Then we can write:

$$A_{CL} = \frac{A_{CL}(\infty)}{\left(1 + \frac{1}{A_{OL}} (1 - A_{CL}(\infty))\right)}$$

## 14.2.2 Noninverting Amplifier Closed-Loop Gain

- Figure 14.3 shows the circuit of the noninverting amplifier with a finite open-loop gain  $A_{OL}$ .
- The open-loop input differential resistance is assumed to be infinite.
- We have  $i_1 = i_2$ :

$$-\frac{v_1}{R_1} = \frac{v_1 - v_O}{R_2}$$
$$\frac{v_O}{R_2} = v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

- The output voltage is:
- $$v_O = A_{OL}(v_2 - v_1)$$
- Since  $v_2 = v_I$ , voltage  $v_1$  can be written:

$$v_1 = v_I - \frac{v_O}{A_{OL}}$$

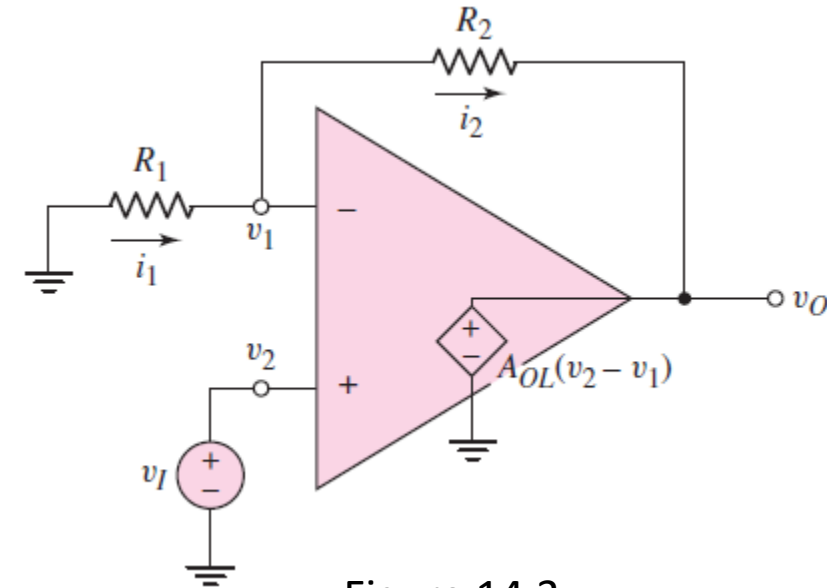


Figure 14.3

## 14.2.2 Noninverting Amplifier Closed-Loop Gain

- **Combining** Equations the following two equations:

$$\frac{v_O}{R_2} = v_1 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$
$$v_1 = v_I - \frac{v_O}{A_{OL}}$$

- **Rearranging** terms, we have an expression for the closed-loop voltage gain:

$$A_{CL} = \frac{v_O}{v_I} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A_{OL}} \left( 1 + \frac{R_2}{R_1} \right)}$$

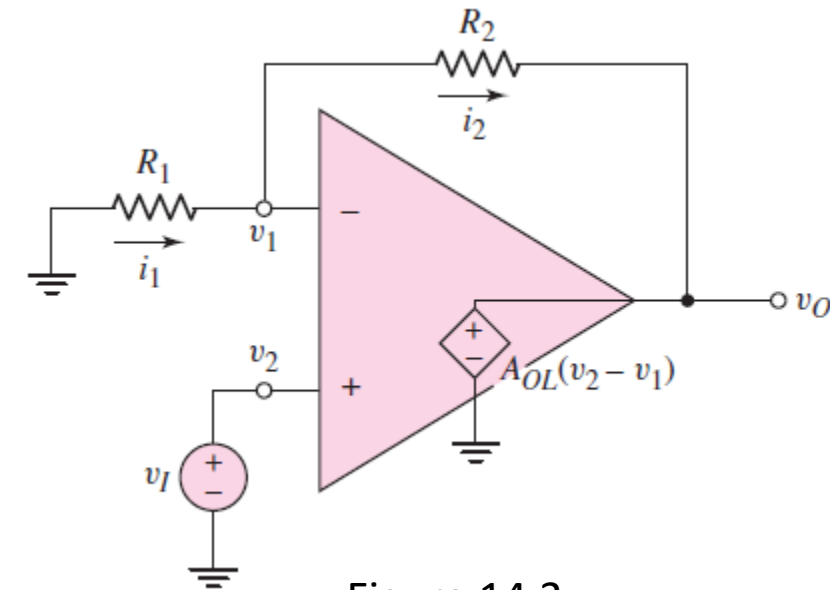


Figure 14.3

## 14.2.2 Noninverting Amplifier Closed-Loop Gain

$$A_{CL} = \frac{v_O}{v_I} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A_{OL}} \left( 1 + \frac{R_2}{R_1} \right)}$$

- In the limit as  $A_{OL} \rightarrow \infty$ , the ideal closed-loop gain is:

$$A_{CL}(\infty) = 1 + \frac{R_2}{R_1}$$

- Then we can write:

$$A_{CL} = \frac{v_O}{v_I} = \frac{A_{CL}(\infty)}{1 + \frac{A_{CL}(\infty)}{A_{OL}}}$$

- The **result** for the noninverting amplifier is very similar to that for the inverting amplifier!

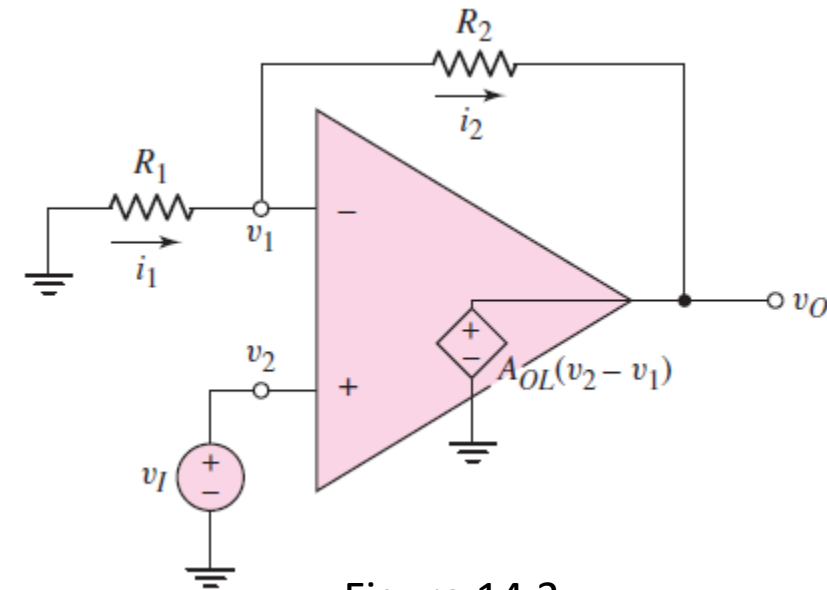


Figure 14.3

# Closed-Loop Gain Comparison

	Inverting Amplifier	Noninverting Amplifier
Closed loop gain	$A_{CL} = \frac{v_O}{v_I} = - \frac{\left(\frac{R_F}{R_1}\right)}{\left(1 + \frac{1}{A_{OL}} \left(1 + \frac{R_F}{R_1}\right)\right)}$	$A_{CL} = \frac{v_O}{v_I} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A_{OL}} \left(1 + \frac{R_2}{R_1}\right)}$
Closed Loop gain assumed $A_{OL} \rightarrow \infty$	$A_{CL}(\infty) = - \frac{R_2}{R_1}$	$A_{CL}(\infty) = 1 + \frac{R_2}{R_1}$
$A_{CL}$ as a function of ideal $A_{CL}(\infty)$	$A_{CL} = \frac{A_{CL}(\infty)}{\left(1 + \frac{1}{A_{OL}} (1 - A_{CL}(\infty))\right)}$	$A_{CL} = \frac{v_O}{v_I} = \frac{A_{CL}(\infty)}{1 + \frac{A_{CL}(\infty)}{A_{OL}}}$