

L06

Practical *Operational Amplifiers*

Op-Amps 2

Chapter 14

Nonideal Effects in Operational Amplifier

Circuits *Donald A. Neamen (2009). **Microelectronics: Circuit Analysis and Design**,
4th Edition, Mc-Graw-Hill*

Prepared by: Dr. Hani Jamleh, *School of Engineering, The University of Jordan*

14.2.3 Inverting Amplifier

Closed-Loop Input Resistance

- The closed-loop **input resistance** R_{if} of the inverting amplifier is defined in Figure 14.4(a).
 - It **includes** the effect of **feedback**.
- The equivalent circuit **includes**:
 1. Finite open-loop gain A_{OL} ,
 2. Finite open-loop input **differential resistance** R_i ,
 3. Nonzero **output resistance** R_o .

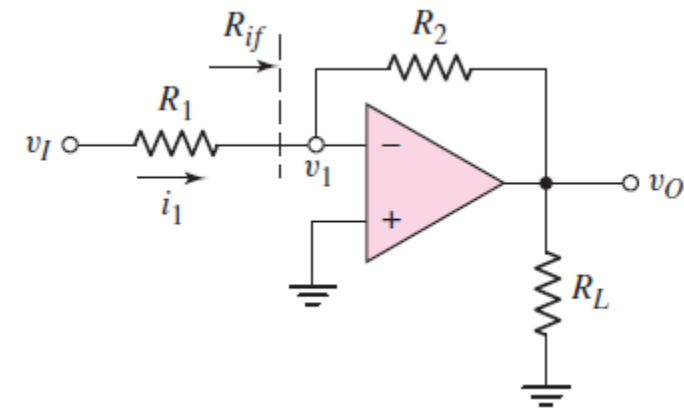


Figure 14.4(a)

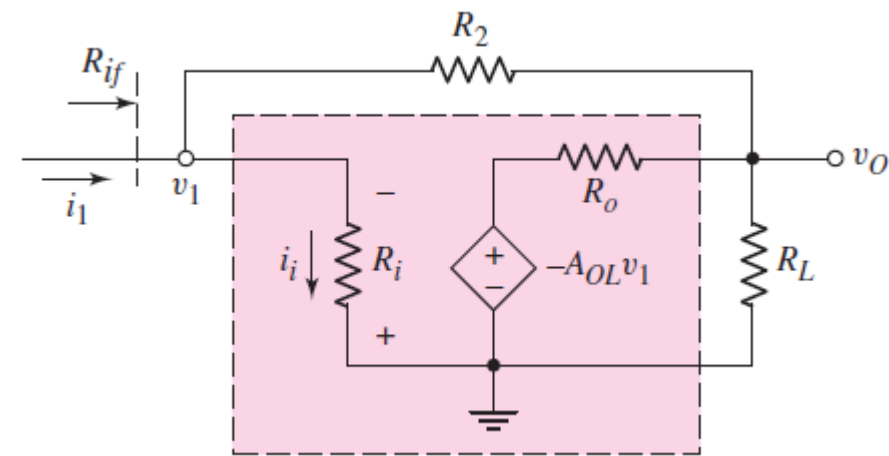


Figure 14.4(b)

14.2.3 Inverting Amplifier Closed-Loop Input Resistance

- A **KCL1** equation at the output node **yields**:

$$\frac{v_o}{R_L} + \frac{v_o - (-A_{OL}v_1)}{R_o} + \frac{v_o - v_1}{R_2} = 0$$

- **Solving** for the output voltage, we have:

$$v_o = \frac{-v_1 \left(\frac{A_{OL}}{R_o} - \frac{1}{R_2} \right)}{\frac{1}{R_L} + \frac{1}{R_o} + \frac{1}{R_2}}$$

- A second **KCL2** equation at the input node **yields**:

$$i_1 = \frac{v_1}{R_i} + \frac{v_1 - v_o}{R_2}$$

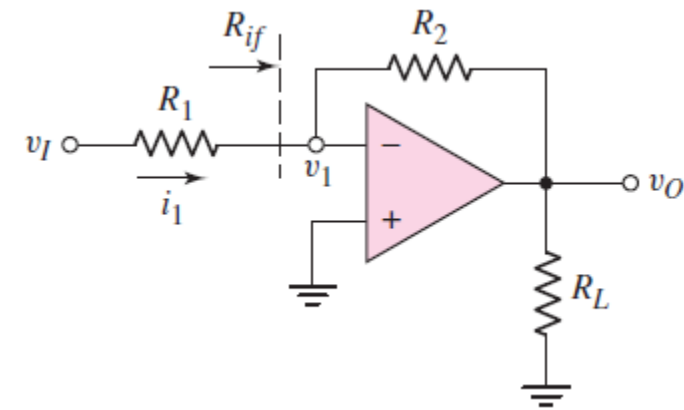


Figure 14.4(a)

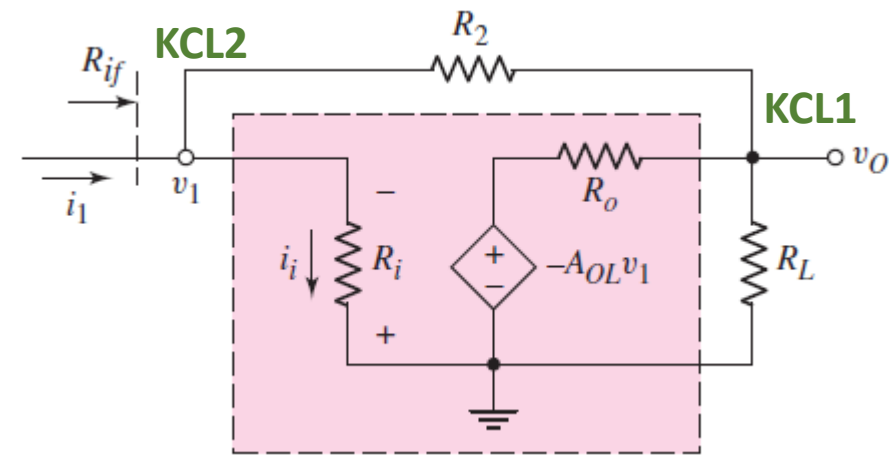


Figure 14.4(b)

14.2.3 Inverting Amplifier Closed-Loop Input Resistance

- Combining the following two equations:

$$v_o = \frac{-v_1 \left(\frac{A_{OL}}{R_o} - \frac{1}{R_2} \right)}{\frac{1}{R_L} + \frac{1}{R_o} + \frac{1}{R_2}}$$

$$i_1 = \frac{v_1}{R_i} + \frac{v_1 - v_o}{R_2}$$

and rearranging terms produces:

$$\frac{i_1}{v_1} = \frac{1}{R_{if}} = \frac{1}{R_i} + \frac{1}{R_2} \frac{\left(1 + A_{OL} + \frac{R_o}{R_L} \right)}{1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}}$$

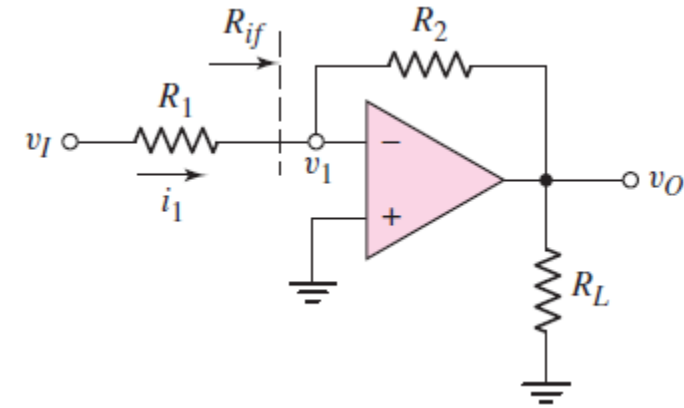


Figure 14.4(a)

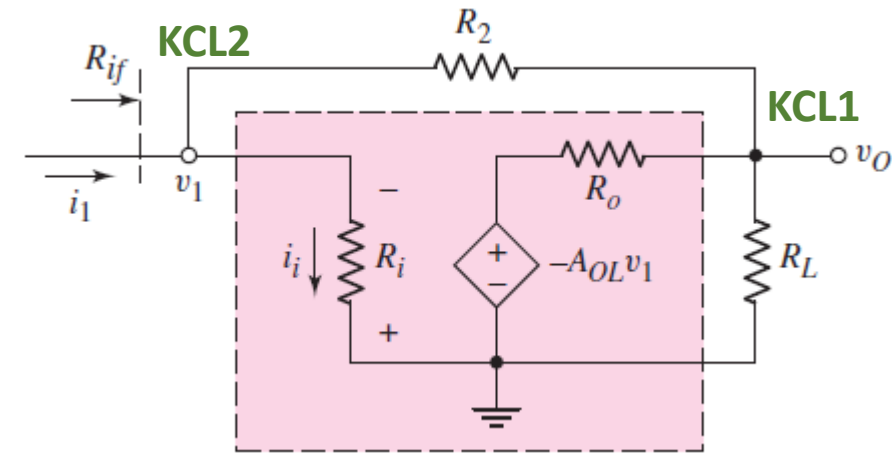


Figure 14.4(b)

14.2.3 Inverting Amplifier Closed-Loop Input Resistance

$$\frac{i_1}{v_1} = \frac{1}{R_{if}} = \frac{1}{R_i} + \frac{1}{R_2} \frac{\left(1 + A_{OL} + \frac{R_o}{R_L}\right)}{1 + \frac{R_o}{R_L} + \frac{R_o}{R_2}}$$

- The equation above describes the closed-loop input resistance R_{if} of the inverting amplifier, with:
 - Finite open-loop gain A_{OL} ,
 - Finite open-loop input resistance R_i , and
 - Nonzero output resistance R_o .
- In the limit as $A_{OL} \rightarrow \infty$, we see that $1/R_{if} \rightarrow \infty$, or $R_{if} \rightarrow 0$.
 - Which means that $v_1 \rightarrow 0$, or v_1 is at virtual ground.
- This is a characteristic of an ideal inverting op-amp.

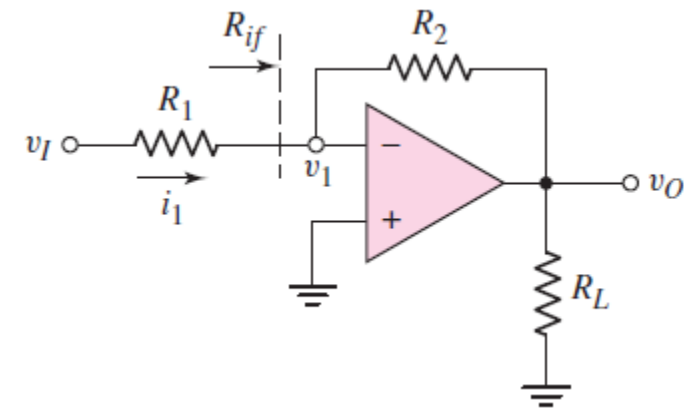


Figure 14.4(a)

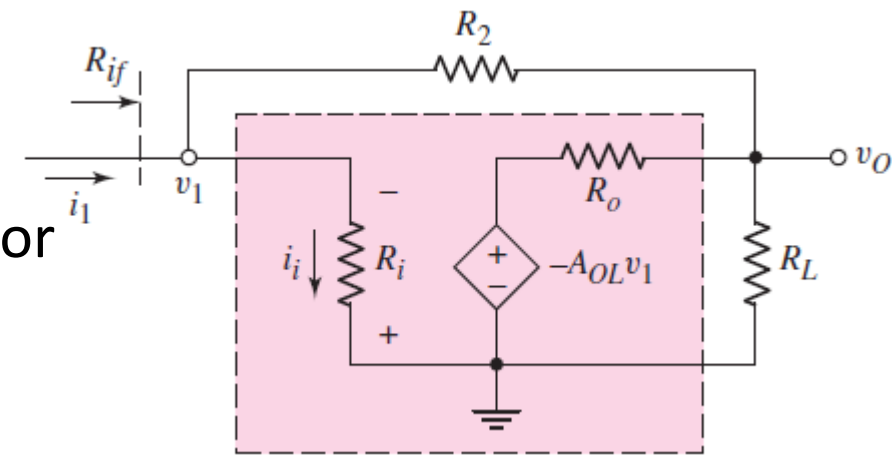


Figure 14.4(b)

EXAMPLE 14.2

- **Consider** an inverting amplifier with a feedback resistor $R_2 = 10k\Omega$, and an op-amp with parameters $A_{OL} = 10^5$ and $R_i = 10k\Omega$.
- **Assume** the output resistance R_o of the op-amp is negligible, e.g. $R_o \rightarrow 0$.
- **Determine** the closed-loop input resistance at the inverting terminal of an inverting amplifier.

- **Solution:** If $R_o = 0$, then:


$$\frac{1}{R_{if}} = \frac{1}{R_i} + \frac{1}{R_2} \frac{\left(1 + A_{OL} + \frac{R_o}{R_L}\right)}{1 + \frac{R_o}{R_i} + \frac{R_o}{R_2}} = \frac{1}{R_i} + \frac{1 + A_{OL}}{R_2} = \frac{1}{10^4} + \frac{1 + 10^5}{10^4} \approx 10^{-4} + 10$$

- The closed-loop input resistance is then $R_{if} \approx 0.1\Omega$.

Comments:

R_{if} of the inverting amplifier is a **very strong function** of the finite open-loop gain A_{OL} .

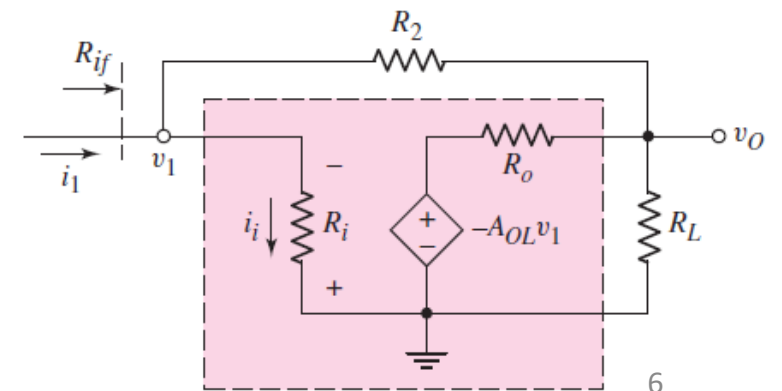R_i essentially **does not affect** the closed-loop input resistance.



14.2.3 Inverting Amplifier

Closed-Loop Input Resistance

- A nonzero R_{if} and a finite R_i implies that:
 - The signal current into the op-amp is not *zero*, as assumed in the ideal case.
- From Figure 14.4(b), we see that:

$$v_1 = i_1 R_{if}$$

- Therefore:

$$i_i = \frac{v_1}{R_i} = i_1 \left(\frac{R_{if}}{R_i} \right)$$

- The fraction of input signal current **shunted away** from R_2 and into the op-amp is (R_{if}/R_i) .
- From the previous example, the fraction is:

$$\frac{R_{if}}{R_i} = \frac{0.1}{10\text{k}} = 10^{-5}!$$

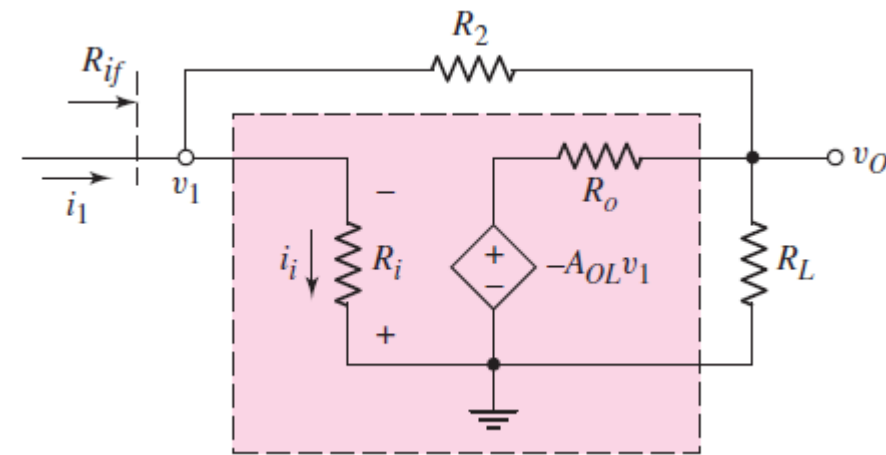


Figure 14.4(b)

14.2.4 Noninverting Amplifier Closed-Loop Input Resistance

- The input resistance seen by the signal source is designated R_{if} .
- The equivalent circuit **includes**:
 1. Finite open-loop gain A_{OL} ,
 2. Finite open-loop input differential resistance R_i ,
 3. Non-zero output resistance R_o .

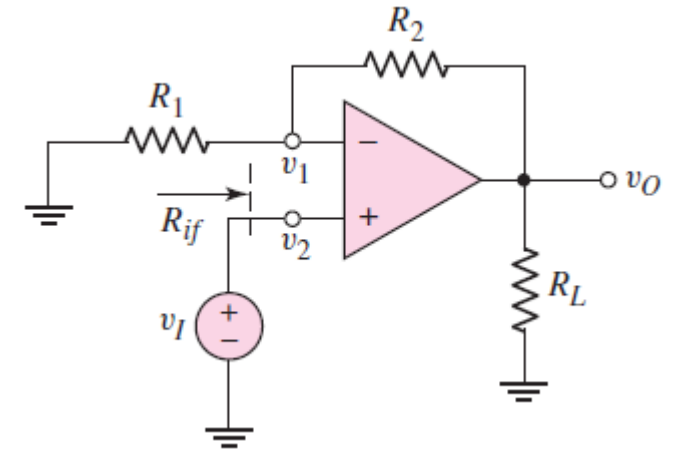


Figure 14.5(a)

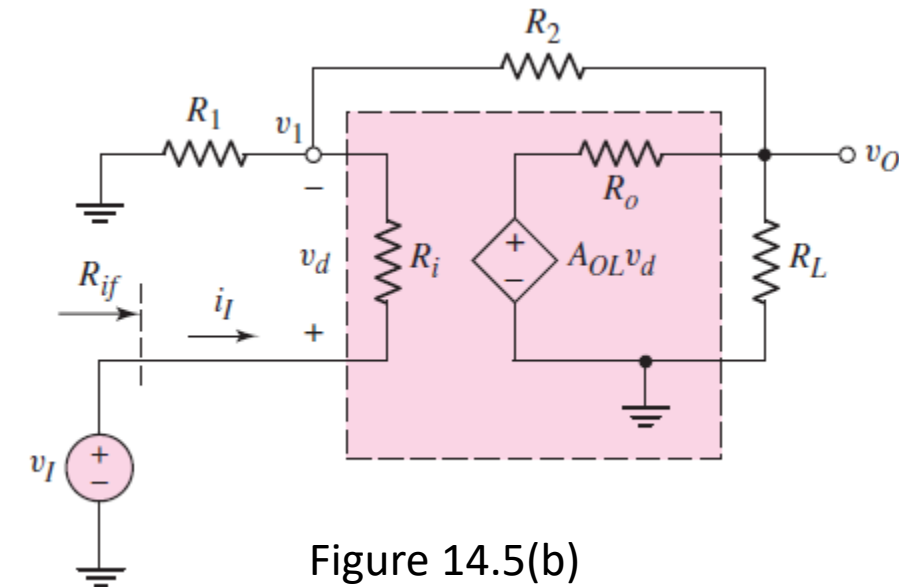


Figure 14.5(b)

14.2.4 Noninverting Amplifier Closed-Loop Input Resistance

- Writing a **KCL1** equation at the output node:

$$\frac{v_O}{R_L} + \frac{v_O - A_{OL}v_d}{R_o} + \frac{v_O - v_1}{R_2} = 0$$

- Solving for the output voltage, we have:

$$v_O = \frac{\frac{v_1}{R_2} + \frac{A_{OL}v_d}{R_o}}{\frac{1}{R_L} + \frac{1}{R_o} + \frac{1}{R_2}}$$

- Another **KCL2** equation at the v_1 node yields:

$$i_I = \frac{v_1}{R_1} + \frac{v_1 - v_O}{R_2}$$


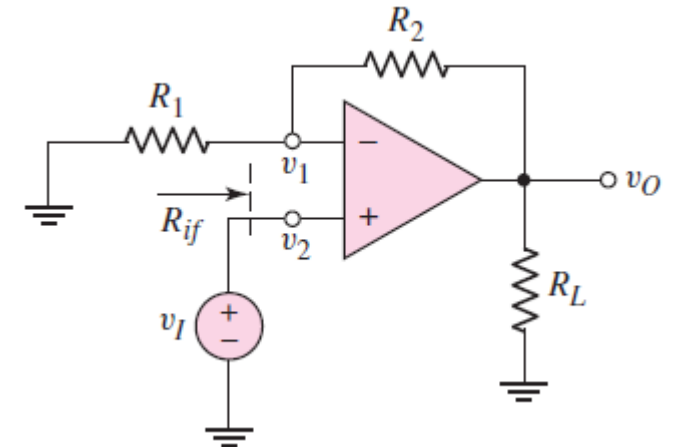


Figure 14.5(a)

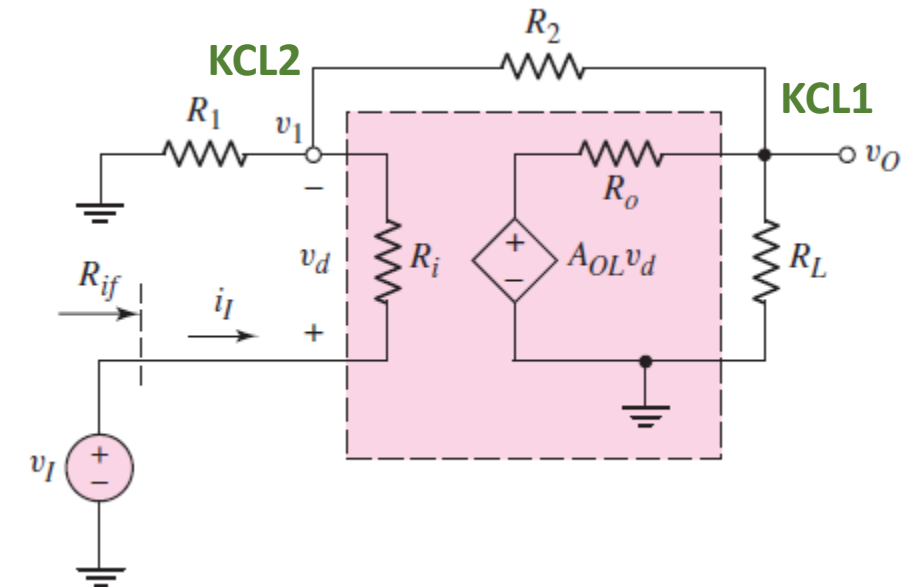

14.2.4 Noninverting Amplifier Closed-Loop Input Resistance

- After substituting equations, we find that R_{if} can be written in the form:

$$R_{if} = \frac{v_I}{i_I} = \frac{R_i(1 + A_{OL}) + R_2 \left(1 + \frac{R_i}{R_1}\right)}{1 + \frac{R_2}{R_1}}$$

- In the limit as $A_{OL} \rightarrow \infty$, or as the $R_i \rightarrow \infty$, we see that $R_{if} \rightarrow \infty$.
 - Which is a property of the ideal noninverting amplifier.

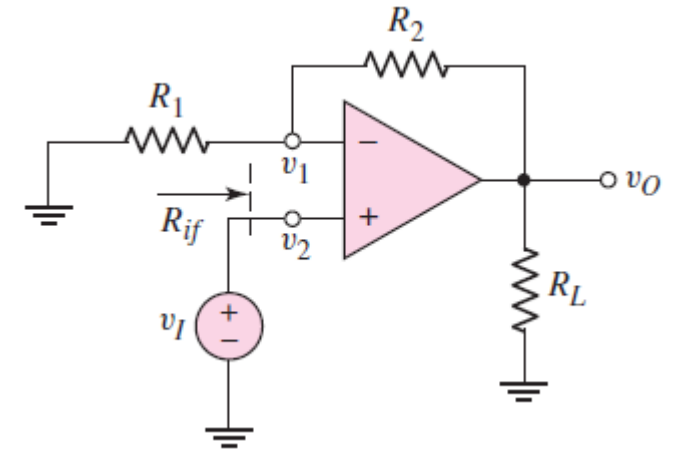


Figure 14.5(a)

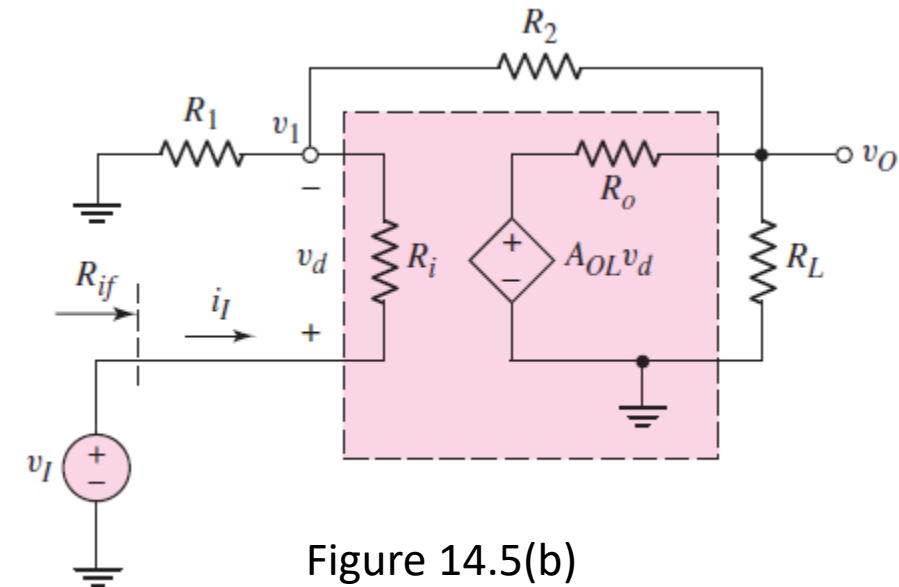


Figure 14.5(b)

EXAMPLE 14.3

- **Consider** an op-amp with an open-loop gain of $A_{OL} = 10^5$ and an input resistance of $R_i = 10k\Omega$ in a noninverting amplifier configuration with resistor values of $R_1 = R_2 = 10k\Omega$.
- **Determine** the closed-loop input resistance at the noninverting terminal of a noninverting amplifier.
- **Solution:** The input resistance is:

$$\bullet R_{if} = \frac{v_I}{i_I} = \frac{R_i(1+A_{OL})+R_2\left(1+\frac{R_i}{R_1}\right)}{1+\frac{R_2}{R_1}} = \frac{10k(1+10^5)+10k\left(1+\frac{10k}{10k}\right)}{1+\frac{10k}{10k}} \approx 500M\Omega$$

EXAMPLE 14.3

$$R_{if} \approx 500M\Omega$$

- **Comments:**

- As **expected**, the closed-loop input resistance of the noninverting amplifier is very large.
- Equation:

$$R_{if} = \frac{v_I}{i_I} = \frac{R_i(1 + A_{OL}) + R_2 \left(1 + \frac{R_i}{R_1}\right)}{1 + \frac{R_2}{R_1}}$$

shows that R_{if} is **dominated** by the term $R_i(1 + A_{OL})$.

- The combination of a large R_i and large A_{OL} **produces** an extremely large input resistance, as **predicted** by ideal **feedback theory**.

14.2.5 Nonzero Output Resistance

- Since the **ideal op-amp** has a *zero* output resistance
 - The output voltage is independent of the load impedance.
 - The op-amp acts as an **ideal voltage source** and there is **no loading effect**.
- An actual op-amp circuit has a *nonzero* R_o , which **means** that:
 - The output voltage and the closed-loop gain are function of the load impedance R_L .

14.2.5 Nonzero Output Resistance

- Figure 14.6 is the equivalent circuit of both an inverting and noninverting amplifier and is used to find R_o .
- The op-amp has:
 1. Finite open-loop gain A_{OL} ,
 2. Nonzero output resistance R_o , and
 3. An infinite input resistance R_i .
- To determine R_o :
 - We set the independent input voltages equal to zero.

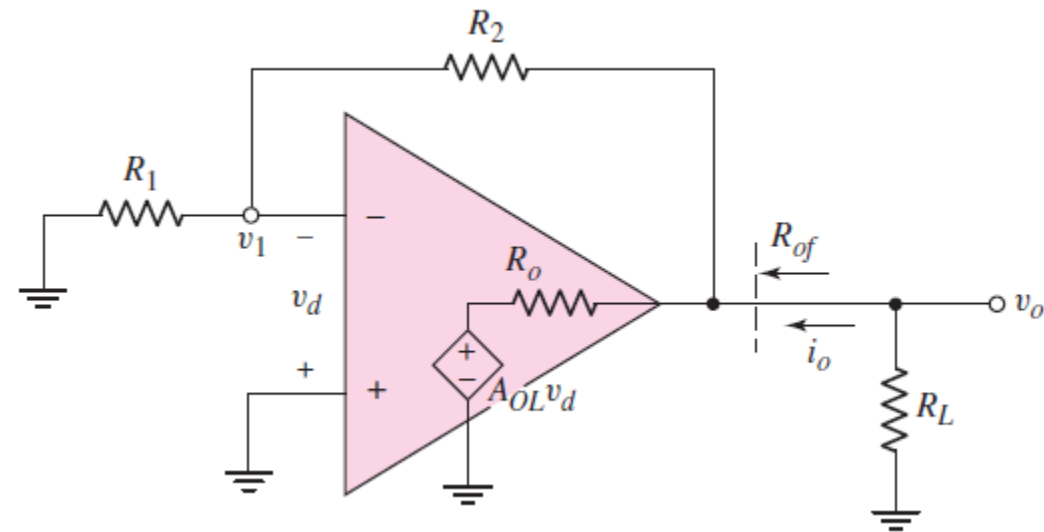


Figure 14.6

14.2.5 Nonzero Output Resistance

- A **KCL** equation at the output node **yields**:

$$i_o = \frac{v_o - A_{OL}v_d}{R_o} + \frac{v_o}{R_1 + R_2}$$

- The differential input voltage is:

$$v_d = v_2 - v_1 = -v_1$$

- But by voltage divider technique:

$$v_1 = \left(\frac{R_1}{R_1 + R_2} \right) v_o$$

$$v_d = - \left(\frac{R_1}{R_1 + R_2} \right) v_o$$

- Combining** the two Equations above, we have:

$$i_o = \frac{v_o}{R_o} - \frac{A_{OL}}{R_o} \left[- \left(\frac{R_1}{R_1 + R_2} \right) v_o \right] + \left(\frac{v_o}{R_1 + R_2} \right)$$

$$\frac{i_o}{v_o} = \frac{1}{R_{of}} = \frac{1}{R_o} \left[1 + \frac{A_{OL}}{1 + R_2/R_1} \right] + \left(\frac{1}{R_1 + R_2} \right)$$

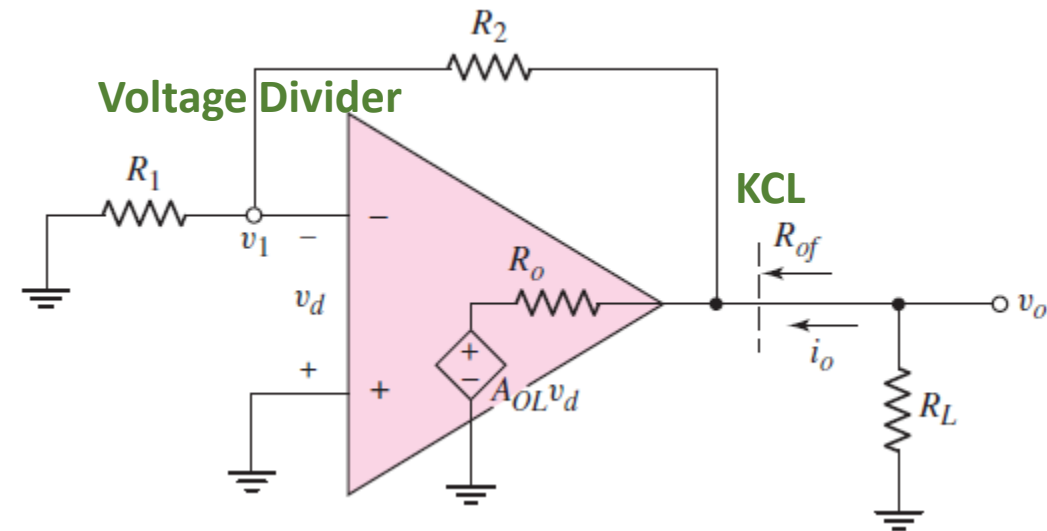


Figure 14.6

14.2.5 Nonzero Output Resistance

$$\frac{i_o}{v_o} = \frac{1}{R_{of}} = \frac{1}{R_o} \left[1 + \frac{A_{OL}}{1 + R_2/R_1} \right] + \left(\frac{1}{R_1 + R_2} \right)$$

- Since R_o is normally small and A_{OL} is normally large, the Equation above, to a good approximation, is as follows:

$$\frac{1}{R_{of}} \approx \frac{1}{R_o} \left[\frac{A_{OL}}{1 + R_2/R_1} \right]$$

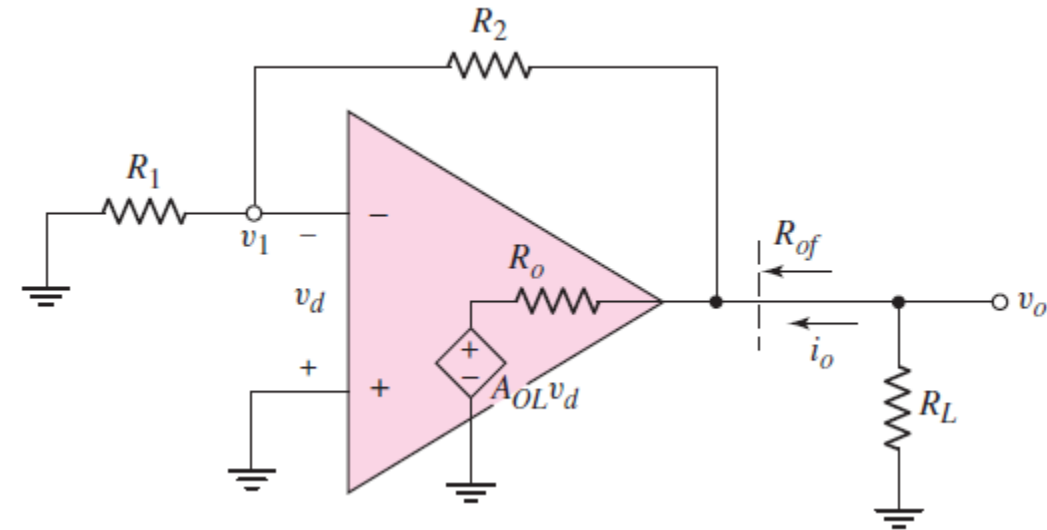


Figure 14.6

14.2.5 Nonzero Output Resistance

$$\frac{1}{R_{of}} \approx \frac{1}{R_o} \left[\frac{A_{OL}}{1 + R_2/R_1} \right]$$

- **Comments:**

- In most op-amp circuits, the **open-loop output resistance** R_o is on the order of 100Ω .
- Since A_{OL} is normally much larger than $(1 + R_2/R_1)$, the R_{of} can be very small.
- R_{of} values in the **milliohm** range are easily **attained** using opamps.

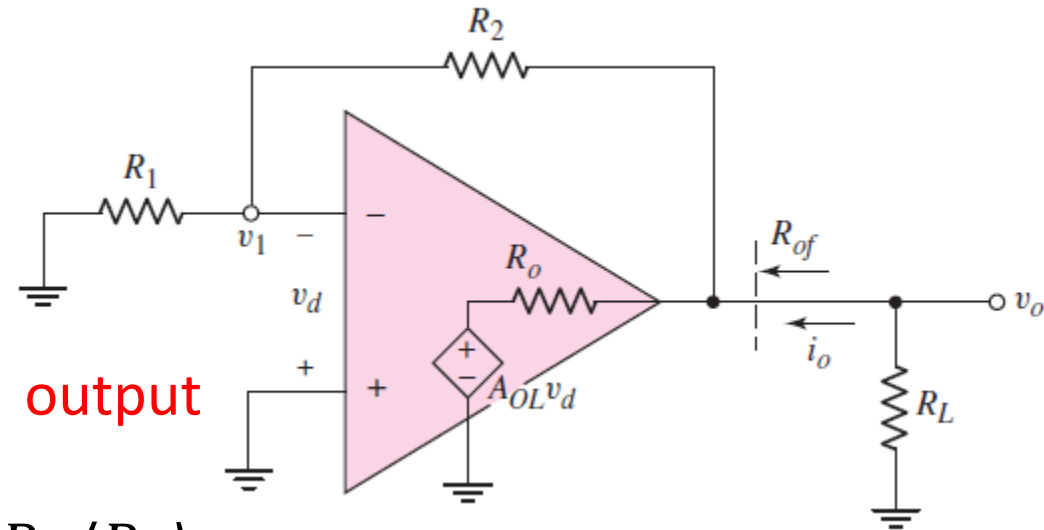


Figure 14.6

EXAMPLE 14.4

- **Objective:** Determine the output resistance of an op-amp circuit R_{of} .
- **Computer Simulation Solution:** Figure 14.7 shows an inverting amplifier circuit with a standard 741 op-amp.

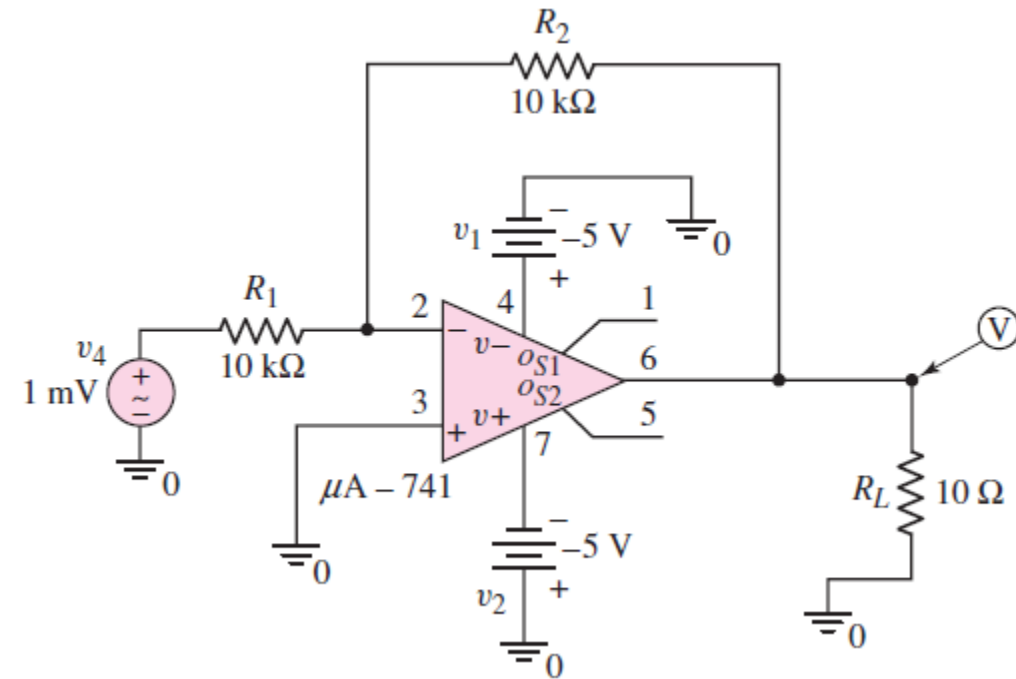


Figure 14.7

How the Output Resistance of an Opamp Circuit is Measured?

- One method of **determining** the output resistance is:
 - **Measure** the output voltage for two different values of **load resistance** connected to the output, i.e. R_{L1} and R_{L2}
 - Then, **treating** the amplifier as a Thevenin equivalent circuit with: a fixed source in series with an output resistance.

$$V_{o1} = A_v V_i \left(\frac{R_{L1}}{R_{L1} + R_{of}} \right)$$
$$V_{o2} = A_v V_i \left(\frac{R_{L2}}{R_{L2} + R_{of}} \right)$$

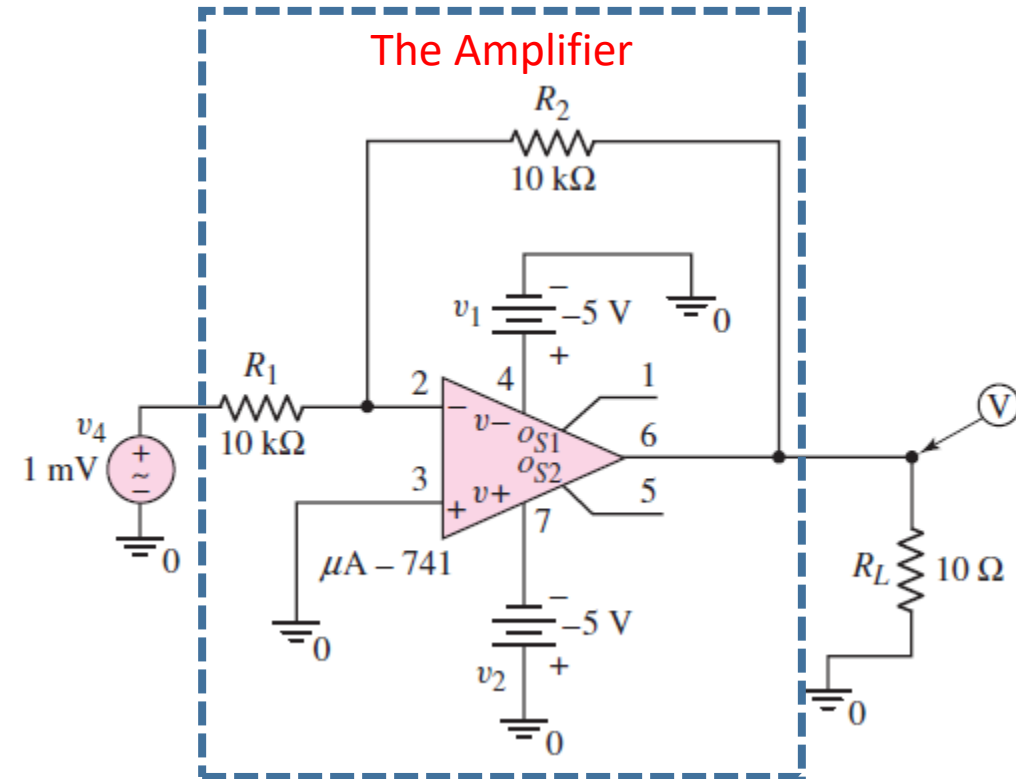


Figure 14.7

How the Output Resistance of an Opamp Circuit is Measured?

$$V_{o1} = A_v V_i \left(\frac{R_{L1}}{R_{L1} + R_{of}} \right)$$

$$V_{o2} = A_v V_i \left(\frac{R_{L2}}{R_{L2} + R_{of}} \right)$$

• Let:

$$\frac{V_{o1}}{V_{o2}} = \left(\frac{R_{L1}}{R_{L1} + R_{of}} \right) \left(\frac{R_{L2} + R_{of}}{R_{L2}} \right)$$

• Then:

$$R_{of} = \frac{R_{L1} R_{L2} \left(1 - \frac{V_{o1}}{V_{o2}} \right)}{R_{L2} \left(\frac{V_{o1}}{V_{o2}} \right) - R_{L1}}$$

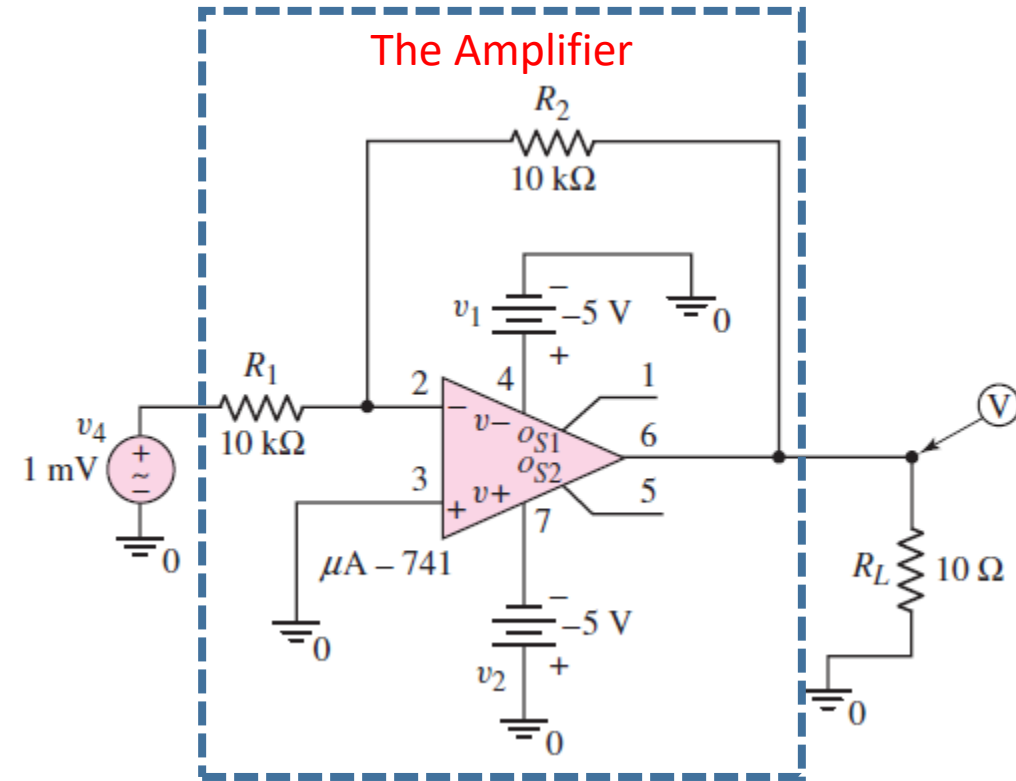


Figure 14.7

EXAMPLE 14.4

- A 1 mV signal was **applied**.
 - For a 10Ω load, the output voltage is 0.999837 mV , and
 - For a 20Ω load, the output voltage is 0.9999132 mV .

$$R_{of} = \frac{R_{L1}R_{L2} \left(1 - \frac{V_{o1}}{V_{o2}}\right)}{R_{L2} \left(\frac{V_{o1}}{V_{o2}}\right) - R_{L1}}$$

$$= \frac{10 \cdot 20 \left(1 - \frac{0.999837\text{ m}}{0.9999132\text{ m}}\right)}{20 \left(\frac{0.999837\text{ m}}{0.9999132\text{ m}}\right) - 10}$$

- This gives an output resistance of:

$$R_{of} = 1.53\text{ m}\Omega$$

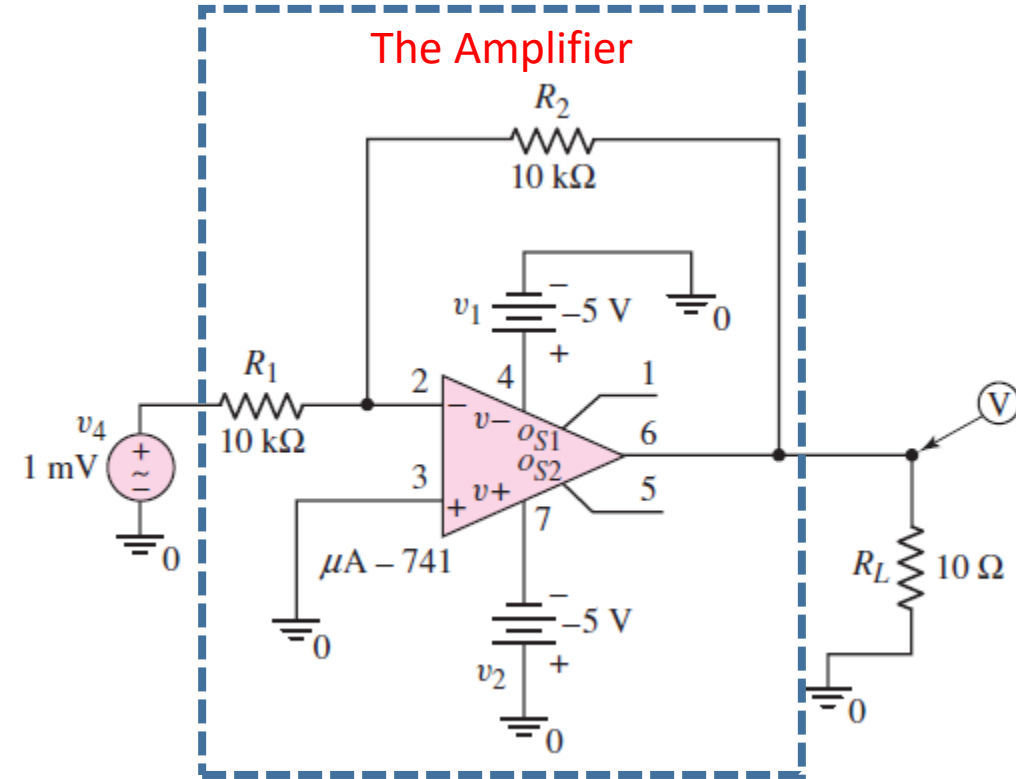


Figure 14.7

EXAMPLE 14.4

$$R_{of} = 1.53 \text{ m}\Omega$$

- **Comments:**

- As mentioned, the output resistance of a voltage amplifier with negative feedback can be very small.
- The ideal output resistance is *zero*, but a practical op-amp circuit can have an output resistance in the *milliohm* range.

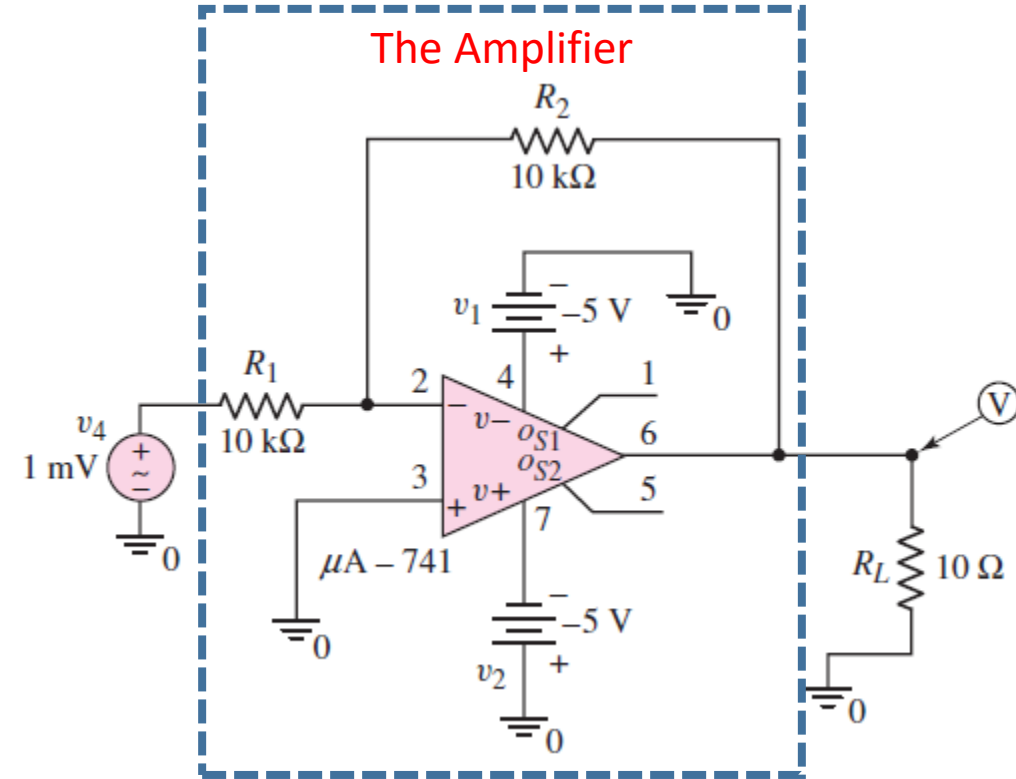


Figure 14.7

Do it yourself

- Solve all the Exercise Problems as well as the Test Your Understanding Questions.