

* Introduction:


* Electric circuit (ckt):

- an interconnection of electric devices (elements).

- to transfer energy from one point to another.


* Two parts of circuits → DC-part
→ AC-part

* D-c (ckt):
Direct current circuit

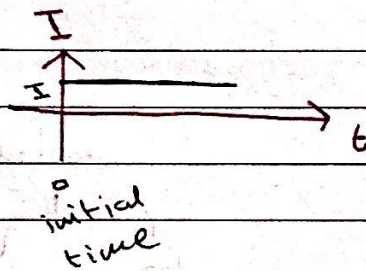

* constant in value and direction.

* A-c (ckt):
alternating current circuit

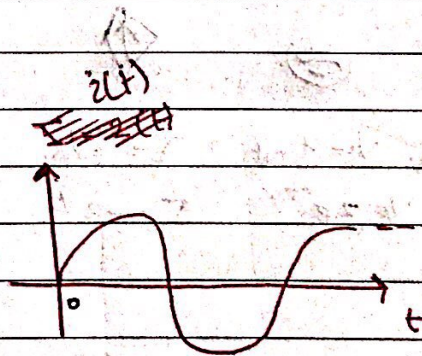

⇒ the current is time-varying.

[1] Electric charge:

Basic quantity in electricity

* units Coulomb "C"

* atom $\left\{ \begin{array}{l} \rightarrow \text{electrons: } (e) \text{ } (-1.6 \times 10^{-19} \text{ C}) \\ \rightarrow \text{protons: } (p) \text{ } (1.6 \times 10^{-19} \text{ C}) \end{array} \right.$

Q) How many (e) in 1 C ?

an: $1/e = 6.24 \times 10^{18}$ electrons.

"C" is a large unit.

[2] Electric current:


* i or $i(t)$: time-varying current.

* I : constant current.

unit: Ampere "A"

$$1 \text{ A} = 1 \text{ C / sec.}$$

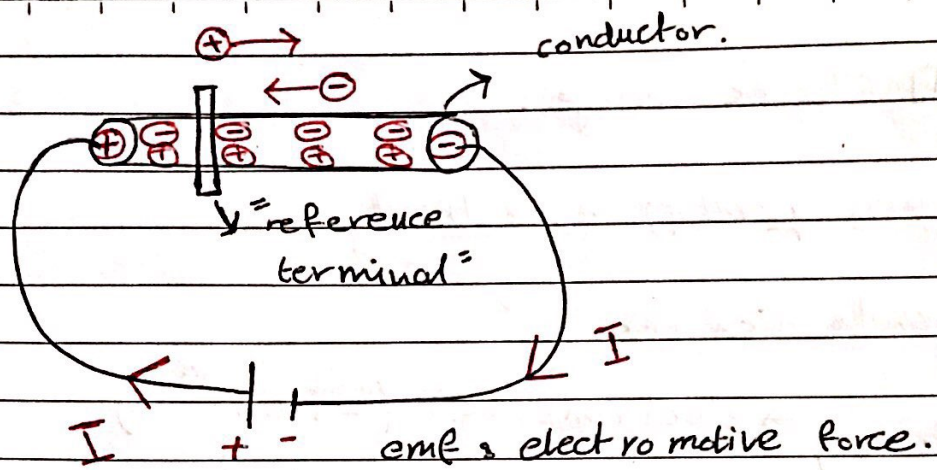
Def: The current means charges in motion (Flow of charges).



* current direction is the same as direction of +ve charges.

~~eg~~

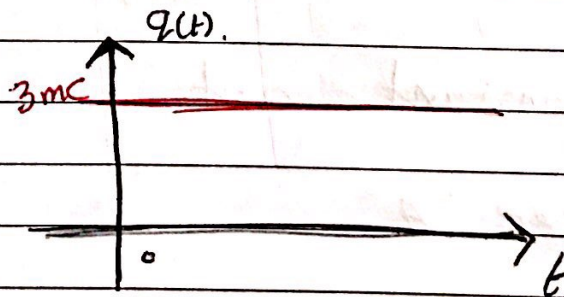* $q(t)$ = the net (total) charges that has passed the reference terminal since the initial time $t=0$ in a specific direction.



Ex:

Sol:

$$q(0) = 3 \text{ mc}$$

$$q(1) = 0$$


$$q(2) = 0$$

⋮

$$\dot{q}(t) = \frac{dq(t)}{dt}$$

Ex: The current is constant (I) only when $q(t)$ is linear function of time.

$$I = \frac{\Delta Q}{\Delta t}$$

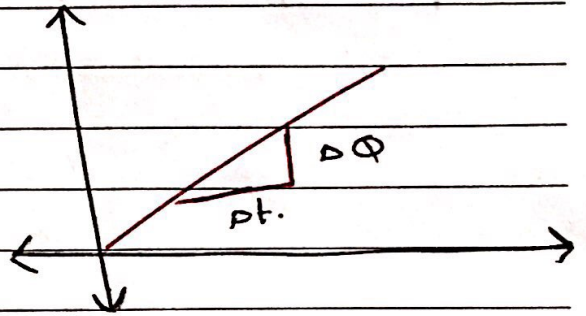

$$i = \frac{dq}{dt} \Rightarrow \int_{q(t_1)}^{q(t_2)} dq = \int_{t_1}^{t_2} i dt \Rightarrow \underbrace{q(t_2) - q(t_1)}_{\text{total net charge flow}} = \int_{t_1}^{t_2} i dt$$


the total net charge flow between $t=t_1$ & $t=t_2$.

$$\text{From (a): } q(t) - q(t_0) = \int_{t_0}^t i(t') dt'$$

$$\Rightarrow q(t) = \int_{t_0}^t i(t') dt' + q(t_0)$$

t_0 and $q(t_0)$ should be given.

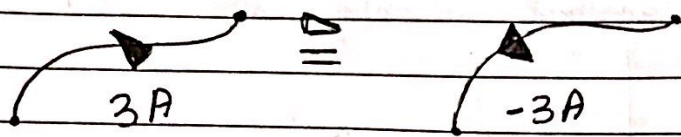• Current direction:
 current $\left\{ \begin{array}{l} \rightarrow \text{numerical value} \\ \text{(either +ve or -ve).} \\ \rightarrow \text{Direction.} \end{array} \right.$






3] Voltage (potential difference)

Def: The amount of energy needed to move $+1\text{C}$ from the "ve" labeled terminal to the "+ve" labeled terminal.



$$V = \frac{dw}{dq}$$

unit: $1\text{V} = 1\text{J}/\text{C}$.

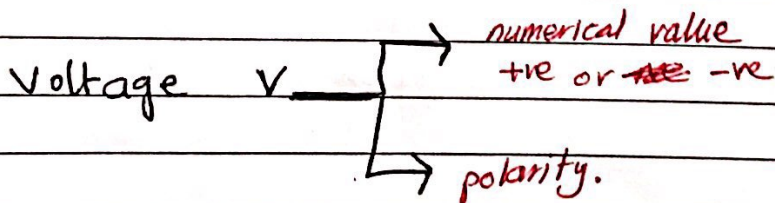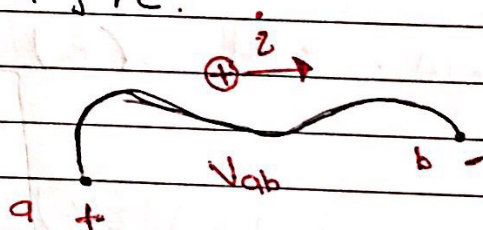

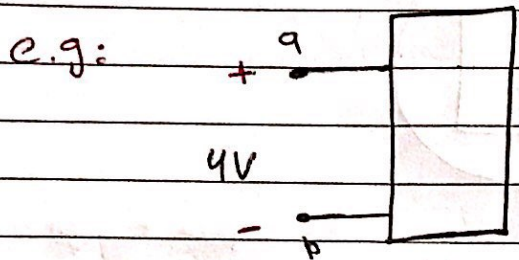

$$V_{ab} = V_a - V_b = 4V.$$

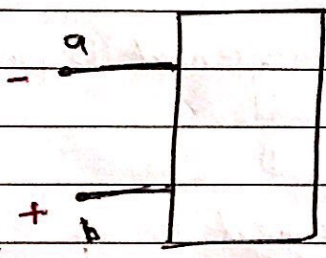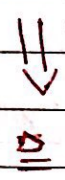

4] Power: $P(t)$, P , unit "W"

Def: the time-rate of energy absorbed by an element.


$$P = \frac{dw}{dt}$$

$$1W = 1J/sec.$$

$$P = \frac{dw}{dt} \times \frac{dq}{dq} = \frac{dw}{dq} \cdot \frac{dq}{dt} = V i$$

$$P = V i$$

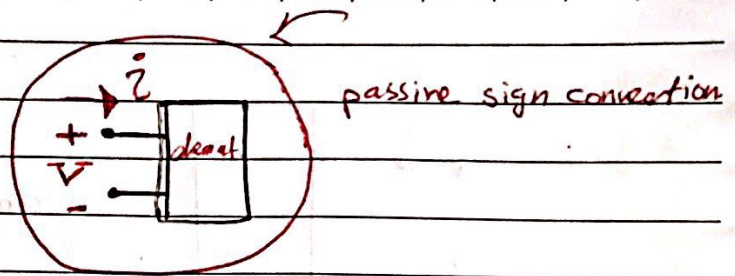$P = \sum V i$
 power absorbed
 by an element.



passive sign convention
 • absorbed \rightarrow passive

• generate \rightarrow active.

step 1: use the passive sign convention.

step 2: $p = \sum iV$

- $\rightarrow +ve$: the element is passive and absorbed.
- $\rightarrow -ve$: the element is active and generate.

Ex: Determine the power absorbed, or generated, or generated or generated by each element.

①

sol:


$P = iV = (2)(3) = 6W$

passive element.


- absorbed 6 W

OR

- generated - 6 W.

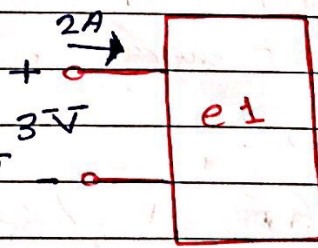

②

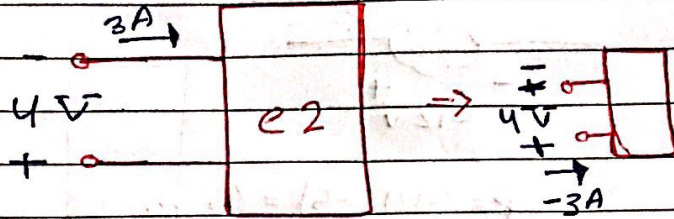


$$p = i(v) = (-3)(4) = -12 \text{ W}$$

- absorbed -12 W

\triangleq
- generated 12 W


active element

Ex 8

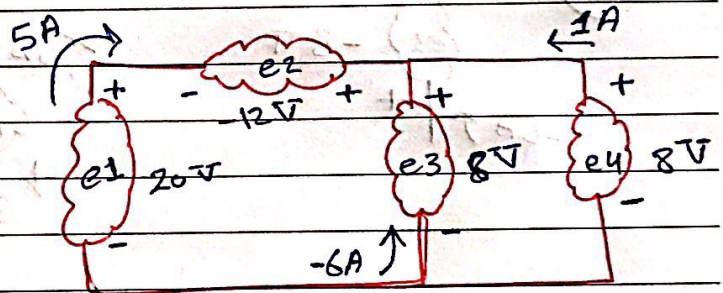

Determine power absorbed by elements?

Sol.

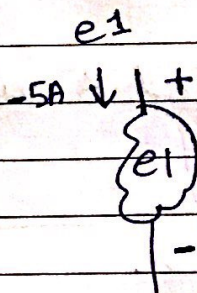


$$p = -100 \text{ W}$$

absorbed -100 W

OR

✓ generated 100 W

active

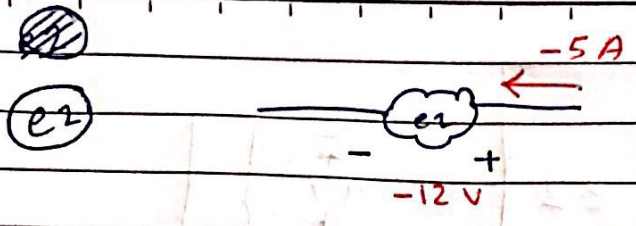


$$P = (-12)(-5) = 60 \text{ W.}$$

✓ absorbed 60 W

⇓
=

generated -60 W

passive

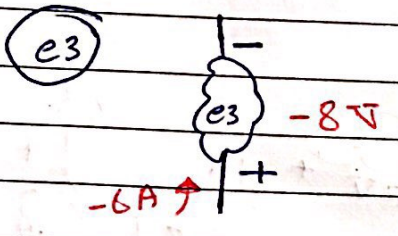


$$P = (-6)(-8) = 48 \text{ W}$$

✓ absorbed 48 watt

passive

⇓
= generated -48 watt.

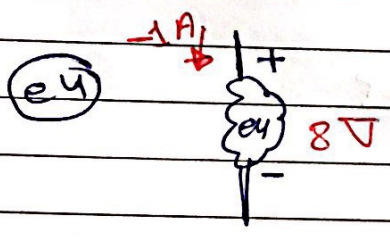

$$P = (-1)(8) = -8 \text{ watt}$$


absorbed. -8 watt


⇓
= generated 8 watt.


active

$$\sum P^{ob} = \sum P^{gen.}$$

* Passive elements :-

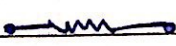
1) Resistors :- 

2) capacitors :- 

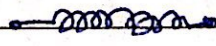
3) inductors :- 

* power \rightarrow +ve \rightarrow absorbed.
 \rightarrow -ve \rightarrow generated (active element.)

* These sources are independent :-

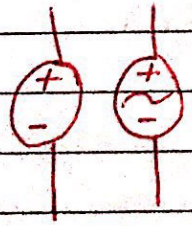


Voltage source

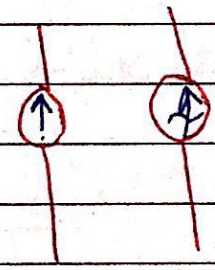


current source

* These sources are dependent :-

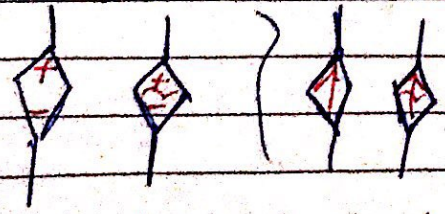


Chapter 2# Resistance & Resistors.

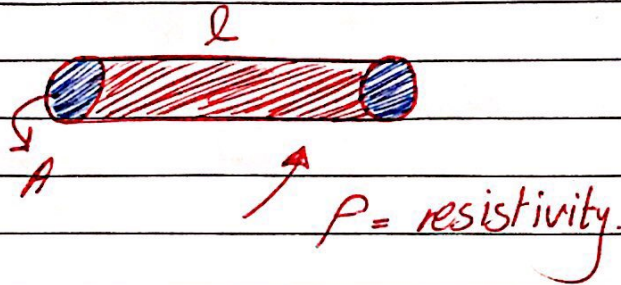* Resistance is a material property to resist the current passing



$$R = \frac{\rho l}{A}$$

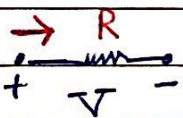* Resistor is  Basic passive element.


Ohm's law

$$V = iR$$

R is constant value

"ثابتة بالقيمة" =

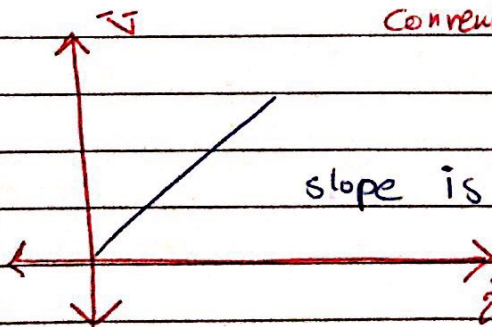"passive sign convention" ان تكون للتيار و الجهد




slope is equal to R because $R = \frac{V}{i}$

$0 < R < \infty$

short circuit $(R = \frac{V}{i} \Rightarrow V=0)$ open circuit $R = \frac{V}{i} \Rightarrow i=0$

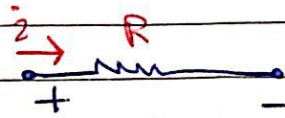* power absorbed (dissipated) by resistors



$$P = V \cdot i$$


$$P = i^2 \cdot R$$

$$P = \frac{V^2}{R}$$

conductance # (G)


$$G = \frac{1}{R} \Rightarrow (\Omega)^{-1}, S^{-1}$$

Ex 8

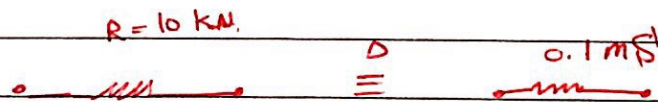

because, $G = \frac{1}{R} = \frac{1}{10 \times 10^3} = 0.1 \text{ mS}$.

$$V = i \cdot R \quad \Leftrightarrow \quad V = \frac{i}{G} \quad \Leftrightarrow \quad G = \frac{i}{V} \quad \Leftrightarrow \quad i = G \cdot V$$

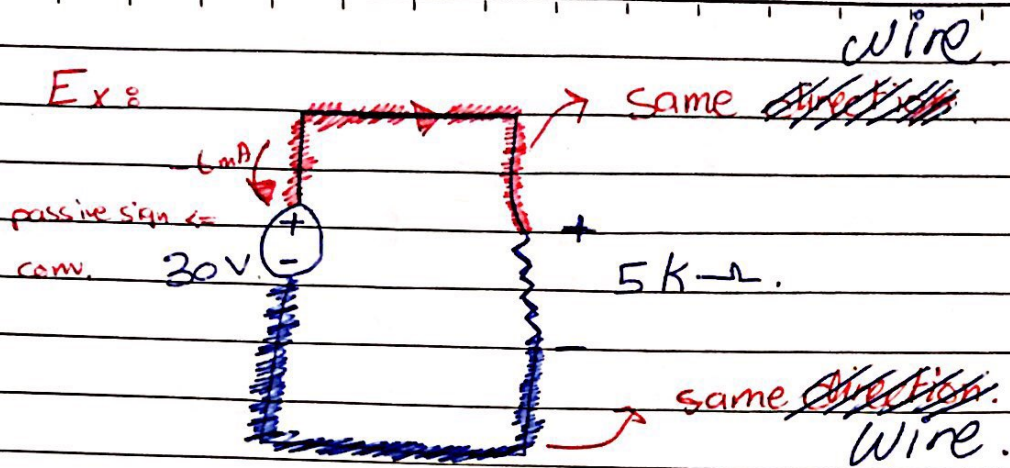

Find 1) current 2) G 3) power dissipated by $5k\Omega$.

4) power generated by the voltage source

Sol.

$$1) V = iR = 30 = i + 510^3 \Rightarrow i = 6mA$$


$$2) G = \frac{1}{R} = \frac{1}{510^3} = 0.2 m\Omega^{-1} \text{ OR } mS$$

$$3) P = i^2 R = 3610^{-6} * 510^3 = 180 mW$$

$$4) P = iV = -610^{-3} * 30 = -180 W \text{ absorbed.}$$

so, it generates +180 W.

Ex: Find the current i

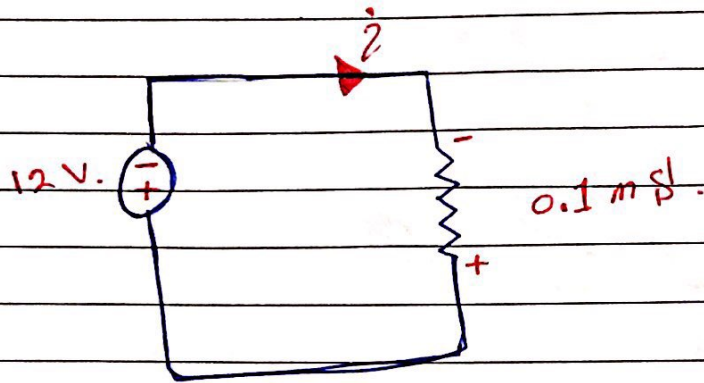

Sol:

$$R = \frac{1}{G} = \frac{1}{0.1 \times 10^{-3}} = 10 \text{ k}\Omega$$




$$i = \frac{V}{R} = \frac{12}{10 \text{ k}\Omega} = 1.2 \text{ mA}$$


$$i = -1.2 \text{ mA}$$

⊗ Branches, Nodes, Loops: a closed path starts from a node and back to the same node.

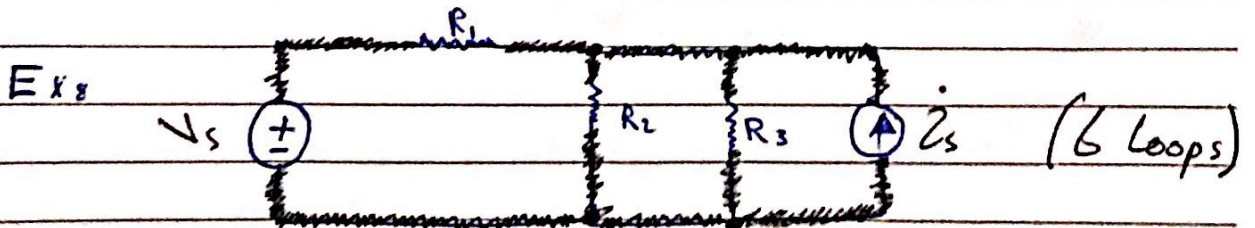The point of connection of 2 or more branches.




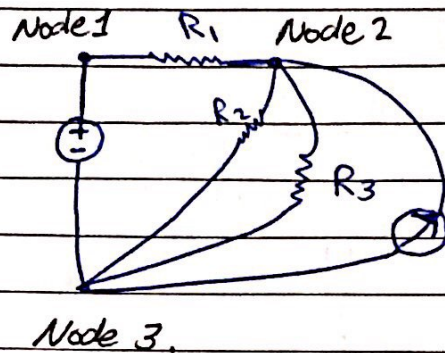branch & a single element connected between 2 nodes.



Element in series :- exclusively share a single node and consequently carry the same current.

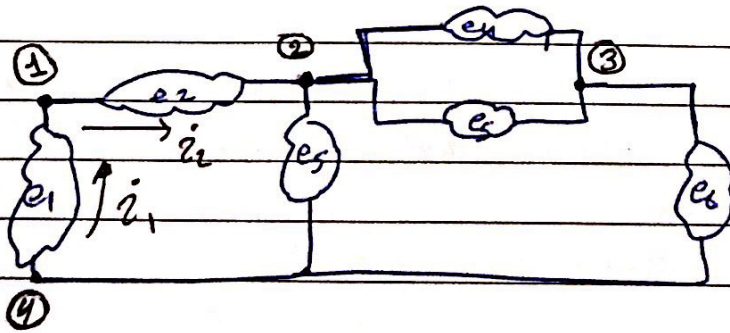
Elements in parallel :- are connected to the same two nodes and consequently have the same voltage.




e_1 & e_2 are in series ($i_1 = i_2$).

e_4 & e_5 are in parallel ($V_4 = V_5$).

Kirchoff's laws:

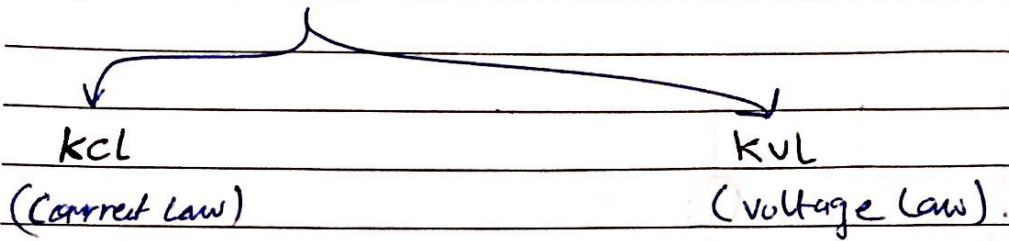

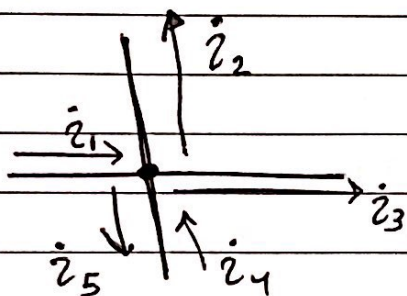1 KCL: The algebraic sum of current entering or leaving a node is zero.



$$i_1 - i_2 - i_3 + i_4 - i_5 = 0$$

(entering).


$$-i_1 + i_2 + i_3 - i_4 + i_5 = 0$$

(leaving).

$$* i_1 + i_4 = i_5 + i_2 + i_3$$

"مجموع التيارات الداخلة يساوي مجموع التيارات الخارجة"


• Current source in parallel:

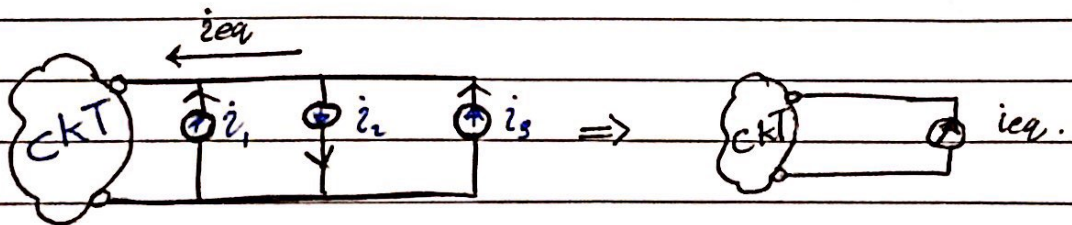

$$KCL: i_1 + i_3 = i_2 + i_{eq}$$

$$i_{eq} = i_1 + i_3 - i_2$$

Ex 2

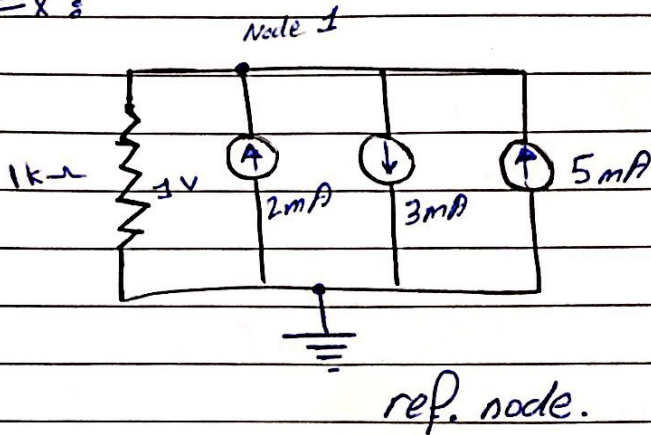

apply KCL at node (1) :-

$$2\text{mA} + 5\text{mA} = 3\text{mA} + \dot{i}$$

$$\dot{i} = (2 + 5 - 3)\text{mA}$$

$$\dot{i} = 4\text{mA}$$

$$V = \dot{i}R$$

$$= 4\text{mA} \times 1\text{k}\Omega$$


$$V = -4\text{V}$$

~~Kirchoff's voltage (KVL).~~

~~The algebraic sum of all voltages in a closed path (loop) is zero.~~

[2] Kirchhoff's voltage law (KVL):

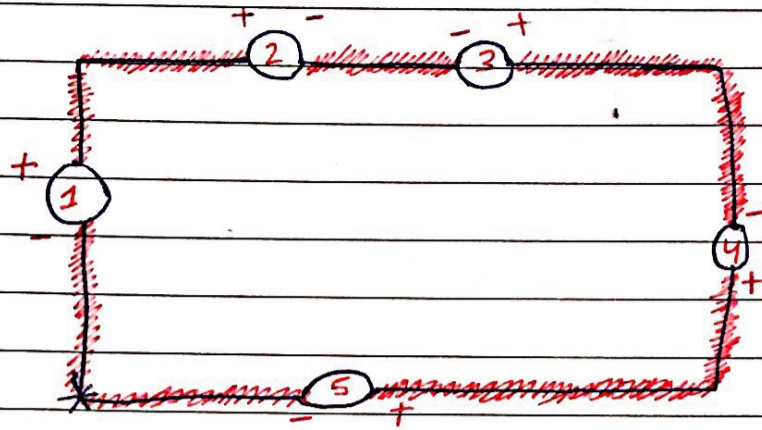The algebraic sum of all voltages in a closed path (loop) is zero.



5 nodes
1 loop.


$\sum V = \text{Zero}$.

$$V_1 - V_2 + V_3 + V_4 - V_5 = 0.$$

OR

$$-V_1 + V_2 - V_3 - V_4 + V_5 = 0.$$

* Voltage source in series:

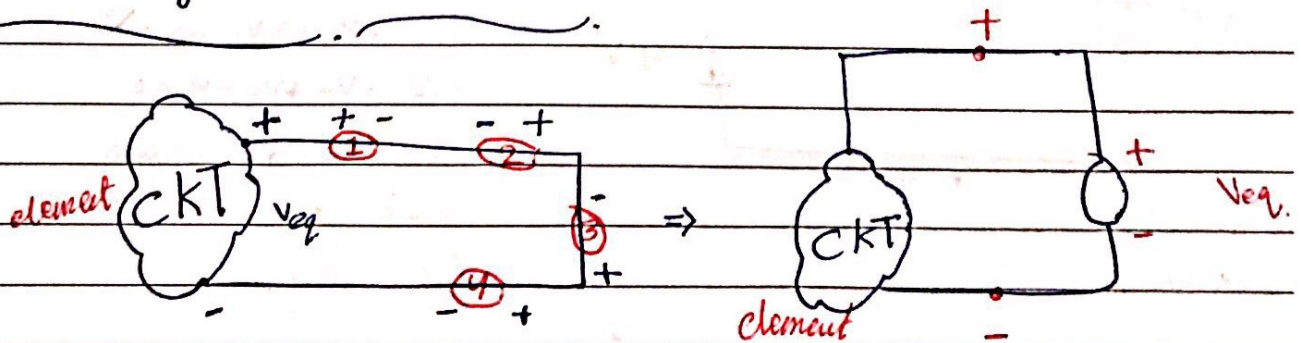


$$KVL = -V_{eq} + V_1 - V_2 - V_3 + V_4 = 0.$$

$$V_{eq} = V_1 - V_2 - V_3 + V_4$$


Ex: Find i_x , V_x .

* Use KVL in single loop.

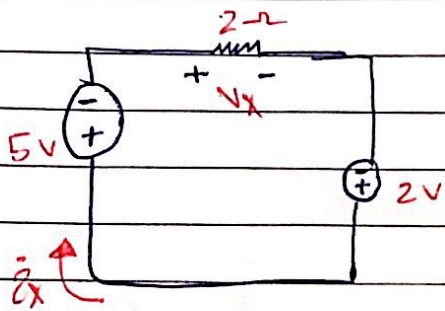


$$\text{KVL} \Rightarrow 5\text{V} + V_x - 2\text{V} = 0.$$

$$V_x = -3\text{V}.$$

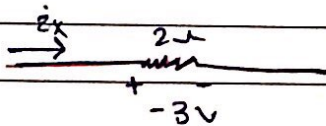

$$i_x = \frac{V}{R} = \frac{-3}{2} = -1.5\text{A}.$$

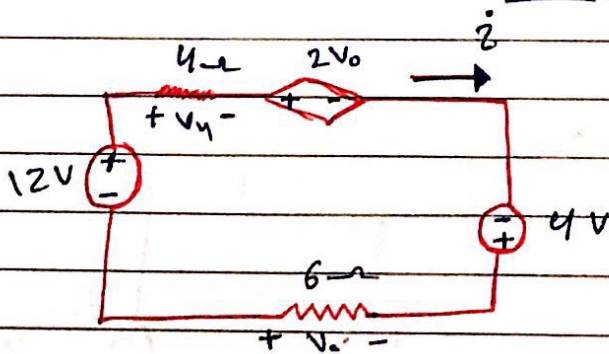Ex: Find V_o , i , Power generated by 4V. * Use KVL in single loop.



KVL:


$$-12 + V_4 + 2V_o - 4 - V_o = 0.$$

$$-12 + V_4 + V_o - 4 = 0$$

$$-12 + 4i - 6i - 4 = 0.$$

$$-2i = 16$$

$$i = -8\text{A}$$

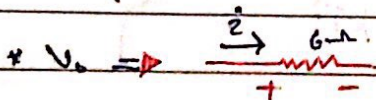

$$V_o = iR$$

$$= -(-8)(6) = 48\text{V}.$$




$$P = iV$$

$$= -(-8)(4) = 32\text{Watt}.$$

So, generated - 32 watt.

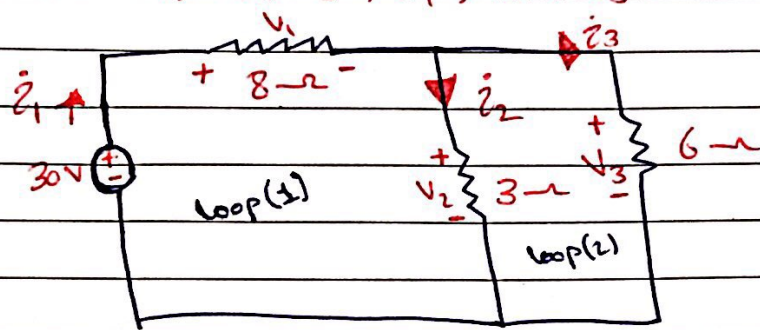Ex 8 Find $V_1, V_2, V_3, i_1, i_2, i_3$.



Sol.

$$-30 \text{ V} + V_1 + V_2 = 0 \quad (\text{KVL Loop 1}).$$

$$30 = 8i_1 + 3i_2 \quad \text{--- (1)}$$

(KCL Loop 2)



$$-i_1 + i_2 + i_3 = 0$$

(KVL Loop 3) $-V_2 + V_3 = 0$.


$$-3i_2 + 6i_3 = 0 \quad \text{--- (2)}$$

جواب سوالات :


Ex: -> Some important cases:-

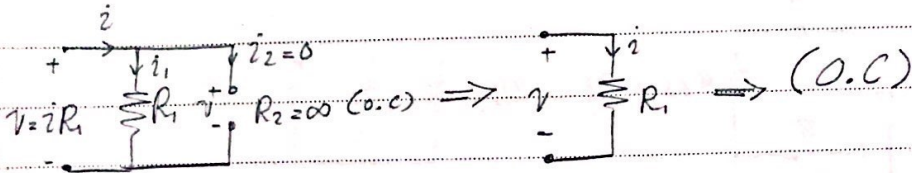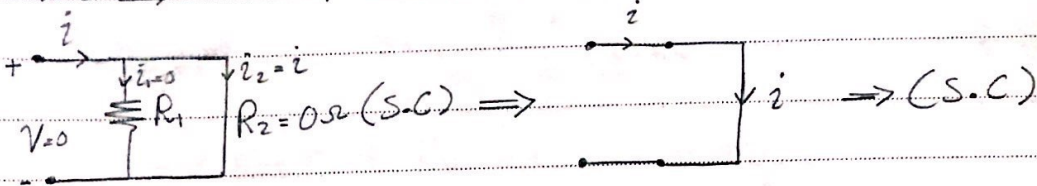

Ex:

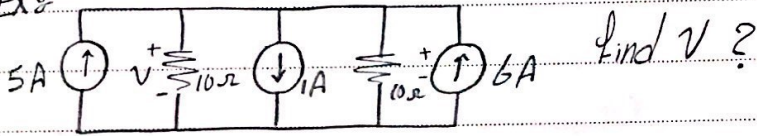


\Downarrow $6+5-1=10A$

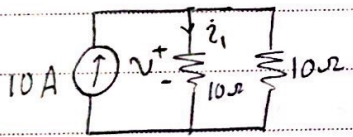

$i_1 = 10 \times \frac{10}{20} = 5A$, $v = Ri = 50V$







Power in 6A $\rightarrow P = Vi \Rightarrow -6 \times 50 = -300 \Rightarrow$ generated.

Ex:

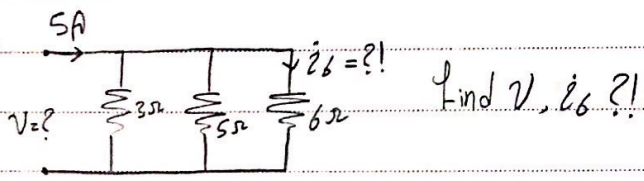


v , $Req = 3||5||6 = \frac{10}{7}$, $v = 5 Req = \frac{50}{7}$ Volt

$i_6 = \frac{50}{7} \times \frac{1}{6} = \frac{50}{42} A$ OR $i_6 = 5 \times \frac{\frac{1}{6}}{\frac{1}{3} + \frac{1}{5} + \frac{1}{6}} = \frac{50}{42} A$

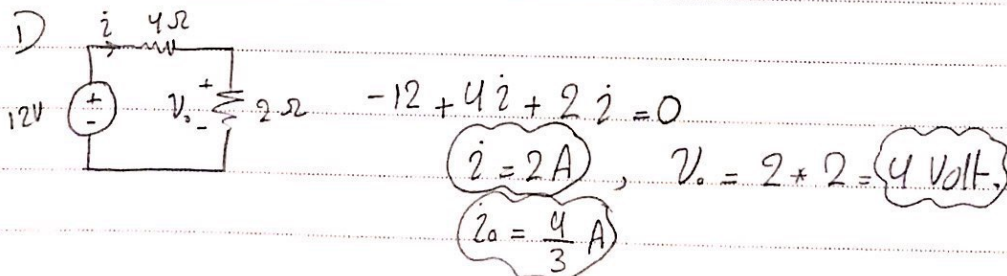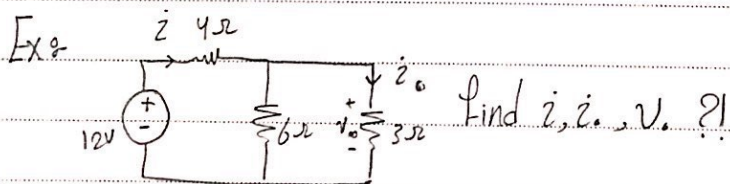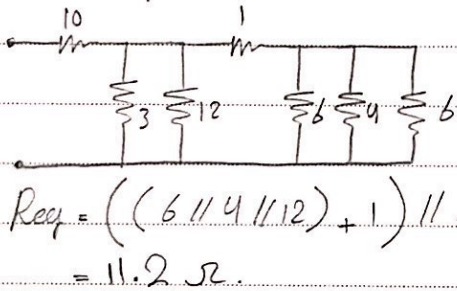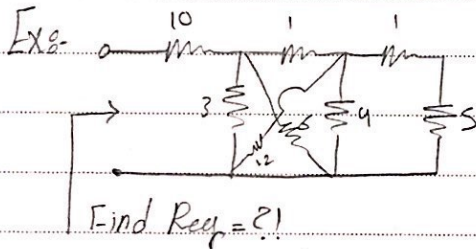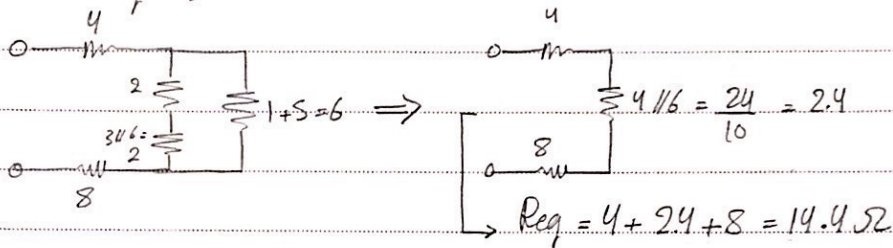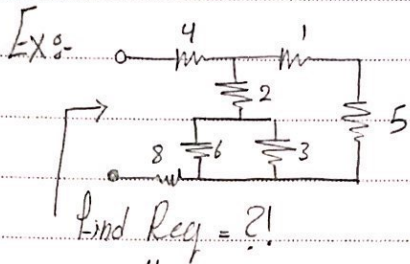


Ex 8-

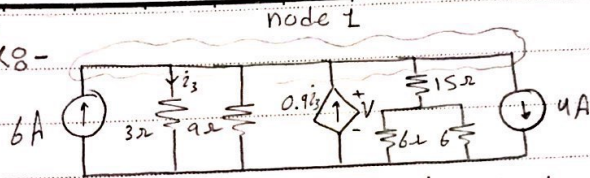

Find V & Power of the dependent source.

1)

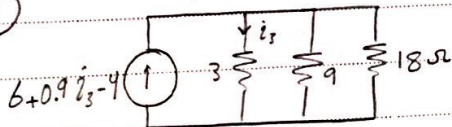

$$i_3 = \frac{\frac{1}{3}}{\frac{1}{3} + \frac{1}{9} + \frac{1}{18}} * (6 + 0.9 i_3 - 4)$$

2) KCL at Node 1

$$6 + 0.9 i_3 = i_3 + \frac{V}{9} + \frac{V}{18} + 4 \rightarrow \textcircled{1}$$

$$\frac{V}{3} = i_3 \rightarrow \textcircled{2}$$

Sub ② into ①:


$$6 + 0.9 \frac{V}{3} = \frac{V}{3} + \frac{V}{9} + \frac{V}{18} + 4 \rightarrow *$$

$$V = 10 \text{ Volt}$$


power

* Wye & Delta Network :-


Wye :-

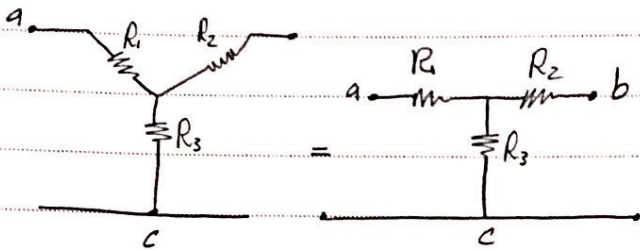

Balanced Wye :- $R_1 = R_2 = R_3 = R_Y$

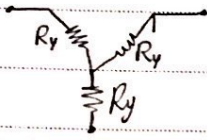


* Delta Network :-

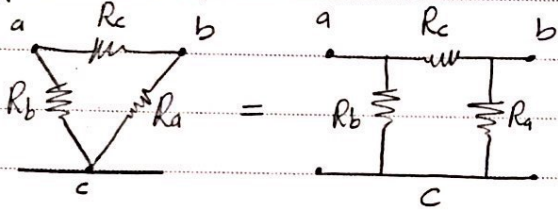


Balanced Delta :-

$$R_a = R_b = R_c \triangleq R_\Delta$$

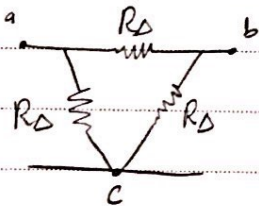

Δ - to - Y Transformation

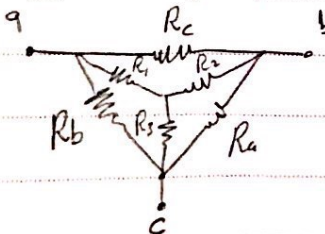

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Y-to-Δ Transformation.

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
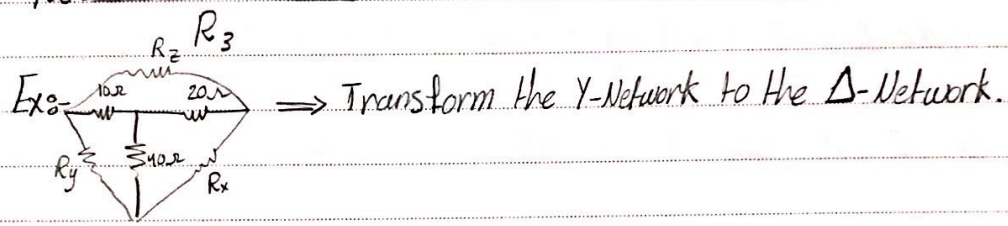
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$




$$R_c = \frac{(10)(20) + (20)(40) + (40)(10)}{40}$$

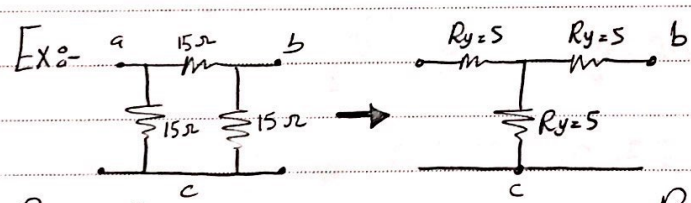
$$R_y = \frac{11}{20}, R_x = \frac{11}{10}$$



$$R_y = \frac{R_\Delta}{3} = 5\Omega$$

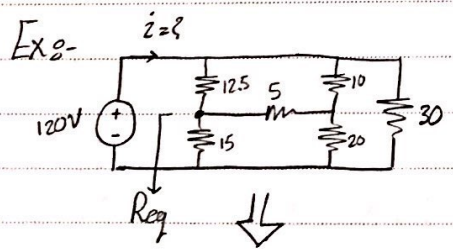


Find Req and i?

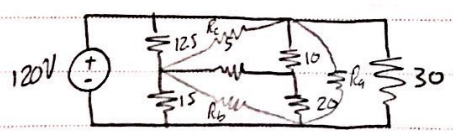

$$Y \rightarrow \Delta \rightarrow R_a = \frac{350}{5} = 70\Omega$$

$$R_b = \frac{350}{10} = 35\Omega$$

$$R_c = \frac{350}{20} = 17.5\Omega$$

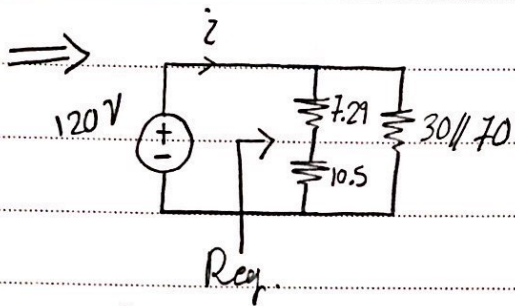

$$R_{eq} = (7.292 + 10.5) \parallel 21$$

$$= 9.632 \Omega$$

$$i = \frac{120}{9.632} = 12.46 \text{ A}$$

* Ch3 :- Nodal & Mesh Analysis :-


Nodal Analysis :-

To find the node voltages →

Based on KCL →

Case I :- CKTs with no voltage sources.

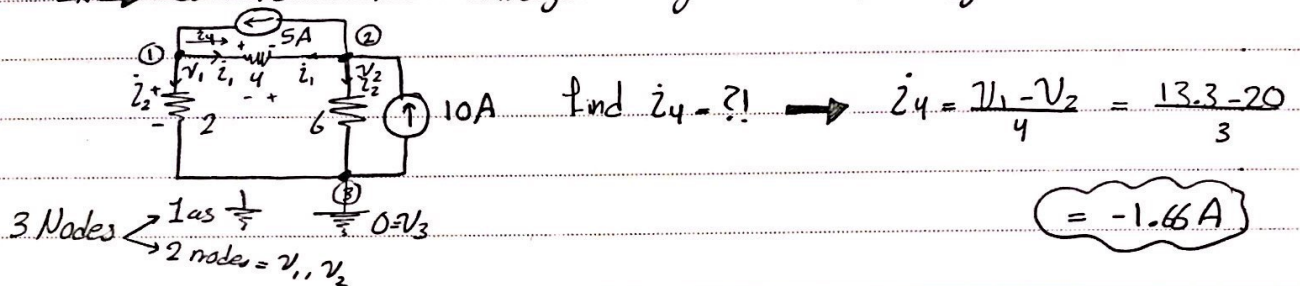Ex → Calculate the node voltages using the Nodal analysis.



kcl at node 1 →

$$5 = i_1 + i_2$$

$$5 = \frac{v_1 - v_2}{4} + \frac{v_1 - v_3}{2} \Rightarrow 5 = \frac{v_1}{4} - \frac{v_2}{4} + \frac{2v_1}{2 \times 2}$$

$$5 = \frac{3v_1}{4} - \frac{v_2}{4} \Rightarrow (0.75v_1 - 0.25v_2 = 5) \rightarrow \textcircled{1}$$

kcl at node 2 →

$$10 = 5 + i_1 + i_2$$

$$10 = 5 + \frac{v_2 - v_1}{4} + \frac{v_2}{6}$$

$$-0.25v_1 + \left(\frac{1}{4} + \frac{1}{6}\right)v_2 = 5$$

$$(-0.25v_1 + 0.42v_2 = 5) \rightarrow \textcircled{2}$$

Solving ① & ②

$$v_1 = 40/3 \text{ V}$$

$$v_2 = 20 \text{ V}$$

* Mesh Analysis :-


- Use the mesh currents as CKT variable *
- Mesh :- loop that does not contain any other loops within it.
- Mesh Analysis :- apply KVL

Case I :- CKT's with no current sources.

Case II :- CKT's with current sources (we use Supermesh)

Case I

Ex :-

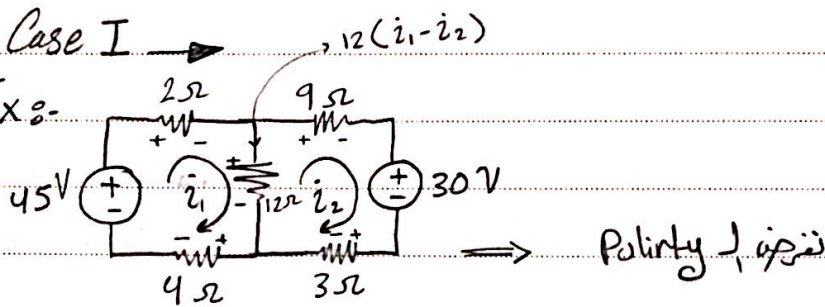

Find the mesh currents :-

- Find i_1 & i_2 :-

KVL at mesh 1 →

$$-45 + 2i_1 + 12(i_1 - i_2) + 4i_1 = 0$$

$$2i_1 + 12i_1 - 12i_2 + 4i_1 = 45$$

$$(18i_1 - 12i_2 = 45) \text{ (1)}$$

KVL at mesh 2 →

$$-12(i_1 - i_2) + 9i_2 + 30 + 3i_2 = 0$$

$$+12i_2 + 12i_1 + 9i_2 + 3i_2 = -30 \rightarrow$$


$$12i_1 = -30$$

$$i_1 =$$

* Mesh Analysis :-

Case I :- No Current sources in Ckt.

Ex →

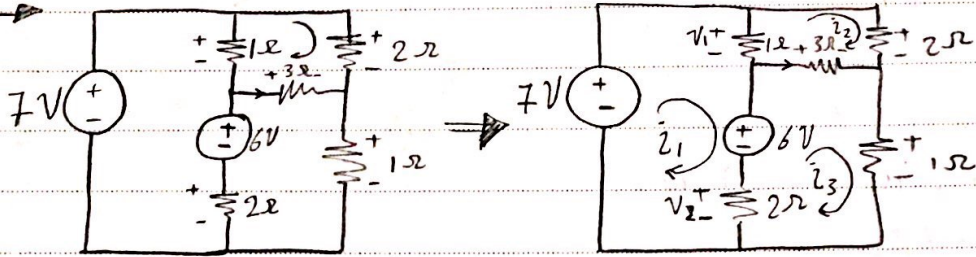

mesh ① →

$$-7 + 1(i_1 - i_2) + 6 + 2(i_1 - i_3) = 0$$

$$(3i_1 - i_2 - 2i_3 = 1) \text{ ①}$$

mesh ② →

$$-1(i_1 - i_2) + 2i_2 - 3(i_3 - i_2) = 0$$

$$(-i_1 + 6i_2 - 3i_3 = 0) \text{ ②}$$

mesh ③ →

$$-2(i_1 - i_3) - 6 + 3(i_3 - i_2) + 1i_3 = 0$$


$$(-2i_1 - 3i_2 + 6i_3 = 6) \text{ ③}$$

Solving ① & ② & ③ :-


$$i_1 = 3 \text{ A}$$

$$i_2 = 2 \text{ A}$$

$$i_3 = 3 \text{ A}$$

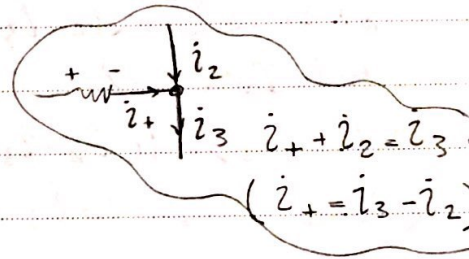

Ex 2

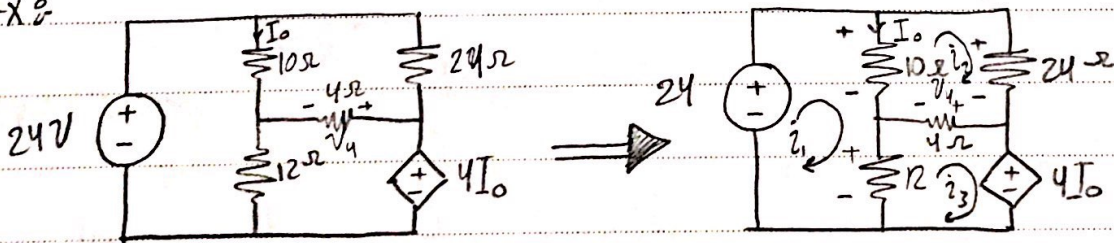

Find V_4 using Mesh analysis :-

Mesh ① :-

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$$

$$(22i_1 - 10i_2 - 12i_3 = 24) \text{ ①}$$

Mesh ② :-

$$-10(i_1 - i_2) + 24i_2 + 4(i_2 - i_3) = 0$$

$$(-10i_1 + 38i_2 - 4i_3 = 0) \text{ ②}$$

Mesh ③ :-

$$-12(i_1 - i_3) - 4(i_2 - i_3) + 4I_0 = 0$$

$$\text{but } I_0 = i_1 - i_2$$

$$-12(i_1 - i_3) - 4(i_2 - i_3) + 4(i_1 - i_2) = 0$$

$$(-8i_1 - 8i_2 + 16i_3 = 0) \text{ ③}$$


Solve ① & ② & ③ :-

$$i_1 = 2.25A \quad \left. \begin{array}{l} V_4 = 4(i_2 - i_3) \\ = 4(-0.75) \\ = -3V \end{array} \right\}$$

$$i_2 = 0.75A$$


$$i_3 = 1.5A$$

Ex 2: Find the mesh currents:-

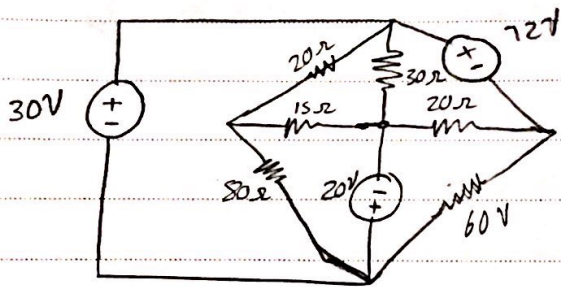

* Case II :- CKTs with current sources.

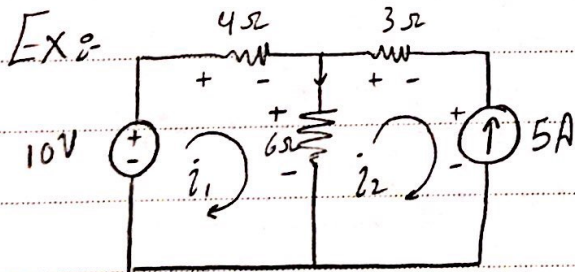↳ Case II-(a) :- when the current source exists only in one mesh.



mesh ② :- $i_2 = -5A$

kVL at mesh ① :- i_2


$$-10 + 4i_1 + 6(i_1 - (-5)) = 0$$

$$10i_1 - 10 + 30 = 0$$


$$(i_1 = -2A)$$

* Case II - (b) :- The current source exist between two meshes :-

Ex :-

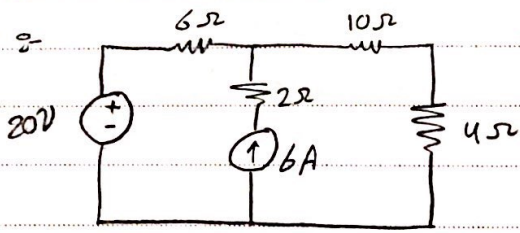

Find i_1 & i_2 using mesh analysis →

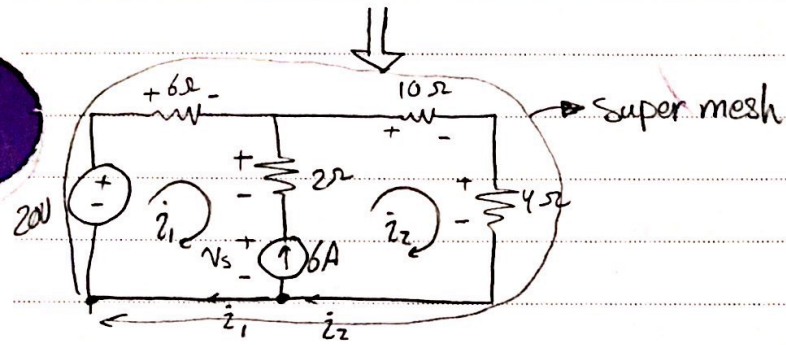

KVL at the Super node :-

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0$$


$$(6i_1 + 14i_2 = 20) \text{ ①}$$

KCL at the current source.

$$i_2 - i_1 = 6$$

$$(-i_1 + i_2 = 6) \text{ ②}$$

Ex :-

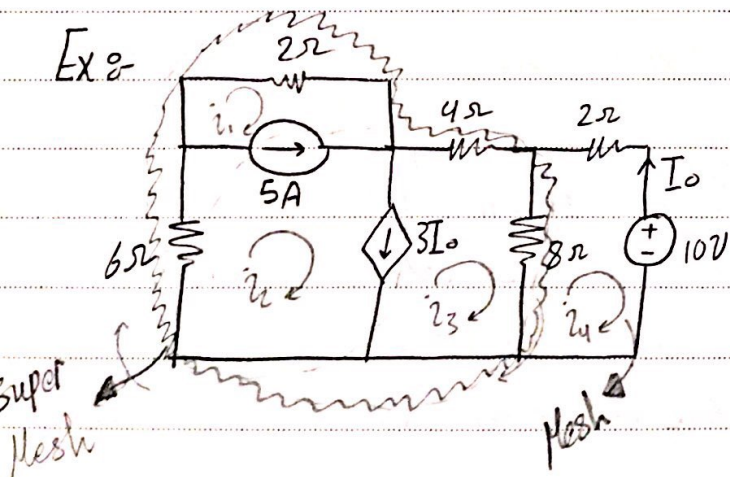

Find the mesh currents :-

* Super mesh \rightarrow

$$+6i_2 + 2i_1 + 4i_3 + 8(i_3 - i_4) = 0$$

$$(i_1 + 3i_2 + 6i_3 - 4i_4 = 0) \text{ ①}$$

* Mesh \rightarrow

$$-8(i_3 - i_4) + 2i_4 + 10 = 0$$

$$(-8i_3 + 10i_4 = -10) \text{ ②}$$

$$i_2 - i_1 = 5A \rightarrow (-i_1 + i_2 = 5) \text{ ③}$$

$$i_2 - i_3 = 3I_0 \rightarrow i_2 - i_3 = 3(-i_4)$$

$$(i_2 - i_3 + 3i_4 = 0) \text{ ④}$$


$$\begin{bmatrix} 1 & 3 & 6 & -4 \\ 0 & 0 & -6 & 10 \\ -1 & 1 & 0 & 0 \\ 0 & 1 & -1 & 3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ -10 \\ 5 \\ 0 \end{bmatrix}$$

Solving 1, 2, 3, 4

$$i_1 = 7.5A, \quad i_3 = 3.93A$$

$$i_2 = -2.5, \quad i_4 = 2.143A$$

Practice 4.10

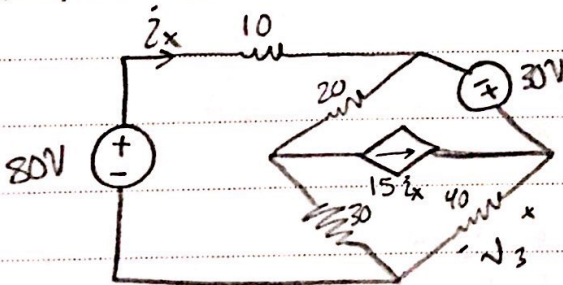

Find :- V_3 using $\begin{cases} \text{Nodal analysis} \\ \text{Mesh analysis} \end{cases}$

Solution $\rightarrow i_1 = 87/149$

$$i_2 = 917/149$$

$$i_3 = 388/149$$



$$V_3 = 40i_3 = 104.16V$$

* Chapter 4 →
(Circuits Theorems)




• Linearity Property :-

A system is said to be Linear System if it satisfies the following two properties :-

1. Scaling property :-

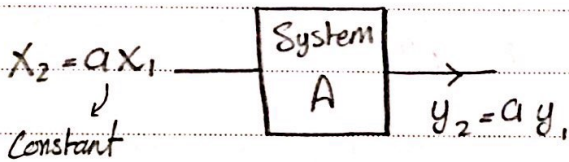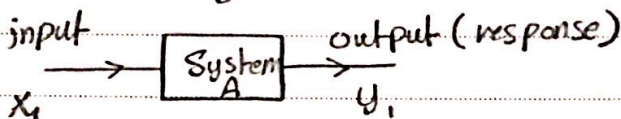

2. Additivity property :-

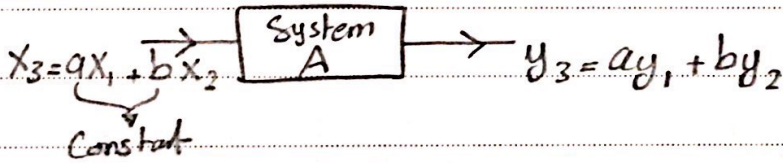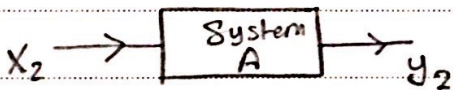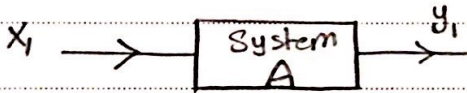


? When the electric circuit is linear?

Ans → when all of its elements are linear.

① The passive elements :- $\frac{R}{\Omega}$, $\frac{C}{F}$, $\frac{L}{H}$
are linear elements.

② The independent source :- are linear.

- check the resistor:-

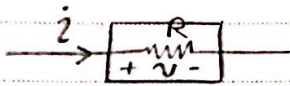

$$i_1 \Rightarrow v_1 = R i_1$$




$$i_2 = a i_1 \Rightarrow v_2 = R i_2$$

$$= R(a i_1)$$


$$= a R i_1$$

$$= a v_1$$

③ The dependant sources:-

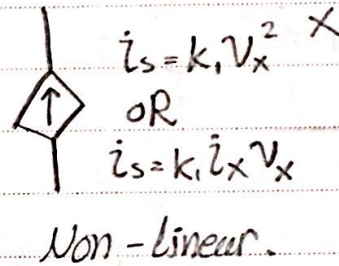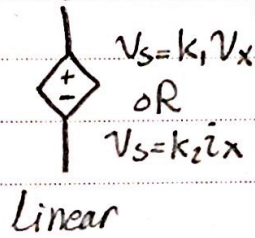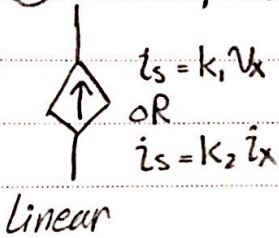

1 Superposition :-

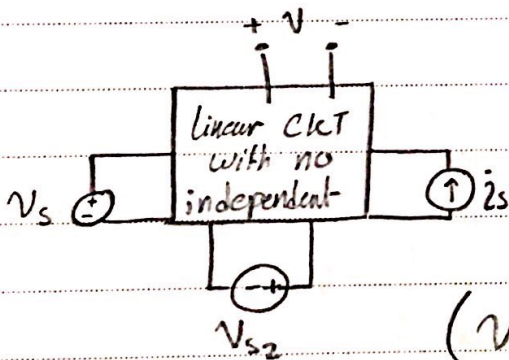

Find v using Superposition and Find P.

$$(v = v' + v'' + v''')$$



The value of v when v_{s2} & i_s are killed (off)
 v', p'

The value of v when v_s & i_s are killed
 v'', p''


The value of v when v_s & v_{s2} are killed
 v''', p'''

$$(i = i' + i'' + i''')$$

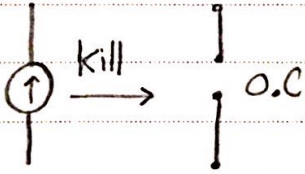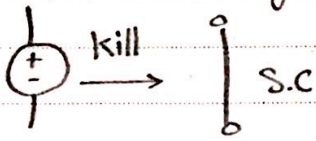- To kill a Voltage Source replace it by a (O-S).C



Ex:-

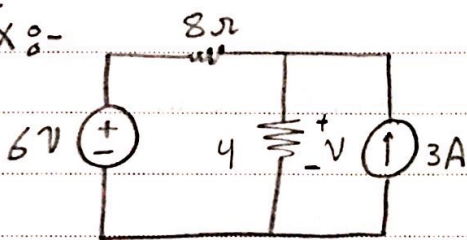


find v & $P_{4\Omega}$ using ① Nodal Analysis
② Super position.

Sol \rightarrow ①


$$v = 10, P_{4\Omega} = \frac{v^2}{4} = \frac{100}{4} = 25W$$

② using Super position

$$v = v' + v''$$

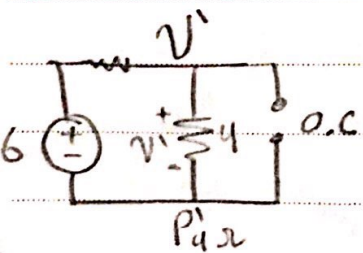


$$v' = \frac{4}{4+8} \cdot 6 = 2V$$

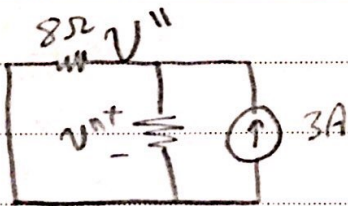

$$v'' = (3) \left(\frac{8}{4} \right) = 8V$$



$$\begin{aligned} v &= v' + v'' \\ &= 2 + 8 = 10V \\ P_{4\Omega} &= \frac{v^2}{4} = 25W \end{aligned}$$

Ex 2

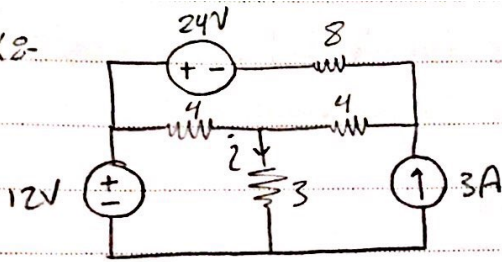


Find i using the super position method:-
 $i = i' + i'' + i'''$

Sol →

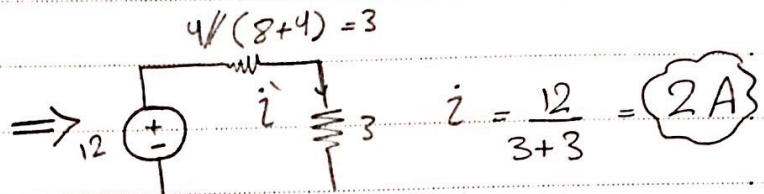
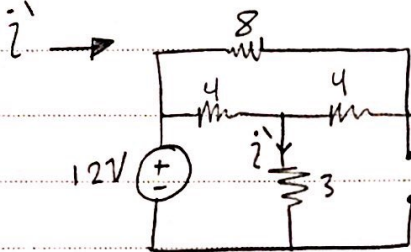


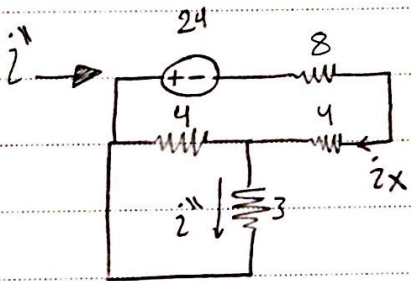open ckt, 3A, short-circuit, 24 Voltage Sor, like #



$$i_x = \frac{-24}{12 + \frac{12}{7}} = -1.75 \quad i'' = \frac{4}{4+3} i_x$$

$$i'' = \frac{4}{7} \times -1.75 = -1A$$

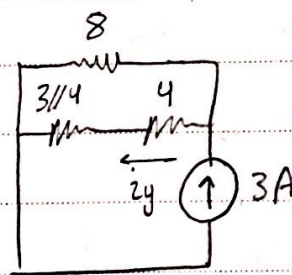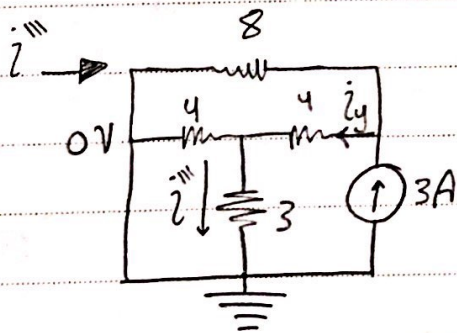


$$i_y = \frac{8}{4/3 + 8}$$

$$i''' = \frac{V}{4+3} i_y = 1A$$

$$i = i' + i'' + i'''$$

$$i = 2 + -1 + 1 = \boxed{2}$$

EX 8:

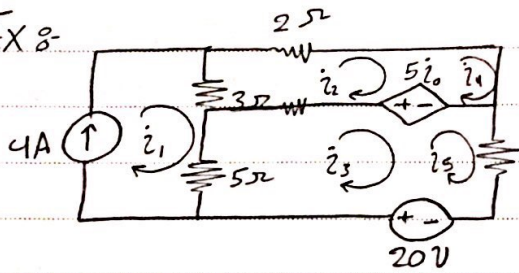

* Note: we don't kill the dependent sources.
 - Find i_o using Superposition.

$$i_o = i_o' + i_o''$$

i_o' :- mesh analysis

$$i_1 = 4$$

$$\text{mesh ②} \quad 6i_2 + 4i_3 - 32 \rightarrow \text{①}$$

$$\text{mesh ③} \quad -i_2 + 5i_3 = 0 \rightarrow \text{②}$$

Solve: ① & ② $i_2 = 80/17$

$$i_3 = 16/17$$

$$i_o' = i_1 - i_3$$

$$\boxed{52/17 \text{ A}}$$

i_o'' mesh analysis

mesh ④

$$6i_4 + 4i_5 = 0 \rightarrow \text{①}$$

mesh ⑤

$$-i_4 + 5i_5 = 20 \rightarrow \text{②}$$

Solving ① & ②


$$i_4 = -40/17$$

$$i_5 = 60/17$$

$$i_o'' = -5i_5 = \frac{-60}{17}, \quad i_o = \frac{52}{17} + \frac{-60}{17} = \boxed{\frac{-8}{17} \text{ A}}$$

$$i_o = \frac{52}{17} - \frac{8}{17} = \boxed{2.58 \text{ A}}$$


2] Source Transformation.

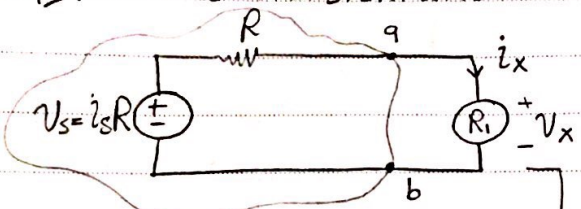

المصدر ان يكون $i_s = \frac{V_s}{R}$

$$V_x = \frac{R_1}{R_1 + R} V_s$$





$$i_x = \frac{V_s}{R_1 + R}$$

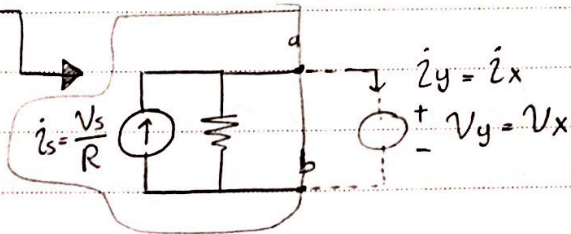

$$i_y = \frac{R}{R + R_1} i_s$$


$$= \frac{R}{R_1 + R} \cdot \frac{V_s}{R} = \frac{V_s}{R_1 + R} = i_x$$
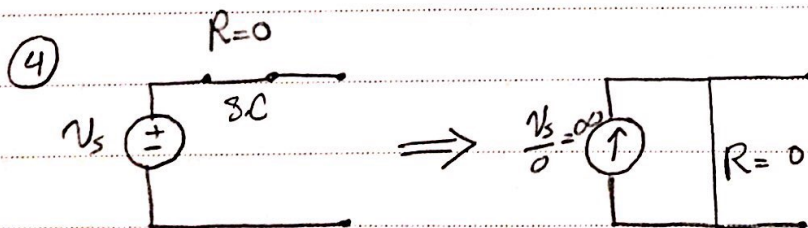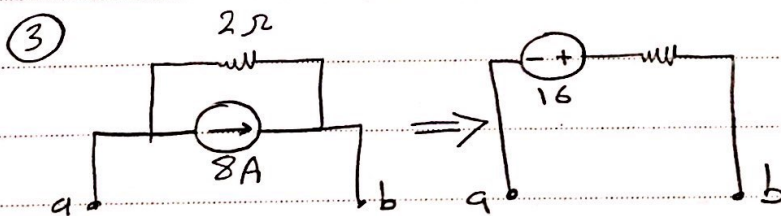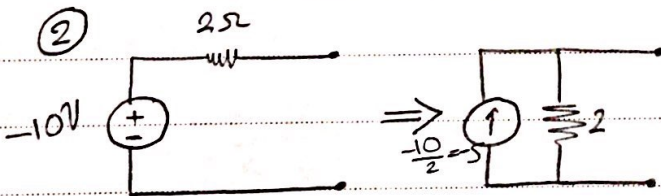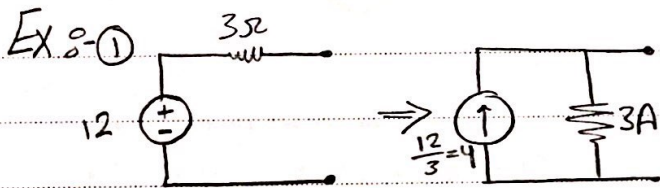
$$V_y = i_y R_1 = \frac{V_s R_1}{R_1 + R} = V_x$$




لا يمكن تحويل $R=0$ الى $R=\infty$ و $R=\infty$ الى $R=0$



Source Transformation :-

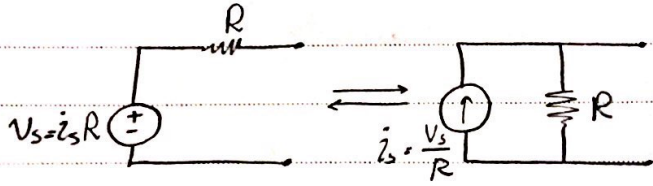

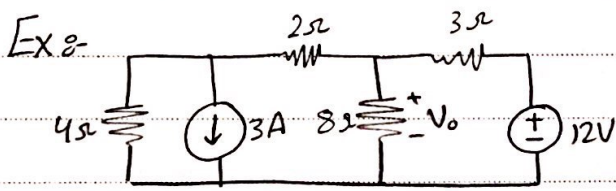Source transformation helps in simplifying :-
The ckt to be single-node ckt or single-loop.



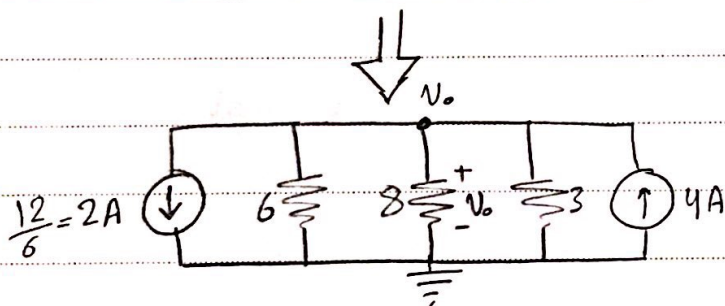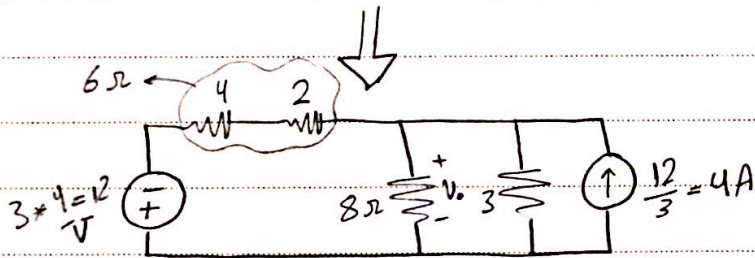Find V_o using source transformation
Sol. \rightarrow




Kcl at the node :-




$$-2 - \frac{V_o}{6} - \frac{V_o}{8} - \frac{V_o}{3} + 4 = 0$$

$$V_o = 3.2 \text{ V}$$



Ex 9

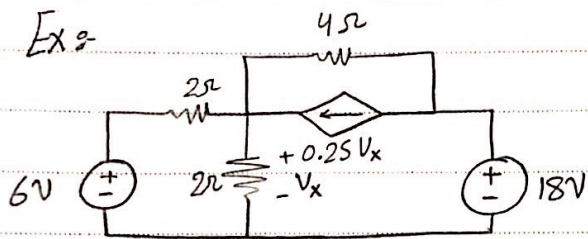

Find V_x using source transformation.

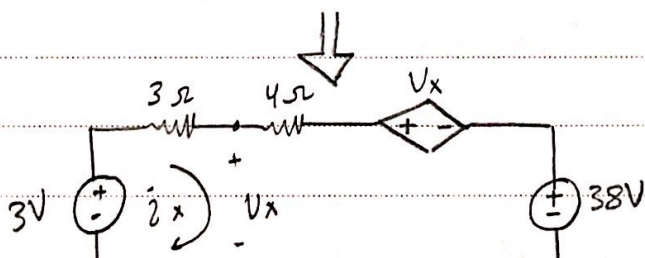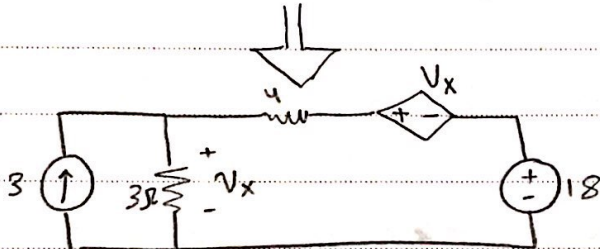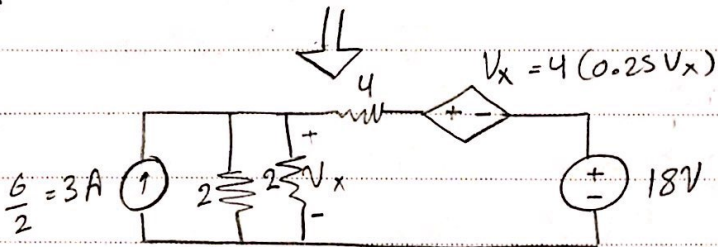


3 Thevenin Theorem:-

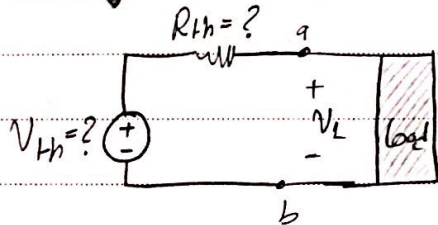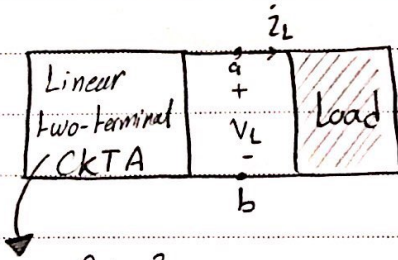

● How to find V_{Th} ?

ans:-

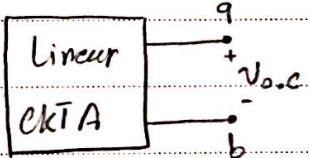


Find $V_{o.c}$ using ckt analysis

$V_{Th} = V_{o.c}$


● How to find R_{Th} ?

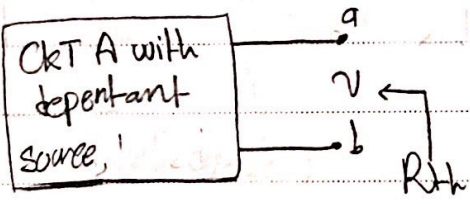Case I :- CKT A has independent Linear CKTA



$R_{Th} = R_{eq}$

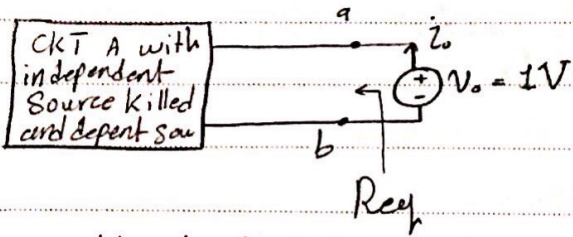Case II: CKT A has independent & dependent sources :-




- add a test voltage source V_o (usually 1V)
using CKT analysis find ?


$$R_{th} = R_{eq} = \frac{V_o}{i_o}$$

OR :- add test current source $i_o = 1A$

find V_o



$$R_{th} = \frac{V_o}{i_o}$$

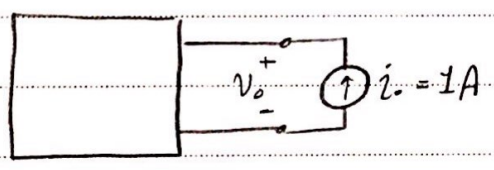

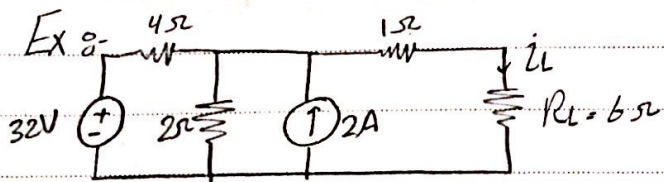

find the Thevenin equivalent CKT seen by R_L
 Then find i_L and power dissipated by R_L

Sol →

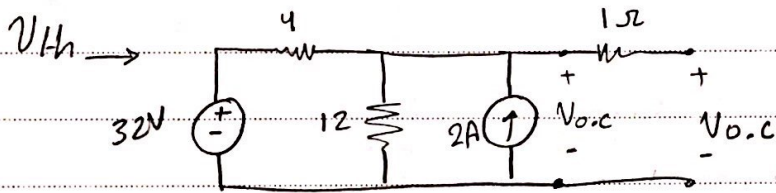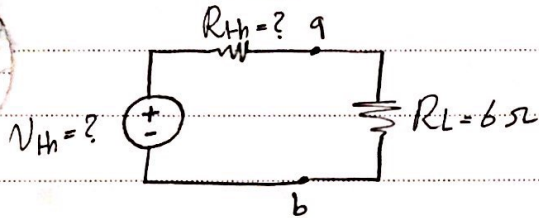

using nodal analysis :-


kcl at node ② →

$$\frac{V_{o.c} - 32}{4} + \frac{V_{o.c}}{12} = 2$$


$$V_{o.c} = 30V$$

$$V_{th} = 30V$$




R_{th} → kill all independent sources in CKT :-

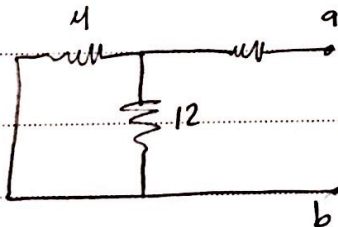

Ex 8-

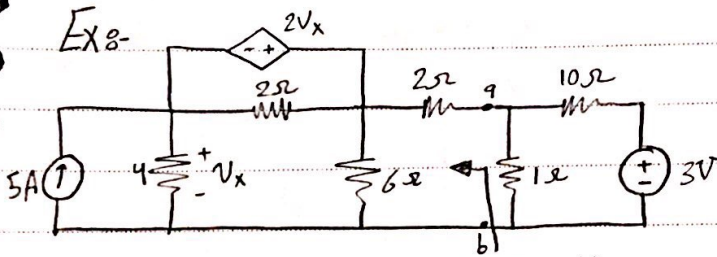

Determine the
Thevenin equivalent ckt ?

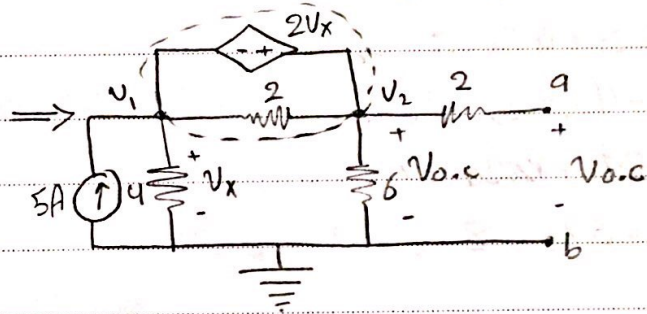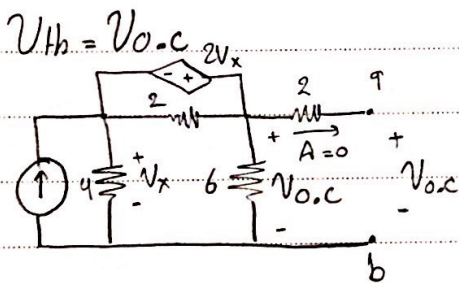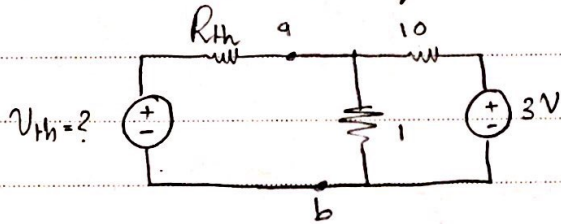

Kcl at the Supernode :-

$$5 = \frac{V_1}{4} + \frac{V_2}{6} \rightarrow \textcircled{1}$$

$$V_2 - V_1 = 2V_x, \quad V_x = V_1 \rightarrow \textcircled{2}$$

$$-3V_1 + V_2 = 0 \rightarrow \textcircled{2}$$


Solving ① & ②

$$V_1 = 20/3V$$

$$V_2 = 20V$$

$$\Rightarrow V_{o.c} = V_2 = 20V$$

Find R_{th} :-

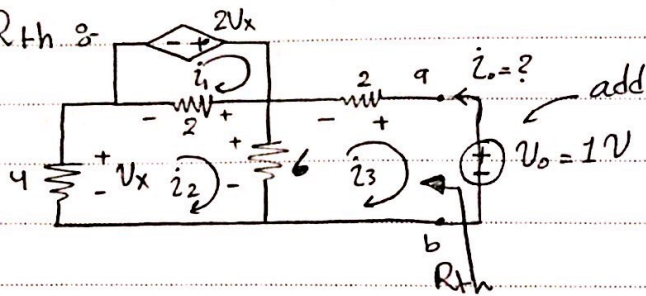

$$R_{th} = \frac{V_0}{i_0} = \frac{1}{i_0} \leftarrow ?$$

Find i_0 using ckt analysis

use mesh analysis \rightarrow

mesh ① $\rightarrow 2(i_1 - i_2) - 2V_x = 0$, $V_x = -4i_2$

$$\Rightarrow 2(i_1 - i_2) - 2(-4i_2) = 0$$

$$2i_1 + 6i_2 = 0 \rightarrow \text{①}$$

mesh ② $\rightarrow -4(-i_2) - 2(i_1 - i_2) + 6(i_2 - i_3) = 0$

$$-2i_1 + 12i_2 - 6i_3 = 0 \rightarrow \text{②}$$

mesh ③ $\rightarrow -6i_2 + 8i_3 = -1 \rightarrow \text{③}$


Solving ① & ② & ③ :-

$$i_1 = \frac{1}{6} A, i_2 = -1/18 A, i_3 = -1/6 A$$

$$i_0 = -i_3 = 1/6 A$$

$$R_{th} = \frac{V_0}{i_0} = \frac{1}{1/6} = 6$$


4] Norton Equivalent CKT :-

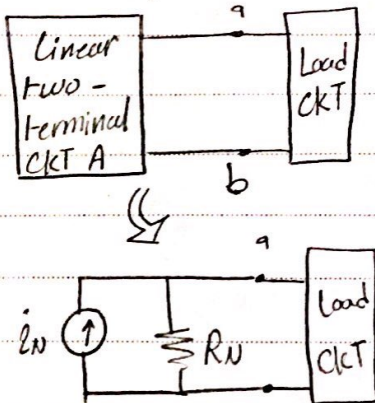


$R_N = R_{Th}$ → always.

Method ① :-


Find the Thevenin CKT :-

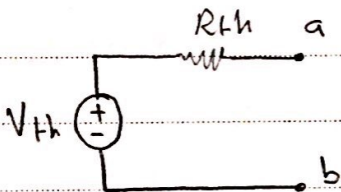

Then by source Transformation →

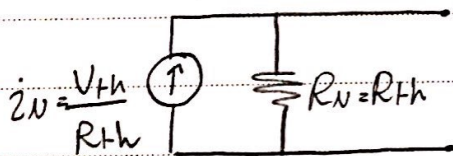



Method ② :-

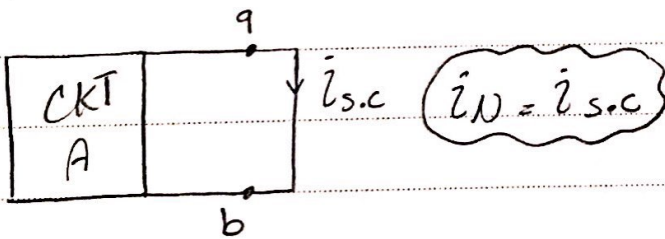

$$R_N = R_{Th}$$

same steps
we follow to
find R_{Th} .

Ex 8-

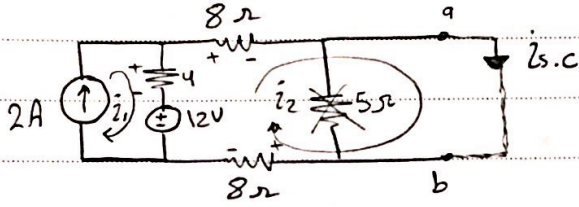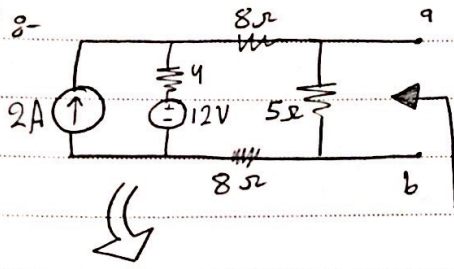

Sol $\rightarrow (i_N = i_{s.c})$

using mesh analysis :-


$$i_1 = 2A \quad \left. \begin{array}{l} -12 - 4(2 - i_2) + 8i_2 + 8i_2 = 0 \\ 20i_2 = 20 \\ i_2 = 1 \end{array} \right\}$$

$$20i_2 = 20$$

$$i_2 = 1$$


$$i_{s.c} = i_2 = 1A$$

$R_N = R_{th}$

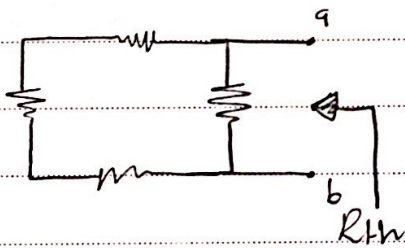



$$= (8 + 4 + 8) // 5$$

$$= 4\Omega$$

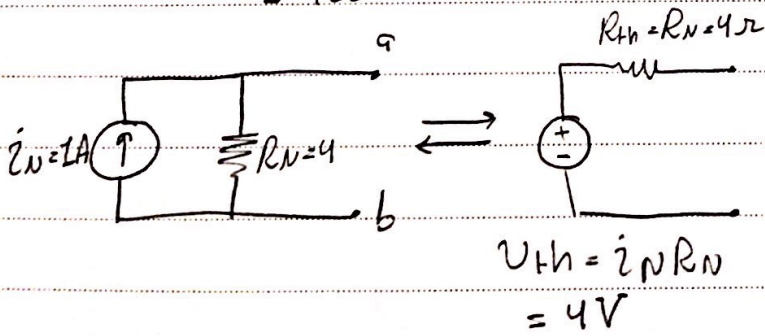


$$V_{th} = i_N R_N = 4V$$

Ex 8

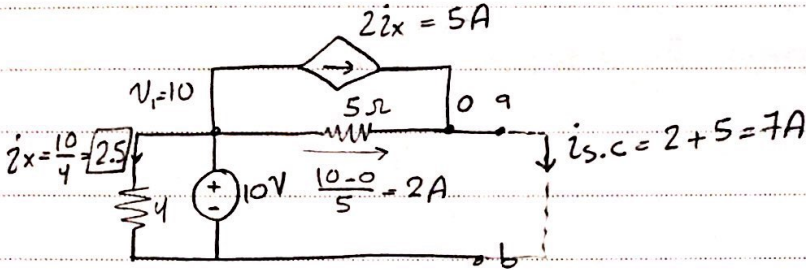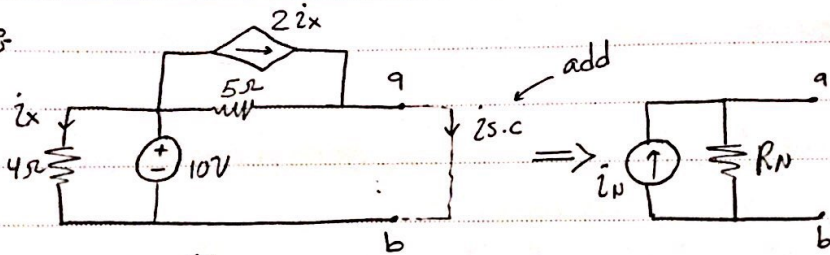


Sol $\rightarrow i_{s.c} = i_N = \boxed{7A}$

$R_N = R_{th}$

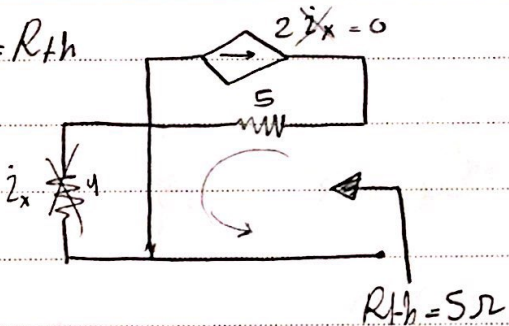


* Maximum Power Transfer :-

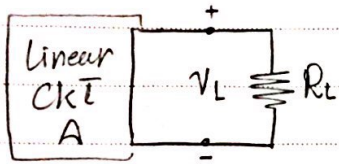

What is the value of \$R_L\$ such that it will absorb the maximum power :-

$$P_L = i_L^2 R_L \quad \text{Find } R_L \text{ when } P_L = P_L^{\max}$$

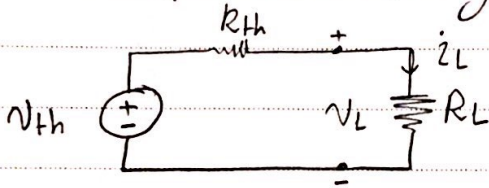Replace Ckt A by its Thevenin equivalent :-



$$P_L = i_L^2 R_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$

To find \$R_L\$ that maximum \$P_L\$:-

$$\frac{dP_L}{dR_L} = \frac{(R_{th} + R_L)^2 V_{th}^2 - V_{th}^2 R_L 2(R_{th} + R_L)}{(R_{th} + R_L)^4} = 0$$


$$(R_{th} + R_L)^2 V_{th}^2 - V_{th}^2 R_L 2(R_{th} + R_L) = 0$$

$$(R_{th} + R_L) - 2R_L = 0$$

$$R_{th} - R_L = 0 \rightarrow R_L = R_{th}$$

$$P_L^{\max} = \frac{V_{th}^2 R_{th}}{(R_{th} + R_{th})} \Rightarrow P_L^{\max} = \frac{V_{th}^2}{4 R_{th}}$$

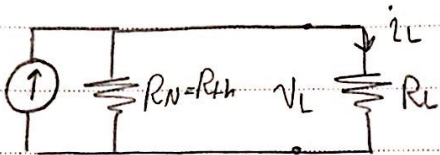if we replace CKTA by its Norton equivalent e-









$$① P_L = i_L^2 R_L = \left(\frac{R_N i_N}{R_N + R_L} \right)^2 R_L$$

$$\frac{dP_L}{dR_L} = 0 = 0 \rightarrow R_L = R_N = R_{Th}$$

$$P_L^{max} = \frac{i_N^2 R_N}{4}$$

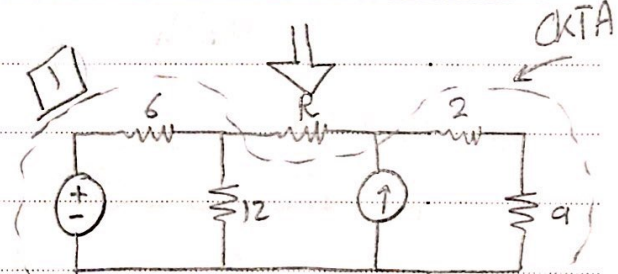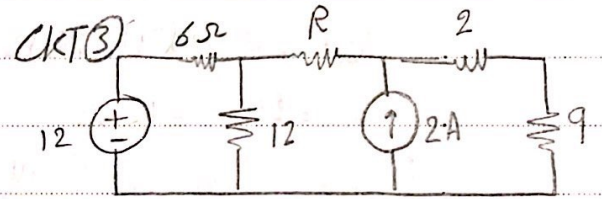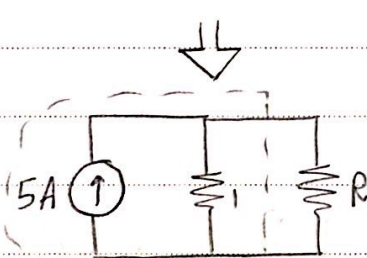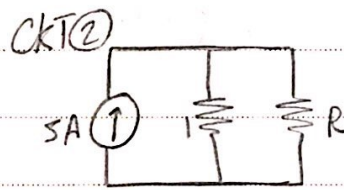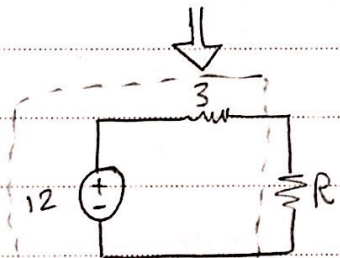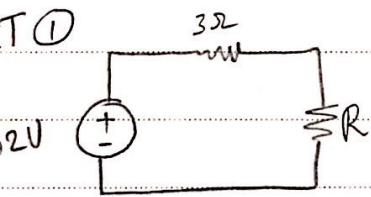Ex:- For each of following CKTs determine the value of R such that it will absorb the maximum Power and then find that max power:-





$$V_{th} = V_{oc} = V_a - V_b$$

$$V_a = \frac{12}{12+6} \cdot 12 = 8V$$

$$V_b = 2(2+9) = 22V$$

$$V_{th} = 8 - 22 = -14V$$

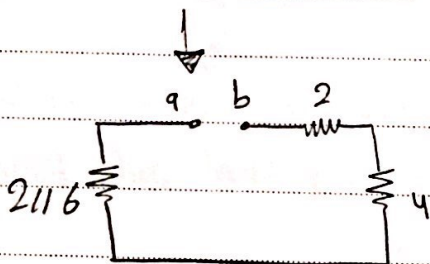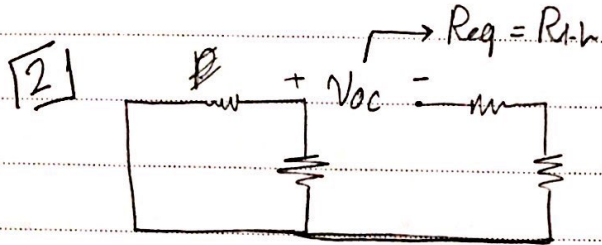


$$R_{th} = 4 + 2 + 9 = 15\Omega$$




$$R = R_{th} = 15\Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(-14)^2}{(4)(15)}$$


* practice 8-

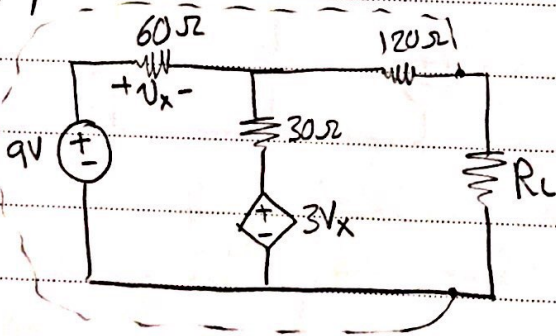

Find R_L to absorb the max power.

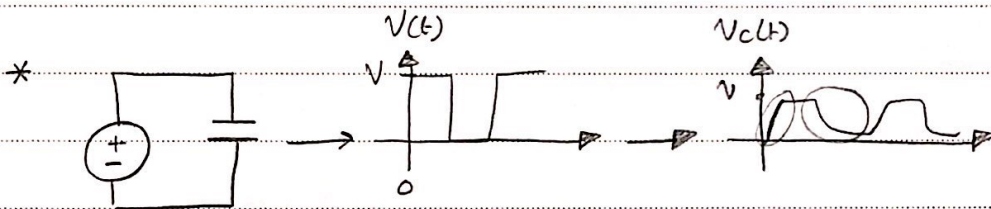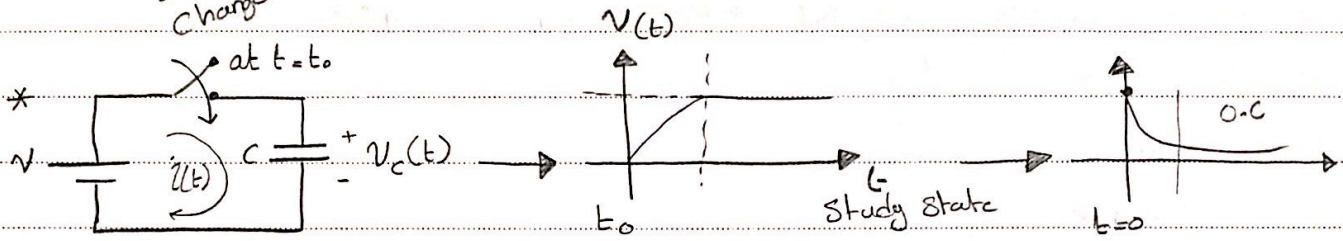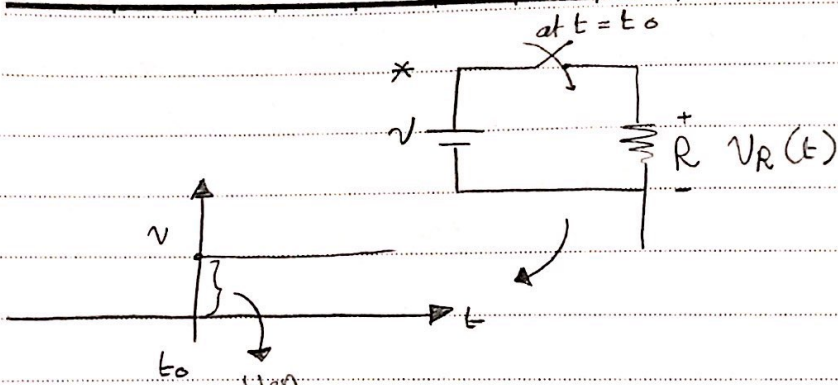

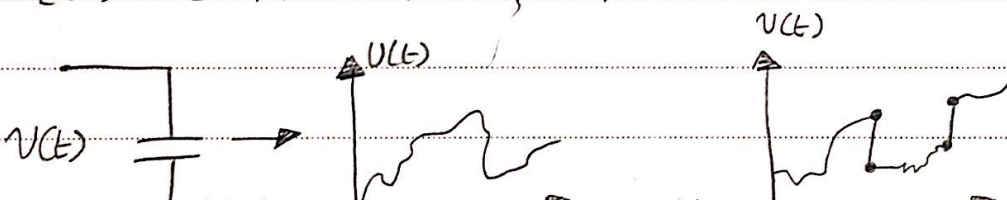Note :- The capacitor resists the Sudden change of V .
 $V_c(t)$:- Continuous function of t .



* Voltage - Current relationship in Capacitors :-


$$q(t) = C v(t)$$

$$\frac{dq}{dt} = C \frac{dv(t)}{dt}$$

$$\Rightarrow i(t) = C \frac{dv(t)}{dt}$$

$v(t), i(t) \rightarrow$ Both have same sign (charging), opposite sign (discharging)

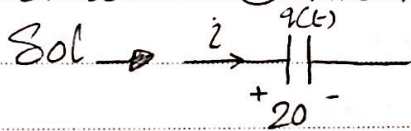Ex:- (a) Calculate the charge stored on a 3 pF capacitor with 20V across it. (b) Find the current.




(a) $q(t) = C v(t)$

$$= (3 \text{ pF})(20 \text{ V})$$

$$= 60 \text{ pC} = Q$$

(b) $i = 0$ (in steady state)

Ex:-

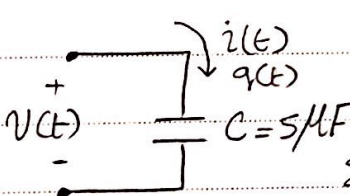


$$v(t) = 10 \cos(6000t) \text{ V}$$

Find $q(t)$ & $i(t)$



Sol $\rightarrow q(t) = C v(t) = 50 \cos(6000t) = \mu\text{C}$

$$i(t) = C \frac{dv}{dt} = -(5 \times 10^{-6})(10)(6000) \sin(6000t) \text{ A}$$

$$= -0.3 \sin(6000t) \text{ A}$$

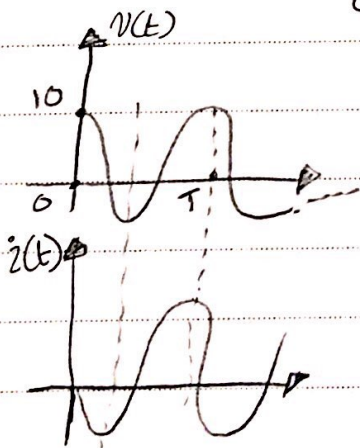


Ex:-

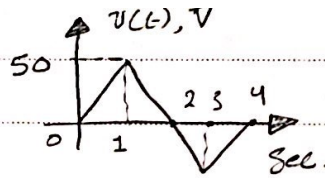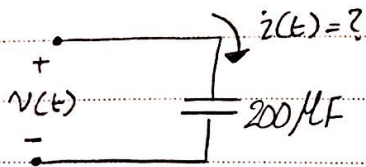

Sol:- $i(t) = C \frac{dv(t)}{dt}$

$$v(t) = \begin{cases} 50t, & 0 < t < 1 \\ 100 - 50t, & 1 < t < 3 \\ -200 + 50t, & 3 < t < 4 \end{cases}$$
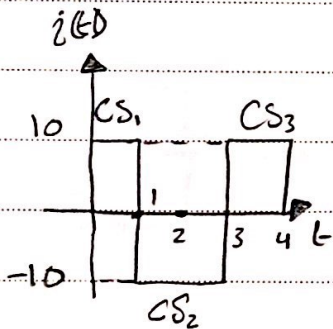
$$i(t) = C \frac{dv(t)}{dt} = \begin{cases} (200 \cdot 10^{-6})(50) = 10 \text{ mA}, & 0 < t < 1 \\ (200 \cdot 10^{-6})(-50) = -10 \text{ mA}, & 1 < t < 3 \\ 10 \text{ mA}, & 3 < t < 4 \end{cases}$$



* Find $v(t)$ from $i(t) =$

$$i(t) = C \frac{dv}{dt} \Rightarrow \frac{1}{C} \int_{t_0}^t i(t) dt = \int_{v(t_0)}^{v(t)} dv(t)$$

$$\Rightarrow v(t) - v(t_0) = \frac{1}{C} \int_{t_0}^t i(t) dt$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0) \quad (*)$$



t_0 = initial time
 $v(t_0)$ = Capacitor voltage
 at $t = t_0$ } always given

$$v(t_0) = \frac{q(t_0)}{C} \quad \text{initial stored charge}$$

Ex: Let $i(t) = 6e^{-300t}$

Find $v(t) = ?!$

Such that $v(0) = 0 \text{ V}$

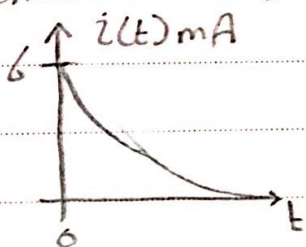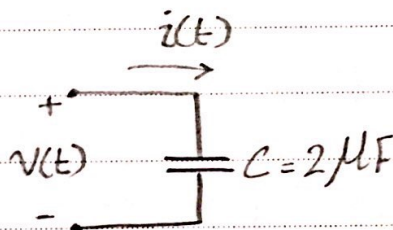


using (*)



$$v(t) = \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-300t} \times 10^{-3} dt + 0$$

$$\Rightarrow \frac{10^{-3}}{2 \times 10^{-6}} \left(\frac{6e^{-3000t}}{-3000} \right)$$

$$= - \left[e^{-3000t} - 1 \right]$$

$$= 1 - e^{-3000t}$$

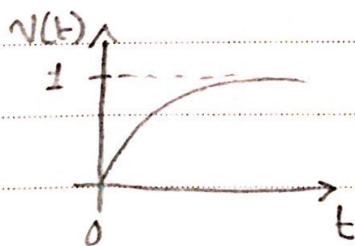

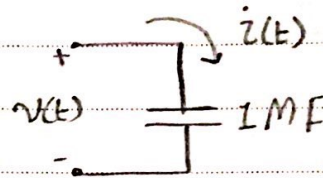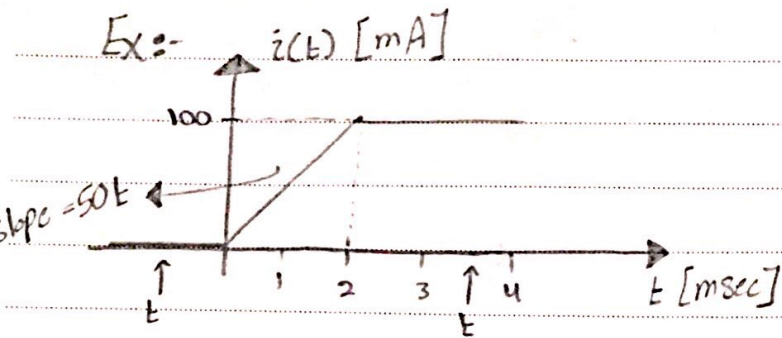

Find $V(t)$? $V(-\infty) = 0 \text{ V}$

Case I: $t \leq 0$, $V(t) = \frac{1}{10^{-3}} \int_{-\infty}^t 0 dt + V(-\infty)$

$$V(t) = 0 \text{ V}$$

Case II: $0 < t \leq 2$

$$V(t) = \frac{1}{10^{-3}} \int_0^t 50t dt + V(0), \quad V(0) = 0 \rightarrow \text{Laplace rule}$$

$$V(t) = \frac{1}{10^{-3}} \int_0^t 50t dt + V(0)$$

$$= 10^{+3} \times \frac{50t^2}{2} \Big|_0^t = 25t^2 \times 10^{+3} \text{ V}$$

$$V(2) = 25 \times (2 \times 10^{-2})^2 \times 10^{+3}$$

$$= 0.1 \text{ V}$$

Case III: $2 < t$

$$V(t) = \frac{1}{10^{-3}} \int_{2 \text{ mSec}}^t 100 \times 10^{-3} dt + V(2 \text{ Sec})$$

$$= \frac{1}{10^{-3}} \times 100 \times 10^{-3} (t - 2 \times 10^{-3}) + 0.1 \text{ V}$$

$$V(t) = \begin{cases} 0, & t \leq 0 \\ 25t^2 \times 10^{-3}, & 0 < t \leq 2 \\ 100(t - 0.02) + 0.1, & 2 < t \end{cases}$$


$\rightarrow q(3) = 10^{-3} (100(3 \times 10^{-3} - 0.02) + 0.1)$

95

* Energy stored in the Capacitor :-

$$P(t) = V(t) i(t)$$

$$P(t) = \frac{dw(t)}{dt}$$

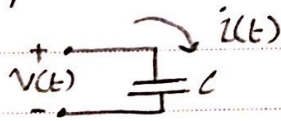

$$W(t) = ?$$

$$q(t) = V(t) C$$

$$W(t) = \int_{t_0}^t P(t) dt + W(t_0)$$

↘ initial stored energy

$$= \int_{t_0}^t V(t) i(t) dt + W(t_0)$$

$$= \int_{V(t_0)}^{V(t)} C V' dt + W(t_0)$$

$$\Rightarrow W(t) = \int C V' dV' + W(t_0)$$

$$W(t) = \left(C \frac{V'^2}{2} \right)_{V(t_0)}^{V(t)} + W(t_0)$$


$$W(t) = \frac{1}{2} C V^2(t) - \frac{1}{2} C V^2(t_0) + W(t_0)$$

$$W(t) = \frac{1}{2} C V^2(t) \text{ "J"}$$

$$* P(t) = \frac{dw(t)}{dt} \text{ "Watt"}$$

$$q(t) = C V(t) \Rightarrow V(t) = \frac{q(t)}{C}$$
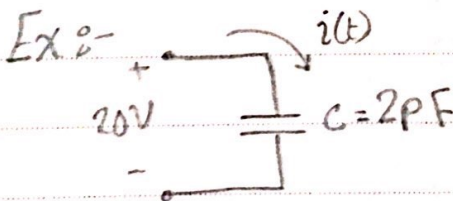
$$W(t) = \frac{q^2(t)}{2C} \Rightarrow *$$



$$\textcircled{1} q(t) = C V(t) = 20 \times 3 \text{ pF} = 60 \text{ pC}$$


$$\textcircled{2} i(t) = C \frac{dV}{dt} = 0 \text{ A (} \frac{\Delta}{\Delta t} = 0 \text{ C)}$$

$$\textcircled{3} W(t) = \frac{1}{2} C V^2(t) = \frac{1}{2} (20)^2 (3 \text{ pF}) = 600 \text{ pJ}$$

$$\textcircled{4} P(t) = \frac{dw}{dt} = 0 \text{ Watt}$$

* Ex 2:

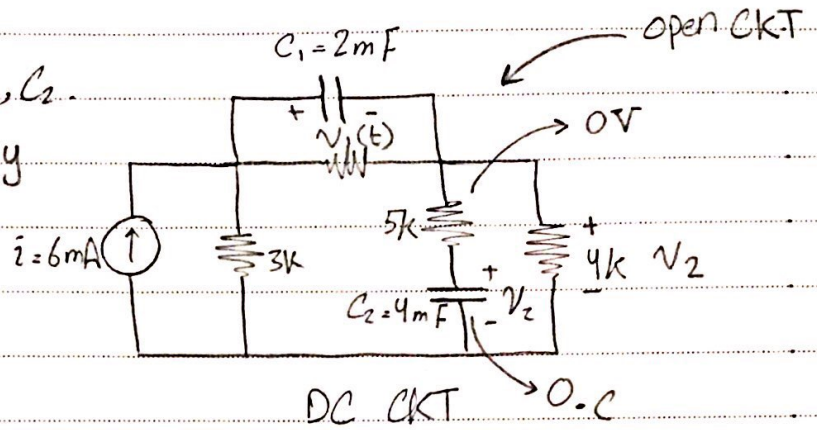1. Find the energy stored in C_1, C_2 .
2. Find the energy dissipated by the $3k\Omega$ resistor.



$$i_x = \frac{3k}{3k+6k} * 6mA$$




$$i_x = 2mA$$


$$v_1 = 2mA (2k\Omega) = 4V$$

$$v_2 = 2mA (4k\Omega) = 8V$$

$$w_1(t) = \frac{1}{2} * 2Fm * 4^2 = 16mJ$$
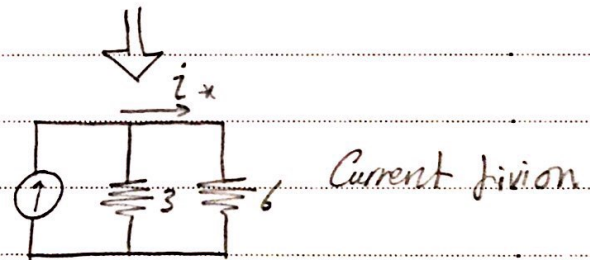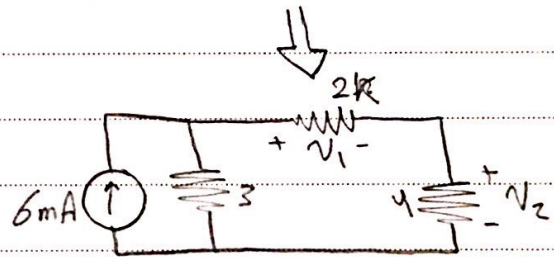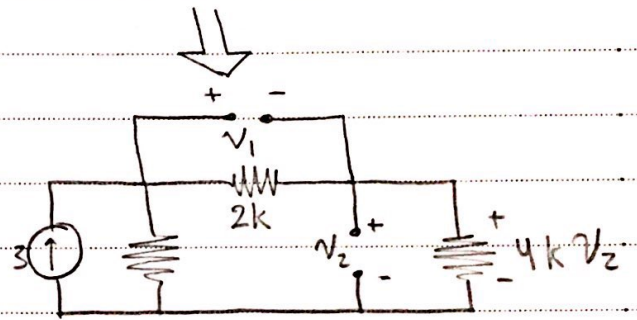
$$w_2(t) = \frac{1}{2} C_2 v_2^2 = \frac{1}{2} * 4mF * 8^2 = 128mJ$$



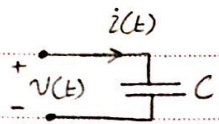

$$q(t) = C v(t)$$

$$i(t) = C \frac{dv(t)}{dt}$$


DC - Ckt :- $i(t) = 0$

—|— \cong O.C
(steady state)


$$W_c(t) = \frac{1}{2} C v^2(t)$$

$$= \frac{q^2(t)}{2C} \text{ "J"}$$

* practice :-

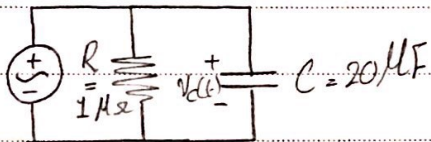

$$v(t) = 100 \sin(2\pi t) \text{ V}$$

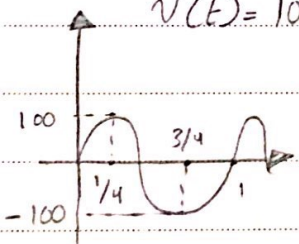


Find (a) $W_c(t) = \dots ?$ ($0.1 \sin^2(2\pi t) \text{ J}$)

(b) $W_R(t) = \dots ??$


$$P(t) = i^2 R = \frac{v^2}{R}$$

• Capacitors in parallel :-

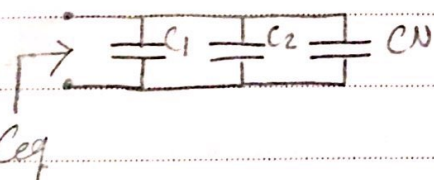



$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

• Capacitors in Series :-

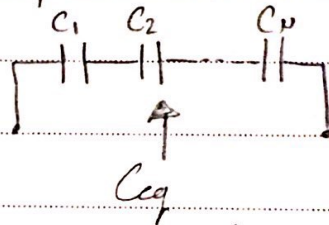
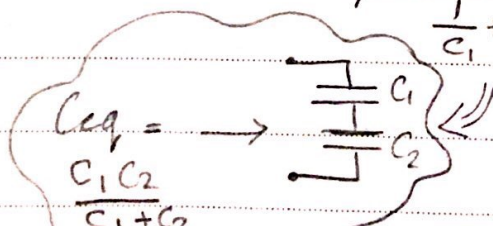
$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_N}}$$



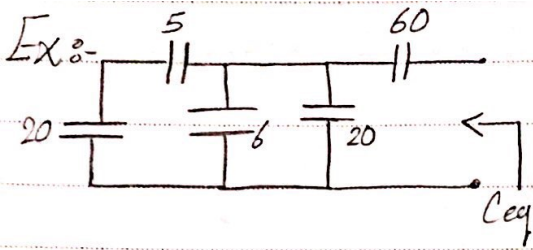


Sol $\rightarrow \frac{(5)(20)}{5+20} = 4 \mu F$

$4 \mu F + 6 \mu F + 20 \mu F = 30 \mu F$


$\frac{(30) \mu (60) \mu}{30 \mu + 60 \mu} = 20 \mu F \rightarrow \left[\begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} \right] 20 \mu F$

Ex:-

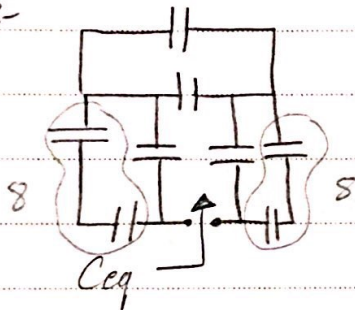

all Capacitors are $4 \mu F$.

Sol $\rightarrow C_{eq} = 2.1818 \mu F$


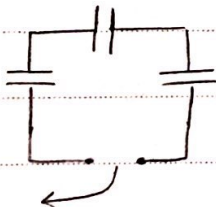


$C_{eq} = \frac{1}{\frac{1}{4} + \frac{1}{4} + \frac{1}{4}} = 2.1818$


[2] Inductors

Symbol \rightarrow 

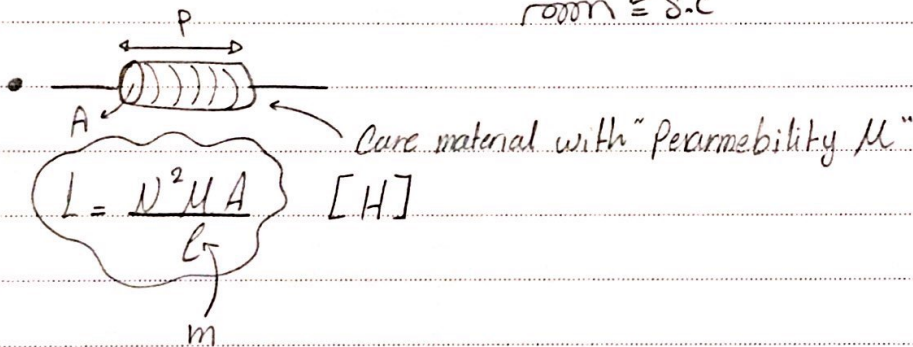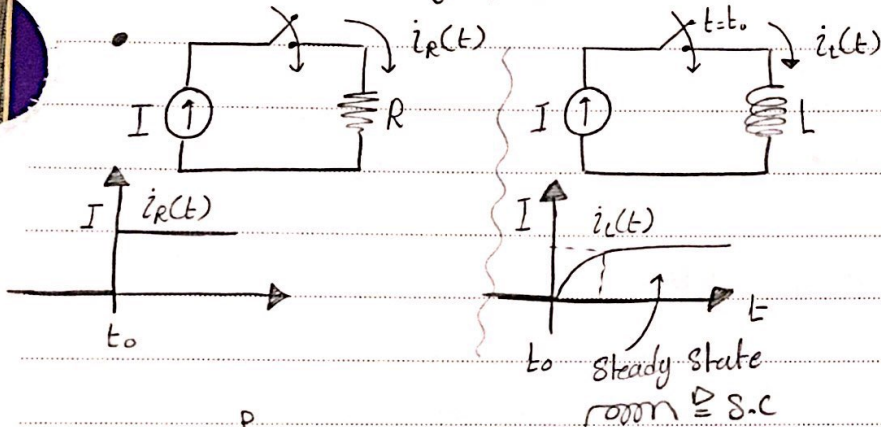
- passive element.
- Store energy as magnetic field
- The inductor has "inductance" L with unit "Henry" (H)



- Current - Voltage - relationship.
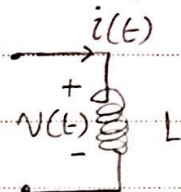
$$V(t) = L \frac{di(t)}{dt}$$

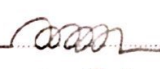
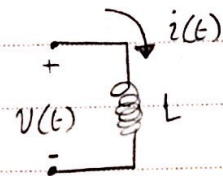
if $i(t) = I$ (DC) (KT)

$V(t) = 0V$, i.e.  \cong S.C.
in DC

$$i(t) = \frac{1}{L} \int_{t_0}^t V(t) dt + i(t_0)$$

$t_0 \cong$ initial time.
 $i(t_0) \cong$ initial current.


• energy stored in the inductor :-

$$w(t) = \frac{1}{2} L i^2(t)$$


proof :-

$$w(t) = \int_{t_0}^t P(t) dt + w(t_0)$$
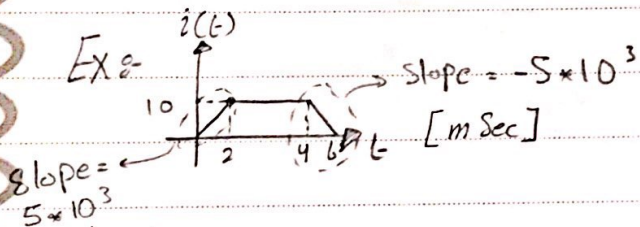
$$= \int_{t_0}^t L \frac{di(t)}{dt} (i) dt + w(t_0)$$




Find $v(1 \text{ mSec}) = ? \Rightarrow 25 \text{ V}$


$v(3 \text{ mSec}) = ? \Rightarrow 0$

$v(5 \text{ mSec}) = ? \Rightarrow -25 \text{ V}$

Sol :- $v(t) = L \frac{di}{dt}$

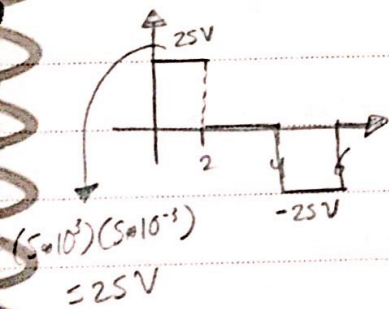


Ex 8

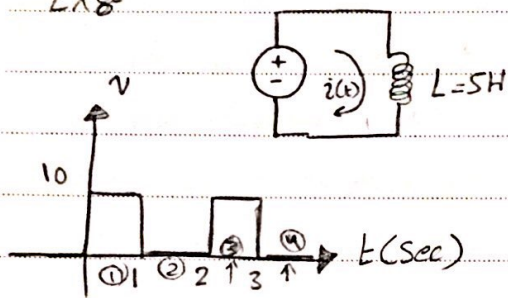

Find $i(t)$?!

$$i(0) = -1 \text{ A}$$

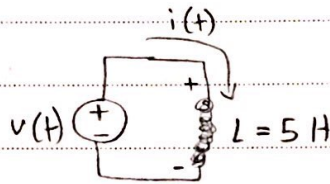

Sol.

$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$0 < t < 1; i(t) = \frac{1}{5} \int_0^t 10 dt + (-1) \Rightarrow \frac{1}{5} (10t) - 1 \Rightarrow 2t - 1 \text{ A}$$

$$1 < t < 2; i(t) = \frac{1}{5} \int_1^t 0 dt + i(1)$$


$$\Rightarrow i(1) = (2)(1) - 1 = 1 \text{ A}$$

$$2 < t < 3; i(t) = \frac{1}{5} \int_2^t 10 dt + i(2)$$


$$= 2(t-2) + 1$$

$$= 2t - 3 \text{ A}$$
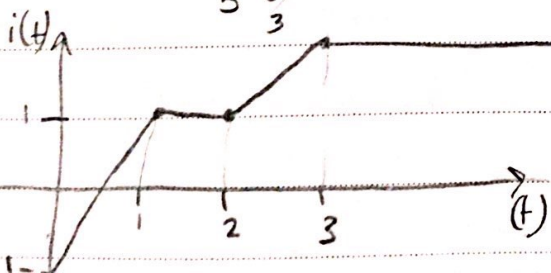
$$3 < t; i(t) = \frac{1}{5} \int_3^t 0 dt + i(3) = i(3) = (2)(3) - 3 = 3 \text{ A}$$



Ex:-

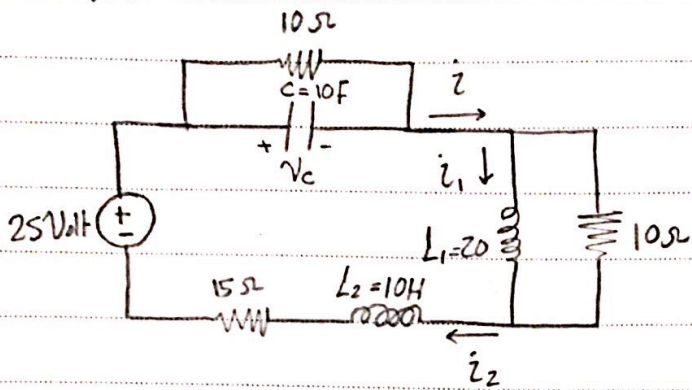

Find the w_L, w_{L_1}, w_{L_2} under the steady state condition.


Sol:-

DC - Ckt \rightarrow = O.C
= S.C

$$w_C = \frac{1}{2} C V^2$$

$$w_{L_1} = \frac{1}{2} L_1 i_1^2$$

$$w_{L_2} = \frac{1}{2} L_2 i_2^2$$

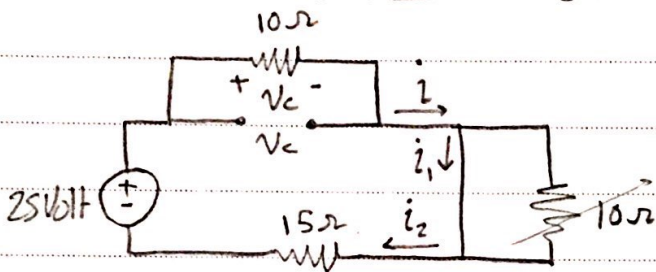

$$V_c = \frac{10}{10+15} * 25 = 10 \text{ Volt}$$


$$i_1 = i_2 = \frac{25}{10+15} = 1 \text{ A}$$

$$w_L = \frac{1}{2} (10) (10)^2 = 500 \text{ J}$$

$$w_{L_1} = \frac{1}{2} (20) (1)^2 = 10 \text{ J}$$

$$w_{L_2} = \frac{1}{2} (10) (1)^2 = 5 \text{ J}$$



* Series Induction :-

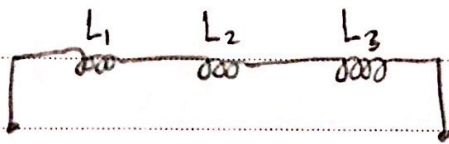

$$L_{eq} = L_1 + L_2 + \dots + L_N$$


* parallel Induction
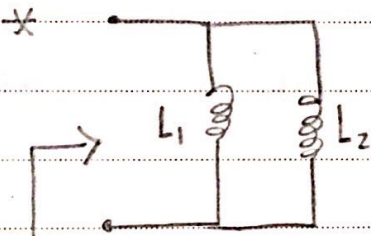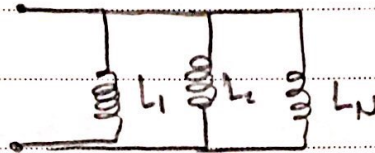
$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}}$$



$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

* Exe-

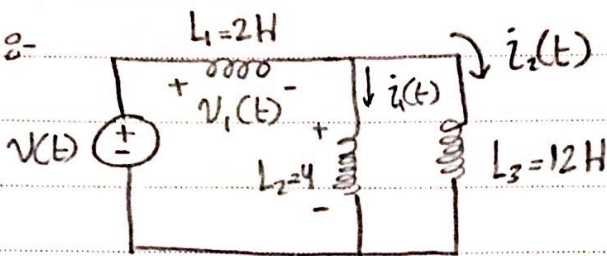

$$\text{Let } i(t) = 8 - 4e^{-10t} \text{ mA}$$

$$i_2(0) = -1 \text{ mA}$$


Find $i_1(0)$, $v(t)$, $v_1(t)$, $v_2(t)$, $i_1(t)$, $i_2(t)$

$$\boxed{a} \quad i(t) = i_1(t) + i_2(t)$$

$$i(0) = i_1(0) + i_2(0)$$

$$4 - (-1) = 5 \text{ mA}$$

\boxed{b}

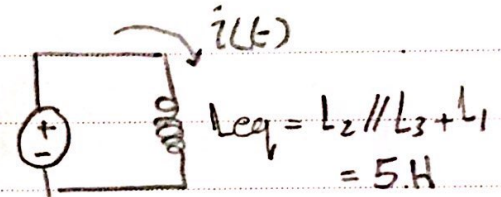

$$v(t) = L_{eq} \frac{di(t)}{dt} = 5(-4)(-10)$$

$$= 200e^{-10t} \text{ mV}$$

$$v_1(t) = L_1 \frac{di_1(t)}{dt} = 2(-4)(-10)e^{-10t} = 80e^{-10t} \text{ mV}$$


$$v_2(t) = v(t) - v_1(t) = 120e^{-10t} \text{ mV}$$

$$i_1(t) = \frac{1}{L_2} \int_0^t v_2(t) dt + i_1(0) = \frac{1}{4} \int_0^t 120e^{-10t} dt + 5 \text{ mA}$$

$$30 \left(\frac{e^{-10t}}{-10} \right) + 5 \rightarrow 8 - 3e^{-10t} \text{ mA}$$


$$i_2(t) = i(t) - i_1(t) = 8 - 4e^{-10t} - 8 + 3e^{-10t} = -e^{-10t} \text{ mA}$$

CH7 :- 1st order CKTs (RC and RL CKTs)

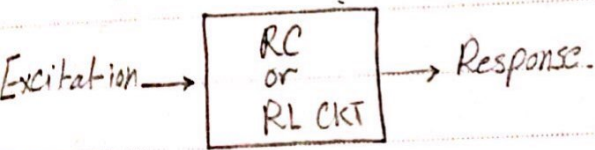


Two Types of Excitation


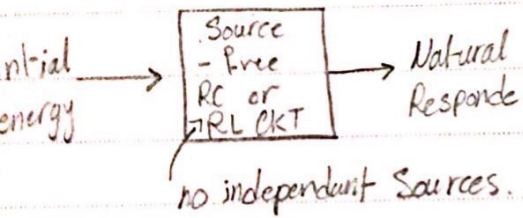
[1] Initial stored energy
(Source-free CKTs)
"initial conditions"



[2] Driven CKTs :-

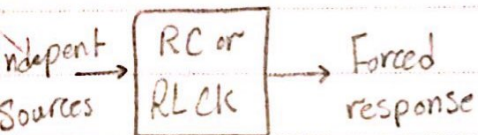

① Source-Free RC CKT

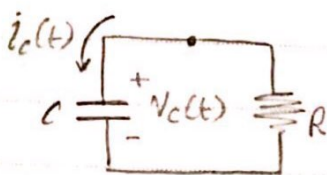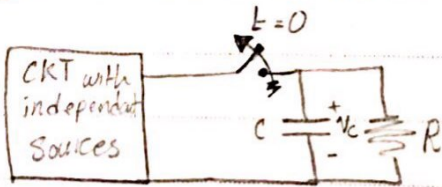

$$v_c(0) = V_0$$

$$W_c(0) = \frac{1}{2} C V_0^2$$

} initial conditions

} obtain form

$t < 0$ CKT

* Find $V_c(t)$, $t > 0$ Natural response

$$i_c(t) + i_R(t) = 0$$

$$C \frac{V_c(t)}{dt} + \frac{1}{R} V_c(t) = 0 \quad (*) \leftarrow \text{1st order Differ. equations.}$$

$$\Rightarrow \text{proposed solution :- } V_c(t) = A e^{Bt} \quad (**)$$

Find A & B

$$V_c(0) = A e^{B(0)} = V_0$$


$$\Rightarrow \boxed{A = V_0}$$

Sub $(**)$ into $(*)$:-

$$C [A B e^{Bt}] + \frac{1}{R} A e^{Bt} = 0$$

$$\Rightarrow CB + \frac{1}{R} = 0 \Rightarrow B = -1/RC$$
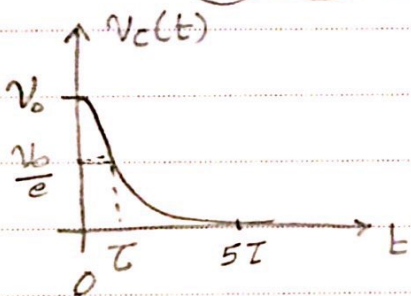
$$\Rightarrow V_c(t) = V_0 e^{-t/RC} \quad t > 0$$



The $-t$ is discharging

$$V_c(\infty) = 0, W_c(\infty) = 0 \text{ J}$$

• Time Constant τ :-

$$V_c(\tau) = \frac{V_0}{e}$$

$$V_0 e^{-\tau/RC} = V_0 e^{-1}$$

$$\rightarrow \tau/RC = 1 \Rightarrow \boxed{\tau = RC}$$

$$\left. \begin{array}{l} V_c(5\tau) \approx 0 \text{ V} \\ W_c(5\tau) \approx 0 \text{ J} \end{array} \right\}$$


• Energy Dissipated by R: $w_R(t), t > 0$

$$P_R(t) = v_R(t) i_R(t) \\ = \frac{v_R^2(t)}{R} = \frac{v_C^2(t)}{R} = \frac{V_0^2}{R} e^{-2t/RC}$$

$$w(t) = \int_0^t P_R(\lambda) d\lambda + w_R(0)$$

$$\int_0^t \frac{V_0^2}{R} \cdot e^{-2\lambda/RC} d\lambda = \frac{V_0^2}{R} \left[\frac{e^{-2\lambda/RC}}{-2/RC} \right]_0^t = -\frac{1}{2} V_0^2 \left[e^{-2t/RC} - 1 \right]$$
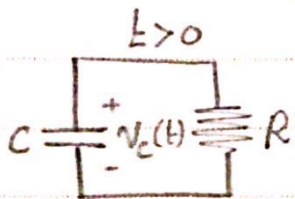
$$= \frac{1}{2} V_0^2 \left[1 - e^{-2t/RC} \right] \text{ J, } t > 0$$





$$= -\frac{1}{2} C V_0^2 \left[e^{-2t/RC} - 1 \right]$$

$$= \frac{1}{2} C V_0^2 \left[1 - e^{-2t/RC} \right] \text{ J, } t > 0$$

$$w_R(0) = 0 \text{ J}$$


$$w_R(\infty) = \frac{1}{2} C V_0^2$$

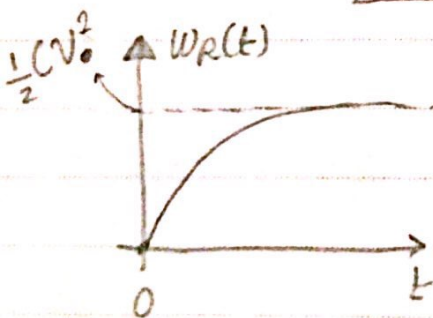

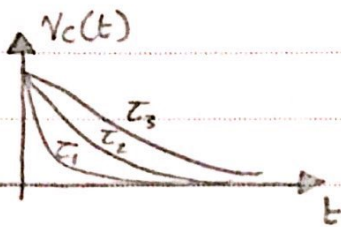

$$\tau_1 < \tau_2 < \tau_3$$

$$\tau = RC$$

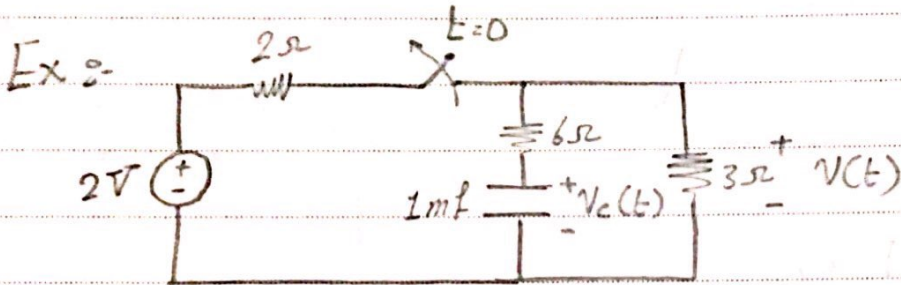

Find (a) $W_C(0)$


(b) $V_C(t)$, $t > 0$

(c) $V(t)$, $t > 0$

Sol. \rightarrow

(a) $W_C(0) = \frac{1}{2} C V_C^2(0)$

Find $V_C(0)$ from $t < 0$ CKT :-

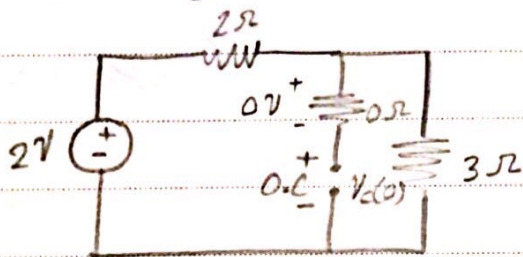


$$V_C(0) = \frac{3}{3+2} (2V) = 1.2V$$

$$W_C(0) = \left(\frac{1}{2}\right) (1 \times 10^{-5}) (1.2)^2$$

$$= 0.72 \text{ mJ}$$

(b) $t > 0$

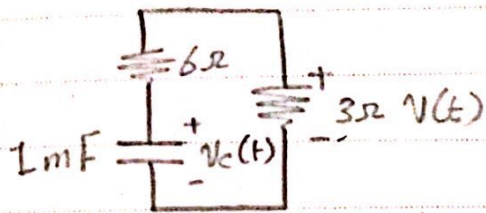

$$V_c(t) = V_c(0) e^{-t/\tau}$$

$$V_c(0) = 1.2 \text{ V}$$

$$\tau = R_{eq}C = (3+6)(1 \times 10^{-3})$$


$$= 9 \times 10^{-3} \text{ sec}$$

$$V_c(t) = 1.2 e^{-\frac{1000}{9}t}, t > 0$$

(c) $V(t) = \frac{3}{3+6} V_c(t)$

$$= \frac{1.2}{3} e^{-\frac{1000}{9}t}, t > 0$$

Ex:-

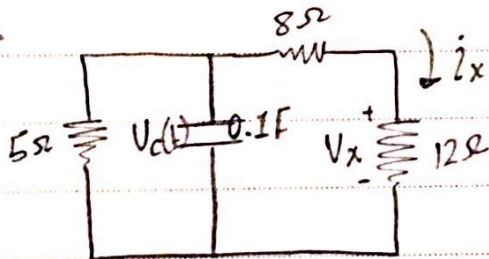

$$V_c(0) = 15 \text{ V}$$

find $V_x(t)$, $i_x(t)$, $w(t)$ $t > 0$

$$t > 0, V_c(t) = V_c(0) e^{-t/Rc}$$

$$V_c(t) = 15 * e^{-t/0.4}, t > 0$$


1) $V_x(t) = V_c(t) * \frac{12}{20}$

$$V_x(t) = 15 e^{-t/0.4} * \frac{12}{20} = 9 e^{-t/0.4} \text{ V}, t > 0$$

2) $i_x(t) = \frac{V_x(t)}{12} = \frac{9 e^{-t/0.4}}{12} \text{ A}$


3) $w_{12}(t) = \int_0^t \frac{V_x^2(\lambda)}{12} d\lambda$

2)

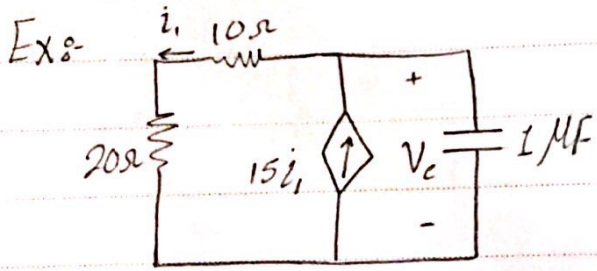


IF $V_c(0) = 2V$
 Find $V_c(t)$, $t > 0$

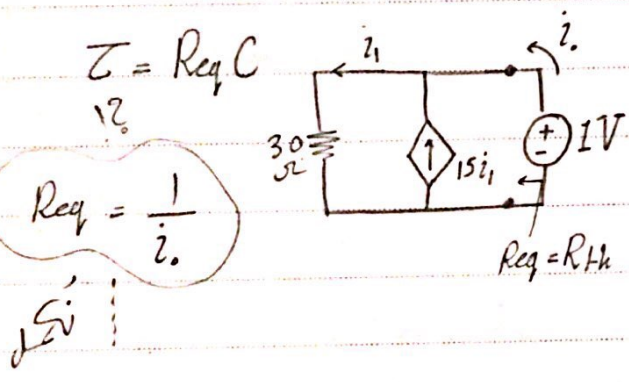Sol \rightarrow
 $V_c(t) = V_c(0) e^{-t/\tau}$
 $= 2 e^{-t/\tau} V$



(*) Source-Free RL CKT :-

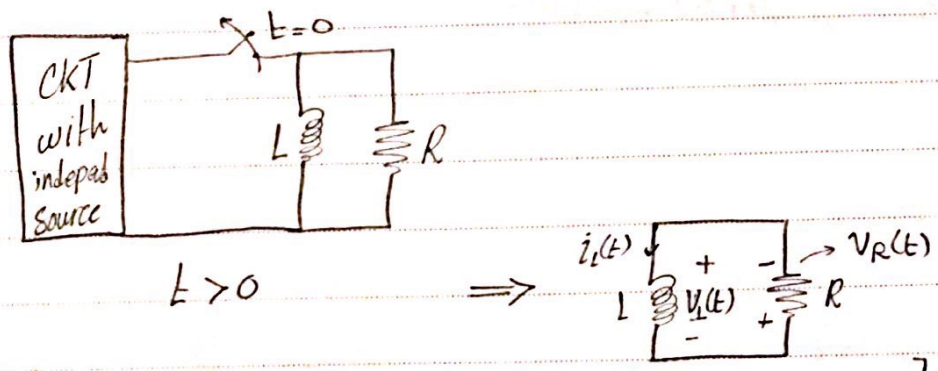

initial condition $\rightarrow i_L(0) = I_0$
 initial stored energy $\rightarrow W_L(0) = \frac{1}{2} L I_0^2$ } From $t < 0$ CKT

The natural response is $i_L(t)$:-

$V_L(t) + V_R(t) = 0$
 $L \frac{di_L(t)}{dt} + R i_L(t) = 0$ (*)

1-st-order diff equation.

proposed solution: $i_L(t) = Ae^{Bt}$ (***)


find A & B?

$$i_L(0) = I_0 = Ae^{B(0)} \Rightarrow A = I_0$$

Subst (***) into (*):

$$L A B e^{Bt} + R A e^{Bt} = 0 \rightarrow \text{Sub (***) into (*)}$$
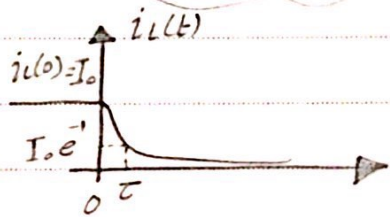
$$\Rightarrow i_L(t) = i_L(0) e^{-\frac{R}{L}t}, \quad t > 0$$



$$i_L(\tau) = I_0 e^{-1} = I_0 e^{-\frac{R}{L}\tau}$$

$$1 = \frac{R}{L}\tau \Rightarrow \tau = L/R$$

$$i_L(t) = I_0 e^{-t/\tau}$$


$$I_0 = i_L(0) \quad A, \quad t > 0, \quad i_L(5\tau) \approx 0$$

$$\tau = L/R$$


* energy dissipated by R is:

$$W_R(t) = \int_0^t i_L^2(\lambda) R \, d\lambda + W_R^0(0)$$
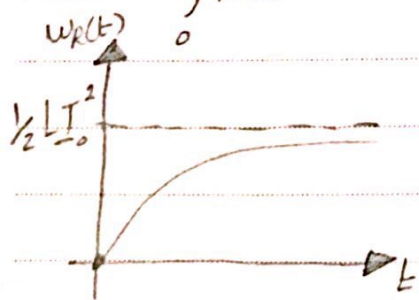
$$= \int_0^t R I_0^2 e^{-2\lambda/\tau} \, d\lambda = \dots = \frac{1}{2} L I_0^2 [1 - e^{-2t/\tau}], \quad t > 0$$


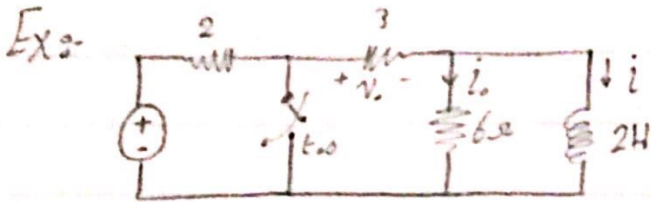
$$W_R(5\tau) \approx \frac{1}{2} L I_0^2$$




Find v_o, i_o, i for $t > 0$

Sol →

$$i(t) = I_0 e^{-t/\tau}$$

$$I_0 = i(0)$$


From $t < 0$

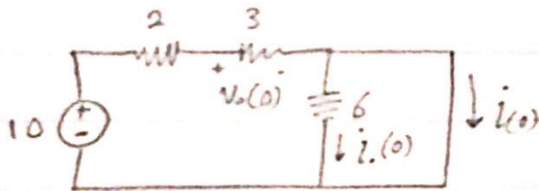

$$i(0) = \frac{10}{2+3} = 2A = I_0$$

$$i_o(0) = 0A, v_o(0) = \frac{3}{3+2} 10 = 6V$$

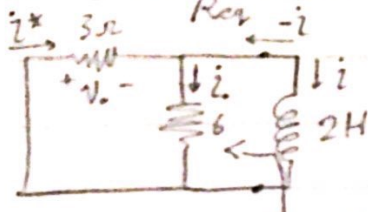Find $\tau = \frac{L}{R_{eq}}$ from $t > 0$



$$R_{eq} = R_{th} = 6 \parallel 3 = 2$$

$$\tau = \frac{2}{2} = 1 \text{ Sec}$$

$$i(t) = 2 e^{-t}$$

$$i_o(t) = \frac{3}{3+6} \cdot -i = -\frac{6}{9} e^{-t} A$$

$$v_o(t) = 3 i^*$$

$$= 3(i + i_o)$$

$$= 3 \left[2e^{-t} + \frac{-6}{9} e^{-t} \right] = 3 \left[2 - \frac{6}{9} \right] e^{-t} V = 4 e^{-t} V$$

$$\begin{aligned} v_o(t) &= -v_L(t) = \\ &= -L \frac{di(t)}{dt} \\ &= -2 \left[-2e^{-t} \right] = 4e^{-t} \end{aligned}$$

* Note:

$$i(0^-) = 2$$


$$i(0^+) = 0$$

$$i(0^+) = -6/9 \neq$$

$$V_o(0^-) = 6V$$

$$V_o(0^+) = 4V$$

Ex:-

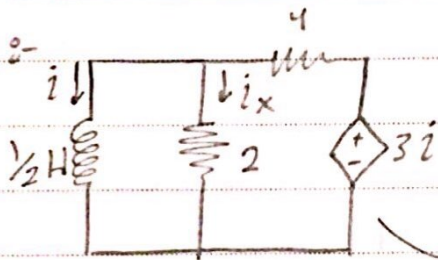

If $i(0) = 10A$ find $i(t)$ & $i_x(t)$ for $t > 0$

$$i(t) = i(0) e^{-t/\tau}$$


$$= 10 e^{-t/\tau}$$

$$i(t) = i(0) e^{-t/\tau}$$

$$= 10 e^{-t/\tau}$$

$i(t)$
 $i_x(t)$

$$\tau = \frac{L}{R_{th}}$$

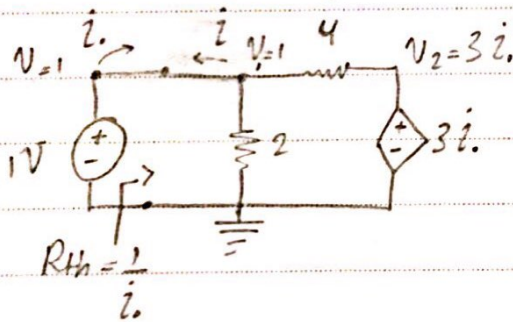

Kcl at Node ①:-

$$i_o = 1/2 + \frac{1 - 3i_o}{4}$$

$$i_x(t) = 1/2$$

$$i_o - 3/4 i_o = 1/2 + 1/4$$












$$i_o = \frac{3/4}{1/4}, \quad i_o = 3, \quad R_{th} = \frac{1}{3}$$


$$R_{th} = 1/3, \quad \tau = 3/2 \text{ Sec}$$

$$i(t) = 10 e^{-\frac{2t}{3}}$$

* Step Response of an RC CKT:-
 Singularity (switching) function
 - Unit step function:-
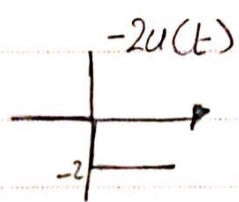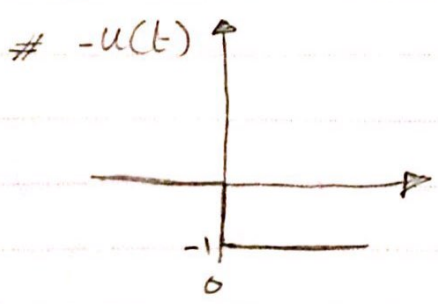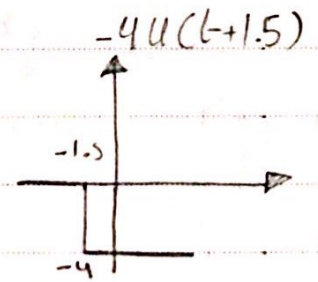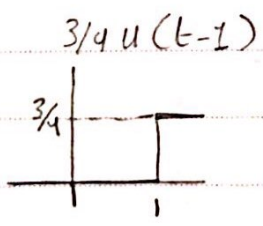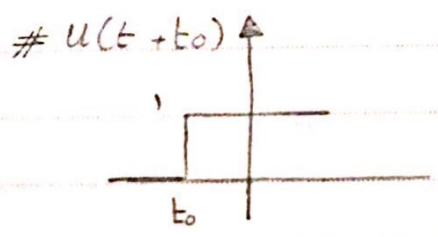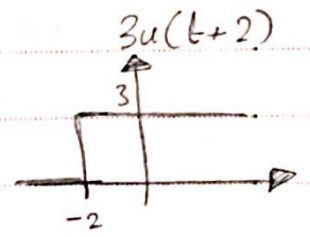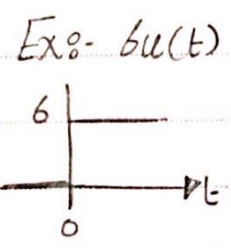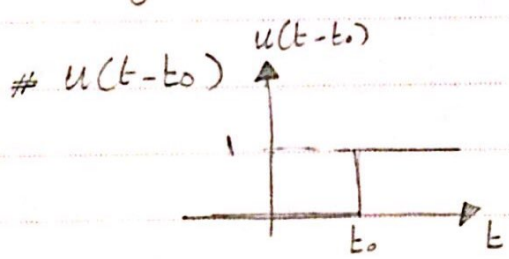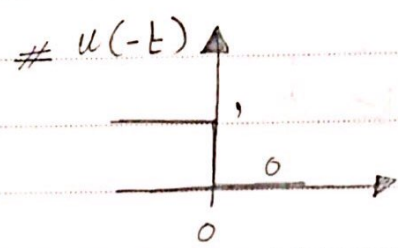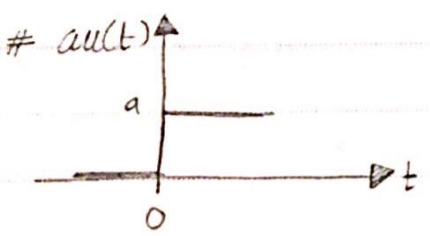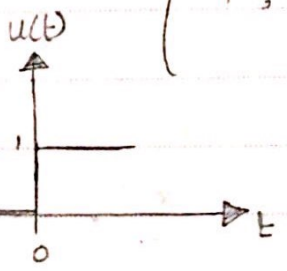
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$



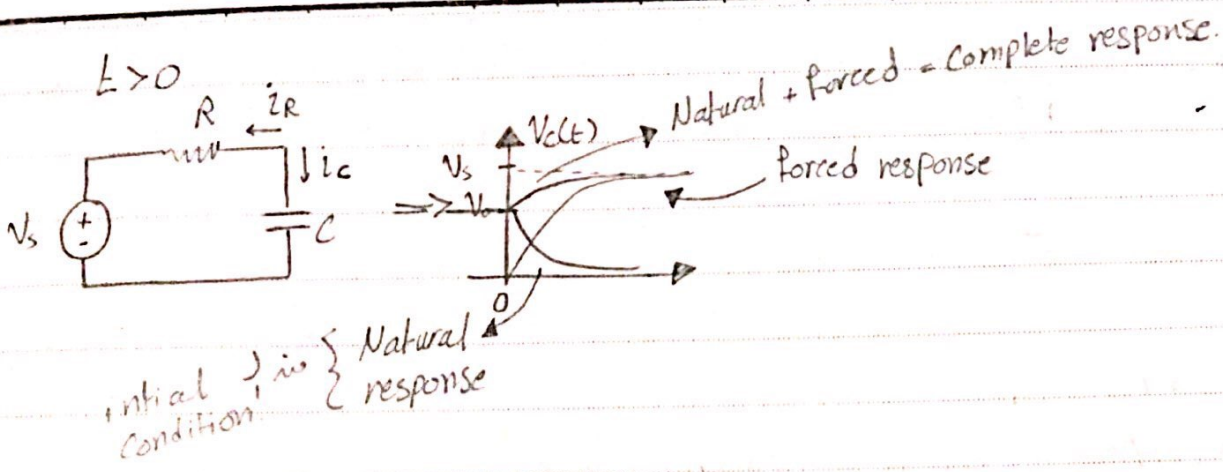

Find the Complete response $V_c(t)$?

$$V_c(t) = \begin{cases} V_0, & t < 0 \\ V_s + [V_0 - V_s] e^{-t/\tau}, & t > 0 \end{cases}$$


$\tau = RC$

$$\left. \begin{aligned} V_c(0^-) &= V_0 \\ V_c(0^+) &= V_0 \end{aligned} \right\} =$$


$$V_c(\infty) = V_s$$

—||— \cong O.C
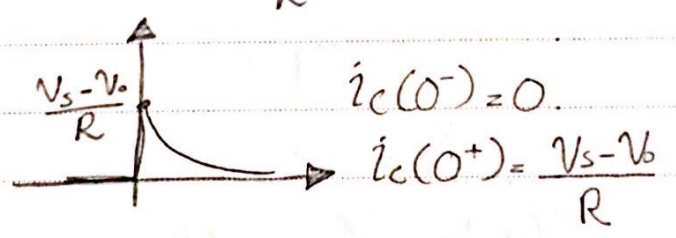
$$i_c(t) = C \frac{dV_c}{dt} = \begin{cases} 0, & t < 0 \\ -\frac{C[V_0 - V_s]}{\tau} e^{-t/\tau}, & t > 0 \end{cases} = \begin{cases} 0, & t < 0 \\ \frac{[V_s - V_0]}{R} e^{-t/\tau}, & t > 0 \end{cases}$$




* applications :-


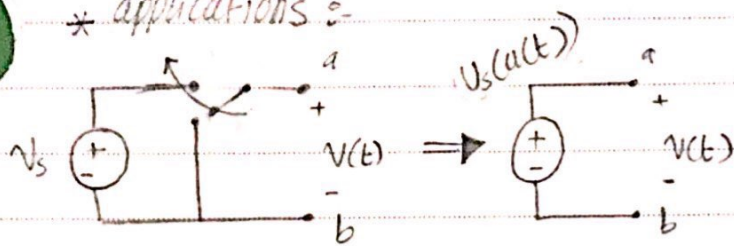


$$v(t) = \begin{cases} 0, & t < 0 \\ v_s, & t > 0 \end{cases} \Rightarrow \begin{array}{c} v_s \\ \uparrow \\ U(t) \\ \downarrow \\ 0 \end{array}$$


$$= v_s u(t)$$

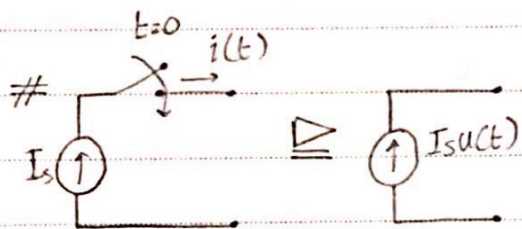

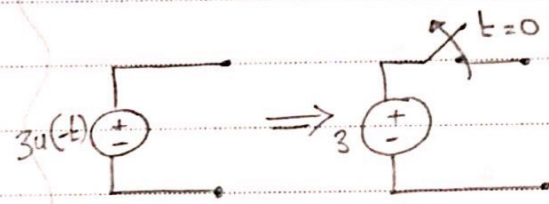
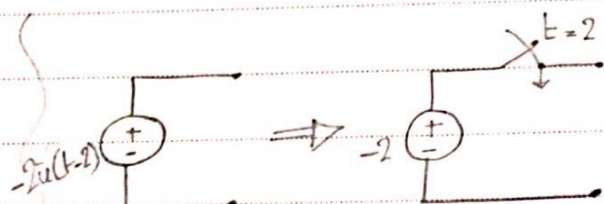
$$i(t) = \begin{cases} 0, & t < 0 \\ I_s, & t > 0 \end{cases}$$



$$* 3u(-t-1) = 3u(-(t+1))$$

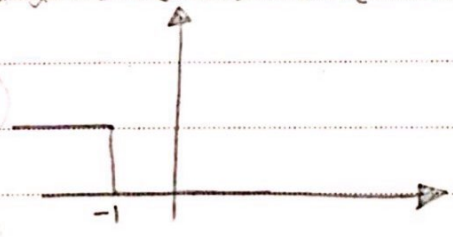

$$* u(-t+1) = u(-1(t-1))$$

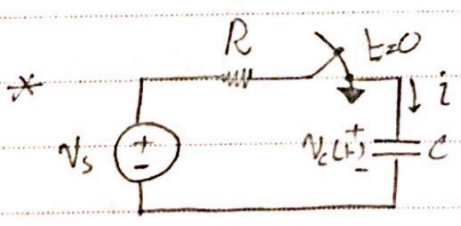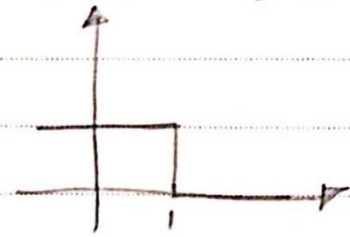

$t < 0$

- $v_c(0^-) = v_c(0^+) = v_c(0) = v_0$
- $w_c(0) = \frac{1}{2} C v_0^2$

initial conditions.

$$v_0 < v_s$$

* To find the complete response in RC or in RL ckt's :-


$$f(t) = f(\infty) + [f(0^+) - f(\infty)] e^{-t/\tau}, t > 0$$

$$f(0^+) \left\{ \begin{array}{l} t > 0, \tau \text{ from } t > 0 \\ \text{CKT} \end{array} \right.$$

$$f(\infty) \left\{ \begin{array}{l} \text{CKT} \end{array} \right.$$

$$f(0^+) = f(0^-)$$

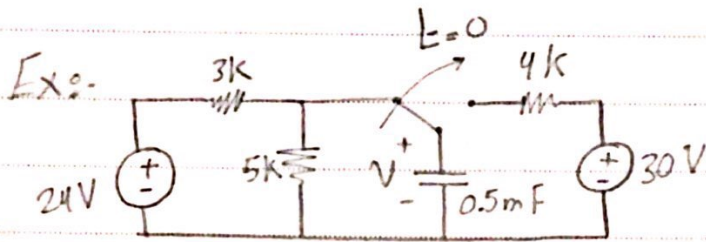
only for capacitor voltage or inductor current.



Find a) V b) energy stored at the capacitor for all t


Sol \rightarrow
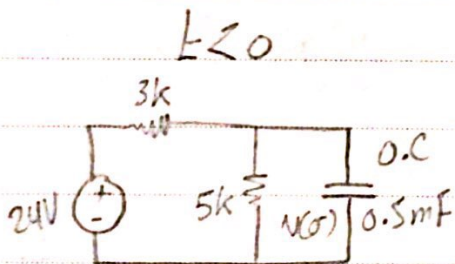
$$V(t) = \begin{cases} V(0^-), t < 0 & \leftarrow \text{from } t < 0 \text{ ckt} \\ V(\infty) + [V(0^+) - V(\infty)] e^{-t/\tau}, t > 0 \end{cases}$$




$$V(0^-) = \frac{5k}{5k+3k} \times 24$$
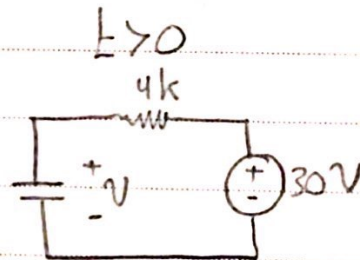
$$= \frac{5}{8} \times 24 = 15 \text{ V}$$




- $V(0^+) = V(0^-) = 15 \text{ V}$
- $V(\infty) = 30 \text{ V}$
- $\tau = RC = (4k) \times (1/2 \text{ mF})$
- $(\tau = 2 \text{ sec})$
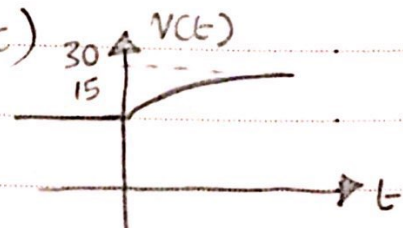
$$V(t) = \begin{cases} 15, t < 0 \\ 30 + [15 - 30] e^{-t/2}, t > 0 \end{cases}$$




* Step-Response of RC CKT
The Complete response
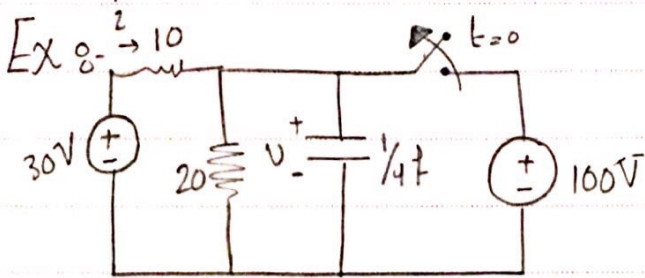
$$f(t) = \begin{cases} f(0^-), & t < 0 \\ f(0) + [f(0^+) - f(0)] e^{-t/\tau}, & t > 0 \end{cases} \quad \tau = RC$$




Find the Complete response:-

Sol. \rightarrow

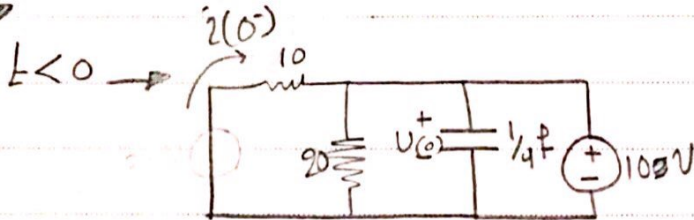
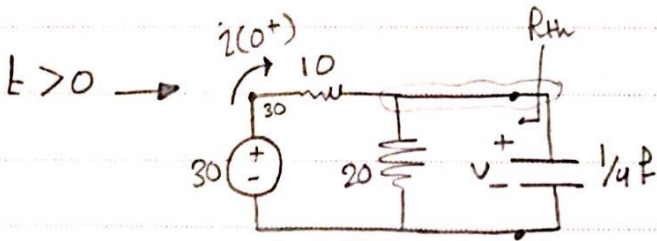
$$(V(0^-) = 10 \text{ Volt}), \quad i(0^-) = \frac{-10 \text{ V}}{10 \Omega} = -1 \text{ A}$$



$$i(0^+) = \frac{30 - V_C}{10} = 2 \text{ A}$$

$$V(\infty) = 30 \times \frac{20}{30} = 20 \text{ Volt}$$

$$V(t) = \begin{cases} 10, & t < 0 \\ 20 + [20 - 10] e^{-t/\tau}, & t > 0 \end{cases}$$

$$= 2 \text{ A}$$


$$R_{th} = (20 \parallel 10) = 6.66$$

$$\tau = R_{th} C$$

$$\tau = 6.66 \times 0.25 = 5/3$$

$$V(t) = \begin{cases} 10, & t < 0 \\ 20 - 10 e^{-3t/5}, & t > 0 \end{cases}$$


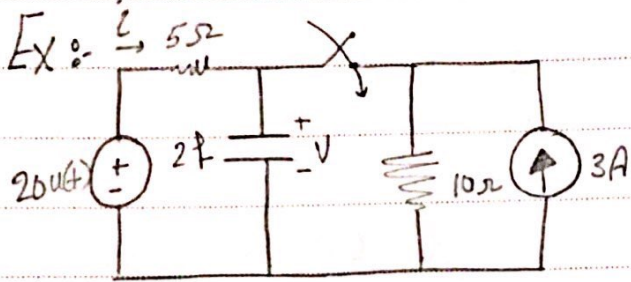
$$i(t) = \begin{cases} -1, & t < 0 \\ 1 + e^{-3t/5}, & t > 0 \end{cases}$$



Find $V(t)$ & $i(t)$ for all t ?

Sol. \rightarrow

$t < 0$

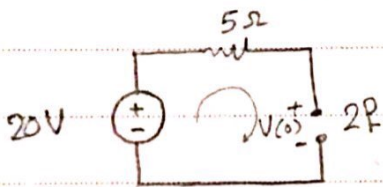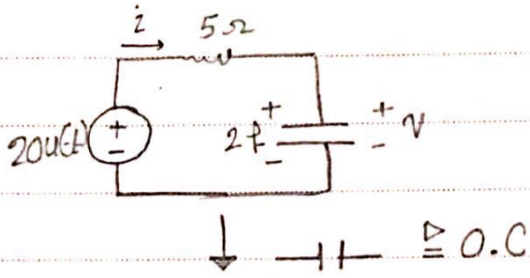


-20 A

$$V(0^-) = 20 \text{ V}$$

$$i(0^-) = 0 \text{ A}$$

$t > 0$

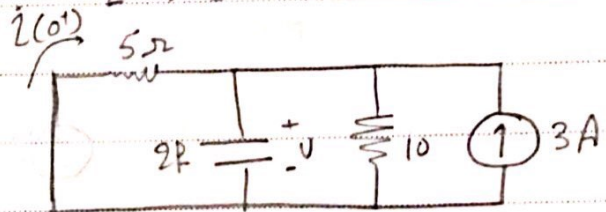

$$V(0^+) = V(0^-) = 20 \text{ Volt}$$

$$i(0^+) = \frac{-20}{5} = -4 \text{ A}$$


$$V(\infty) = (10 \parallel 5) \times 3 = 10$$

$$i(\infty) = 3 \times \frac{10}{15} = -2 \text{ A}$$


$$\tau = R_{th}C$$

$$= (5 \parallel 10) \left(\frac{2}{10} \right) = \frac{2}{3} \text{ sec}$$
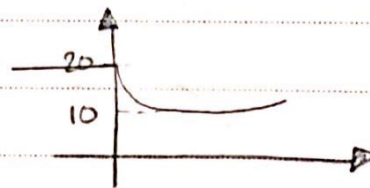
$$V(t) = \begin{cases} 20, & t < 0 \\ 10 + 10e^{-3t/2}, & t > 0 \end{cases}$$



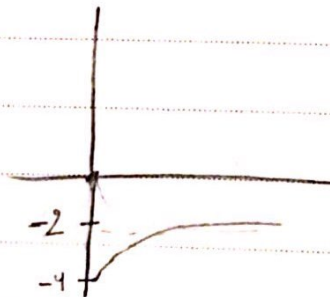
$$i(t) = \begin{cases} 0, & t < 0 \\ -2 + 6e^{-3t/2}, & t > 0 \end{cases}$$





* rect - function :-

$$V_s(t) = B [u(t-t_1) - u(t-t_2)]$$


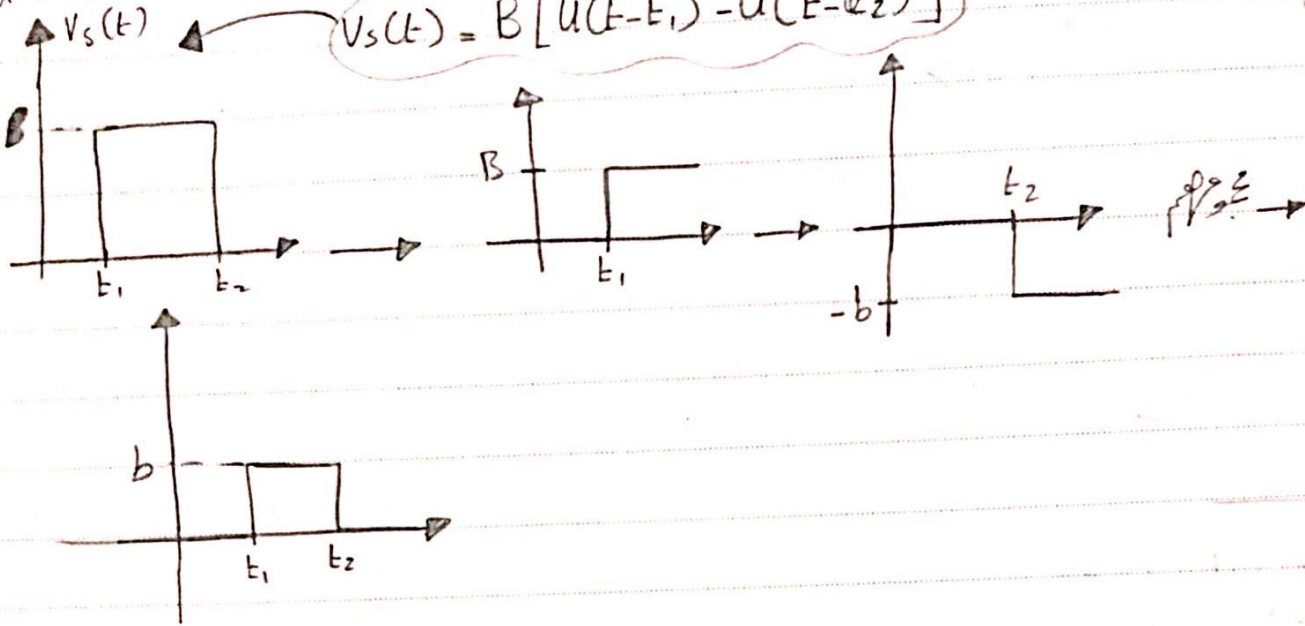


Ex :-

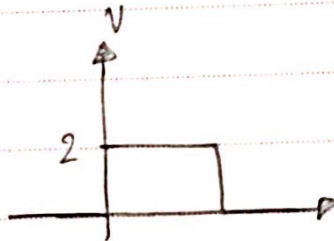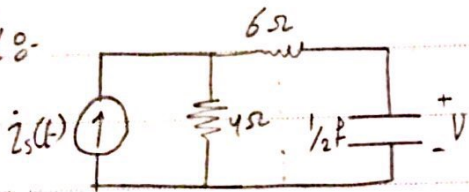

assume $V(0) = 0$

find V as a function of t

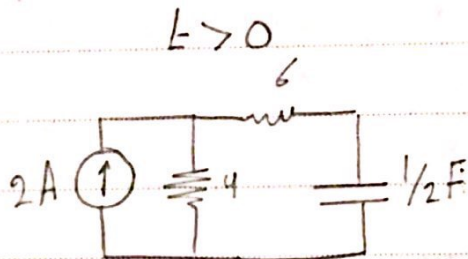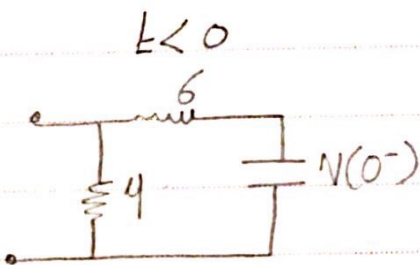

$$V(0^+) = V(0^-) = 0$$

$$V(\infty) = (2A)(4\Omega) = 8 \text{ Volt}$$

$$\tau = (6+4) \cdot \frac{1}{2} = 5$$

$$V(t) = \begin{cases} 0, & t < 0 \\ 8 - 8e^{-t/5}, & 0 < t < 1 \\ V(\infty) + [V(1^+) - V(\infty)], & t > 1 \end{cases}$$

$t < 1$

$$V(1^-) = 8 - 8e^{-1/5} = 1.45 \text{ V}$$


$t > 1$

$$V(1^+) = V(1^-) = 1.45 \text{ V}$$

$$\tau = 5 \text{ sec}$$

$$V(t) = \begin{cases} 0, & t < 0 \\ 8 - 8e^{-t/5}, & 0 < t < 1 \\ 45e^{-(t-1)/5}, & t > 1 \end{cases}$$

* Step response of RL CKT

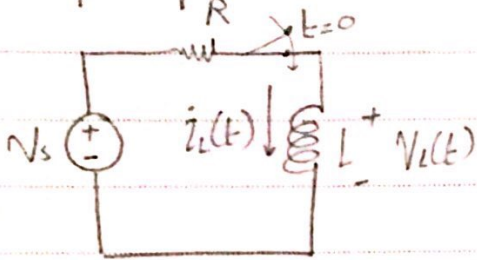


$$t < 0, \quad i_L(0^-) = i_L(0^+) = I_0 \\ W_L(0) = \frac{1}{2} L I_0^2$$

$t > 0$

$$-V_s + Ri + L \frac{di(t)}{dt} = 0$$


$$i_L(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}$$
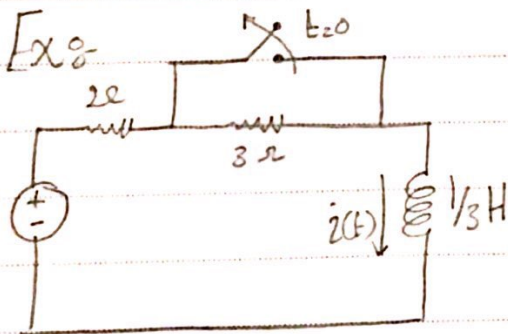
$$V_L(t) = L \frac{di(t)}{dt} \quad V_L(0^+) \neq V_L(0^-)$$




Find $i(t)$ for all time

$t < 0$

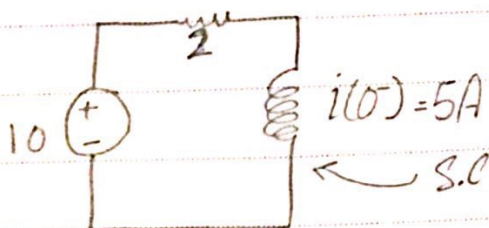

$t > 0$

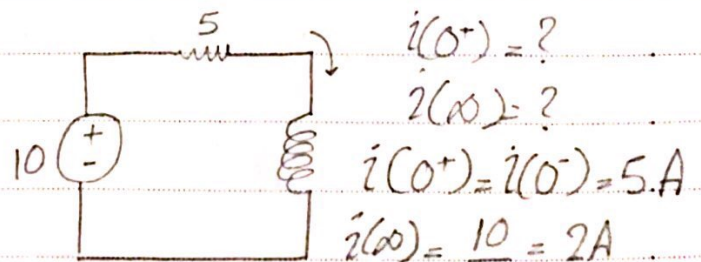

$$i(0^+) = ?$$


$$i(\infty) = ?$$

$$i(0^+) = i(0^-) = 5A$$


$$i(\infty) = \frac{10}{5} = 2A$$

$$\tau = \frac{L}{R} = \frac{1/3}{5} = 1/15 \Rightarrow$$


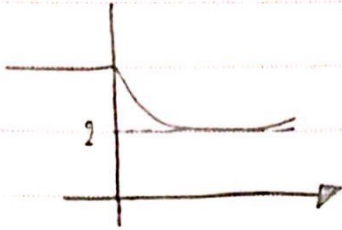
$$i(t) = \begin{cases} i(0^-), & t < 0 \\ i(\infty) + [i(0^-) - i(\infty)]e^{-t/\tau}, & t > 0 \end{cases} \Rightarrow \begin{cases} 5, & t < 0 \\ 2 + 3e^{-15t}, & t > 0 \end{cases}$$



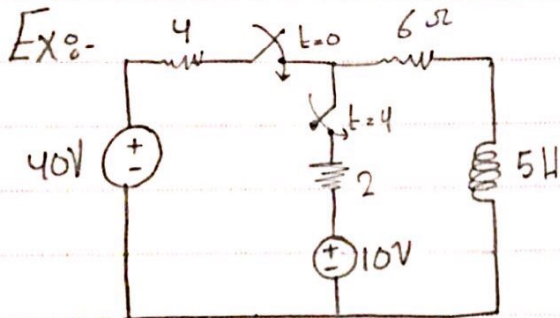
$$V(t) = \begin{cases} 0, & t < 0 \\ -\frac{45}{3}e^{-15t}, & t > 0 \end{cases} \quad \begin{aligned} V(0^+) &= -15V \\ V(\infty) &= 0V \end{aligned}$$


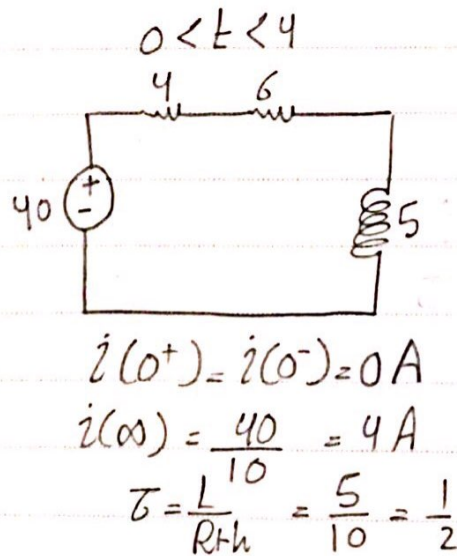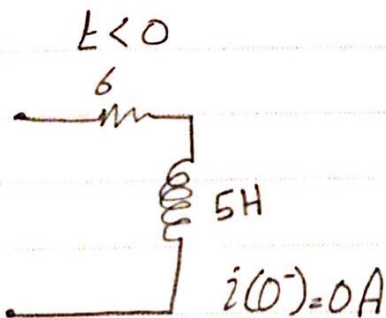
$$i(t) = \begin{cases} i(0^-), & t < 0 \\ i(\infty) + [i(0^-) - i(\infty)]e^{-t/\tau}, & 0 < t < 4 \\ i(\infty) + [i(4^-) - i(\infty)]e^{-(t-4)/\tau}, & 4 < t \end{cases}$$



$$i(t) = 4 - 4e^{-2t}, \quad 0 < t < 4$$

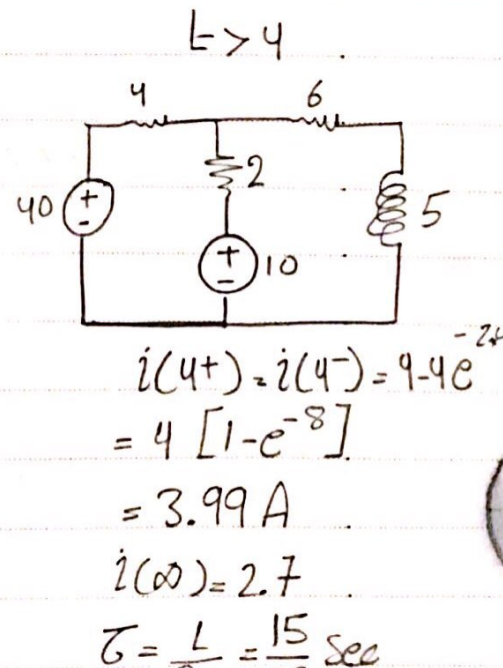


* Chgs:- 2nd-order RLC CkTs :-

- Source-Free Series RLC CkTs :- $t > 0$
initial conditions

• $i(0^+) = i(0^-) = I_0$

• $V_c(0^+) = V_c(0^-) = V_0$

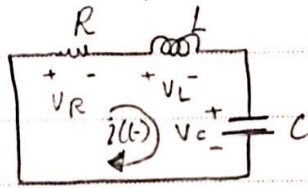

The natural response $i(t)$ or $V_c(t)$

Find $i(t)$?

KVL :- $V_R(t) + V_L(t) + V_C(t) = 0$

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t) dt + V_0 = 0$$

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i(t) = 0$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

Define

$$\alpha = \frac{R}{2L}$$

damping factor.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

resonant frequency
rad/Sec.

$$f_0 = \frac{\omega_0}{2\pi}$$

$$\frac{d^2i}{dt^2} + 2\alpha \frac{di}{dt} + \omega_0^2 i = 0 \quad (*)$$

Solve for $i(t)$ to find $i(t)$?

propose $i(t) = Ae^{st}$ — $(*) (*)$

Substitut $(*) (*)$ into $(*)$:-

$$\rightarrow (As^2e^{st} + 2\alpha Ase^{st} + \omega_0^2)$$

Two roots :-

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

works for ① $\alpha > \omega_0$

② $\alpha < \omega_0$

For ③ $\alpha = \omega_0$ →

$$i(t) = (A_2 + A_1 t) e^{st}$$

□ $\alpha > \omega_0$:- overdamped CKT


$$\Rightarrow \frac{R}{2L} > \frac{1}{\sqrt{LC}} \Rightarrow C > \frac{4L}{R^2}$$

$$\left. \begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{aligned} \right\} \text{Two different negative and real roots.}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Find :- A_1 & A_2 from $i(0^+) = i(0^-)$

$\frac{di}{dt}(0^+)$ ← From 0^+ CKT

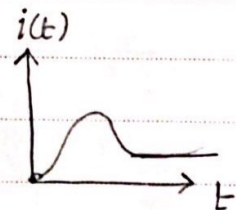

2 $\alpha < \omega_0$:- Underdamped CKT

$$C < \frac{4L}{R^2}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\alpha \pm \sqrt{-(\omega_0^2 - \alpha^2)}$$

$$= -\alpha \pm \sqrt{-1} \sqrt{\omega_0^2 - \alpha^2}$$

$$s_{1,2} = -\alpha \pm j\omega_d \quad , \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad \leftarrow \text{damping frequency}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$= A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t}$$

$$= A_1 e^{-\alpha t} \cdot e^{j\omega_d t} + A_2 e^{-\alpha t} \cdot e^{-j\omega_d t}$$

$$= e^{-\alpha t} [A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t}]$$

$$= e^{-\alpha t} [A_1 \cos(\omega_d t) + jA_1 \sin(\omega_d t) + A_2 \cos(\omega_d t) + jA_2 \sin(-\omega_d t)]$$

$$= e^{-\alpha t} \left[\underbrace{(A_1 + A_2)}_{B_1} \cos(\omega_d t) + j \underbrace{(A_1 - A_2)}_{B_2} \sin(\omega_d t) \right]$$

$$i(t) = e^{-\alpha t} [B_1 \cos(\omega_d t) + jB_2 \sin(\omega_d t)]$$

طرق
2P)

- $i(0^+)$
- $\frac{di}{dt}(0^+)$


$$i(t) = \sqrt{B_1^2 + B_2^2} e^{-\alpha t} \cos(\omega_d t + \tan^{-1}\left(\frac{B_2}{B_1}\right))$$


$$e^{j\theta} = \cos(\theta) + j \sin(\theta)$$

$$\cos(-\theta) = \cos(\theta)$$

$$\sin(-\theta) = -\sin(\theta)$$

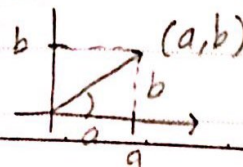
$$a + jb = \sqrt{a^2 + b^2} \cdot \tan^{-1}\left(\frac{b}{a}\right)$$



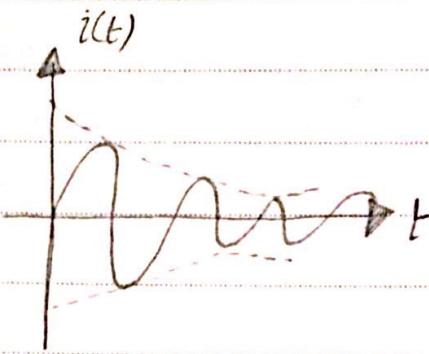

Special case $R=0 \Rightarrow \alpha=0$
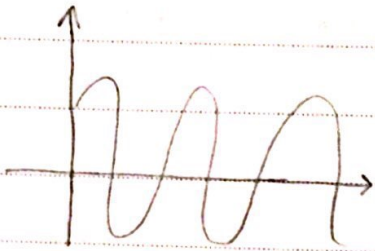
$$i(t) = B_1 \cos(\omega_0 t) + j B_2 \sin(\omega_0 t)$$



oscillation ω
damping α

3


$$\alpha = \omega_0$$

$$s_1 = -\alpha$$


$$s_2 = -\alpha$$

$$s_1 = s_2 = -\alpha$$


$$i(t) = (A_2 + A_1 t) e^{-\alpha t}$$

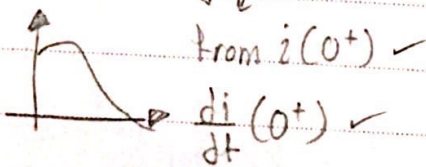

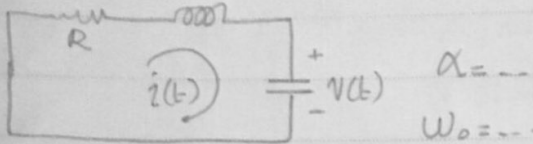
* Source-Free series RLC ckt:-
 $t < 0$ L



Ex:-

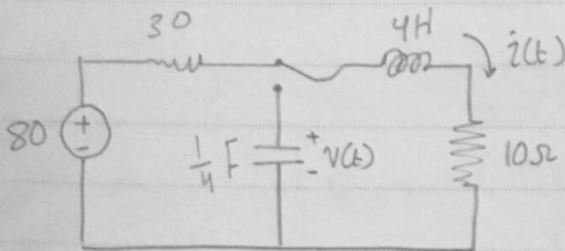


Find $v(t)$ and $v_c(t)$ for $t > 0$

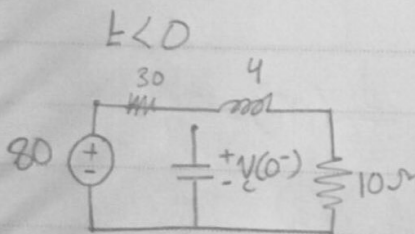

$$i(0^-) = \frac{80}{30+10} = 2A$$

$$v_c(0^-) = 0V$$

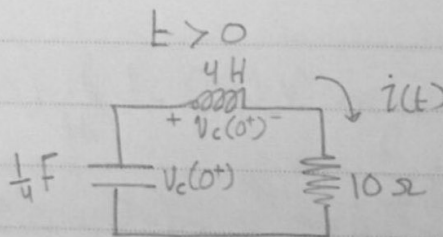

$$\alpha = \frac{R}{2L} = (1.25) \text{ neper/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1 \text{ rad/sec}$$

$\alpha > \omega_0 \rightarrow$ over damped series RLC ckt

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -0.5$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -2$$

$$i(t) = A_1 e^{t/2} + A_2 e^{-2t}, \quad t > 0$$

$$v_c(t) = A_3 e^{-0.5t} + A_4 e^{-2t}$$



Find A_1 & A_2 $\begin{cases} i(0^+) \\ \frac{di}{dt}(0^+) \end{cases}$

$$i(0^+) = i(0^-) = 2A$$

$$i(0) = A_1 + A_2 = 2 \rightarrow \textcircled{1}$$

$$\frac{di}{dt}(0^+) = \rightarrow v_L = L \frac{di}{dt} \text{ w/suppl. i/s}$$

$$\text{KVL} \therefore -V_C(0^+) + V_L(0^+) + 10 i(0^+) = 0$$

$$V_L(0^+) = V_C(0^+) - 10 i(0^+)$$

$$= 0 - (10)(2) \text{ V} = -20 \text{ V}$$

$$V_L(t) = L \frac{di}{dt} \rightarrow V_L(0^+) = L \frac{di}{dt}(0^+) \rightarrow \frac{di}{dt}(0^+) = \frac{-20}{4} = -5$$

$$\frac{di}{dt} = -0.5A_1 e^{-0.5t} - 2A_2 e^{-2t} \rightarrow (-5 = -0.5A_1 - 2A_2) \textcircled{2}$$


Solving $\textcircled{1}$ & $\textcircled{2}$ $A_1 = -2/3$

$$i(t) = -2/3 e^{-0.5t} + 8/3 e^{-2t}, t > 0$$

$$-i(0^+) = V_C \frac{dv}{dt}(0^+) \text{ OR } V_C(t) = \frac{1}{C} \int_{t^c} i(\tau) d\tau + V(0)$$

$$= -\frac{1}{C} \int_0^t \left(-\frac{2}{3} e^{-0.5\tau} + \frac{8}{3} e^{-2\tau} \right) d\tau + V(0)$$
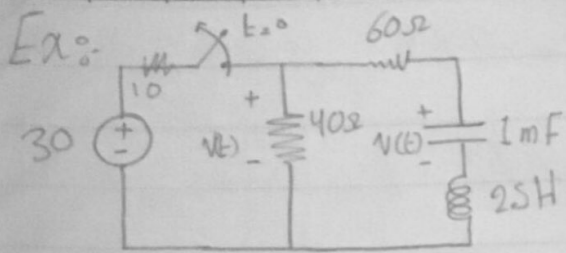
$$V_{10}(t) = 10 i(t), V_C(t) = L \frac{di}{dt}$$




find $v(t)$ for $t > 0$

Sol →

find $i(t)$ then $v(t) = -40i(t)$


$t < 0$

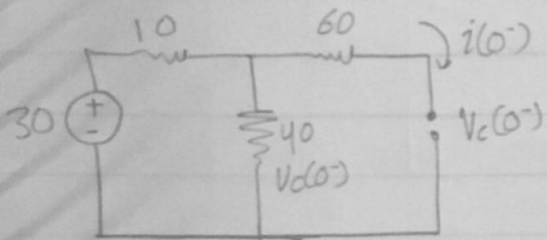

$$i(0^-) = 0 \text{ A}$$

$$v_C(0^-) = \frac{40}{40+10} \cdot 30 = 24 \text{ V}$$

$t > 0$

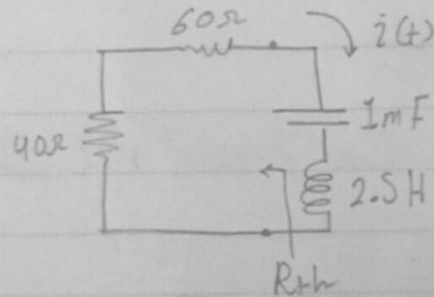

$$\alpha = \frac{R}{2L} = \frac{100}{2 \left(\frac{5}{2}\right)} = 20 \text{ Naper/sec}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 20 \text{ rad/sec}$$

$\alpha = \omega_0 \rightarrow$ Critically damped ckt

$$i(t) = (A_2 + A_1 t) e^{-\alpha t}$$

$$= (A_2 + A_1 t) e^{-20t} \text{ A, } t > 0$$

find

$$A_1 \quad i(0^+)$$

$$A_2 \quad \frac{di}{dt}(0^+)$$

$$i(0^+) = i(0^-) = 0 = A_2 \rightarrow A_2 = 0$$

$$i(t) = A_1 t e^{-20t}$$

$$\frac{di}{dt} = ? \rightarrow \text{KVL: } 40i(0^+) + 60i(0^+) + v_L(0^+) + v_C(0^+) = 0$$

$$0 + 0 + v_L(0^+) + 24 = 0$$

$$v_L(0^+) = -24 \text{ V} \Rightarrow$$

$$V_L(0^+) = L \frac{di}{dt}(0^+) \rightarrow \frac{di}{dt}(0^+) = \frac{-24}{\frac{5}{2}} = -9.6 \text{ A}$$

$$\frac{di}{dt} = A_1 t (-20 e^{-20t}) + A_1 e^{-20t} \rightarrow \boxed{-9.6 A_1}$$


$$i(t) = -9.6 t e^{-20t} \text{ A}, t > 0$$

$$N(t) = 40 (-9.6 t e^{-20t})$$

$$\tau = \frac{1}{20}$$

* Source-Free parallel RLC CKT :-

$t > 0$

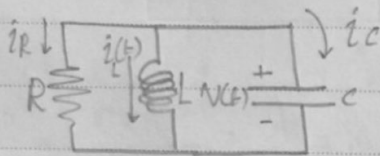

initial conditions:

$$V_C(0^+) = V_C(0^-) = V_0$$

$$i_L(0^+) = i_L(0^-) = I_0$$

natural response is $V_C(t)$ or $i_L(t)$

$$\text{Kcl} \rightarrow i_R + i_L + i_C = 0$$

$$\frac{V}{R} + \frac{1}{L} \int V(t) dt + i(0) + C \frac{dV}{dt} = 0$$

$$C \frac{d^2 V}{dt^2} + \frac{1}{R} \left(\frac{dV}{dt} \right) + \frac{1}{LC} V = 0$$

$$\frac{d^2 V}{dt^2} + \frac{1}{R} \left(\frac{dV}{dt} \right) + \frac{1}{LC} V = 0$$

$$\frac{d^2 V}{dt^2} + 2\alpha \frac{dV}{dt} + \omega_0^2 V = 0$$

$$\alpha = \frac{1}{2RC}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Cases :-

Case ① $\alpha > \omega_0$:- over damped

s_1, s_2 :- differential real negative roots

$$V(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$V(0^+) \leftarrow$$

$$\frac{dV}{dt}(0^+) \leftarrow$$

Case ② under damped

s_1, s_2 :- Complex roots

$$\omega_0 \sqrt{\omega_0^2 - \alpha^2}$$

$$V(t) = e^{-\alpha t} [B_1 \cos(\omega t) + j B_2 \sin(\omega t)]$$

$$V(0^+), \frac{dV}{dt}(0^+) \leftarrow$$


Case ③ critically damped

$$s_1 = s_2 = -\alpha$$

$$V(t) = (A_2 + A_1 t) e^{-\alpha t}$$

A_2 & A_1 = from initial conditional


Ex =

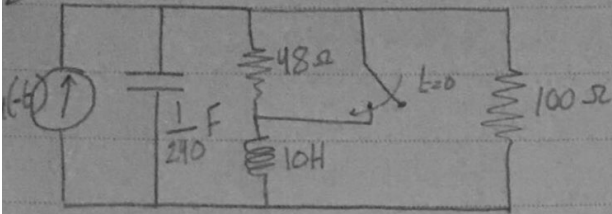

Find $v(t)$ & $i(t)$ $t > 0$

Sol →


$t < 0$

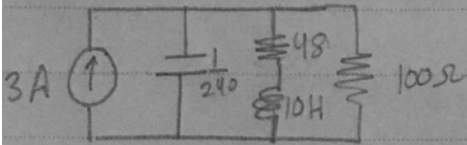

$$V(0^-) = (3)(48 // 100) = 97.3 \text{ V}$$

$$i(0^-) = \frac{100}{100+48}(3) = 2.027 \text{ A}$$

$t > 0$

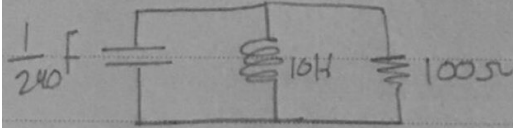

Source free parallel RLC ckt

$$\alpha = \frac{1}{2RC} = 1.2 \text{ Neper/sec}$$

$$\omega_d = \frac{1}{\sqrt{LC}} = 4.9 \text{ rad/sec}$$

$\alpha < \omega_0$:- Under damped case.

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 4.75 \text{ rad/sec}$$

$$v(t) = e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)]$$

Find B_1 & B_2 using $v(0^+)$ & $\frac{dv}{dt}(0^+)$

$$v(0^+) = v(0^-) = 97.3 = 1 [B_1(1) + B_2(0)]$$

$$B_1 = 97.3$$

$$i_C(0^+) + i_L(0^+) + i_R(0^+) = 0 \text{ in Zero ckt}$$

$$\frac{1}{240} \frac{dv(0^+)}{dt} + \frac{97.3}{100} = 0, \quad \frac{dv(0^+)}{dt} = -720$$

$$\frac{dv}{dt} = e^{-\alpha t} [B_1 \omega_d \sin(\omega_d t) + B_2 \omega_d \cos(\omega_d t)] +$$

$$-\alpha e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)] \Rightarrow$$

$$-720 = B_2 \omega j - \alpha B_1$$

$$-720 = -1.2 B_1 + 4.7 B_2 = -720 \rightarrow (2)$$

$$B_2 = -127$$

$$\Rightarrow v(t) = e^{-1.2t} [97.3 \cos(4.75t) - 127 \sin(4.75t)] \text{ V}, t > 0$$

$$i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau + i(0)$$

$$= \frac{1}{10}$$

$$\text{OR } i(t) = e^{-\alpha t} [B_3 \cos(\omega t) + B_4 \sin(\omega t)]$$

$$B_3 \& B_4 \quad i(0^+) \quad ? \quad \frac{di(0^+)}{dt}$$

$$i(0^+) = i(0) = 2.027 \triangleq B_3$$

$$v_L(0^+) = L \frac{di(0^+)}{dt} \rightarrow \frac{di(0^+)}{dt} = \frac{97.3}{10} = 9.73$$

$$9.73 = B_4 \omega - \alpha B_3$$


$$B_4 = 2.4$$

* Step response RLC CKT $\begin{cases} \swarrow \text{Series} \\ \searrow \text{parallel} \end{cases}$

- The $t > 0$ ckt has independent Dc sources
- The response = The steady state response + The transient response


$$f(t) = f(\infty) + f(t), t > 0$$

Ex: Prob 8:33 :-

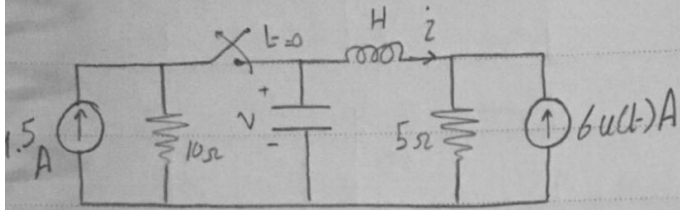

Find $v(t)$ and $i(t)$:-


Sol :- $t < 0$

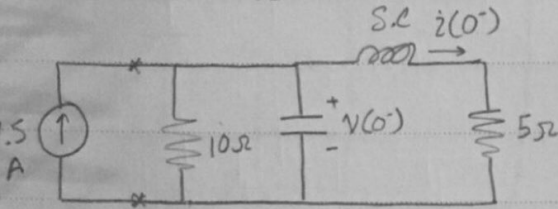

$$v(0^-) = (1.5)(10 \parallel 5) = 15 \text{ V}$$

$$i(0^-) = \frac{15}{5} = 3 \text{ A}$$

$t > 0$

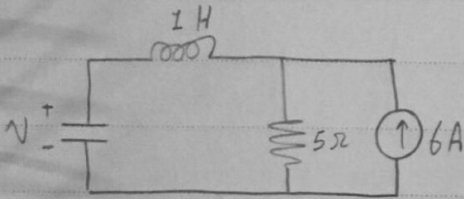

Step-response series RLC ckt

$$\alpha = \frac{R}{2L} = 2.5 \text{ nep/sec}$$

to determine
kill all independent
sources.

$$\omega_0 = \frac{1}{\sqrt{LC}} = 0.5 \text{ rad/sec}$$

$\alpha > \omega_0 \rightarrow$ **overdamped**

let $f(t) = v(t)$

$$\begin{aligned} v(t) &= v(\infty) + v_f(t) \\ &= v(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t} \end{aligned}$$

$$V(\infty) = (5)(6) = 30V$$

$$\begin{array}{l} \uparrow \\ t \rightarrow \infty \\ \text{---} : 0.1 \\ \text{---} : 8.2 \end{array}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -4.95$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -0.0505$$

$$V(t) = 30 + A_1 e^{-4.95t} + A_2 e^{-0.0505t}, \quad t > 0$$

Find A_1 & A_2 using $V(0^+)$?
 $\cdot \frac{dV}{dt}(0^+)$?

$$V(0^+) = V(0^-) = 15V$$

$$15 = 30 + A_1 + A_2$$

$$\Rightarrow A_1 + A_2 = -15 \quad \textcircled{1}$$

$$-i(t) = 4 \frac{dV}{dt}, \quad t > 0$$

$$-i(0^+) = 4 \frac{dV}{dt}(0^+)$$

$$\Rightarrow \frac{dV}{dt}(0^+) = \frac{-i(0^+)}{4} = \frac{-3}{4}$$

$$\frac{dV}{dt}(0^+) = -4.95A_1 e^{-4.95t} - 0.0505A_2 e^{-0.0505t}$$

$$\frac{-3}{4} = -4.95A_1 - 0.0505A_2 \quad \textcircled{2}$$

Solving for $\textcircled{1}$ & $\textcircled{2}$: $A_1 = 0.3077$
 $A_2 = -15.3076$

$$\rightarrow V(t) = \begin{cases} 15 & , t < 0 \\ 30 + 0.3077 e^{-4.95t} - 15.3076 e^{-0.0505t} & , t > 0 \end{cases}$$

* AC Circuits :-
 - Complex number

• Complex number →

$$x^2 = -1 \Rightarrow x = \sqrt{-1} = j$$

$$j^2 = -1, j^3 = j \cdot j \cdot j = -j$$


$$j^4 = 1, j^5 = j$$

[1] In rectangular form $Im\{ \cdot \}$

$$\vec{x} = a + jb$$

$$a = Re\{ \vec{x} \}$$

$$b = Im\{ \vec{x} \}$$

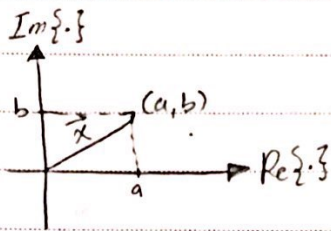


$$\vec{x}_1 = 1 + j2$$

$$\vec{x}_2 = 3 - j4$$

$$\vec{x}_3 = -1 - j2$$


$$\vec{x}_4 = -2 + j3$$

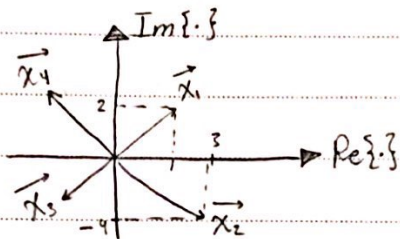

[2] Exponential form

$$\vec{x} = |\vec{x}| e^{j\theta_x}$$


length b
 magnitude
 $= |\vec{x}|$

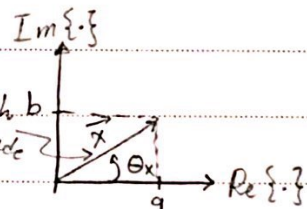

[3] Polar form

$$\vec{x} = |\vec{x}| \angle \theta_x$$
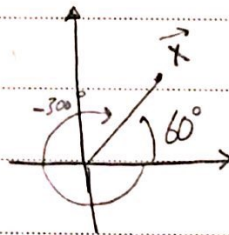
$$Ex: \vec{x} = 10 e^{j60^\circ} = 10 \angle 60^\circ = 10 \angle -300^\circ$$




$$* \vec{x} = a + jb \rightarrow \vec{x} = |\vec{x}| e^{j\theta_x}$$

$$|\vec{x}| = \sqrt{a^2 + b^2}$$

$$\theta_x = \tan^{-1}\left(\frac{b}{a}\right)$$

$$\vec{x} = 3 + j5 \cong \sqrt{3^2 + 5^2}$$

$$= 6 / 59.03^\circ$$

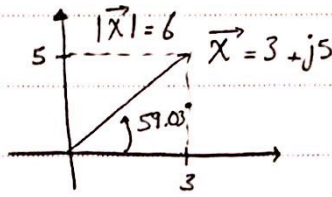


$$* \vec{x} = |\vec{x}| \theta_x \rightarrow \vec{x} = \underbrace{|\vec{x}| \cos(\theta_x)}_a + j |\vec{x}| \sin(\theta_x)$$

$$\text{Ex: } \vec{x} = 18 / -30^\circ = 18 / 330$$

$$\cong 18 \cos(-30^\circ) + j(18) \sin(-30^\circ)$$

$$= 15.58 - j9$$

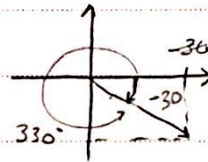

18.7.

$$\vec{x}_1 = e^{j\theta} \cong \cos(\theta) + j \sin(\theta) \rightarrow \textcircled{1}$$

$$\vec{x}_2 = e^{-j\theta} = \cos(-\theta) + j(-\theta)$$

$$= \cos(\theta) - j \sin(\theta) \rightarrow \textcircled{2}$$

$$\textcircled{1} + \textcircled{2} \rightarrow \cos(\theta) = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

$$\textcircled{1} - \textcircled{2} \rightarrow \sin(\theta) = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

$$* \vec{x}_1 = a + jb \cong |\vec{x}_1| \theta_{x_1}$$

$$\vec{x}_2 = c + jd \cong |\vec{x}_2| \theta_{x_2}$$

$$\vec{x}_1 = -a - jb \cong |\vec{x}_1| \theta_{x_1} \pm 180^\circ$$

$$\text{Ex: } \vec{z} = 30 / -40^\circ$$

$$-\vec{z} = -(30 / -40^\circ)$$

$$= 30 / (-40 \pm 180^\circ)$$

$$= 30 / 140^\circ$$

$$= 30 / -220^\circ$$

* Conjugate of $\vec{x}_1 \triangleq \vec{x}_2^*$

$$\vec{x}_1^* = a - jb$$

$$= |\vec{x}_1| - \theta_{x_1}$$

Ex:- $\vec{z}_1 = 2 + j3$

$$\vec{z}_2 = -2 - j4$$

$$\vec{z}_3 = 50 \angle 220^\circ$$

$$\vec{z}_4 = 10 \angle -170^\circ$$

Sol \rightarrow

$$\vec{z}_1^* = 2 - j3$$

$$\vec{z}_2^* = -2 + j4$$

$$\vec{z}_3^* = 50 \angle -220^\circ = 50 \angle -140^\circ$$


$$\vec{z}_4^* = 10 \angle 170^\circ$$

* Sum and difference of two complex numbers:

$$\vec{x}_1 + \vec{x}_2 = (a + jb) + (c + jd)$$

$$= (a + c) + j(b + d)$$
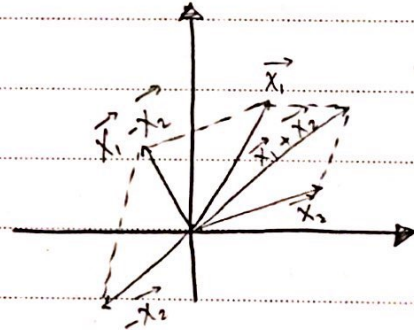
$$\vec{x}_1 - \vec{x}_2 = (a - c) + j(b - d)$$



Ex:- $\vec{x}_1 = 3 + j4$

$$\vec{x}_2 = -2 - j3$$

$$\vec{x}_1 + \vec{x}_2 = 1 + j \triangleq \sqrt{2} \angle \tan^{-1}(1)$$

$$\vec{x}_1 - \vec{x}_2 = 5 + j7 = \sqrt{25 + 49} \angle \tan^{-1}(7/5)$$

* multiplication:-

$$\begin{aligned}\vec{x}_1 \cdot \vec{x}_2 &= (a+jb)(c+jd) \\ &= ac + jad + jbc - bd \\ &= (ac - bd) + j(ad + bc)\end{aligned}$$

$$\begin{aligned}\vec{x}_1 \cdot \vec{x}_2 &= \left(|\vec{x}_1| \angle \theta_{x_1} \right) \left(|\vec{x}_2| \angle \theta_{x_2} \right) \\ &= |\vec{x}_1| |\vec{x}_2| (\theta_{x_1} + \theta_{x_2})\end{aligned}$$

$$\begin{aligned}\text{Ex:- } \vec{z} &= 3 \angle 73^\circ, \vec{y} = 6 \angle 12^\circ \\ \vec{z} \vec{y} &= 18 \angle 85^\circ\end{aligned}$$

* Division:-

$$\begin{aligned}\frac{\vec{x}_1}{\vec{x}_2} &= \frac{a+jb}{c+jd} \cdot \frac{\vec{x}_2^*}{\vec{x}_2^*} = \frac{(a+jb)(c-jd)}{\vec{x}_2 \cdot \vec{x}_2^*} = \frac{(a+jb)(c-jd)}{|\vec{x}_2|^2} \\ &= \frac{(ac - bd) + j(bc - ad)}{c^2 + d^2}\end{aligned}$$

$$\frac{\vec{x}_1}{\vec{x}_2} = \frac{|\vec{x}_1| \angle \theta_{x_1}}{|\vec{x}_2| \angle \theta_{x_2}} = \frac{|\vec{x}_1|}{|\vec{x}_2|} (\theta_{x_1} - \theta_{x_2})$$

$$\text{Ex:- } \frac{30 \angle 12^\circ}{5 \angle 3^\circ} = 6 \angle 9^\circ$$

$$\begin{aligned}\# \text{ Notes:- } \vec{x} + \vec{x}^* &= (a+jb) + (a-jb) \\ &= 2a\end{aligned}$$

$$\bullet \vec{x} - \vec{x}^* = 2jb$$

$$\bullet \vec{x} \cdot \vec{x}^* = |\vec{x}|^2$$

$$\bullet (\vec{x}^*)^* = \vec{x}$$


$$\bullet \frac{\vec{x}}{\vec{x}^*} = \frac{|\vec{x}| \angle \theta_x}{|\vec{x}| \angle \theta_x} = 1 \angle 2\theta = e^{j2\theta_x}$$

- $\vec{z} = 1 \angle 90^\circ \triangleq e^{j90^\circ}$
 $\triangleq 1 \cos(90^\circ) + j(1) \sin(90^\circ)$
 $\triangleq j$

$$j \triangleq 1 \angle 90^\circ = e^{j90^\circ}$$

$$-j \triangleq 1 \angle -90^\circ = e^{-j90^\circ}$$

Ex: $\vec{z} = 5 \angle 0^\circ$
 $= 5 \angle 36^\circ$
 $= 5 \angle -36^\circ$
 $= 5 + j0$
 $= 5$

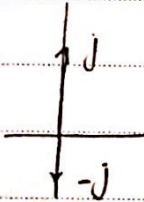
-  $\vec{z} = 5 \angle \pm 180^\circ$
 $= -5 + j0$

* AC Circuits :-

• Sinusoids Characteristics :-

$$v(t) = V_m \sin(\omega t)$$

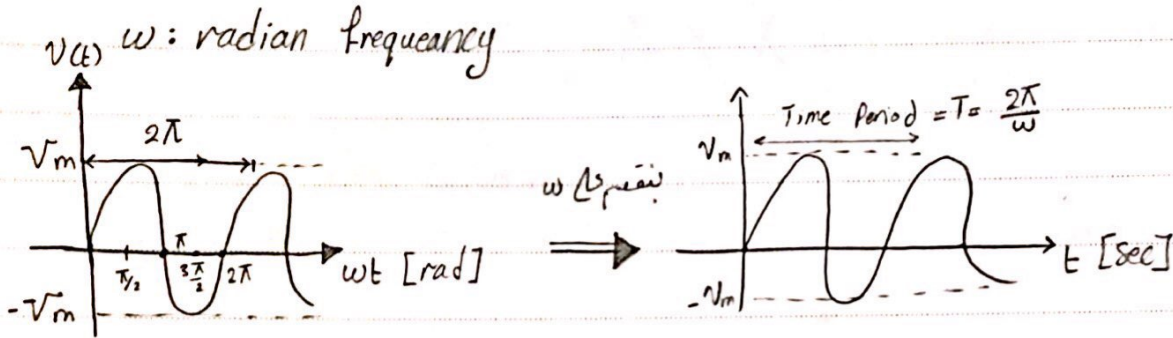V_m : peak value or amplitude
 ωt : argument (angle) [rad]



Frequency $\Rightarrow F = \frac{1}{T}$ [Hz] # number of cycles per sec.

$$\omega = \frac{2\pi}{T} \Rightarrow \omega = 2\pi f$$

Ex:- $v(t) = 20 \sin(1000t)$


Find f and T

Sol $\rightarrow f = \frac{\omega}{2\pi} = \frac{1000}{2\pi} = \dots$

Ex:- $v(t) = 10 \sin(2000\pi t)$, find f & T

$$f = \frac{\omega}{2\pi} = \frac{2000\pi}{2\pi} = 1000 \text{ Hz}$$

$$T = \frac{1}{f} = 1 \text{ m sec}$$

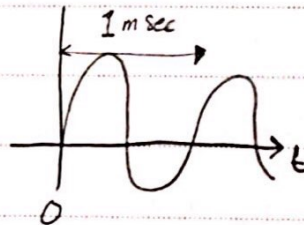

Ex:- $v(t) = 220 \cos(100\pi t)$

$$f = \frac{\omega}{2\pi} = 50 \text{ Hz}$$

* more general case :-


$$V(t) = V_m \sin(\omega t + \theta)$$

argument or angle "Phase"

If $\theta = 0 \rightarrow V_1(t)$

If $\theta < 0 \rightarrow V_2(t)$

If $\theta > 0 \rightarrow V_3(t)$

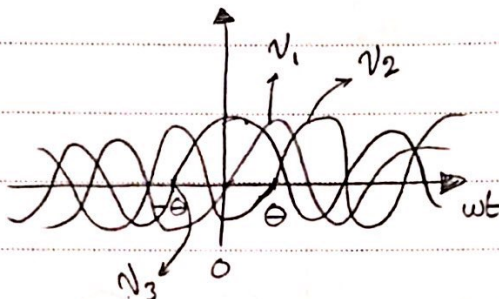

Lagging & Leading :-

$V_3(t)$ leads $V_1(t)$ by θ

$V_2(t)$ lags $V_1(t)$ by θ

$V_1(t)$ lags $V_2(t)$ by $-\theta = (2\pi - \theta)$

$V_2(t)$ leads $V_1(t)$ by $-\theta$

V_3 leads V_2 by 2θ

▶ To Compare two signals :-


- ① Both must be cosine or sine.
- ② Both must have +ve amplitude
- ③ Both must have same " ω "

* Note →

$$\begin{aligned} -\sin(\omega t) &= \sin(\omega t \pm 180^\circ) \\ -\cos(\omega t) &= \cos(\omega t \pm 180^\circ) \\ \mp \sin(\omega t) &= \cos(\omega t \pm 90^\circ) \\ \pm \cos(\omega t) &= \sin(\omega t \pm 90^\circ) \end{aligned}$$

Ex: $v_1(t) = 10 \cos(1000\pi t - 10^\circ)$

$v_2(t) = 2 \cos(1000\pi t + 40^\circ)$

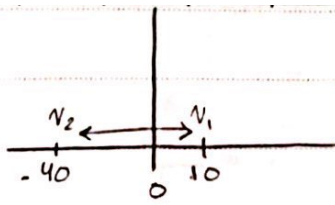

- v_2 leads v_1 by 50° (-310°)

v_1 lags v_2 by 50°


v_2 lags v_1 by -50° (310°)

Ex: $v_1(t) = -2 \cos(100\pi t + 20^\circ)$

$v_2(t) = 12 \sin(100\pi t - 40^\circ)$

Sol. $\rightarrow v_1 = 2 \sin(100\pi t + 20^\circ - 90^\circ)$

$v_1(t) = 2 \sin(100\pi t - 70^\circ)$

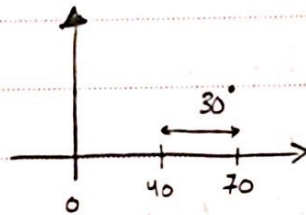

* phasors:

Convert the sinusoids from time-domain to phasor domain (complex number)

$v(t) = V_m \cos(\omega t + \theta)$

let $Z(t) = V_m e^{j(\omega t + \theta)}$

$= V_m \cos(\omega t + \theta)$

$= V_m \cos(\omega t + \theta) + j V_m \sin(\omega t + \theta)$

$v(t) = \text{Re} \{ Z(t) \} = \text{Re} \{ V_m e^{j(\omega t + \theta)} \} = \text{Re} \{ V_m e^{j\theta} \cdot e^{j\omega t} \}$

* Time-domain \rightarrow phasor domain

* $v(t) = V_m \cos(\omega t + \theta) \rightarrow \vec{V} = V_m \angle \theta$

* Ckt analysis using differential eq \rightarrow Ckt analysis using algebraic eq

* very complicated analysis.


Ex: $i_1(t) = 6 \cos(50t - 40^\circ) \Rightarrow \vec{I}_1 = 6 \angle -40^\circ \text{ A}$

$v_1(t) = -4 \sin(30t + 50^\circ)$

$= 4 \cos(30t + 50^\circ + 90^\circ)$

$= 4 \cos(30t + 140^\circ)$

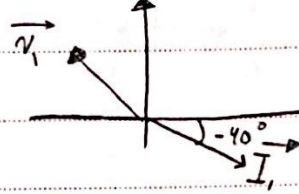$\Rightarrow \vec{v}_1 = 4 \angle 140^\circ \text{ V}$



$\vec{I} = 30 \angle -20^\circ \rightarrow i(t) = 30 \cos(\omega t - 20^\circ)$

$\vec{I} = -3 + j4 \text{ A}$

$= \sqrt{9+16} \angle \tan^{-1}(4/-3)$

$= 5 \angle 126.87^\circ \rightarrow i(t) = 5 \cos(\omega t + 126.87^\circ)$

Find $\rightarrow i(t) = \underbrace{4 \cos(\omega t + 30^\circ)}_{i_1(t)} + \underbrace{5 \sin(\omega t - 20^\circ)}_{i_2(t)}$

$i_1(t) \rightarrow \vec{I}_1 = 4 \angle 30^\circ$

$i_2(t) = 5 \cos(\omega t - 20^\circ - 90^\circ)$

$\vec{I}_2 = 5 \angle -110^\circ$

* $\vec{I} = \vec{I}_1 + \vec{I}_2 = 4 \angle 30^\circ + 5 \angle -110^\circ$

$= 3.218 \angle -56.97^\circ$


$i(t) = 3.218 \cos(\omega t - 56.97^\circ)$

* Phasors :-

$$v(t) = V_m \cos(\omega t + \theta) \rightarrow \vec{V} = V_m \angle \theta$$

$$i(t) = I_m \cos(\omega t + \theta) \rightarrow \vec{I} = I_m \angle \theta$$

* Impedance Z [Ω]

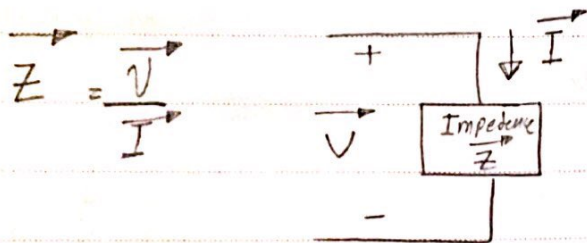


$$\vec{Z} = R + jX$$

resistor
absorb energy

reactance
"store element"

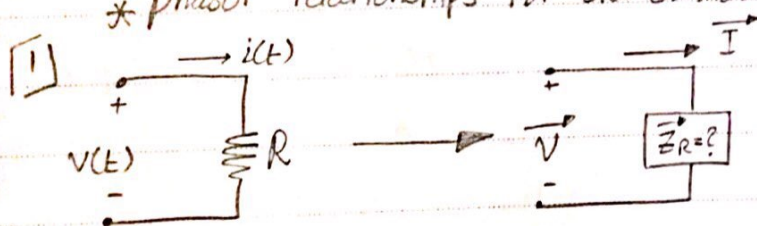* phasor relationships for CKT elements :-



time-domain

$$v(t) = V_m \cos(\omega t + \theta_v) \Rightarrow \vec{V} = V_m \angle \theta_v \text{ V}$$

$$i(t) = I_m \cos(\omega t + \theta_i) \Rightarrow \vec{I} = I_m \angle \theta_i \text{ A}$$

$$v(t) = R i(t)$$

$$= R I_m \cos(\omega t + \theta_i) \rightarrow \vec{V} = V_m \angle \theta_v$$


$$= R I_m \angle \theta_i$$

$\rightarrow V_m = R I_m \rightarrow v(t) \text{ \& } i(t) \text{ for } R$
are in phase.



$$\vec{V} = R I_m \angle \theta_i$$

$$\vec{V} = R \vec{I}$$

$$\vec{Z}_R = R$$

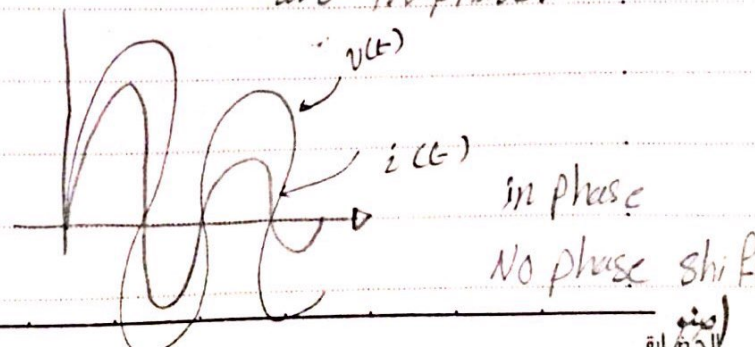

2 Inductors :-

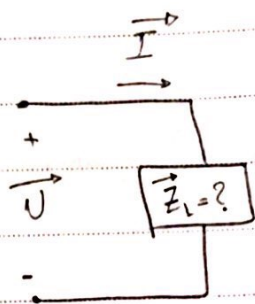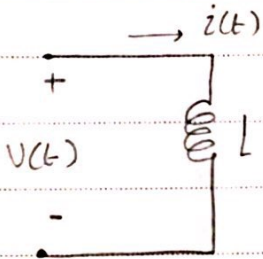

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$v(t) = L \frac{di(t)}{dt}$$

$$\vec{V} = V_m \angle \theta_v$$

$$\vec{I} = I_m \angle \theta_i$$


$$= -L I_m \omega \sin(\omega t + \theta_i)$$

$$= \omega L I_m \cos(\omega t + \theta_i + 90^\circ)$$

$$\vec{V} = \omega L I_m \angle \theta_i + 90^\circ$$

$$V_m = \omega L I_m$$

$$\theta_v = \theta_i + 90^\circ$$

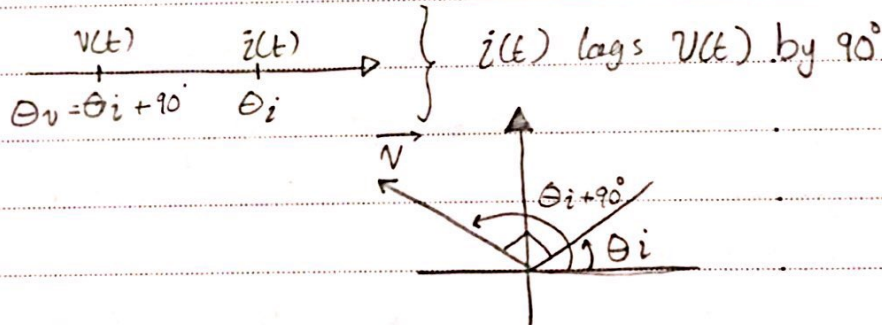

$$\vec{V} = \omega L I_m \angle \theta_i + 90^\circ$$


$$\vec{V} = (\omega L \angle 90^\circ) (I_m \angle \theta_i)$$

$$\vec{V} = j\omega L \vec{I}$$

$$\vec{Z}_L = j\omega L$$

→ ωL


3] Capacitor :-

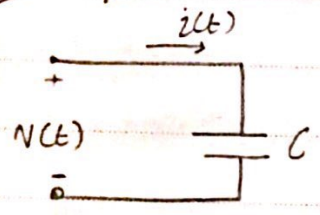

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$i(t) = C \frac{dv}{dt}$$

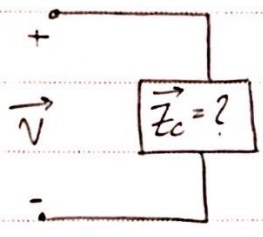

$$\vec{V} = V_m \angle \theta_v$$

$$\vec{I} = I_m \angle \theta_i$$

$$\Rightarrow i(t) = -C V_m \omega \sin(\omega t + \theta_v)$$

$$= \omega C V_m \cos(\omega t + \theta_v + 90^\circ)$$

$$\vec{I} = \omega C V_m \angle \theta_v + 90^\circ$$

$$I_m = \omega C V_m$$

$$\theta_i = \theta_v + 90^\circ$$



$i(t)$ leads $v(t)$ by 90°
 The is called leading element.

$$\vec{I} = (\omega C \angle 90^\circ) (V_m \angle \theta_v)$$


$$\vec{I} = j\omega C \vec{V}$$

$$\vec{V} = \frac{1}{j\omega C} \vec{I}$$
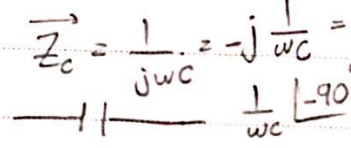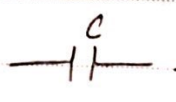
$$\vec{Z}_c = \frac{1}{j\omega C} = -j \frac{1}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$$



Ex: Find $i(t)$ →

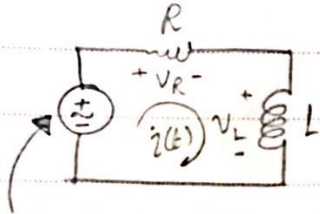

$$v(t) = V_m \cos(\omega t + \theta)$$

Sol →

$$-v(t) + v_R(t) + v_L(t) = 0$$

$$-v(t) + Ri(t) + L \frac{di}{dt} = 0$$

$$\Rightarrow L \frac{di}{dt} + Ri = V_m \cos(\omega t + \theta)$$

we propose → $i(t) = I_m \cos(\omega t + \phi)$

$$\Rightarrow -L I_m \omega \sin(\omega t + \theta) + R I_m \cos(\omega t + \theta) = V_m \cos(\omega t + \theta) \Rightarrow$$

$i(t)$ leads $v(t)$ by 90°


using $A \cos \alpha + B \sin \alpha = \sqrt{A^2 + B^2} \cos(\alpha + \tan^{-1}(\frac{-B}{A}))$ The $+$ is called leading element.

$$\sqrt{R^2 I_m^2 + \omega^2 L^2 I_m^2} \cos(\omega t + \theta + \tan^{-1}(\frac{\omega L I_m}{R I_m})) = V_m \cos(\omega t + \theta)$$

$$I_m \sqrt{R^2 + \omega^2 L^2} \cos(\omega t + \theta + \tan^{-1}(\frac{\omega L}{R})) = V_m \cos(\omega t + \theta)$$

$$\rightarrow I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \rightarrow i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \theta - \tan^{-1}(\frac{\omega L}{R}))$$

$$\phi = \theta - \tan^{-1}(\frac{\omega L}{R})$$

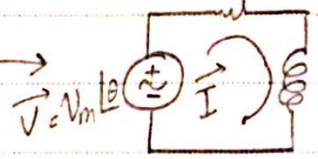OR →  $j\omega L = \omega L \angle 90^\circ \rightarrow I = \frac{V}{R + j\omega L} = \frac{V_m \angle \theta}{\sqrt{R^2 + \omega^2 L^2} \angle \tan^{-1}(\frac{\omega L}{R})}$

$$= \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle \theta - \tan^{-1}(\frac{\omega L}{R}) \rightarrow$$

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \theta - \tan^{-1}(\frac{\omega L}{R}))$$



1 Time-Domain \longrightarrow phasor Domain

$$u(t) = V_m \cos(\omega t + \theta)$$



$$i(t) = I_m \cos(\omega t + \phi)$$

$$\vec{V}^D = V_m \angle \theta^\circ$$

$$\vec{I}^D = I_m \angle \phi^\circ$$

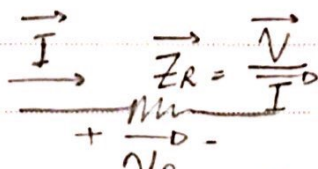
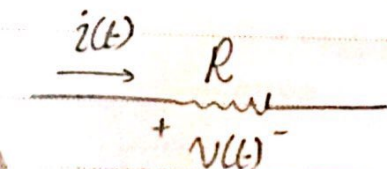


$$V_R^D = R I_R^D$$

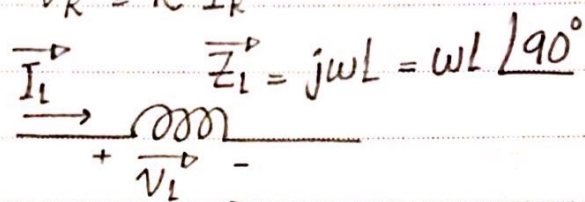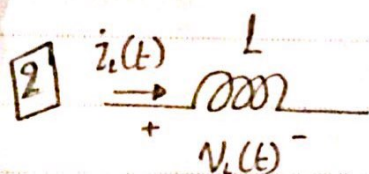

$$V_L^D = Z_L^D I_L^D = (j\omega L) I_L^D$$

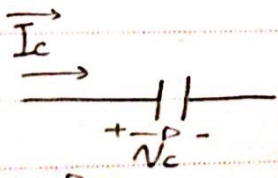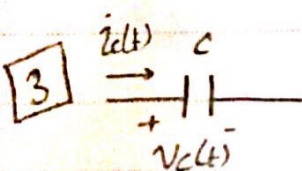I_L^D lags V_L^D by 90°
 lagging element.




$$Z_C^D = \frac{1}{j\omega C} = -j \frac{1}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$$


$$V_C = Z_C I_C$$

I_C leads V_C^D by 90°
 is called leading element.

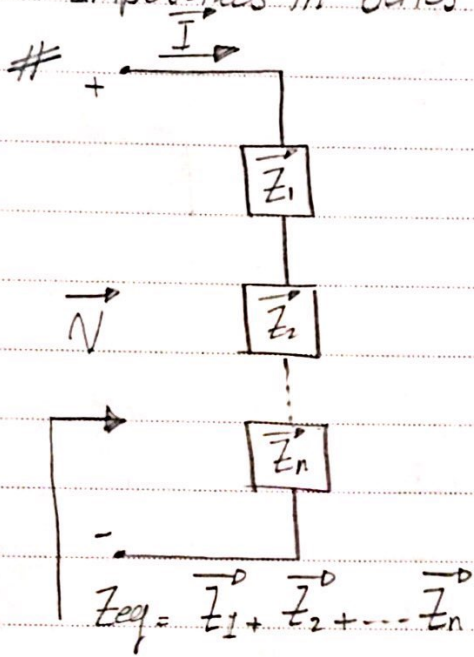
• Impedances in Series & Voltage Division:




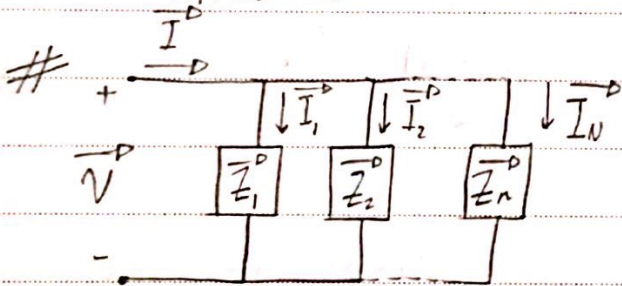
$$\vec{V}_n = \frac{\vec{Z}_n}{\vec{Z}_1 + \vec{Z}_2 + \dots + \vec{Z}_n} \vec{V}$$


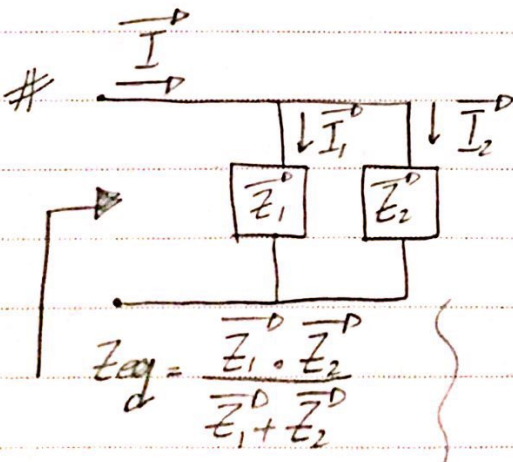
$$\vec{I}_n = \frac{\frac{1}{\vec{Z}_n}}{\frac{1}{\vec{Z}_1} + \frac{1}{\vec{Z}_2} + \dots + \frac{1}{\vec{Z}_n}} \vec{I} \quad (\text{Current division})$$




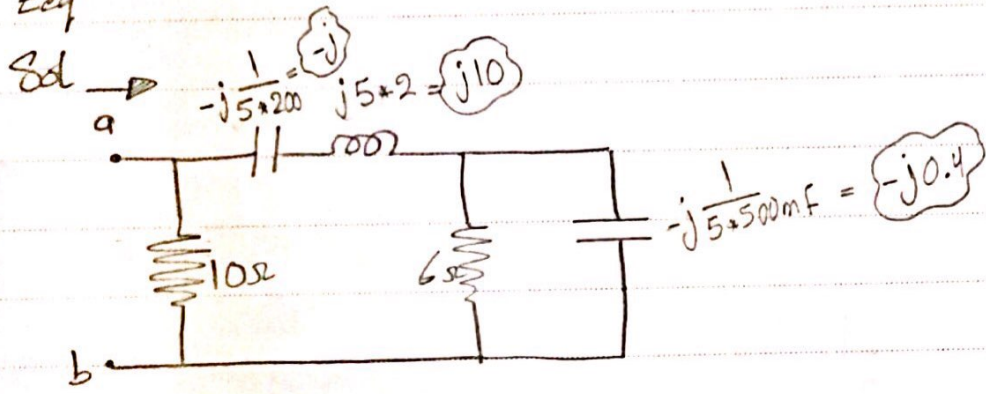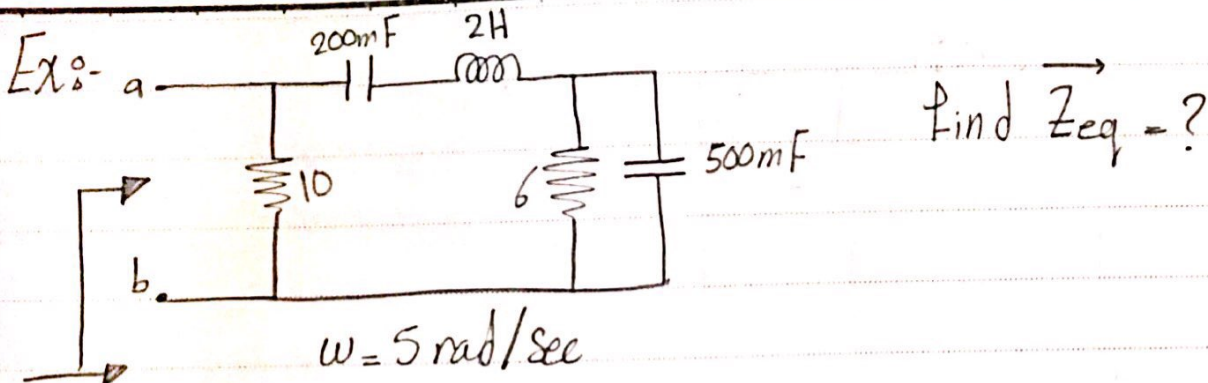
$$\vec{I}_1 = \frac{\vec{Z}_2}{\vec{Z}_1 + \vec{Z}_2} \vec{I}$$



- $(-j0.4) \parallel 6\Omega = \frac{-j0.4 \times 6}{-j0.4 + 6} = \frac{-j2.4}{6 - j0.4} = 0.02655 - j0.3985\Omega$
 $\cong 0.39911 \angle -86.18$
- $-j + j10 + 0.02655 - j0.3982 = 0.02655 + j8.602\Omega$
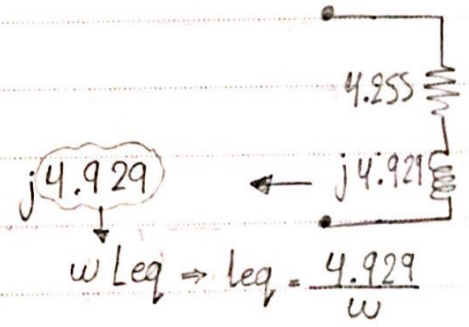
$$Z_{eq} = (10) \parallel (0.02655 + j8.602) = \frac{0.2655 + j86.02}{10.02655 + j8.602} = \underbrace{4.255}_R + j \underbrace{4.929}_I$$



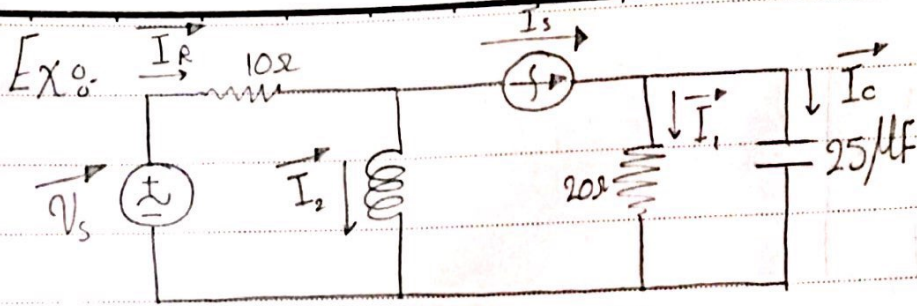


$$\omega = 1200 \text{ rad/Sec}$$

$$\vec{I}_c = 1.2 \angle 28^\circ \text{ A}$$

$$\vec{I}_L = 3 \angle 53^\circ \text{ A}$$

Find \vec{I}_s , \vec{V}_s , $i_R(t)$?

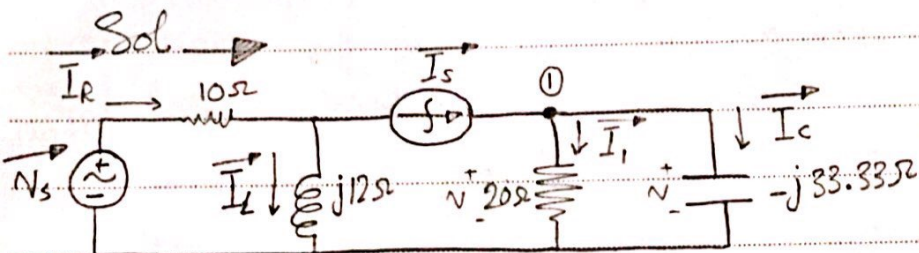

at ① $\vec{I}_s = \vec{I}_L + \vec{I}_c$
 $\vec{I}_s = \frac{\vec{I}_c(-j33.33)}{20} + \vec{I}_c$

$$\vec{I}_s = \frac{(1.2 \angle 28^\circ)(-j33.33)}{20} + 1.2 \angle 28^\circ$$

$$\vec{I}_s = 1.99 \angle -62^\circ + 1.2 \angle 28^\circ$$

$$= 2.33 \angle -31^\circ \text{ A}$$

2) $\vec{I}_R = \vec{I}_L + \vec{I}_s$
 $= 3 \angle 53^\circ + 2.33 \angle -31^\circ$
 $= 3.99 \angle 17.42^\circ \rightarrow i_R(t) = 3.99 \cos(1200t + 17.42^\circ) \text{ A}$

3) $\vec{V}_s = ?$



$$-\vec{V}_s + 10 \vec{I}_R + \vec{I}_L(j12) = 0$$

$$\vec{V}_s = 10(3.99 \angle 17.42^\circ) + (3 \angle 53^\circ)(12 \angle 90^\circ)$$

$$\vec{V}_s = 39.9 \angle 17.42^\circ + 36 \angle 143^\circ$$


$$= 39.9 \angle 74.5^\circ \text{ V}$$
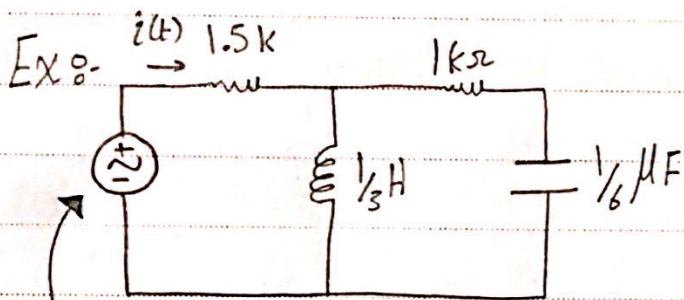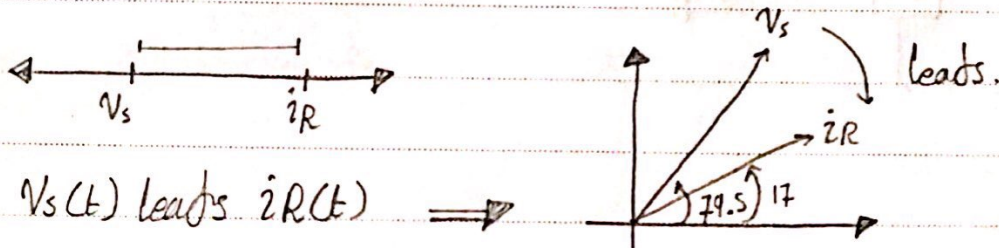
$$V_s(t) = 39.9 \cos(1200t + 74.5) \text{ V}$$



$$V_s(t) = 40 \sin(3000t) \text{ V}$$

find $i(t)$?

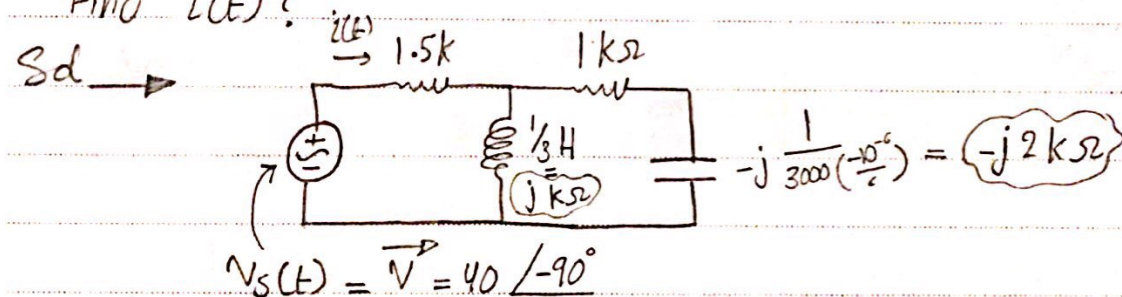


$$\vec{Z}_{eq} = [(1-j2) \parallel j] + 1.5 = \frac{(1-j2)(j)}{(1-j2)+j} + 1.5 = 2 - j1.5 \text{ k}$$

$$\vec{I} = \frac{\vec{V}}{\vec{Z}_{eq}} = \frac{40 \angle -90^\circ}{(2-j1.5) \cdot 10^3} = 16 \angle -53^\circ \text{ mA}$$

$$i(t) = 16 \cos(3000t - 53^\circ) \text{ mA}$$

* Admittance :- \vec{Y}

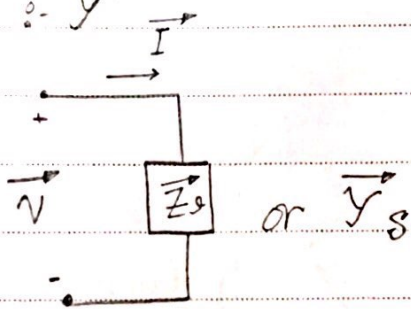

$$\vec{Z} = \frac{\vec{V}}{\vec{I}}$$

$$\vec{Y} = \frac{\vec{I}}{\vec{V}} = \frac{1}{\vec{Z}}$$

$$\vec{Z} = R + jX \text{ [}\Omega\text{]}$$


$$\vec{Y} = G + jB \text{ (S)}$$

Condensitors \swarrow Substance \searrow


$$\vec{Y} = \frac{1}{\vec{Z}} = \frac{1}{R + jX} = \frac{R - jX}{R - jX}$$

$$\frac{R - jX}{R^2 + X^2} = \frac{R}{R^2 + X^2} - j \frac{X}{R^2 + X^2}$$
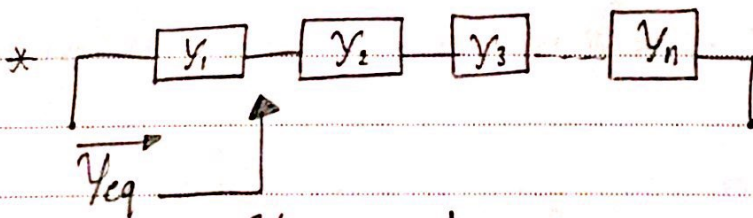
$$G = \frac{R}{R^2 + X^2}, \quad B = \frac{-X}{R^2 + X^2}$$



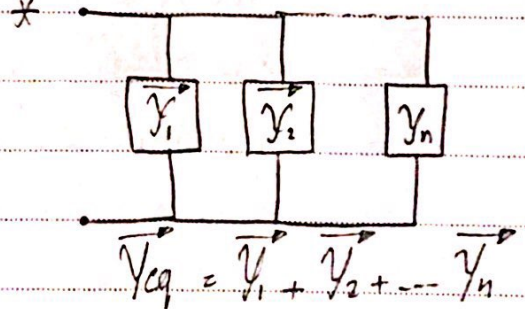
$$\vec{Y}_{eq} = \frac{1}{\frac{1}{\vec{Y}_1} + \frac{1}{\vec{Y}_2} + \frac{1}{\vec{Y}_n}}$$



$$\vec{Y}_{eq} = \vec{Y}_1 + \vec{Y}_2 + \dots + \vec{Y}_n$$

* Nodal & Mesh Analysis :-

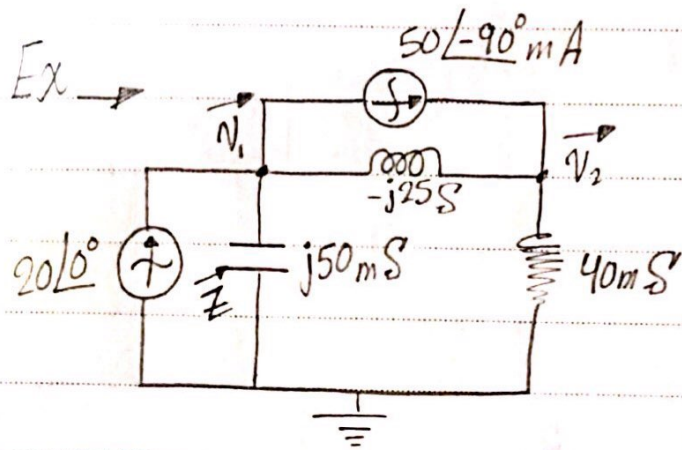

Find \vec{V}_1 & \vec{V}_2 using Nodal Analysis.

$$\text{Node ①: } 20\angle 0^\circ = \vec{V}_1(j50\text{ S}) + (\vec{V}_1 - \vec{V}_2)(-j25\text{ S}) + 50\angle -90^\circ\text{ A}$$

$$j50\vec{V}_1 - j25\vec{V}_1 + j25\vec{V}_2 = 20\angle 0^\circ - 50\angle -90^\circ$$

$$\rightarrow j25\vec{V}_1 + j25\vec{V}_2 = 20 + j50 \quad \text{①}$$


$$\text{Node ②: } 50\angle -90^\circ\text{ mA} = (\vec{V}_2 - \vec{V}_1)(-j25\text{ mS}) + \vec{V}_2 40\text{ mS}$$

$$j25\vec{V}_1 + (40 - j25)\vec{V}_2 = 50\angle -90^\circ \quad \text{②}$$


Solving \rightarrow

$$\vec{V}_1 = 1.062\angle 23.3^\circ\text{ V}$$
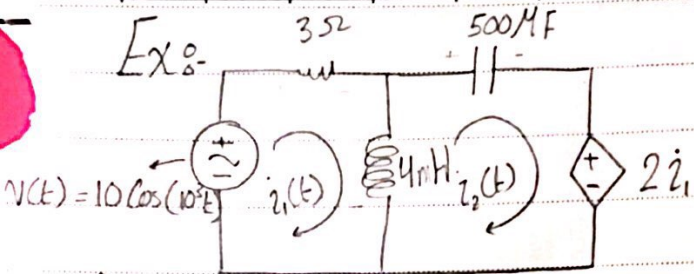
$$\vec{V}_2 = 1.593\angle -80^\circ\text{ V}$$



Find $i_1(t)$ & $i_2(t)$

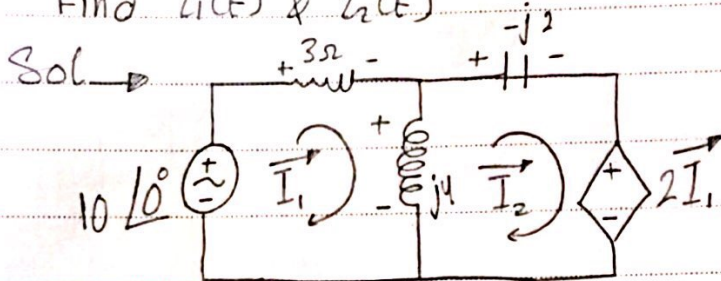


mesh 1 → $-10 + 3\vec{I}_1 + j4(\vec{I}_1 + \vec{I}_2) = 0$
 $(3 + j4)\vec{I}_1 - j4\vec{I}_2 = 10 \rightarrow \textcircled{1}$

mesh 2 → $-j4(\vec{I}_1 - \vec{I}_2) + (-j2\vec{I}_2) + 2\vec{I}_1 = 0$
 $(2 - j4)\vec{I}_1 + j2\vec{I}_2 = 0 \rightarrow \textcircled{2}$


Solving $\textcircled{1}$ & $\textcircled{2}$ → $\vec{I}_1 = 1.24 \angle 29.7^\circ \text{ A}$
 $\vec{I}_2 = 2.77 \angle 56.3^\circ \text{ A}$

$i_1(t) = 1.24 \cos(1000t + 29.7^\circ) \text{ A}$

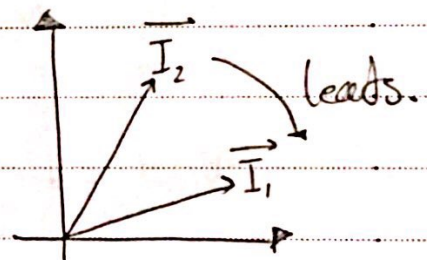$i_2(t) = 2.77 \cos(1000t + 56.3^\circ) \text{ A}$





* Superposition :-

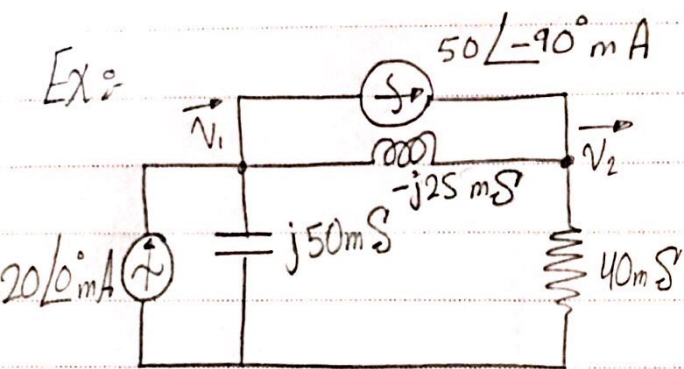

Find \vec{V}_1 using the superposition.

Sol →

Find \vec{V}_1'

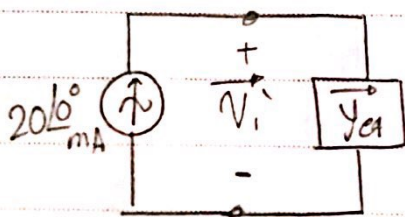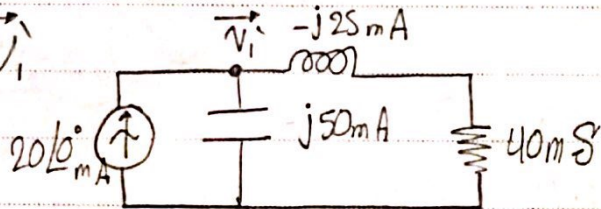


$$Y_{eq} = \frac{(-j25m)(40m)}{(40-j25)m} + j50mS$$

$$= \frac{-j}{40-j25} + j50 \times 10^{-3} = 0.011 + j0.032$$

$$\vec{V}_1' = \frac{20 \angle 0^\circ}{0.011 + j0.032} \times 10^{-3} = 0.195 - j0.556 \text{ V}$$


Find \vec{V}_1''

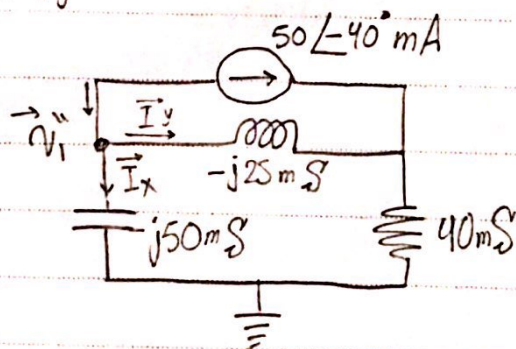

$$I_x = \frac{1}{\frac{-j25mS}{j25mS + \frac{1}{40mS} + \frac{1}{j50mS}} (-50 \angle -90^\circ)}$$

$$= \frac{j40}{j40 + 25 + j20} (50 \angle 90^\circ)$$

$$V_1'' = I_x * (j50m)$$

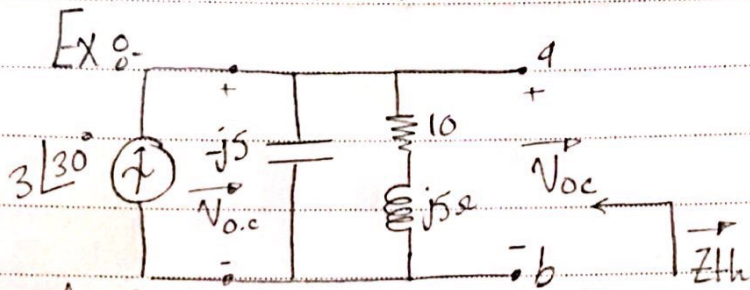

Find the Thevenin equivalent ckt
Seen by points a & b

