

Answers should be written in ink

Exam Duration: 70 min

Useful information : for silicon , $\mu_n = 1350 \text{ cm}^2/\text{V-s}$ and $\mu_p = 480 \text{ cm}^2/\text{V-s}$.

$n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$. $V_T = 0.026 \text{ V}$ at 300K.

Use the linearized diode model with $r_f = 0 \text{ ohm}$ unless otherwise mentioned.

Q1 a) Consider n-type ~~Ge~~ at T = 300 K doped to a concentration of $N_d = 5 \times 10^{15} \text{ cm}^{-3}$. Assume mobility values of $\mu_n = 1350 \text{ cm}^2/\text{V-s}$ and $\mu_p = 480 \text{ cm}^2/\text{V-s}$. Determine the conductivity of the material.

$$n_i^2 = \beta T^{3/2} \cdot e^{-E} \\ n_i^2 = n_0 P_0$$

because of $N_d > n_i^2$

$$N_d = P_0 = 5 \times 10^{15}$$

$$n_0 = \frac{n_i^2}{P_0} = \frac{(2.25 \times 10^{10})^2}{5 \times 10^{15}}$$

$$n = 45 \times 10^3$$

$$\sigma = e n \mu_n + e P \mu_p$$

$$\sigma = (1.6 \times 10^{19}) (45 \times 10^3) \left(\frac{1350}{480} \right) + (1.6 \times 10^{19}) (5 \times 10^{15}) (480) \\ = 9.72 \times 10^{12} + 384 \times 10^{-3} = 0.384 \text{ (cm-s)}^{-1}$$

Determine the applied electric field that induces a drift current density of 175 A/cm².

$$J = \sigma E$$

$$\frac{175}{0.384} = E \Rightarrow E = 455.72 \text{ N/C}$$

b) A silicon pn junction at T = 300 K is doped with $N_d = 10^{16} \text{ cm}^{-3}$ and $N_a = 10^{15} \text{ cm}^{-3}$. The junction capacitance is to be 0.8 pF when a reverse bias voltage of 13 V is applied. Find the zero-biased junction capacitance.

$$C_j = 0.8 \text{ pF}$$

$$V_{Rb} = 13 \text{ V}$$

Final answer

$$C_{j0} = 3.70 \text{ pF}$$

$$C_j = C_{j0} \left(1 + \frac{V_R}{V_{bi}} \right)^{-1/2}$$

$$0.8 = C_{j0} \left(1 + \frac{13}{V_{bi}} \right)^{-1/2}$$

$$0.8 = C_{j0} \left(1 + \frac{13}{0.637} \right)^{-1/2}$$

$$\frac{0.8}{0.216} = \frac{C_{j0}}{0.216}$$

$$V_{bi} = V_T \ln \left(\frac{N_a N_d}{n_i^2} \right)$$

$$6V_{bi} = 0.026 \ln \left(\frac{10^{16} \cdot 10^{15}}{(1.5 \times 10^{10})^2} \right)$$


$$= 0.026 \ln \left(\frac{1 \times 10^{31}}{2.25 \times 10^{20}} \right)$$

$$= 0.637$$

Q3 a) The circuit and diode parameters for the circuit shown are $V_{PS} = 9.7$ V, $R = 9.9$ K ohm, $V_y = 0.7$ V, $r_f = 100$ ohm and $v_i = 0.2 \sin \omega t$ V.

Calculate the time-varying diode current and voltage.

First $v_i || V_i$ source: we get a DC-circuit

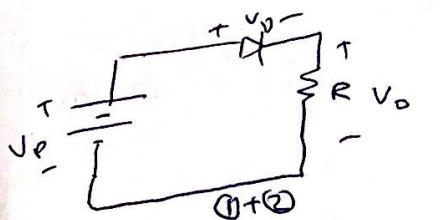

$$V_D = I_D \cdot R + V_D$$

$$9.7 = 9.9 I_D + V_D$$

$$9.7 = 9.9 I_D + V_D$$

$$-0.7 = 100 I_D - V_D$$

$$8.18 \times 10^{-5}$$

$$q = \frac{109.9 I_D}{109.9} \Rightarrow I_D = 8.18 \times 10^{-5} A$$

$$V_D = I_D r_f + V_y$$

$$V_D = 100 I_D + 0.7$$


$$-0.7 = 100 I_D - V_D$$

$$11.97 V$$

2.5

$$V_D = \frac{V_T}{I_D} = \frac{0.026}{0.08} = 0.325 V$$

then when we switch off v_i

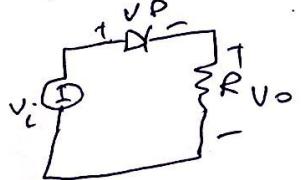

$$U_i = i_D (R + r_d)$$

$$\text{then } i_D = \frac{U_i}{R + r_d} = \frac{0.2 \sin(\omega t)}{9.9 + 0.325} = 1.957 \times 10^{-5} \sin(\omega t) A$$

time varying current

$$r_d = r_d / i_d$$

b) Assume each diode in the circuit shown has a cut-in voltage of $V_y = 0.7$ V, $r_f = 50$ ohm and $V_t = 6.1$ V. Determine the value of R_1 required such that I_{D1} is one-half the value of I_{D2} .

$$V_y = 0.7 = V_{D1} \text{ because of the sign}$$

$$I_{D2} = \frac{V_{D1}}{R_2} = \frac{0.7}{1 \times 10^3} = 7 \times 10^{-4} A = I_{D2} \rightarrow \text{then } V_{D2} = \frac{I_{D2}}{r_f} = \frac{7 \times 10^{-4}}{50} = 1.4 \times 10^{-5} V$$

if we apply KV1

$$-V_1 + V_{R1} + V_{D2} + V_{R2} = 0$$

$$-6.1 + V_{R1} + 1.4 \times 10^{-5} + 0.7 = 0$$

$$V_{R1} = 5.39 V$$


and

$$V_{R2} = \frac{V_R}{R_2} = 0.7$$

2.5

$$\text{then } R_1 = \frac{V_{R1}}{I_{D2}} = \frac{5.39}{7 \times 10^{-4}} = 7700 \Omega$$

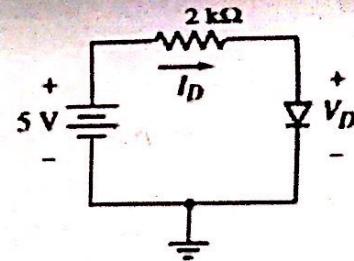Q2 a) Consider the following circuit, where $I_s = 10^{-12} \text{ A}$. Determine V_D , and I_D , using the diode equation and the trial and error method.



$$V_{PS} = R I_D + V_D$$

$$5 = 2 \times 10^3 \cdot \left(I_s \left[e^{\frac{V_D}{0.026}} - 1 \right] \right) + V_D$$


$$5 = 2 \times 10^3 \left(10^{-12} \left[e^{\frac{V_D}{0.026}} - 1 \right] \right) + V_D$$

after many trials

$$V_D = 0.5596 \text{ V}, \quad I_D = 2.2 \text{ mA}$$

4

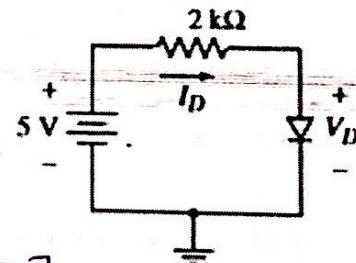b) Consider the circuit shown. Assume $V_T = 0.7 \text{ V}$, $r_f = 20 \text{ ohm}$, and $I_D = 1.2 \text{ mA}$. Use the piecewise linear model to calculate the voltage drop on the 2 K ohm resistor.



$$V_{PS} = 2 I_D R_D + V_D$$

$$5 = 2 \times 10^3 \cdot 2 \times 10^{-3} + V_D$$

~~not correct~~

~~incorrect~~

$$V_D = I_D r_f + V_T$$

$$V_D = (1.2 \times 10^{-3})(20) + 0.7$$

$$= 0.724 \text{ V}$$


What is the power dissipated in the diode?

2

$$P = I_D V_D = 8.688 \times 10^{-4} \text{ W}$$


Q4 Consider the circuit shown, where $V_D = 0.7 \text{ V}$, $r_f = 50 \text{ ohm}$ and $R_2 = 2 \text{ K ohm}$.

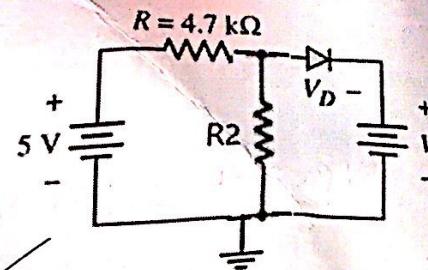i) Find the supply voltage V such that the diode current is 0.2 mA .



$$V_D = I_D \cdot r_f + V_D \\ = (0.2 \times 10^{-3})(50) + 0.7 = 0.71 \text{ V}$$

$$V_{R_2} = V + 0.71$$

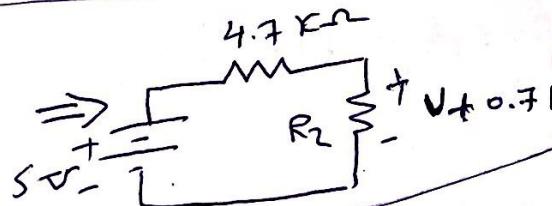

by applying KVL:

$$-5 + 4.7 \times 10^3 I_1 + 2 \times 10^3 I_1 = 0$$

$$\frac{5}{6700} = \frac{6700 I_1}{6700}$$

$$I_1 = 7.46 \times 10^{-4} \text{ A}$$

$$V_{R_2} = \frac{I_1}{R_2} = \frac{7.46 \times 10^{-4}}{2 \times 10^3} \\ = 3.73 \times 10^{-7} \text{ V}$$

$$V_{R_2} = V + 0.71 \\ \Rightarrow V = 0.71 \text{ V}$$

2-5

ii) Calculate the current in the R_2 resistance when $V = 2 \text{ V}$.

according to this relation that we determine in the previous question:

$$V_{R_2} = V + 0.71 \Rightarrow V_{R_2} = 1.42 \text{ V}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{1.42}{2 \times 10^3} = 7.1 \times 10^{-4} \text{ A}$$

0

2-5