


Problem 1. Solve the following short problems.

(10.5 points) 4

3 a. For an 8-to-256 decoder implemented using decoder expansion, determine the required number of 2-input AND gates and inverters.

I. Number of 2-input AND gates = 304

II. Number of inverters = 8


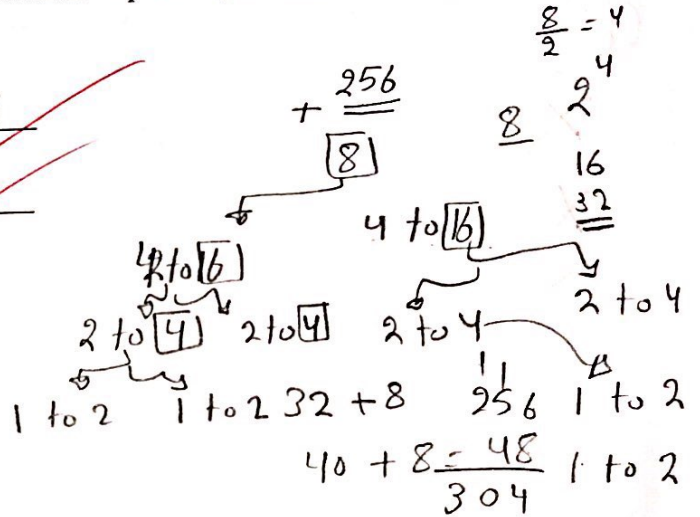


b. In order to implement an 8-to-1 Dual MUX with minimal cost using a decoder(s), 2-input AND gates and two OR gates, specify:

I. The type and number of decoders required? Dual 3-to-8 decoder.

II. The number of 2-input AND gates required? 8

 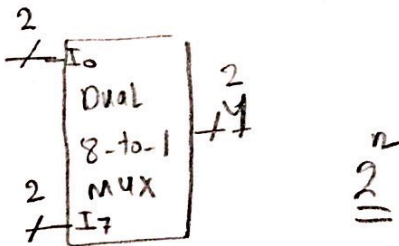III. Number of inputs for each OR gate? 8



$2^3 = 8 \Rightarrow 3-10-8$

$$\frac{000000_2}{\text{value}} \Rightarrow 100000$$

c. Using 5-bits:

100000

I. The minimum negative number using Sign-Magnitude format in binary = ~~100000~~

II. The minimum negative number using 1's complement format in binary = ~~011111~~

$$\begin{array}{r} 10 \\ \downarrow \\ 100000 \\ \underline{011111} \end{array}$$

d. Given an 8-to-3 high priority encoder with inputs D7-D0 and outputs A2-A0 and valid bit (V). Write the Boolean equations for A2, A1, and V.

①

~~$$A_2 = D_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + D_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + D_5 \bar{D}_6 \bar{D}_7 + D_6 \bar{D}_7$$~~

~~$$A_1 = D_1 \bar{D}_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + D_2 \bar{D}_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + D_3 \bar{D}_4 \bar{D}_5 \bar{D}_6 \bar{D}_7 + D_4 \bar{D}_5 \bar{D}_6 \bar{D}_7$$~~


~~$$V = D_0 + D_1 + D_2 + D_3 + D_4 + D_5 + D_6 + D_7$$~~

V	A ₂	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	0	X	X	X	X	X	X	X	X
0	0	0	1	1	0	0	0	0	0	0	0
0	0	1	0	X	X	1	0	0	0	0	0
0	0	1	1	X	X	X	1	0	0	0	0
1	0	0	0	X	X	X	X	1	0	0	0
1	0	1	0	X	X	X	X	X	1	0	0
1	1	0	0	X	X	X	X	X	X	1	0
1	1	1	0	X	X	X	X	X	X	X	1

e. Using only the two half adders given below, implement function $F(x,y,z)$ given by the equation: $F(x,y,z) = (x.z) \oplus y$

Hint: You must show clearly all connections and labeling.

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

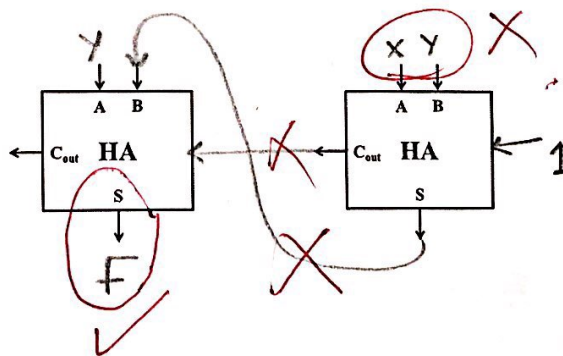




x	o/r
0	0
0	1
1	0
1	0
<hr/>	
x	
z	
x?	

Problem 2. A digital circuit receives three 1-bit inputs (A, B, and M) and produces 1-bit output (F). The behavior of the circuit is described in the table below. Formulate the truth table of the circuit. Don't derive the expression for the output and Don't design the circuit. (2 points)

When M = 0	F = Minimum of A and B.
When M = 1	F = Maximum of A and B.

A	B	M	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 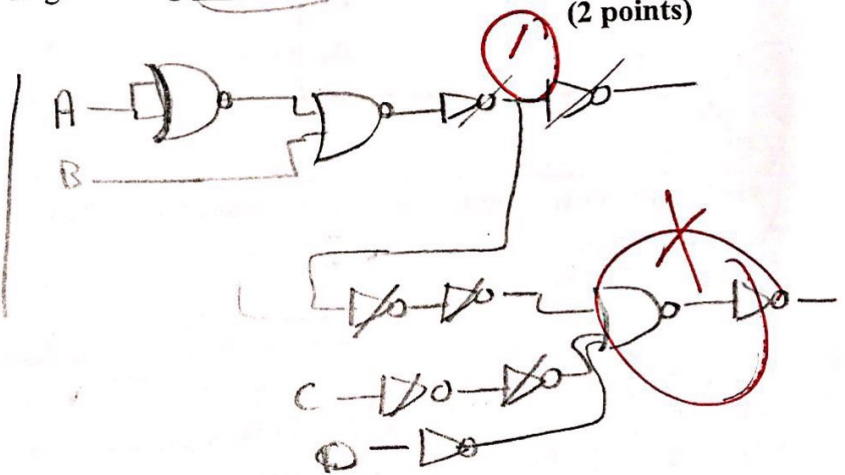 
Problem 3. Implement the following logic diagram using only NOR gates. The number of NOR gates should be minimum. (2 points)



Problem 4. Draw the required connections in the circuit below in order to implement functions F and G . You are allowed to add as many inputs as you need to the OR gate and the AND gate. You are also allowed to add three inverters (if needed).


X	Z	
0	0	0 D_0
0	1	1 D_1
1	0	1 D_2
1	1	0 D_3

$F(X,Z) = X\bar{Z} + \bar{X}Z \Rightarrow (X+\bar{X})(\bar{Z}+Z)$ (2 points)
 $G(X,Y,Z) = \prod_M(0,4,7) \Rightarrow (1,2,3,5,6)$

 





Problem 5. Given the following implementation of the function $F(X,Y,Z)$, write the minterms of F in the equation below.

X	Y	Z	F
S_1	S_0	A	
0	0	0	1 m_0
0	0	1	0 m_1
0	1	0	0 m_2
0	1	1	0 m_3
1	0	0	0 m_4
1	0	1	1 m_5
1	1	0	1 m_6
1	1	1	1 m_7

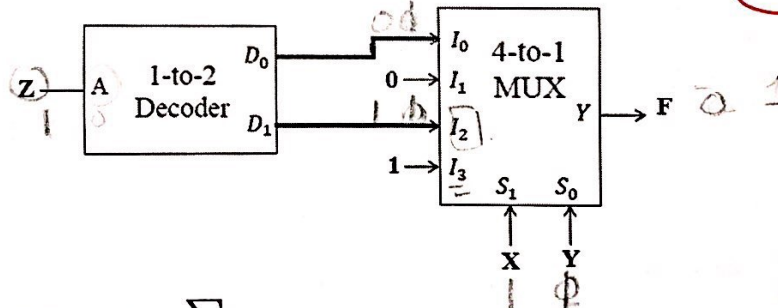


$F(X,Y,Z) = \sum_m(0, 5, 6, 7)$


Problem 6. Implement a 3-to-8 decoder using any number of 1-to-4 DMUXes (block shown below). The 3-to-8 decoder has 3 inputs ($A_2 A_1 A_0$) and 8 outputs ($D_7 D_6 D_5 D_4 D_3 D_2 D_1 D_0$). Make sure that you label all inputs/outputs and clearly show the connections of your design. (3 points)

    

 Problem 7. Given the following 6-bit adder/subtractor, answer the three questions below: (4.5 points)



 
I. Assume that inputs A and B are unsigned numbers set to the following values: $A = (101110)_2$ and $B = (011101)_2$. The $\overline{Add/Sub}$ control is set to 0. Accordingly, compute the sum bits $S[5:0]$ and determine if there is an overflow or not.



$S_5 S_4 S_3 S_2 S_1 S_0 = 001011$

Is there an overflow? Yes

 
II. Assume that inputs A and B are signed numbers in 2's complement format set to the following values: $A = (110110)_2$ and $B = (011001)_2$. The $\overline{Add/Sub}$ control is set to 0. Accordingly, compute the sum bits $S[5:0]$ and determine if there is an overflow or not.



$S_5 S_4 S_3 S_2 S_1 S_0 = 001111$


Is there an overflow? No

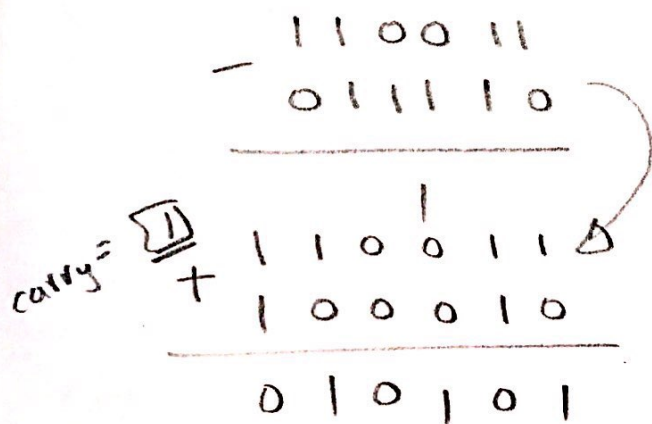III. Assume that inputs A and B are signed numbers in 2's complement format set to the following values: $A = (110011)_2$ and $B = (011110)_2$. The $\overline{Add/Sub}$ control is set to 1. Accordingly, compute the sum bits $S[5:0]$ and determine if there is an overflow or not.



$S_5 S_4 S_3 S_2 S_1 S_0 = 010101$

Is there an overflow? No

 

Problem 8. Assume X is a 4-bit unsigned number and Y is a 3-bit unsigned number. Using only the following 4-bit ripple carry adder, two 3-bit adder/subtractors, 5-bit 2-to-1 MUX, and any number of 2-input XOR gates, design a circuit that outputs a 5-bit unsigned number Z such that: (4 points)

$$Z = \begin{cases} Y \times 3, & \text{when } X \geq 2 \\ 7 - Y, & \text{when } X < 2 \end{cases}$$

1.75

Hints:

- You must show clearly all connections and labeling. Keep in mind that each of X consists of four bits: $X_3X_2X_1X_0$, Y consists of three bits: $Y_2Y_1Y_0$, and Z consists of five bits $Z_4Z_3Z_2Z_1Z_0$.
- $(3)_{10} = (011)_2$, $(7)_{10} = (111)_2$, and $(2)_{10} = (0010)_2$

