

▶ POWER UNIT

DEYA' ABUL-NADI
CIRCUITS I

MOHAMMED ZIAD

 POWER UNIT-JU



<http://POWER UNIT-JU.COM>

CH 12

- charges -

$Q, q, q(t)$

coulomb (c)

- current -

$I, i, i(t)$

$$I = \frac{dq}{dt}$$

amperes, A


- Voltage (potential difference) -

V_{ab} : the energy or work needed to move a unit charge from a to b

$$dV = \frac{dW}{dq}$$

$$V = \frac{dW}{dq}$$

W : work (energy)

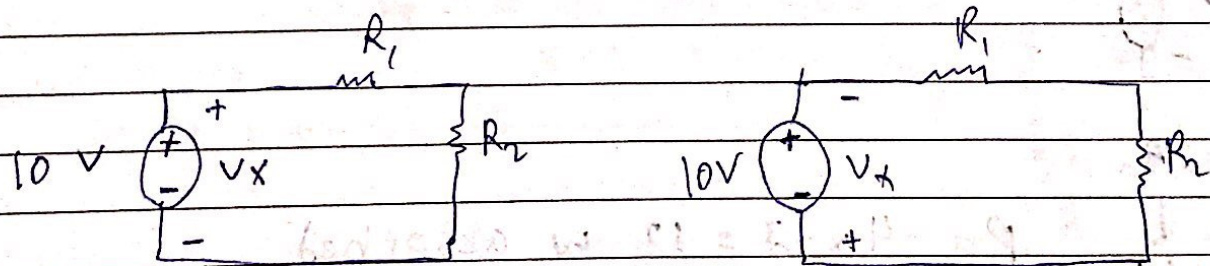

$$V_x = 10 \text{ V}$$

$$V_x = -10 \text{ V}$$

*Power and Energy :-

$P, p, P(t) \rightarrow$ watt (W)

$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} \quad P = v i$$


$$W = \int_{t_0}^{t_1} p \cdot dt$$

$$P(t) = v(t) \cdot i(t)$$

instantaneous Power


Absorbed or generated power

Passive Sign ~~Convention~~ convention

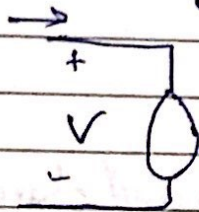


$$P = i \cdot v \text{ watt absorbed}$$

Ex $I = 3A$

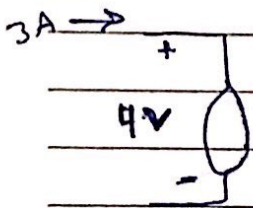


$$P = 4 \times 3 = 12 \text{ w absorbed}$$

$I = -3A$

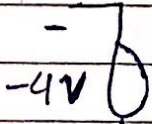

$$P = -4 \times -3 = 12 \text{ w absorbed}$$

$I = -3A$

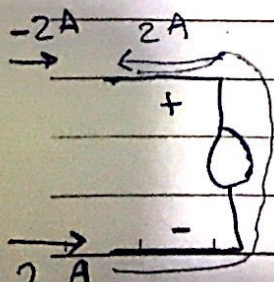

$$P = 5 \times -2 = -10 \text{ w absorbed} \\ = 10 \text{ w generated}$$

Total absorbed = Total generation

energy (work)

$W, w, w(t) \rightarrow$ joules, J, kWh, Ws


$$w = \int_{t_0}^{t_1} p \cdot dt \quad w = p(t_1 - t_0)$$

Circuit Elements


1) Voltage Sources

a) independent voltage sources

(+, -) و قبة (i, v)

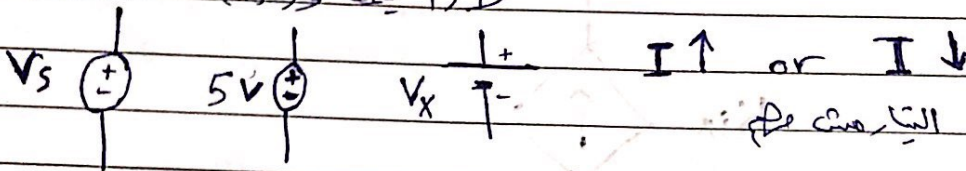

b) dependant voltage source

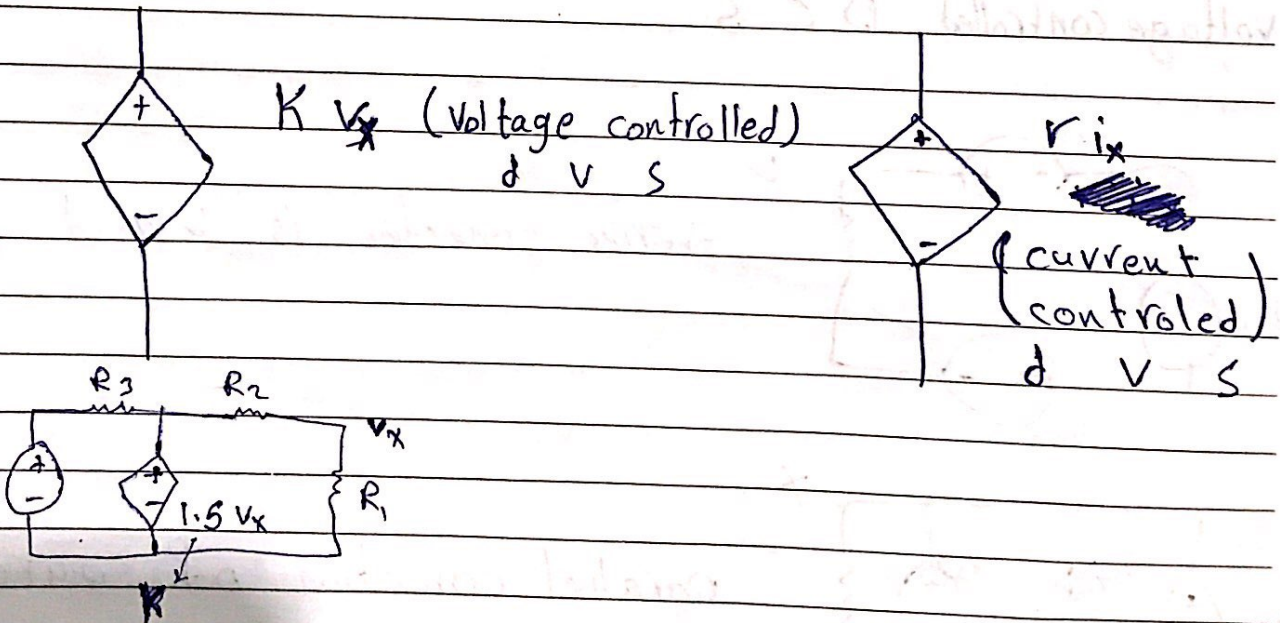

$V_x \rightarrow$ موجودة اي مكان بالدائرة


2) Current source

a) independent current sources :-




نقطة الجهد لا يهم

b) Dependent current source :-

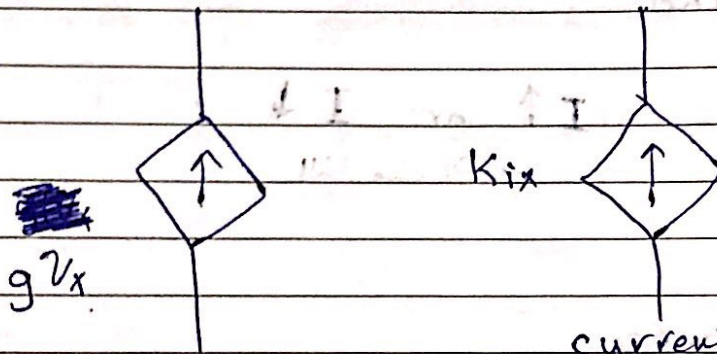


current controlled D.C.S


voltage controlled D.C.S

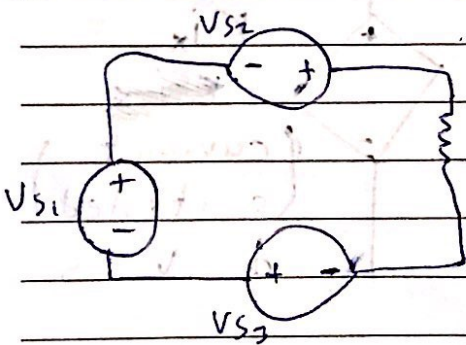


series connection is valid

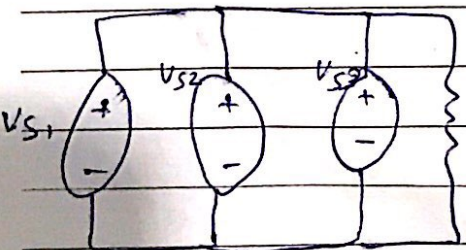

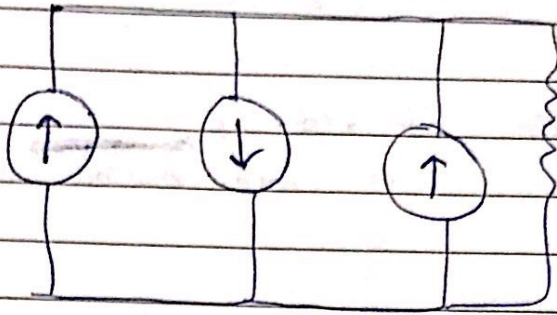parallel connection of sources is invalid




current sources in parallel is valid

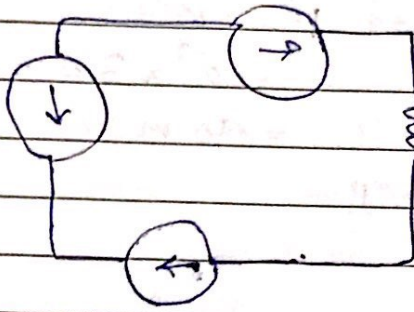


current sources in series is invalid

CH2:

* Ohm's Law :-

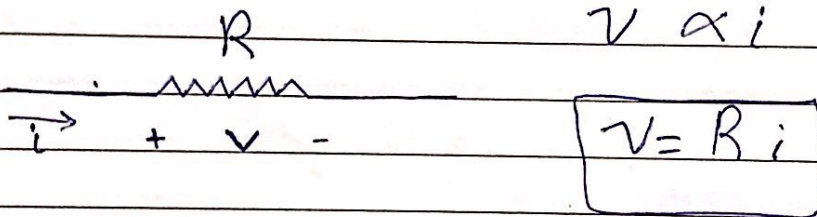

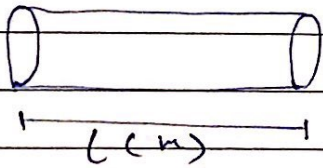A: cross sectional area (m^2) R: resistance of the conductor (Ω)



ρ : resistivity ($\Omega \cdot m$)


$$R = \frac{\rho L}{A} \rightarrow R = \frac{L}{\sigma A} \quad \left(\frac{1}{\sigma} = \rho \right)$$

$$P = iV = i^2 R = \frac{V^2}{R}$$

The Conductance (G) $\left(\frac{1}{\Omega} = \text{siemens} = \Omega^{-1} \right)$

$$G = \frac{1}{R} = \frac{i}{V} \quad (\text{Siemens } S) \rightarrow (\text{mhos } \mu)$$

practice problem 2.2

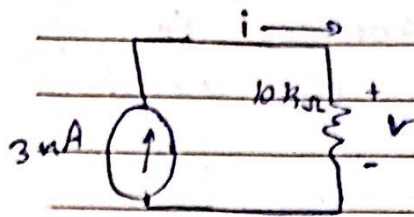

calculate v, G, P
absorbed by $10k\Omega$

Solu.


$$V = iR$$
$$= 3 \times 10^{-3} \times 10 \times 10^3$$
$$= 30$$

$$G = \frac{1}{R}$$
$$= \frac{1}{10 \times 10^3}$$
$$= 10^{-4} \text{ S} = 100 \mu\text{S}$$

$$P = iV$$
$$= 3 \times 10^{-3} \times 30$$
$$= 90 \text{ mW}$$

CHD

Nodes, Branches, paths and loops

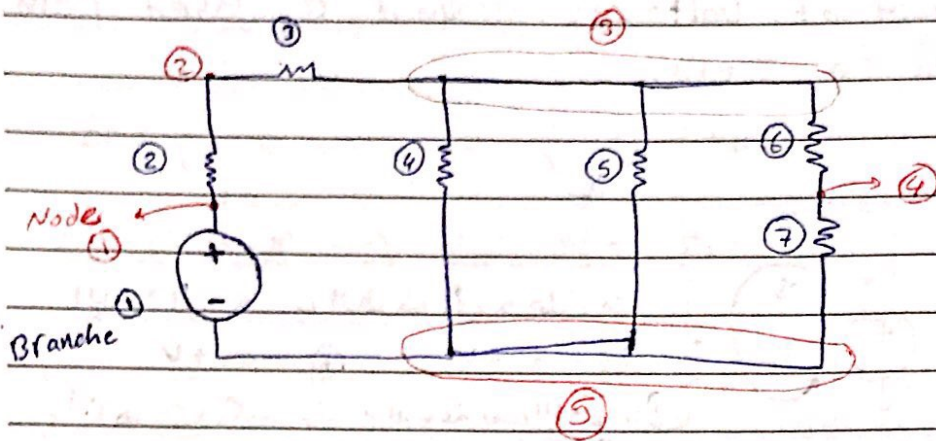


path → أي نقطة أخرى

loop → closed path

Handwritten signature

* Kirchhoff's current Law (KCL) :-

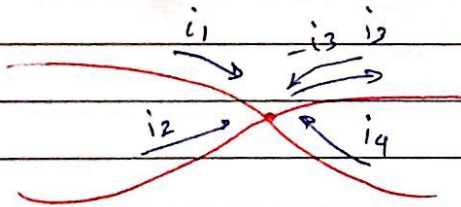
the algebraic sum of current entering a node is equal 0



$$i_1 + i_2 - i_3 + i_4 = 0$$

$$i_1 + i_2 + i_4 = i_3$$

التيار الداخل = التيار الخارج

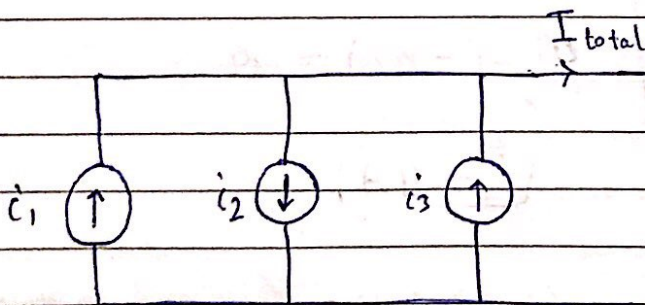


$$i_1 - i_2 + i_3 - I_T = 0$$


$$I_T = i_1 + i_3 - i_2$$

Kirchhoff's Voltage Law (KVL) :-

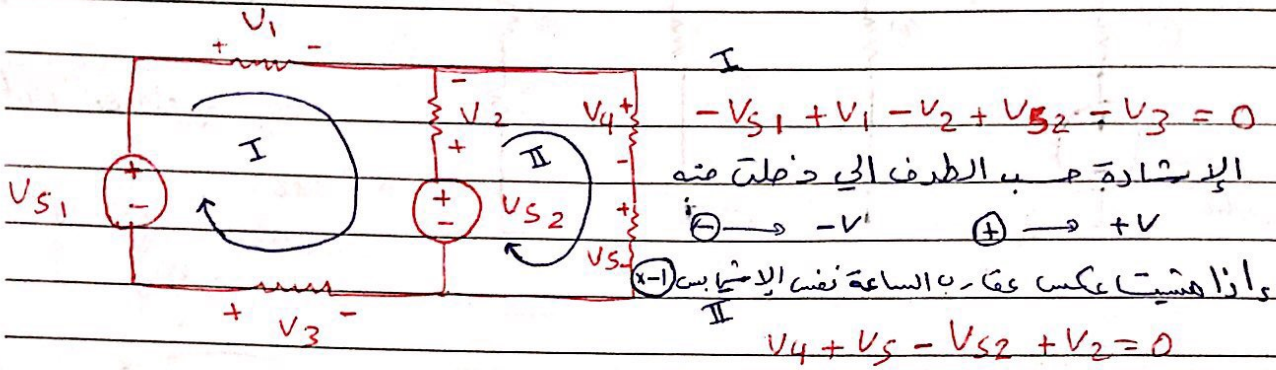The algebraic sum of voltages around a closed path (loop) is equal to zero.



Practice Problem 2.5 page 41 :-

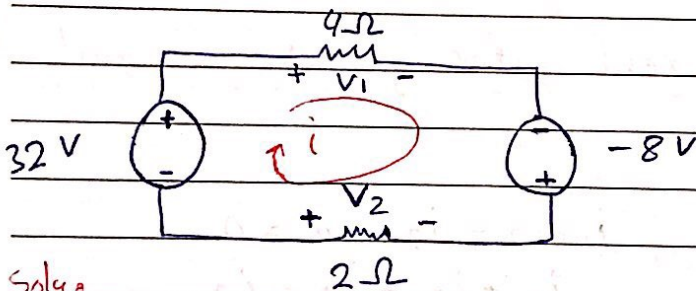

Find V_1 and V_2 ?

Soln:

apply KVL

$$-32 + V_1 - (-8) - V_2 = 0$$

$$V_1 - V_2 = 24 \quad \text{--- (1)}$$

by ohms law

$$V_1 = 4i$$

$$V_2 = -2i$$

$$4i - (-2i) = 24$$


$$6i = 24$$

$$i = 4A$$

$$V_1 = 4 \times 4 = 16V$$

$$V_2 = -2 \times 4 = -8V$$

Practice 2.6 :-

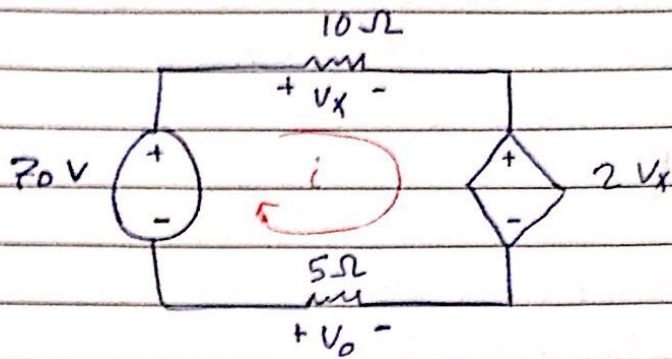

Find V_x and V_o ?

Solve

by KVL

by ohm's Law

$$-70 + V_x + 2V_x - V_o = 0$$

$$V_x = 10i \quad V_o = -5i$$

$$3V_x - V_o = 70 \quad \text{--- (1)}$$

$$3(10i) - (-5i) = 70$$


$$35i = 70 \rightarrow \boxed{i = 2A}$$

$$\therefore V_x = 20V$$

$$V_o = -10V$$

Practice 2.8 Page 43

Observe KVL

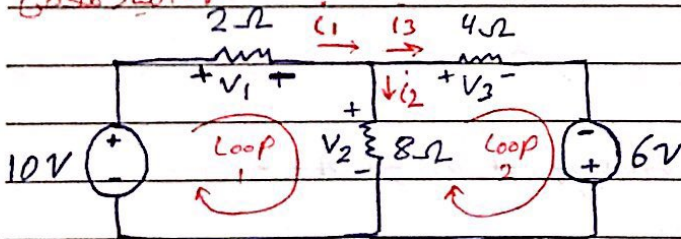

Find $V_1, V_2, V_3, i_1, i_2, i_3$?

by KCL

$$i_1 = i_2 + i_3 \quad \text{--- (1)}$$

Apply KVL for Loop 1

$$V_1 = 2i_1$$

$$-10 + V_1 + V_2 = 0 \quad \text{--- (2)}$$

$$V_2 = 8i_2$$

Apply KVL for Loop 2

$$V_3 = 4i_3$$

$$-6 - V_2 + V_3 = 0 \quad \text{--- (3)}$$

From ②

$$-10 + 2i_1 + 8i_2 = 0$$

$$2i_1 + 8i_2 = 10$$

$$2(i_2 + i_3) + 8i_2 = 10$$

$$5i_2 + i_3 = 5 \dots \text{--- (A)}$$

From ③

$$-6 - 8i_2 + 4i_3 = 0$$

$$-8i_2 + 4i_3 = 6 \dots \text{--- (B)}$$

A+B

$$-8i_2 + 4i_3 = 6$$

$$+ (5i_2 + i_3 = 5) \times -4$$

$$-28i_2 = -14 \rightarrow i_2 = \frac{-14}{-28}$$

$$i_2 = 0.5 \text{ A}$$

$$5(0.5) + i_3 = 5$$

$$i_3 = 2.5 \text{ A}$$

$$i_1 = 3 \text{ A}$$

$$V_1 = 2 \times 3 = 6 \text{ V}$$

$$V_2 = 8(0.5) = 4 \text{ V}$$

$$V_3 = 4(2.5) = 10 \text{ V}$$

∴ $\sum P_{\text{gen}} = \sum P_{\text{abs}}$

$$P_{10\text{V}} = 10 \times 3 = 30 \text{ W generated}$$

$$P_{2\Omega} = 3^2 \times 2 = 18 \text{ W absorbed}$$



$$P_{6\text{V}} = 6(2.5) = 15 \text{ W "}$$

$$P_{8\Omega} = (0.5)^2 \times 8 = 2 \text{ W "}$$

$$P_{4\Omega} = (2.5)^2 \times 4 = 25 \text{ W "}$$

generated = absorbed ∴ ✓

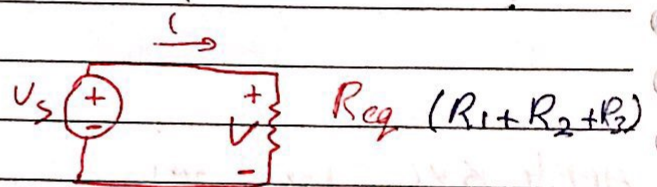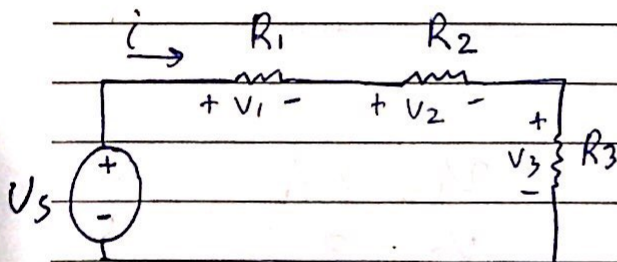2.5 Series resistors and voltage division :-



$$-V_s + V_1 + V_2 + V_3 = 0$$


$$V_s = iR_1 + iR_2 + iR_3$$

$$V_s = i(R_1 + R_2 + R_3)$$

$$-V_s + V = 0$$

$$V_s = iR_{eq}$$
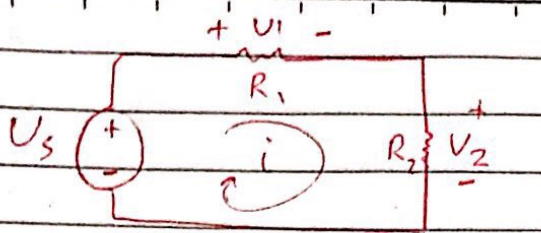
$$R_{eq} = R_1 + R_2 + \dots + R_n \text{ (series resistors)}$$



$$i = \frac{U_s}{R_1 + R_2}$$

$$U_1 = \frac{R_1}{R_1 + R_2} \times U_s$$

$$U_2 = \frac{R_2}{R_1 + R_2} \times U_s$$


} Voltage Division

$$U_1 = i R_1$$

$$U_2 = i R_2 \rightarrow U_s = U_1 + U_2$$

$$U_s = i (R_1 + R_2)$$

Ex

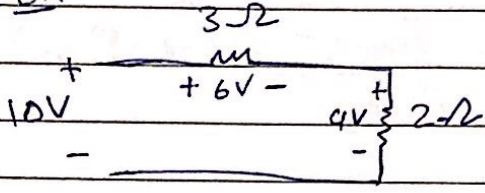


$$\frac{3}{3+2} \times 10 = 6V$$

$$\frac{2}{3+2} \times 10 = 4V$$

} 10V ✓

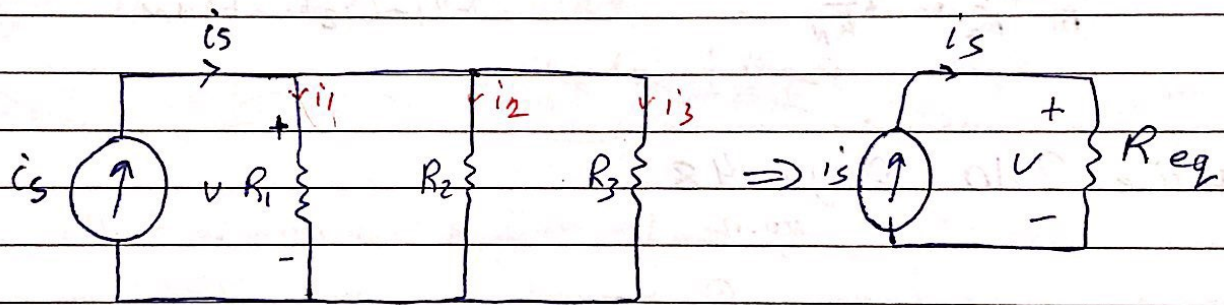2.6 parallel Resistors and current Division



by KCL:

$$i_s = i_1 + i_2 + i_3$$

$$i_s = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$i_s = \frac{V}{R_{eq}}$$

$$i_s = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\frac{1}{R_{eq}} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

resistor in parallel

$$I_1 = \frac{V}{R_1} \quad V = I_1 R_1 = I_2 R_2$$

$$I_2 = \frac{V}{R_2}$$

$$V = I_s \left(\frac{R_1 R_2}{R_1 + R_2} \right) \rightarrow I_1 R_1 = I_s \left(\frac{R_1 R_2}{R_1 + R_2} \right), I_2 R_2 = I_s \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$



$$I_1 = \frac{R_2}{R_1 + R_2} I_s$$


$$I_2 = \frac{R_1}{R_1 + R_2} I_s$$

current Division rule :-

$$I_k = \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} \cdot I_s \quad \text{or} \quad I_k = \frac{G_k}{G_1 + G_2 + \dots + G_N} \cdot I_s$$

بصورتی (I₁, I₂) ایفون

practice 2.10 page 48

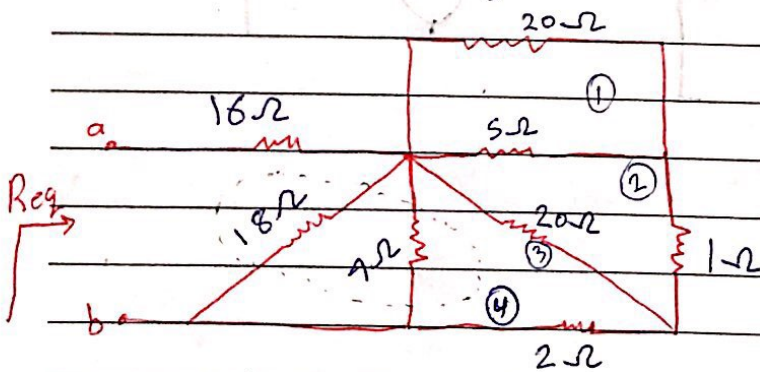

$$\textcircled{1} \frac{20 \times 5}{25} = 4 \Omega \quad \textcircled{2} \frac{1}{5} + \frac{1}{20} = \frac{1}{4} \text{ for parallel} \quad \frac{1}{R_{eq}} = \frac{1}{18} + \frac{1}{4} + \frac{1}{6}$$

$$\textcircled{2} 4 + 1 = 5 \Omega \quad \textcircled{4} 4 + 2 = 6 \Omega \quad \frac{1}{R_{eq}} = \frac{1+2+3}{18} = \frac{6}{18} = \frac{1}{3}$$


$$R_{eq} = 3 \Omega$$

$$R_{eq} = 3 + 16 = 19 \Omega$$

Five Apple

* Wye - Delta Transformation :-

T, π , Y

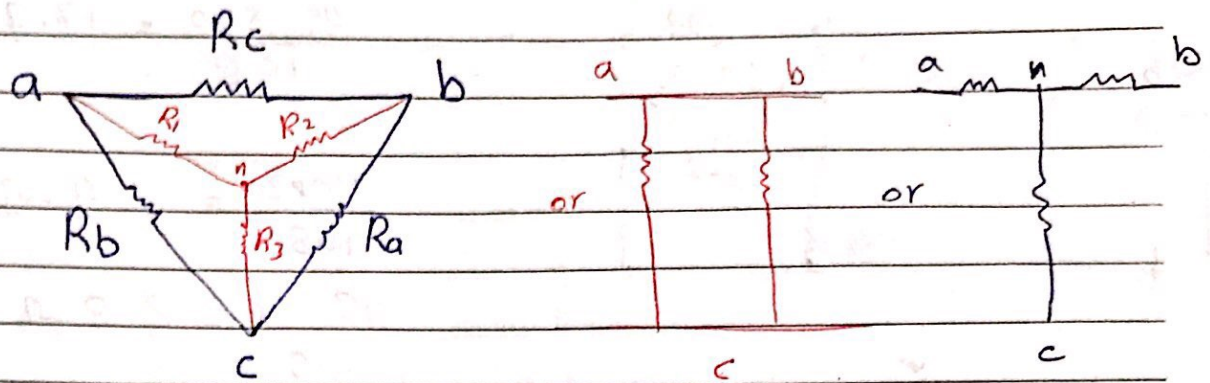

Delta to wye conversion:


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}, \quad R_2 = \frac{R_c R_a}{R_a + R_b + R_c}, \quad R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$



wye to Delta conversion:-

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}, \quad R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}, \quad R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


دائماً بالقرابة بالقاعدة البعيدة إلى منقوساتة بال Node

practice 2.15 page 57

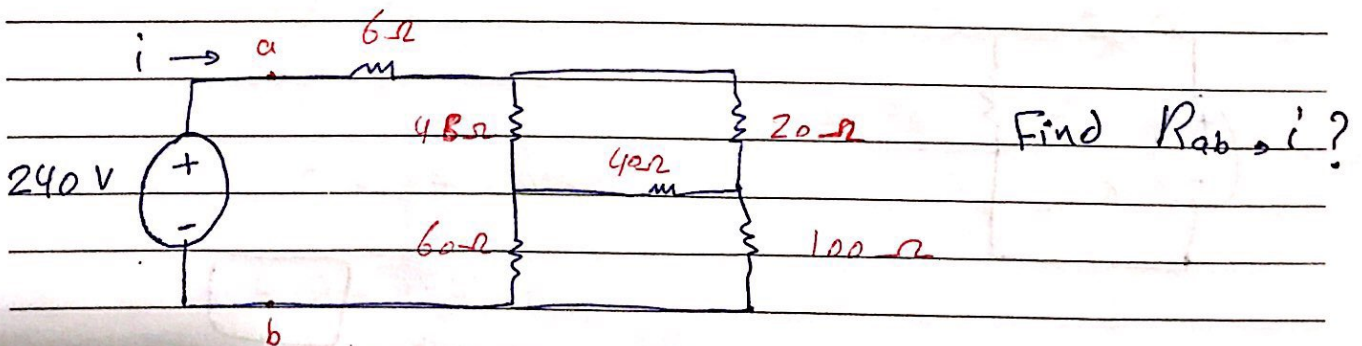

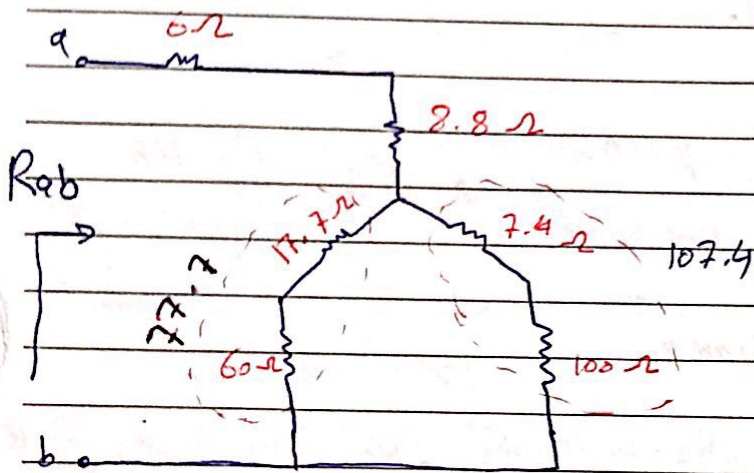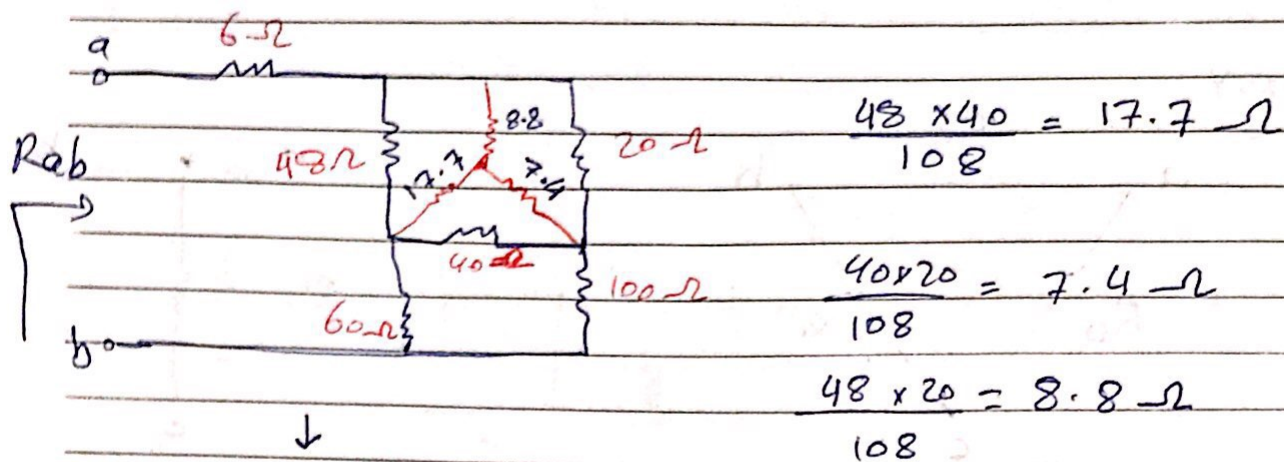
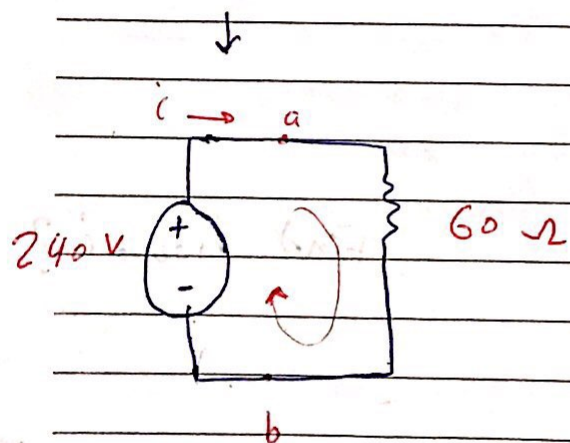
$$R_{ab} = \left(\frac{77.7 \times 107.4}{77.7 + 107.4} \right) + 8.8 + 6 = 60 \Omega$$





$$-240 + 60i = 0$$

$$i = \frac{240}{60} = 4 \text{ A}$$

Chapter 3 "Methodes of analysis" :-

* Nodal Analysis

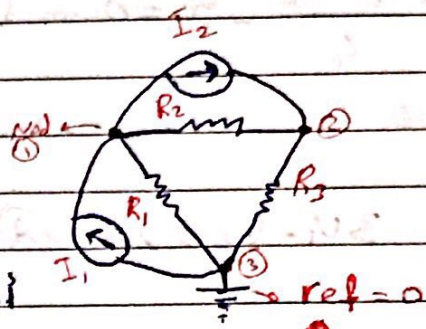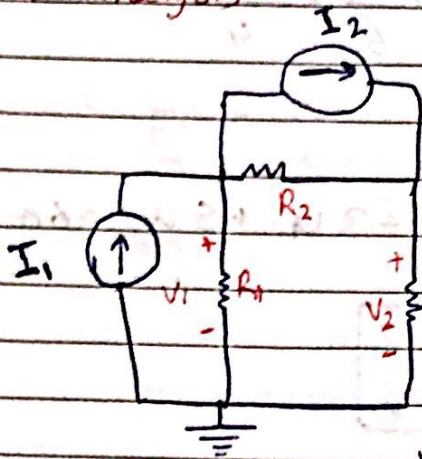

أول خطوة ببساطة
الأثرية لتقليل عدد

و ref=0 (الأرض)

و باقى ال Node بالترتيب

Node (1) → V1

Node (2) → V2

Node (3) → ref = 0

by Kcl at Node 1 :-



$$-I_1 + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2} + I_2 = 0 \quad \boxed{1}$$

التيار اللى دا داخلى على ال Node (-)
" خارج عن " (+)

by Kcl at Node 2 :-

$$\frac{V_2}{R_3} + \frac{V_2 - V_1}{R_2} - I_2 = 0 \quad \boxed{2}$$

Ex:-

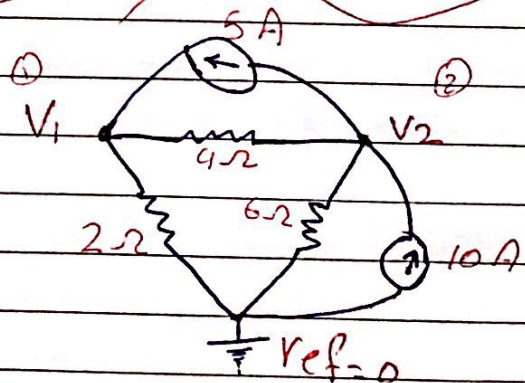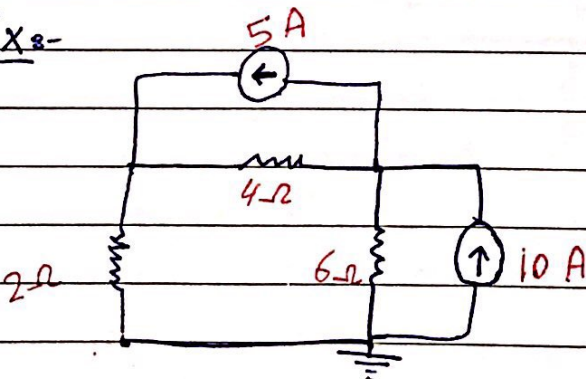

و إعادة الرسم لتسهيل العمل
خطوة ضرورية

Find V1, V2 :-

Kcl at Node 1 :-

$$\frac{V_1}{2} + \frac{V_1 - V_2}{4} - 5 = 0 \quad \text{--- (1)}$$

Kcl at Node 2 :-

$$-10 + \frac{V_2}{6} + \frac{V_2 - V_1}{4} + 5 = 0 \quad \text{--- (2)}$$

$$\text{(1)} \times 4 \Rightarrow 2V_1 + V_1 - V_2 - 20 = 0$$

$$\text{(2)} \times 12 \Rightarrow 2V_2 + 3V_2 - 3V_1 = 60$$


$$3V_1 - V_2 = 20 \quad \text{--- (A)}$$

$$-3V_1 + 5V_2 = 60 \quad \text{--- (B)}$$

(A+B)


$$4V_2 = 80 \Rightarrow V_2 = 20 \text{ V}$$
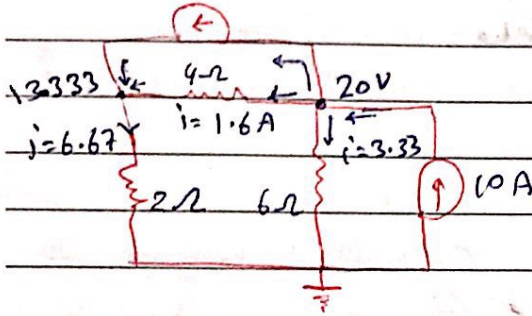
$$3V_1 = 20 + 20 \Rightarrow V_1 = 13.333 \text{ V}$$



لدينا التيارات الداخل يساري الخارج وينتقل في اتجاه اليساري
 معادلة من $i = \frac{V}{R}$
 وبهذه الطريقة نطلب أي شيء
 Power energy

Nodals with Voltage sources :-

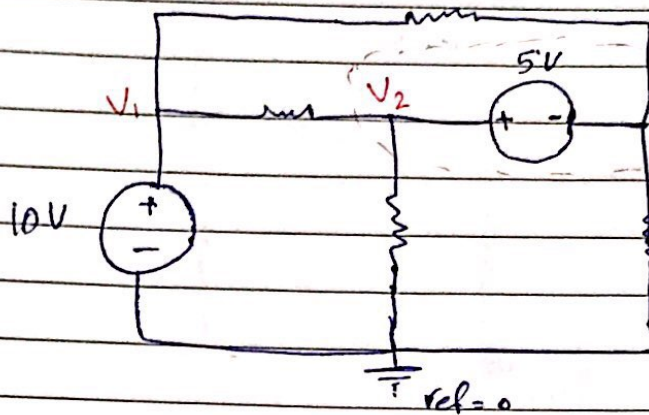

لو قمنا بتأدية معادلات كيرشوف
بالضرب

Case 1 → Voltage source between ref and nonref Node (V_1)


then $V_1 = 10V$ --- (1)

Case 2 → Voltage source between two nonref node (V_2, V_3)

Super node --- (2)
↓ KCL معادلات


$V_2 - V_3 = 5$ --- (3)

Ex * practice Problem 3.3 Page 88

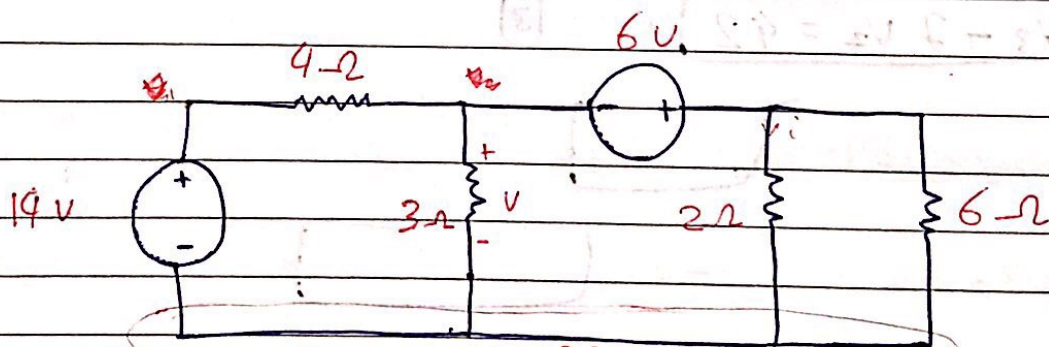

ref
معادلات كيرشوف مع (KCL)

Find v and i :-

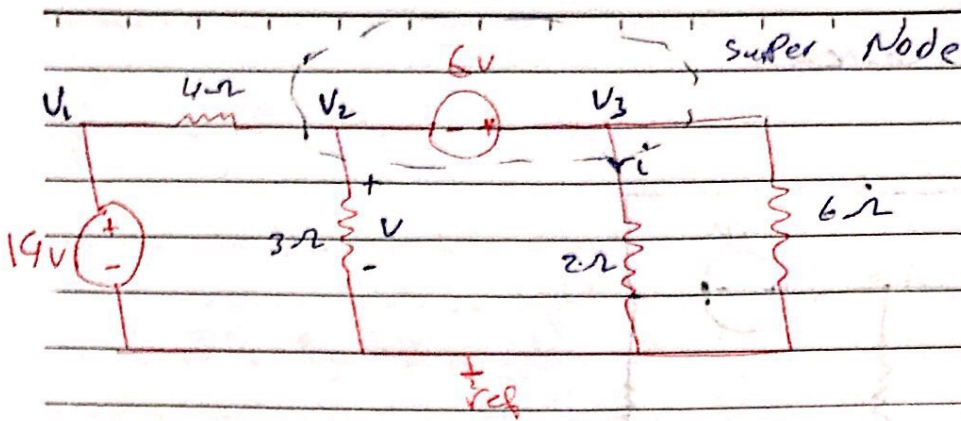

$$V_1 = 14 \text{ V} \quad \text{--- (1)}$$

Kcl on the Super Node

$$\left(\frac{V_2 - V_1}{4} + \frac{V_2}{3} + \frac{V_3}{2} + \frac{V_3}{6} = 0 \right) \times 12$$

$$3V_2 - 3V_1 + 4V_2 + 6V_3 + 2V_3 = 0$$

$$7V_2 - 3(14) + 8V_3 = 0$$

$$7V_2 + 8V_3 = 42 \quad \text{--- (2)}$$

$$(V_3 - V_2 = 6) \times 7$$


$$7V_3 - 7V_2 = 42 \quad \text{--- (3)}$$

$$(2+3) \quad 15V_3 = 84 \rightarrow V_3 = \frac{84}{15}$$

$$V_2 = V_3 - 6 = 5.6 - 6 = -0.4 \text{ V} = V_2$$

$$i = 2.8 \text{ A}$$

Ex: Practice 3.4

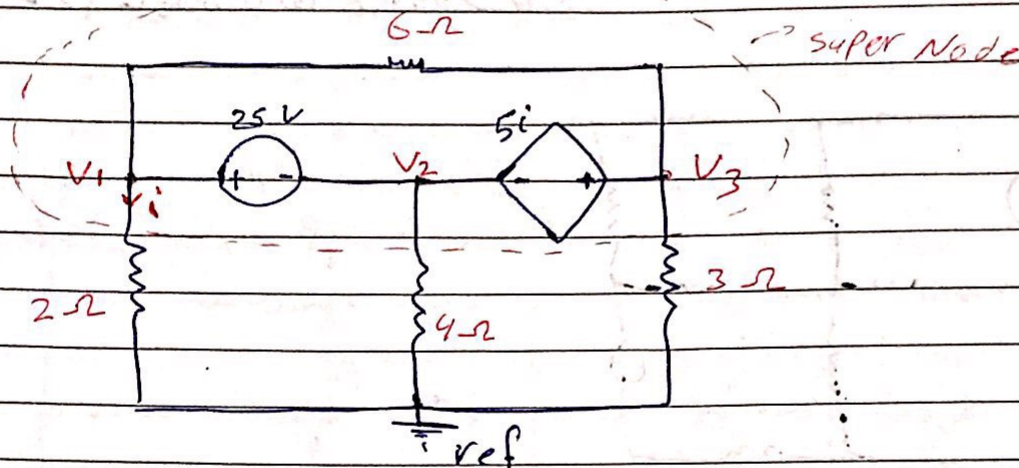

Req at the superNodes

$$\left(\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{3} = 0 \right) \cdot 12$$

$$6V_1 + 3V_2 + 4V_3 = 0 \quad \text{--- (1)}$$

$$V_1 - V_2 = 25 \quad \text{--- (2)}$$

$$V_3 - V_2 = 5i \rightarrow V_3 - V_2 = 5 \left(\frac{V_1}{2} \right)$$

$$\left(2.5V_1 + V_2 - V_3 = 0 \right) \cdot 4 \quad \text{+ (1)}$$

$$16V_1 + 7V_2 = 0$$

+

$$7(V_1 - V_2 = 25)$$

$$23V_1 = 175$$

$$V_1 = \frac{175}{23} \text{ V}$$


$$\Rightarrow \left. \begin{aligned} V_1 &= 7.609 \text{ V} \\ V_2 &= -17.39 \text{ V} \\ V_3 &= 1.63 \text{ V} \end{aligned} \right\}$$

بقدر اطلب
كل البتات
والتي هي

* Mech Analysis :-


"planar circuit"

لازم ما يكون في نفس المستوى

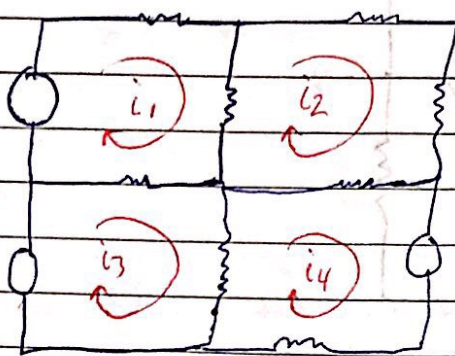

يؤخذ في الحسبان اتجاه التيار
و يطبق معادلة كيرشوف

Ex:

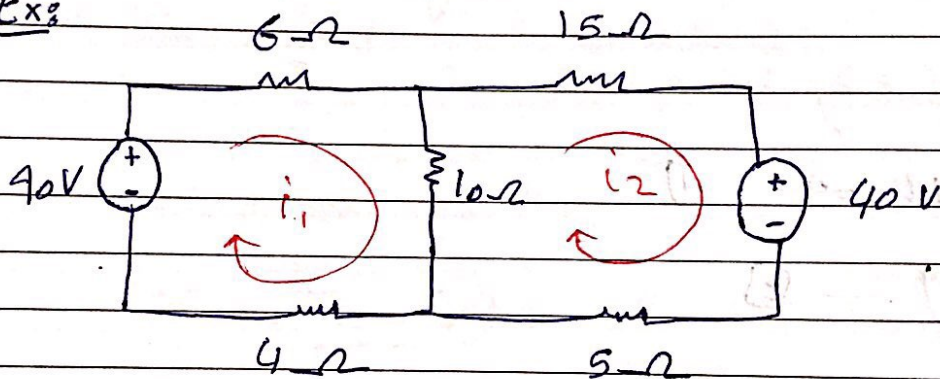

Find i_1 i_2 ?

Apply KVL for mesh 1 :-

$$-90 + 6i_1 + 10(i_1 - i_2) + 4i_1 = 0$$

$$20i_1 - 10i_2 = 90 \quad \text{--- [1]}$$

Apply KVL for Mesh 2 :-

$$40 + 5i_2 + 10(i_2 - i_1) + 15i_2 = 0$$

$$-10i_1 + 30i_2 = -40 \quad \text{--- [2]}$$


[2] x 2

$$i_2 = \frac{1}{5} = 200 \text{ mA}$$

$$i_1 = \frac{92}{20} = 4.6 \text{ A}$$

Power \leftarrow بعد من بعد يطبق أي شيء

Mesh with current source :-

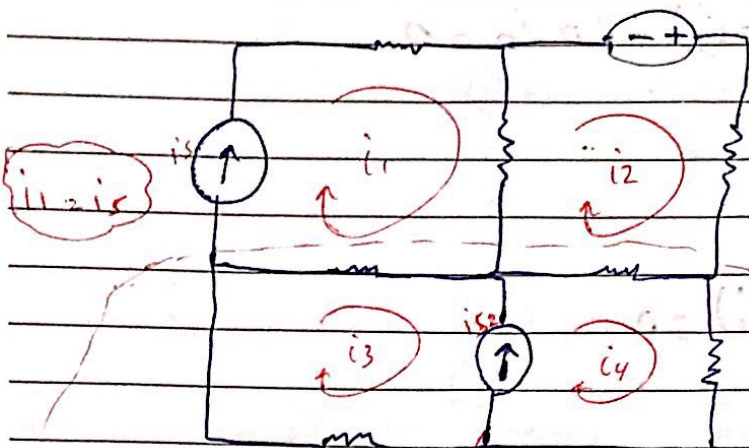

ياخذ (super mesh)

ونفس ال current source

ويعني موكل مقاومة ~~التي~~ والنا
اي بمرضيها بطلع معادلة بوجهولين


1 current source

ال معادلة الثانية بجمعها من ال current source نفس

~~$i_2 - i_3 = i_{s2}$~~

$$i_4 - i_3 = i_{s2}$$

Practice 3.7 Page 98

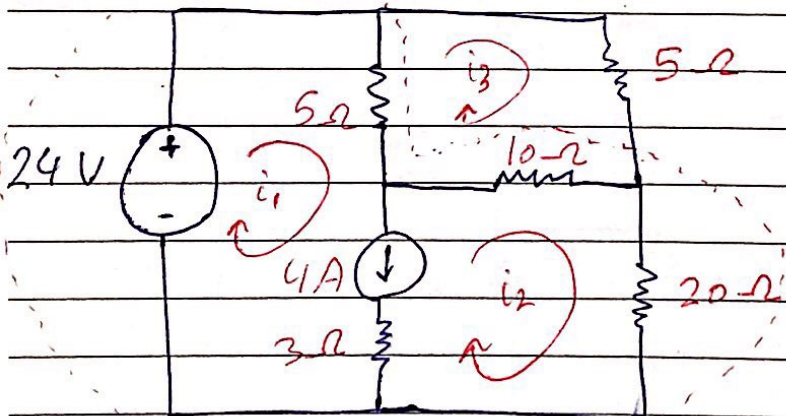

super mesh
(skip current source)

Find i_1, i_2, i_3 :- "البرجمات النهائية بالكتاب داخلية"

وصنع بطلع أي باشي بالدارة

KVL at the super meshes -

$$-24 + 5(i_1 - i_2) + 10(i_2 - i_3) + 20i_2 = 0$$

$$5i_1 + 30i_2 - 15i_3 = 24 \quad \text{--- (1)}$$

KVL at mesh 3 -

$$5i_3 + 10(i_3 - i_2) + 5(i_3 - i_1) = 0$$

$$-5i_1 - 10i_2 + 20i_3 = 0 \quad \text{--- (2)}$$

$$i_1 - i_2 = 4 \quad \text{--- (3) current source}$$

$$i_1 = 4.8 A \quad i_2 = 0.8 A \quad i_3 = 1.6 A \quad \text{وذلك المصادر}$$

CH 4: Linearity and superposition =

- superposition is applied if the circuit is linear

- The circuit is linear if all elements in the circuit are linear.

$$R_2 \quad V = Ri \quad \text{linear}$$

Voltage and current sources:

all independent sources are linear (Voltage, current)

- Dependent sources =



$V_s = k V_x \rightarrow$ linear dependent voltage source

$i_s = k \sqrt{i_x} \rightarrow$ non linear

$V_s = k i_x i_z \rightarrow$ non linear

$V_s = k_1 V_{x1} + k_2 V_{x2} \rightarrow$ linear

$V_s = k V_x^2 \rightarrow$ non linear

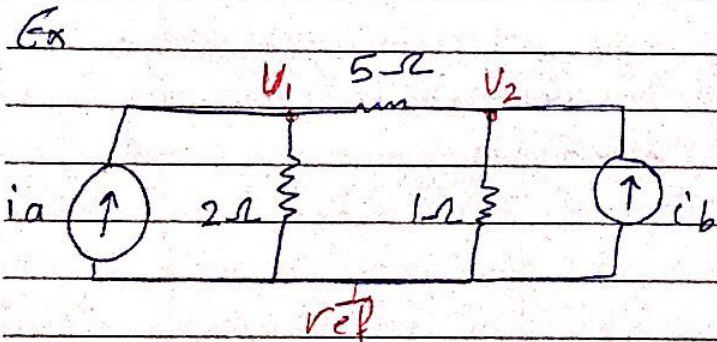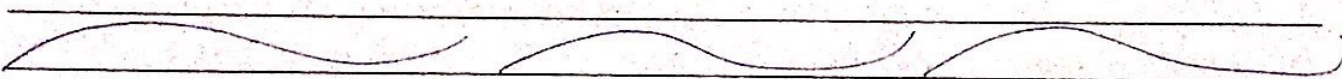

by Use Nodal Analysis

Kcl at Node 1


$$-i_a + \frac{V_1}{2} + \frac{V_1 - V_2}{5} = 0$$

$$0.7 V_1 - 0.2 V_2 = i_a \quad \text{--- (1)}$$

by Kcl at Node 2

$$-i_b + \frac{V_2}{1} + \frac{V_2 - V_1}{5} = 0 \rightarrow -0.2 V_1 + 1.2 V_2 = i_b \quad \text{--- (2)}$$

(Superposition) الطريقة الأخرى

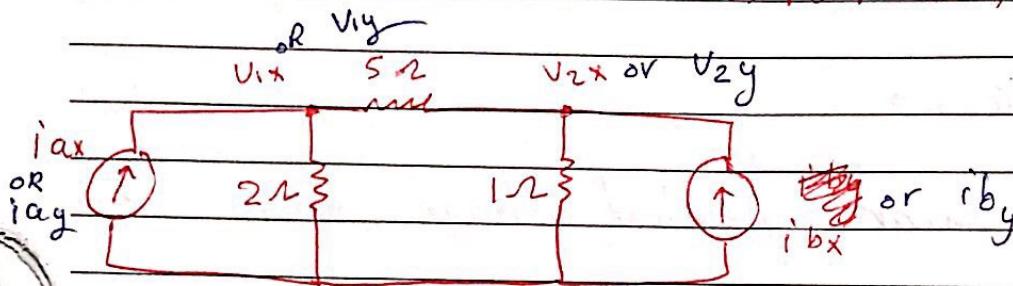

~~Experiment (x)~~

Experiment (x)

$$0.7 V_{1x} - 0.2 V_{2x} = i_{ax}$$

$$-0.2 V_{1x} + 1.2 V_{2x} = i_{bx}$$

Experiment (y)

Exp x
+
Exp y

$$0.7 V_{1y} - 0.2 V_{2y} = i_{ay}$$

$$-0.2 V_{1y} + 1.2 V_{2y} = i_{by}$$


$$0.7 (V_{1x} + V_{1y}) - 0.2 (V_{2x} + V_{2y}) = (i_{ax} + i_{ay})$$

$$\rightarrow 0.7 V_1 - 0.2 V_2 = i_a$$

$$-0.2 (V_{1x} + V_{1y}) + 1.2 (V_{2x} + V_{2y}) = (i_{bx} + i_{by})$$


$$\rightarrow -0.2 V_1 + 1.2 V_2 = i_b$$

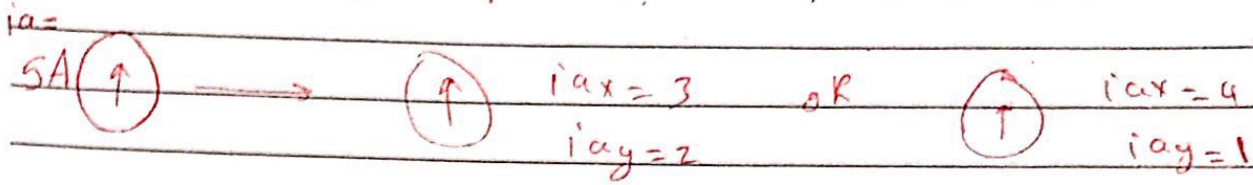ال (Super position) عبارة عن تجميع النتائج التي نحصل عليها



الجميع يعطيني نفس النتيجة

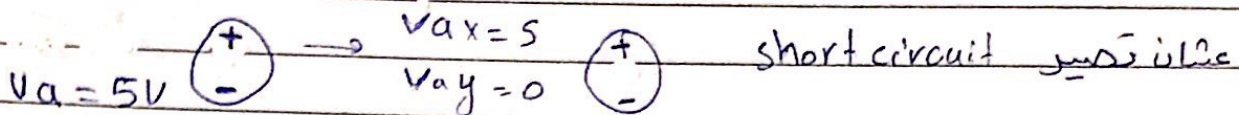
أو أن هناك طريقة أفضل جزء وأعطى جزء كل القيمة





Short circuit \rightarrow killing the source

Kill always to dependant

Ex

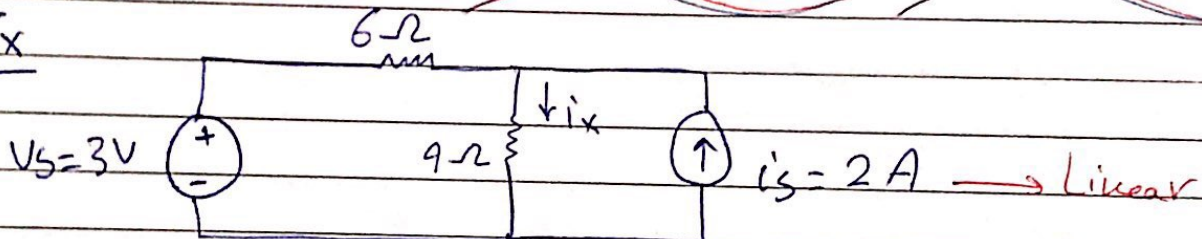

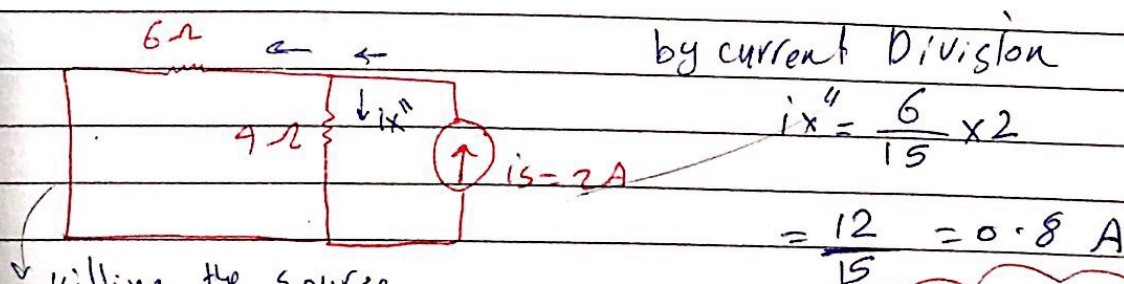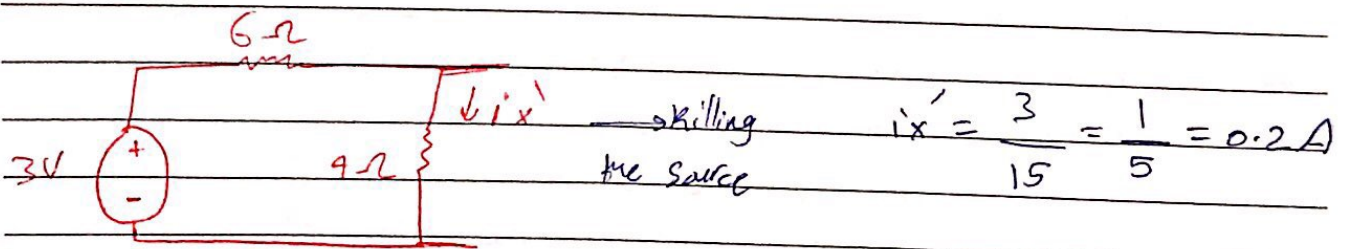use (Super Position) to find i_x in the circuit?




$i_x = i_x' + i_x'' = 1A$

open cir \rightarrow current source \rightarrow short cir \rightarrow Kill Voltage source


Five Apple

Practice problem 4.4 Page 132

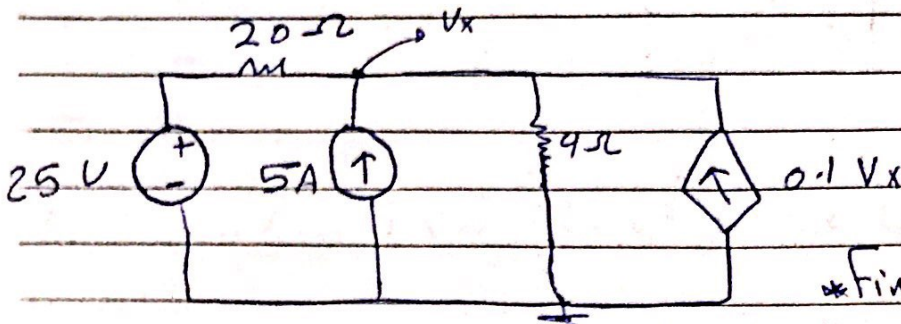

*Find V_x using superposition

step 1

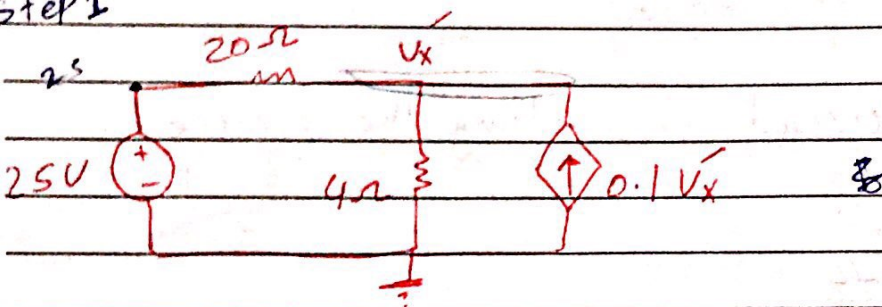


by Nodal

$$\frac{V_x - 25}{20} + \frac{V_x}{4} - 0.1V_x = 0 \quad \times 20$$

هاد الجزء من ال V_x

$$V_x - 25 + 5V_x - 2V_x = 0 \rightarrow 4V_x = 25 \rightarrow V_x = 6.25V$$

step 2

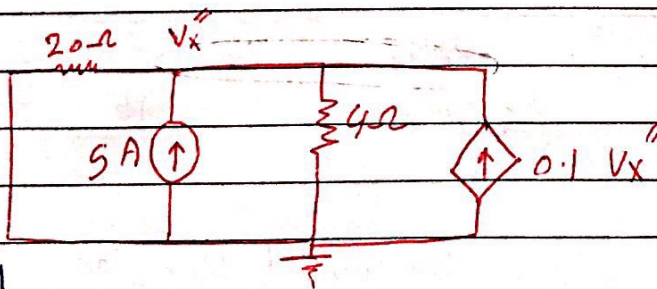

by Nodal

$$\frac{V_x'' - 0}{20} + \frac{V_x''}{4} - 0.1V_x'' = 0 \quad \times 20$$


هاد الجزء الثاني من ال V_x

$$V_x'' - 0 + 5V_x'' - 2V_x'' = 0 \rightarrow V_x'' = 25V$$


$$\therefore V_x = V_x' + V_x'' = 6.25 + 25 = 31.25V$$

لو حلينا نودال من اول بطوع نفس الجواب


Practice problem 4.5

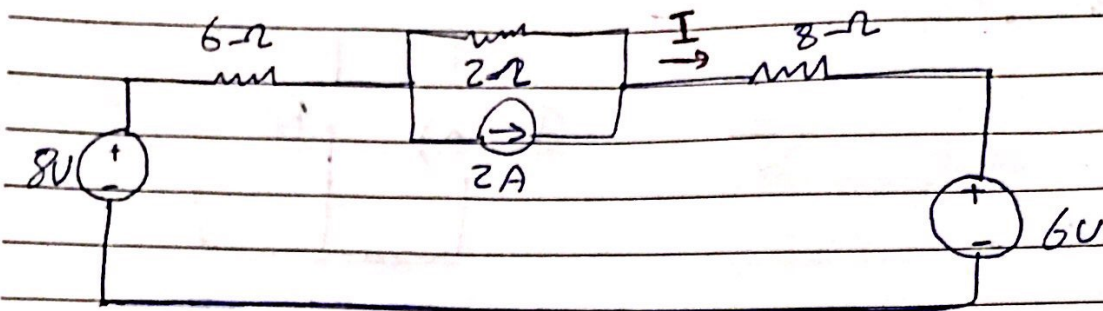


Find "I" using super position :-

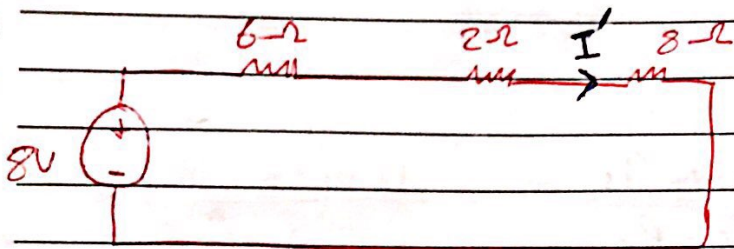

$$I' = \frac{8}{8+2+6} = 0.5 \text{ A}$$

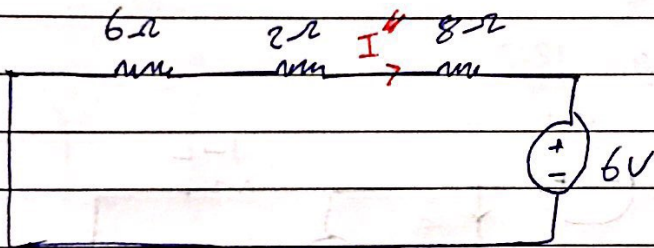
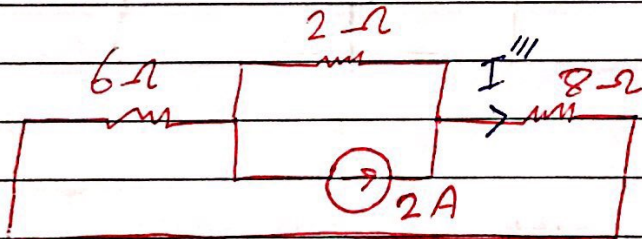
$$I'' = \frac{-6}{16} = -0.375 \text{ A}$$




by current Division :-

$$I''' = \frac{2}{16} \times 2 = 0.25 \text{ A}$$

$$I = I' + I'' + I''' = 0.5 - 0.375 + 0.25 = 0.375 \text{ A} = \boxed{375 \text{ mA}}$$

* Source transformation:-

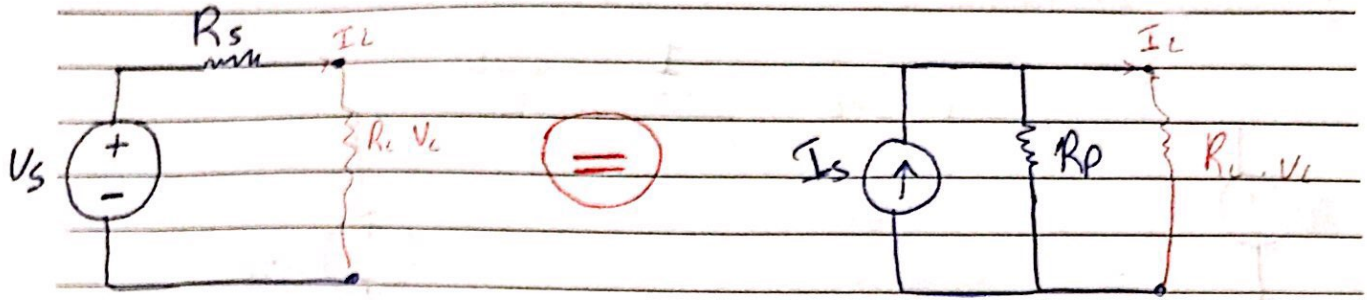

بقدر أعود voltage source ومقاومة على التوالي
 ب current source ومقاومة على التوازي


$$V_L = \frac{R_L}{R_L + R_s} V_s$$

$$V_s = R_p I_s$$

$$R_p = R_s$$


$$V_L = \left(\frac{R_L \cdot R_p}{R_p + R_L} \right) I_s$$



Practice Problem 4.6 Page 135

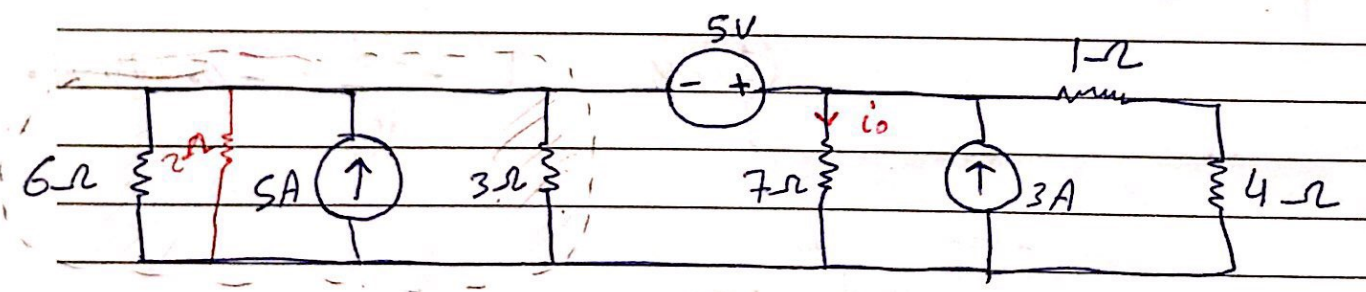

Find i_o :-

source transformation in current source

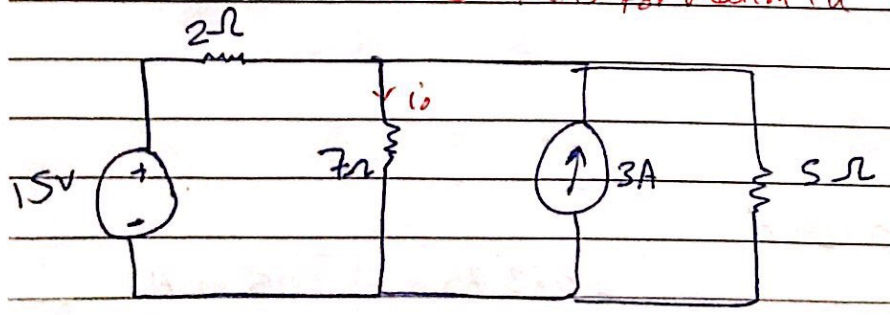

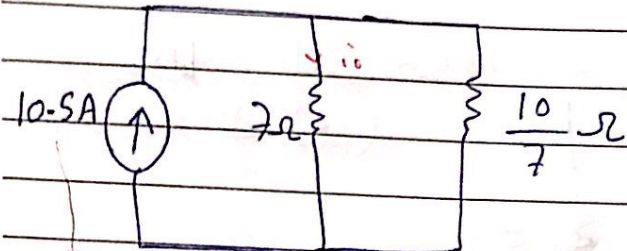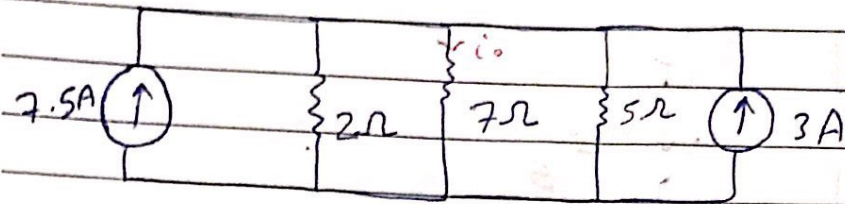

by current division


$$i_o = \left(\frac{\frac{10}{7}}{\frac{10}{7} + 7} \right) \times 10.5$$

$$= \boxed{1.78 \text{ A}}$$

حساب التيار
تقسيم التيار


Notes:


بقي أحد ال dependent source

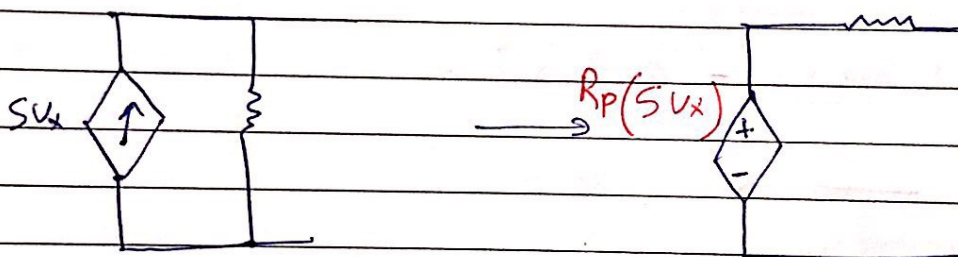


ممنوع أعيد أو أحد ال Branch المتبقي بال (u_x)

practice problem 4.7

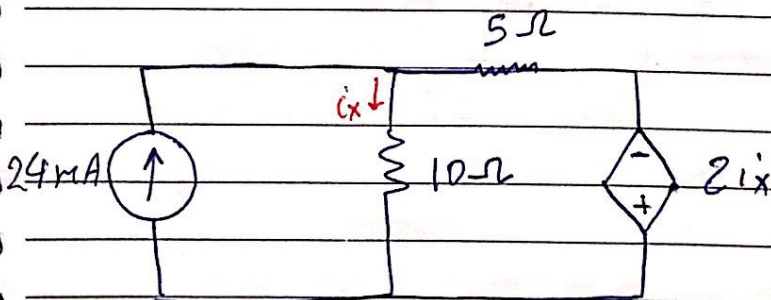

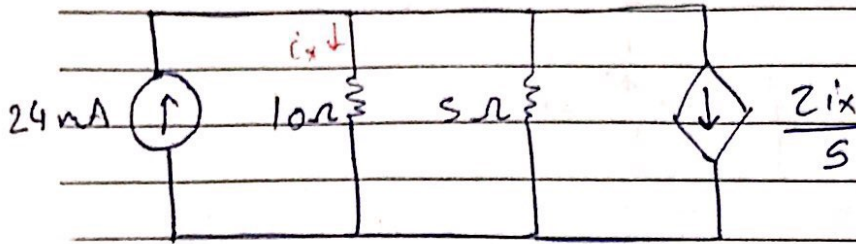

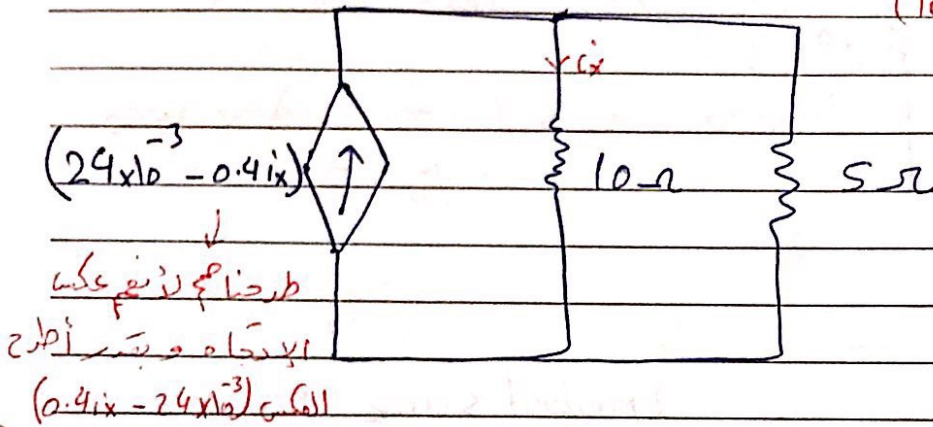ما اشتغلنا على مقاومة (10Ω)
نؤنق عليها ال (ix)





$$i_x = \left(\frac{5}{15} \right) (24 \times 10^{-3} - 0.4 i_x)$$

$$i_x = 8 \times 10^{-3} - \frac{0.4}{3} i_x$$

$$\frac{34}{30} i_x = 8 \times 10^{-3}$$

$$i_x = 8 \times 10^{-3} \times \frac{30}{34} = \boxed{7.06 \text{ mA}}$$

* Thevenin and Norton Equivalents *

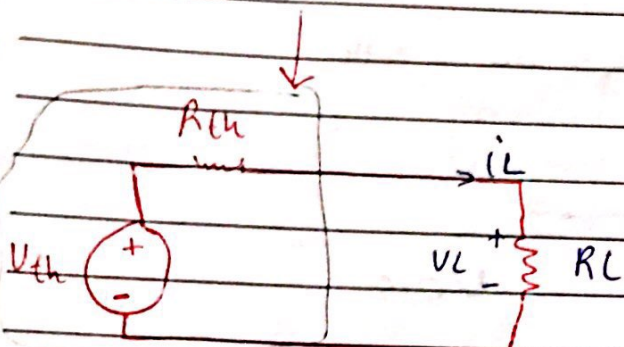
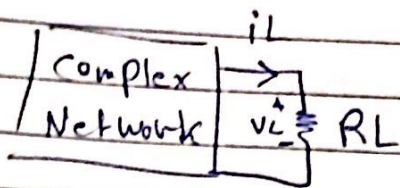



Case 1: all independent sources =

$R_{th} \rightarrow$ kill all sources and find $R_{eq} = R_{th}$



$V_{th} = V_{open\ circuit}$ ~~kill~~ $V_{th} = V_{o.c}$

Ex: practice problem 4.8 page 140

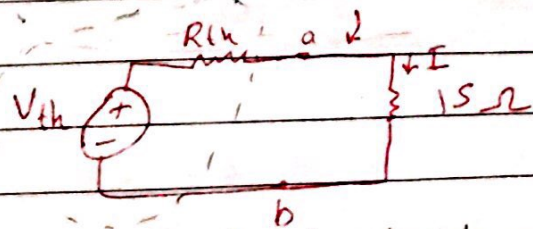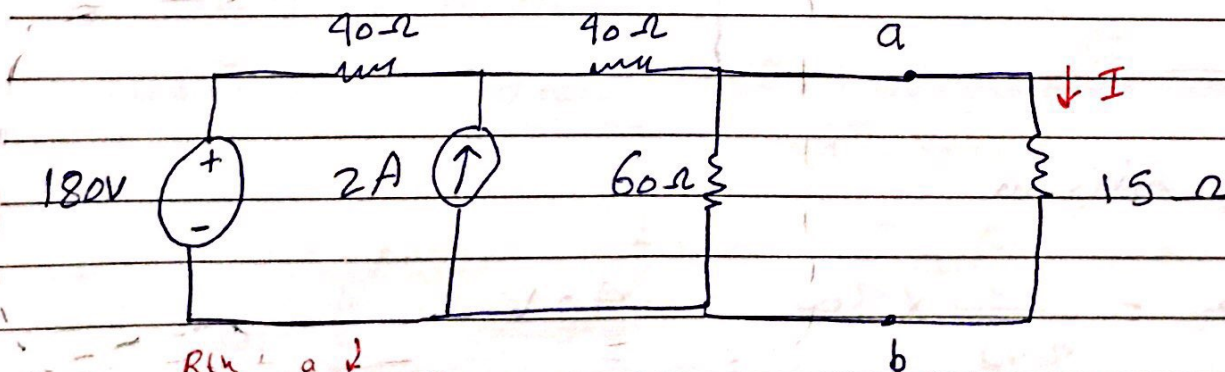


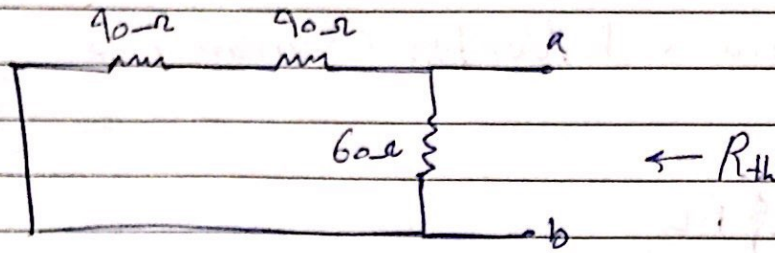
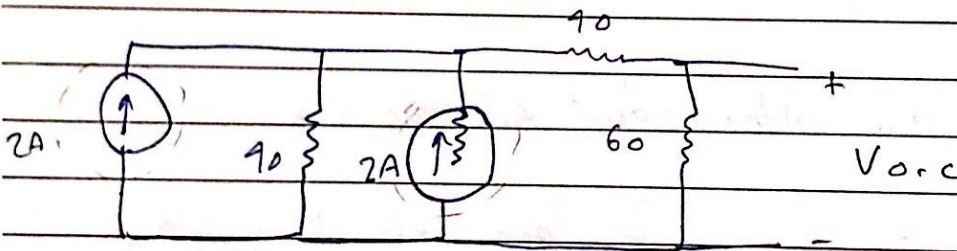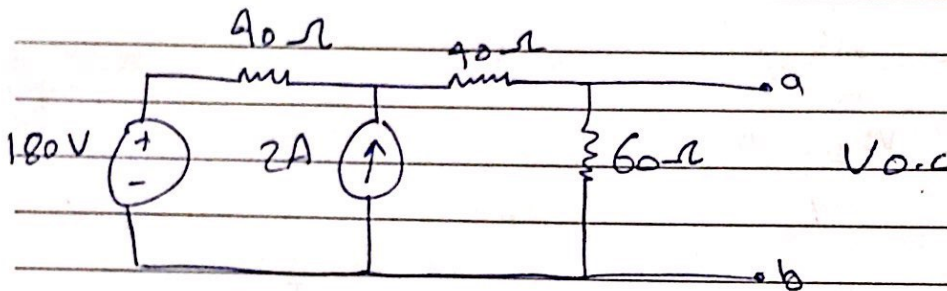
$$90 + 90 = 180 \Omega \rightarrow \frac{180 \times 60}{180 + 60} = 45 \Omega = R_{th}$$



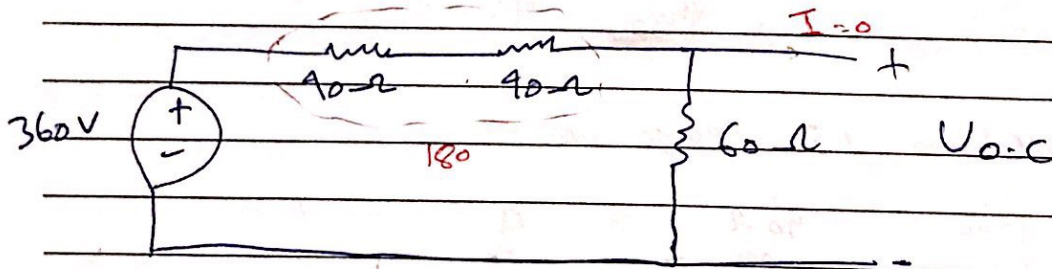current transformation \rightarrow \rightarrow




Voltage division

$$V_{o.c} = \frac{60}{240} \times 360 = 90V$$

$$I = \frac{90}{60} = 1.5$$

Case 2: independent and dependent sources -

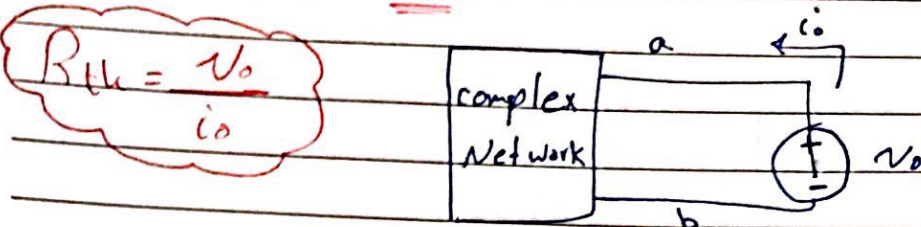- 1) Kill all independent source
- 2) induce a voltage source V_0 between the two terminals
- 3) calculate i_0 generated by the source V_0
- 4) calculate R_{th}



- Alternative method -


- 1) Kill all independent source
- 2) induce a current source i_0 between the two terminals
- 3) calculate V_0 across the current source
- 4) calculate $R_{th} = \frac{V_0}{i_0}$

for simplicity let $V_0 = 1V$




let $i_0 = 1A \Rightarrow V_0 ?$

to find $V_{th} \Rightarrow$ proceed as in case 1.



Practice problem 4.9

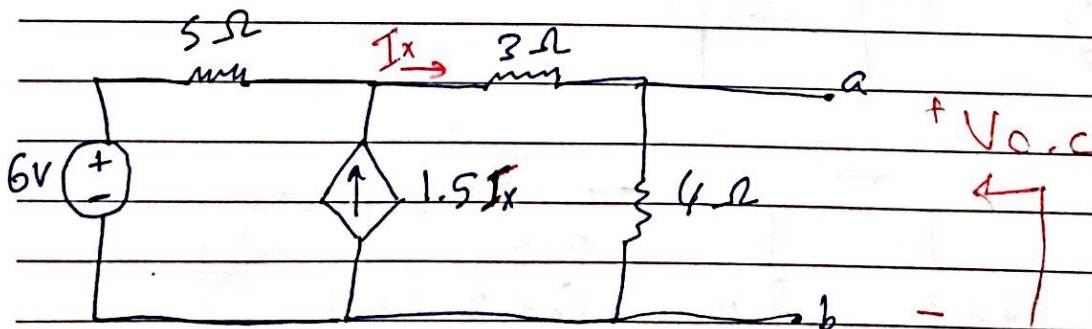

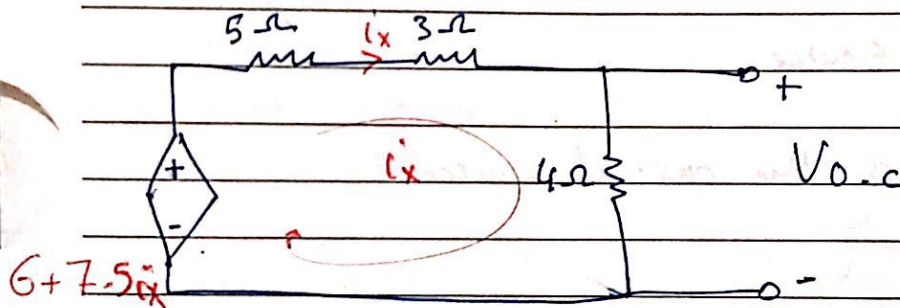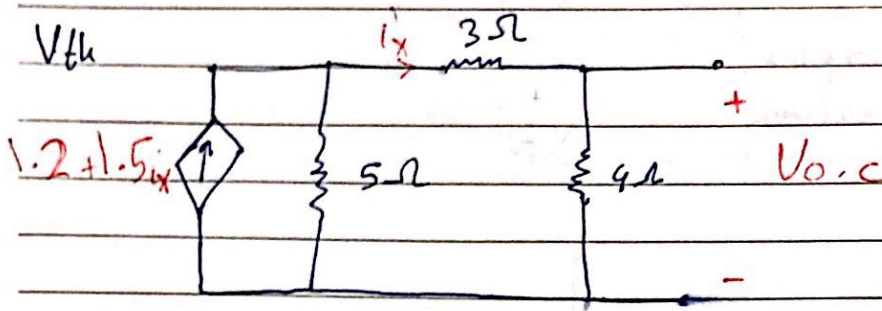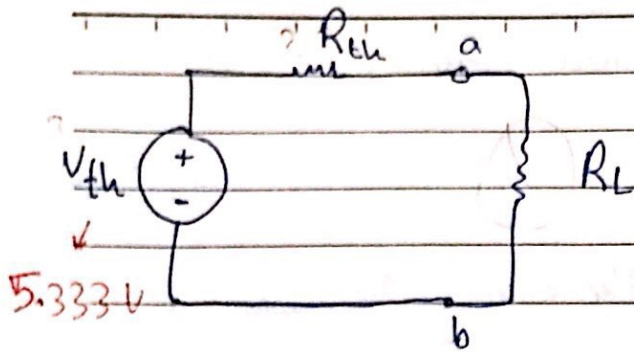find the thevenin equivalent of the circuit above -



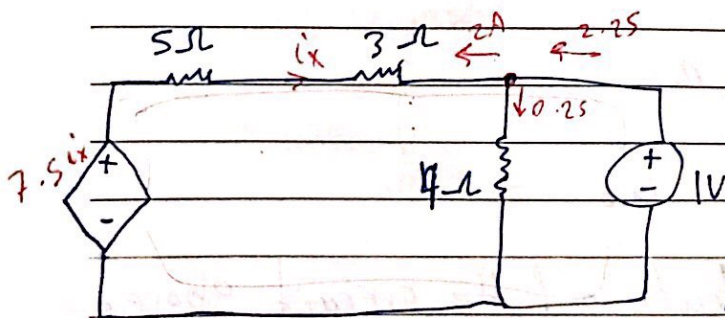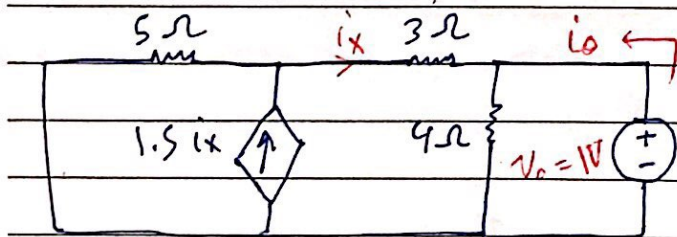
$$i_x = \frac{6 + 7.5i_x}{12} \rightarrow i_x = \frac{4}{3} A \quad \left. \begin{array}{l} \\ \end{array} \right\} V_{o.c} = 4 \left(\frac{4}{3} \right) = \frac{16}{3} = 5.333V$$



$$\begin{aligned}
 -7i_x + 5i_x + 3i_x + 1 &= 0 \\
 0.5i_x &= -1 \rightarrow i_x = -2 \\
 i_o &= 2.25 A
 \end{aligned}$$

$$R_{th} = \frac{V_o}{i_o} = \frac{1}{2.25} = 0.444\Omega$$


Norton equivalent

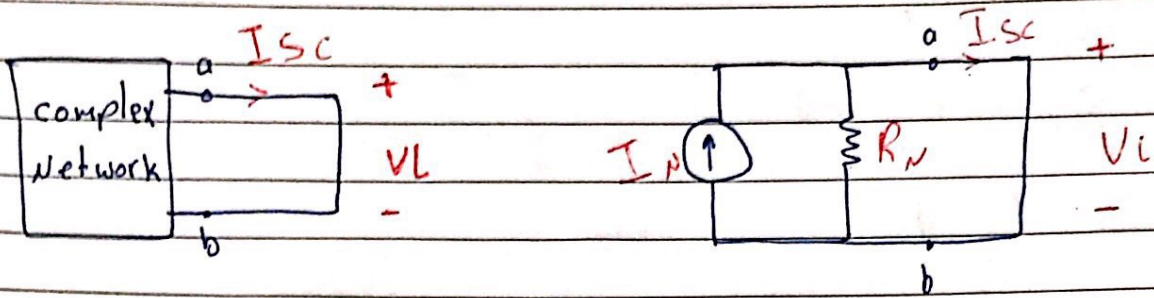


$$R_N = R_{th} \text{ (case 1 and case 2)}$$

$$V_{th} = I_N \cdot R_N = I_N \cdot R_{th}$$


Source transformation

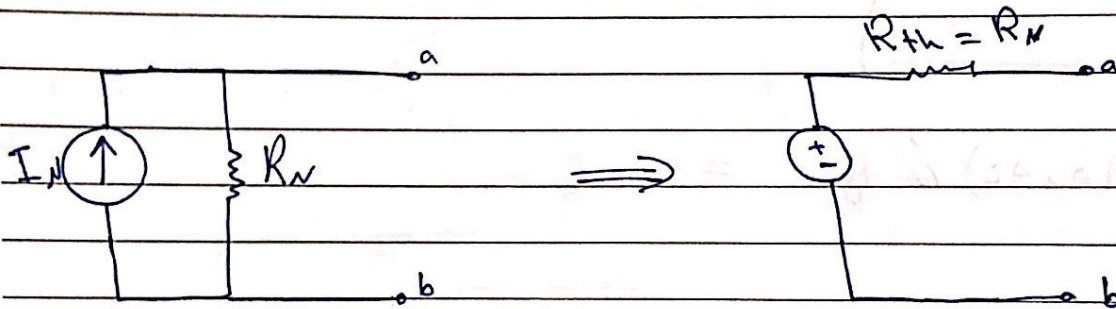


practice problem :- (4.11)

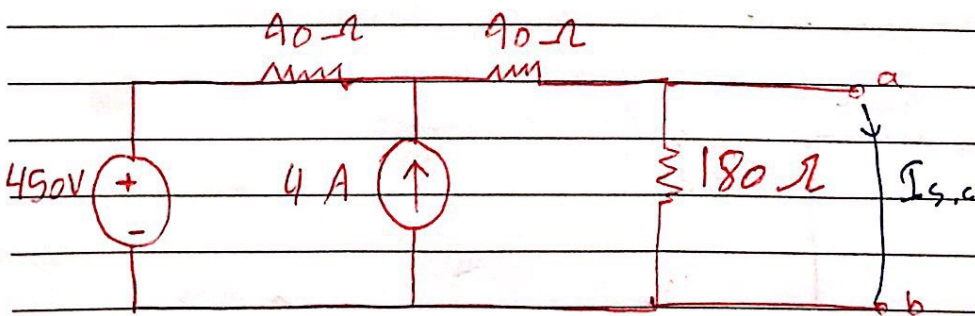



Find Norton equivalent

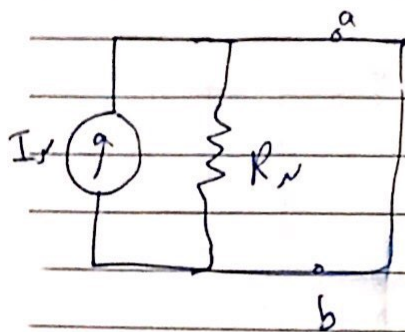

R_N :

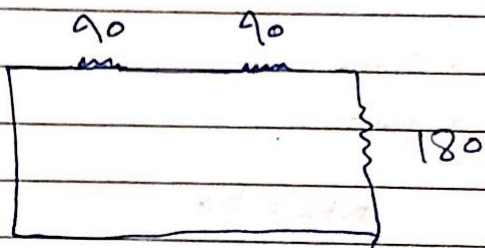

$$(90 + 90) // 180 = 90 \Omega$$

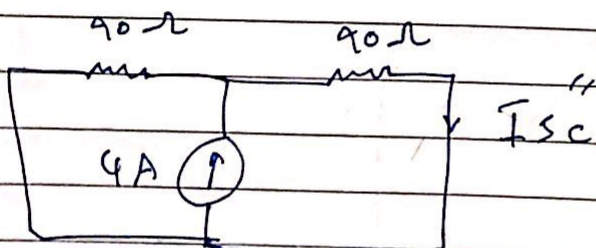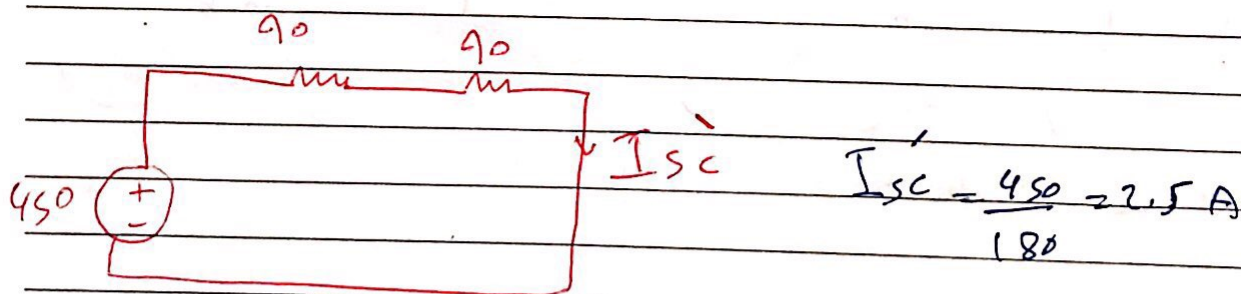


~~$I_{sc}'' = 2 \text{ A}$~~
 $I_{sc}'' = 2 \text{ A}$

$$\begin{aligned} I_{sc} &= I_{sc}' + I_{sc}'' \\ &= 2.5 + 2 \\ &= 4.5 \text{ A} \end{aligned}$$

$$I_N = 4.5 \text{ A}$$

practice problem 4.10

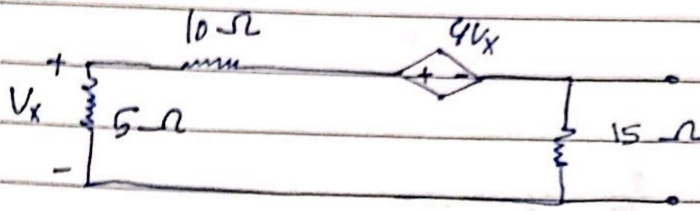


find the thevenin eqn:-

$$5i + 10i + 4V_x + 15i = 0 \quad (V_x = -5i)$$

$$5i + 10i + 4(-5i) + 15i = 0 \rightarrow i = 0$$

$V_{o.c} = V_{th} = 0$

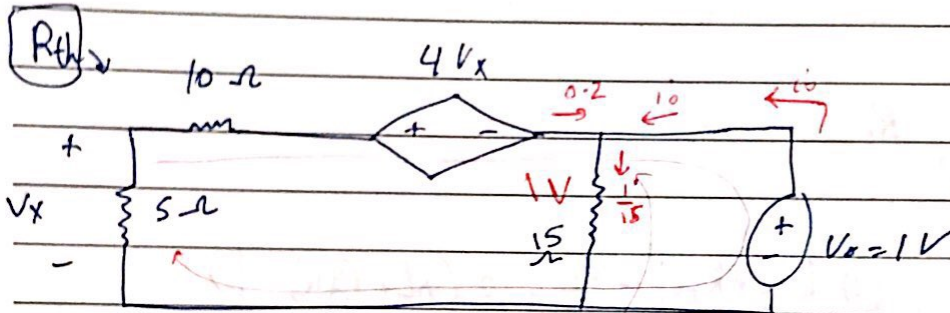


$$5i + 10i + 4V_x + 1 = 0$$

$$V_x = -5i$$

$$\rightarrow 5i + 10i - 20i + 1 = 0 \rightarrow i = +\frac{1}{5} A$$

$$0.2 + i_0 - \frac{1}{15} = 0 \rightarrow i_0 = -\frac{1}{5} + \frac{1}{15} = \frac{-2}{15}$$
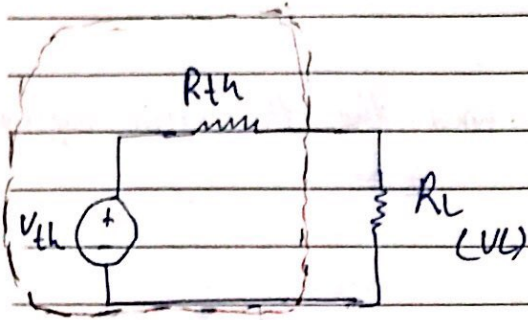
$$R_{th} = \frac{V_o}{i_0} = \frac{1}{-\frac{2}{15}} = -\frac{15}{2} = -7.5 \Omega$$



$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$P_{RL} = V_L \cdot I_L$$

OR


$$P_{RL} = I^2 R_L$$

$$P_{RL} = \frac{V_{th}^2}{(R_L + R_{th})^2} R_L$$

$$\frac{dP_{RL}}{dR_L} = V_{th}^2 \left[\frac{(1)(R_L + R_{th})^2 - R_L \cdot 2(R_L + R_{th})}{(R_L + R_{th})^4} \right]$$

$$= V_{th}^2 \left[\frac{R_L + R_{th} - 2R_L}{(R_L + R_{th})^3} \right] = 0$$
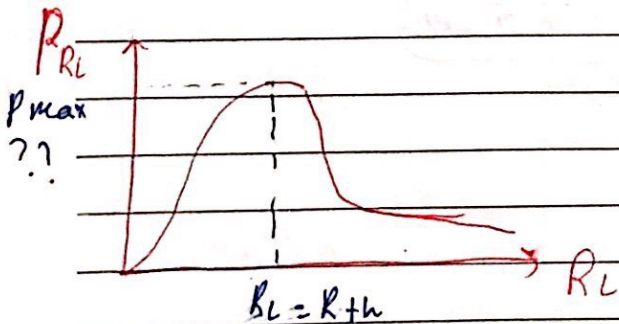
$$R_L + R_{th} - 2R_L = 0 \rightarrow R_L = R_{th}$$




$$P_{max} = \frac{V_{th}^2 \cdot R_{th}}{(2R_{th})^2}$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

CH 5 → ملغي

CH 6's capacitors and inductors :-

* capacitor (C) :-

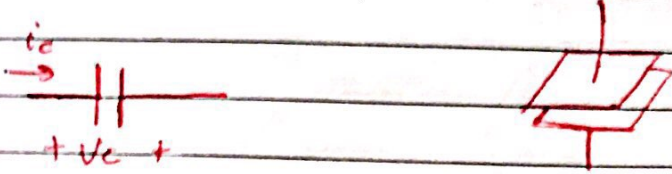

$$i_c(t) = C \frac{d v_c(t)}{dt}$$

C: capacitance in Farad (F).

$$C = \frac{\epsilon \cdot A}{d} \quad \epsilon = \text{permittivity of the insulator}$$

$$\epsilon = \epsilon_0 \epsilon_r$$

↳ permittivity of free space ($8.85 \times 10^{-12} \frac{F}{m}$)

$$i(t) = \frac{dq}{dt}, \quad i = C \frac{dv}{dt} \quad \rightarrow \quad q(t) = C v(t)$$

$$\int_{t_0}^t dv = \int_{t_0}^t \frac{1}{C} i(t) dt$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$$

Assume $t_0 \rightarrow -\infty$ and $v(t = -\infty) = 0$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i dt$$

Ex: determine the current flowing through a 5 μ F capacitor in response to a voltage v equal to

a) -20 V

b) $2e^{-5t}$ V


Solve

a) $i = C \frac{dv}{dt} = 0$

b) $i = 5 \times 10^{-3} \times -10 e^{-5t}$

$i(t) = -50 e^{-5t}$ mA

* A capacitor is open circuit to dc

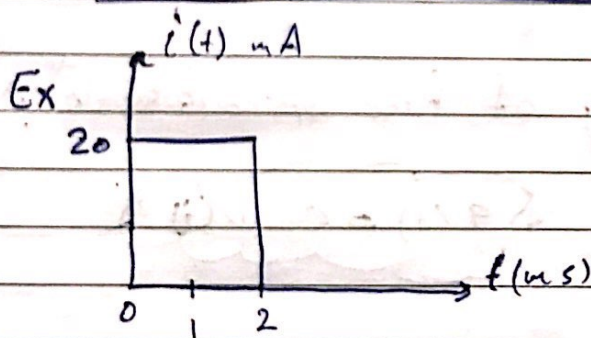

find $v(t)$ for all t :-

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$$

We have three intervals $t \leq 0$, $0 \leq t \leq 2 \mu$ s, $t > 2 \mu$ s

$t \leq 0$

$$v(t_0) = v(-\infty) = 0$$

$$v(t) = \frac{1}{5 \times 10^{-6}} \int_{-\infty}^t 0 \cdot dt + 0 = 0 \quad \cdot t \leq 0$$


$$0 \leq t \leq 2 \text{ ms}$$

$$V(t) = \frac{1}{5 \times 10^{-6}} \int_0^t 20 \times 10^{-3} dt + V(0) \quad 0 \leq t \leq 2 \text{ ms}$$


$$V(t) = 4000 t \quad 0 \leq t \leq 2 \text{ ms}$$

$$t \geq 2 \text{ ms}$$
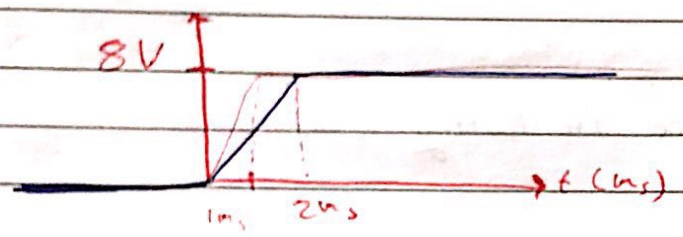
$$V(t) = 0 + V(2 \text{ ms}) = 8 \text{ V}$$



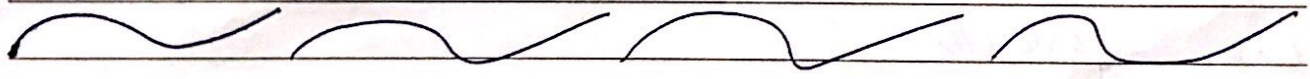* the voltage across a capacitor cannot be changed abruptly.



Energy storage in the capacitor = (J)


$$P = iV = C \frac{dV}{dt}$$

$$W_c(t) - W_c(t_0) = \int_{t_0}^t P dt = C \int_{t_0}^t V \frac{dV}{dt} \cdot dt$$

$$= C \int_{V(t_0)}^{V(t)} V \cdot dV = \frac{1}{2} C [V^2(t) - V^2(t_0)] \rightarrow W_c(t) = \frac{1}{2} C V^2(t)$$

* A finite amount of energy can be stored in a capacitor even if the current through of capacitor is zero, when $V_c(t) = \text{constant}$

* The inductor - (L)

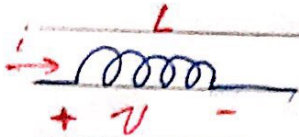


$$V = L \frac{di}{dt}$$

L: inductance in henry (H).


* For constant current $\frac{di}{dt} = 0 \Rightarrow V = 0$

The inductor is short circuit to dc


Ex:

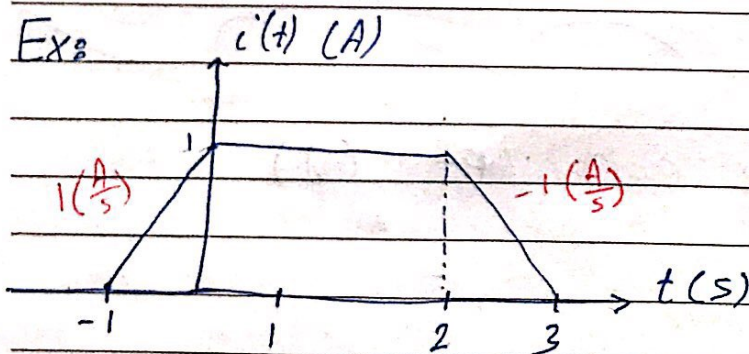

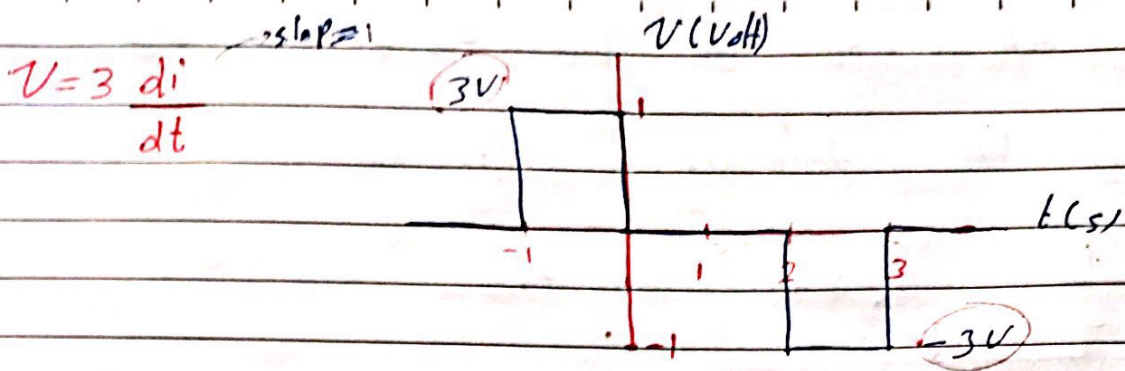Given the current waveform above passing through 3 H inductor, determine the inductor voltage:-



another example..

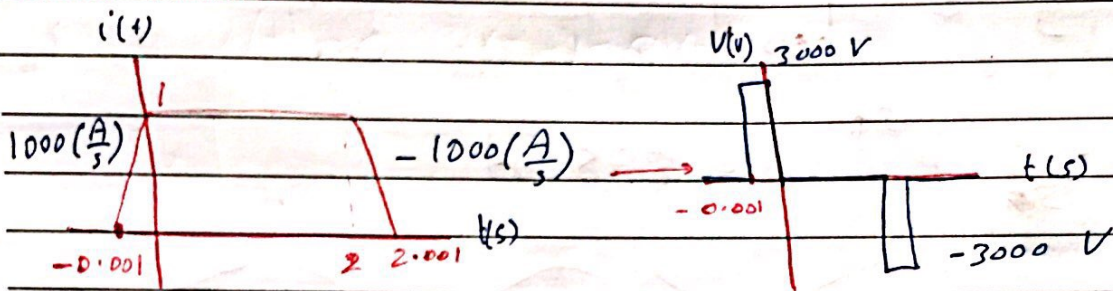

* The current passing through an inductor cannot be changed abruptly.

$$V_L = L \frac{di}{dt}$$

$$\int_{i(t_0)}^{i(t)} di = \frac{1}{L} \int_{t_0}^t V_L dt$$

$$i(t) - i(t_0) = \frac{1}{L} \int_{t_0}^t V_L dt \rightarrow i(t) = \frac{1}{L} \int_{t_0}^t V_L dt + i(t_0)$$

$$i(t_0) = 0 \text{ at } t_0 = -\infty$$

$$i(t) = \int_{-\infty}^t V_L dt$$


Ex: A 100 mH inductor has $v_L(t) = 2 e^{-3t}$ V and

$i_L(-0.5) = 1$ A, determine $i_L(t)$:-

$$i(t) = \frac{1}{L} \left[\int_{t=-0.5}^t 2 e^{-3t} dt \right] + 1$$

$$= \frac{1}{0.1} \left[\frac{-2}{3} e^{-3t} \Big|_{-0.5}^t \right] + 1$$
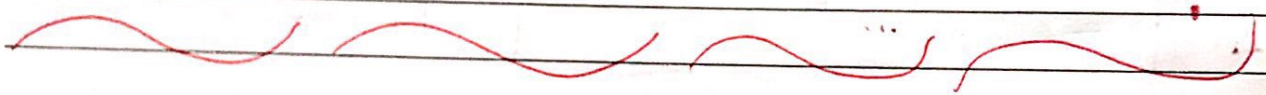
$$i(t) = \frac{-20}{3} e^{-3t} + 30.878 \text{ A}$$



* Energy Storage :-

$$P = v i = \left(L \frac{di}{dt} \right) i = L i \frac{di}{dt}$$

$$\int_{t_0}^t P dt = L \int_{t_0}^t i \frac{di}{dt} dt$$

$$w_L(t) - w_L(t_0) = L \int_{i(t_0)}^{i(t)} i di = \frac{1}{2} L [i(t)^2 - i(t_0)^2]$$

$$w_L(t) = \frac{1}{2} L i(t)^2$$

Ex 8 $L = 25 \text{ mH}$ a) find v_L at $t = 12 \text{ ms}$ if $i_L = 10t e^{-100t} \text{ A}$

b) find i_L at $t = 0.1 \text{ s}$ if $v_L = 6 e^{-12t} \text{ V}$ and $i_L(0) = 10 \text{ A}$

* if $i_L = 8(1 - e^{-40t}) \text{ mA}$, find :-

c) The power being delivered to the inductor at $t = 50 \text{ ms}$


d) The energy stored in the inductor at $t = 40 \text{ ms}$.

~~solu~~ solu: a) -15.06 mV b) 23.98 A

c) $7.49 \mu\text{W}$ d) $0.51 \mu\text{J}$

* inductance and capacitance combinations :-

1) inductors in series

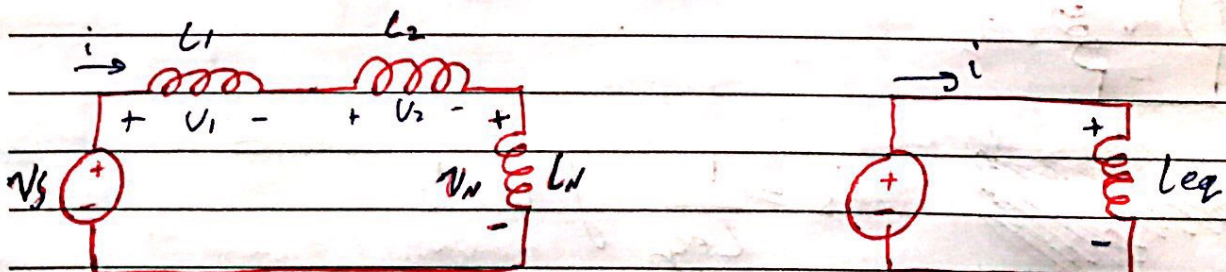

$$V_S = V_1 + V_2 + \dots + V_N$$


$$= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$

$$V_S = L_{eq} \frac{di}{dt}$$

$$V_S = \underbrace{(L_1 + L_2 + L_N + \dots)}_{L_{eq}} \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + \dots + L_N$$


inductors in parallel :-

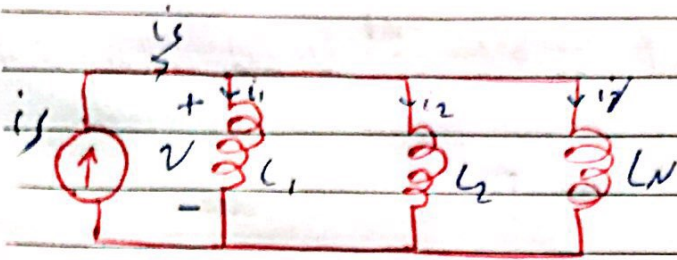

$$i_s = i_1 + i_2 + \dots + i_n$$

$$= \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt + \dots + \frac{1}{L_n} \int v dt$$
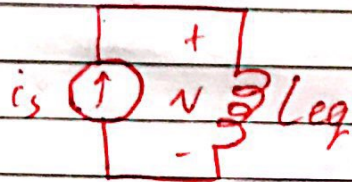
$$i_s = \left[\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right] \int v dt$$





~~is = 1/L_eq ∫ v dt~~

$$i_s = \frac{1}{L_{eq}} \int v dt$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$

$$* \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} \rightarrow L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

* Capacitors in series

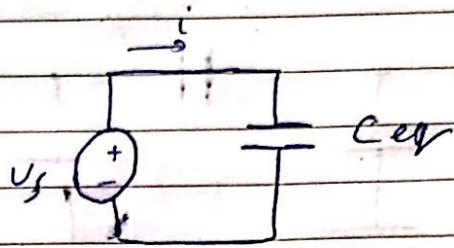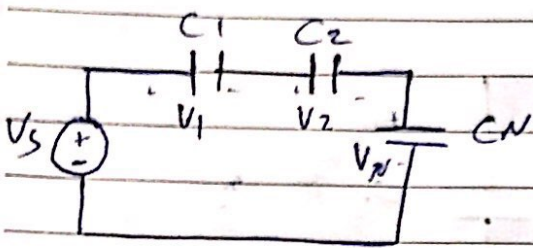

$$V_s = V_1 + V_2 + \dots + V_N$$



$$= \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt + \dots + \frac{1}{C_N} \int i dt$$

$$V_s = \frac{1}{C_{eq}} \int i dt$$

$$V_s = \left[\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right] \int i dt$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

* capacitors in parallel

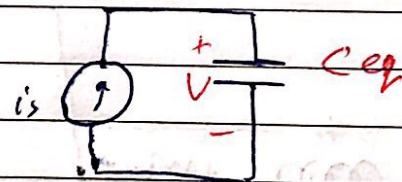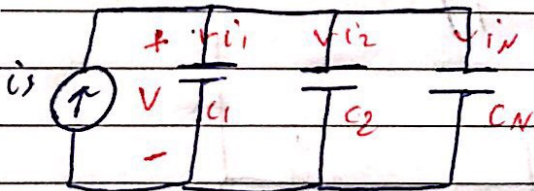

$$i_s = i_1 + i_2 + \dots + i_N$$


$$= C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt} + \dots + C_N \frac{dV}{dt}$$

$$i_s = C_{eq} \frac{dV}{dt}$$

$$= [C_1 + C_2 + \dots + C_N] \frac{dV}{dt}$$

$$C_{eq} = C_1 + C_2 + \dots + C_N$$

Ex 2

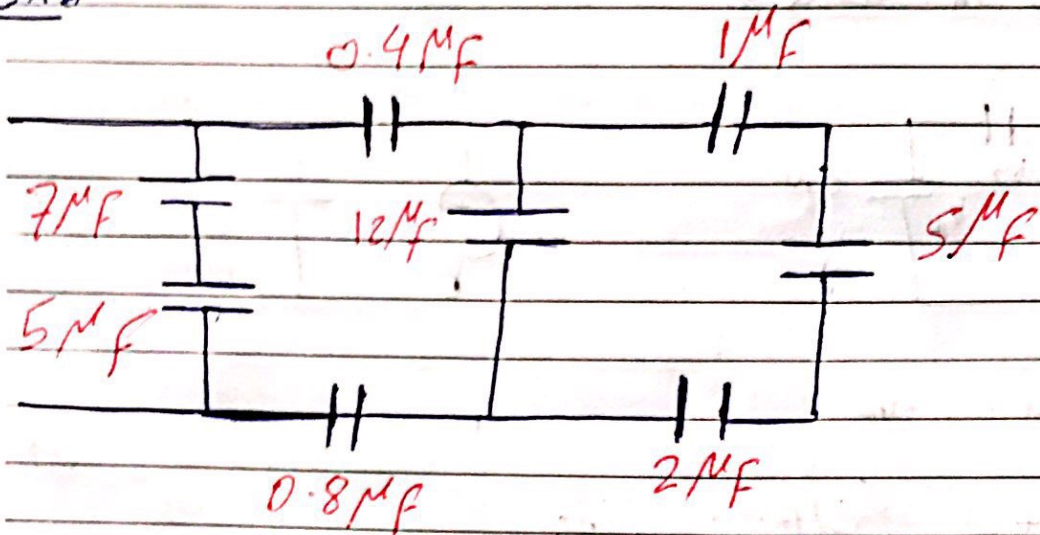


① $\frac{1 \times 5}{6} = \frac{5}{6} \text{ MF}$

② $\left(\frac{\frac{5}{6} \times 2}{\frac{5}{6} + 2} \right) \text{ MF} = \frac{10}{17} \text{ MF}$

continue the solution



$C_{eq} = 3.178 \text{ MF}$

Ex

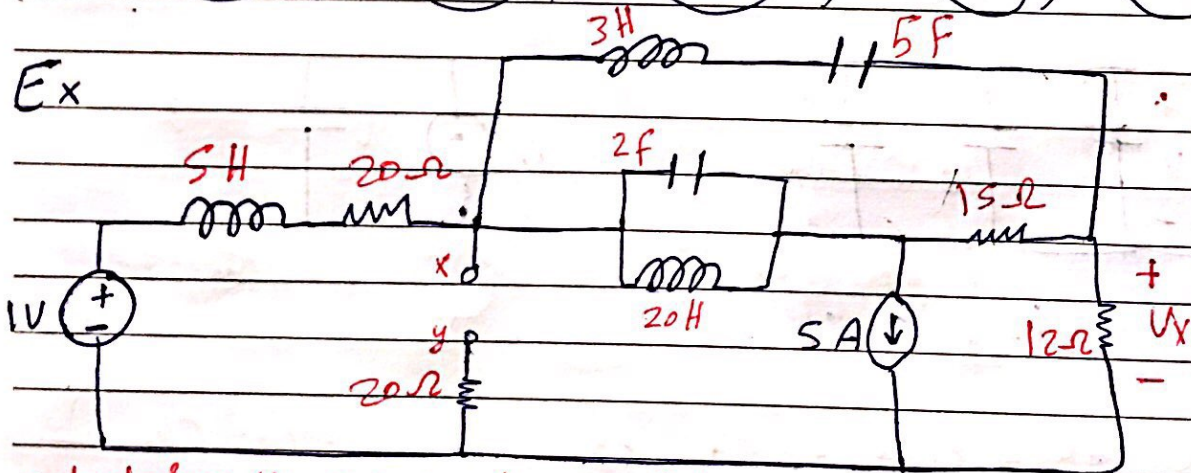

calculate V_x assuming the circuit has been running a long time if:-


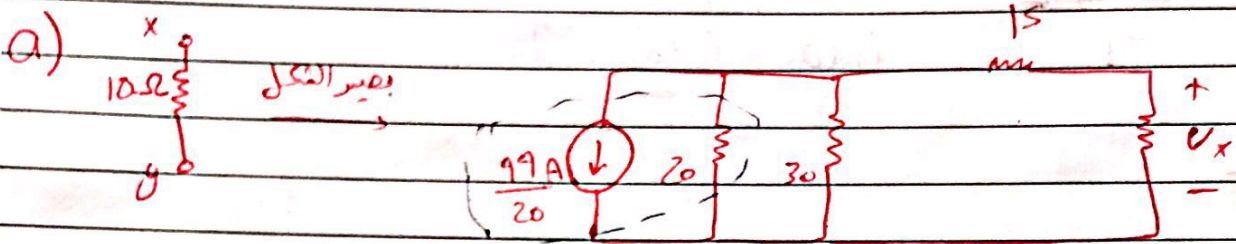
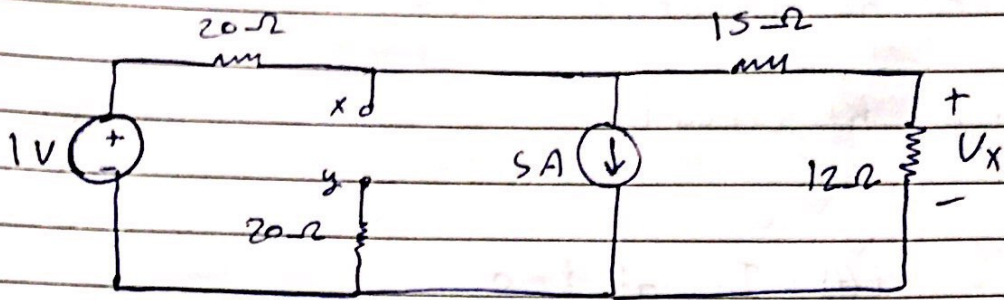
- a) a $10\text{-}\Omega$ resistor is connected between x and y
- b) a 1H inductor " " " " "
- c) a 1F capacitor " " " " "
- d) a 4H in parallel with $1\text{-}\Omega$ is connected between x and y



source transformation and addition current sources

$$\frac{30 \times 20}{30 + 20} = 12 \Omega$$


$$V_x = 12 \frac{49}{20} \left(\frac{12}{39} \right) = -18.64 \text{ V}$$

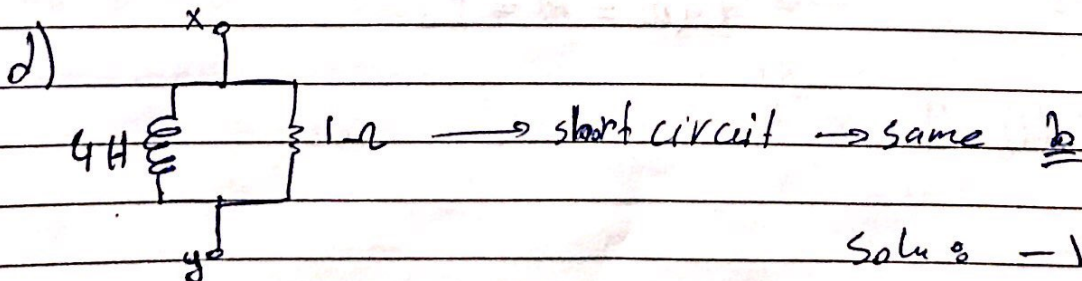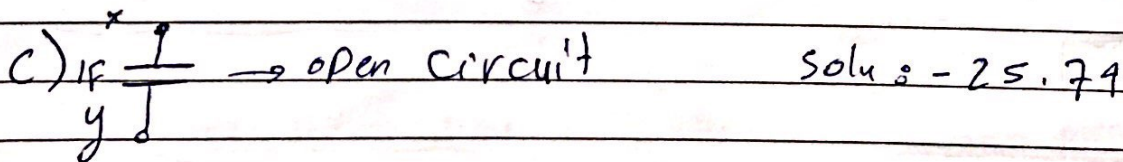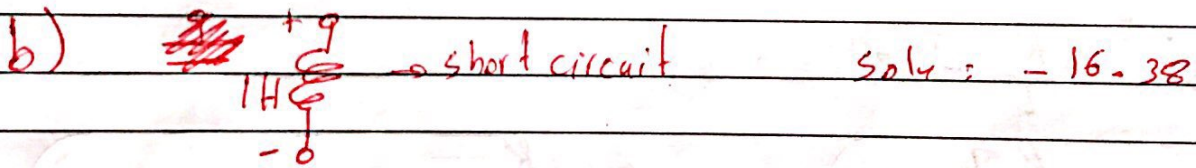

CH 7: First order circuits

* Basic RL and RC circuits :-

- The source-free RL circuit :-

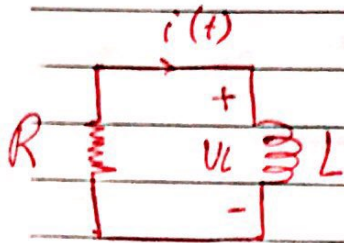

$$i(t) = I_0 \text{ at } t=0$$

$$i_L(0) = i_L(0^+) = I_0$$

by KVL

$$L \frac{di}{dt} + iR = 0 \rightarrow \frac{di}{dt} + \frac{R}{L} i = 0$$

$$i(t) = A e^{s_1 t} \rightarrow \frac{di}{dt} = A s_1 e^{s_1 t}$$

$$A s_1 e^{s_1 t} + \frac{R}{L} A e^{s_1 t} = 0$$

$$A e^{s_1 t} \left[s_1 + \frac{R}{L} \right] = 0 \rightarrow s_1 + \frac{R}{L} = 0$$

$$s_1 = -\frac{R}{L}$$


$$i(t) = A e^{-\frac{Rt}{L}} \rightarrow i(0) = A = I_0$$

$$i(t) = I_0 e^{-\frac{Rt}{L}}$$

ex8

500 nH

10000

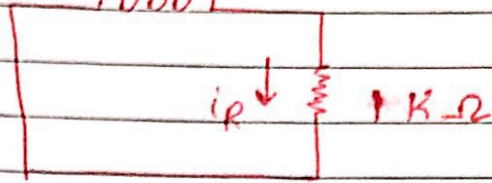


Determine the current i_R through the resistor at $t = 1 \mu s$
 if $i_R(0) = 6 A$

$$i_R = i_L = I_0 e^{-\frac{Rt}{L}}$$

$$= 6 e^{-\frac{10000 t}{500 \times 10^{-9}}} = 6 e^{-2 \times 10^4 t} \quad | \quad t = 1 \mu s$$


$$= 6 e^{-2} = 0.812 A = 812 \mu A$$

Ex8

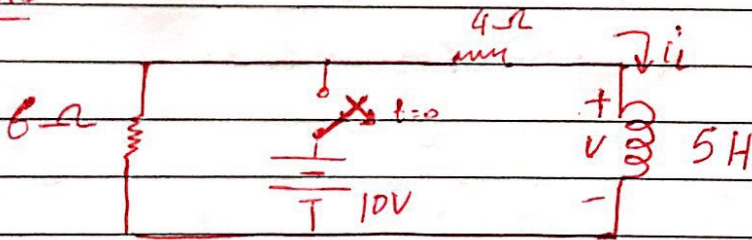


Determine the inductor voltage v_L in the circuit shown for $t > 0$.

$t < 0$

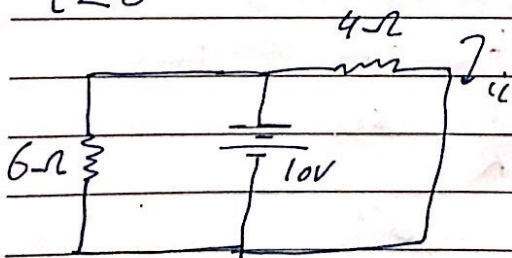

$$i_L = \frac{10}{4} = 2.5 A$$

$$i_L(0^-) = i_L(0^+) = 2.5 A$$

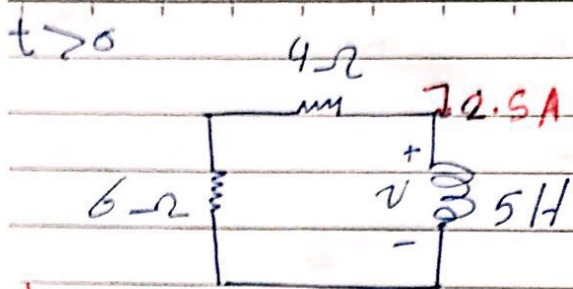

1st way

$$i_L(t) = I_0 \cdot e^{-\frac{Rt}{L}} = 2.5 e^{-\frac{10t}{5}} = 2.5 e^{-2t}$$

$$v_L(t) = L \frac{di}{dt} = 5(2.5)(-2)e^{-2t} = -25 e^{-2t} \text{ V}$$


2nd way

$$v(t) = A e^{-2t} \quad (v(0) = A)$$

$$v(0) = (-2.5)(6+4) = -25 \text{ V} \rightarrow \text{mesh loop}$$

$$v(t) = -25 e^{-2t} \text{ V} \rightarrow \text{same answer}$$

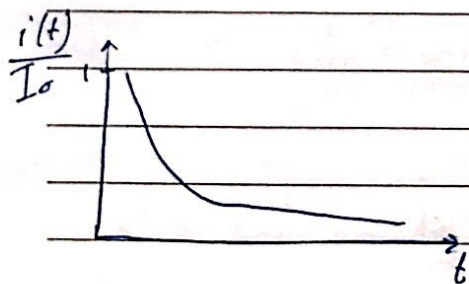* Properties of the exponential response -



$$i(t) = I_0 e^{-\frac{Rt}{L}} = I_0 e^{-\frac{t}{\tau}}$$


τ = the time constant

$$\tau = \frac{L}{R} \text{ sec}$$

~~$$i(t) = I_0 e^{-\frac{t}{\tau}}$$~~

$$\frac{i(t)}{I_0} = e^{-\frac{t}{\tau}} \rightarrow \frac{i(t=\tau)}{I_0} = e^{-1}$$

* The source-free RC circuits :-

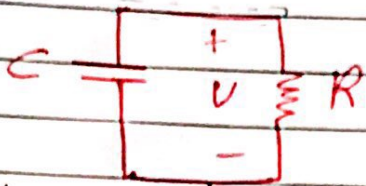

by Nodal $\frac{1}{\square}$

$$\frac{V}{R} + C \frac{dV}{dt} = 0 \quad (V(0) = V_0)$$

$$\frac{dV}{dt} + \frac{1}{RC} V = 0$$


$$V(t) = A e^{-t/\tau}$$

ليس يوجد مصدر الجهد في الدارة

$$V(t) = V_0 e^{-t/RC}$$


* the time constant $\tau = RC$ sec

Ex:

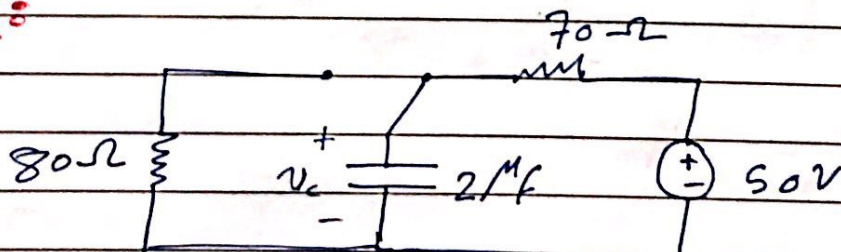


Determine $V(t)$ at $t=0$ and $t=160 \mu s$.

$t < 0$

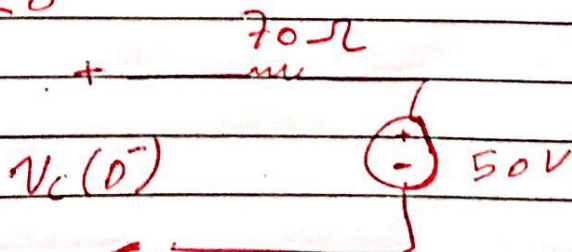

$$V_c(0^-) = V_c(0^+) = 50V$$


$t > 0$

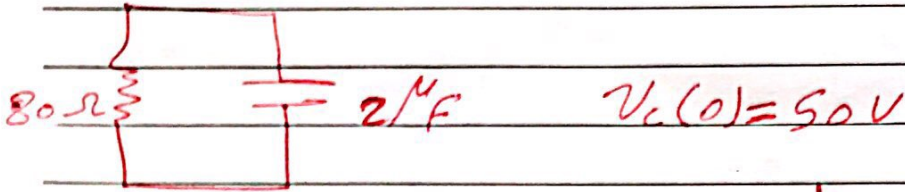

$$V(t) = V_0 e^{-\frac{t}{R_c}} = 50 e^{-\frac{t}{80 \times 2 \times 10^{-6}}} = 50 e^{-6250 t}$$

$$V(0) = 50 V$$
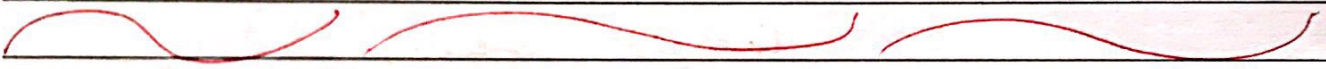
$$V(t = 160 \mu s) = 50 e^{-6250 (160 \times 10^{-6})} = 18.39 V$$



* The unit step function:-


$$u(t) = \begin{cases} 1, & t > 0 \\ 0, & t < 0 \end{cases}$$

$$u(t-t_0) = \begin{cases} 1, & t > t_0 \\ 0, & t < t_0 \end{cases}$$



$$t-t_0 > 0 \quad t > t_0$$

$$u(-t) = \begin{cases} 0, & t > 0 \\ 1, & t < 0 \end{cases}$$

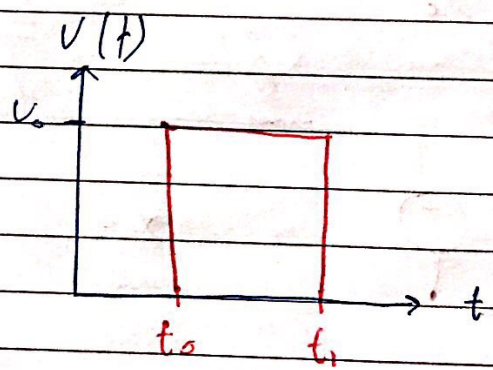
$$v(t) = \begin{cases} 0, & t < t_0 \\ V, & t_0 \leq t \leq t_1 \\ 0, & t > t_1 \end{cases}$$



$$v(t) = V_0 [u(t-t_0) - u(t-t_1)]$$

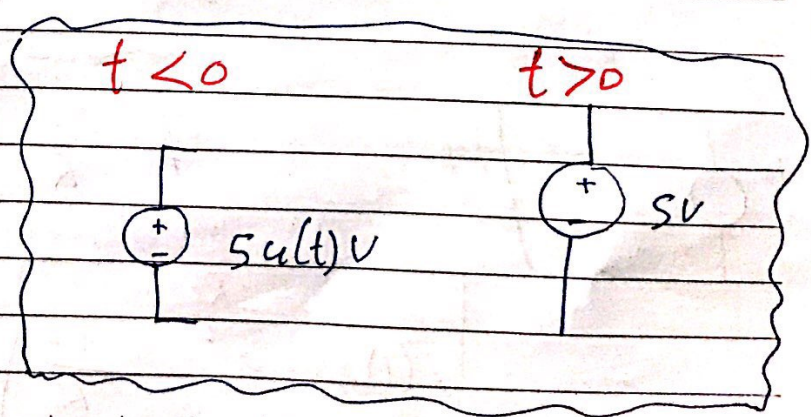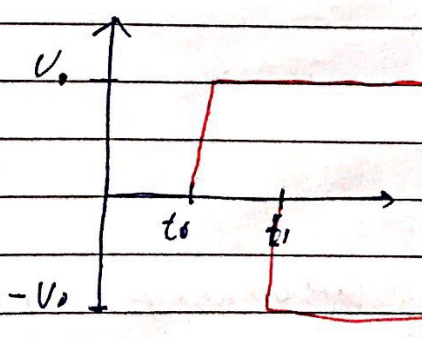

Driven RL circuit

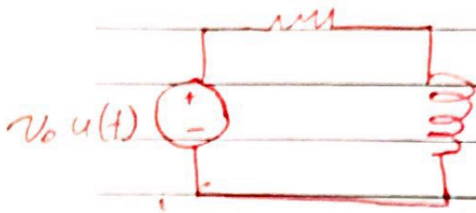


$$i(t) = i_n + i_f$$

i_n = Natural current


i_f = forced current

if $t < 0$

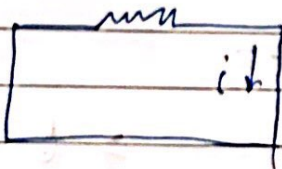


$$i_L(0^-) = i_L(0^+) = 0$$

$t > 0$

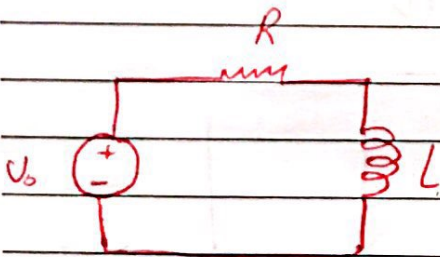

$$i_n = A e^{-\frac{Rt}{L}}$$

$t \rightarrow \infty$

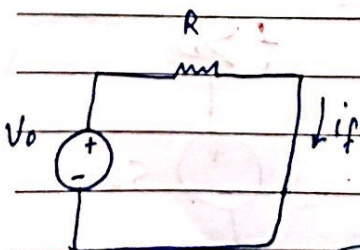

$$i_f = \frac{v_0}{R}$$


if v_0 goes $A = \dots$

$$i(t) = A e^{-\frac{Rt}{L}} + \frac{v_0}{R}$$


$$0 = A + \frac{v_0}{R}$$

$$\therefore A = -\frac{v_0}{R}$$
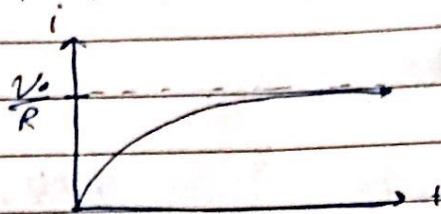
$$i(t) = \frac{V_0}{R} \left[1 - e^{-\frac{Rt}{L}} \right]$$




Ex:

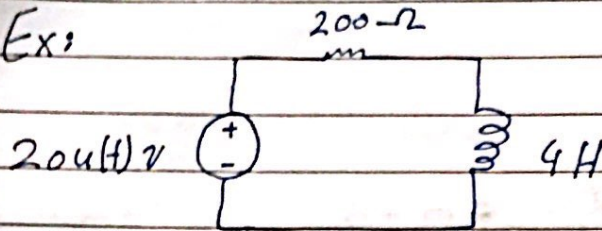


- Find $i(0^-)$, $i(0^+)$ and $i(15\mu s)$

$t < 0$

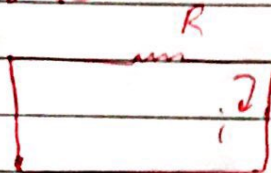

$$i(0^-) = i(0^+) = 0$$

$t > 0$

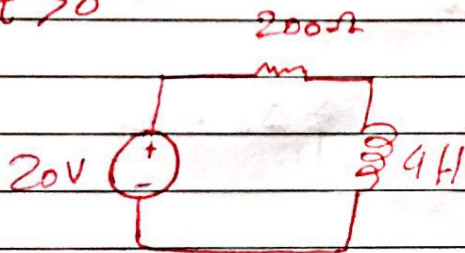

$$i(t) = i_n + i_p$$

$$i_n = A e^{-50t}$$

$$i_p = \frac{20}{200} = 0.1 \text{ A}$$

$$i(t) = A e^{-50t} + 0.1$$

$$0 = A + 0.1 \rightarrow A = -0.1$$

$$\therefore i(t) = 0.1 \left[1 - e^{-50t} \right] \text{ A}$$

$$i(15\mu s) = 0.1 \left[1 - e^{-50(15 \times 10^{-6})} \right]$$

$$= \boxed{52.8 \text{ nA}}$$

نفس السؤال إذا بدى أو صر

$$V(t) = V_n + V_f$$

$$= A e^{-st} + V_f$$

$$V(0^+) = i(0^+) \times 200 = 0$$


at $t \rightarrow \infty$

$$V_f = 20V$$

$$V(t) = A e^{-st} + 20 \rightarrow V(0^+) = 0 = A + 20 \rightarrow A = -20$$


$$V(t) = 20(1 - e^{-st})$$

Driven RC circuit :-

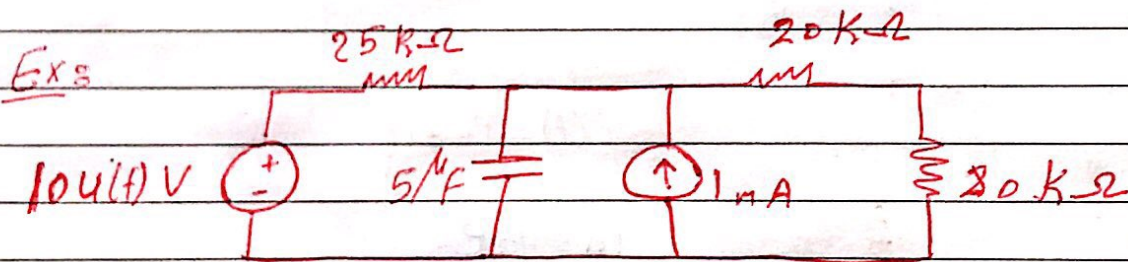



Find, $V_c(0^-)$, $V_c(0^+)$, $V_c(\infty)$ and $V_c(0.08 \text{ sec})$:-

$t < 0$

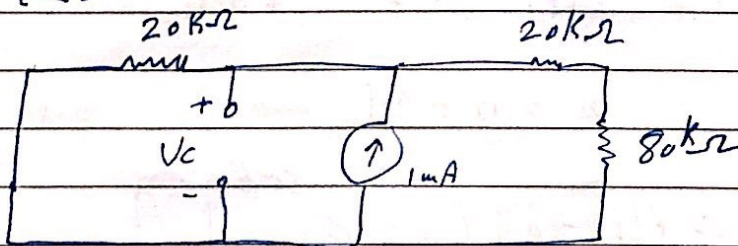

$$V_c(0^-) = V_c(0^+) = \left(\frac{100K}{125K} \cdot 1mA \right) 25K = 20V$$



$t > 0$

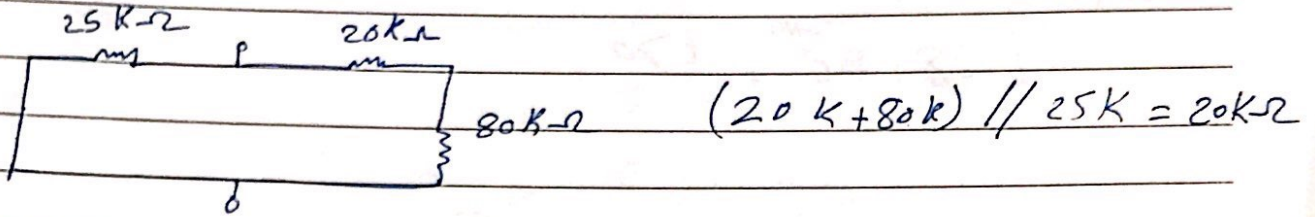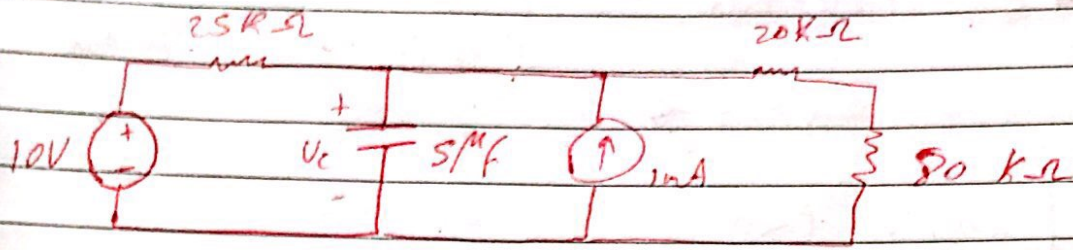

$$V_c(t) = V_{cN} + V_{cF}$$

$$V_{cN} = A e^{-\frac{t}{R_{eq}C}} = A e^{-\frac{t}{(20 \times 10^3 \times 5 \times 10^{-6})}} = A e^{-10t}$$

$t \rightarrow \infty$

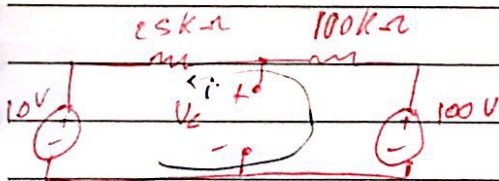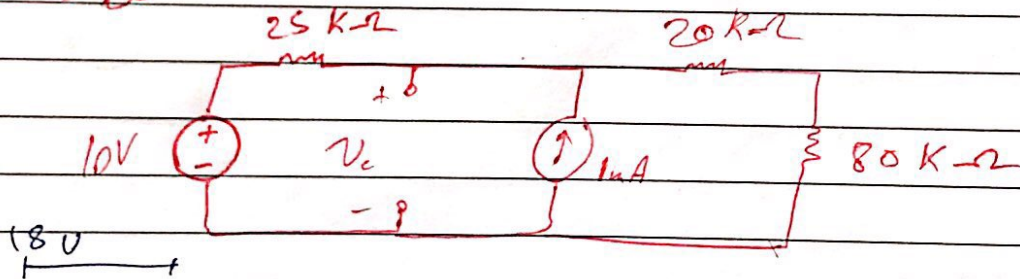

$$i = \frac{100 - 10}{125k} = 0.72 \mu A$$

KVL


$$-10 - 18 + V_c = 0 \rightarrow V_c = 28V$$

$$V_c(t) = A e^{-10t} + 28 = 20V$$

$$20 = A + 28 \rightarrow A = -8$$


$$V_c(t) = 20 + 8(1 - e^{-10t}) U(t)$$
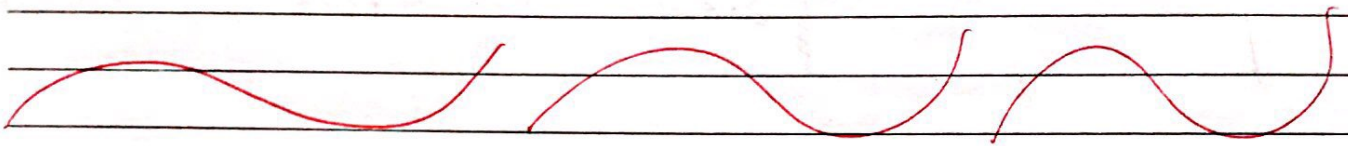
$$V_c(t) = \begin{cases} 20, & t < 0 \\ 28 - 8e^{-10t}, & t > 0 \end{cases}$$



* The RLC circuit :

- the source-free parallel RLC circuit :

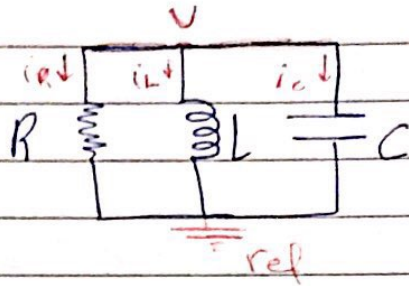

KCL :-

$$\frac{v}{R} + \frac{1}{L} \int_{t_0}^t v dt - i_L(t_0) + C \frac{dv}{dt} = 0 \quad \left] \frac{d}{dt} \right.$$

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

$$\frac{d^2 v}{dt^2} + \frac{1}{Rc} \frac{dv}{dt} + \frac{1}{Lc} v = 0$$

with $i_L(0^+) = I_0$ and $v_C(0^+) = V$

and T need

$$i_C(t) = C \frac{dv}{dt}$$

$$\longrightarrow \frac{dv}{dt}(0^+) = \frac{i_C(0^+)}{C}$$

$$\frac{dv}{dt} = \frac{i_C}{C}$$

$$= - \frac{[i_L(0^+) + i_R(0^+)]}{C}$$

$$i_R(0^+) = \frac{V_0}{R}$$

The form of solutions-

$$v = A e^{st}$$

$$\frac{dv}{dt} = s A e^{st} \quad \rightarrow \quad \frac{d^2 v}{dt^2} = s^2 A e^{st}$$

$$s^2 A e^{st} + \frac{1}{R_c} s A e^{st} + \frac{1}{L_c} A e^{st} = 0$$

$$A e^{st} \left[s^2 + \frac{1}{R_c} s + \frac{1}{L_c} \right] = 0$$

$$s^2 + \frac{1}{R_c} s + \frac{1}{L_c} = 0$$

$$= \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$s_{1,2} = \frac{-1}{2R_c} \pm \sqrt{\left(\frac{1}{2R_c}\right)^2 - \left(\frac{1}{L_c}\right)^2}$$

① if s_1 and s_2 are real and distinct \rightarrow (overdamped system).

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

② if $s_1 = s_2$ and real \rightarrow (critically damped system)

$$v(t) = e^{st} [A_1 t + A_2]$$

③ if s_1 and s_2 are complex conjugates \rightarrow underdamped


$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega^2}$$

$$s_{1,2} = -\alpha \pm j\omega_d$$

$$\alpha = \frac{1}{2RC}, \quad \omega = \frac{1}{\sqrt{LC}}$$


$$\text{where } \omega_d = \sqrt{\omega^2 - \alpha^2}$$

Ex 3

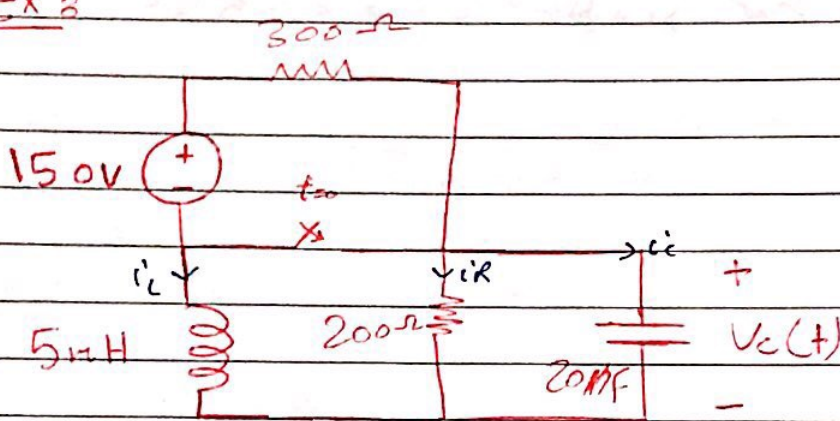

Find expression for $V_c(t)$ for $t > 0$


~~for~~ $t < 0$

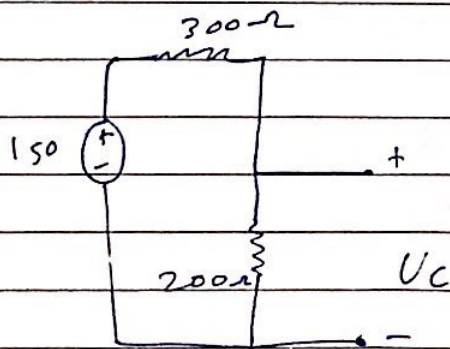

$$V_c(0^-) = \frac{200}{500} \times 150 = 60 \text{ V} = V_c(0^+)$$

$$i_L(0^-) = \frac{-150}{500} = -300 \mu\text{A} = i_L(0^+)$$

$t > 0$

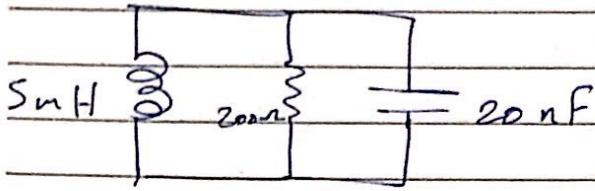

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 200 \times 20 \times 10^{-9}} = 125,000 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 10^{-9} \times 20 \times 10^{-9}}} = 100,000 \text{ s}^{-1}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -50,000$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -200,000$$

$$v_c(t) = A_1 e^{-50,000t} + A_2 e^{-200,000t}$$

$$v_c(0^+) = 60 = A_1 + A_2 \quad \text{--- (1)}$$

$$C \frac{dv}{dt} = i_c \longrightarrow \frac{dv}{dt}(0^+) = \frac{i_c(0^+)}{C}$$

$$i_R(0^+) = \frac{60}{200} = 300 \text{ mA}$$

$$i_c(0^+) = -\left[\frac{i_R(0^+) + i_c(0^+)}{C} \right] \longrightarrow \frac{dv}{dt} = 0 \text{ V/s}$$


$$\frac{dV_C(t)}{dt} \Big|_{t=0} = -50000 A_1 e^{-50000t} - 200000 A_2 e^{-200000t}$$

$$-50000 A_1 - 200000 A_2 = 0$$

$$(1) A_1 + 4A_2 = 0$$

$$(2) A_1 + A_2 = 6 \rightarrow A_1 = 80 \quad A_2 = -20$$

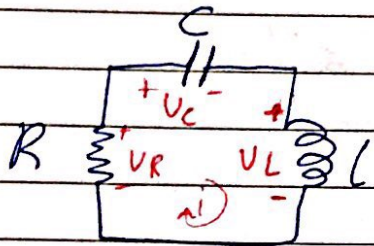* The source free RLC circuit :-
↓ series



$$L \frac{di}{dt} + iR + \left(\frac{1}{C} \int i dt - V_C(t_0) \right) = 0$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{over damped system})$$

$$s_{1,2} = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L} \right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

critically damped system $\alpha = \omega_0$

$$i(t) = e^{-\alpha t} (A_1 t + A_2)$$

for under damped system:


$$i(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

$$\text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

remember:-


$$\text{important } i(0^+) \quad \mathcal{V}_L(0^+) = L \frac{di(0^+)}{dt} \rightarrow \frac{di(0^+)}{dt} = \frac{V_C(0^+)}{L}$$

Ex:

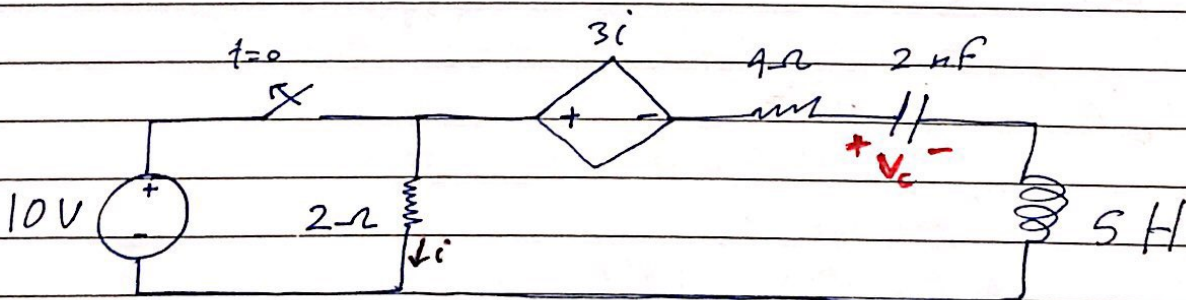

Find an expression for $V_C(t)$ for $t > 0$?


to find R_{th} :-

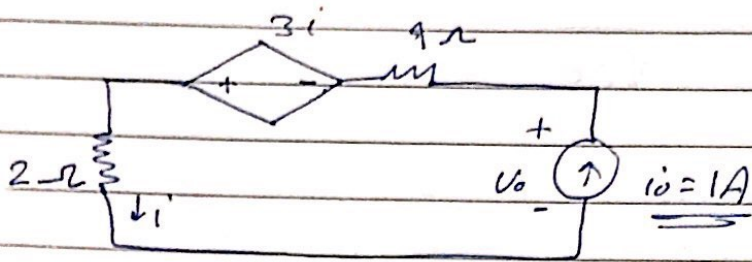

$$4(1) - 3(1) + 2(1) - V_0 = 0 \rightarrow V_0 = 8V$$

$$R_{th} = \frac{8}{1} = 8\Omega \quad \checkmark$$

$t < 0$

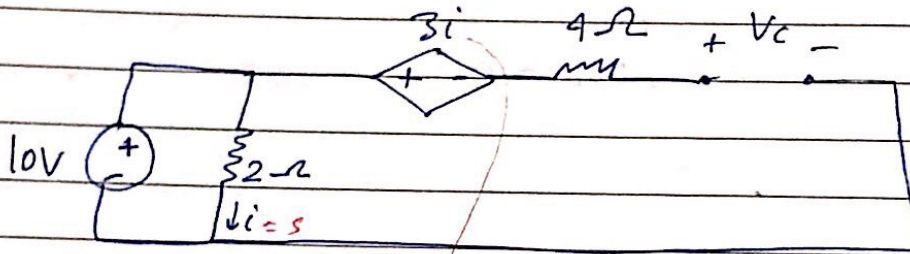

$$i_1 = \frac{10}{2} = 5A$$

$$3i_1 = 15 \text{ volt}$$

KVL


$$-10 + 15 + V_c = 0 \rightarrow V_c = -5V$$

$$V_c(0^+) = V_c(0^-) = -5V$$

$$i_c(0^+) = i_c(0^-) = 0$$

open circuit

$t > 0$

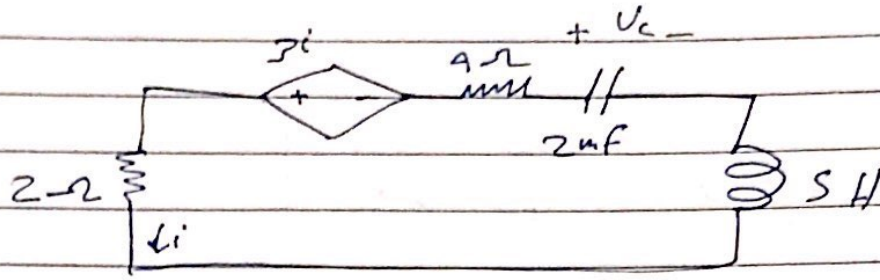

$$\alpha = \frac{R}{2L} = \frac{8}{10} = 0.8 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 2 \times 10^{-3}}} = 10 \text{ rad/sec (underdamped)}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 9.968 \text{ rad/sec}$$

$$* v_c(t) = e^{-\alpha t} [B_1 \cos(9.968t) + B_2 \sin(9.968t)]$$

$$v_c(0^+) = -5 = e^0 [B_1 + 0] \rightarrow B_1 = \underline{\underline{-5}}$$

$$\left. \frac{dv_c}{dt} \right|_{t=0} = -0.8 e^{-0.8t} [B_1 \cos(9.968t) + B_2 \sin(9.968t)] + e^{-0.8t} [-9.986 B_1 \sin(9.968t) + 9.968 B_2 \cos(9.968t)]$$

$$0 = -0.8 B_1 + 9.986 B_2$$

$$c \frac{dv_c(0^+)}{dt} = i_c(t)$$


$$-0.8(-5) + 9.968 B_2 \Rightarrow B_2 = \underline{\underline{-0.4013}}$$

$$= \frac{dv_c(0^+)}{dt} = \frac{i_c(0^+)}{c}$$

نموذج في * لي يحدد اعداد التذبذب


$$= \frac{dv_c}{dt} = 0 \rightarrow v_c(t) = -e^{-0.8t} [5 \cos(9.968t) + 0.4013 \sin(9.968t)]$$

Ex 8

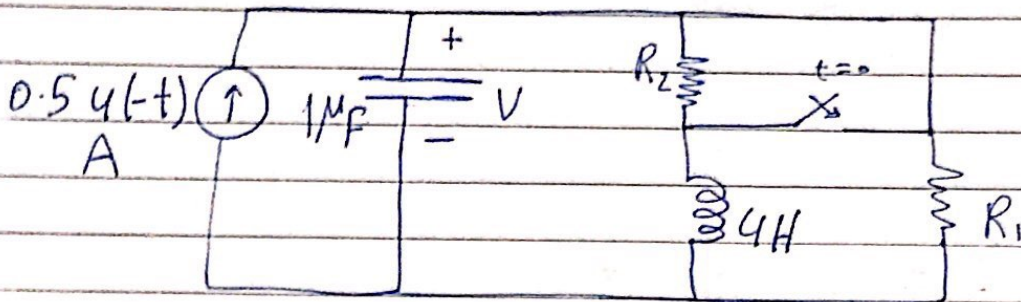

- R_1 such that critically damped system
- R_2 to obtain $v(0) = 100\text{V}$
- find $v(t)$ at $t = 1\text{ms}$

$t > 0$

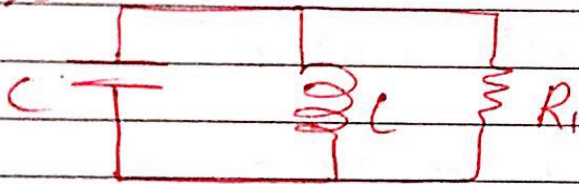


$$\alpha = \frac{1}{2R_1C}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{4 \times 1 \times 10^{-6}}} = 500 \text{ rad/sec}$$

$$500 = \frac{1}{2R_1(1 \times 10^{-6})} \rightarrow R_1 = \frac{1}{500(2 \times 10^{-6})} = 1 \text{ k}\Omega$$

$$v(t) = e^{-500t} [A_1 t + A_2]$$

$t < 0$

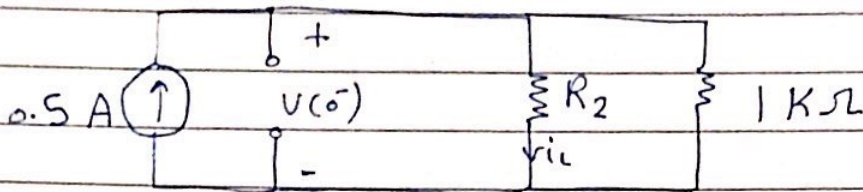


$$100 = (R_1 \parallel R_2) (0.5) \rightarrow 100 = \frac{1000 R_2 (0.5)}{1000 R_2}$$

$$R_{eq} = 200 \Omega$$

$$R_2 = 250 \Omega$$

Back to ~~t < 0~~ $t > 0$

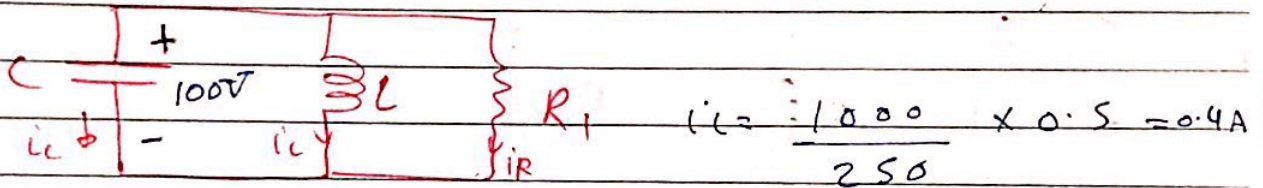

$$\frac{dv_c(t^+)}{dt} = \frac{i_c(t^+)}{C} = - \frac{[i_c(t^+) + i_R(t^+)]}{C} \text{ SA}$$
$$= - \frac{[0.1 + 0.4]}{1 \times 10^{-6}} = -500 \text{ rad/s}$$

$$\frac{dv(t^+)}{dt} = -0.5 \times 10^6 \text{ V/s}$$

$$v(t) = 100 = A_2$$

$$\left. \frac{dv}{dt} \right|_{t=0} = -500 e^{-500t} (A_1 t + A_2) + A_1 e^{-500t} \Big|_{t=0}$$

$$= -500 A_2 + A_1 = -0.5 \times 10^6$$


$$A_1 = -450,000$$

$$v(t) = e^{-500t} (100 - 450,000t)$$

$$t = 1 \text{ ms} = e^{-0.5} (100 - 450) = -2123 \text{ V}$$


* Driven Series RLC circuit :-

Ex. 8

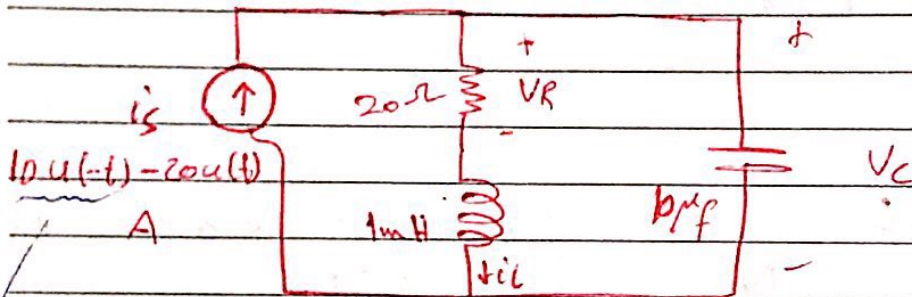

Find : $i_c(0^-)$, $v_C(0^+)$, $v_R(0^+)$, $i_c(\infty)$ and ~~$i_c(0.1 \text{ ms})$~~
 $i_c(0.1 \text{ ms})$

$t < 0$

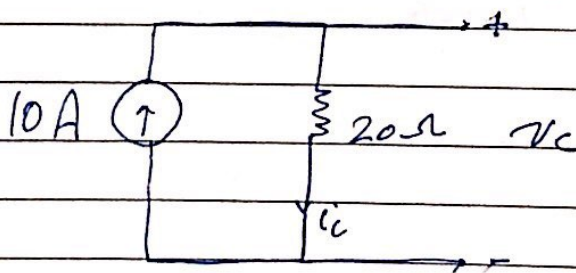


$$i_c(0^+) = i_c(0^-) = 10 \text{ A}$$

$$v_C(0^-) = 20 \times 10 = 200 \text{ Volt} = v_C(0^+)$$


$t > 0$

$10A = i_L$ (initial current)

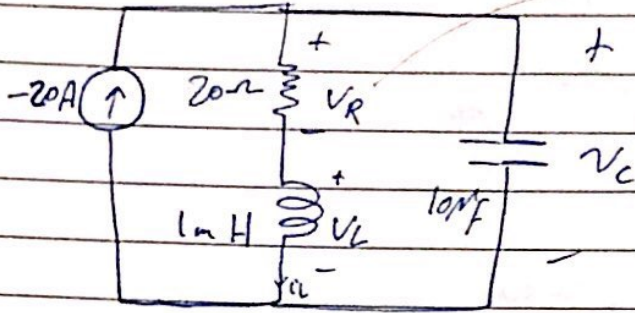$V_R(0^+) = i_L(0^+) \times 20 = 200 \text{ Volt}$



$t \rightarrow \infty$

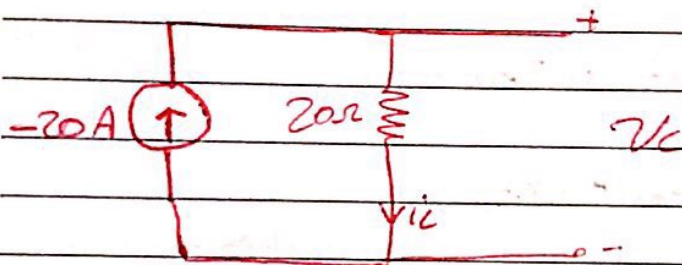

$i_L(\infty) = -20 \text{ A}$

$V_C(\infty) = -20 \times 20 = -400 \text{ V}$

$\alpha = \frac{R}{2L} = \frac{20}{2 \times 1 \times 10^{-3}} = 10,000 \text{ s}^{-1}$

$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10^{-3} \times 10 \times 10^{-6}}} = 10,000 \text{ rad/s}$

$\alpha = \omega_0 \rightarrow$ critically damped

$i_L(t) = i_n + i_p$

$= e^{-10000t} [A_1 t + A_2] - 20$

$$i(0^+) = 10 = A_2 - 20 \rightarrow A_2 = 30$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = -10000 e^{-10000t} [A_1 t + A_2] \Big|_{t=0}$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = -10000 A_2 + A_1 = 0$$

$$\frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{0}{L} = 0$$

$$v_C(0^+) = 200$$

$$v_R(0) = 200$$

$$v_C = v_R + v_L \text{ parallel}$$

$$A_1 = (10,000)(30) \rightarrow A_1 = 300,000$$

$$i(t) = -20 + e^{-10000t} [300,000 t + 30]$$

$t > 0$

$$i(0.1 \text{ ms}) = -20 + e^{-1} (30 + 30)$$


$$i(0.1 \text{ ms}) = 2.07 \text{ A}$$

CH9-CH10 :- sinusoidal steady-state Analysis :-


characteristics of sinusoidal :-

$$V(t) = V_m \sin(\omega t)$$

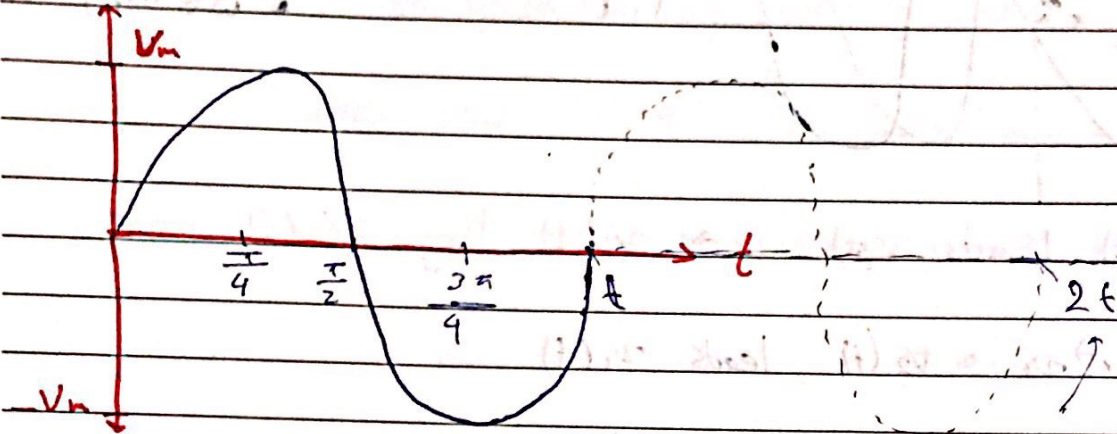$\sin A$
 $\sin(\omega t)$
 ωt (rad)
 ω (rad/sec)



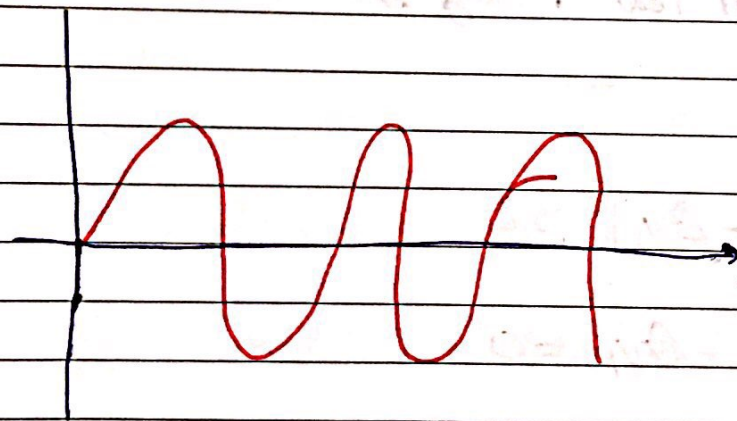periodical signal $\rightarrow V(t) = V(t+T)$



$$\omega T = 2\pi$$


$$\omega = \frac{2\pi}{T} \text{ rad/sec}$$

(radial frequency)

The frequency :-

$$f = \frac{1}{T} \text{ (Hertz) (Hz)}$$

$$\omega = 2\pi \cdot f$$

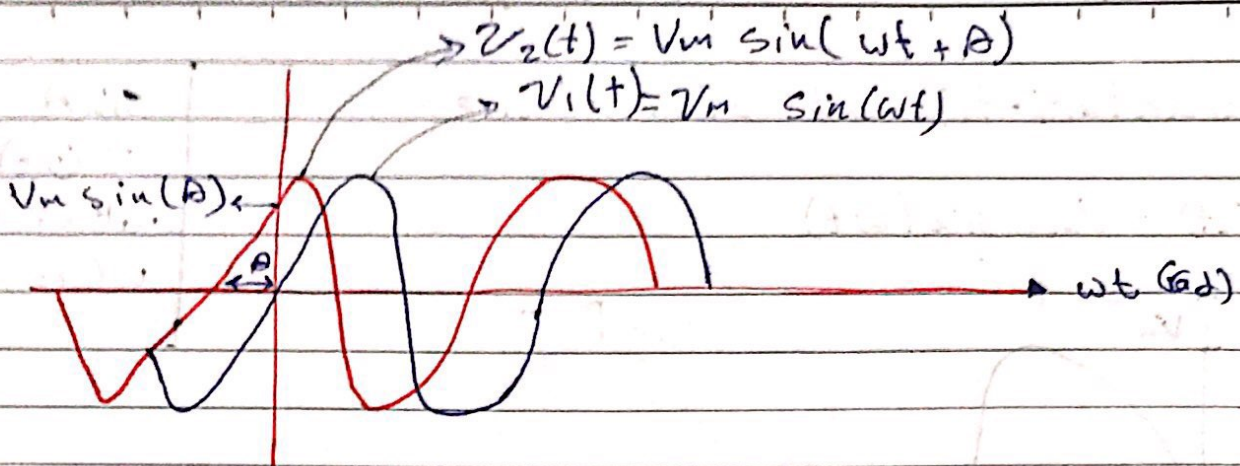

* $v_2(t)$ leads $v_1(t)$ * $v_1(t)$ lags $v_2(t)$

$\theta_2 - \theta_1 = \theta$ $v_2(t)$ leads $v_1(t)$

$\theta_1 - \theta_2 = -\theta$ $v_1(t)$ lags $v_2(t)$

$\theta - 0 = \theta$ $v_2(t)$ lead v_1 by θ

Phase angle:

out of phase $|\theta_2 - \theta_1| > 0$

in phase $\theta_2 - \theta_1 = 0$

Two sinusoidal waves whose phases are to be compared must


- 1) Both be written as \sin waves, or Both as \cos waves.
- 2) Both be written with positive amplitudes.
- 3) Each have the same frequency.

$$* -\sin \omega t = \sin(\omega t \pm 180^\circ) = \sin \omega t \overset{-1}{\cancel{\cos 180}} \pm \cos \omega t \overset{2 \times 90}{\cancel{\sin 180}}$$

$$-\sin(\omega t - 70^\circ) = \sin(\omega t - 70^\circ + 180^\circ) = \sin(\omega t + 110^\circ)$$

$$-\cos \omega t = \cos(\omega t \pm 180^\circ), \pm \cos(\omega t) = \sin(\omega t \pm 90^\circ)$$
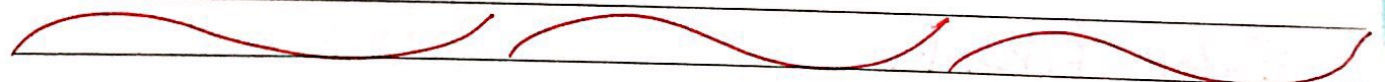
$$\mp \sin \omega t = \cos(\omega t \pm 90^\circ)$$



Ex 8 $v_1(t) = 120 \cos(120\pi t - 40^\circ) \text{ V}$

(a) $i_1 = 2.5 \cos(120\pi t + 20^\circ) \text{ A}$ (b) $i_1 = 1.4 \sin(120\pi t - 70^\circ) \text{ A}$



Find the angle at which v_1 leads i_1 :-

a) $\theta_{v_1} - \theta_{i_1} = -40 - 20 = -60^\circ$

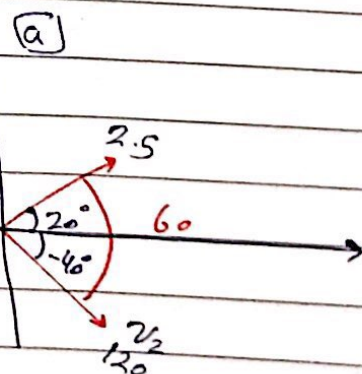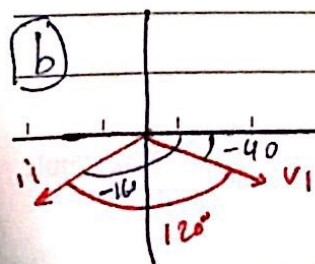b) $i_1 = 1.4 \cos(120\pi t - 70^\circ - 90^\circ)$

$$= 1.4 \cos(120\pi t - 160^\circ)$$

$$\theta_{v_2} - \theta_{v_1} = -40 - (-160) = 120^\circ$$




Complex Number 8-

$a + jb$ → imaginary part

↳
the real part

$$A = 3 + j4$$

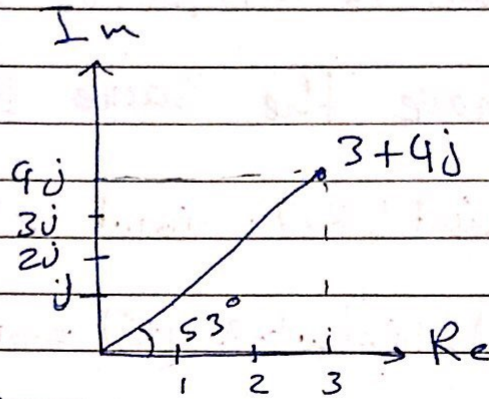

$$A = 3 + j4 = 5e^{j53}$$

$$= 5 [\cos(53) + j \sin(53)] = 3 + j4$$

Euler formula

$$e^{j\theta} = \cos\theta + j \sin\theta$$

↙ rectangular ↘ polar form

$$A = 3 + j4 = 5 \angle 53^\circ$$

$$B = -3 + j4 = 5 \angle 127^\circ$$

$$A+B = 0 + j8 = 8 \angle 90^\circ \quad / \quad A-B = 6 + j0 = 6 = 6 \angle 0^\circ$$

$$\frac{A}{B} = \frac{3+j4}{-3+j4} \times \frac{-3-j4}{-3-j4} = \frac{(3+j4)(-3-j4)}{A+16}$$

$$= \frac{-9 - j12 - j12 + 16}{25} = \frac{7 - j24}{25} = \frac{7}{25} - \frac{j24}{25}$$

$$\frac{A}{B} = \frac{5 \angle 53^\circ}{5 \angle 127^\circ} = \frac{5 e^{j53^\circ}}{5 e^{j127^\circ}} = \frac{5}{5} \angle 53^\circ - 127^\circ$$

$$= 1 \angle -74^\circ \rightarrow 1 \cos(-74^\circ) + j 1 \sin(-74^\circ)$$

$$A \cdot B = (3+j4) \cdot (-3+j4) = -9 + j12 - j12 - 16$$

$$= -25 = 25 \angle 180^\circ$$

$$\text{Rea}(S_2, S_3) = 3 + j4$$

$$\text{Pol}(3, 4) = 5 \angle 53^\circ$$





$$A \cdot B = 5 \angle 53^\circ \cdot 5 \angle 127^\circ$$

$$= 5 e^{j53^\circ} \cdot 5 e^{j127^\circ}$$

$$= 25 \angle 53^\circ + 127^\circ = 25 \angle 180^\circ$$

The complex forcing function:-

$$V_m \cos(\omega t + \theta)$$

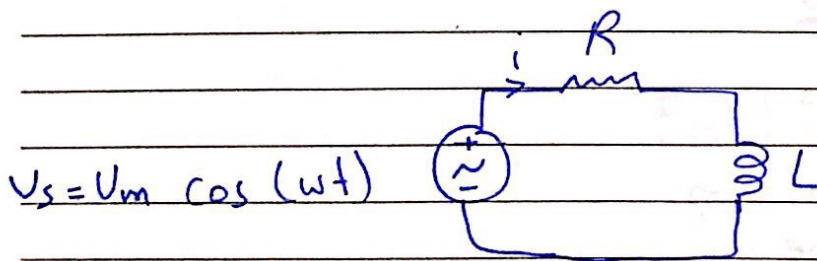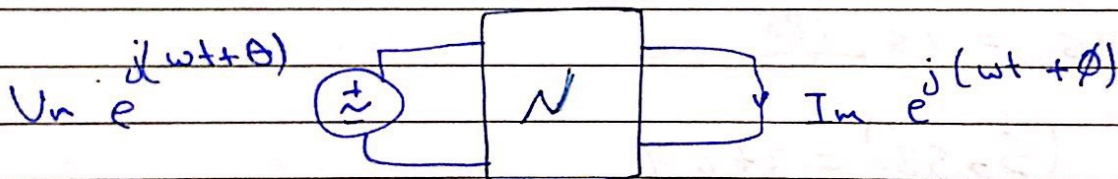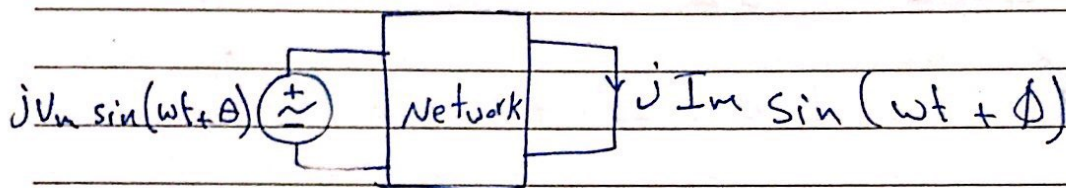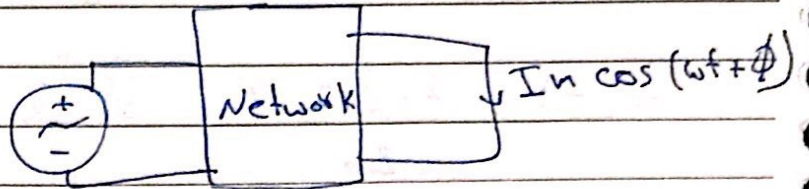

$$V_m \cos(\omega t) = \text{Re} \{ V_m e^{j\omega t} \}$$

$$I = I_m e^{j(\omega t + \theta)}$$

$$V_m e^{j\omega t} = V_m [\cos \omega t + j \sin \omega t]$$

$$= V_m \cos(\omega t) + j V_m \sin \omega t$$

$$Ri + L \frac{di}{dt} = V_s$$

$$R I_m e^{j(\omega t + \phi)} + j\omega L I_m e^{j(\omega t + \phi)} = V_m e^{j\omega t}$$

$$R I_m e^{j\phi} + j\omega L I_m e^{j\phi} = V_m$$

$$I_m e^{j\phi} = \frac{V_m}{R + j\omega L}$$

$$I_m \angle \phi = \frac{V_m}{R + j\omega L}$$

$$= \frac{V_m \angle 0^\circ}{\sqrt{R^2 + \omega^2 L^2} \angle \tan^{-1}\left(\frac{\omega L}{R}\right)}$$

$$= \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \left(\cos\left(\omega t - \tan^{-1}\left(\frac{\omega L}{R}\right)\right) \right) A$$


The ~~phasor~~ phasor -

$$v(t) = V_m \cos(\omega t) = V_m \cos(\omega t + 0^\circ)$$

$$V = V_m \angle 0^\circ \text{ V.}$$

$$V_m \cos(\omega t) = \operatorname{Re} \left\{ V_m e^{j(\omega t + 0^\circ)} \right\}$$
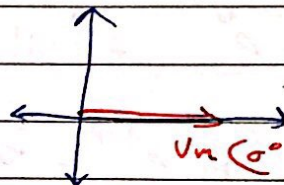
$$V_m e^{j0^\circ} = V_m \angle 0^\circ \text{ V}$$




$$i(t) = I_m \cos(\omega t + \phi)$$

$$I = I_m \angle \phi \text{ A.}$$


Ex: $V = 115 \angle -45^\circ \text{ V}$ with $\omega = 500 \text{ rad/sec}$ Find $V(t)$:

$$V(t) = 115 \cos(500t - 45^\circ) \text{ V.}$$

*the resistor

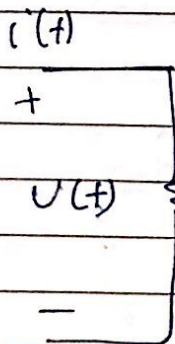

time domain

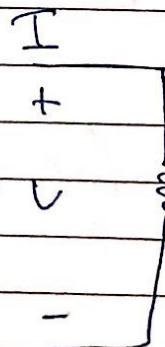

phasor domain

$$V = iR$$

$$v(t) = R i(t) \longrightarrow V(t) = V_m e^{j(\omega t + \theta)}$$

$$i(t) = I_m e^{j(\omega t + \phi)}$$


$$V_m e^{j(\omega t + \theta)} = R i(t) = R I_m e^{j(\omega t + \phi)}$$

$$V_m e^{j\theta} = R I_m e^{j\phi}$$

$$V_m \angle \theta = R I_m \angle \phi$$

$$\boxed{V = RI}$$

* The inductors -

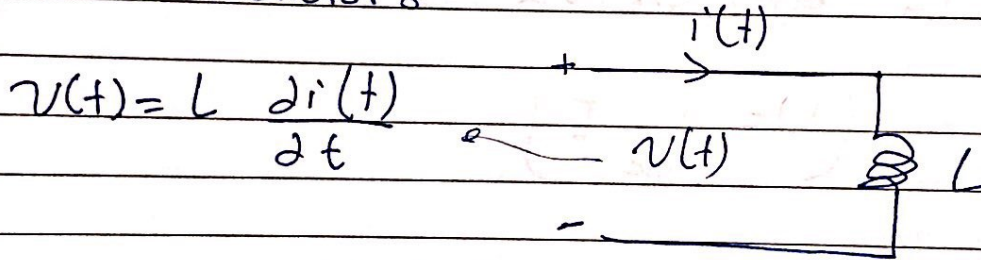

$$v(t) = L \frac{di(t)}{dt}$$


$$V(t) = V_m e^{j(\omega t + \theta)} = L \frac{d}{dt} (I_m e^{j(\omega t + \phi)})$$

$$V_m e^{j(\omega t + \theta)} = j\omega L I_m e^{j(\omega t + \phi)}$$

$$V_m e^{j\theta} = j\omega L I_m e^{j\phi}$$

$$V_m \angle \theta = j\omega L I_m \angle \phi$$


$$\boxed{V = j\omega L I}$$

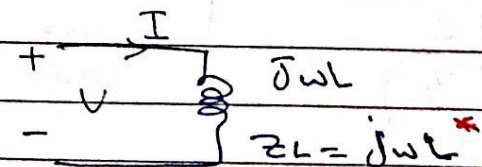

The impedance of L $\Rightarrow Z_L = j\omega L \Omega$

$$\boxed{Z = \frac{V}{I}}$$

The capacitor :-

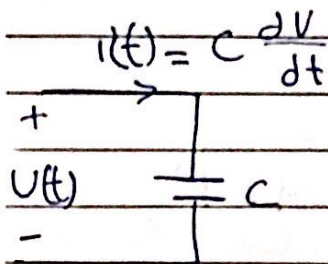

$$i = C \frac{dV}{dt}$$


$$I_m e^{j(\omega t + \phi)} = C \frac{d}{dt} (V_m e^{j(\omega t + \theta)})$$

$$I_m e^{j(\omega t + \phi)} = j\omega C V_m e^{j(\omega t + \theta)}$$


$$I_m \angle \phi = j\omega C V_m \angle \theta$$


$$I = j\omega C V$$

$$V = \frac{1}{j\omega C} I$$

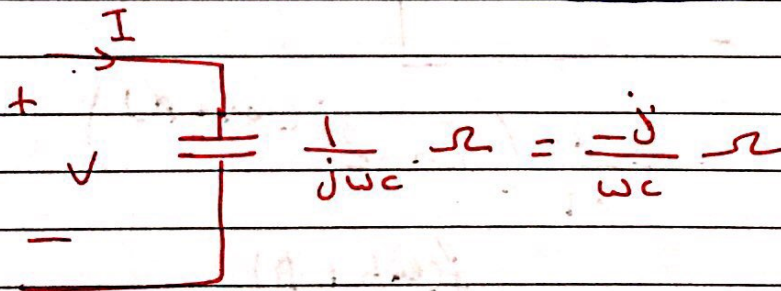

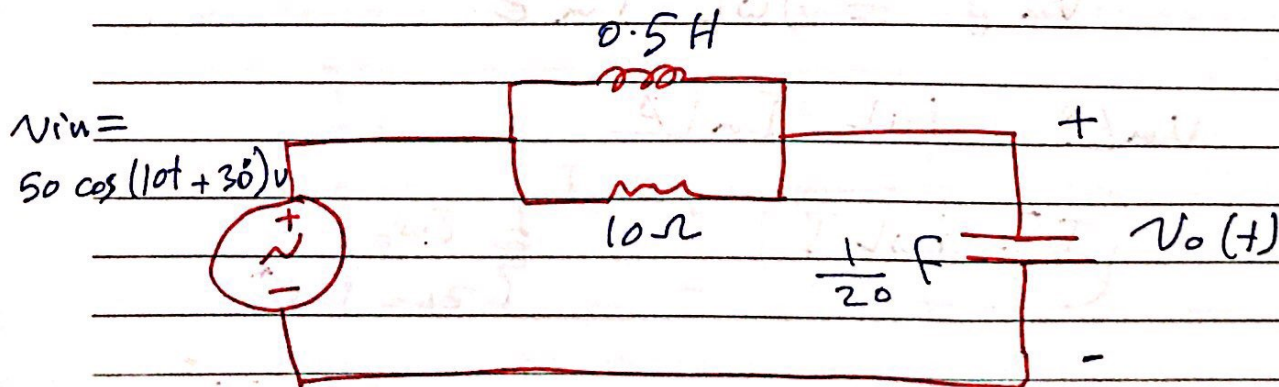Ex Find $v_o(t)$ in the circuit showing -



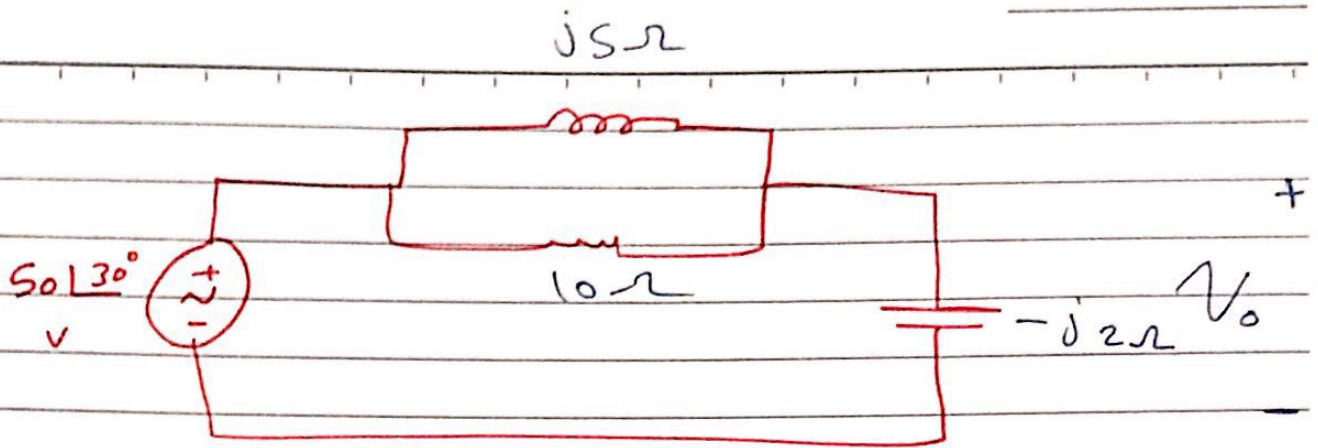

$$Z_L = j10(0.5) = j5 \Omega$$

$$Z_C = \frac{-j}{10 \frac{1}{20}} = -j2$$

parallel // $\rightarrow \frac{j5 \times 10}{10 + j5} = \frac{j50}{11.18 \angle 26.57^\circ} = 4.47 \angle 63.43^\circ \Omega = 2 + j4 \Omega$

Voltage Division

$$V_o = \frac{-j2}{2 + j4 - j2} \times 50 \angle 30^\circ$$


\downarrow
 $2 + j2$

$$V_o = \frac{2 \angle -45^\circ \cdot 50 \angle 30^\circ}{2.83 \angle 45^\circ} = 35.34 \angle -105^\circ \text{ V}$$

Back from phasor
to time domain

$$V_o(t) = 35.34 \cos(10t - 105^\circ) \text{ V}$$

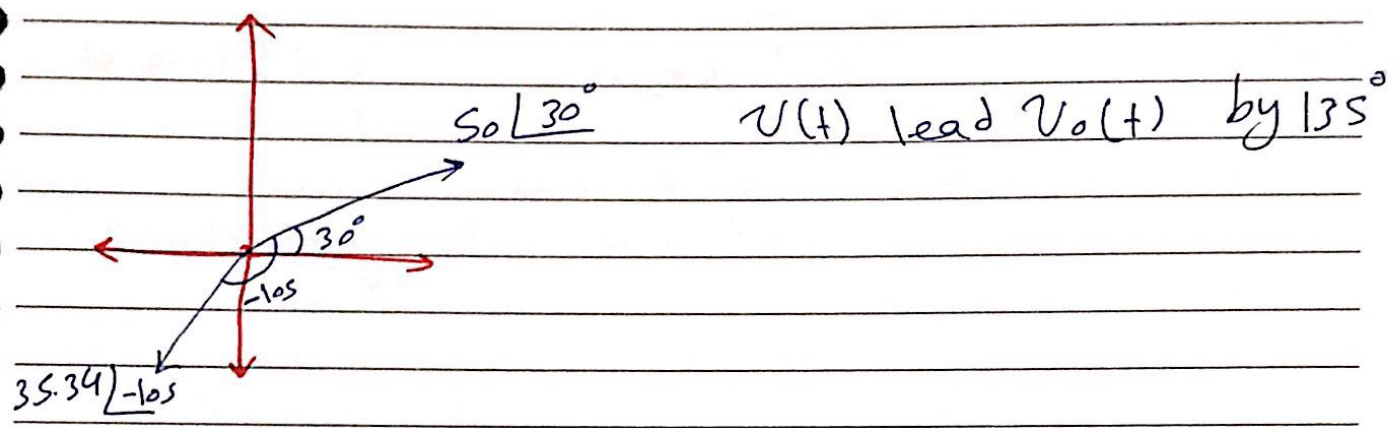Draw phasor diagram for $v_i(t)$ and $v_o(t)$



The impedance $Z = \frac{V}{I}$

$$Z = R \pm jX$$

↙ resistance
↘ reactance


The Admittance Y

$$Y = \frac{I}{V} = \frac{1}{Z} \text{ Siemens (S)}$$

$$Y = G \pm jB$$

↙ conductance (S)
↘ susceptance (S)

Ex:-

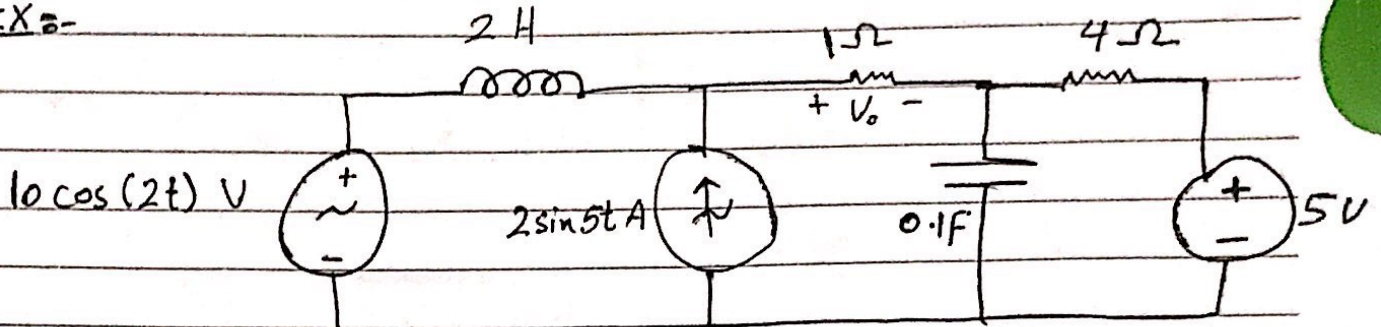

Find $V_o(t)$:- (use superposition)
* ~~~~~

Notes:-

$$V(t) = V_m \cos(\omega t + \theta)$$

DC $\omega = 0$


$$R \rightarrow R$$

$$L \rightarrow j\omega L$$

$$C \rightarrow \frac{-j}{\omega C} = \frac{-j}{(0)C} = \infty$$

$$j(0)L = 0 \Omega$$


Solu:-

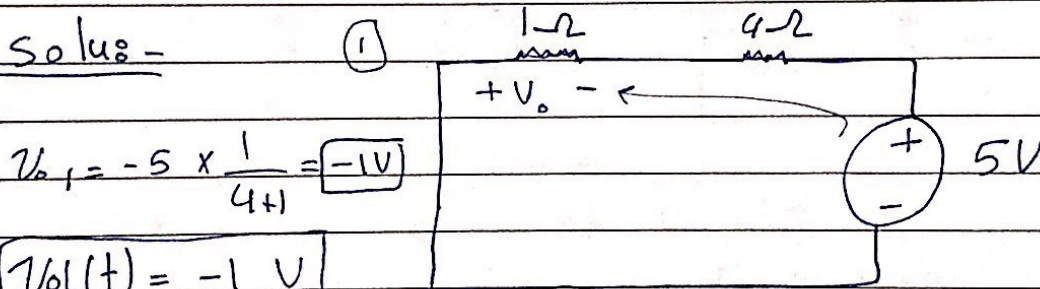

$$V_{o1} = -5 \times \frac{1}{4+1} = -1V$$

$$V_o(t) = -1V$$

$\omega = 2 \text{ rad/sec}$

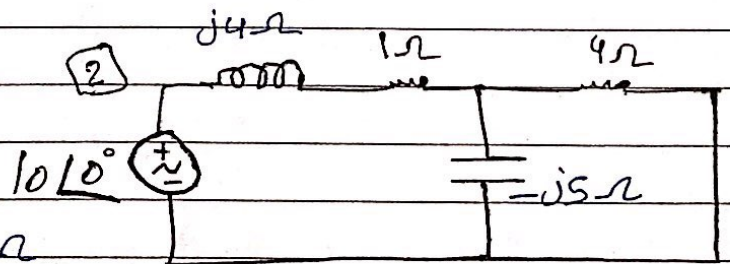

$$2H \rightarrow j(2)(2) = j4 \Omega$$

$$0.1F \rightarrow \frac{-j}{0.1 \times 2} = -j5 \Omega$$

$$\parallel \rightarrow \frac{4(-j5)}{4-j5} = \frac{-20j}{4-j5} \text{ after Polar form } = 2.439 - j1.951 \Omega$$


calculator

$$V_{o2} = \left(\frac{1}{1 + j4 + 2.434 - j1.951} \right) (10 \angle 0^\circ)$$

$$= \frac{10 \angle 0^\circ}{3.434 + j2.044} = 2.498 \angle -30.79^\circ \text{ V}$$

$$V_{o2}(t) = 2.498 \cos(2t - 30.79^\circ) \text{ V}$$

3

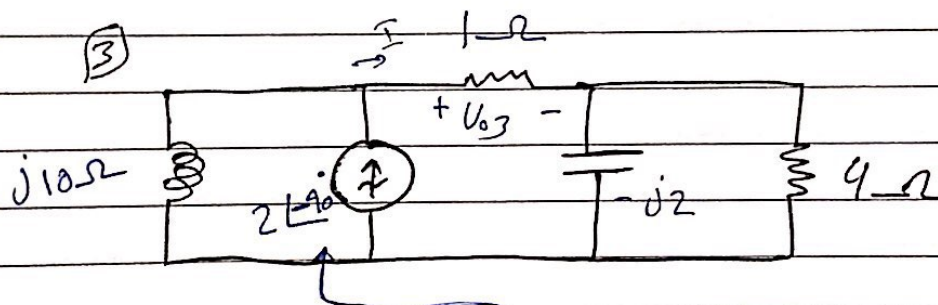

$2 \sin 5t \rightarrow 2 \cos(5t - 90^\circ)$ بـلـكـة
 $\omega = 5 \text{ rad/sec}$

$2 \text{ H} \rightarrow j(s)(2) = j10 \Omega$

$0.1 \text{ F} \rightarrow \frac{-j}{0.1 \times 5} = -j2$

$-j2 \parallel 4 \rightarrow \frac{-j2 \times 4}{4 - j2} = 0.8 - j1.6 \Omega$

$$I = \frac{j10}{j10 + 1 + 0.8 + -j1.6} \cdot 2 \angle -90^\circ = \frac{10 \angle 90^\circ \cdot 2 \angle -90^\circ}{1.8 + j8.4} = 2.328 \angle -80^\circ \text{ A}$$

$V_{o3} = 2.328 \angle -80^\circ \times 1 = 2.328 \angle -80^\circ \text{ V} \Rightarrow V_{o3}(t) = 2.328 \cos(5t - 80^\circ) \text{ V}$

$V_o(t) = V_{o1}(t) + V_{o2}(t) + V_{o3}(t)$
 $= -1 + 2.498 \cos(2t - 30.79^\circ) + 2.328 \cos(5t - 80^\circ) \text{ V}$