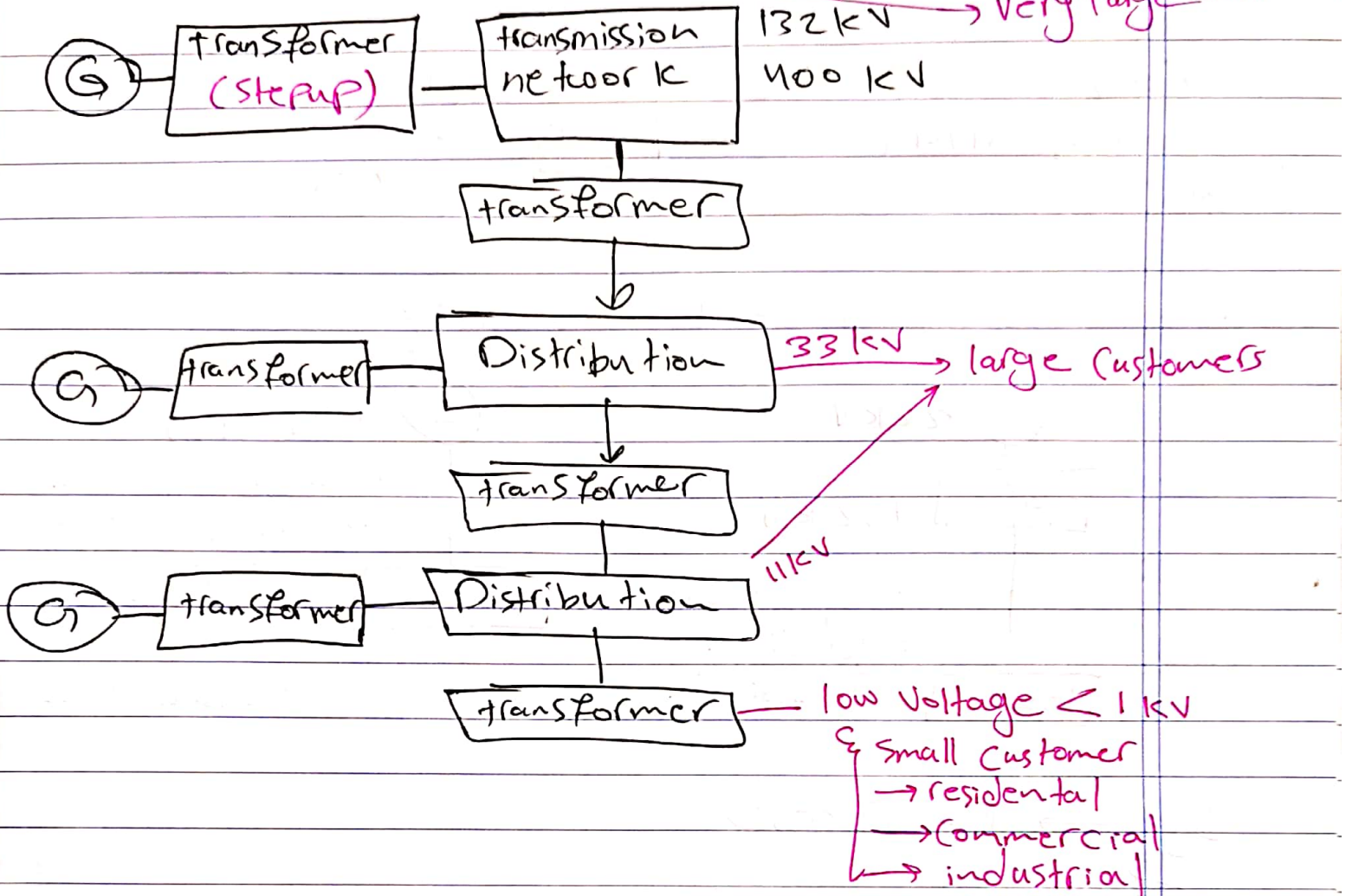


\*\* power 1 :-

\*\* structure & power systems.



\*\* Why 50 or 60 Hz?

- reactance in inductor in (generators, lines ...)

$$X_L = 2\pi fL, \text{ as } f \text{ increases, } X \text{ increases}$$


So when  $X_L$  is great, a greater voltage drop occurs.

- flicker
- reactance in capacitance



$$X_C = \frac{1}{2\pi fC}$$

• Power losses =  $P_u + P_e$  → both types of losses are directly proportional to frequency.

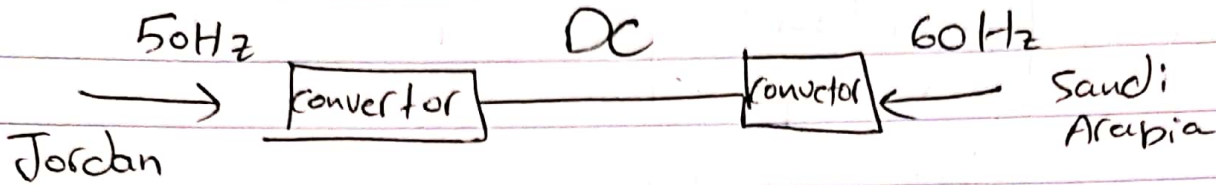→ To connect systems of different frequencies, converters are used.



\*\* Why Such variety of Voltage levels?

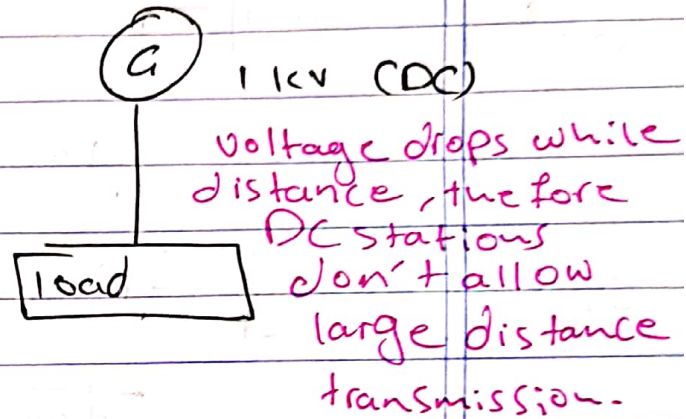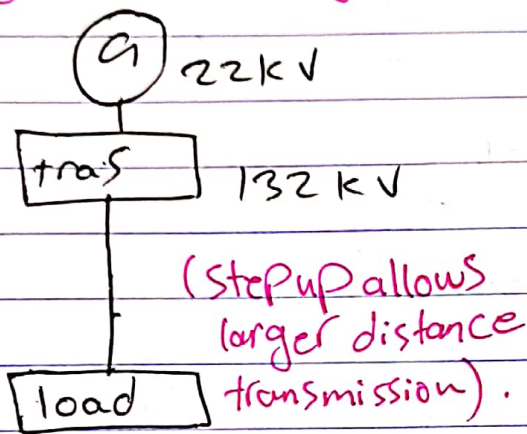


Load  $\rightarrow P = VI \cos \theta$   
 $I \phi$

$V \uparrow \rightarrow I \downarrow \rightarrow \text{losses (lines)} = I^2 R \downarrow$

→ higher voltages reduce losses, but have higher Capital Cost.

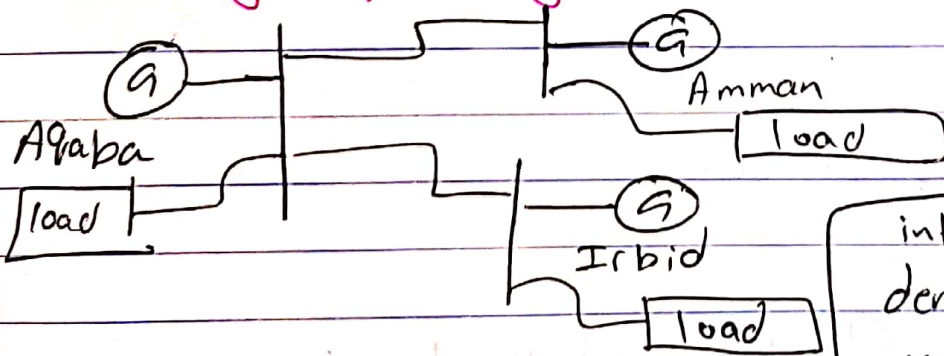
\*\* Why is power system interconnected with other systems?



\*\* Systems are interconnected to fulfill demand as a whole, as no generator fulfill on its own.

→ more generators are put for emergency cases.

# Daily load curve (profile)

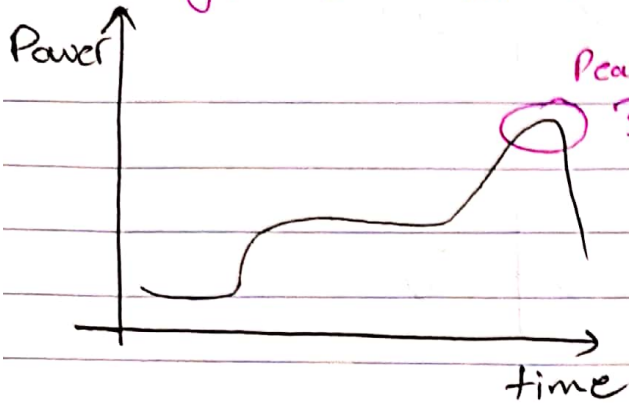


"Independent System Operator"  
ISO

ensures that load = generation  
 ↳ to preserve  
 $f = 50 \text{ Hz}$


## Single line diagram

Generator (G)

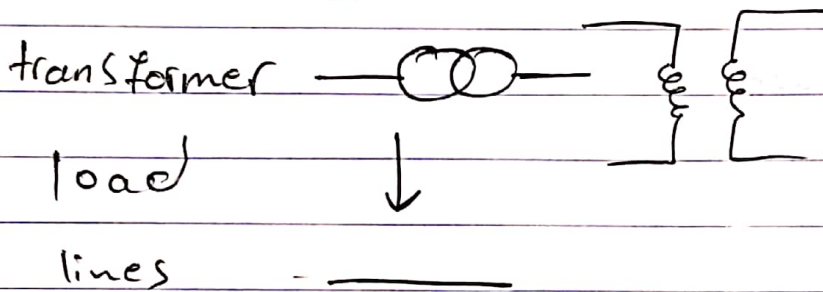


Motor (M)


Circuit breaker / switch

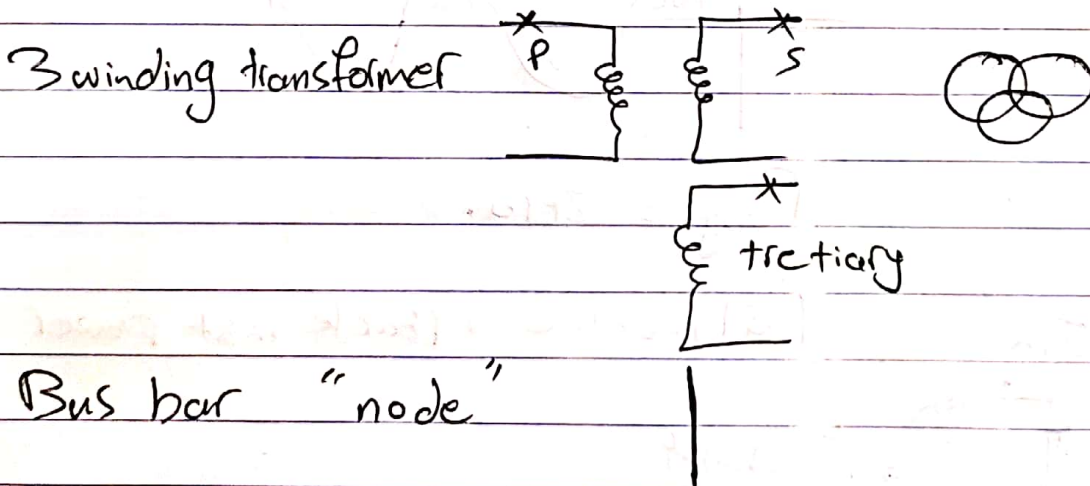

## Radial (single line)

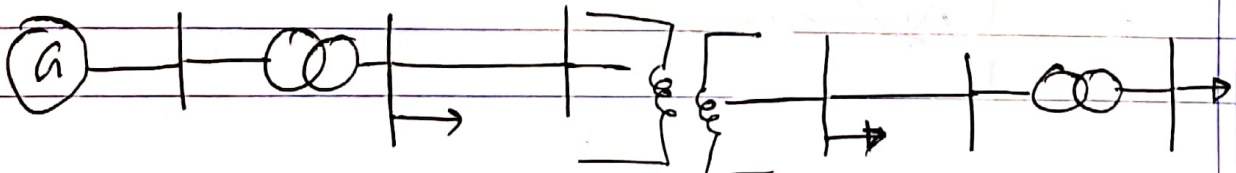

**Mesh 1**

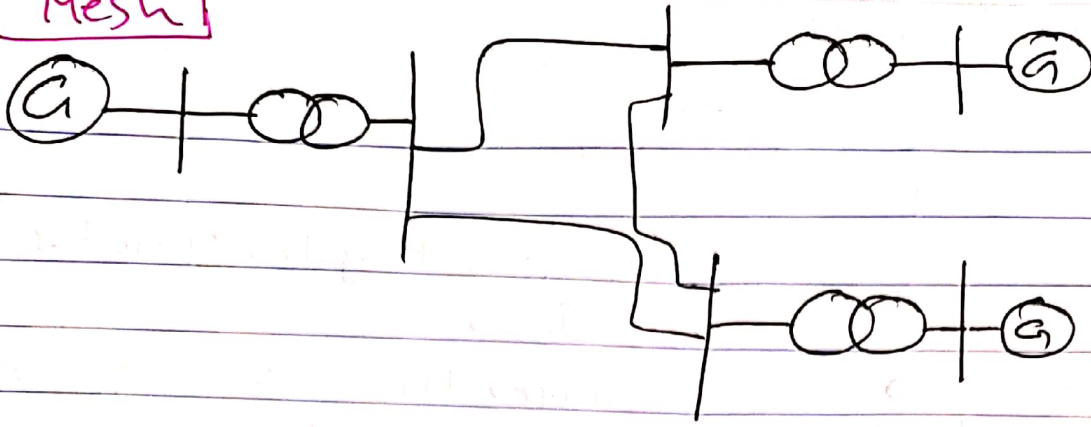


**Circuits 2 Review**

$$Z = R + jX$$

$$Y = \underbrace{G}_{\text{Conductance}} + j \underbrace{B}_{\text{Susceptance}}$$


Admittance

$$Y = \frac{1}{Z}$$

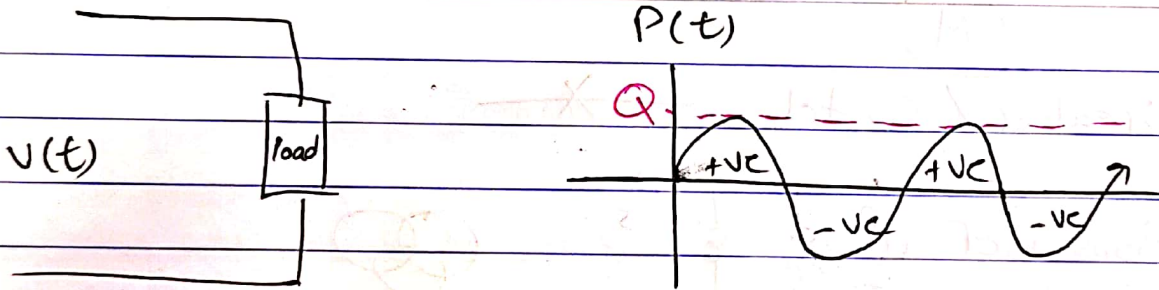

$$P_{avg} = \text{Zero}$$

$|Q|$  reactive = Peak inst Power

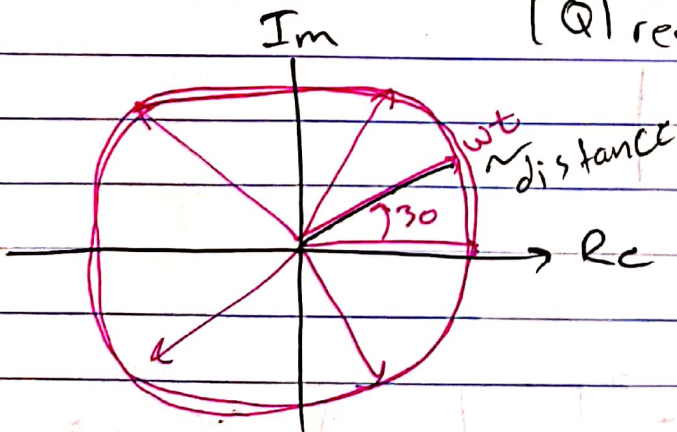


# Revision

## [1] phasor




$$v(t) = \underbrace{V_m \cos(\omega t + \Theta)}_{\text{time}} \rightsquigarrow \underbrace{V_m \angle \Theta}_{\text{Phasor}}$$

$$v(t) = \text{Re} \{ V_m e^{j\omega t} e^{j\Theta} \}$$

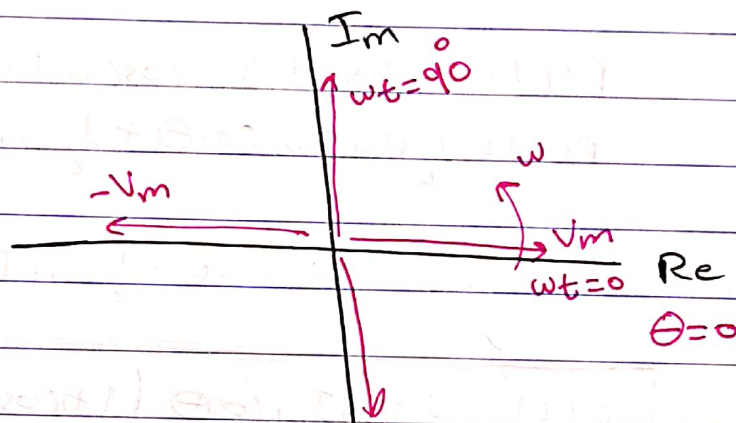
$$\text{when } \Theta = \text{zero} \Rightarrow \text{Re} \{ V_m e^{j\omega t} \}$$




$$V_m \cos(\omega t)$$

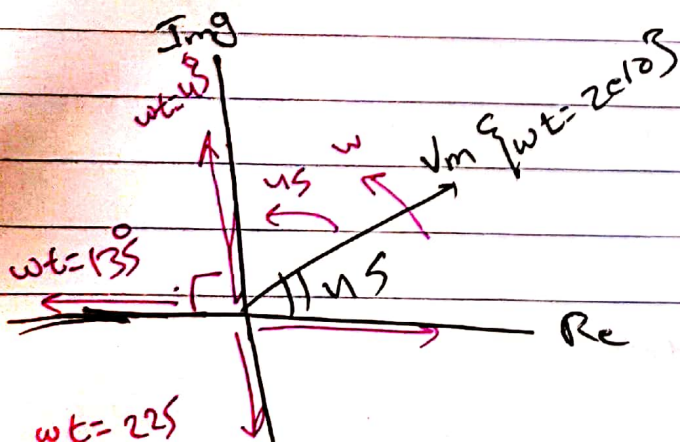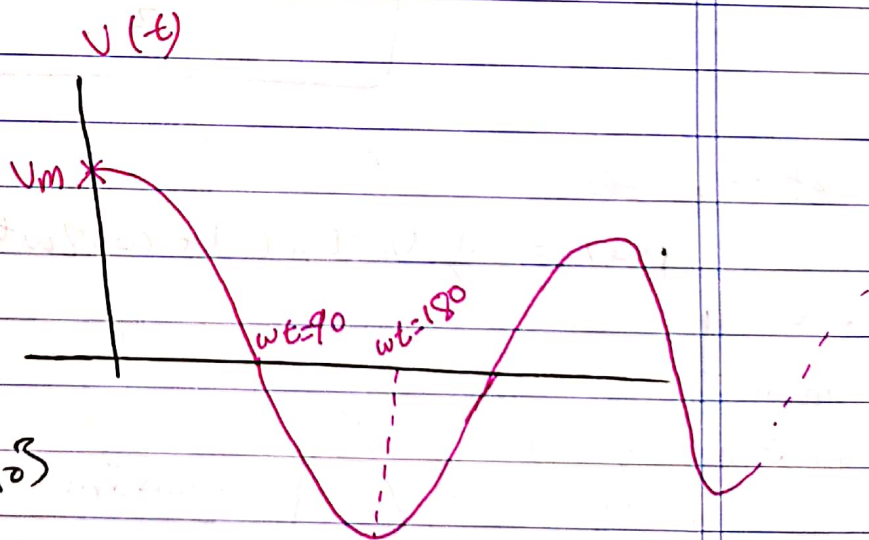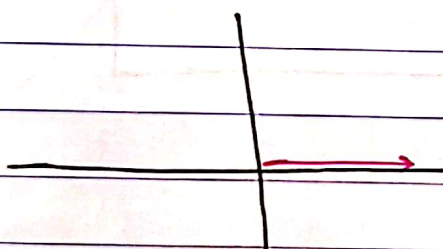
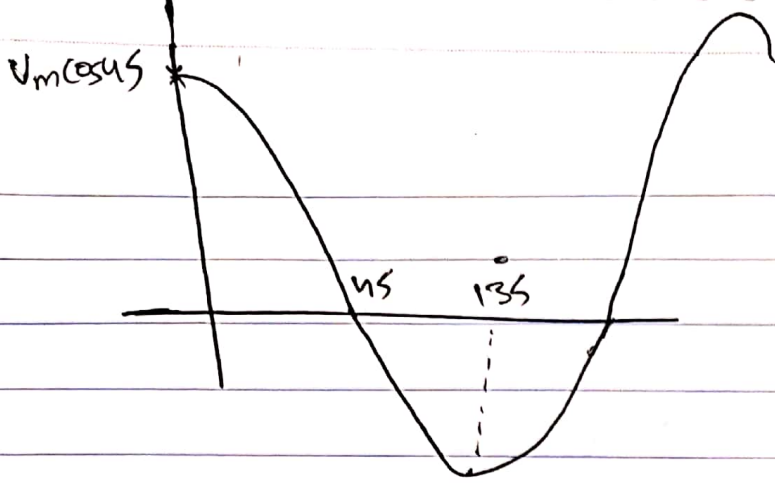
$$\Rightarrow v(t) = V_m \cos(\omega t + 45) = \text{Re} \{ V_m e^{j\omega t} e^{j45} \}$$



**\*\* Power , reactive power**

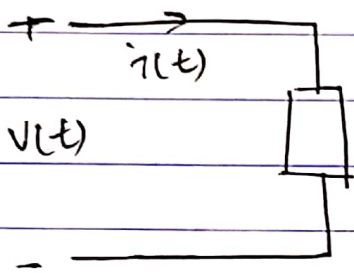

let  $P(t) = V(t) i(t)$   
 $V(t) = V_m \cos(\omega t)$   
 $i(t) = I_m \cos(\omega t + \theta)$

$$P(t) = V_m \cos \omega t I_m \cos(\omega t + \theta)$$


$$P(t) = \frac{1}{2} V_m I_m \cos \theta + \frac{1}{2} V_m I_m \cos(2\omega t + \theta)$$

$$P(t) = \frac{1}{2} V_m I_m \cos \theta + \frac{1}{2} V_m I_m \cos 2\omega t - \frac{1}{2} V_m I_m \sin \theta \sin 2\omega t$$

$$P(t) = \frac{1}{2} V_m I_m \cos \theta (1 + \cos 2\omega t) - \frac{1}{2} V_m I_m \sin \theta \sin 2\omega t$$

let  $\theta = 0$
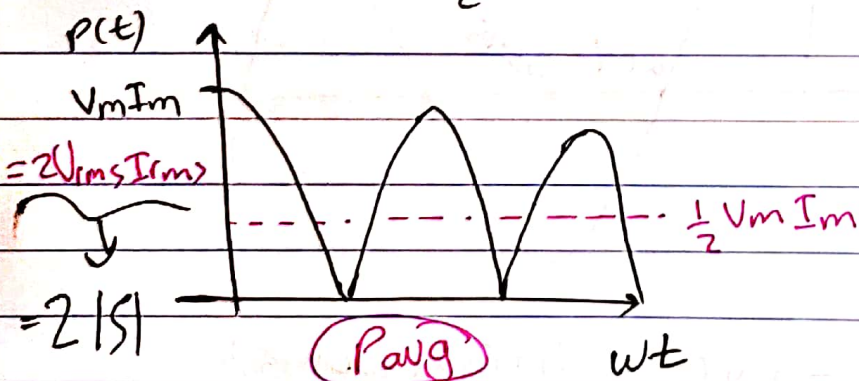
$$P(t) = \frac{1}{2} V_m I_m (1 + \cos 2\omega t)$$




$= 2 |S|$   
 $= 2$  apparent power

$V_{rms} = \frac{V_m}{\sqrt{2}}$	$ S  = V_{rms} I_{rms}$
$I_{rms} = \frac{I_m}{\sqrt{2}}$	


$\underline{L} \quad \theta = -90 \rightarrow P(t) = \frac{1}{2} V_m I_m \sin 2\omega t$

**Q reactive Power**

$\frac{1}{2} V_m I_m$   
 Q (Peak)

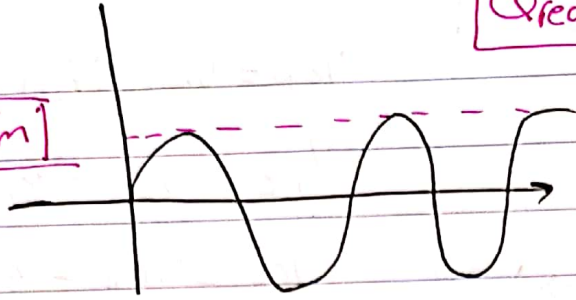


avg = 0

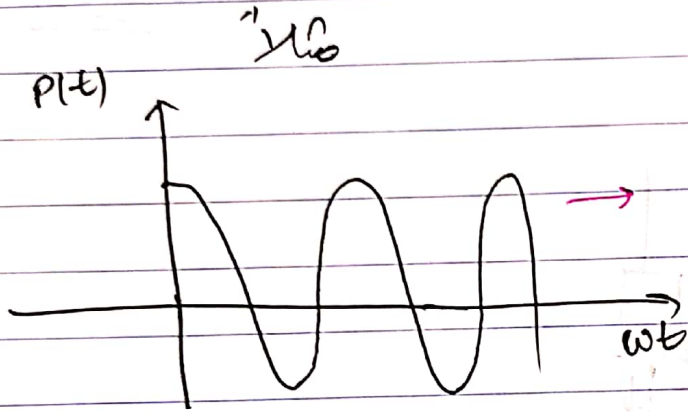


- ① Avg Power  
 ② from peak-to-peak  
 apparent power

Q

\*remember

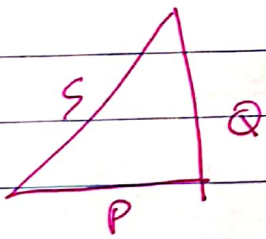

\*\* 3-phase system

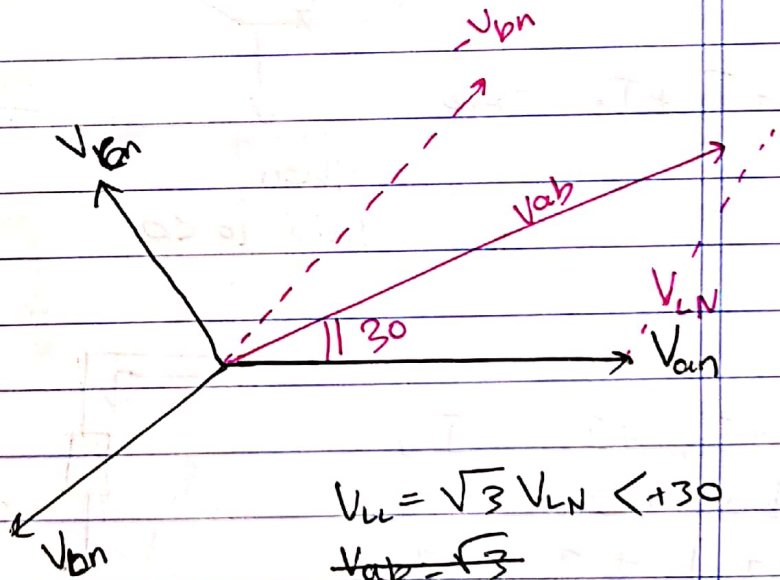


$V_{LL} = \sqrt{3} V_{LN} \angle +30$


$V_{ab} = \sqrt{3} V_{an}$

$V_{ab} = V_{an} - V_{bn}$

$V_{ab}, V_{bc}, V_{ca}$  }  $120^\circ$

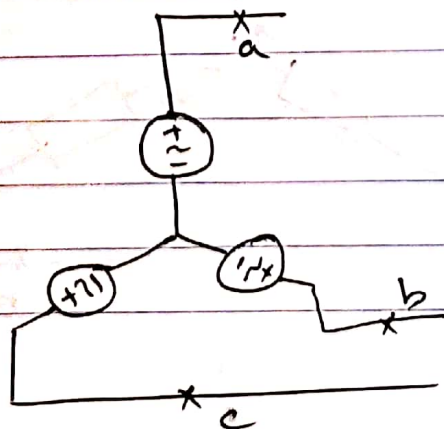
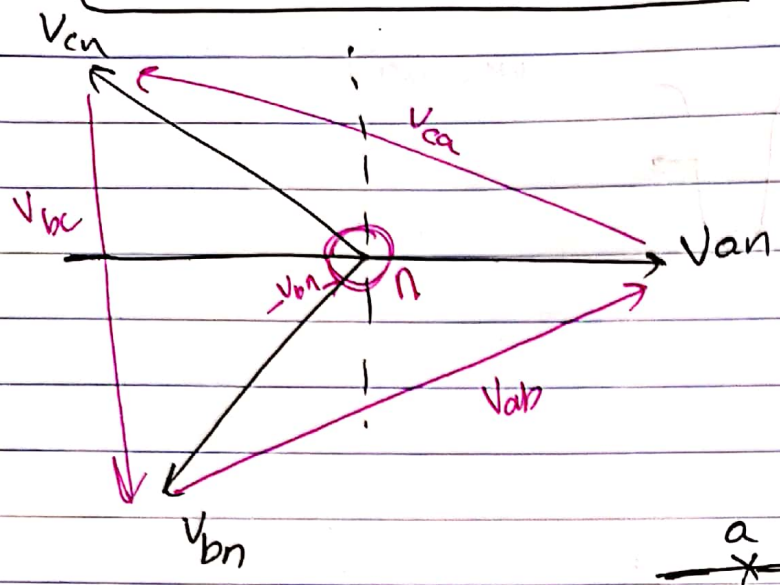
$$S_3\phi = 3S_1\phi = \sqrt{3} V_L I_L$$




$$V_{ab} = V_{an} - V_{bn}$$

$$V_{bc} = V_{bn} - V_{cn}$$

$$V_{ca} = V_{cn} - V_{an}$$

$$V_{ab} + V_{bc} + V_{ca} = \text{zero} \rightarrow \underline{\underline{KVL}}$$

ungrounded neutral

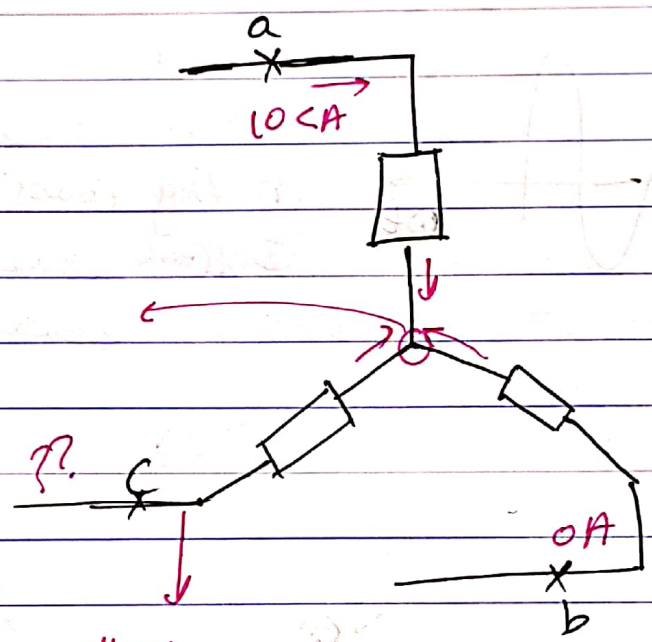


$$I_a + I_b + I_c = \text{zero}$$

then this is 0 < 0

$$I_a + I_b + I_c = I_N$$


→ balanced

$$I_a + I_b + I_c = \text{zero}$$

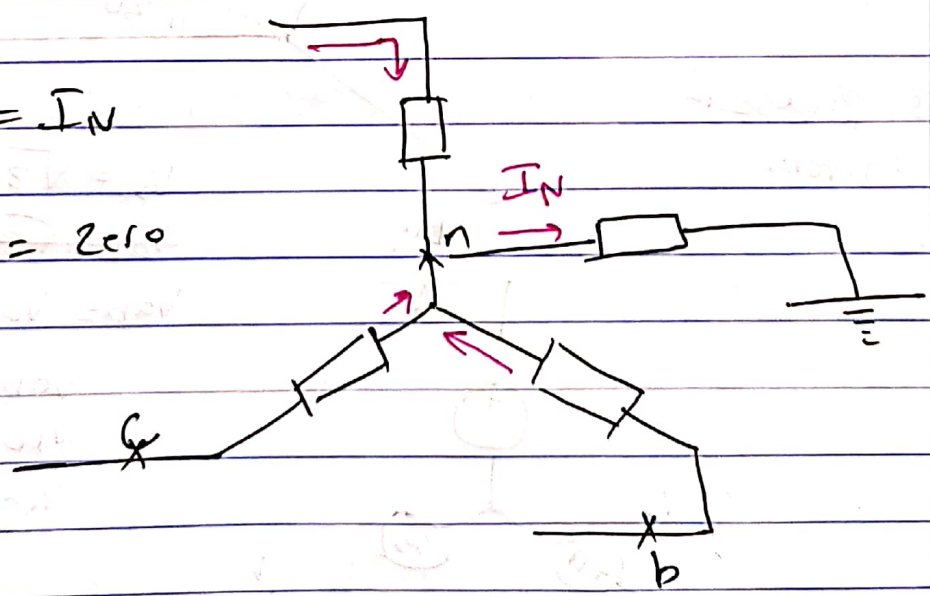







# LV "low voltage"

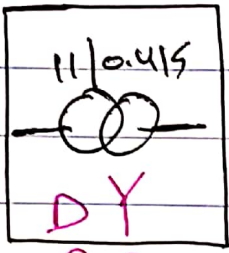

11 kV  
0.415 kV

↓  
3 phase  
4 wires

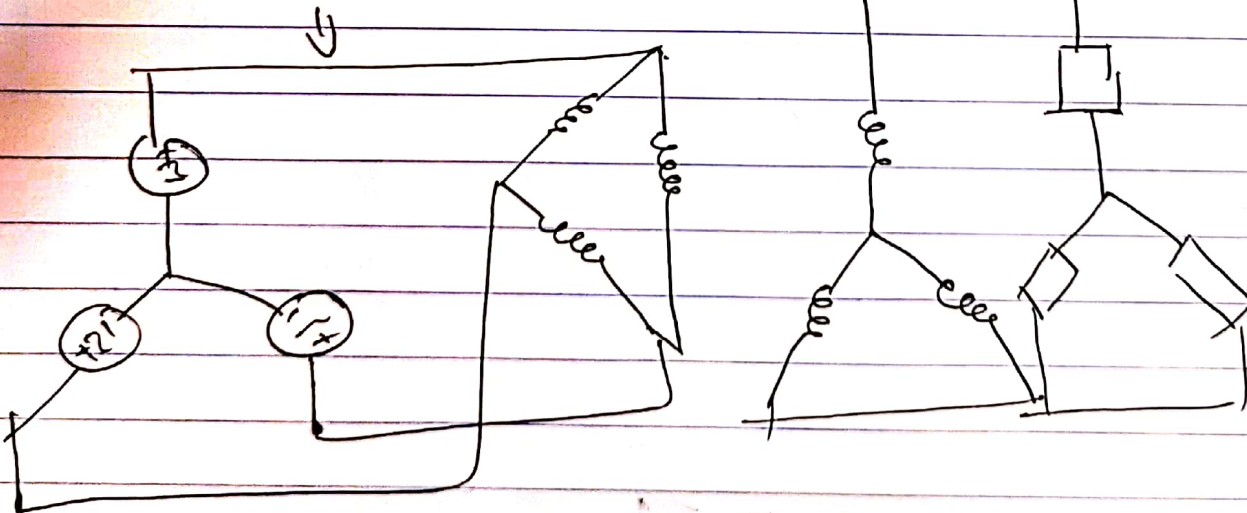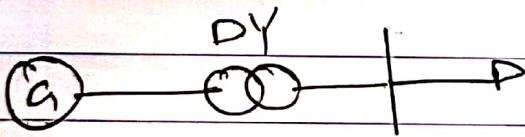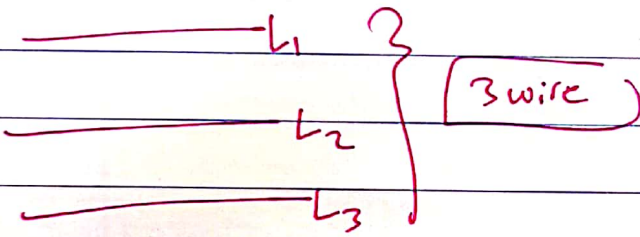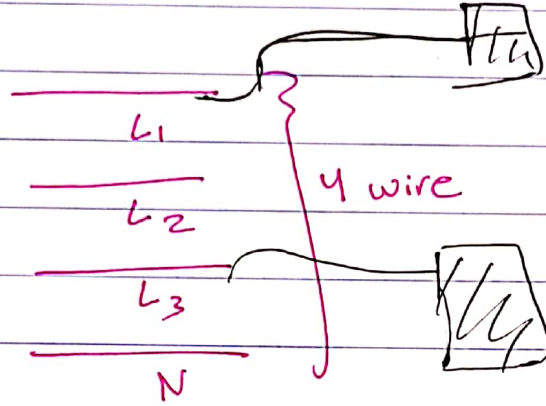


3-phase

\* Power System analysis

- power flow  
↳ V, I, P
- fault analysis

## \*\* Per unit Systems

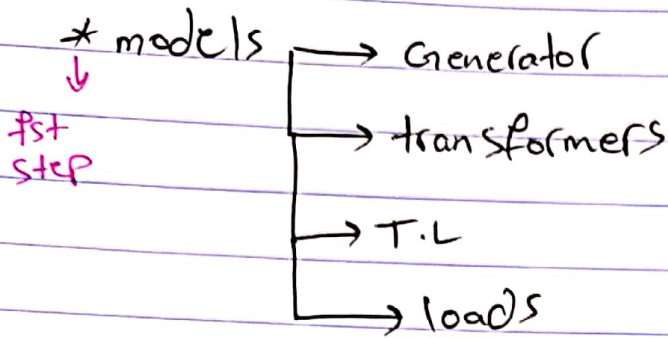

$$\text{Per unit} = \frac{\text{Actual}}{\text{Base}}$$

let  $V = 240\text{V}$ ,  $V_{\text{Base}} = 230 \Rightarrow V_{\text{p.u.}} = \frac{240}{230} \text{ p.u.}$   
(Voltage rise)

let  $V = 240 \times 0.2 \Rightarrow V_{\text{p.u.}} = \frac{240}{230} \times 0.2 \text{ p.u.}$


\* why using per unit system is easier?


□ Power System  $\Rightarrow$  multi-voltage levels

33, 11, 6.6 kV, 3.3 kV, 0.4 kV

$\Rightarrow$  impedance of the transformer depends on the side which it is observed.

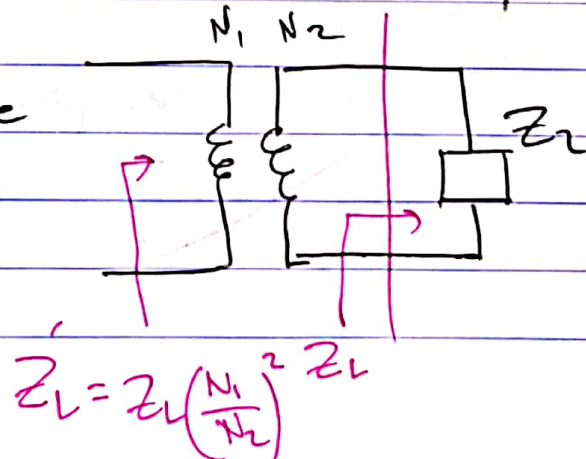
↳ Equipments with the same type have the same p.u impedance regardless of size.



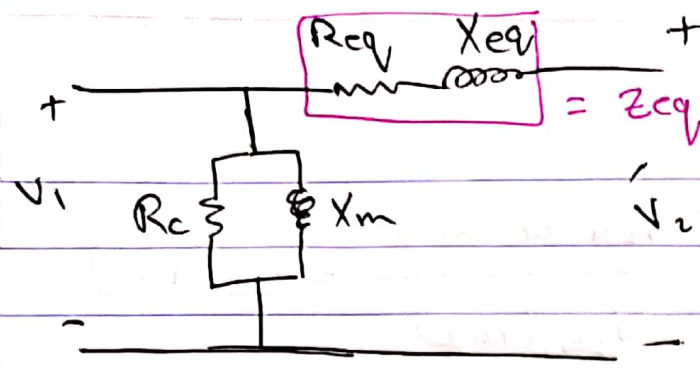

- \* 250 kVA, 11/0.415 kV
  - \* 630 kVA, 11/0.415 kV
  - \* 100 kVA, 11/0.415 kV
  - \* 100 kVA, 11/0.415 kV
- } Same  $Z_{eq}$  (P.u)  $\approx 4\% - 6\%$

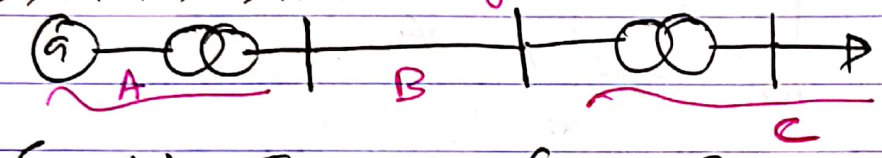
- \* 10 MVA, 33/11 kV
  - \* 25 MVA, 33/11 kV
- }  $Z_{eq}$  (P.u)  $\approx 15\%$



$S, V, I, Z$  {Base}

$\rightarrow 3\phi$

$$S = \sqrt{3} V_L I_L$$

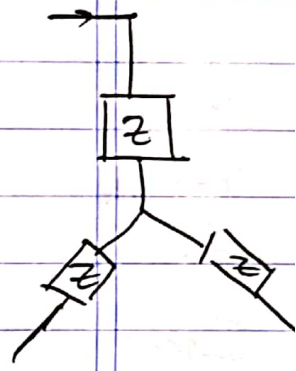

$$I_{base} = \frac{S_{base}}{\sqrt{3} V_{L-L, base}}$$

$$Z_{base} = \frac{V_{L-N, base}}{I_{base}} = \frac{(V_{L-L, base})/\sqrt{3}}{S_{base}/(\sqrt{3} V_{L, base})}$$

$$Z_{base} = \frac{(V_{L-L, base})^2}{S_{base}}$$

$$S_{actual} = \sqrt{3} V_L I_L$$

$$S_{p.u} = \frac{S_{actual}}{S_{base}} = \frac{\sqrt{3} V_L I_L}{\sqrt{3} V_{L, base} I_{base}}$$



\* we use  $\sqrt{3}$  with actual values only

$$|S_{p.u}| = |V_{p.u}| |I_{p.u}|$$



$$S_{p.u} = V_{p.u} I_{p.u}^*$$

$$V_{LL}(\text{P.u.}) = V_{LN}(\text{P.u.})$$
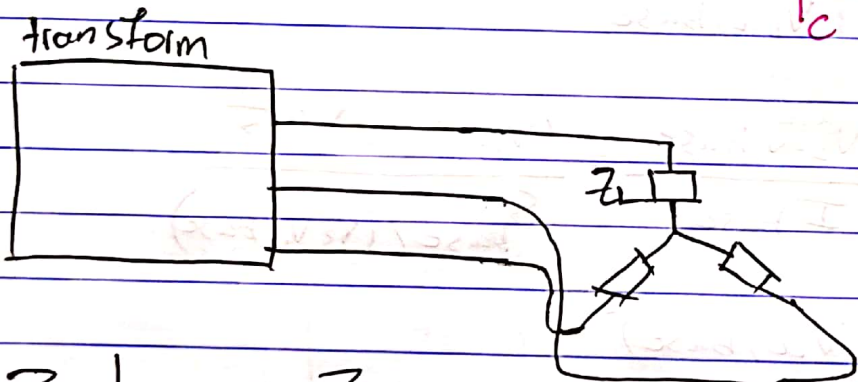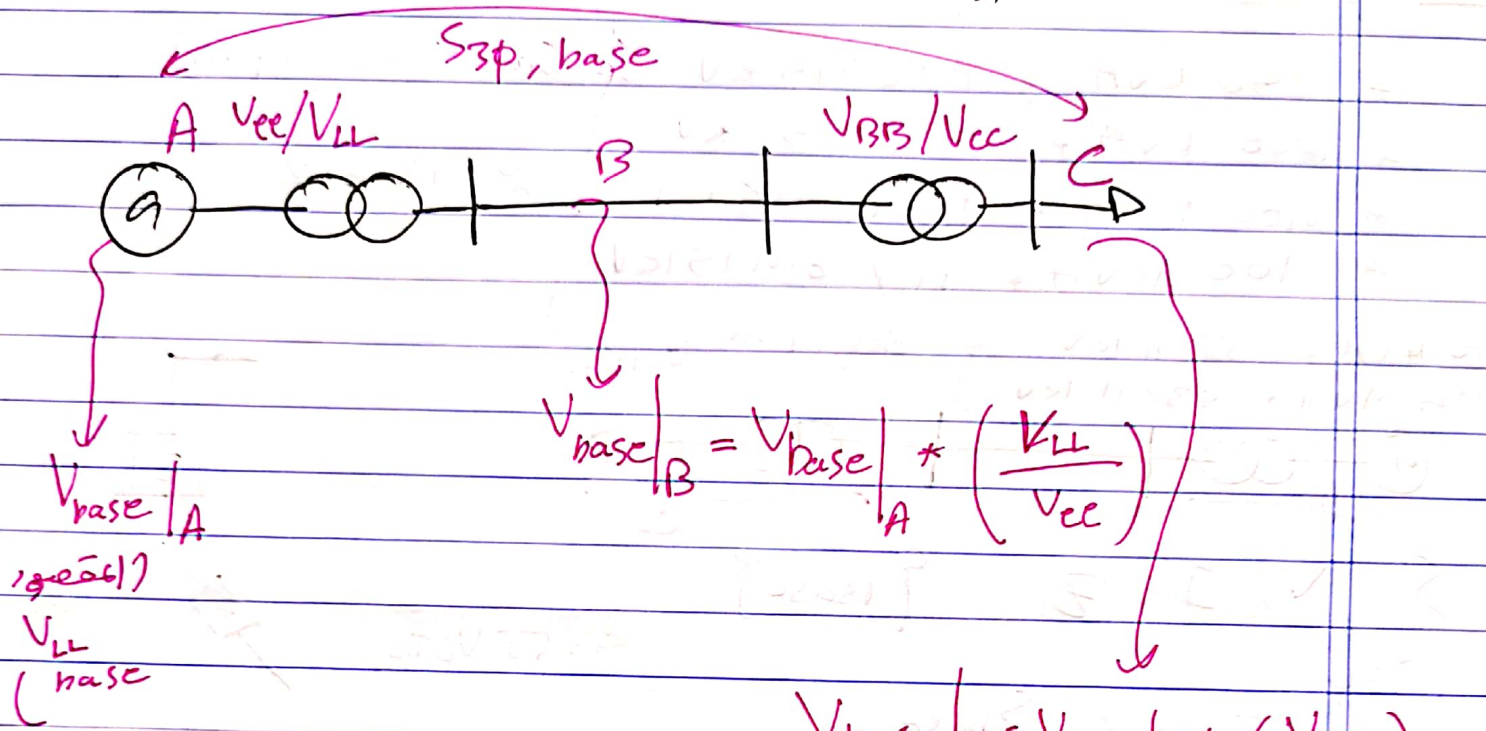
$$V_{LL}(\text{P.u.}) = \frac{V_{LL}(\text{actual})}{V_{LL \text{ base}}} = \frac{\sqrt{3} V_{LN}(\text{actual})}{\sqrt{3} V_{LN}(\text{base})} = V_{LN}(\text{P.u.})$$




$$Z_L|_{\text{P.u.}} = \frac{Z_L}{Z_{\text{base}}}$$

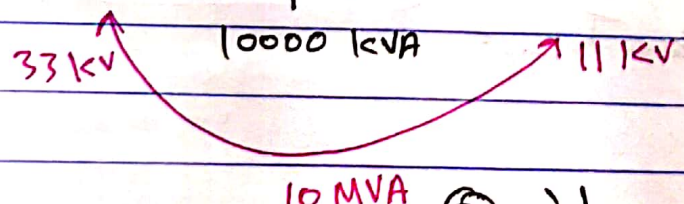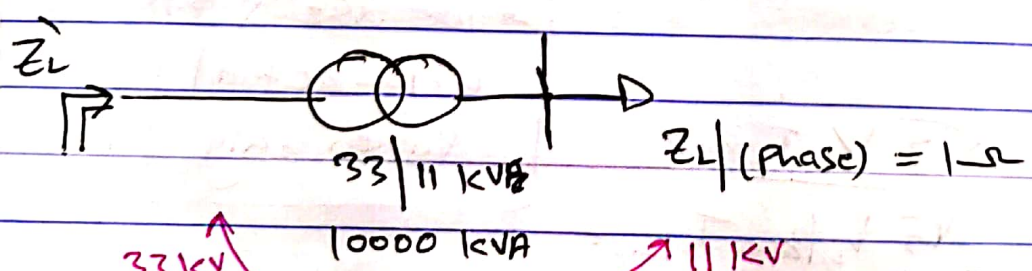

$$\textcircled{1} Z_L(\text{P.u.}) = \frac{1}{(11)^2 / 10} = \frac{10}{(11)^2} \text{ P.u.}$$

$$\textcircled{2} Z_L'|_{\text{P.u.}} = \frac{Z_L'}{Z_{\text{base}}} = 1 * \left( \frac{33}{11} \right)^2$$

$$Z_L \Big|_{p.u} = \frac{9}{(33)^2/10} = \frac{10}{(11)^2} = Z_L (p.u)$$

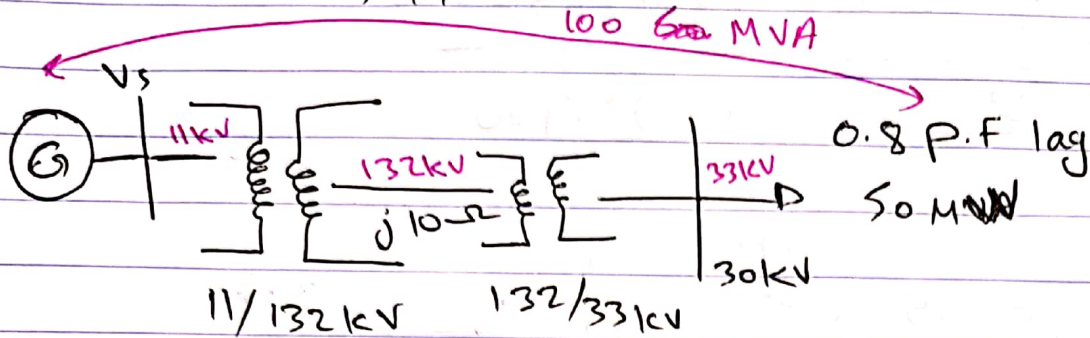

$11/132 \text{ kV}$        $132/33 \text{ kV}$   
 $50 \text{ MVA}$        $X = 12\%$       (choose  $100 \text{ MVA}$  as  
 $X = 10\%$        $50 \text{ MVA}$       base).

1- Find  $V_s$  required to maintain load voltage at  $30 \text{ kV}$ ??  
 "use p.u".

Sol.

$$Z_L (p.u) = \frac{j10}{(132)^2/100} = j0.575 \text{ p.u.}$$

$$T_1 \Rightarrow X = 10\% \quad [50 \text{ MVA}, 11 \text{ kV}/132 \text{ kV}]$$

$$X = ?? \quad [100 \text{ MVA}, 11/132]$$

$$X_{p.u}(\text{old}) \Rightarrow S_{\text{base, old}}, V_{\text{base, old}}$$

$$X_{p.u}(\text{new}) \Rightarrow S_{\text{base, N}}, V_{\text{base, N}}$$


$$X_{p.u}(\text{new}) = \frac{X(\text{actual})}{Z_{\text{base}}} = \frac{X_{p.u}(\text{old}) * \left( \frac{V_{\text{base, old}}}{V_{\text{base, new}}} \right)^2}{\frac{(V_{\text{base, new}})^2}{S_{\text{base, new}}}}$$

$$X_{p.u}(\text{new}) = X_{p.u}(\text{old}) * \left( \frac{S_{\text{base, new}}}{S_{\text{base, old}}} \right) * \left( \frac{V_{\text{base, old}}}{V_{\text{base, new}}} \right)^2$$

$$\frac{X}{T_1} = 0.1 * \left( \frac{100}{50} \right) * \left( \frac{11 \text{ kV}}{11 \text{ kV}} \right)^2 = 0.2$$

$$X(T_2) = 0.12 * \left(\frac{100}{50}\right) = 0.24$$
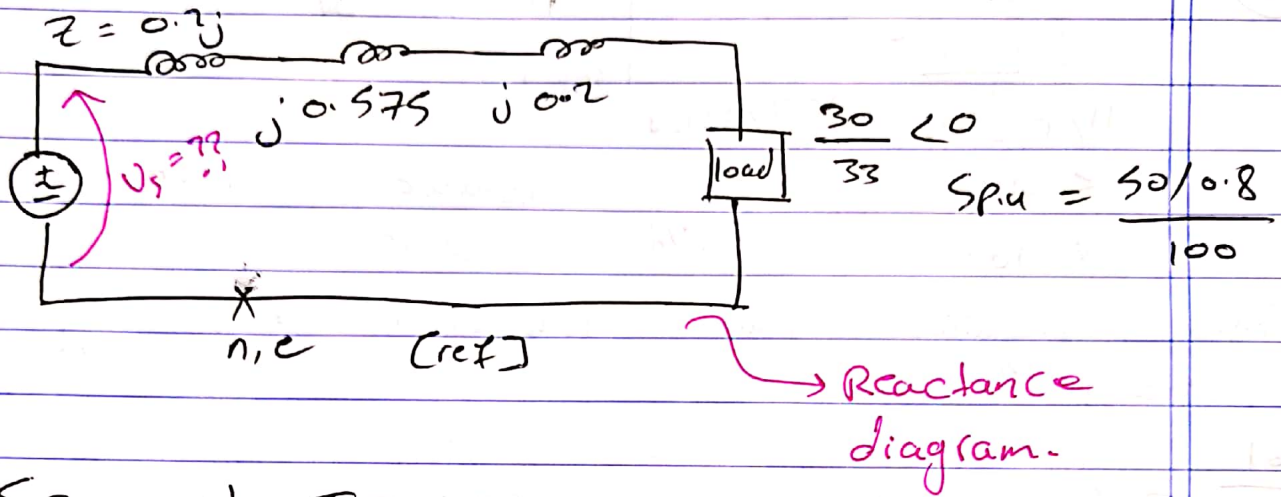
$$Z_{load} (P.u) = \frac{Z_{actual}}{Z_{base}} = \frac{(30)^2 / (50 / 0.8)}{(33)^2 / 100}$$



$$S_{pu} = V_{pu} I_{pu}$$


$$\frac{50/0.8}{100} = \frac{30}{33} I_{pu}$$

$$I_{pu} = 0.687 \angle -\cos^{-1}(0.8)$$

$$V_s = \frac{30}{33} \angle 0 + I (j0.2 + j0.575 + j0.2)$$

$$V_s = 1.328 + j0.558$$

$$V_s (actual) = 1.44 * (11 \text{ kV}) = 15.84 \text{ kV}$$

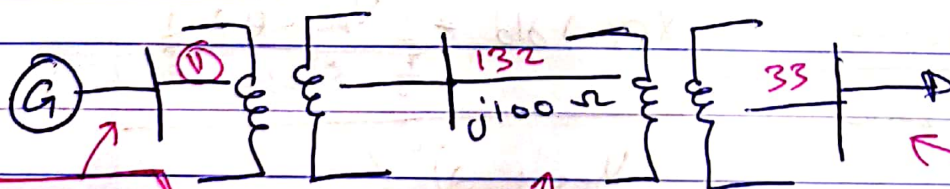


let 11.5 kV  
Base

$$\frac{11.5 * 132}{11}$$

$$\frac{11.5 * 132}{11} * \frac{33}{1.32}$$

$$T_1 \Rightarrow X_{P.u} (new) = 0.1 * \left(\frac{100}{50}\right) * \left(\frac{11}{11.5}\right)^2$$
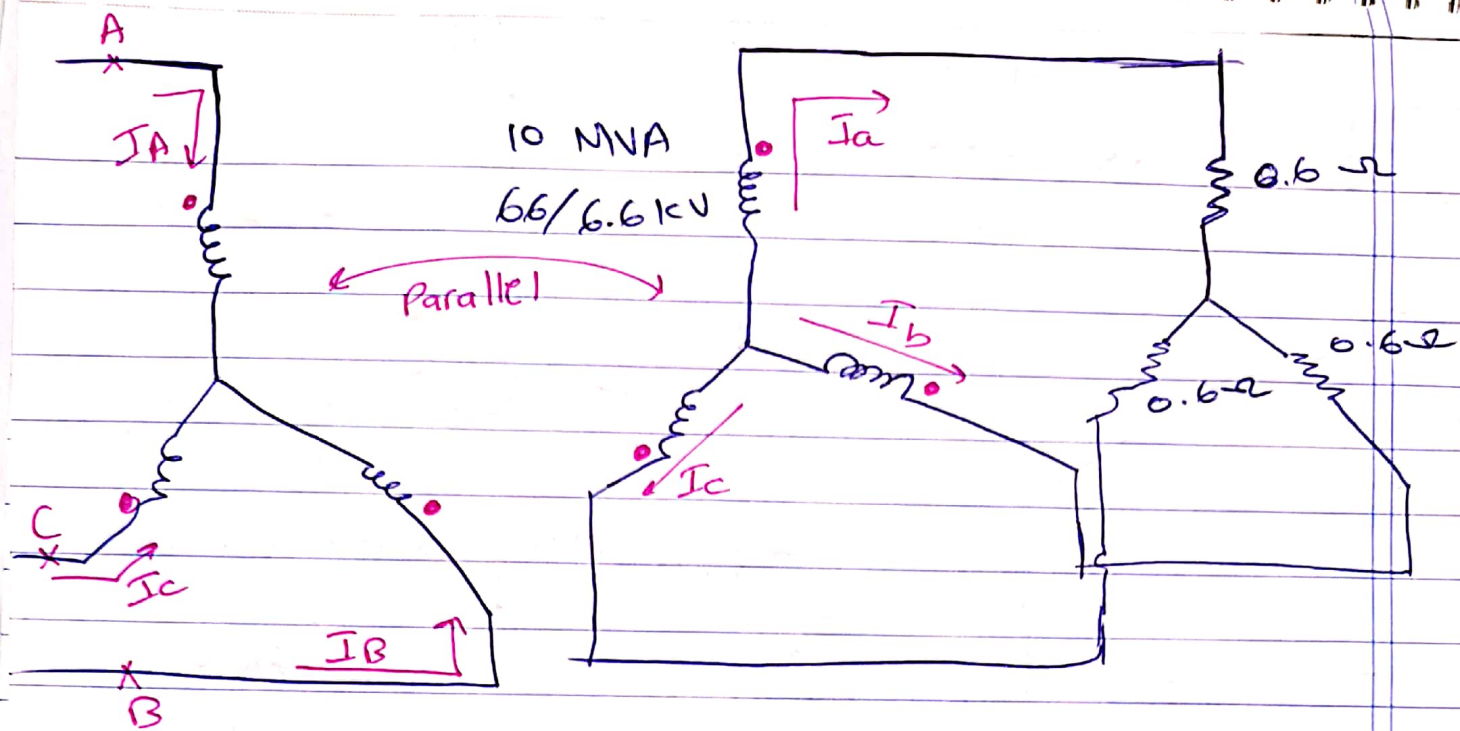
$$= 0.1 * \left(\frac{100}{50}\right) * \left(\frac{132}{11.5 * \frac{132}{11}}\right)^2$$




\*\*  $R_L (P.u) ??$  , rating of the transformer.

$$R_{P.u} = \frac{0.6}{(6.6)^2 / 10} = \underline{\underline{0.13 \text{ p.u}}}$$

on primary side

$V_{ee} / V_{LL} \rightarrow$  transformation ratio

$\rightarrow$  reflected impedance.

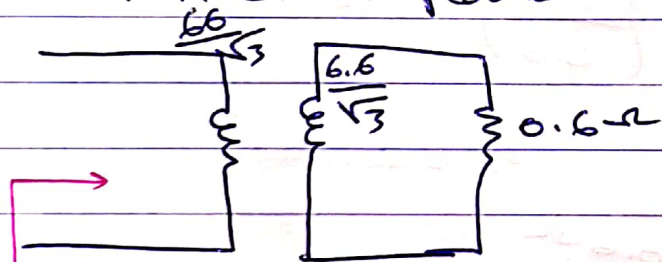



$V_p / V_\phi \rightarrow$  turns ratio  
 $\equiv \frac{n_1}{n_2}$

$\phi$  transform

$$R_p = 0.6 \left( \frac{66/\sqrt{3}}{6.6/\sqrt{3}} \right)^2 = 60 \Omega$$

$$R_p (P.u) = \frac{60}{(66)^2 / 10} = \underline{\underline{0.13 \text{ p.u}}}$$

10 MVA  
66/6.6 kV

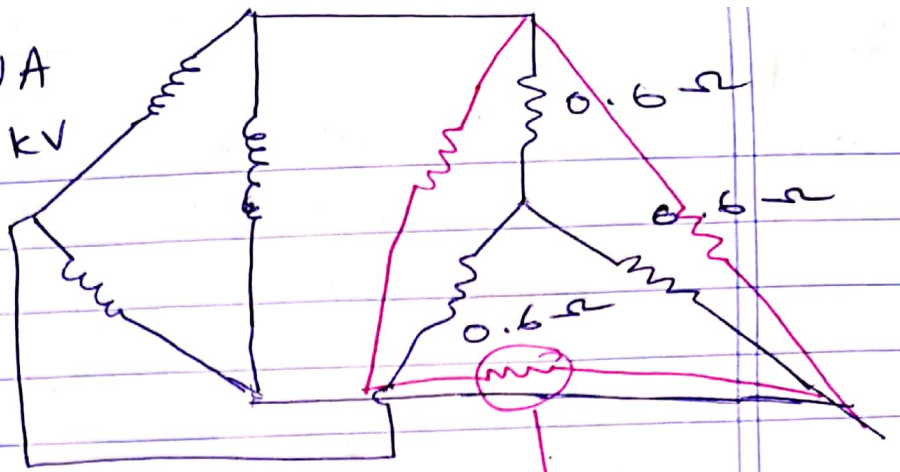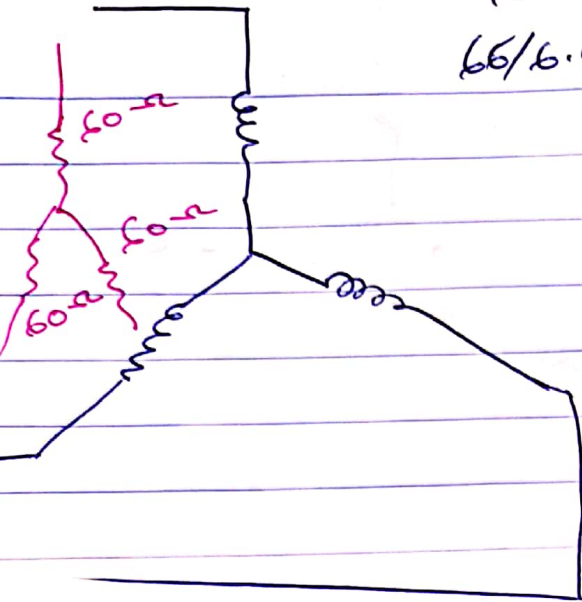


$* R_p (\Omega) = ??$

$3 * 0.6 = 1.8 \Omega$

↓  
Converting  
Y to D

- single phase

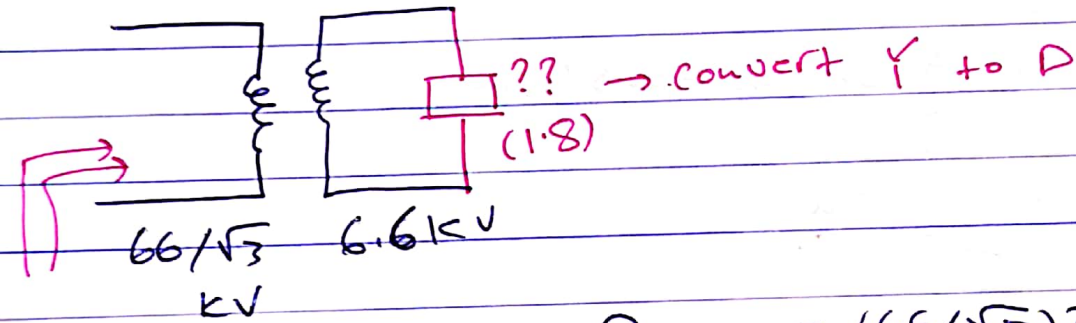


$$R_p = 1.8 \left( \frac{66/\sqrt{3}}{6.6} \right)^2 = 60 \Omega$$

(بالا سکان مباشره)  $R_p = 0.6 * \left( \frac{66}{6.6} \right)^2 = 60 \Omega$


(سکان يقين صار الادي لاديم يكون)

Ex:-

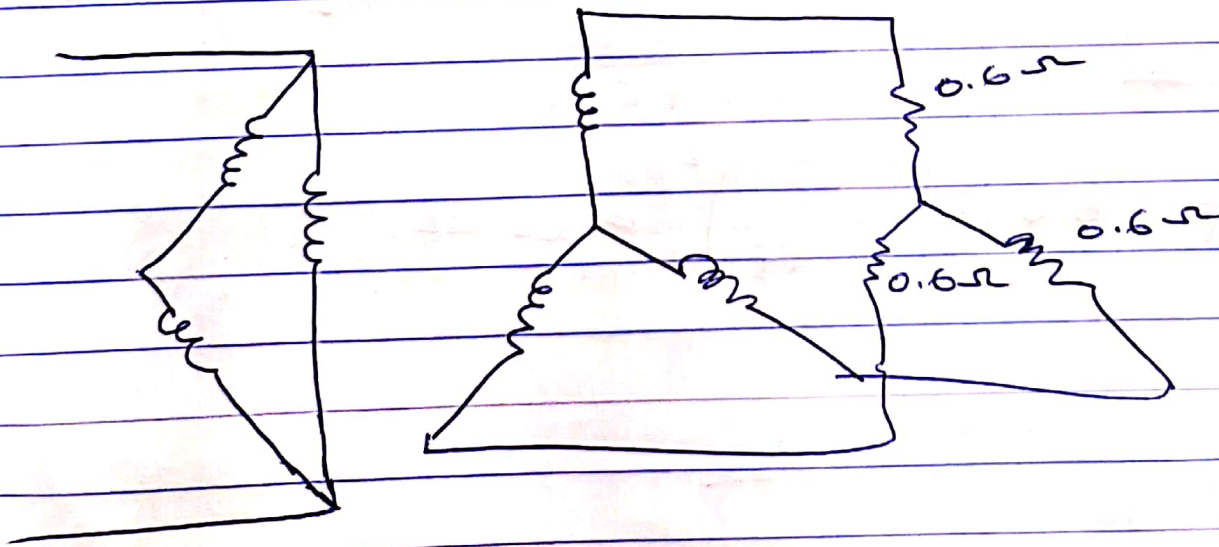




In Single phase:-

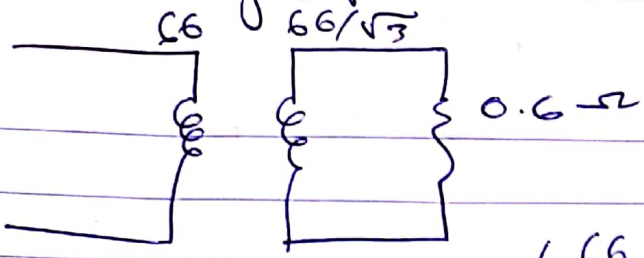

$$0.6 * \left( \frac{66}{66/\sqrt{3}} \right)^2 = 180$$


$Y_{eq} \longleftrightarrow Y_{eq \text{ load}}$

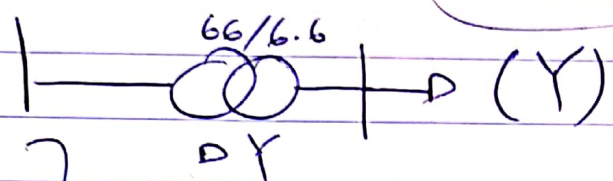$Y_{-eq} \longleftrightarrow Y_{-eq \text{ load}}$   
(transf. ratio)<sup>2</sup>




$$0.6 * \left( \frac{66}{6.6} \right)^2$$

EX:

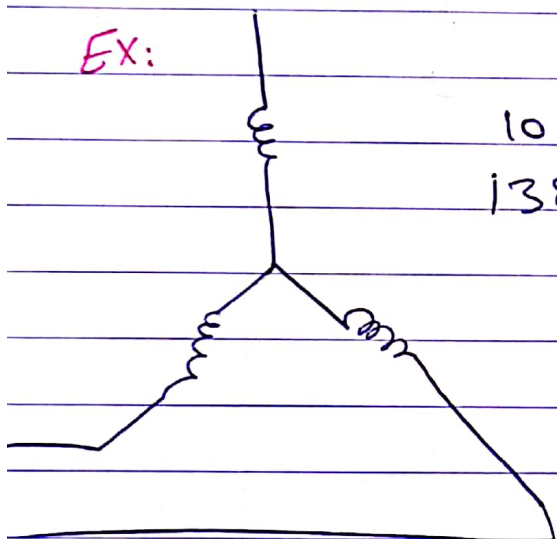

10 MVA  
138/13.8 kV

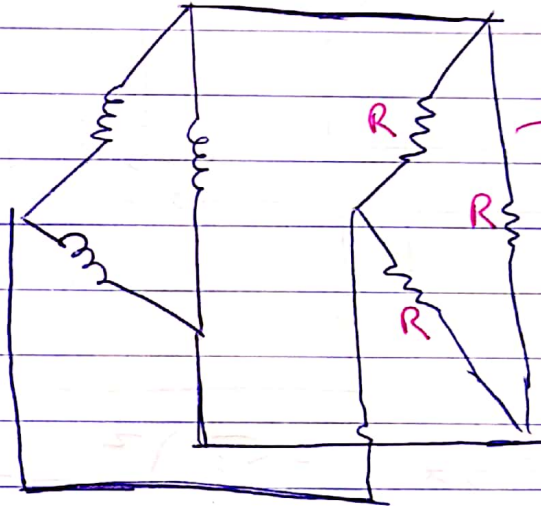

800 kW  
@ rated voltage  
"balanced"

\*\*  $Y_{eq}$  resistance seen from the high voltage side?


$$P = 3 * \left( \frac{V^2}{R} \right)$$

$$800 = 3 * \left( \frac{(13.8)^2}{R} \right)$$

$$R = 0.7 \Omega$$

$$R_Y = \frac{0.7}{3} * \left( \frac{138}{13.8} \right)^2$$

OR

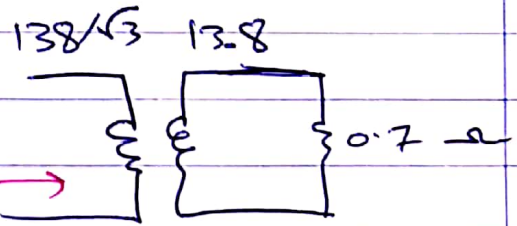



$$R = 0.7 + \left( \frac{138/\sqrt{3}}{13.8} \right)^2$$

EX: 3(1 $\phi$ ) transformer  $\overset{3\phi}{1.2/0.12 \text{ kV}}, 7.2 \text{ kVA}$

$X = 5\%$ ,  $T_r$ . Find Y-eq impedance seen from primary.  
 (منظر المعاوقة في الاسئلة باله قبل)

$7.2 \times 3 \text{ kVA} \rightarrow 3\phi$

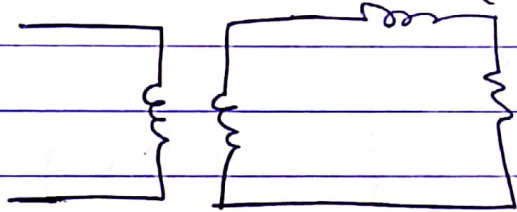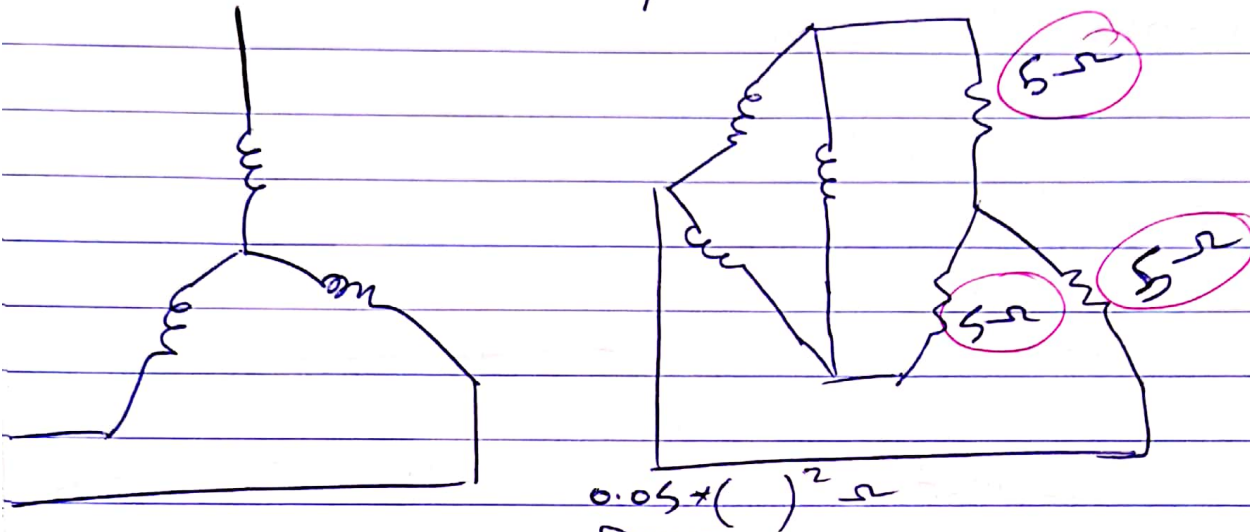$V_{LL}/V_{\phi\phi} \rightarrow 1.2/\sqrt{3}/0.12 \text{ kV}$







$$R_p = 5 * \left( \frac{1.2\sqrt{3}}{0.12} \right)^2 \text{ } \Omega$$

$$X(\Omega) = 0.05 * \left( \frac{(1.2 * \sqrt{3})^2}{7.2 * 3} \right) =$$


$$Z = R + jX$$

# \* Synchronous Generator

Generator  
Power Plant

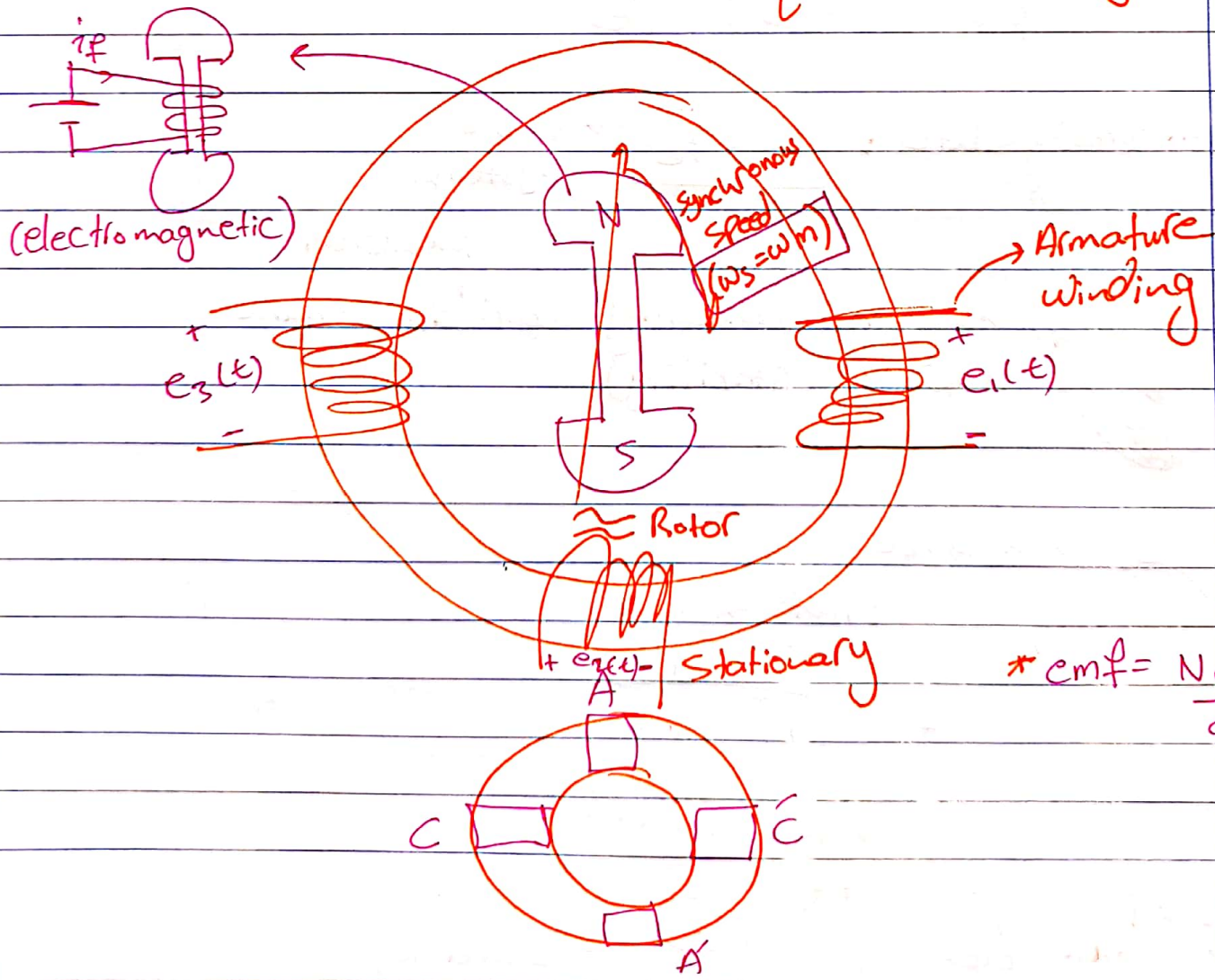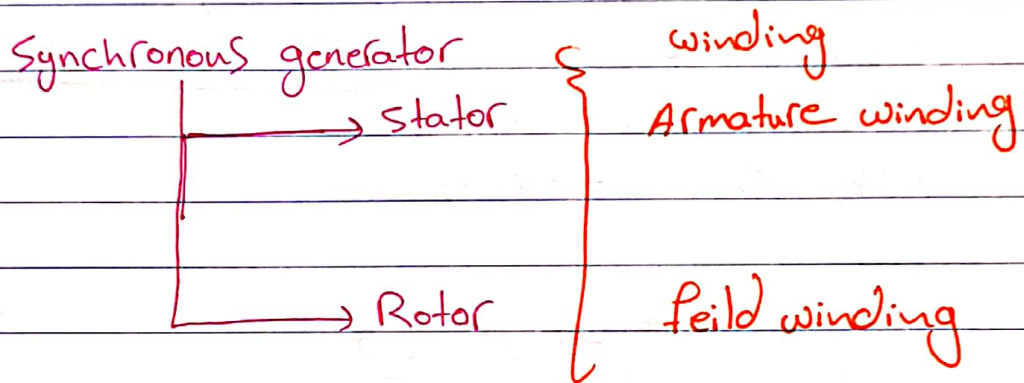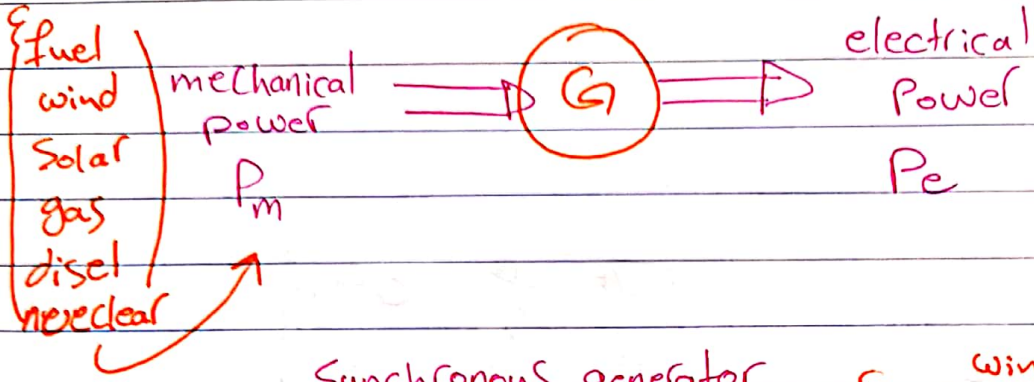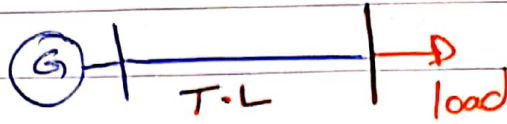

$$* \text{cmf} = N \frac{d\phi}{dt}$$

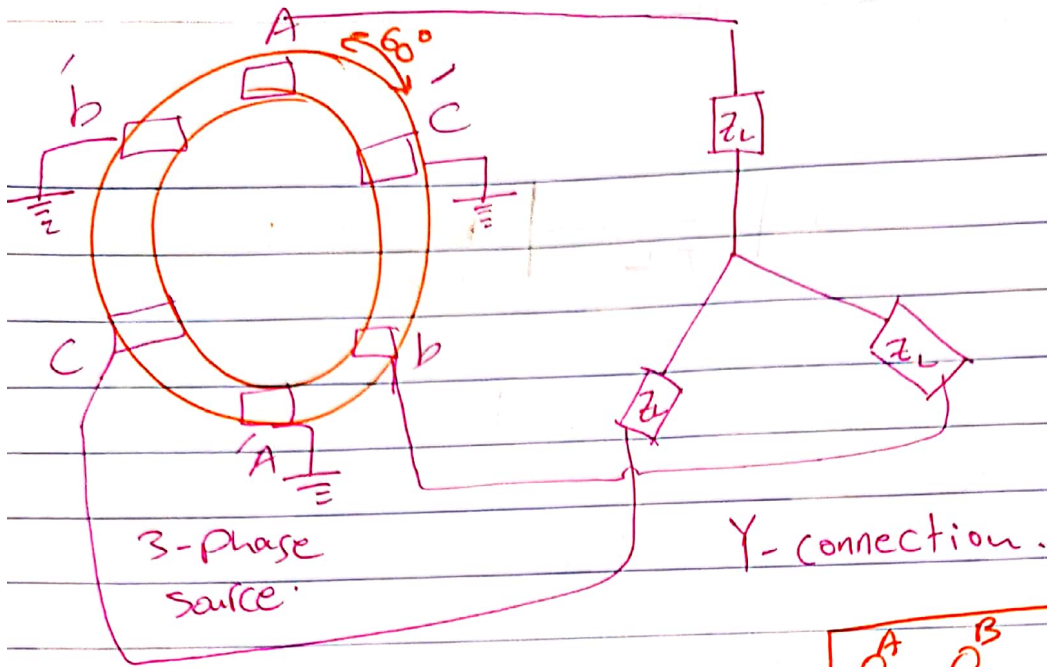


$\phi^A$	$\phi^B$	$\phi^C$	$\phi^N$
$\phi^A$	$\phi^B$	$\phi^C$	$\phi^N$



$$e_a(t) = E_m \sin \omega t$$

$$e_b(t) = E_m \sin(\omega t - 120^\circ)$$
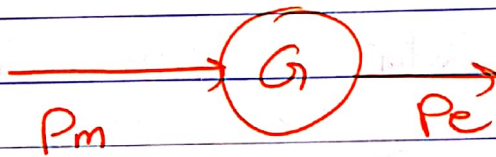
$$e_c(t) = E_m \sin(\omega t + 120^\circ)$$



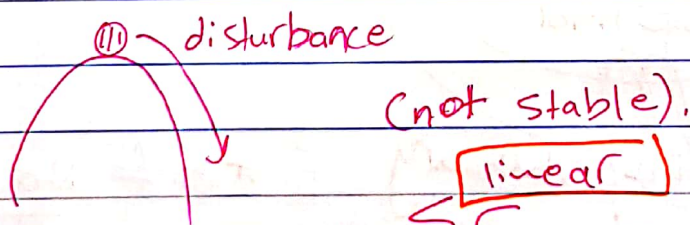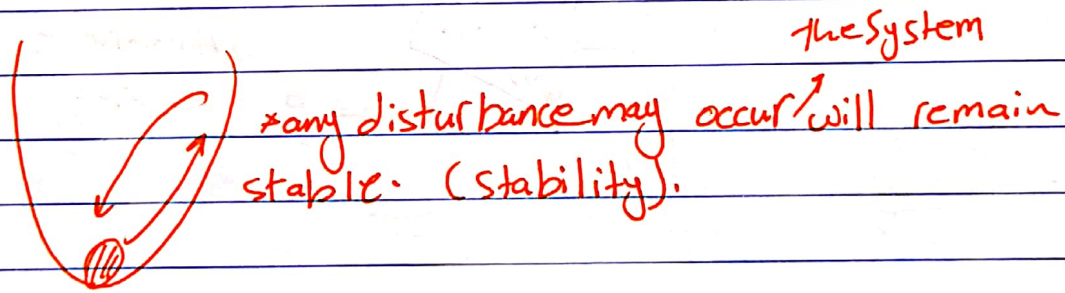\* in steady state:  $P_m = P_e$  → stable system



$$* \sum F = ma$$



\* Rotational


$$J \frac{d\omega_m}{dt} = T_{mech} - T_{elec}$$



$$\frac{d\omega_m}{dt} \approx \equiv \left[ k \frac{d^2 \Theta_m}{dt^2} \right] = P_m - P_e$$


→ rotor angle.

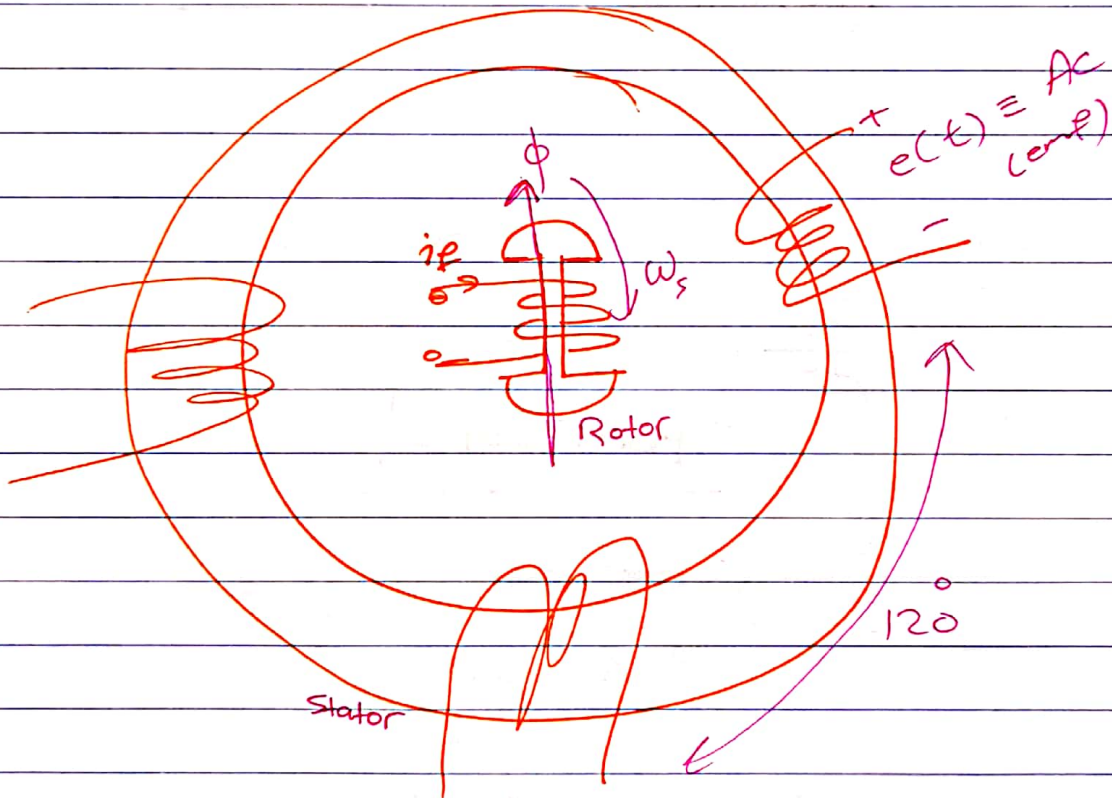$\Theta$  can be replaced with  $\delta$  (power angle).





$i_f \equiv$  field current, excitation

$$E_{rms} = f(N, \text{freq}, i_f)$$

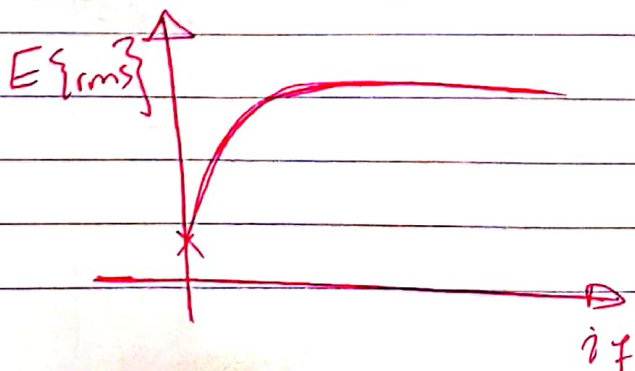

Stator Flux  $\vec{\phi}_a + \vec{\phi}_b + \vec{\phi}_c =$
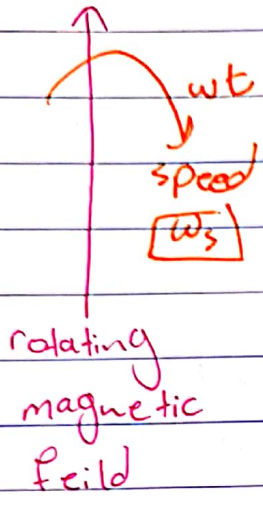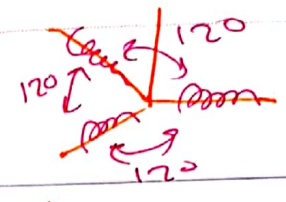
$$\phi_m \sin(\omega t) + \phi_m \sin(\omega t - 120) + \phi_m \sin(\omega t + 120)$$



Synchronous speed =  $\frac{120 f}{\text{Poles}}$

$$\frac{k d^2 \theta_m}{dt^2} = P_m - P_e$$

Rotor angle

$$\frac{k d^2 \delta}{dt^2} = P_m - P_e$$




Power angle

two fluxes → one from Rotor  
 → one from stator (called  $\delta$ )

Phase shift distance  
120°
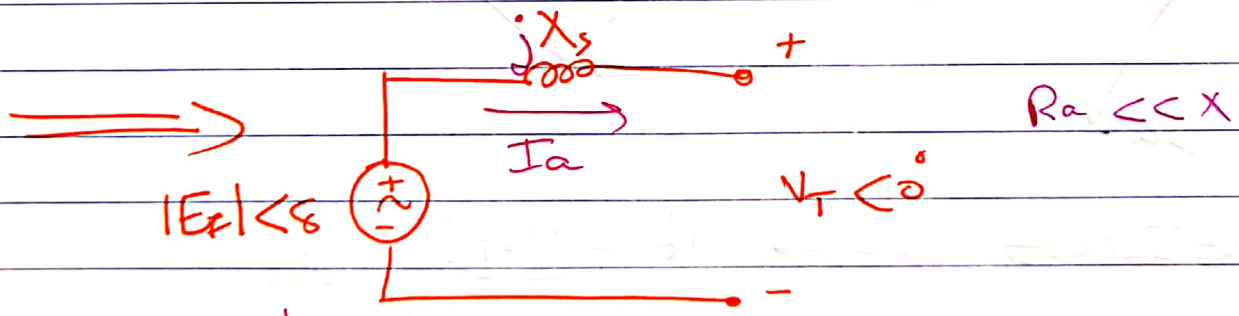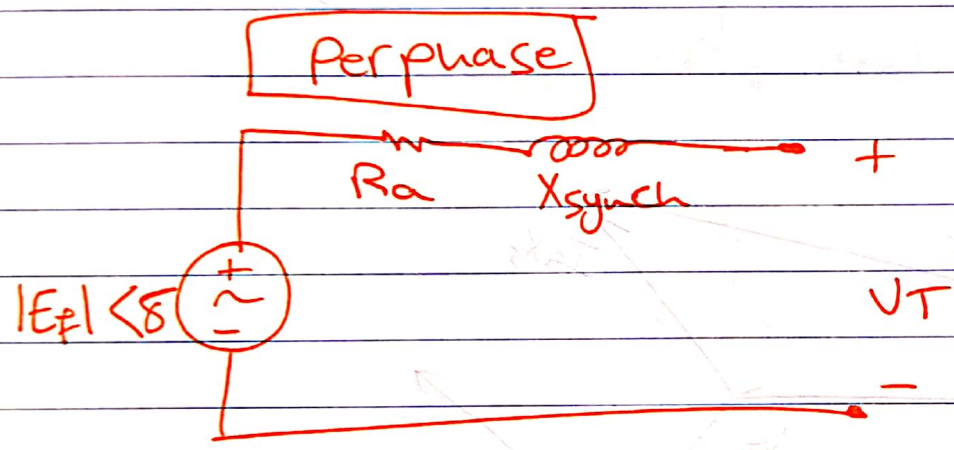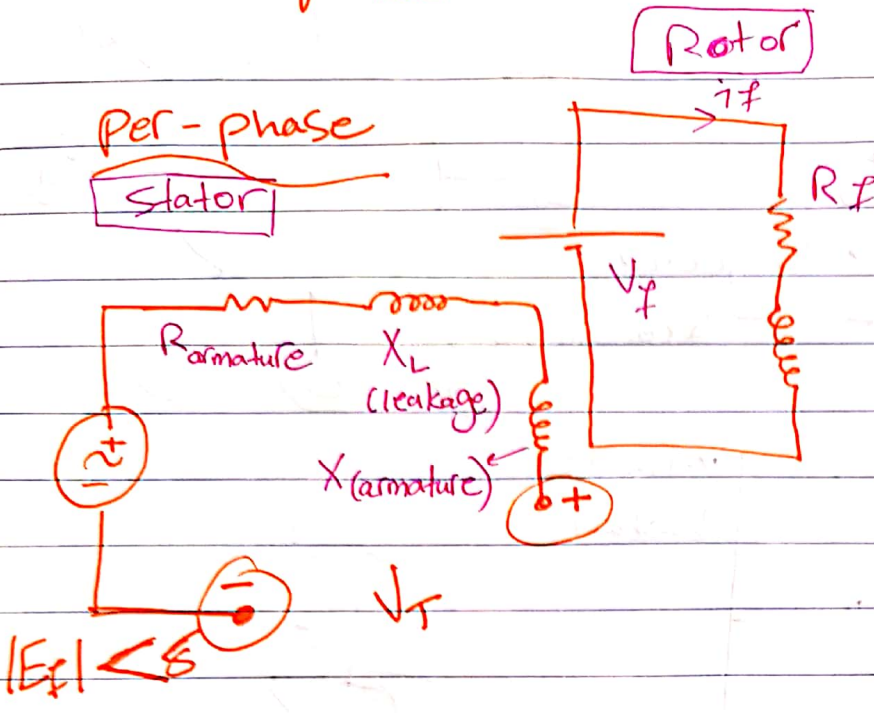
# Model "equivalent ckt"



\* \*  
the stator  
gives reaction  
opposite to  
the rotor



→ we'll study  
→ power  
→ reactive power


→ power -> Motor

# Generator equivalent ckt

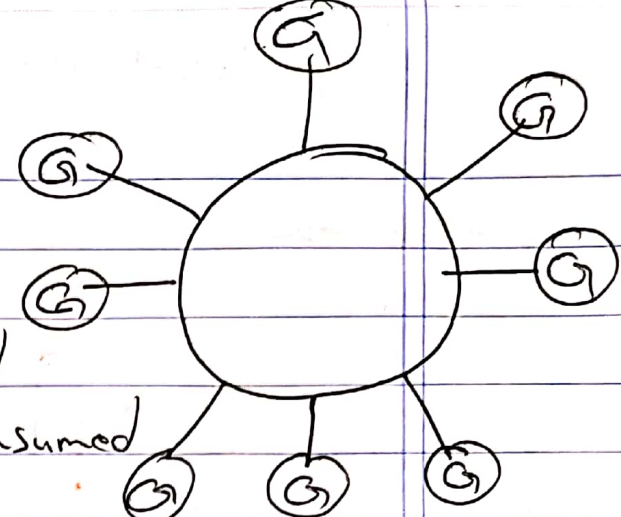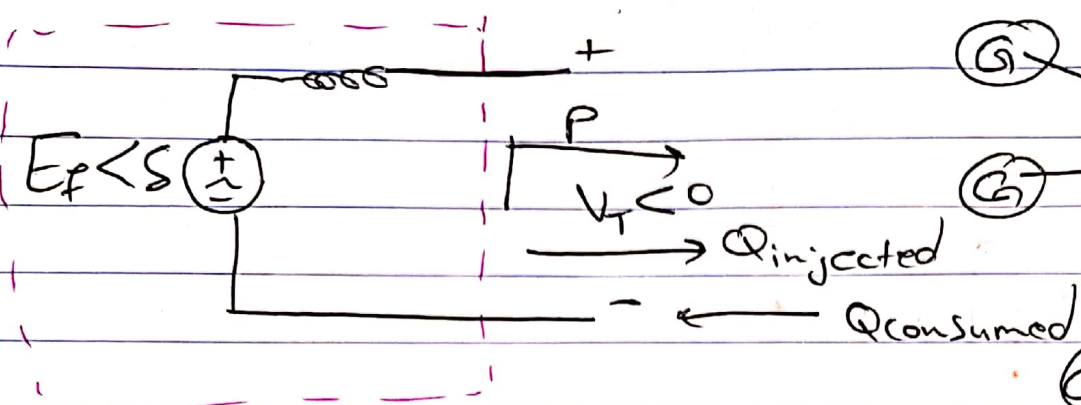

mech position  
for rotor

infinite  
busbar

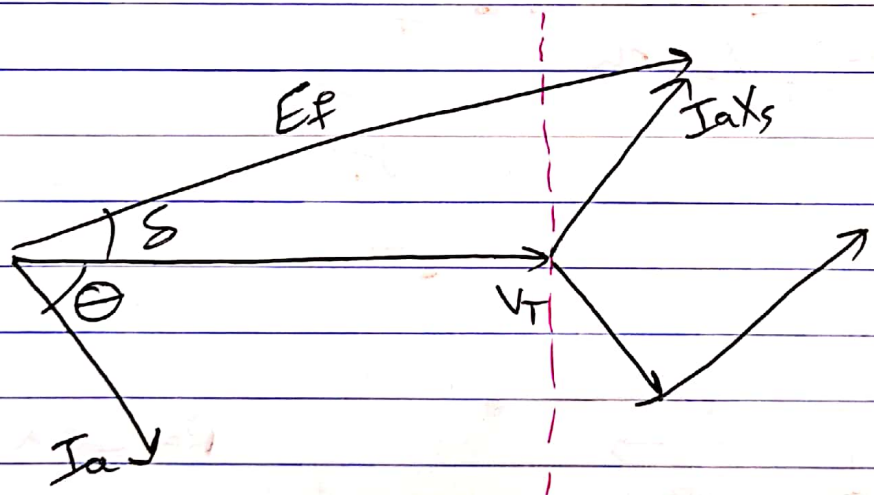


$$P = 3V_T I_a \cos \theta \longrightarrow P_e = \frac{3V_T E_f \sin \delta}{X_s}$$

$P \propto \delta$

$$I_a X_s \cos \theta = E_f \sin \delta$$
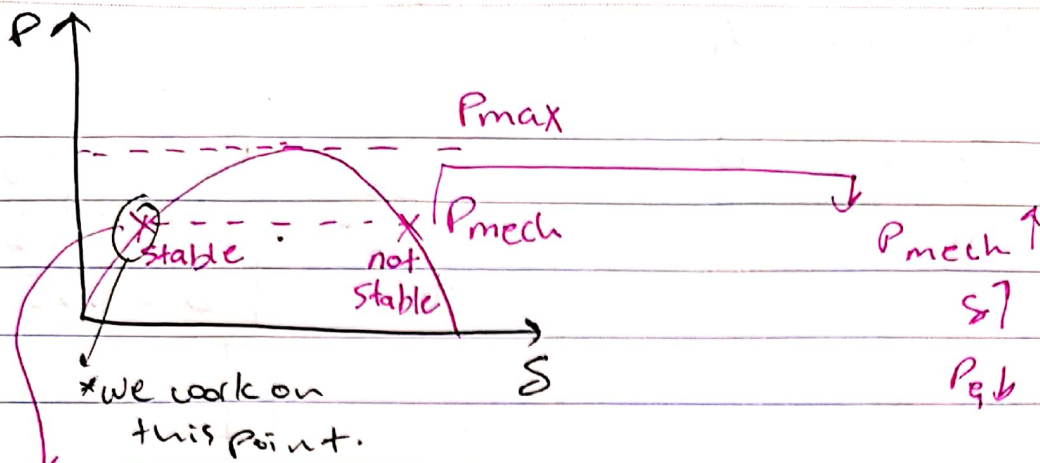
$$I_a \cos \theta = \frac{E_f \sin \delta}{X_s}$$








$P_{mech} \uparrow$   
 $\delta \uparrow$  (diff)  
 $P_g \downarrow$

**\* Steady state**

$$K \frac{d^2 \delta}{dt^2} = P_{mech} - P_{electrical}$$

$$P_{mech} = P_{electrical}$$

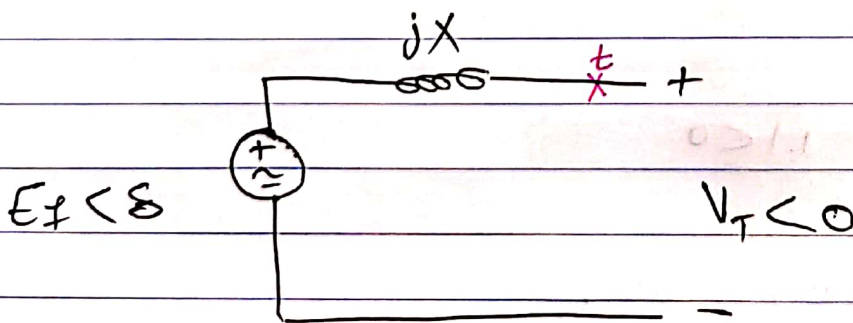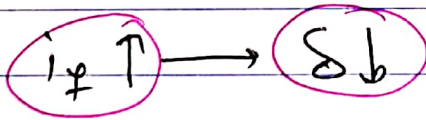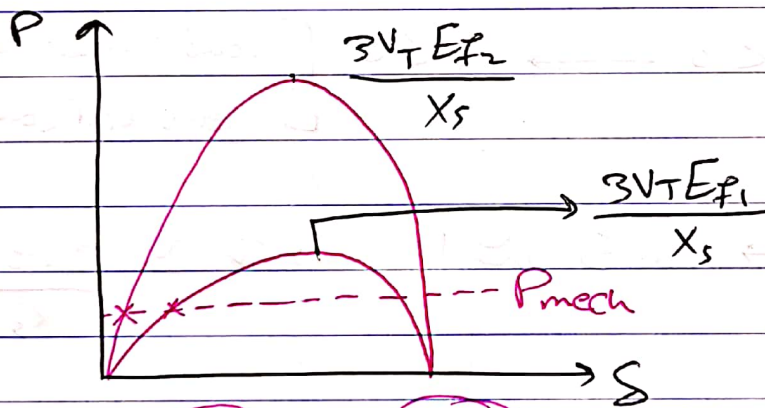


$$Q_t = 3 V_t I_a \sin \theta$$

$$I_a X_s \sin \theta = E_f \cos \delta - V_T$$

{ from phasor diagram }
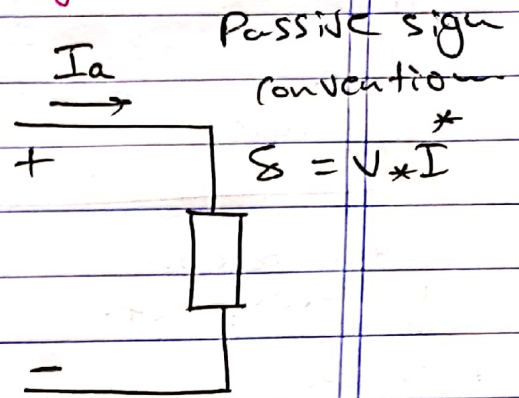
$$Q = \frac{3 V_T (E_f \cos \delta - V_T)}{X_s}$$




$P_+ \rightarrow$  consume  
 $Q_+ \rightarrow$  consume

$$E_f \cos \delta - V_T > 0 \rightarrow Q > 0 \quad \left( \begin{array}{l} * \text{ generator supplies } Q \\ * \text{ load consumes } Q \end{array} \right)$$

$$E_f \cos \delta - V_T < 0 \rightarrow Q < 0 \quad \left[ \begin{array}{l} \text{load inject } Q \\ \text{generator consumes } Q \end{array} \right]$$

$$\delta \text{ (small)} \rightarrow \cos \delta \approx 1 \rightarrow Q \approx \frac{3 V_T}{X_s} (E_f - V_T)$$

\* Example:-

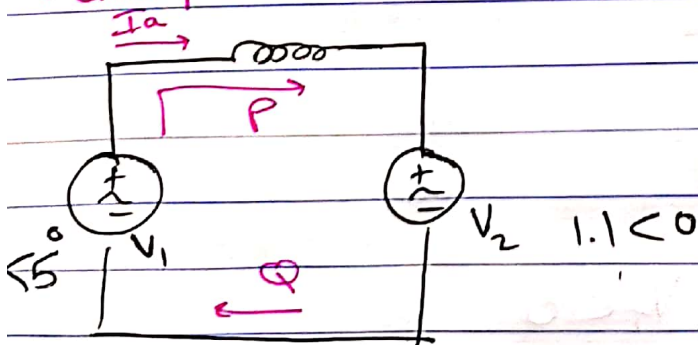

1.0, 1.1 pu  
 $0^\circ, 5^\circ$

Find  $V_1, V_2$  ??  
 $P_1, Q_1, P_2, Q_2$  ??

$$I_a = \frac{V_1 - V_2}{jX}$$

$$S_2 = V_2 I_a^* = P_2 + jQ_2$$

if +ve consumed  
consumed Q  
if -ve inject P  
" Q

P (+ve)  
Q (-ve)


$$S_1 = VI^*$$

$S_1 = -VI^*$  (Passive sign convention)


+ → consumed  
- → inject

$$P = \frac{3VTE_f}{X_s} \sin \delta$$
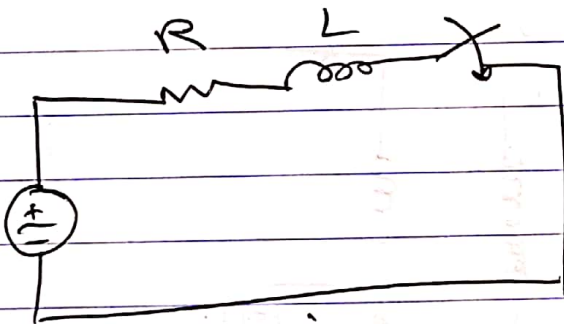
$$= 3 \frac{V_{TL}}{\sqrt{3}} \frac{E_{fL}}{\sqrt{3}} \sin \delta = \frac{V_{TL} E_{fL} \sin \delta}{X_s}$$






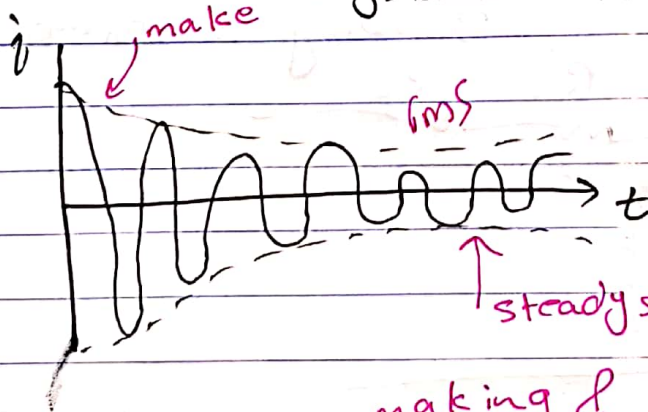$i(t) = \overset{\text{steady state}}{i} + \overset{\text{transient}}{i}$





making & Breaking current


3 $\phi$  fault

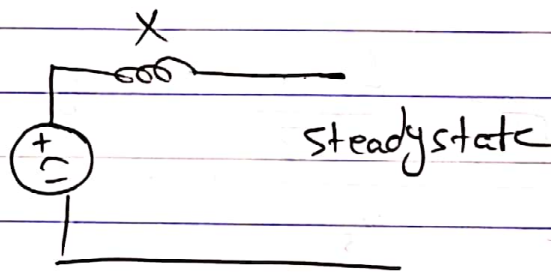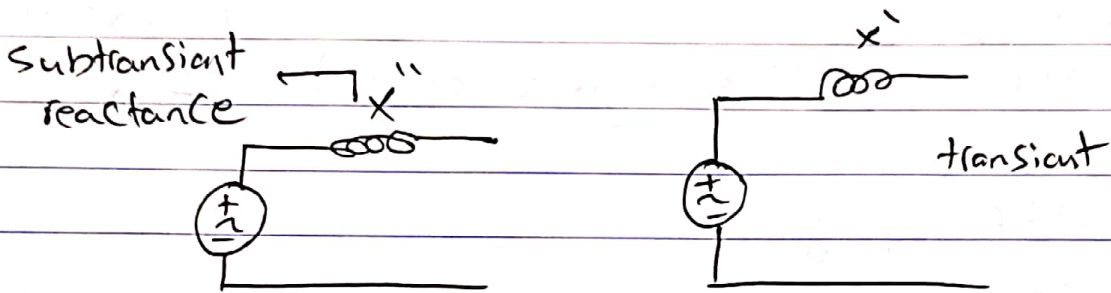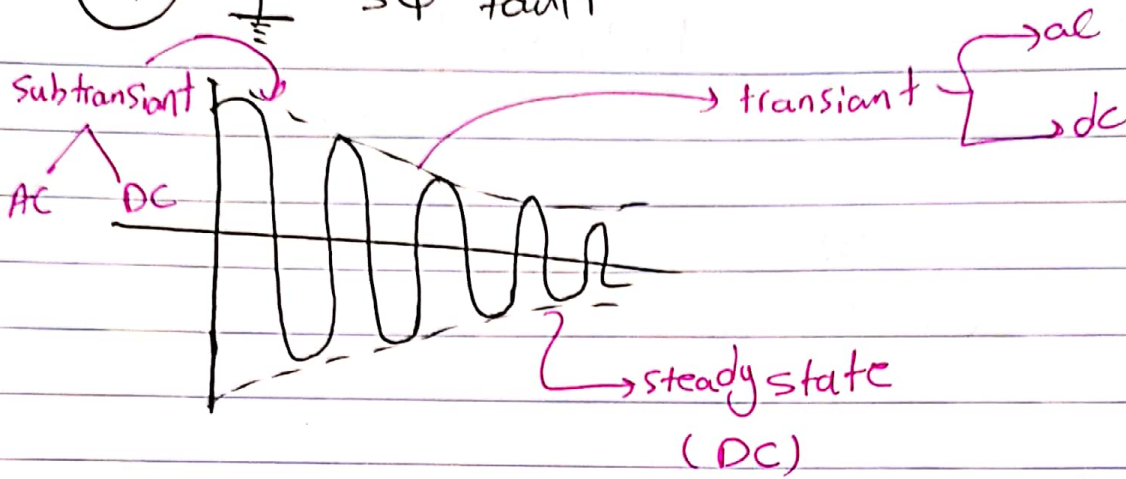

$$X'' < X' < X$$

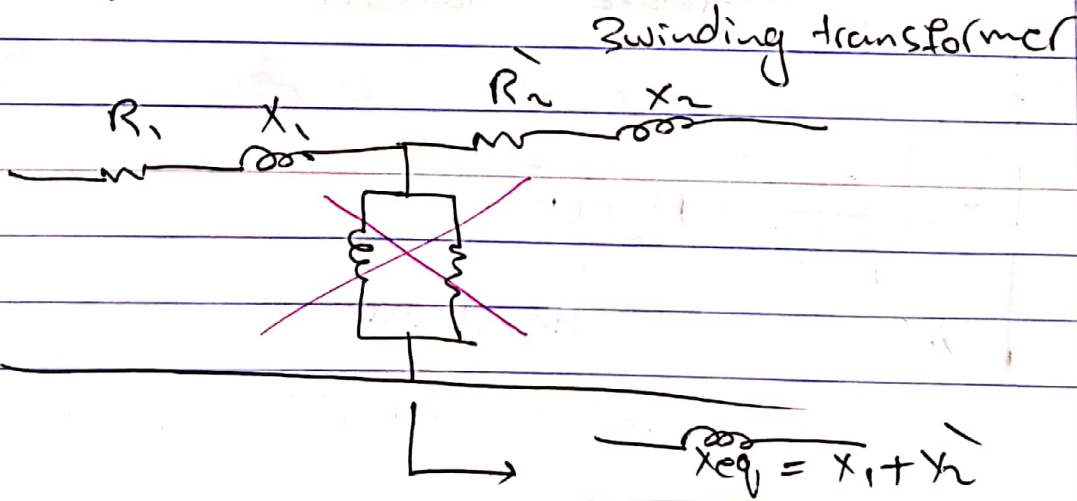
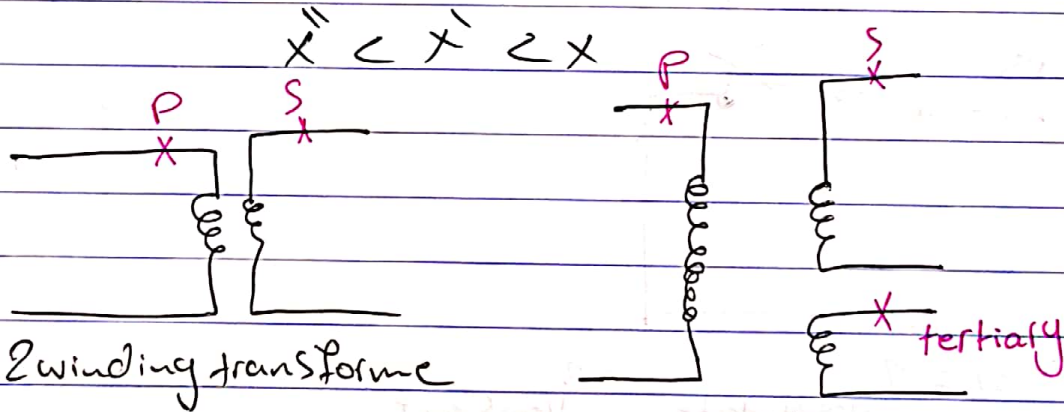


Req  
Xeq } Sc test

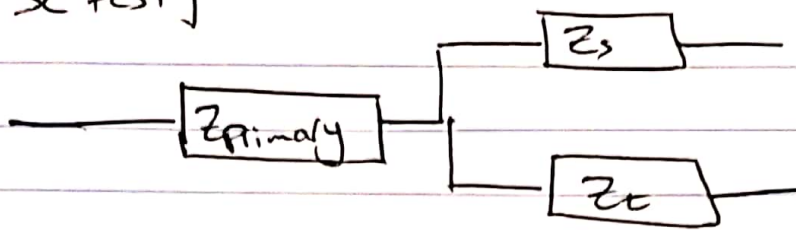

all referred to primary

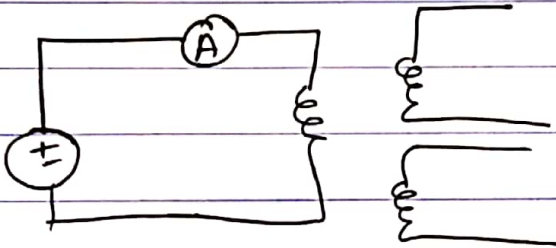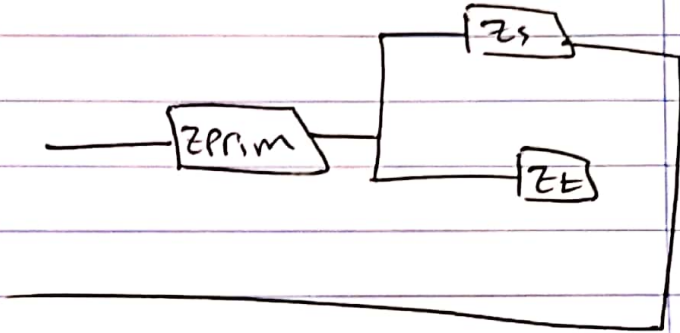$Z_{ps}$   
seen from primary  
short ckt  
 $t = \text{open ckt}$



$$Z_{ps} = Z_p + Z_s' \quad \text{ref to prim}$$

$$Z_{pt} = Z_p + Z_t'$$

$$Z_{st} = Z_s + Z_t \quad \text{referred to secondary}$$

$$Z_{st}' = Z_s' + Z_t'$$