

* Design


- 1- ترجمة السؤال
- 2- Truth table جدول
- 3- k-map جدول
- 4- logic diagram برسم

* Mapping to NoR, NAND

NoRAND \rightarrow OR + Inputs, outputsOR \rightarrow NoR + Inverter.NANDAND \rightarrow NAND + InverterOR \rightarrow AND + ^{inputs} Input, outputs

END of part 1

1) Decoder

 

n : Inputs
 2^n : outputs


* Decoder is a minterm generator

* n خطي 1 على الـ line الـ رقم نفسه
 رقم الـ Input

 * (1-2) decoder : Inverter + علامة على الـ

Decoder expansion: $1 \rightarrow$ no. of (1-2) line decoders


$n \rightarrow$ no. of 2-input AND gates
 $= 2^n$



Traditional \Rightarrow (No. AND * No. Inputs) + No. Inverters

Decoder exp. \Rightarrow (No. AND + 2) + No. (1-2) line decoders

2) Encoder

 


2^n : Inputs
 n : outputs

* Opposite of Decoder.

* Input دس (D) و اسی (A) کے برعکس

* High priority Encoder → MSD (Most Significant Digit) کی طرف سے 1 بائیں (Left) وغیرہ (X).

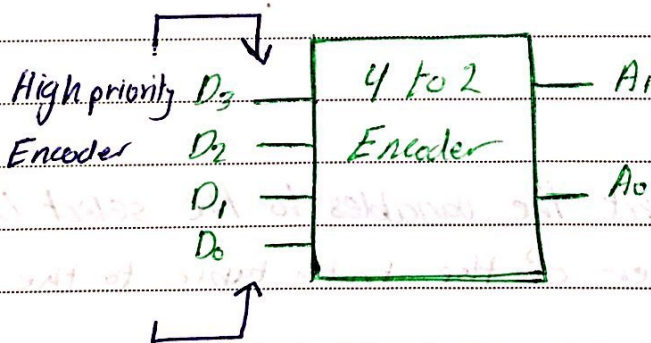* Low priority Encoder → LSD (Least Significant Digit) کی طرف سے 1 بائیں (Left) وغیرہ (X).




Low priority Encoder.

3) Multiplexer

 2^n : Input n : select lines.

one output

 * To Build $2^n \rightarrow 1$ MUX, you need:

- 1) $n \rightarrow 2^n$ decoder.
- 2) 2^n 2-input AND gates.
- 3) one 2^n -input OR gate.

* Function Implementation using muxes:

~~Approach~~

Approach 1: connect the variables to the select lines and copy the answer of the truth table to the inputs.


Approach 2: 1) use $2^{(n-1)} \rightarrow 1$ mux where n is the No. of variables

- 2) find the truth table
- 3) Separate the truth table into pairs without the least sig. digit.
- 4) make a relation between the truth table & the LSD, and copy it to the inputs.

 4) D Mux.

* opposite of mux.

* 1 input.
 n select lines.
 2^n outputs.



Dmux = Decoder with enable


* إذا كان $S=0$ يفتح قنطرة الـ I إلى Line 0، وإلا تبقى Zeros.

* Half adder : 2-bits adder


* Full adder : 3 bits adder

* Ripple carry adder : a group of bits adder

Half adder

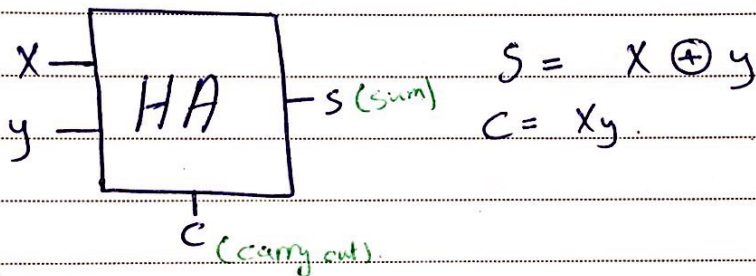

Full adder

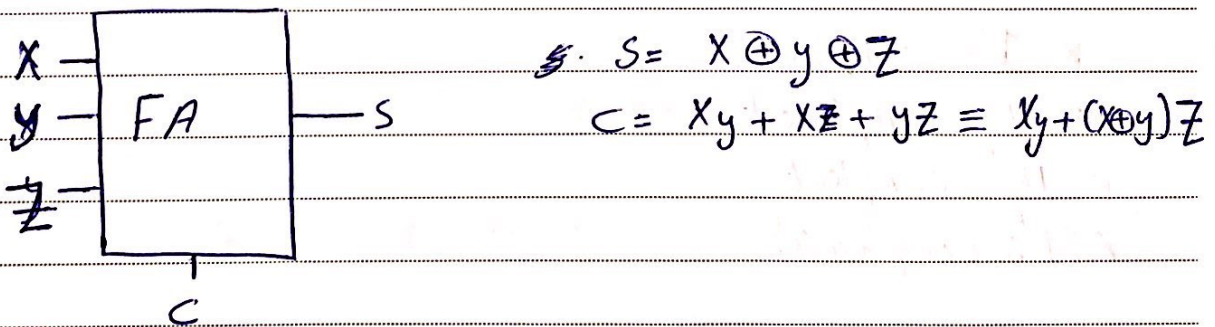

Sub:

$$M - N \rightsquigarrow B = 0 \rightsquigarrow M > N$$

$$M - N \rightsquigarrow B = 1 \rightsquigarrow M < N$$

The right answer is to subtract \leftarrow

the answer from 2^n and put the negative sign.

where n is the
No. of bits.

Complements

1) one's complement $\equiv (r^n - 1)$'s complement.

* 1's complement

* 7's complement

* 15's complement

* 9's complement

$$(r^n - 1) = (r - 1)(r - 1)(r - 1) \dots$$

. (n) bits الـ complement

* Find 1's complement for N : $\Rightarrow (r^n - 1) - N$.

بمسك الرقم، وبخمس كل اثنى فيه

2) r's complement.

- * 2's complement.
- * 10's complement.
- * 16's complement.
- * 8's complement.

Find r's complement for $N_r \rightarrow (r^n - N)$

* خصي بالرقم كل (0) باضه زي ما هو لما اشفوف (1) باضه وبعكس كل اثنى بعده.

* 2's complement \Rightarrow سال الرقم

sub. with 2's complement.

~~$M < N$~~ ~~$M > N$~~


$$M - N \Rightarrow M + (-N) = \boxed{M + (2^n - N)}$$

$$B=0, C=1, M > N$$

$$B=1, C=0, M < N$$

* Signed Integers.

* Sign Magnitude :-

 

- * sign bit (0) \Rightarrow positive number
 " " (1) \Rightarrow negative number

* Signed 1's complement

الأرقام الموجبة زي ال sign magnitude \leftarrow

= السالبة باي 1's comp للرقم مع ال sign-bit \leftarrow

* إذا بي أريف في قيمة الرقم

بمشوف ال sign bit بعدد ال

* Signed 2's complement.

للرقم 2's comp.

الأرقام الموجبة زي ال sign-magnitude \leftarrow

= السالبة باي 2's comp للرقم مع ال sign-bit \leftarrow

* Over Flow

* Unsigned numbers

- addition:

Carry = 1 \Rightarrow overflow ✓

- subtraction:

No way for overflow.

* Signed numbers

- addition:

Two numbers with the same sign (⚠️!)

Carryout ⚠️!

+	⊕	+	=	-
-	⊕	-	=	+
overflow ✓				

$$OV = C_{n-1} \oplus C_n$$

- subtraction:

Two numbers with different signs.

* Multiplication & Division

$X \times 2^n \Rightarrow$ shift left by n -positions.

$X / 2^n \Rightarrow$ Shift Right by n -positions.

* Zero Fill: Two different numbers with different width.

\Rightarrow ~~Fill~~ Fill zeros from the left.
for (unsigned).

* Sign Extension: for (signed).

copy the sign bit to the left

ex: $1111001 \Rightarrow -7$
extend to 10 bits

$\$111111001 \Rightarrow$ still -7

$11101 \Rightarrow -3$

extend to 8 bits

$11111101 \Rightarrow -3$