

~~27/5~~

22

0907231 Digital Logic	Second Exam	University of Jordan
9 Problems	75 Minutes	Summer 2019
الرقم الجامعي:		الاسم:
د. محمد عبد المجيد		د. وليد الدويك
اختار المدرس:		(5 points)

Problem 1. Solve the following short problems.


a. Compute the GN cost of 5-to-32 decoder when implemented using decoder expansion.

GN = ~~101~~

$$(48 \times 2) + 5$$

$$= 96 + 5$$

$$= 101$$

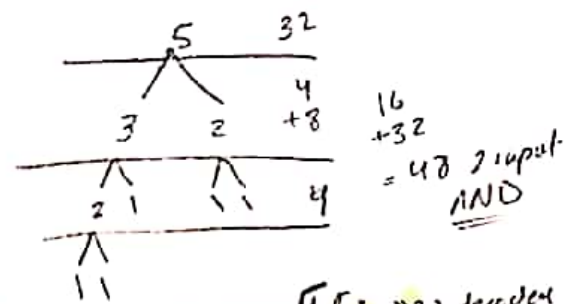

b. Given a 6-to-3 low priority encoder with inputs D5-D0 and outputs A2-A0 and valid bit (V; write the Boolean equation for output A2.

$$A2 = D_5 \bar{D}_4 \bar{D}_3 \bar{D}_2 \bar{D}_1 \bar{D}_0 + D_5 \bar{D}_4 \bar{D}_3 \bar{D}_2 \bar{D}_1 D_0$$


D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀	V
X	X	X	X	X	1	0	0	0	1
X	X	X	X	1	0	0	0	1	1
X	X	X	1	0	0	0	1	0	1
X	X	1	0	0	0	0	1	1	1
X	1	0	0	0	0	0	1	0	1
1	0	0	0	0	0	0	1	0	1

c. Using 6-bits, the minimum negative number using Sign-Magnitude format is = $(111111)_2$

d. What is the decimal value of the 6-bits signed number $(100111)_2$ if it is represented using signed 2's complement format? (~~-25~~)₁₀

e. What is the Boolean expression of output F in the figure below in terms of X and Y?

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	0

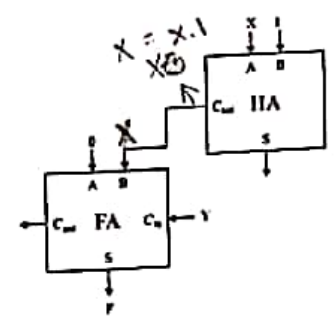

$$F(X, Y) = \sum m(1, 2) = \bar{X}Y + X\bar{Y}$$

$$F = X \oplus Y \oplus 0$$

$$0 \oplus 0 = 0$$

$$0 \oplus 1 = 1$$

$$1 \oplus 0 = 1$$

$$1 \oplus 1 = 0$$

$$\bar{X}Y + X\bar{Y}$$

$$01 + 10$$

Problem 2. A digital circuit receives 3-bit input A (A_2, A_1, A_0) and produces 3-bit output Z (Z_2, Z_1, Z_0). The behavior of the circuit is described in the table below. **Formulate the truth table of the circuit.** Don't derive the expression for the output and Don't design the circuit. (2 points)

2




When $A \leq 4$	$Z = 4 - A$
When $A > 4$	Z is Don't Care

A_2	A_1	A_0	Z_2	Z_1	Z_0
0	0	0	1	0	0
0	0	1	0	1	1
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	0	0	0
1	0	1	X	X	X
1	1	0	X	X	X
1	1	1	X	X	X


POWERUNIT

Problem 3. Implement the following logic diagram using only NAND gates. The number of NAND gates should be minimum. (2 points)

2

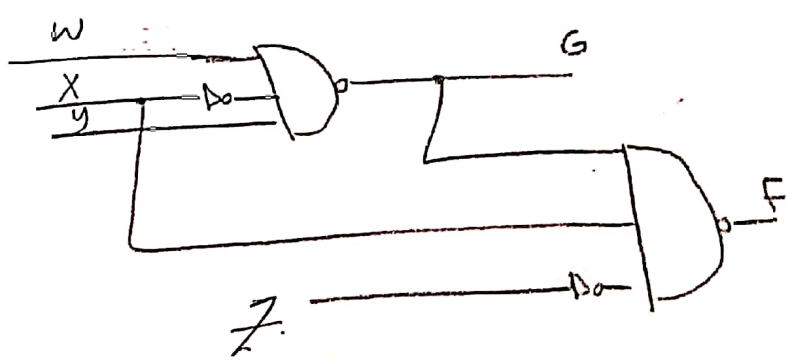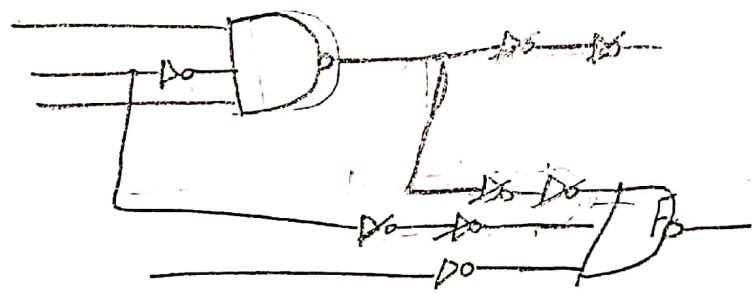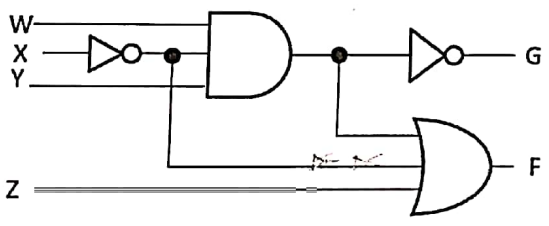


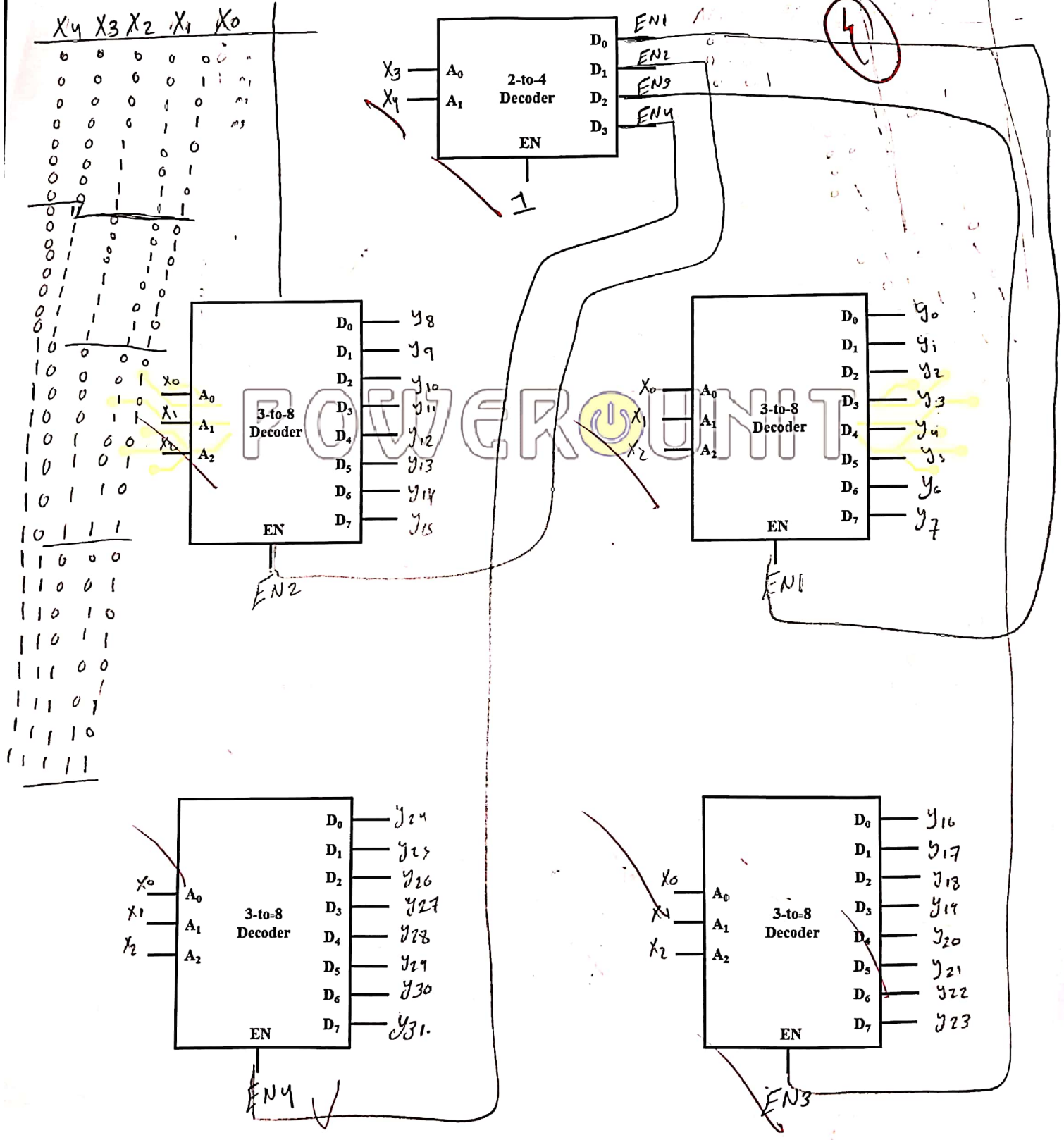Problem 4. Implement a 5-to-32 decoder using only the blocks given below. The 5-to-32 decoder has 5 inputs ($A_4 A_3 A_2 A_1 A_0$) and 32 outputs ($D_{31} D_{30} \dots D_1 D_0$). Make sure that you label all inputs/outputs and clearly show the connections of your design. (4 points)




Problem 5. Using only the components in the circuit below, implement functions F and G given by the following truth table. Make sure that you label all inputs/outputs and clearly show the connections of your design. (3 points)

W	X	Y	F	G
0	0	0	1	1
0	0	1	1	1
0	1	0	0	1
0	1	1	0	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	1
1	1	1	1	0

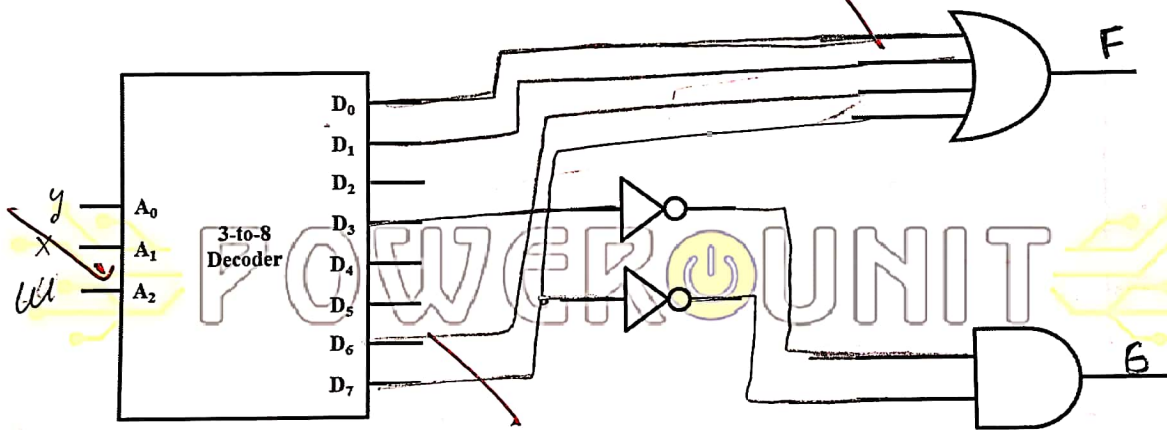


Problem 6. Using only the components in the circuit below, implement function F given by the following truth table. Make sure that you label all inputs/outputs and clearly show the connections of your design. (3 points)


W	X	Y	Z	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

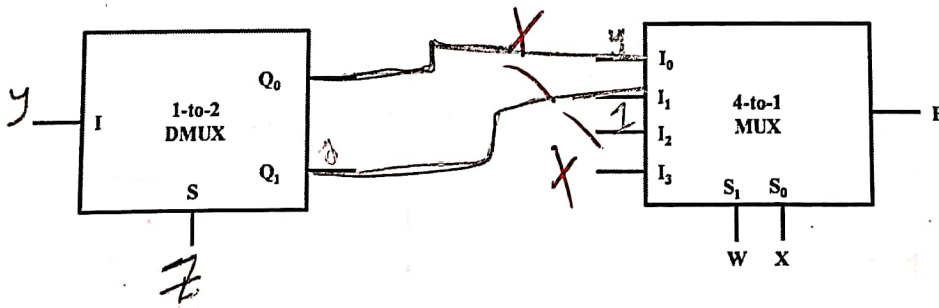

Problem 7. Implement a 16-to-1 MUX using only the three 8-to-1 MUXes given below. The 16-to-1 MUX has 16 inputs ($I_{15} I_{14} \dots I_1 I_0$) and 1 output (Y). Make sure that you label all inputs/outputs and clearly show the connections of your design. (3 points)

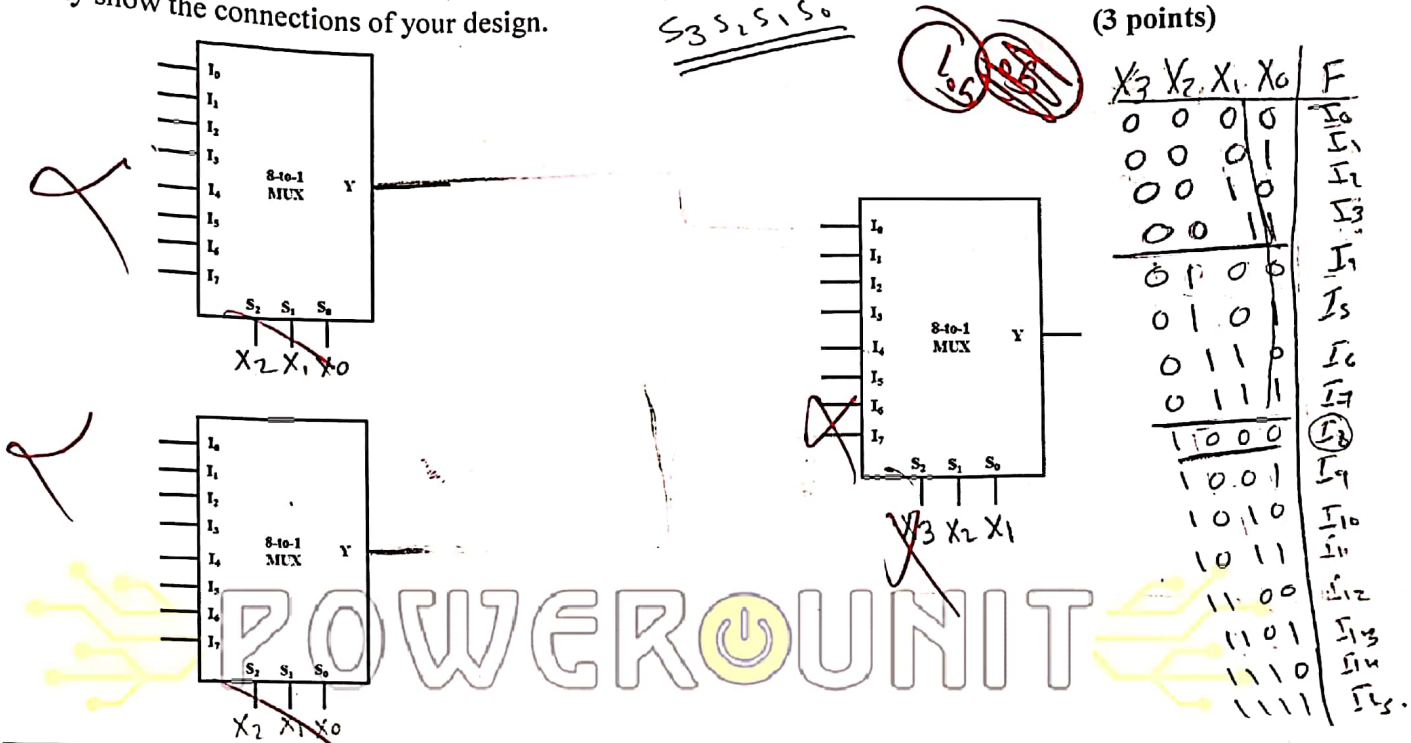

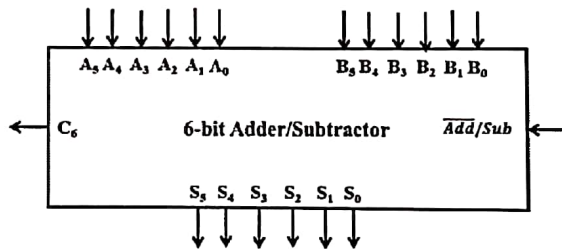Problem 8. Given the following 6-bit adder/subtractor, answer the two questions below: (3 points)



I. Assume that inputs A and B are unsigned numbers set to the following values: $A = (011010)_2$ and $B = (001100)_2$. The \overline{Add}/Sub control is set to 0. Accordingly, compute the sum bits $S[5:0]$ and determine if there is an overflow or not.

$$\begin{array}{r} 011010 \\ + 001100 \\ \hline 100110 \end{array}$$

$S_5 S_4 S_3 S_2 S_1 S_0 = 100110$

Is there an overflow? No.

II. Assume that inputs A and B are signed numbers in 2's complement format set to the following values: $A = (110111)_2$ and $B = (111001)_2$. The \overline{Add}/Sub control is set to 1. Accordingly, compute the sum bits $S[5:0]$ and determine if there is an overflow or not.

$$\begin{array}{r} 110111 \\ + 111001 \\ \hline 111110 \end{array}$$

$S_5 S_4 S_3 S_2 S_1 S_0 = 111110$

Is there an overflow? No.

$X_0 X_1 X_2 \rightarrow Y_0 Y_1 Y_2$

Problem 9. Assume X and Y are 3-bits signed 2's complement numbers. Using only the following 5-bit ripple carry adders, and any number of inverters and XOR gates design a circuit that generates the following outputs:

(5 Points)

- 5-bit signed 2's complement number Z , such that: $Z = Y + 2X$
- 1-bit output Q , such that: $Q = \begin{cases} 1, & \text{when } Z \geq 7 \\ 0, & \text{when } Z < 7 \end{cases}$

You must show clearly all connections and labeling. Keep in mind that X consists of three bits: $X_2 X_1 X_0$, Y consists of three bits: $Y_2 Y_1 Y_0$, and Z consists of five bits $Z_4 Z_3 Z_2 Z_1 Z_0$.

