

Relation	$\text{Resistor } R$	$\text{Capacitor } C$	$\text{Inductor } L$
<u>Voltage</u>	$V = IR$	$V = \frac{1}{C} \int_{t_0}^t i(t) dt + V_0$	$V = L \frac{di}{dt}$
<u>Current</u>	$I = \frac{V}{R}$	$I = C \frac{dv}{dt}$	$I = \frac{1}{L} \int_{t_0}^t V(t) dt + I_0$
<u>P/w</u>	$P = \frac{V^2}{R}, I^2 R, IV$	$W = \frac{1}{2} CV^2$	$\omega_L = \frac{1}{L} LZ^2$

Chapter 7^o

RC-circuit	Discharge $V_{(t)} = V_0 e^{-t/\tau}$	$\tau = RC$
	V is the voltage of capacitor	
RL-circuit	Charge $V_{(t)} = V_0 + [V_0 - V_\infty] e^{-t/\tau}$	$\tau = \frac{L}{R}$
	Discharge $I_{(t)} = I_0 e^{-t/\tau}$	



if the C or L Charge or Discharge at $t \neq 0$

Then $e^{-t/\tau} \rightarrow e^{-(t-c)/\tau}$

c is the time when it charge or discharge

TIP^o The Rules at top of the page are for current going from + to -

Ch80 -

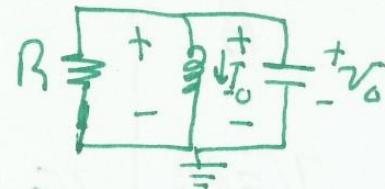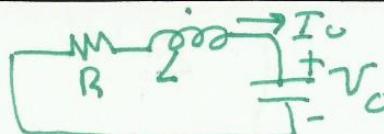

Series RLC Circuit

$$\alpha = \frac{R}{2L}, \omega_0 = \frac{1}{\sqrt{LC}}, S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \left\{ \begin{array}{ll} \alpha > \omega_0 & \text{Over critical} \\ \alpha = \omega_0 & \\ \alpha < \omega_0 & \text{Under} \end{array} \right\} \text{Damping}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad u(-t) = \begin{cases} 0 & t > 0 \\ 1 & t \leq 0 \end{cases}$$

Discharging :

$$\left\{ \begin{array}{ll} \alpha > \omega_0 & i(t) = A_1 e^{S_1 t} + A_2 e^{-\alpha t} \\ \alpha = \omega_0 & i(t) = (A_2 + A_1 t) e^{-\alpha t} \\ \alpha < \omega_0 & i(t) = e^{-\alpha t} (B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)) \end{array} \right.$$

i(t) is the current of inductor R

$\left(\frac{di(t)}{dt} \right) = -\frac{1}{L} (RI_o + V_o)$ Always Check Polarity of Capacitor here

$$\left\{ \begin{array}{ll} \alpha > \omega_0 & v(t) = V_\infty + A_1 e^{S_1 t} + A_2 e^{-\alpha t} \\ \alpha = \omega_0 & v(t) = V_\infty + (A_1 + A_2 t) e^{-\alpha t} \\ \alpha < \omega_0 & v(t) = V_\infty + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \end{array} \right.$$

v(t) is the voltage of capacitor R

$$\text{Parallel RLC circuit : } \alpha = \frac{1}{2RC}, \omega_0 = \frac{1}{\sqrt{LC}}, \frac{dv(t)}{dt} = -\frac{(V_o + RI_o)}{RC}$$

Discharging

$$\left\{ \begin{array}{ll} \alpha > \omega_0 & v(t) = A_1 e^{S_1 t} + A_2 e^{-\alpha t} \\ \alpha = \omega_0 & v(t) = (A_1 + A_2 t) e^{-\alpha t} \\ \alpha < \omega_0 & v(t) = e^{-\alpha t} (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)) \end{array} \right. \quad \} \text{ Voltage of Capacitor R}$$

$$\text{Charging : } I(t) = I_\infty + A_1 e^{S_1 t} + A_2 e^{-\alpha t} \quad (\alpha > \omega_0)$$

$$I(t) = I_\infty + (A_1 + A_2 t) e^{-\alpha t} \quad (\alpha = \omega_0)$$

$$I(t) = I_\infty + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\alpha < \omega_0)$$

} Current of Inductor R

$$v(0) = L \left(\frac{di(0)}{dt} \right)$$