

Description

In this experiment, you will design the simple two-bit TDM communication circuit shown in Figure 1.

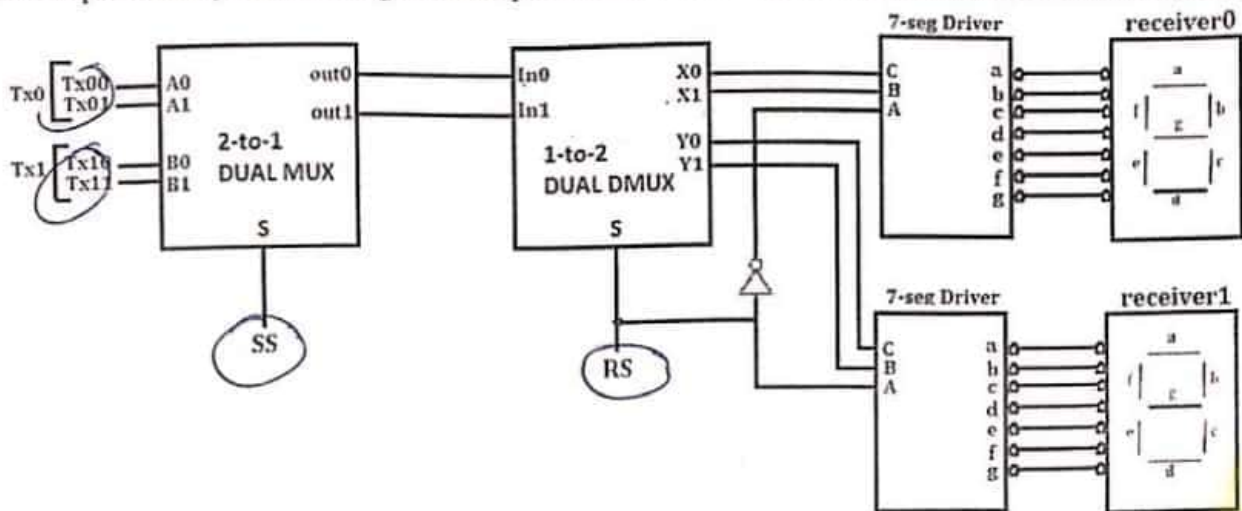


Figure1. 2- Bit TDM Communication Circuit

On the sender side, 2-to-1 dual multiplexer is used to determine which transmitter (Tx0 or Tx1) is allowed to send data. On the receiver side, 1-to-2 dual demultiplexer is used to determine which port (X which is connected to receiver0 or Y which is connected to receiver1) is used to receive data. Two 7-segment displays are connected to the receivers to display the value received (in decimal) if the receiver is selected. If the receiver is not selected, the (-) sign should be displayed on its 7-segment display.

The experiment is divided into four parts. First, you will implement the 2-to-1 dual multiplexer. Second, you will implement the 1-to-2 dual demultiplexer. In the third part, you will implement the 7-segment driver. Finally, you will instantiate these components to implement the overall circuit.


Part 1: 2-to-1 Dual MUX implementation.

- a) Fill-in the truth table for the 2-to-1 (1-bit) MUX shown in Figure 2.

S	I1	I0	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Figure 2. 2-to-1 MUX

(Pre Lab)

 

- b) Determine the output equation for the 2-to-1 MUX.

$$\text{out} = S I_0 + \bar{S} I_1$$

(Pre Lab)

- c) Implement the **2-to-1 MUX** using Verilog code **structurally** in a module named *mux1* inside the "mux1.v" file. This module should have 3 inputs (I1, I0, and S) and one output (out).
- d) Implement the **2-to-1 dual MUX** using Verilog code **structurally** in a module named *dualmux* inside the "dualmux.v" file by instantiating two instances from the module *mux1* according to Figure 3. This module should have 5 inputs (A1, A0, B1, B0, and S) and 2 outputs (out1, out0).

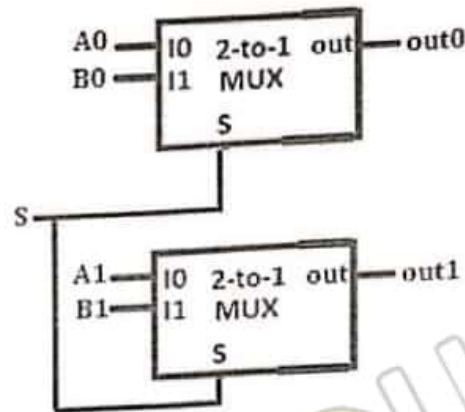


Figure 3.2-to-1 Dual MUX

$$\sum_{w_2} + \sum_{w_3}$$

Part 2: 1-to-2 Dual DMUX implementation.

- a) Fill-in the truth table for the 1-to-2 (1-bit) DMUX shown in Figure 4.

S	D	\bar{Y}	Y	\bar{X}	X
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	0	0	0
1	1	1	1	0	0

(Pre Lab)

 


Figure 4.1-to-2 DMUX

- b) Find the equations of outputs X and Y for the 1-to-2 DMUX module.

(Pre Lab)

$$Y = SD \quad X = \bar{S}D$$

- c) Implement the **1-to-2 DMUX** using Verilog code **structurally** in a module named *dmux1* inside the "dmux1.v" file. This module should have 2 inputs (D and S) and 2 outputs (X and Y).

- d) Implement the **1-to-2 dual DMUX** using Verilog code **structurally** in a module named *dualdmux* inside the "dualdmux.v" file by instantiating two instances from the module *dmux1* according to Figure 5. This module should have 3 inputs (In1, In0, and S) and 4 outputs (Y1, Y0, X1, and X0).

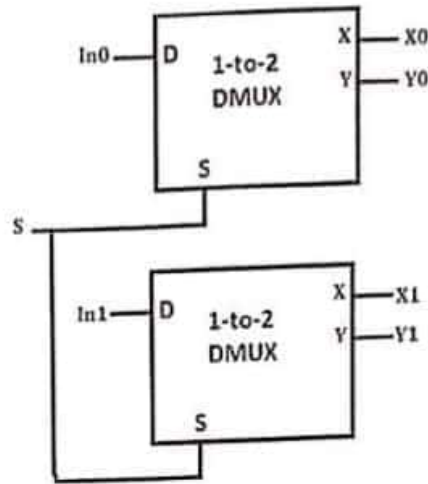


Figure 5. 1-to-2Dual DMUX

Part 3: 7-segment Driver implementation.

The 7-segment driver of this circuit has three inputs: A, B, and C. Input A represents a control signal which identifies whether the receiver represented by the corresponding display is selected to receive data or not.

- If A=0, then regardless of the values of B and C, a dash symbol (-) should be displayed to indicate that this receiver is not receiving data. (Dash symbol can be generated by making segment "g" ON and turn off all the remaining segments)
- If A=1, then the decimal value corresponding to the received bits (B and C) should be displayed.

a) Fill-in the truth table for a common anode 7-segment driver according to these specifications: (Pre Lab)

A	B	C	a	b	c	d	e	f	g
0	0	0	1	1	1	1	1	1	0
0	0	1	1	1	1	1	1	1	0
0	1	0	1	1	1	1	1	1	0
0	1	1	1	1	1	1	1	1	0
1	0	0	0	0	0	0	0	0	1
1	0	1	1	0	0	1	1	1	1
1	1	0	0	0	1	0	0	1	0
1	1	1	0	0	0	0	1	1	0

$$\begin{aligned}
 a &= \bar{A} + (\bar{B}C) \\
 b &= \bar{A} \\
 c &= \bar{A} + BC \\
 d &= \bar{A} + (\bar{B} \cdot C) \\
 e &= \bar{A} + C \\
 f &= \bar{A} + B + C \\
 g &= A + \bar{B} + \bar{A}\bar{B}
 \end{aligned}$$

b) Implement the driver using Verilog code **behaviorally** in a module named *segdriver* inside the "segdriver.v" file. This module should have 3-inputs: A, B and C (where A is the MSB) and 7-outputs (a, b, c, d, e, f, and g).

Part 4: Final Circuit Implementation.

a) Implement the whole circuit which is shown in Figure 1 using Verilog code **structurally** in a module named *circuit1* inside the "circuit1.v" file. This module should have:

- 6-inputs (Tx01, Tx00, Tx11, Tx10, selection lines SS and RS) which are connected to switches.
- 14-outputs:
 - ❖ 7: (a, b, c, d, e, f, g) for (receiver 0) 7-segment display.
 - ❖ 7: (a1, b1, c1, d1, e1, f1, g1) for (receiver 1) 7-segment display.

b) Make the pins assignment for your inputs and outputs (as shown below).

7-Segment pins: Hex3 (RECEIVER 0):		
a1	oHEX3_D[0]	PIN_P6
b1	oHEX3_D[1]	PIN_P4
c1	oHEX3_D[2]	PIN_N10
d1	oHEX3_D[3]	PIN_N7
e1	oHEX3_D[4]	PIN_M8
f1	oHEX3_D[5]	PIN_M7
g1	oHEX3_D[6]	PIN_M6
7-Segment pins: Hex 4 (RECEIVER 1):		
a	oHEX4_D[0]	PIN_P1
b	oHEX4_D[1]	PIN_P2
c	oHEX4_D[2]	PIN_P3
d	oHEX4_D[3]	PIN_N2
e	oHEX4_D[4]	PIN_N3
f	oHEX4_D[5]	PIN_M1
g	oHEX4_D[6]	PIN_M2

Input Switch:		
Tx00	iSW[1]	PIN_AB26
Tx01	iSW[2]	PIN_AB25
Tx10	iSW[5]	PIN_AC24
Tx11	iSW[6]	PIN_AC23
SS	iSW[8]	PIN_AD24
RS	iSW[9]	PIN_AE27

c) Download your Verilog program on FPGA and test it.