

- * Electrical machines (2): concerned with ac machines.
- * Recently more than 90% of motor are ac.

- * Two major types: 1) Induction Machines.
 - mainly used as Motors.
 - Also called Asynchronous Machine.
 - pure ac machine. (no Dc.)
 - special case → in wind farms as Generator.

2) Synchronous Machines.

- mainly used as Generators in power stations.
- Motor usage for (p.f.) correction.

Both types depends upon the Rotating Field principles.

- This implies that: the Stator (Armature) converts power. { Stator } called of both types is identical.


- Most of these Machines are 3-phase, you can have poly phase machines but 3 phase is the most common.
- Single phase Induction motor is a common type used in domestic applications.

Induction.

- 2 - 3-phase motors \Rightarrow Equivalent to one single phase Induction motor.
- non-self starting machine. *علاوة على ذلك*
- some motors have 2 capacitors

Starting needs
P.F correction needs (condenser)

PF

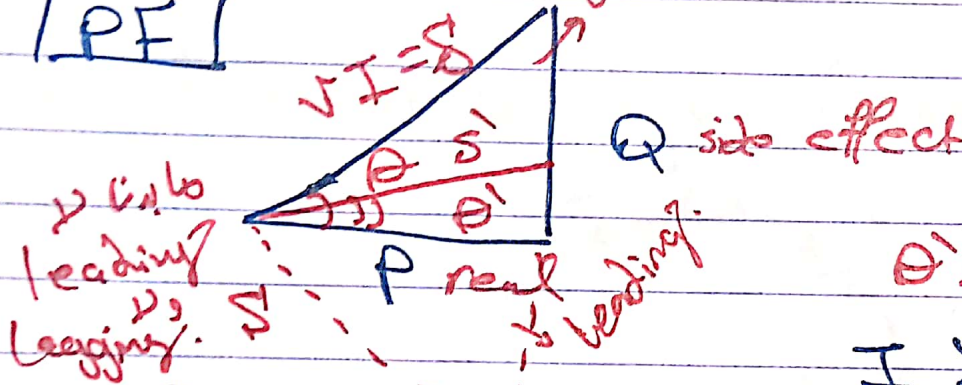


$$\theta' = \arccos \frac{P}{S}$$

$$I > I'$$

- PF capacitor bank in parallel
- condenser (over excitation) (motor): PF leading
- Static VAR compensation (power electronics.)

Condensers

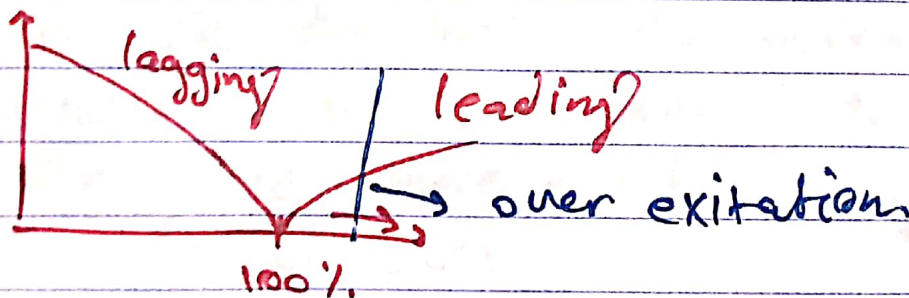


Rotating Field {CHI}

Synchronous or Induction Motors \rightarrow comprises


- ① Stationary Elements common for both types. (Armature)
- ② Rotating Elements.

Armature Structure.

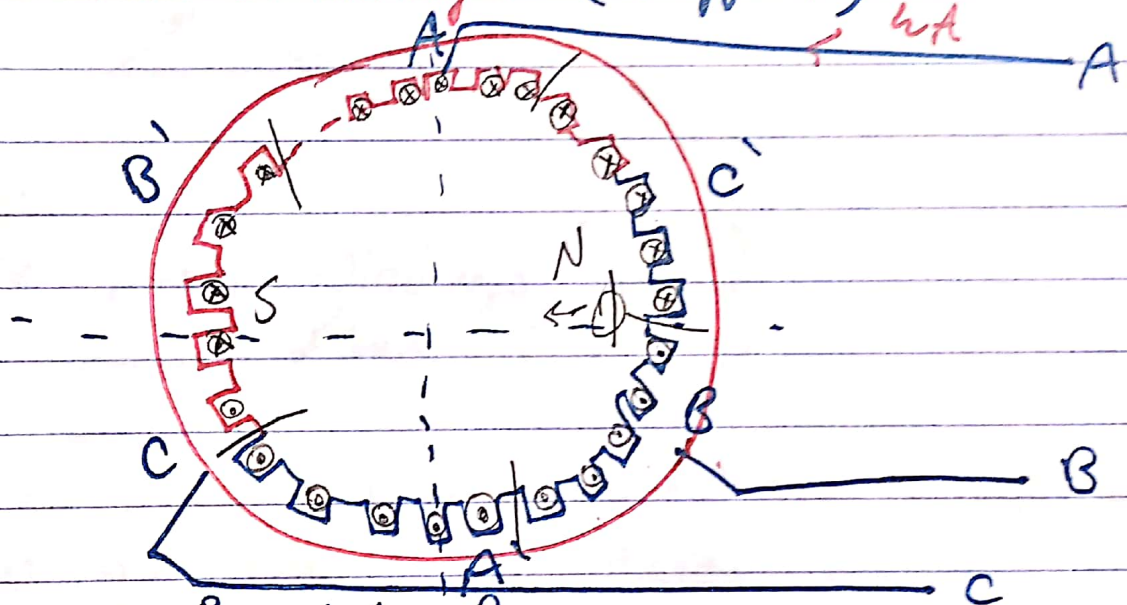- o Cylindrical core (Ferromagnetic)
- o Armature windings (copper)



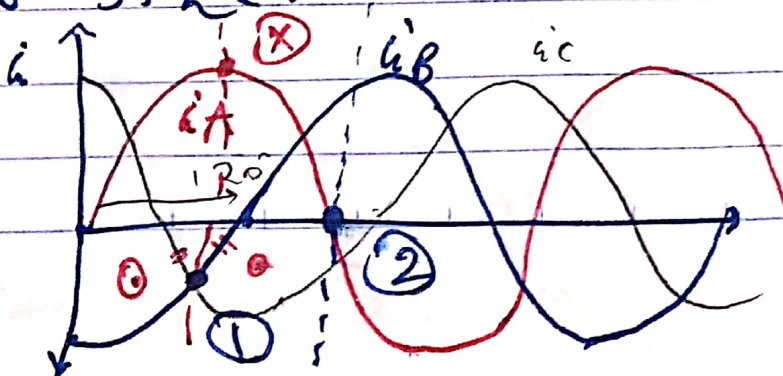- o after 120° slot B.
- o we use the metal to increase slots \rightarrow more inductors, Uniform distribution for the field, more EMF ---
- o number of slots depends on the machine & its size.





التيار \odot \otimes
 حسب اللحظة
 التي تأخذها. ωt

→ $\sum i_A + i_B + i_C = 0$

if current in the negative side (cycle) then \odot , if the current in the positive side (cycle) \otimes .

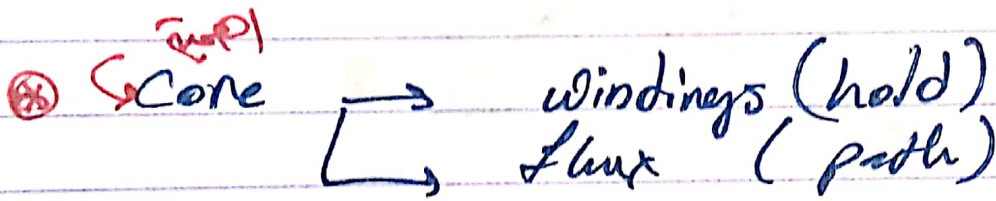
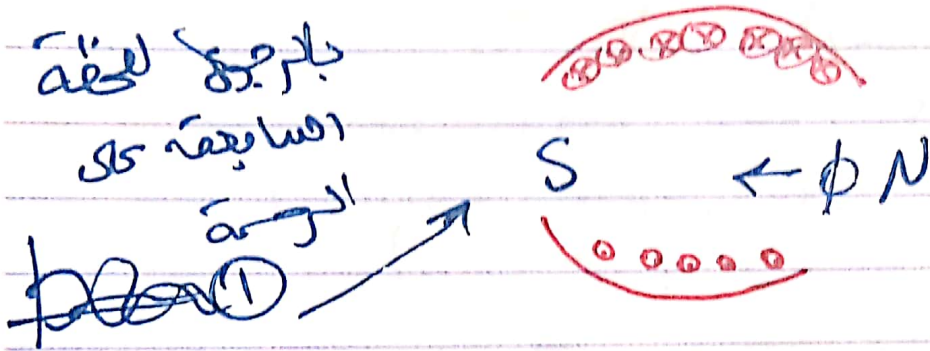
\otimes Flux ϕ as if there is only two poles.



→ In DC machines the poles are physical placed by the manufacture.

→ In AC machines the poles are created by operation & # of poles are controlled by the windings.

\otimes بالرغم من أن (2) للتيار

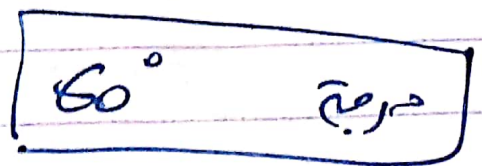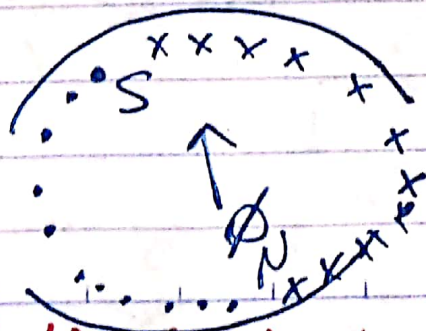

Rotating Field fixed Amplitude but rotating direction with time.

Q. How do we change CW \rightarrow CCW rotation


Ans. we change the phase sequence

$A \rightarrow A, B \rightarrow C, C \rightarrow B.$

Principles of Rotating Field in


3-ph machines.

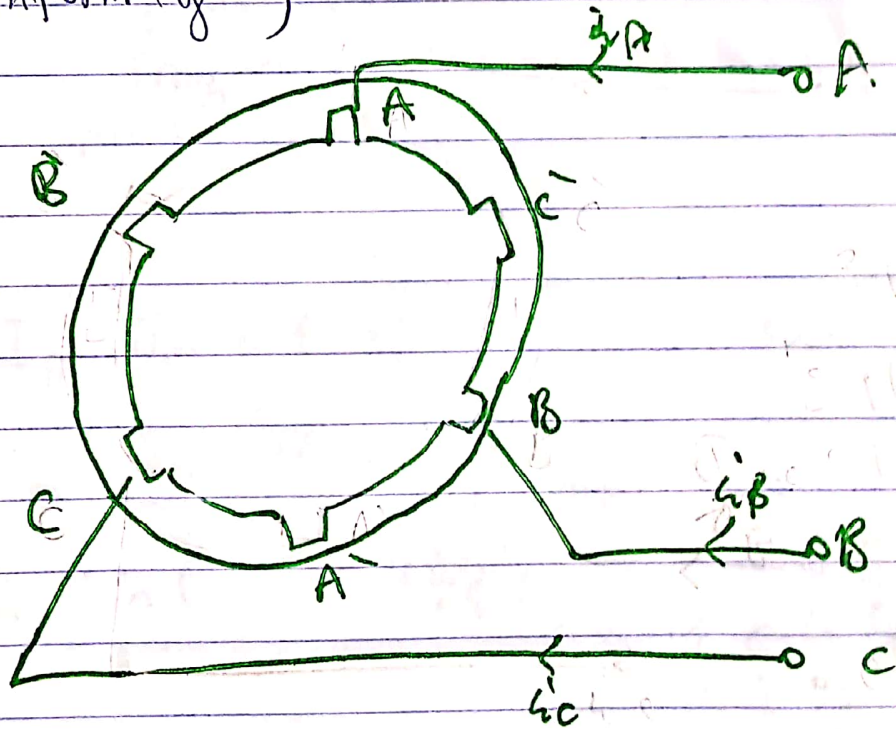- Use concentrated coils for simplicity (practically, coils are distributed uniformly)




Each coil is shifted by 120° (two poles machine)

Y-connection.

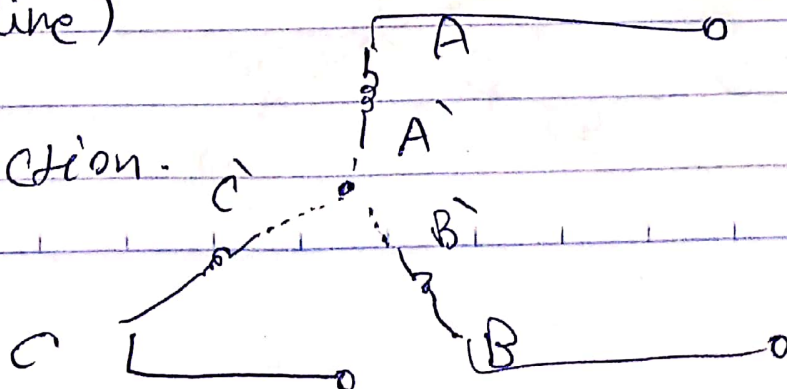

* Wave Form

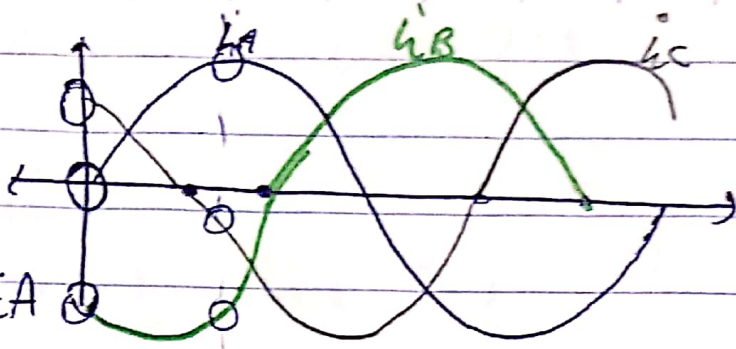

reluctance




$$F = \phi R_m$$

CASE A ($\omega t = 0^\circ$)

$$i_A = I_m \sin \omega t \Rightarrow F_A = N \phi \cdot I_m \cdot \sin \omega t = F_m \sin \omega t$$

$$i_B = I_m \sin(\omega t - 2\pi/3) \Rightarrow F_B = F_m \sin(\omega t - 2\pi/3)$$
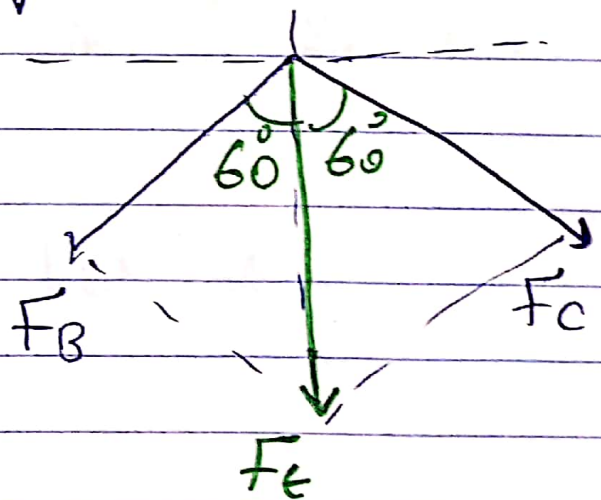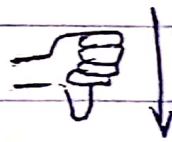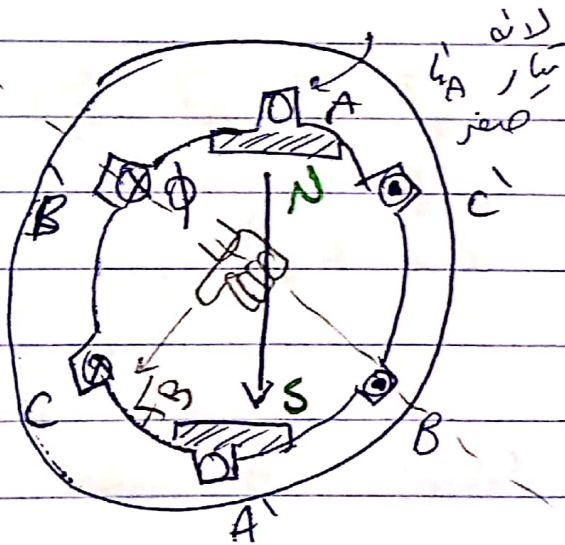
$$i_C = I_m \sin(\omega t - 4\pi/3) \Rightarrow F_C = F_m \sin(\omega t - 4\pi/3)$$



* $F_{e \text{ total}} = 1.5 F_{mph}$



* the angle of this F_e is zero ($\omega t = 0^\circ$)

CASE B ($\omega t = 90^\circ$)

$$\vec{F}_A = F_m$$

$$F_B = F_m \sin(-30^\circ) = -\frac{1}{2} \cdot F_m$$
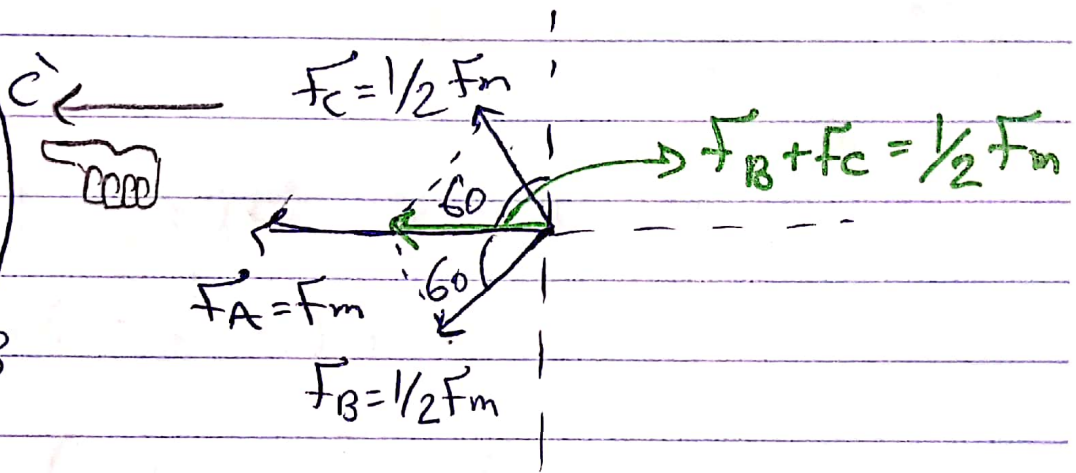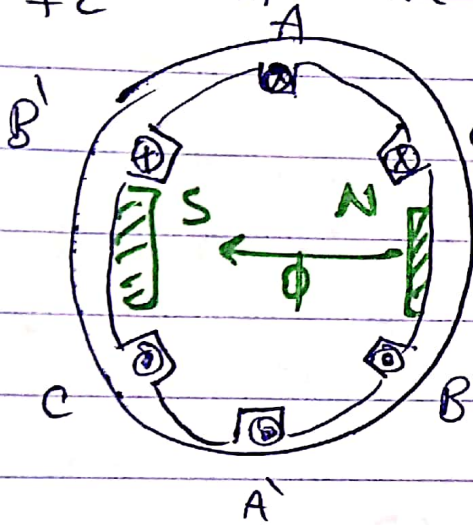
$$F_C = F_m \sin(210^\circ) = -\frac{1}{2} \cdot F_m$$





$$\vec{F}_C = \vec{F}_A + \vec{F}_B + \vec{F}_C$$

$$\frac{1}{2} F_m + F_m = 1.5 F_m \text{ in } \vec{F}_A \text{ direction.}$$

Homework: Solve for 135° #

Solution to homework 3

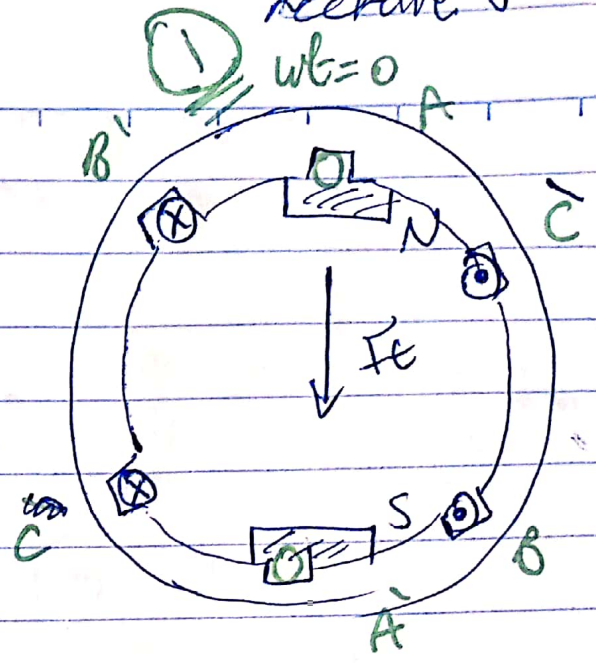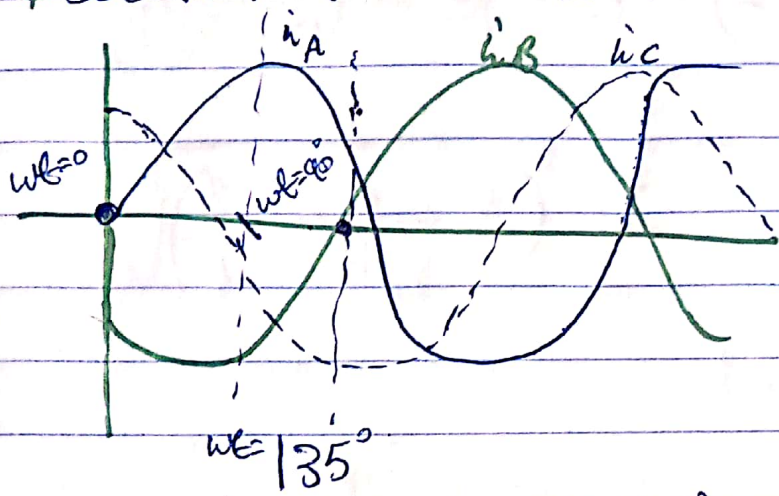

- 1) $\omega t = 0^\circ$ 2) $\omega t = 90^\circ$ 3) $\omega t = 135^\circ$

① $i_a = I_m \sin \omega t = I_m \sin 0 = 0$

$F_a = 0$

$i_b = I_m \sin (\omega t - 120^\circ) = I_m \sin (-120^\circ)$

$= \frac{-\sqrt{3}}{2} I_m$


نقطة بعيدا الاعتبار عن الرسم، الإيجاب

$i_c = I_m \sin (\omega t - 240^\circ) = I_m \sin (-240^\circ) = \frac{\sqrt{3}}{2} I_m$

Zero
 $\vec{F}_T = \vec{F}_a + \vec{F}_b + \vec{F}_c$

$F_T = \sqrt{F_b^2 + F_c^2 + 2F_b \cdot F_c \cos \phi}$

الزاوية بين

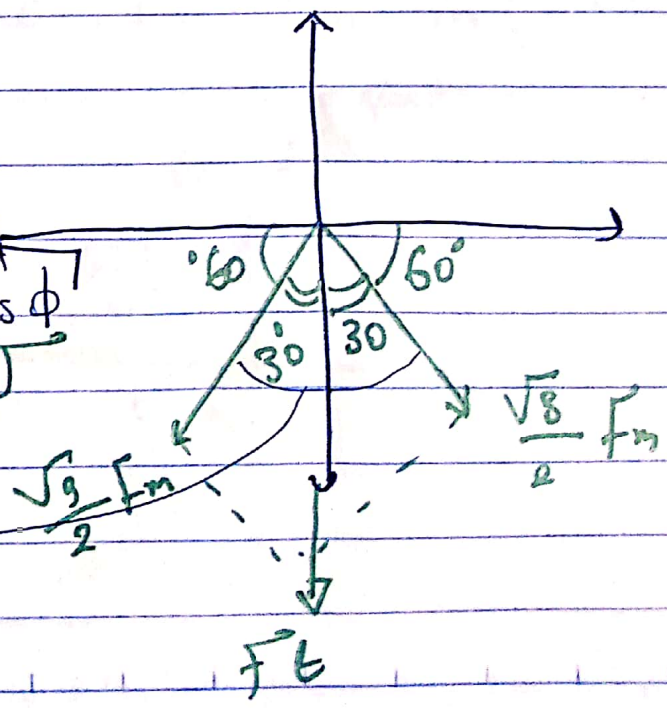

$$\sqrt{\left(\frac{\sqrt{3}}{2} F_m\right)^2 + \left(\frac{\sqrt{3}}{2} F_m\right)^2 + \left(2 \times \frac{\sqrt{3}}{2} \times \frac{\sqrt{3}}{2} \times \frac{1}{2}\right)}$$

$$\sqrt{\left(\frac{3}{4} + \frac{3}{4} + \frac{3}{4}\right) F_m^2} = \sqrt{\frac{9}{4} F_m^2} = \frac{3}{2} F_m$$

$$= 1.5 F_m \#$$

② $\rightarrow i_a = I_m \sin 90^\circ = I_m$

$$F_a = F_m$$

$$\rightarrow i_b = I_m \sin(90 - 120)$$

$$I_m \sin(-30) = -\frac{1}{2} I_m$$



له لكن لانه راجع لزاوية الارتفاع
معتاد، لان يكون اسالب بالقانون

$$F_b = -\frac{1}{2} F_m$$

$$\rightarrow i_c = I_m \sin(90 - 240) = I_m \sin(-150)$$

$$-\frac{1}{2} I_m$$

$$F_c = -\frac{1}{2} F_m$$

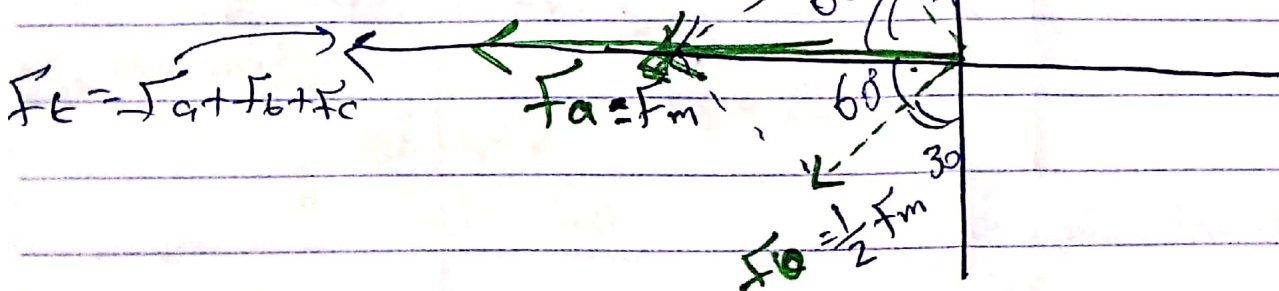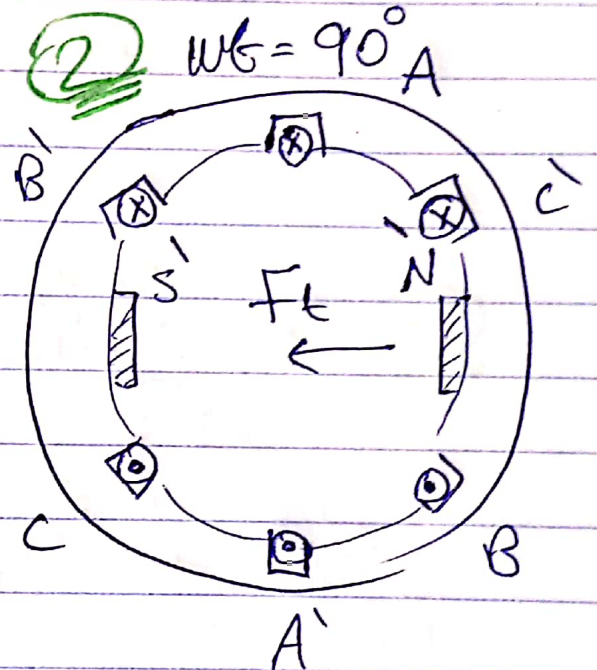

$$F_b + F_c = \sqrt{\frac{1}{4} F_m^2 + \frac{1}{4} F_m^2 + 2 \times \frac{1}{2} F_m \times \frac{1}{2} F_m \left(-\frac{1}{2}\right)}$$

$$F_b + F_c = \frac{1}{2} F_m$$

$$F = \omega \times N \phi$$

بعض الرضا لان كل واحد

$$F_t = \frac{1}{2} F_m + F_m = \frac{3}{2} F_m$$

مع لا Nph
الامplitude بال 60/1

* Rotation of F vector (poles) by 90°
From $\omega t = 0$ to $\omega t = 90$ clockwise

⊗ change phase sequence to change the direction of an AC machine.

$$F_t = 1.5 \text{ of } F_m / \text{phase.}$$

③ $\rightarrow i_a = I_m \sin(135^\circ)$
 $= 0.707 I_m$



$$F_a = 0.707 F_m$$

$\rightarrow i_b = I_m \sin(15^\circ)$
 $= 0.259 I_m$

$$F_b = 0.259 F_m$$

$\rightarrow i_c = I_m \sin(-105^\circ)$
 $= -0.966 I_m$

$$F_c = -0.966 F_m$$

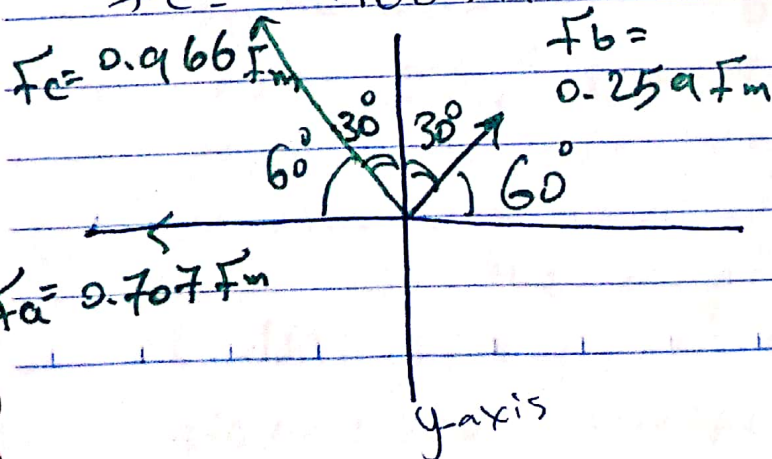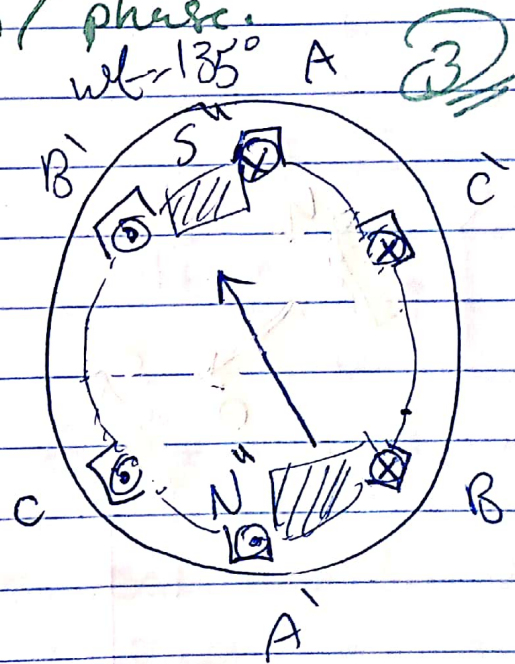


⊗ يجب ان نخلل سلاسل
x-axis

$$F_x = 0.707 F_m - 0.259 F_m \cdot \cos(60^\circ) + \dots$$

$$\dots 0.966 F_m \cos(60^\circ)$$


$$F_x = 1.06 F_m$$

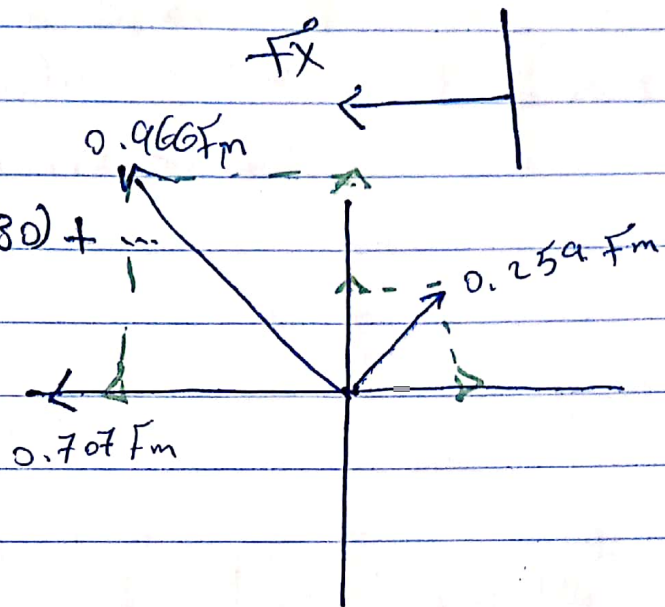


$$F_y = 0 + 0.966 F_m \cos(30^\circ) + \dots$$

$$\dots 0.259 F_m \cos(30^\circ)$$

$$F_y = 1.06 F_m$$

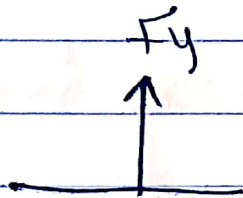
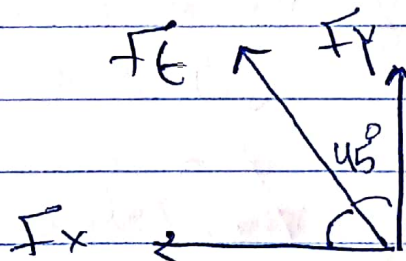
$$F_t = \sqrt{(1.06^2 + 1.06^2) F_m} = 1.5 F_m$$



When 3 windings are used and distributed in stator (Armature) of a 3-ph machine with a displacement of 120° shift and supplied by 3-ph ^{positive} sequence balanced supply an MMF is created such that:

① The Amplitude of the total MMF is 150% of the amplitude of the maximum of MMF per phase ($F_t = 1.5 F_m$ (ph)).

(This is fixed irrespective of time.)

② The MMF Vector is rotating (Rotating Field) clock-wise at a fixed speed same as the electric speed of the supply

⊗ currents Under this condition the MMF (vector speed) $\omega_m = \omega_{\text{electric speed}}$

$$\omega_m = 2\pi f \omega$$


↑
Supply Frequency

⊗ Field speed decided by the supply frequency.

⊗ Under the given structure a non physical poles are created (N and S)

⊗ To change the number of poles, more slots and windings are required

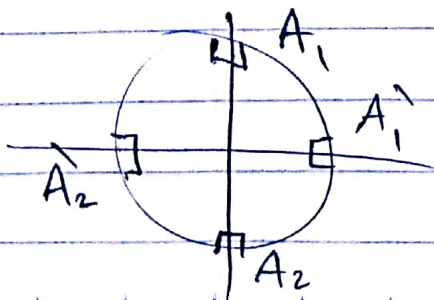(6 instead of 3) & (60° shift degree instead of 120° is applied),




Homework, old homework but change the sequence $\omega t = 0^\circ$ & $\omega t = 90^\circ$


$$\begin{aligned} i_a &\rightarrow i_c \\ i_b &\rightarrow i_c \\ i_c &\rightarrow i_b \end{aligned}$$

$\omega_m = \frac{1}{p} \omega$ $\omega \rightarrow$ electric, where p : No. of poles pairs.



Second Homework Solution.

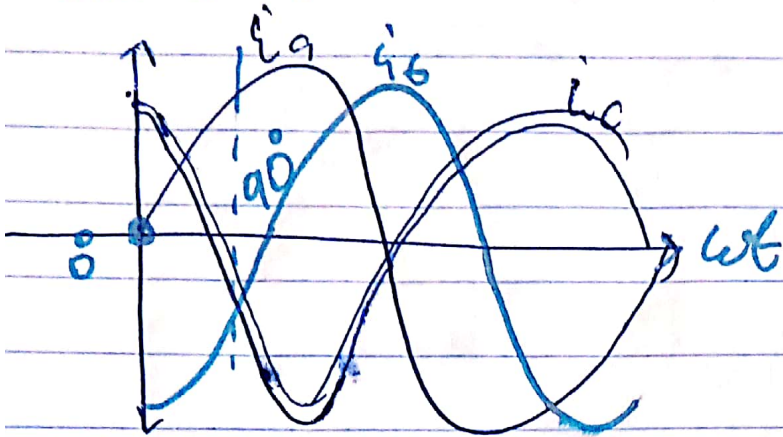


$\omega t = 0$

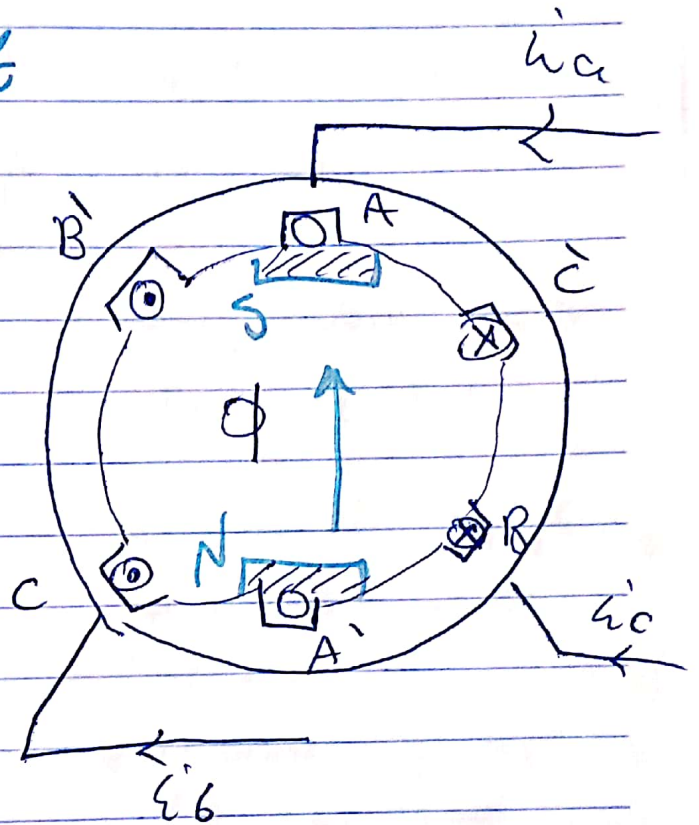

$\omega t = 90$

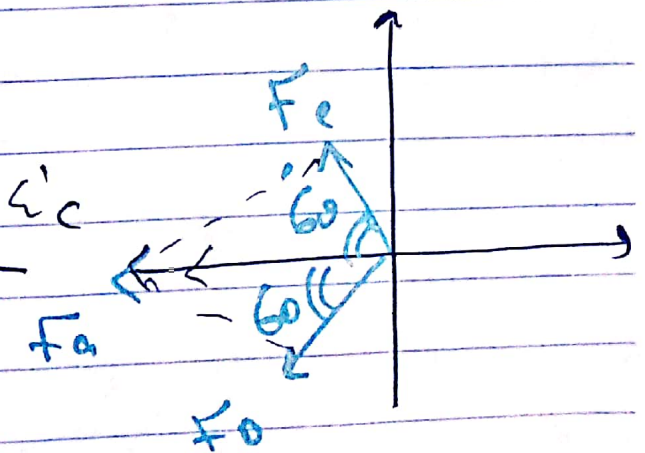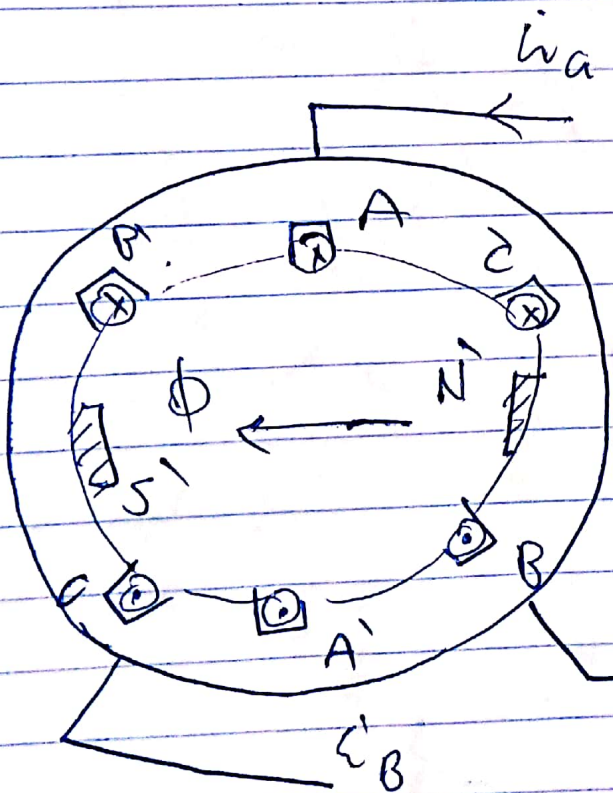

Structure required to create 4 poles.

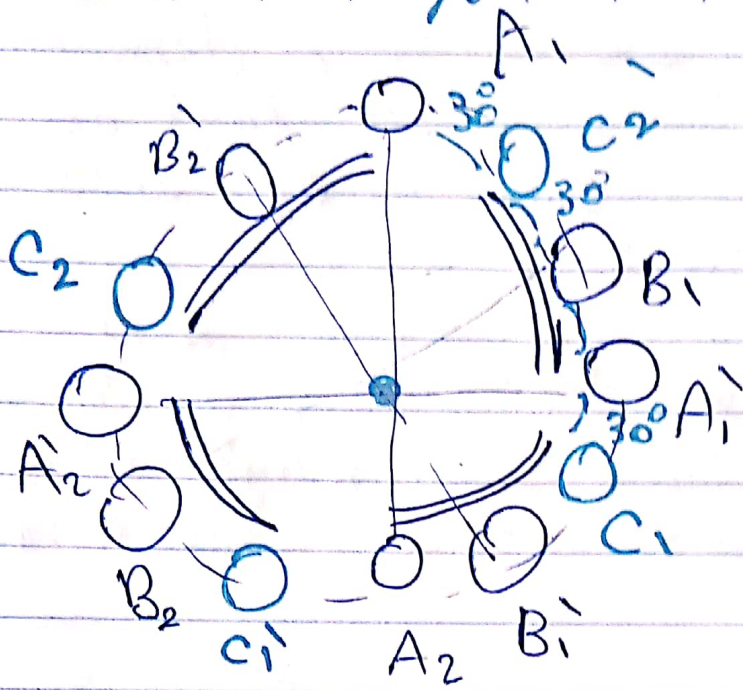

$A_1 \& A_2$ 180°

$A_1 \& A_1'$ 90°


$A_1 \& B_1$ 60°

$A_1 \& C_1$ 120°


* i_A will enter both $A_1 \& A_2$

⑩ Connecting $A_1 \& A_2$ in parallel \rightarrow high current

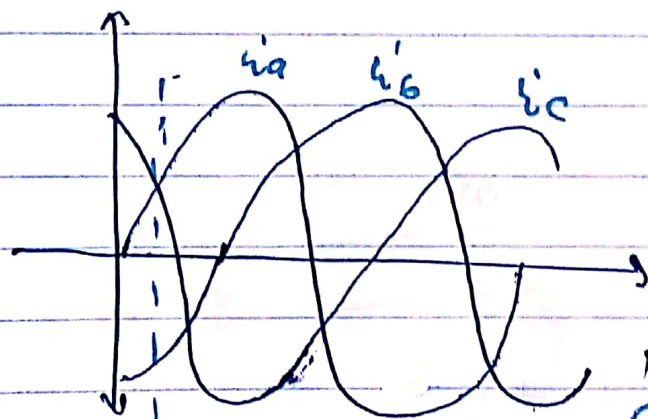⑪ connecting $A_1 \& A_2$ in series \rightarrow high voltage.



$\omega t = 30^\circ$

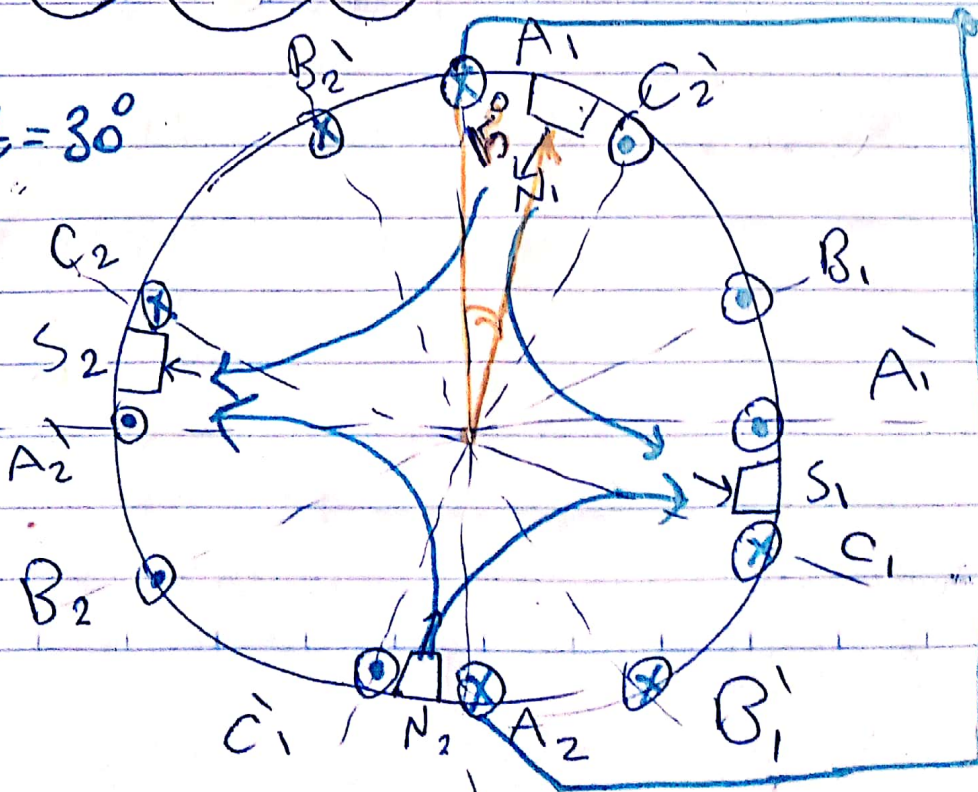

$V_f \rightarrow$
 N_1 القطب
 30°
 i_A هو i_s
 i_B هو i_s
2 pole

Inversely proportional ← rotating speed
to that of the field
of poles pairs.

$$\omega_m = \frac{\omega}{p}$$

electric speed
poles pair

in Asyn.
no dc.

In Synchronous machines, rotating field & rotor are the same (we add Dc to rotor).

$$\begin{aligned} A_1 \& B_1 \Rightarrow 1 \\ A_2 \& A_2 \Rightarrow 1 \\ B_1 \& B_1 \Rightarrow 1 \end{aligned} \rightarrow A = DA_1 \& A_2$$

2p


@ 60 Hz

@ 50 Hz


3600	3000	لا يقبل ان يكون 1000
1800	1500	
1200	1000	Integer عدد poles
900	750	
720	600	P=5
600	500	

600 بـ 600
P=6

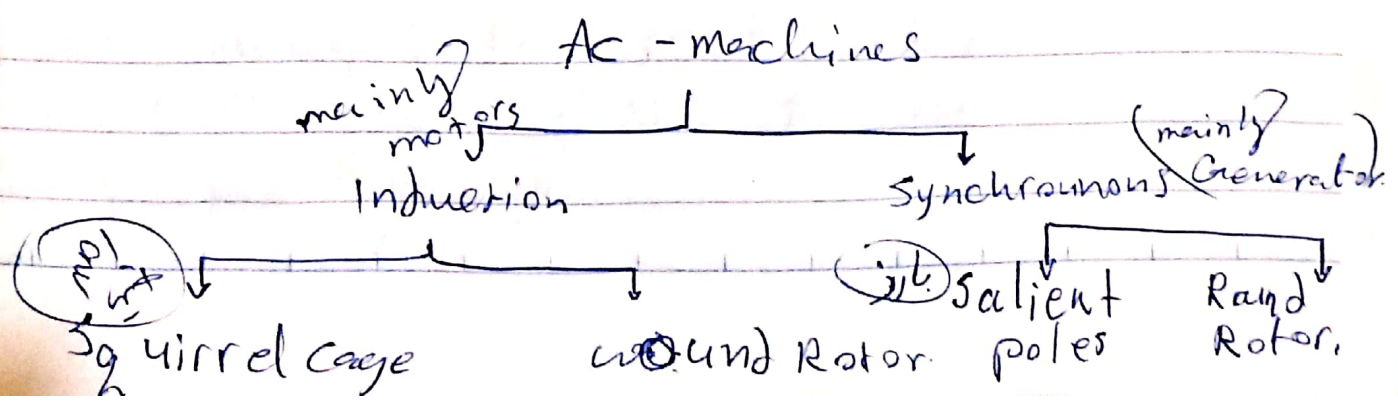
Induction machines. (Asynchronous machine)
الآلة التزامنية .
الآلة الكهربية .



Salient pole synchronous

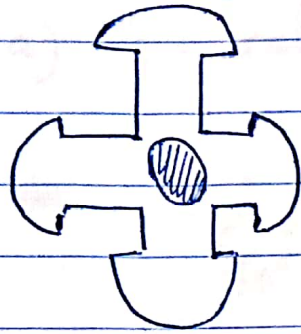


2-poles

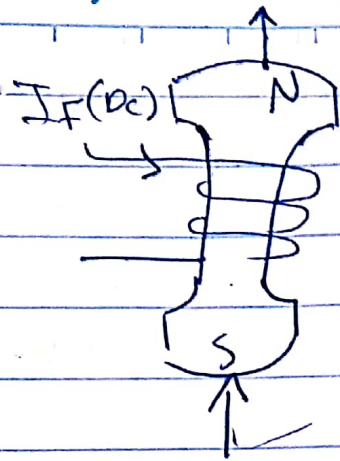

Single pole

Round rotor synchronous

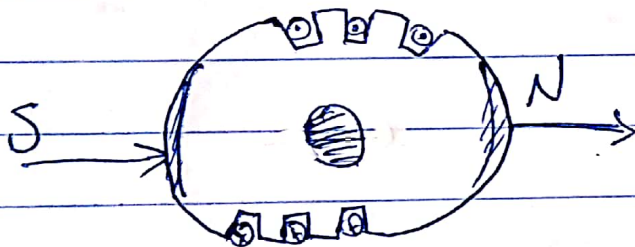

- 3 & single phase induction motor type squirrel cage are the most important types of motors.

Structure of induction machine

Stator : Armature


cylindrical core with slots. 3-ph windings are arranged to create rotating field at certain speed (No. of pole pairs) at certain frequency.

Rotor



a) Squirrel-cage

cu of AL


clips

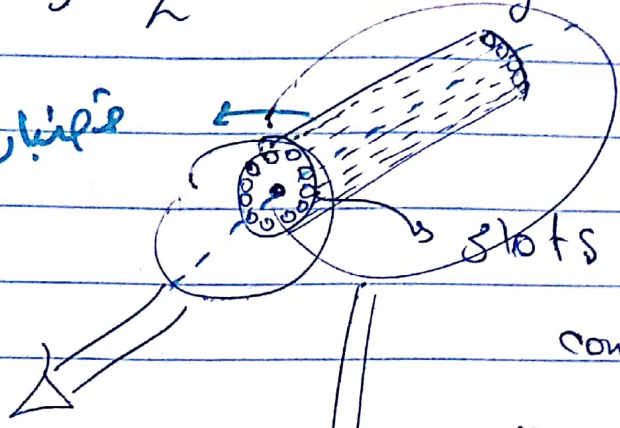

could be:
double cage ⇒

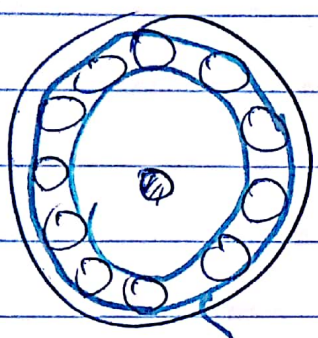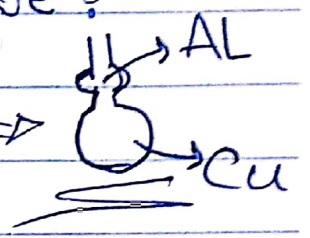


Short circuit ending ring

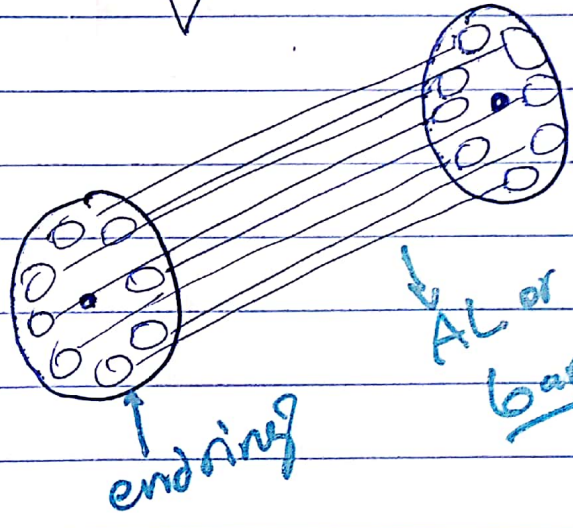

AL or Cu bars

b) Wound Rotor

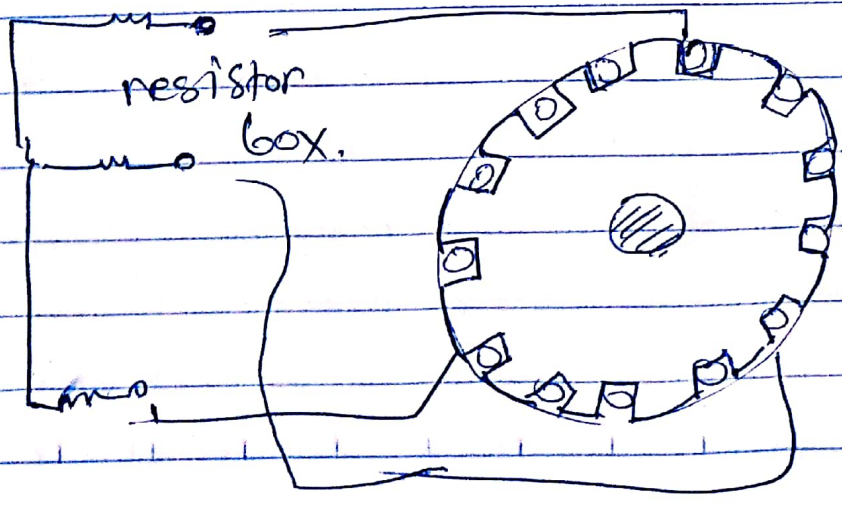


resistor box.

Inside the slots 3ph copper winding are existing

95% of AC Motors are Induction Squirrel-Cage motors.


Wound-Rotor Machine

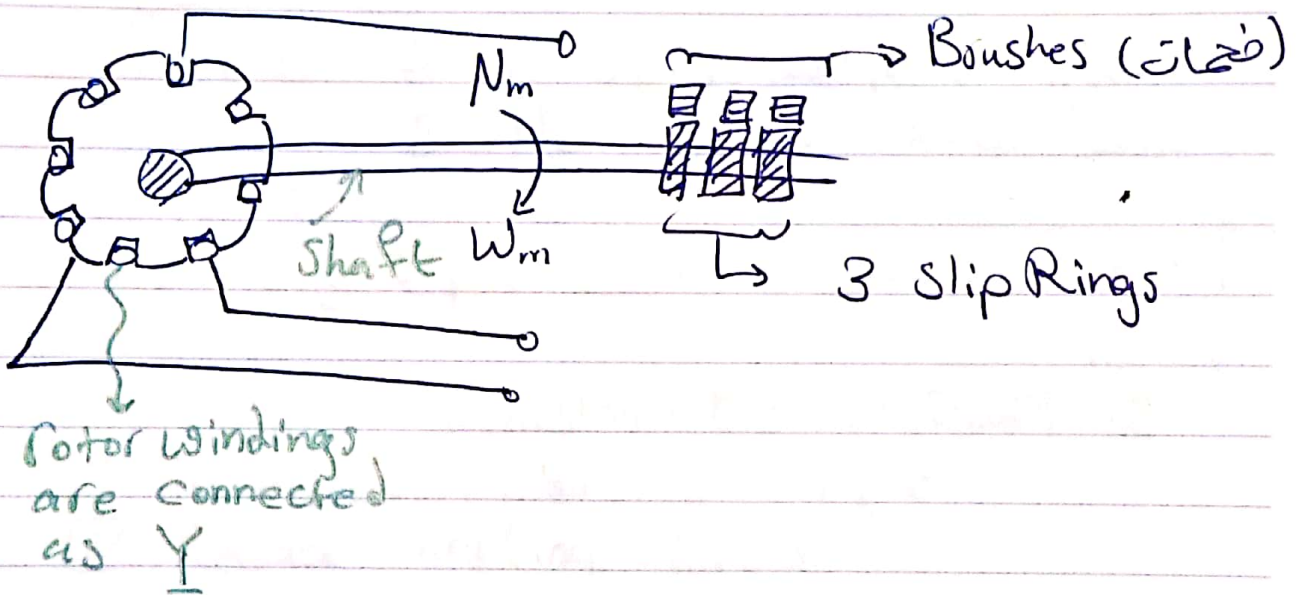

Slip Rings


Copper

منه برآ

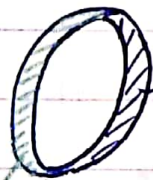

منه برآ ضلوع او
 ای کازل عنان یخزل
 ار Shaft

Sliders

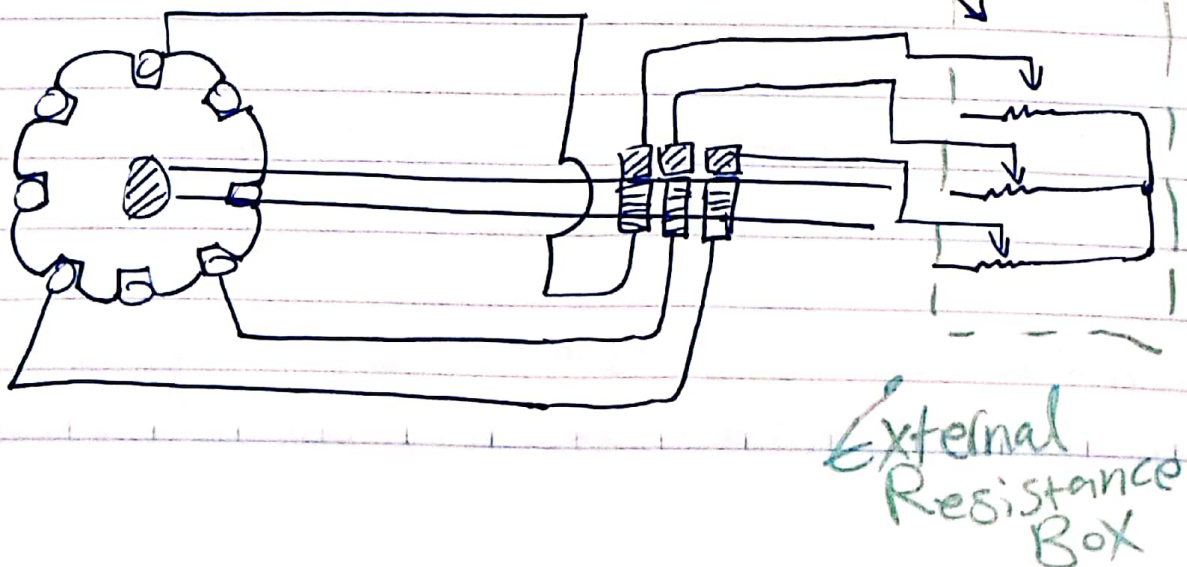


① Wound-rotor costs (2→3) cost of squirrel-cage. (2-3x)

② VVVF = Variable Voltage Variable Frequency control. (V.V.V.F)

Equivalent circuit Development.

Stator /ph Equivalent circuit.

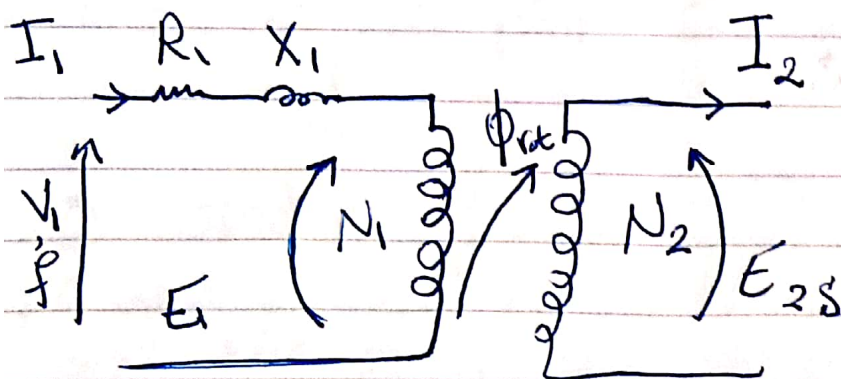

R_1 : Stator resistance /ph.

X_1 : Stator leakage reactance.

V_1 : applied supply voltage.

I_1 : Stator current.

$$X_1 = 2\pi f \cdot \underset{\substack{\uparrow \\ \text{leakage} \\ \text{inductance}}}{L_1}$$

$$E_1 = V_1 - I_1 \underbrace{(R_1 + X_1)}_{\substack{\text{small} \\ \text{drop}}}$$

E_{2s} : Induced EMF per Rotor phase at a slip (s) or a rotor speed (RPM)

⊙ When V_1 is applied, 3ph current will flow in the 3ph stator windings \rightarrow leading to rotating field Φ_{rot} . \rightarrow the speed of this rotating field $\underline{N_s}$

$$N_s = \frac{60f}{p}$$


f = Supply frequency cycles/sec.

p = # of pole pair

Stator.

⊙ windage (slip) & losses are present, therefore -- the power is reduced and the rotor will slip behind the field.

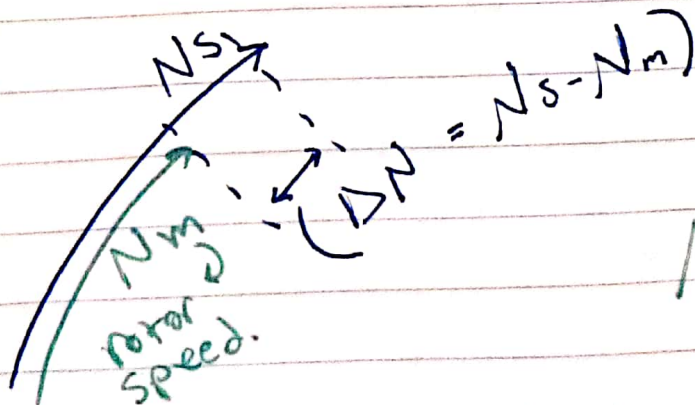I_2 : the rotor current per phase N_m or at a slip, (frequency f_2 = rotor frequency)



$N_m < N_s$ always.

at starting? $N_m \approx N_s$ 100% صرف
بیشتر

define Slip as

$$s = \frac{N_s - N_m}{N_s}$$

relative percentage of speed.

no load slip $\leftarrow 0.001 \ll s \ll 1 \rightarrow$ at starting or blocked rotor ②

\neq
~~Zero~~

\Downarrow
Losses


* s never equals zero \rightarrow no fraction!!
 \rightarrow no losses!!

\rightarrow normal slip values (s):

$$(0.03 \leq s_{rated} \leq 0.07)$$

$s \uparrow \rightarrow$ losses \uparrow
slip \uparrow \rightarrow $\frac{P_{loss}}{P_{in}}$

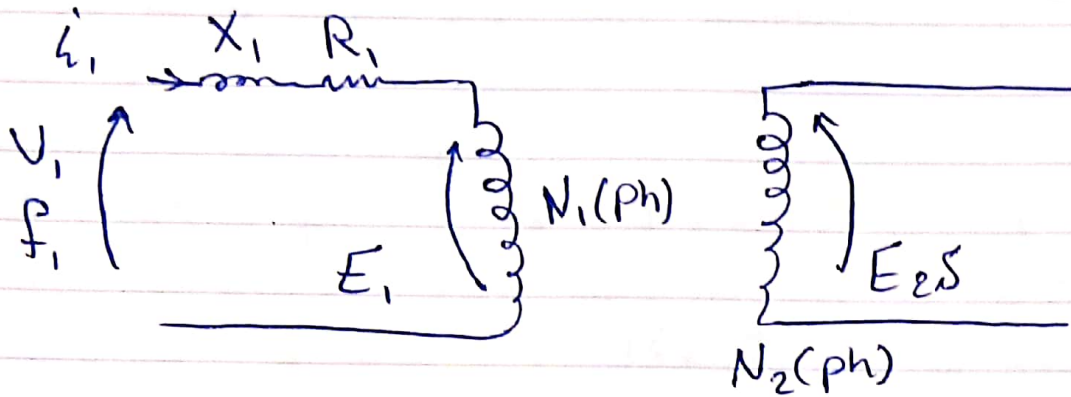Cont. 3-ph - Induction motor Equivalent circuit Development.



○ E_{2s} : Induced rotor EMF at rotor frequency.

○ $s = \frac{N_s - N_m}{N_s}$ → Per Unit (pu) or percentage.
Slip ↓

○ $s = 1 - \frac{N_m}{N_s}$, $N_s = \frac{60f}{p}$

○ $f_1 = \frac{p}{60} N_s$

○ Rotor frequency $f_2 = s f_1$

→ $N_m < N_s$ → due to (losses + load)

$s = \begin{cases} 1.0, & \text{at starting or at Blocked rotor.} \\ (0.03 \rightarrow 0.07), & \text{normal / rated / nominal.} \\ (0.07 \rightarrow 0.05), & \text{special design (rated).} \\ (0.001 \rightarrow 0.005), & \text{no load slip.} \end{cases}$ testing

Higher values of $s' \Rightarrow$ lower efficiency.

$$\eta \approx (1 - s') \equiv \text{approximate}$$

High slip (class D motors) \Rightarrow Slip (15%, 10%, 12% ...) (why?) to increase the starting Torque & decrease the starting current.


$$E_1 = 4.44 * K_{w1} * N_1(\text{ph}) * f_1 * \phi$$

\downarrow
 windings factor.

\rightsquigarrow rotor field

K_{w1} : depends on two things: \square Distribution factor.

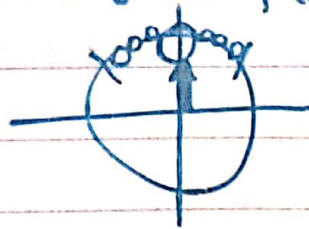Distance between slots \rightarrow flux \rightarrow \rightarrow \rightarrow



\square Skewing factor : to reduce 3rd Harmonics.

$$K_{d1} * K_{s1} = K_{w1} \approx 0.95.$$

$$\text{So, } E_{2s} = 4.44 K_{w2} * N_2(\text{ph}) * f_2 * \phi$$


$$E_{2s} = 4.44 K_{w2} * N_2(\text{ph}) * (s * f_1) * \phi$$

$$E_{2s} = (4.44 k \omega_2 N_2(\text{ph}) * f_1 * \phi) s$$

induced EMF @ supply frequency.

$$E_{2s} = E_2 * s$$

Back to the Equivalent circuit.

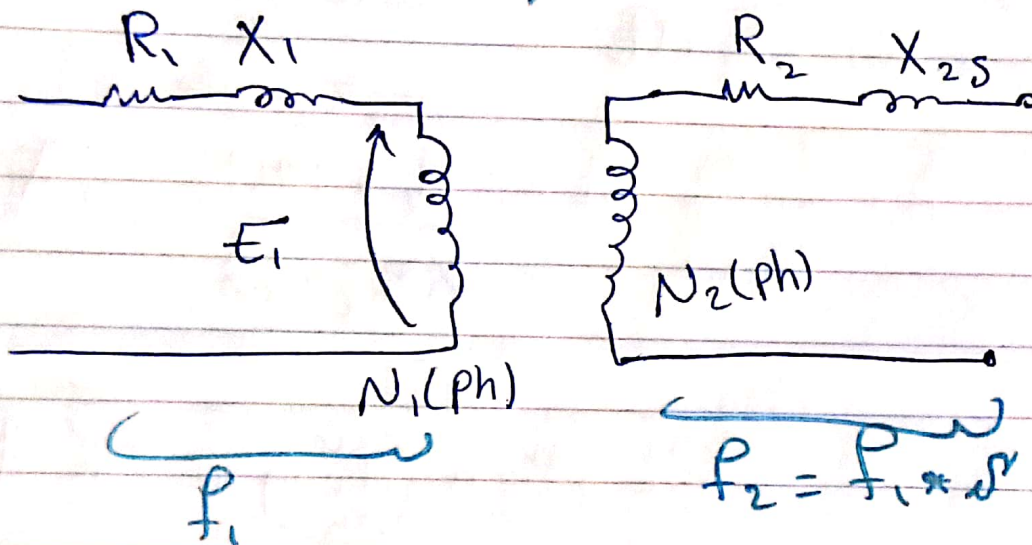


R_2 : Rotor resistance per phase.

X_{2s} : leakage reactance at slip (rotor frequency)

$$\begin{aligned} X_{2s} &= \omega_2 L_2 \\ &= 2\pi f_2 L_2 \\ &= 2\pi (s, f_1) L_2 \\ &= \underbrace{2\pi f_1}_{\omega_1} * L_2 * s \end{aligned}$$

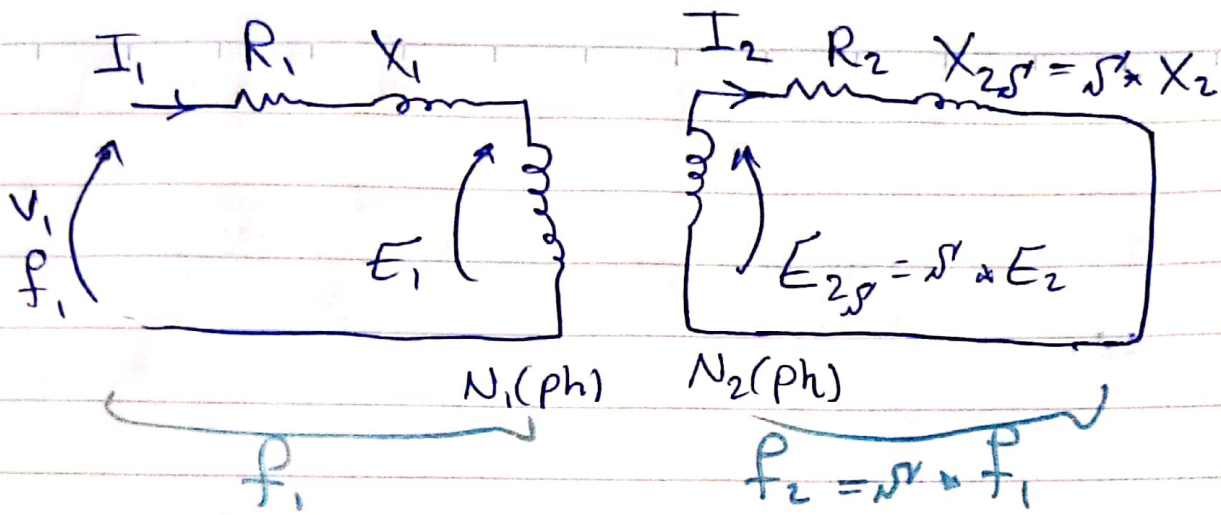$X_{2s} = s X_2$, X_2 : rotor reactance @ supply frequency.
 usually $\approx X_1$



$$I_2 = \frac{E_{2s}}{R_2 + jX_{2s}} \quad \text{--- (A)}$$


$$I_2 = \frac{s \cdot E_2}{R_2 + j s X_2}$$

$$I_2 = \frac{E_2}{\frac{R_2}{s} + jX_2} \quad \text{--- (B)}$$

$$A \equiv B$$

Equivalent

(B) \Rightarrow Equivalent circuit

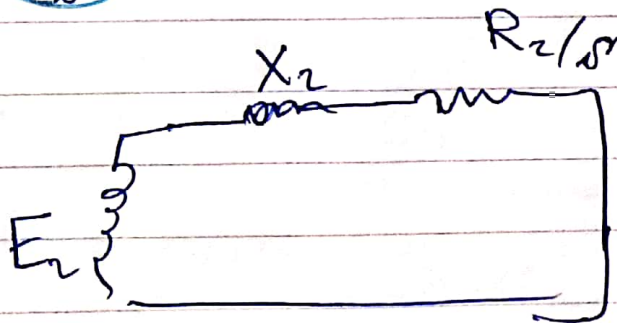

rotor circuit @ Supply frequency.


$$\frac{R_2}{s} = R_2 + \text{??} \rightarrow \text{real mechanical (load) Power.}$$

$$\text{??} = \frac{R_2}{s} - R_2 \Rightarrow R_2 \left(\frac{1}{s} - 1 \right)$$


$$\text{[or]} R_2 \left(\frac{1-s}{s} \right) = \text{real mechanical (load) power.}$$

Modified Rotor Equivalent circuit.

@ supply frequency.

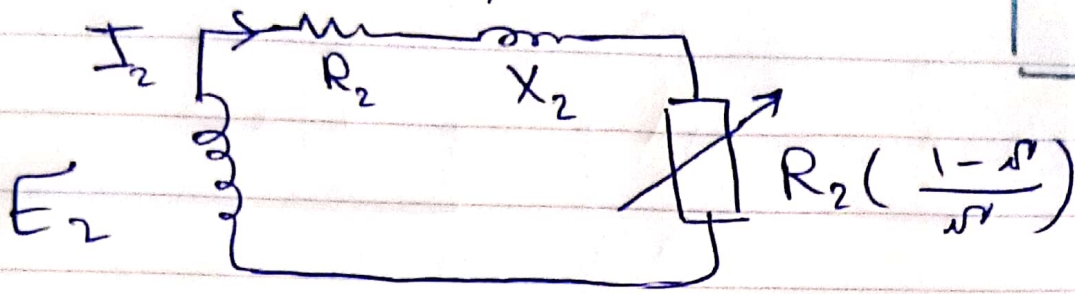

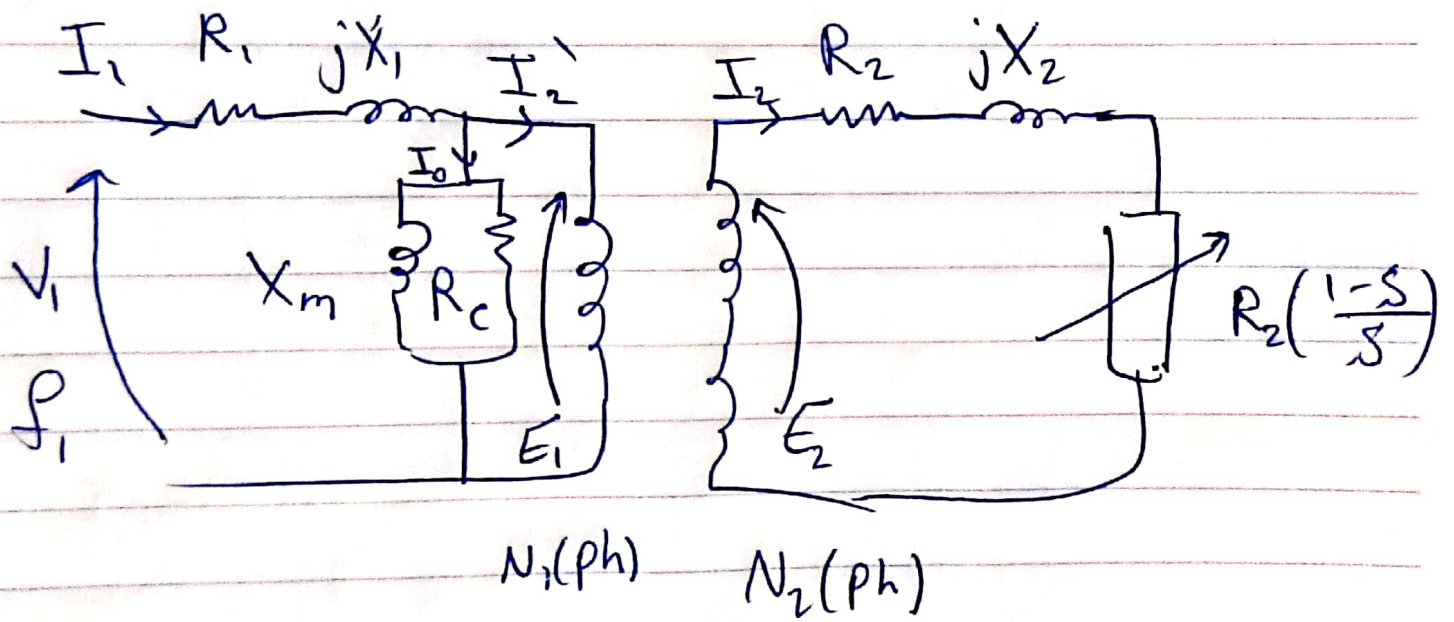- $R_2 \left(\frac{1-s}{s} \right)$, Mechanical load Equivalent Resistance.
- $I^2 \left(R_2 \left(\frac{1-s}{s} \right) \right) = \text{mechanical power}$



- X_m : mutual inductance.
- R_c : Losses
- I_0 : no load current.

$$I_{nl}(IM) \gg I_{nl}(Tr)$$

(no load)

(30-40)%

I_{rated} in Induction Motor.

(3-5)%
 I_{rated} in Transformer

BIG Disadvantage.

بسبب Power Q لكن

● If asked in Exam to justify? (why 30-40%)

ans. ① due to airgap existance.

Impact

② more reluctance,


③ $L = \frac{N^2}{R_m}$, ($L_{IM} \ll L_{Tr}$)

④ $X_m \ll X_m(Tr)$
(I_m)

⑤ $I_m(IM) \gg I_m(Tr)$

Therefore, no load current.

Referre all values to stator side.

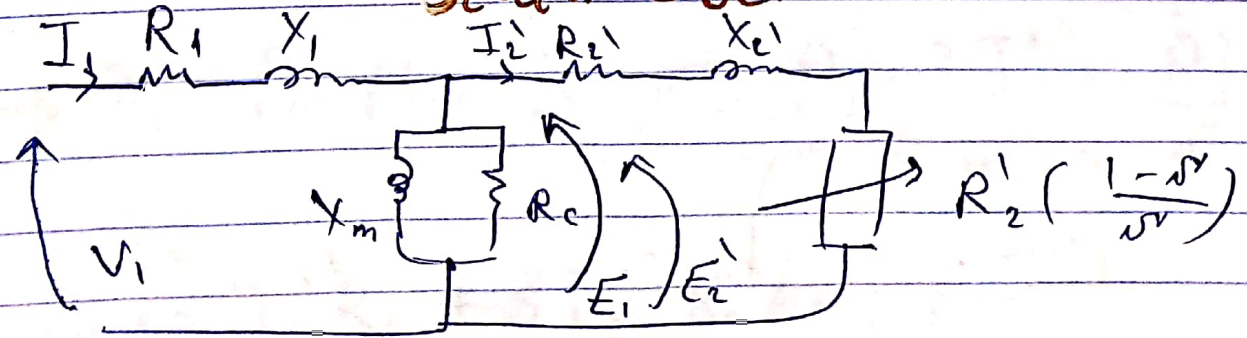


← X_2, R_2 referred.

• We can't move the magnetization branch

دورتي كسر V_1 ، I_1 ، $\cos \phi$ اب، V_2 ، I_2 ، $\cos \phi$ الى

Power Flow Diagram.

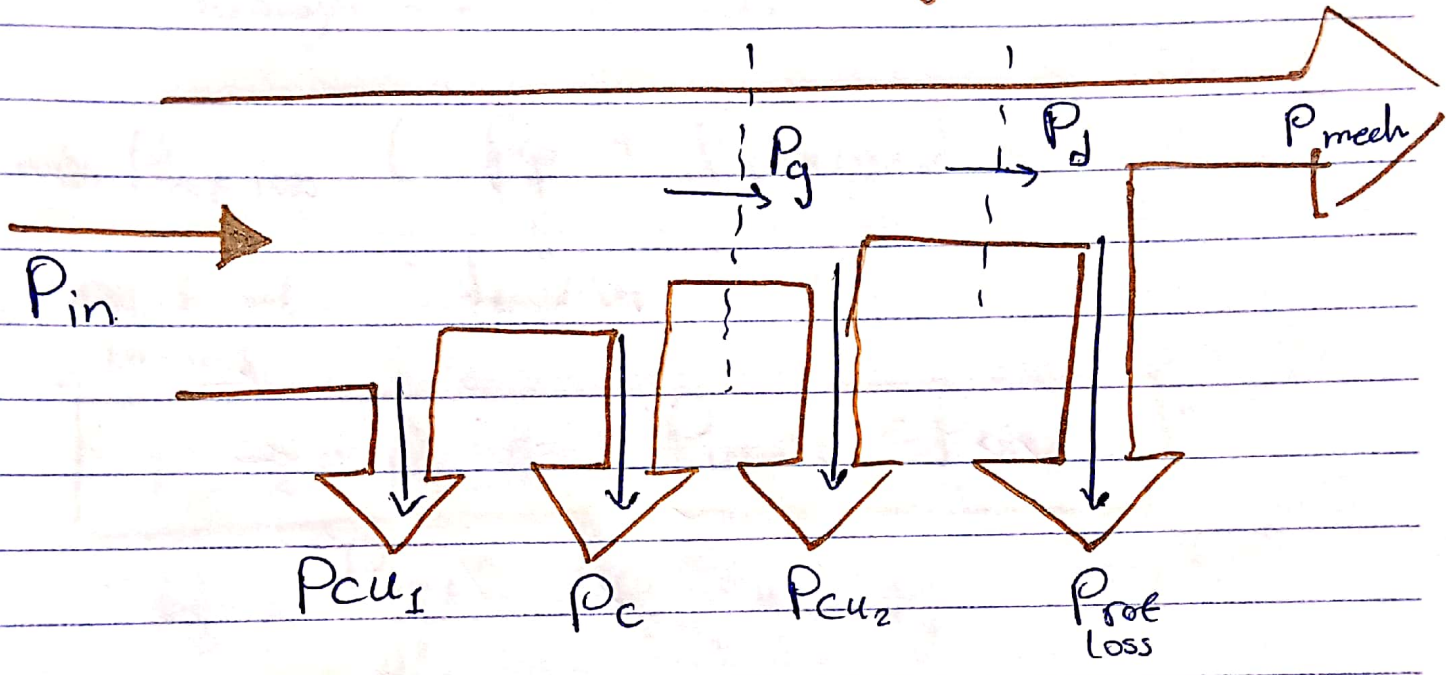

→ $P_{in} = 3 I_1 V_1 \cos \phi$

→ $P_{cu1} = 3 I_1^2 R_1$

→ $P_c = I_c^2 R_c = \frac{E_1^2}{R_c}$

→ $P_g = P_{in} - P_{cu1} - P_c$ [or] $P_g = 3 I_2'^2 \frac{R_2'}{s}$

↳ air gap Power
flux) الى ω سبب

$P_g = 3 I_2'^2 R_2' + 3 I_2'^2 R_2' \left(\frac{1-s}{s} \right)$

P_{cu2}

developed electromechanical power.

$$P_g = 3 I_2'^2 \cdot \frac{R_2'}{s} \quad *$$

• $P_g \equiv$ power Transferred from stator to rotor through the air gap.

→ $P_{rot \text{ loss}} (P_f + P_{\text{windage}})$
 ↓ rotational losses. ↓ friction

$$P_{\text{mech}} = P_{\text{shaft}} = P_{\text{output}} = P_{\text{load}}$$

← written on name plate.

$$P_g = \frac{P_{cu_2}}{s}, \quad P_{cu_2} = s P_g$$

* if slip (s) ↑ \rightsquigarrow $P_{cu} \uparrow \rightsquigarrow$ $\eta \% \downarrow \downarrow$, therefore, we want s as small as possible in order to have high efficiency $\eta \%.$

$$\rightarrow P_d = 3 I_2'^2 \cdot R_2' \left(\frac{1-s}{s} \right)$$

$$P_d = P_g (1-s)$$

$$\rightarrow T_g = \frac{P_g}{\omega_{s1}} = \frac{3 I_2'^2 R_2' / s}{\omega_s}$$

$$\omega_s = \frac{2\pi N_s}{60} \quad \text{Field } \rightsquigarrow \omega_s, \quad N_s = \frac{60f}{p} = \frac{2\pi 60f}{p 60} \rightarrow$$

$$= \frac{2\pi f}{p} = \omega_e \text{ (electrical)}$$

$$\rightarrow T_d = \frac{P_d}{\omega_m} = \frac{P_g(1-s)}{\omega_m \text{ (mechanical)}}$$

$$\rightarrow \omega_m = \omega_s \left(\frac{p}{p} \right) (1-s)$$

$$s = \frac{N_s - N_m}{N_s}, \quad s N_s = N_s - N_m, \quad N_m = N_s(1-s)$$

$$\rightarrow \omega_m = \omega_s (1-s)$$

Synchronous speed

$$\rightarrow T_d = \frac{P_d}{\omega_m} = \frac{P_g(1-s)}{\omega_s(1-s)}$$



field speed

$$T_d = \frac{P_g}{\omega_s} = T_g$$



Approximation

① R_c : can be omitted from the circuit.

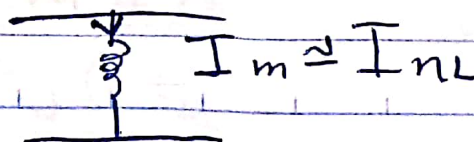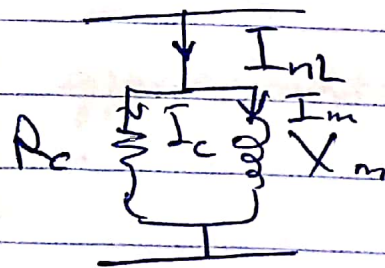\rightarrow R_c is parallel, X_m is series
 $R_c \ll X_m$



$$I_{NL} \approx I_m$$

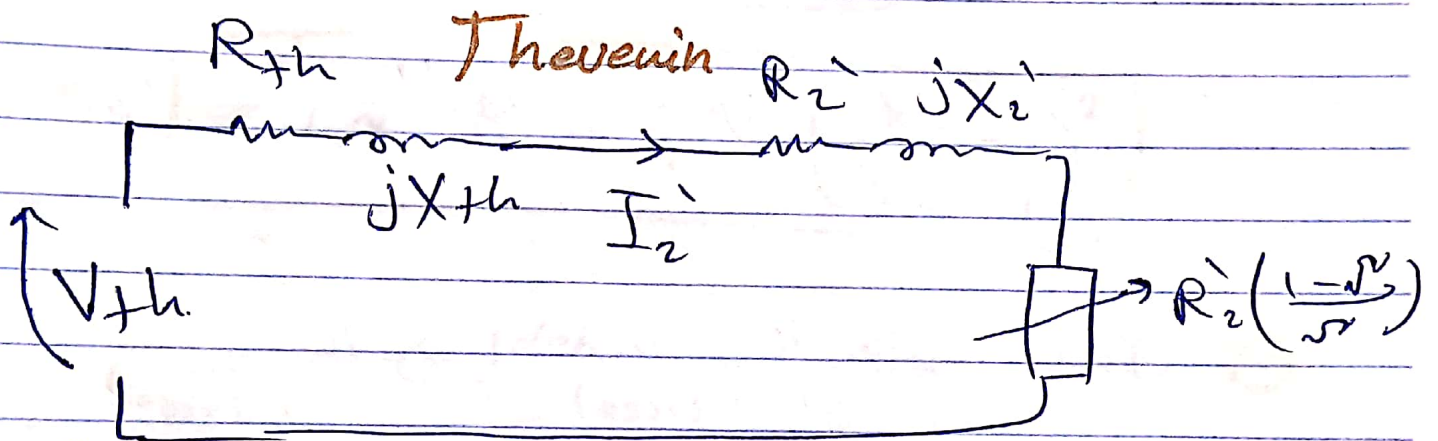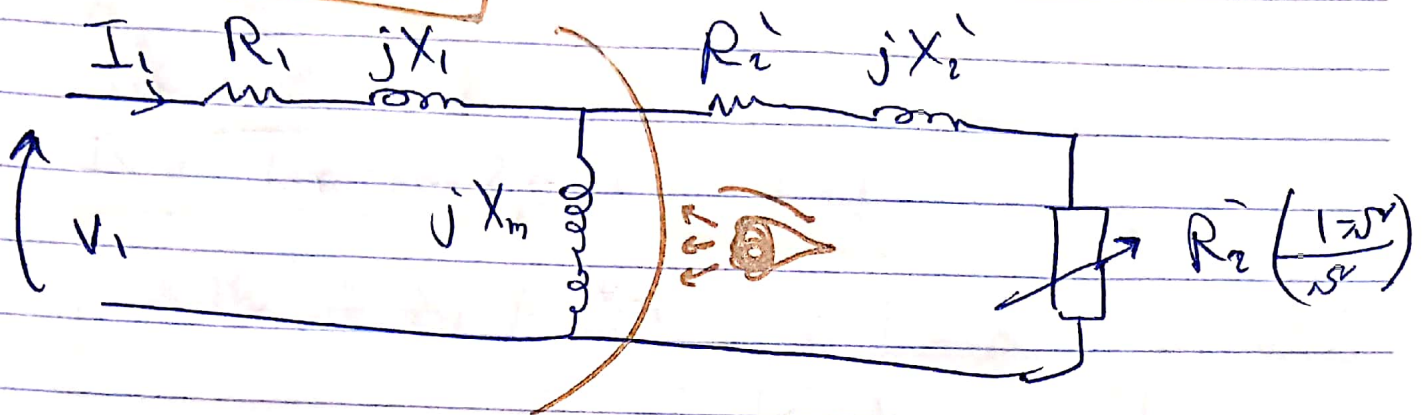

approximation

② Find the Thevenin's Equivalent circuit.

$$\rightarrow V_{th} = \frac{\bar{V}_1}{(R_1 + jX_1 - jX_m)} \cdot jX_m = \frac{\bar{V}_1 \cdot jX_m}{R_1 + j(X_1 + X_m)}$$

$$V_{th} \approx V_1 \left(\frac{X_m}{X_m + X_1} \right) \text{ approximation.}$$

Supply voltage

$$\rightarrow Z_{th} = \frac{jX_m * (R_1 + jX_1)}{R_1 + j(X_m + X_1)} \rightarrow \left(\text{Real} \right) + j \left(\text{Imag} \right)$$

The real part (R_{th})

$$R_{th} \approx R_1 \left(\frac{X_m}{X_m + X_1} \right)^2$$

\Rightarrow


دالة
 V_{th}

The Imaginary part (X_{th})

$$X_{th} \approx X_1$$

So $Z_{th} \approx R_1 + j X_1 \left(\frac{X_m}{X_m + X_1} \right)^2$

Core losses. rotational losses لا يوجد
⊙

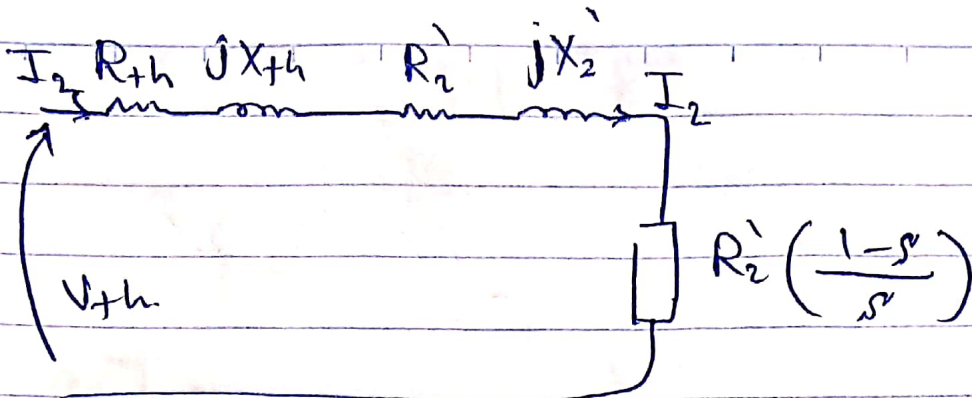

• $P_g = 3 I_2'^2 \frac{R_2'}{s}$


• $T_g = \frac{3 I_2'^2 \cdot R_2' / s}{\omega_s}$

• $I_2' = \frac{V_{th}}{\sqrt{(R_{th} + \frac{R_2'}{s})^2 + (X_{th} + X_2')^2}}$

$= \bar{I}_2' = \frac{\bar{V}_{th}}{(R_{th} + \frac{R_2'}{s}) + j(X_{th} + X_2')}$

• $T_g = \frac{3 V_{th}^2 \cdot R_2' / s}{\omega_s [(R_{th} + \frac{R_2'}{s})^2 + (X_{th} + X_2')^2]}$

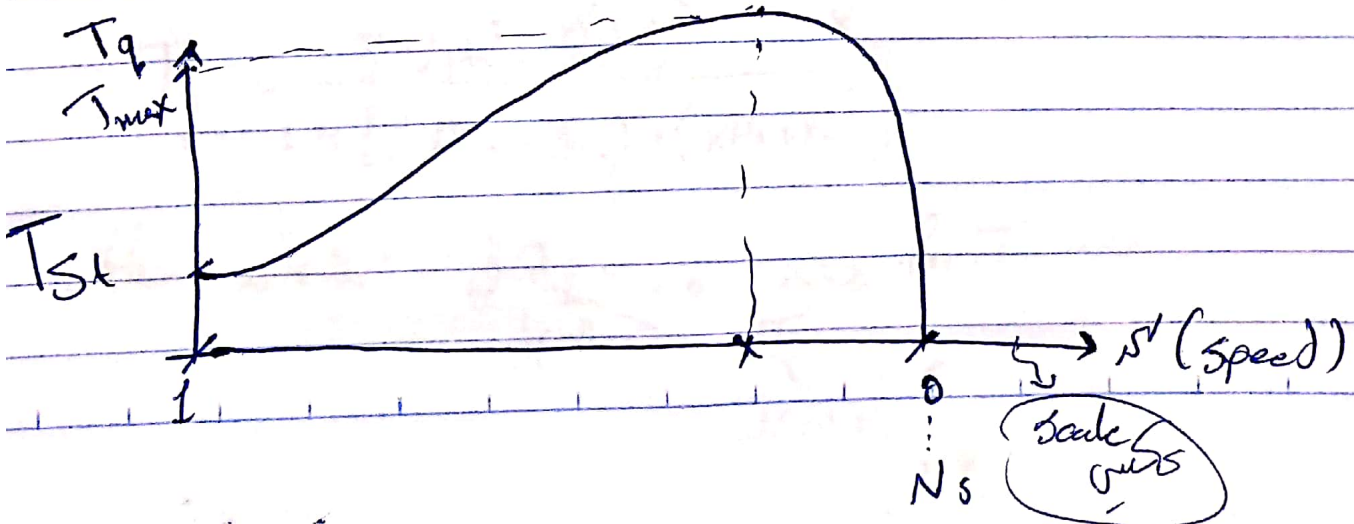• $V_{th} = V_1 \left(\frac{X_m}{X_m + X_1} \right)$



Starting Torque

$$T_{st} = \frac{3V_{th}^2 R_2'}{ws [(R_{th} + R_2')^2 + (X_{th} + X_2')^2]}$$

Starting current

$$I_{st} = \frac{V_{th}}{\sqrt{(R_{th} + R_2')^2 + (X_{th} + X_2')^2}}$$

approx

$$I_2' = \frac{V_{th}}{\sqrt{(R_{th} + \frac{R_2'}{s})^2 + (X_{th} + X_2')^2}}$$

approximation: $R_{th} \ll \frac{R_2'}{s}$, $\frac{R_2'}{s} \gg (X_{th} + X_2')$

So,

$$\frac{V_{th}}{\sqrt{(R_{th} + \frac{R_2'}{s})^2 + (X_{th} + X_2')^2}} \approx \sqrt{s \cdot \frac{V_{th}}{R_2'}}$$

$\Rightarrow I_{st} \approx (5 \rightarrow 20) * I_{rated}$


Maximum Torque:-

\rightarrow load Torque (normal running) $< T_{max}$

$$T_g = \frac{3V_{th}^2 \cdot \frac{R_2'}{s}}{ws [(R_{th} + \frac{R_2'}{s})^2 + (X_{th} + X_2')^2]}$$

Home work: $\frac{dT_g}{ds} = 0 \rightarrow$ for T_{max}

$$\frac{dT_g}{d(R_2'/s)} = 0$$

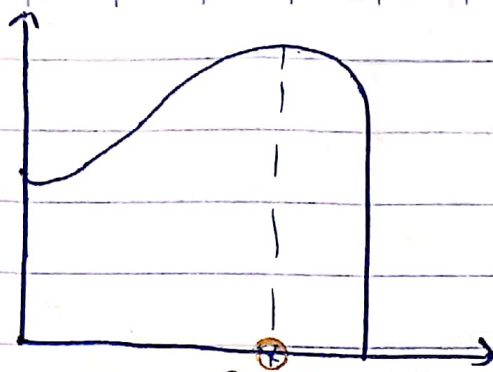

For T_{max} :

$$\frac{R_2'}{s} = \sqrt{R_{th}^2 + (X_{th} + X_2')^2}$$

Sub. in T_g :

$$s_{T_{max}} = \frac{R_2'}{\sqrt{R_{th}^2 + (X_{th} + X_2')^2}}$$


Sub. in T_g :



$$T_{max} = \frac{3}{2\omega_s} \cdot \frac{V_{th}^2}{[R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_2')^2}]}$$

$S_{T_{max}} = f(R_2')$: $S_{T_{max}}$ is directly proportional to R_2' and independent of (V supply).

T_{max} is independent of R_2' .

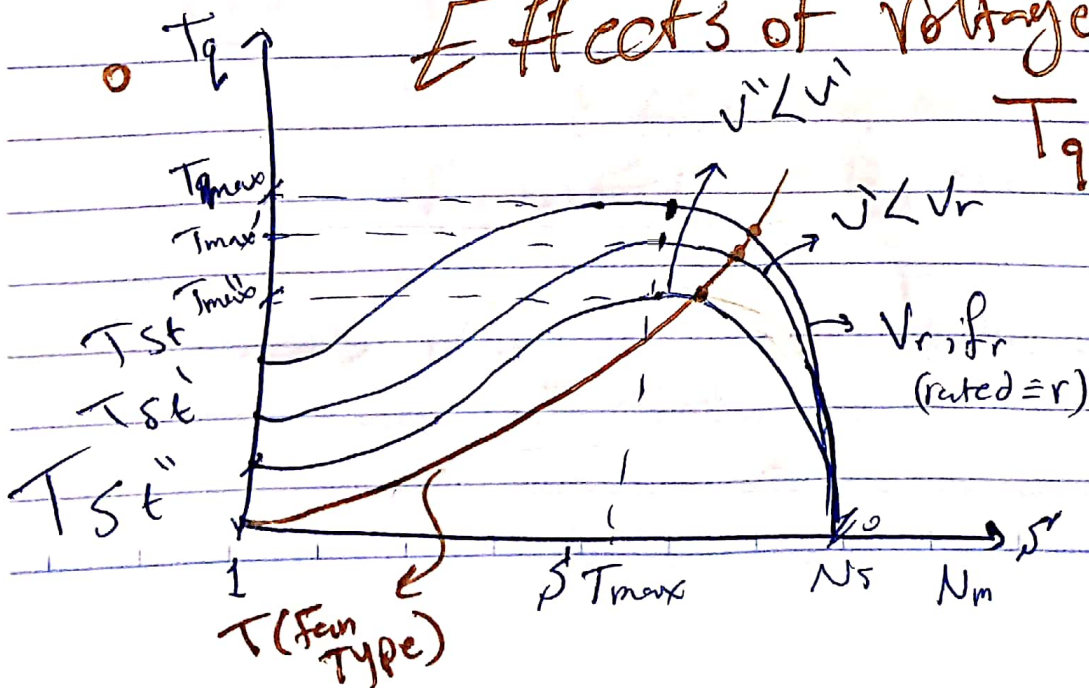Effects of voltage on $T_g = f(s)$ characteristics.



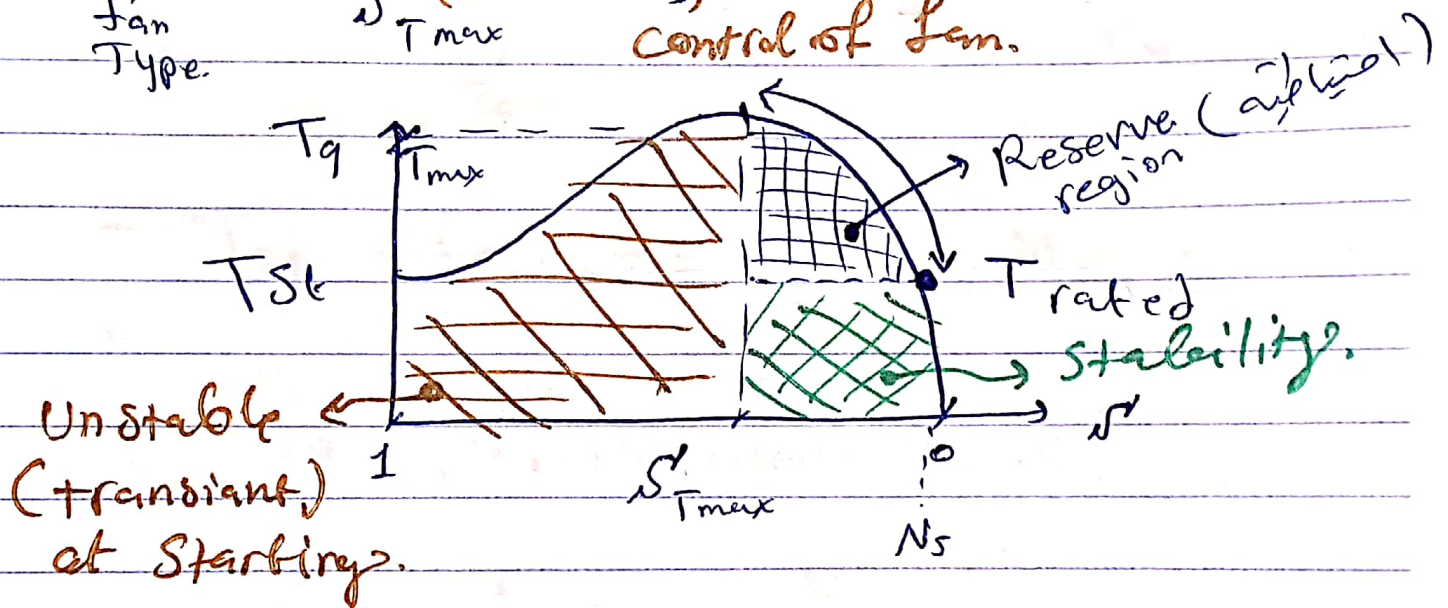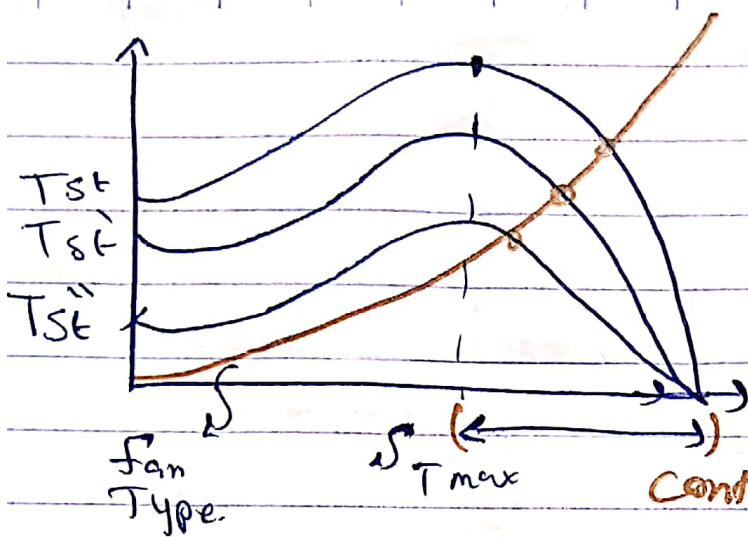


○ $T_{max} \approx (1.5 \rightarrow 2.5) T_g(\text{rated})$

○ $(T_m - T_g \text{ rated}) \Rightarrow$ Reserve Torque, to avoid instability.

Effects of R_2'

if an External Resistance is added

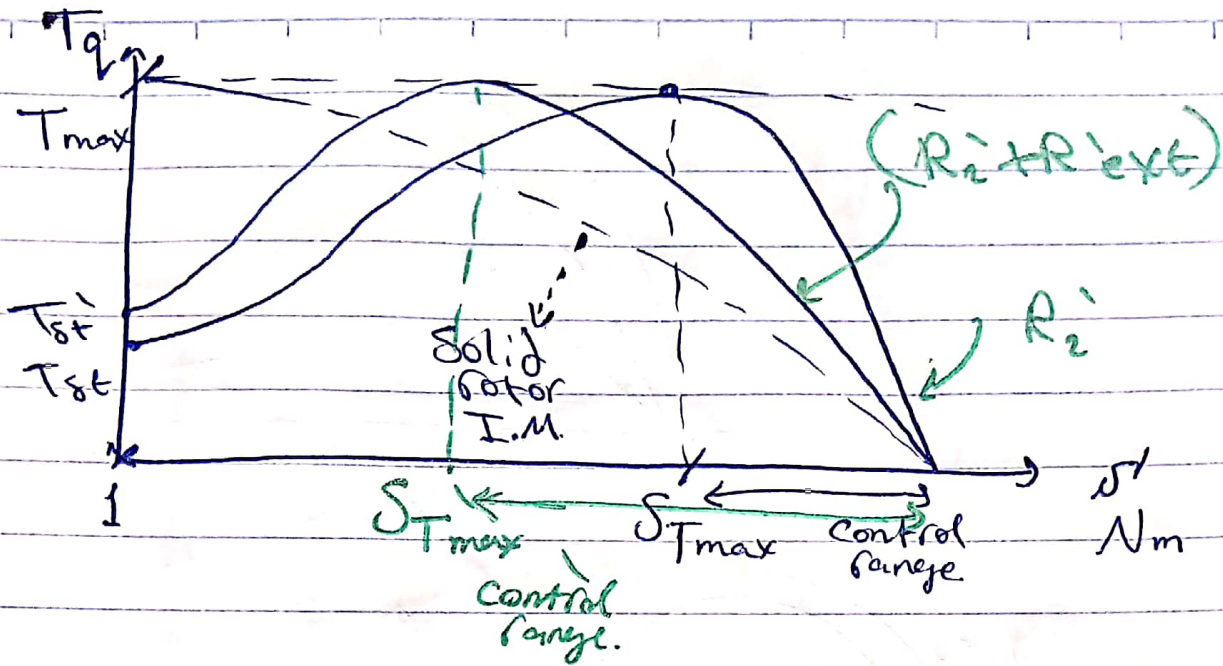\rightsquigarrow Wound-rotor Induction Motor.



• $T_{st} > T'_{st}$, but T_{max} is still the same.

• $I_{st} @ R'_{ext} = \frac{V_{th}}{\sqrt{(R_{th} + R_2) + R_{ext}}^2 + (X_{th} + X_2)^2}$


• $s_{Tmax} @ R'_{ext} = 1 = \frac{R_2 + R_{ext}}{\sqrt{R_{th}^2 + (X_{th} + X_2)^2}}$

$\rightarrow R'_{ext} = \sqrt{R_{th}^2 + (X_{th} + X_2)^2} - R_2$

Supporting R_2 by adding R_{ext} leads to:

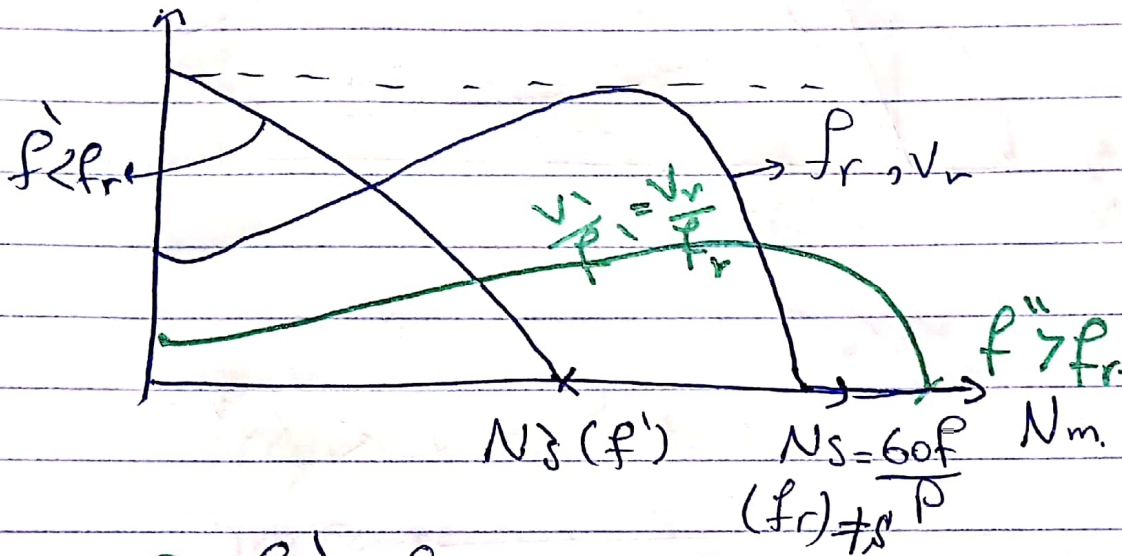- 1) reduction of I_{st} (advantage).
 - 2) Increase T_{st} (advantage).
 - 3) Increase The stable range of speed control (advantage).
 - 4) lower efficiency (disadvantage).
- \rightarrow Solid-rotor I.M (linear.)


Frequency Effects on T / V_r Characteristics.



① $f' < f_r$

T_{max} is independent of (f) if $f' < f_r$.
 assuming $\frac{V_r}{f} = \text{constant}$.
 (rated speed is low $\sim \omega$)

② $f'' > f_r$

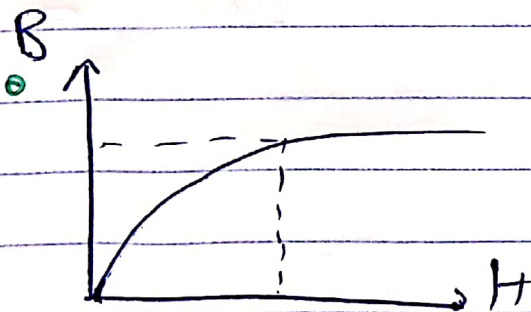


Saturation by core lobbies
 rated. $\sim \omega$ $\sim \omega$

$$V = 4.44 N_f \phi_m f \uparrow$$

$\omega \sim \omega$
 $\omega \sim \omega$

* This is called Field
 weakening.

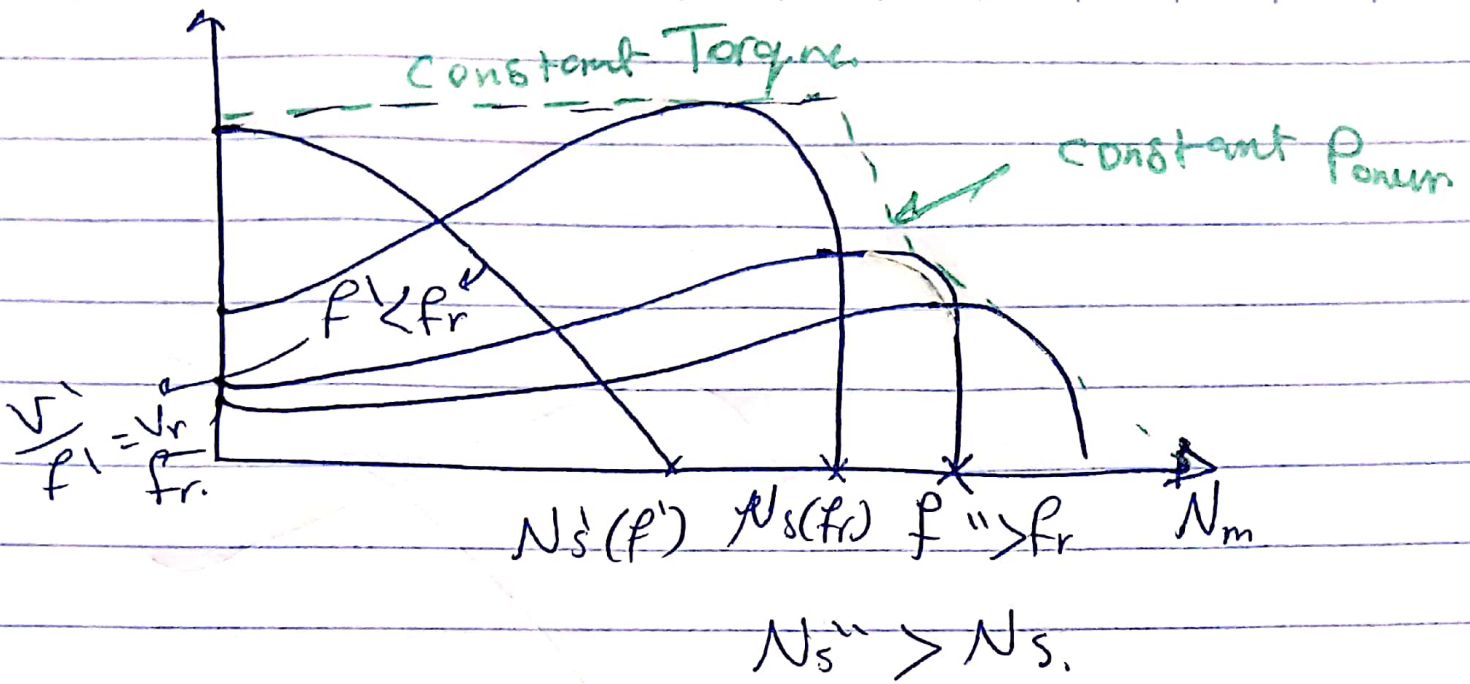

So frequency effects:

- 1) increase in T_{st} .
- 2) Increase the range of speed control. (above rated speed)
- 3) almost constant slip \Rightarrow losses due to slip is constant (fixed).

Do not Memorize These values.

NEMA DESIGN CLASSES OF INDUCTION MOTORS.


nominal/rated

(NEMA is the National Electrical Manufacturers Association - USA)


Slip @ max Tg / Starting current / Starting Torque / Pull-out Torque / maximum Torque as notes.

Design Class	Normal Slip	Slip at Maximum Torque	Starting Current	Starting Torque	Pull-out Torque	Notes
A	Less than 5 %, Less than Class B.	Less than 20 %	500 % - 800 % (Less for Large Motors)	100 % - 200 100 % for Large Motors, 200 % for Small Motors	200 % - 300 %	Standard Design for Most Applications.
B	Less than 5 %	Less than 20 %	350 % - 600 % (Almost 25 % Lower Than Class A)	100 % - 200 100 % for Large Motors, 200 % for Small Motors	150 % - 200 %	To Replace Class A in Recent Days.
C or called deep bars	Less than 5 %	Less than 20 %	200 % - 400 %	100 % - 250 %	150 % - 200 %	Designed with Double-Cage Rotors (More Expensive)
D	7 % to 20 % (Typical) But Can Be 100 % High rotor resistance.	Can Be Up to 100 %	200 % - 400 %	275 % and Higher	Up to 400 %	Design Class A but with Smaller Rotor Bars & with Higher Resistance Rotor Bars.

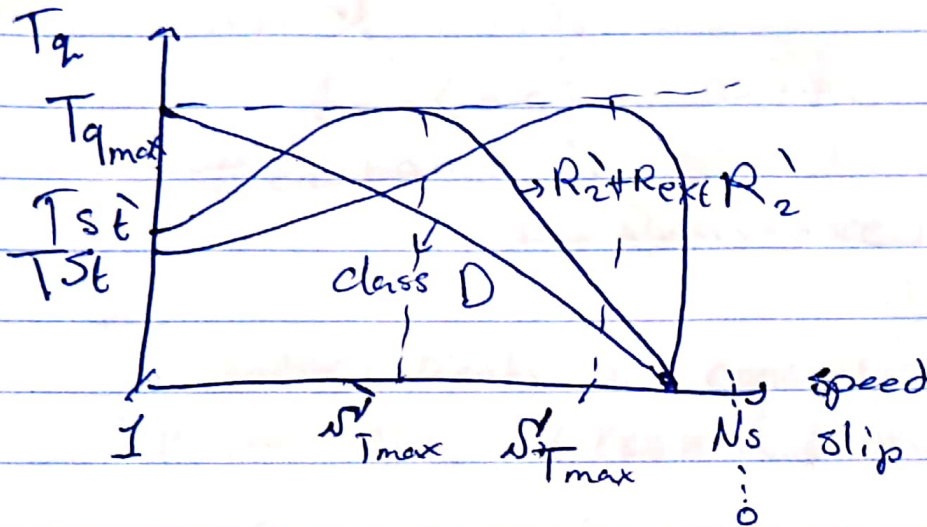Quiz: Draw The $T_g = f(\text{speed})$ with the effect of adding (R_{ext}) .




Double cage rotor

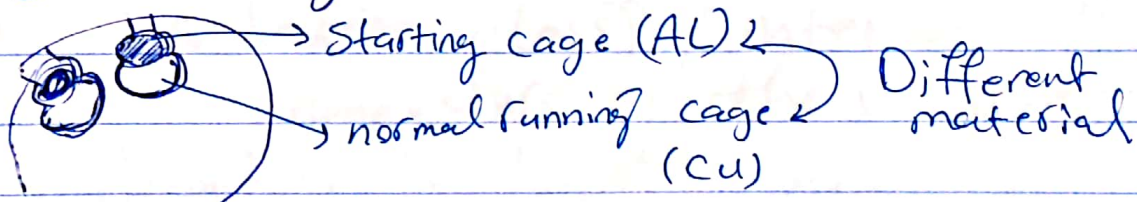


Why double-cage rotor design?

- decrease starting current
- increase starting Torque.

→ due to skin effect

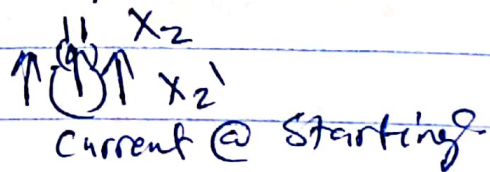

But @ normal

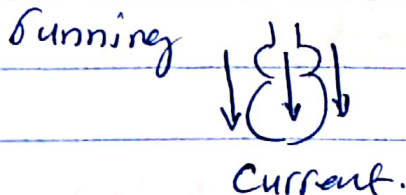

$X_2 \gg X_2'$
 $f_2 = s f_1$
 @ starting $s=1$

at starting $X_2 \gg X_2'$ ($f_2 = f_1$), current is concentrated @ the outer cage since its R_2 is larger than that at the

normal running (internal R) \rightarrow $I_{starting} \downarrow$.

• at normal running:

$$f_2 = (0.03 \rightarrow 0.05) f_1$$

\rightarrow Reactance is reduced

\hookrightarrow Resistance more effective.



rotor currents are concentrated in the internal cage. (normal running cage)

Classifications of Motors according (to insulation class) / internal temperature of the windings:

\rightarrow According to NEMA $\left\{ \begin{array}{l} \text{Type I, II} \\ \text{also} \end{array} \right.$

Design A $\rightarrow 105^\circ C$

Design B $\rightarrow 130^\circ C$


Design F $\rightarrow 155^\circ C$ (more used / cost effective)


Design H $\rightarrow 180^\circ C$ (Very Expensive)

DC: Stator / Method of speed control

□ Armature voltage control.

VARIAC: Variable AC supply

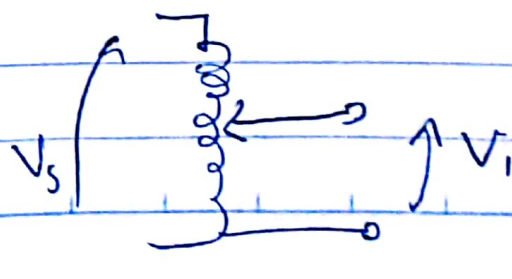

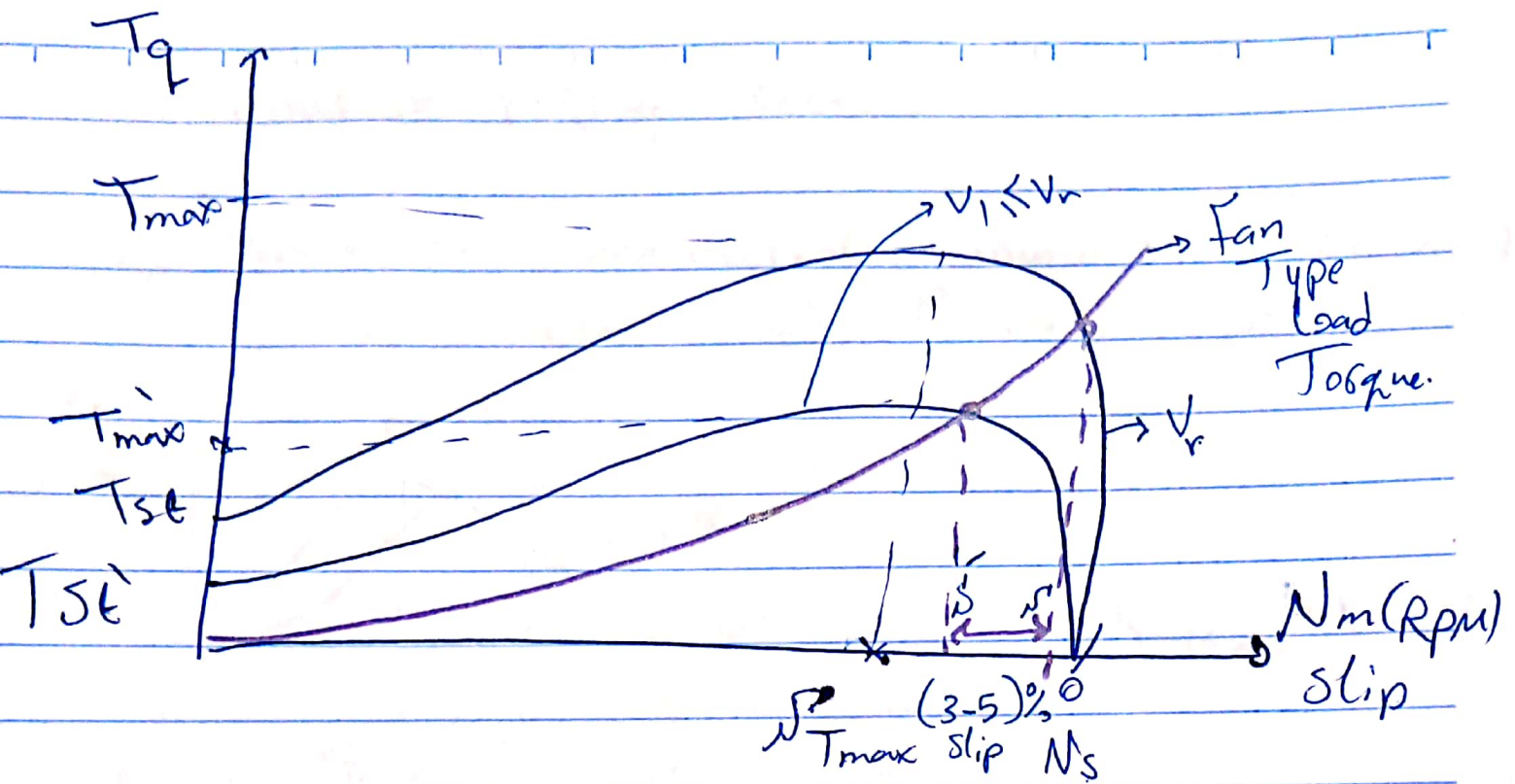

example: $V_1 = 0.5 V_r$

$T'_{max} = 25\% T_{max}$
 0.05 of T_{max} at rated voltage

$T'_{se} = 25\% T_{se}$

as for $s'_{T_{max}}$: It isn't affected

(voltage independent) / as for $s'_{normal\ slip}$


$s' \rightarrow$ less (more losses)

⊙ This is suitable for Fan Type loads Motor control.

(A) Armature voltage control.

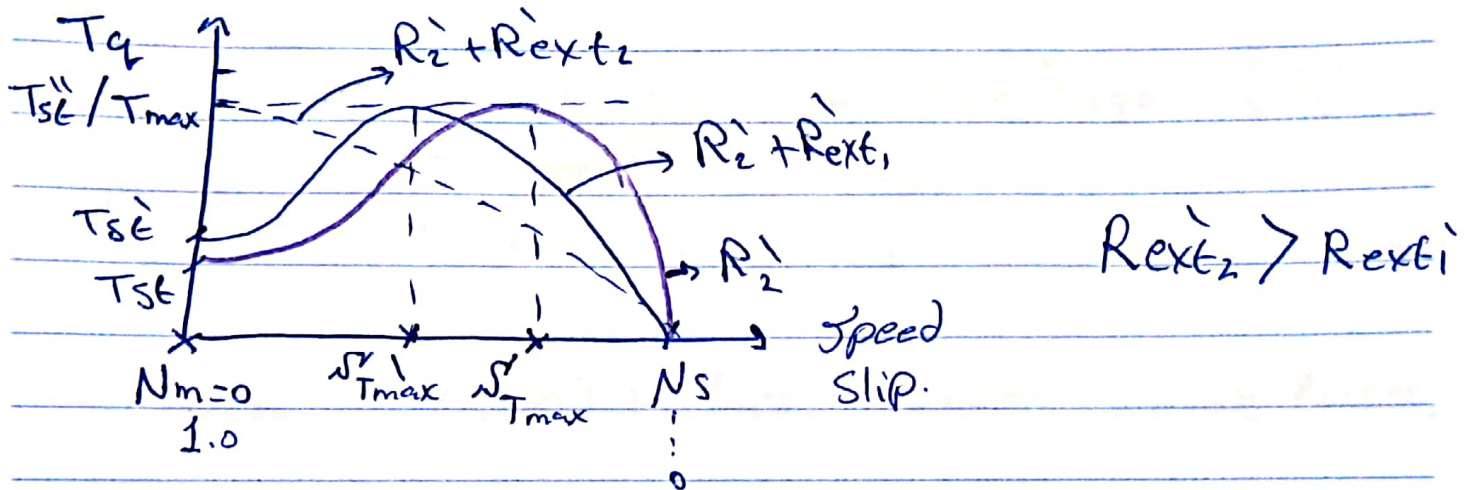(B) Rotor resistance control (wound rotor-machine)

$V_1 = \text{constant (fixed)}$, $f_1 = \text{constant (rated value)}$



● If R_{ext} is added to the rotor:
 $\rightarrow \sqrt{T_{max}}$ is directly affected.


$$\rightarrow \underset{\text{Fixed}}{T_{max}} = \frac{3V_{th}^2}{2\omega_s [R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_2')^2}]}$$

$$\rightarrow \underset{\substack{\uparrow \\ \text{Increased}}}{\sqrt{T_{max}}} = \frac{R_2' + R_{ext}}{\sqrt{R_{th}^2 + (X_{th} + X_2')^2}}$$

$$\rightarrow \underset{\substack{\uparrow \\ \text{Increased}}}{T_{st}} = \frac{3V_{th}^2 (R_2' + R_{ext})}{\omega_s [(R_{th} + R_2' + R_{ext})^2 + (X_{th} + X_2')^2]}$$

$$\rightarrow \underset{\substack{\downarrow \\ \text{reduced}}}{I_{st}} = \frac{V_{th}}{\sqrt{(R_{th} + R_2' + R_{ext})^2 + (X_{th} + X_2')^2}}$$

Control

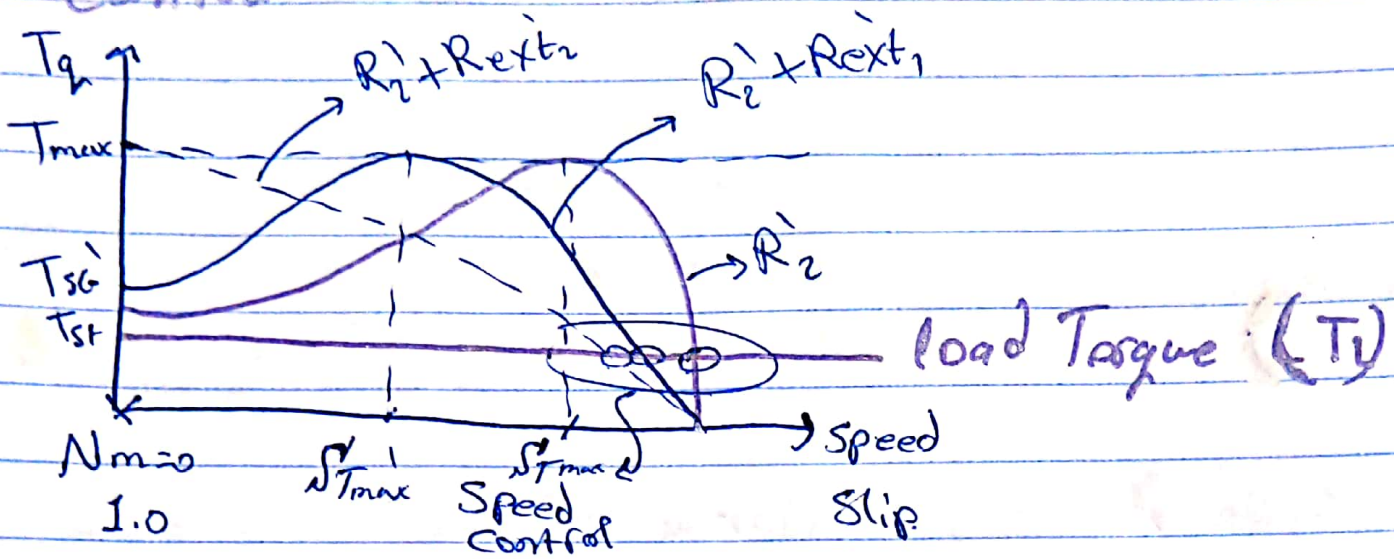

→ s (slip) values increases → more losses.

ADVANTAGES

- Reduce starting current.
- Increase starting torque.

DISADVANTAGE

- Increased value of slip → more losses
Lower efficiency.

In Exam

→ show
Rext effect on speed/Torque
characteristics curve

↑↑ s_{Tmax} و T_{sg} و T_{st} و T_{max}


© Input Frequency control

سرعت را می توان در محدوده $0 < f < \text{up to } 3 \times f_{\text{rated}}$ کنترل کرد

در این محدوده $0 < N_s < N_m < \text{up to } 3 \times N_s \text{ (rated)}$ می توان کنترل کرد

→ Speed can be controlled below & above rated speed.

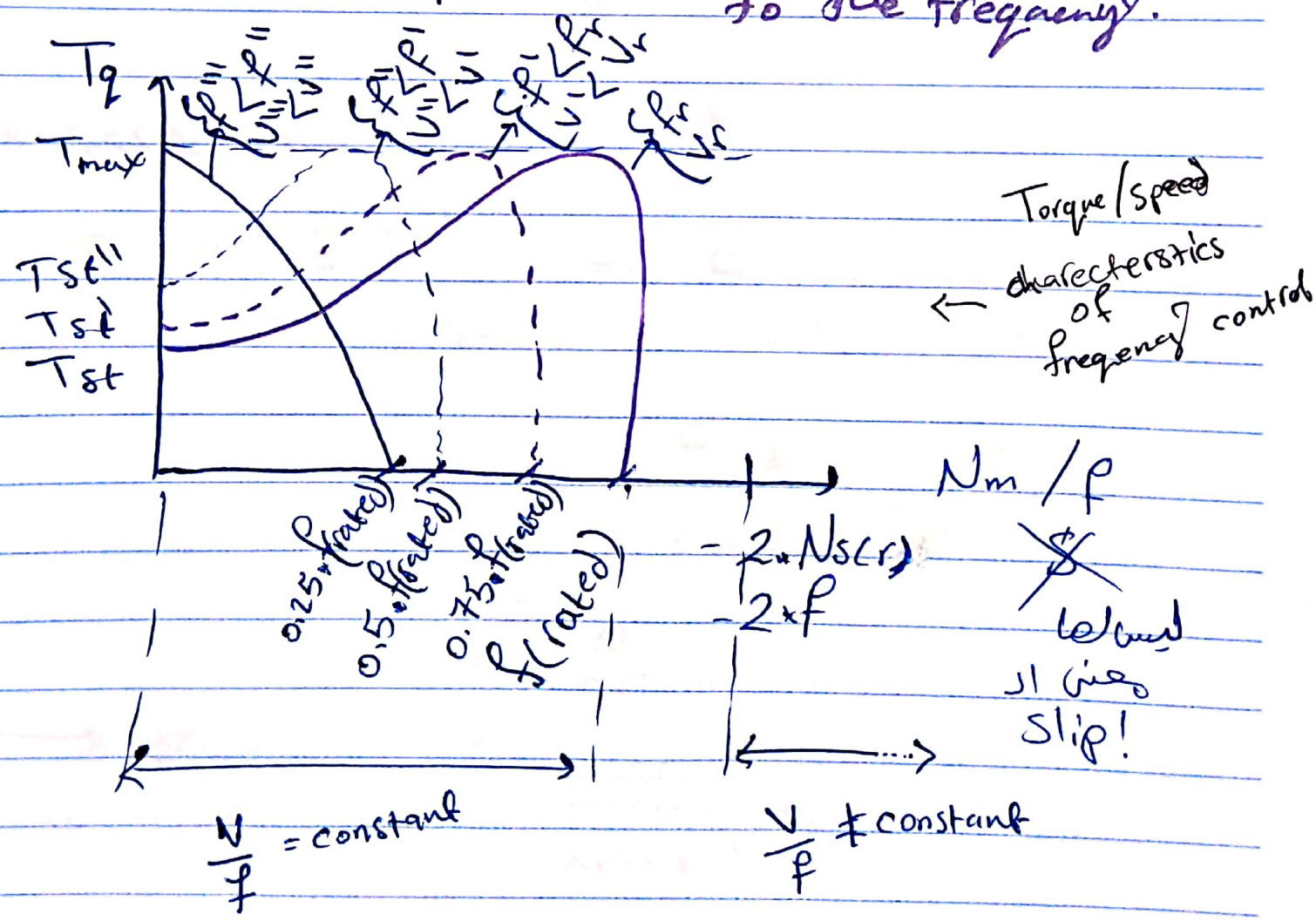→ $N_s = \left(\frac{60}{p}\right) \cdot f$ directly proportional to the frequency.



← Torque/speed characteristics of frequency control

effects of frequency control

$$\rightarrow T_{\max} = \frac{3Vt^2}{2\omega_s [R_{th} + \sqrt{R_{th}^2 + (X_{th} + X'_2)^2}]}$$

$$T_{\max} \approx \frac{3Vt^2}{2k_1 f}$$

(ω_s, X_{th} & X'_2 frequency dependent)

$$\omega = \frac{2\pi N}{60}, N = \frac{60\omega}{2\pi}, N_s = \frac{60f}{P}$$

$$\downarrow \quad \downarrow$$

$$\frac{60\omega}{2\pi} \quad \frac{60f}{P}$$

$$\omega = \frac{2\pi}{P} \cdot f$$

$$\omega = k \cdot f$$

$$R_{th} \ll X'_2 + X_{th}$$

$$T_{\max} \approx \frac{3Vt^2}{2k_1 f [X_{eq}]} \Rightarrow \approx \frac{3Vt^2}{2k_1 (f \cdot k_2) f}$$

$$\approx \underbrace{k_1}_{\text{constant}} \cdot \frac{Vt^2}{f^2}$$

Case $f < f_r$

$$\rightarrow \int T_{\max} = \frac{R'_2}{\sqrt{R_{th}^2 + (X_{th} + X'_2)^2}}$$

$$\approx \frac{R'_2}{X_{th} + X'_2} \approx \frac{R'_2}{X_{eq}} \rightarrow k_2 \cdot f$$

$$k' = \frac{R_2'}{k_2}$$

$$\text{So, } \approx \boxed{k' \cdot \frac{1}{f}}$$

$$\rightarrow I_{st} = \frac{V_{th}}{\sqrt{(R_{th} + R_2')^2 + (X_{th} + X_2')^2}}$$

= 1 ← (circled)

$$I_{st} = \frac{V_{th}}{\sqrt{(R_{th} + R_2')^2 + (X_{th} + X_2')^2}}$$

$$f < f_r \rightsquigarrow I_{st}(f) > I_{st}(f_r)$$

Very BAD!! $I_{st} \approx \frac{V_{th}}{X_{eq}}$

Therefore: $\approx \frac{1}{k_1} \cdot \frac{V_{th}}{f}$ → ratio constant.

$$\rightarrow T_{st} = \frac{3V_{th}^2}{\omega s [(R_{th} + R_2')^2 + (X_{th} + X_2')^2]} \approx \frac{3V_{th}^2}{k_1 \cdot f \cdot k_2 \cdot f}$$

$$\approx k \cdot \frac{V_{th}^2}{f^2}$$

$$\approx \frac{1}{f^2}$$

- The increased values in starting current due to the change in frequency is very dangerous!!

→ Reducing f below rated value leads to $I_{st} \uparrow$, which is more dangerous


Than the rated conditions.

$$\left[\frac{1}{k_1} = k'' \right] \rightarrow I_{st} = k'' \left(\frac{V_{th}}{f} \right)$$

→ To keep I_{st} fixed $\left(\frac{V_1}{f} \right) = \text{constant}$.

Else
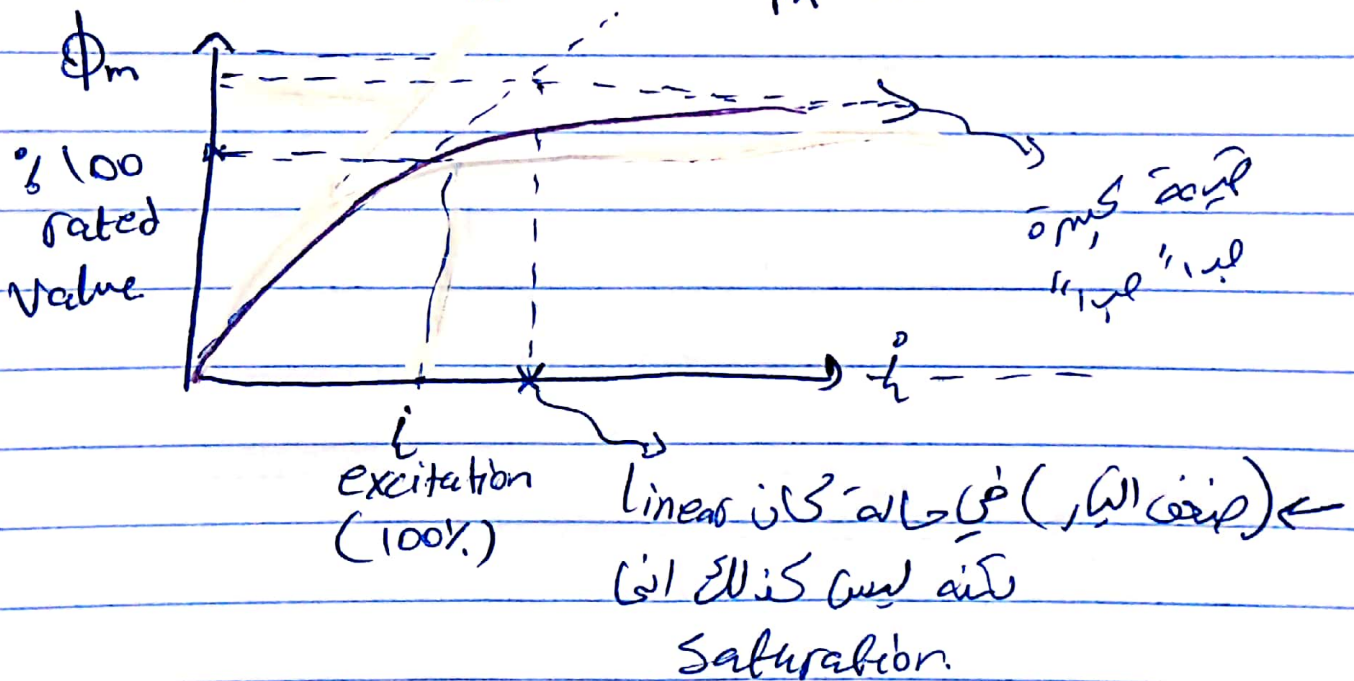
$$E_1 \approx V_1 \approx 4.44 \cdot N_{ph} \cdot \Phi_m \cdot f$$



• If we reduce the frequency while keeping the voltage constant.

$$f < f_r \text{ (ex } f = 0.5 f_r \text{)} :$$

$$V_1 = \text{constant} \rightarrow \Phi_m' > \Phi_m$$

$$\Phi_m' \approx 2 * \Phi_m$$

Therefore the core will be deeply saturated leading to a very high input current

Burning the machine's windings.

○ To keep $\phi_m = \text{constant}$ (design value at the knee of B/H curve.)


→ $\frac{V_1}{f}$ should be kept constant @ rated

Value $\frac{V(r)}{f_r} = \frac{V_1}{f} = \lambda$ constant.

⊗ ملاحظة: كذا ك' : k, k_2, k_1, k, k''

الخ... صيه عبارة عن محاولة لإيجاد علاقة
والهتة وصريجة بين كل ما ذكره واد f

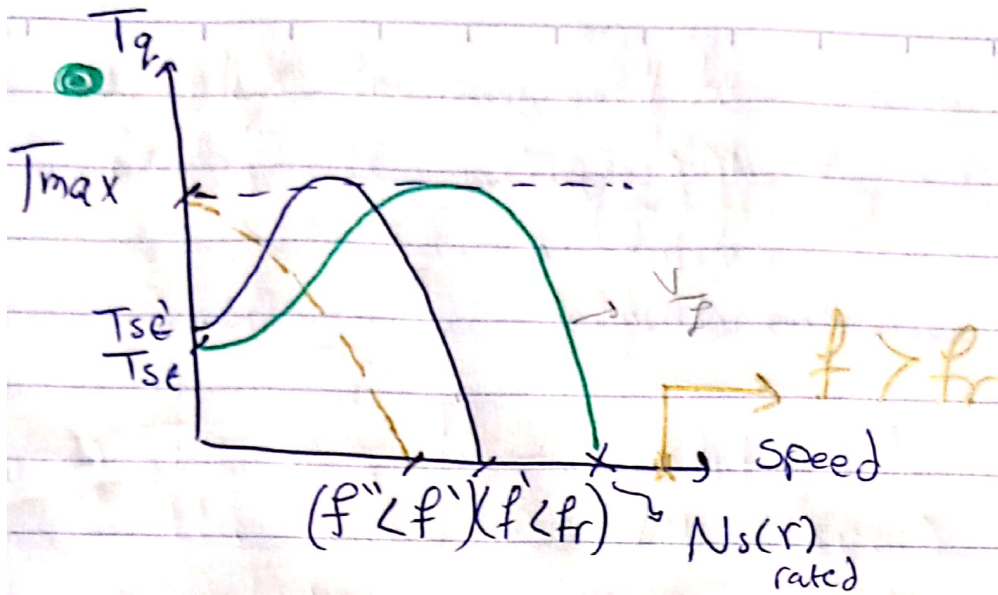← الامتكان: تستخدم العلاقات الرئيسية
وذلك ان exact
values.




- $f < f_r \rightarrow \frac{V_r}{f} = \text{constant}$

- $f > f_r \rightarrow$ we will see that the maximum is a function of $(\frac{1}{f^2})$.

- $\frac{V_r}{f_r} > \frac{V}{f} \downarrow$ (is being reduced)

- $T_{max} = f(\frac{1}{f^2})$

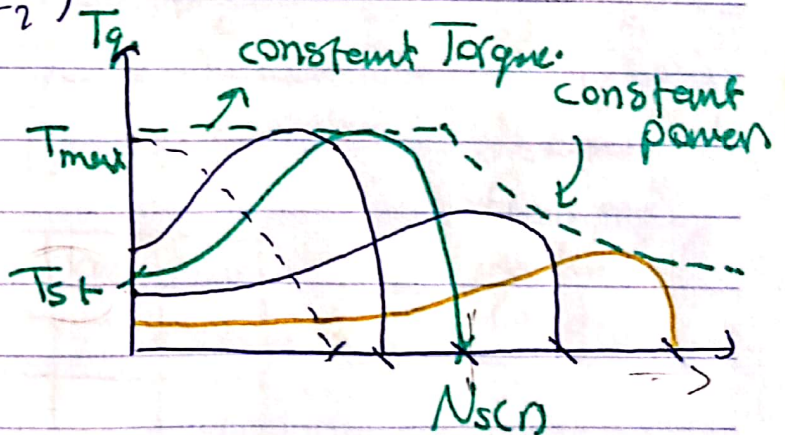

- $\rho = \omega \uparrow \cdot T \downarrow = \text{constant} = \rho_{\text{rated}}$
for constant power

● why V constant in the second case?

$$\rightarrow \left(\phi = \frac{V}{4.44 F \cdot N} = k \left(\frac{V}{F} \right) \right) \quad (f > f_r) \quad \downarrow$$

$$\omega = \frac{2\pi f}{p} \quad \text{windings} \text{ } \leftarrow \leftarrow$$


Induction Motor Testing.

→ No load Test

open circuit (no load) Test.


no V , no I ←


● Wiring diagram

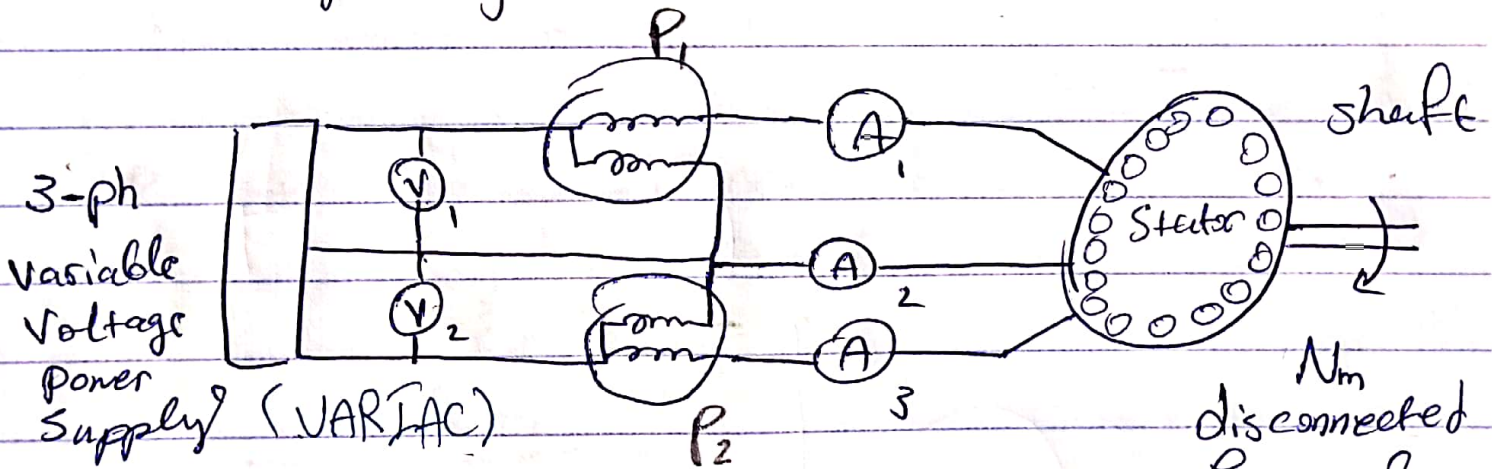

V_1	40%	60%	80%	100%	125%
V_2					
P_1					
P_2					
I_1					
I_2					
I_3					
N_m					



↑ rated conditions. ←

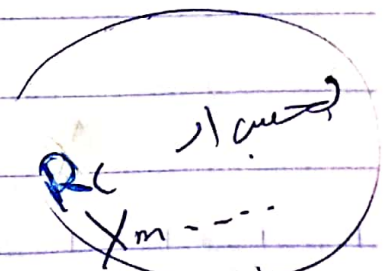

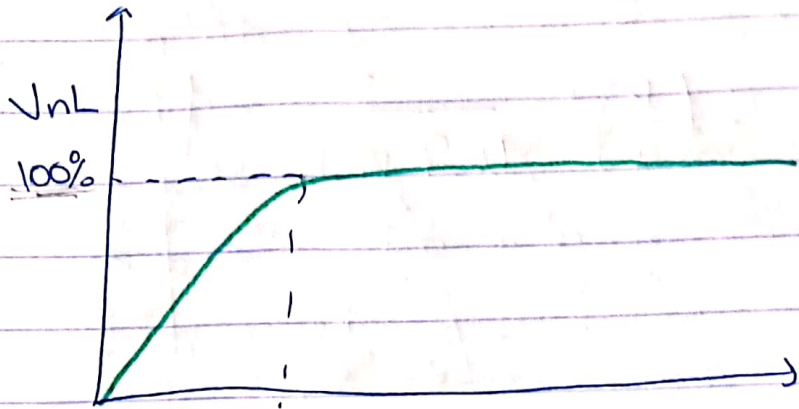

(20-40)% I_{rated}
 ↳ due to air gap reluctance.

• $s_{NL} \approx 0.005$
 slip no-load

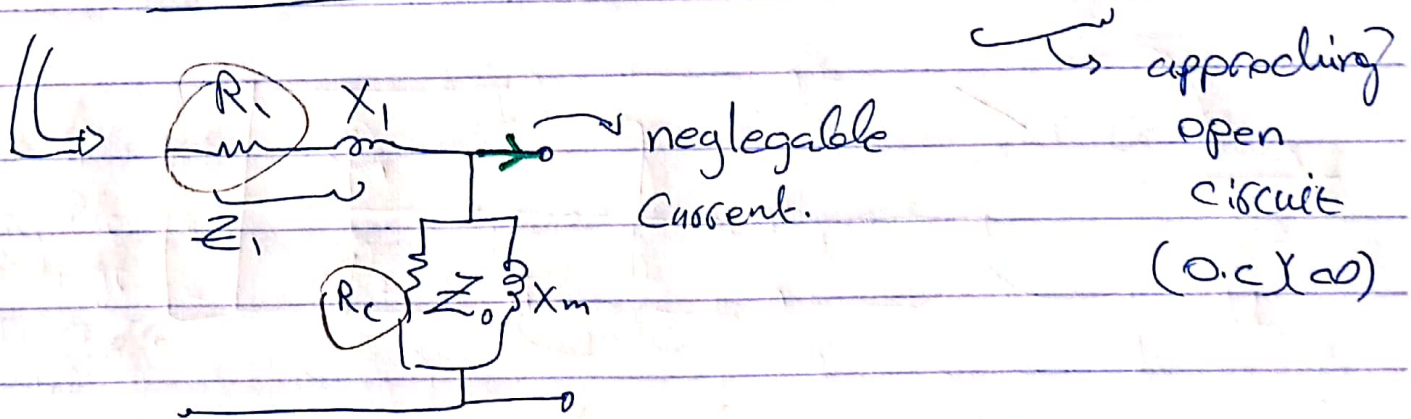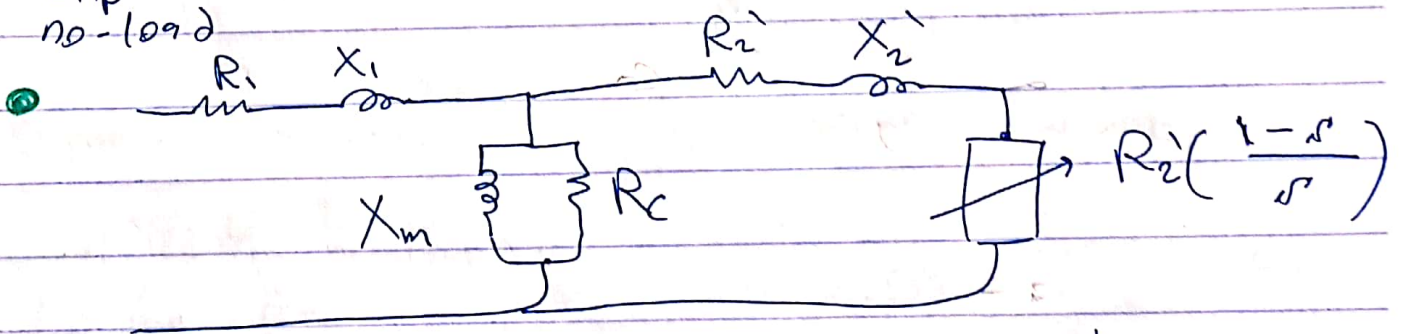

→ Z_1 can be neglected but after taking into consideration the copper losses in R_1 .

↳ $P_{Cu} = 3 I_{nL}^2 R_1$

$P_{in} = P_{nL} = 3 V_{ph} \cdot I_{ph} \cdot \cos \theta_{nL}$

$\sqrt{3} V_L I_L \cos \theta_{nL}$

$P_{core} = P_{NL} - P_{Cu(I)}$

if we are calculating Z_1 & Studying efficiency, we don't neglect it.

$\Rightarrow (0.03)^2 R_1$
 $0.0009 R_1$
 So we can neglect it


$P_{(core)} = P'_{(iron)} + P_{(rotational)}$

$(P_{(hysteresis)} + P_{(eddycurrent)})$

$(P_{(friction)} + P_{(windage)})$

→ we have to separate P_{core} from $P_{rotational}$ to be able to effectively control speed.

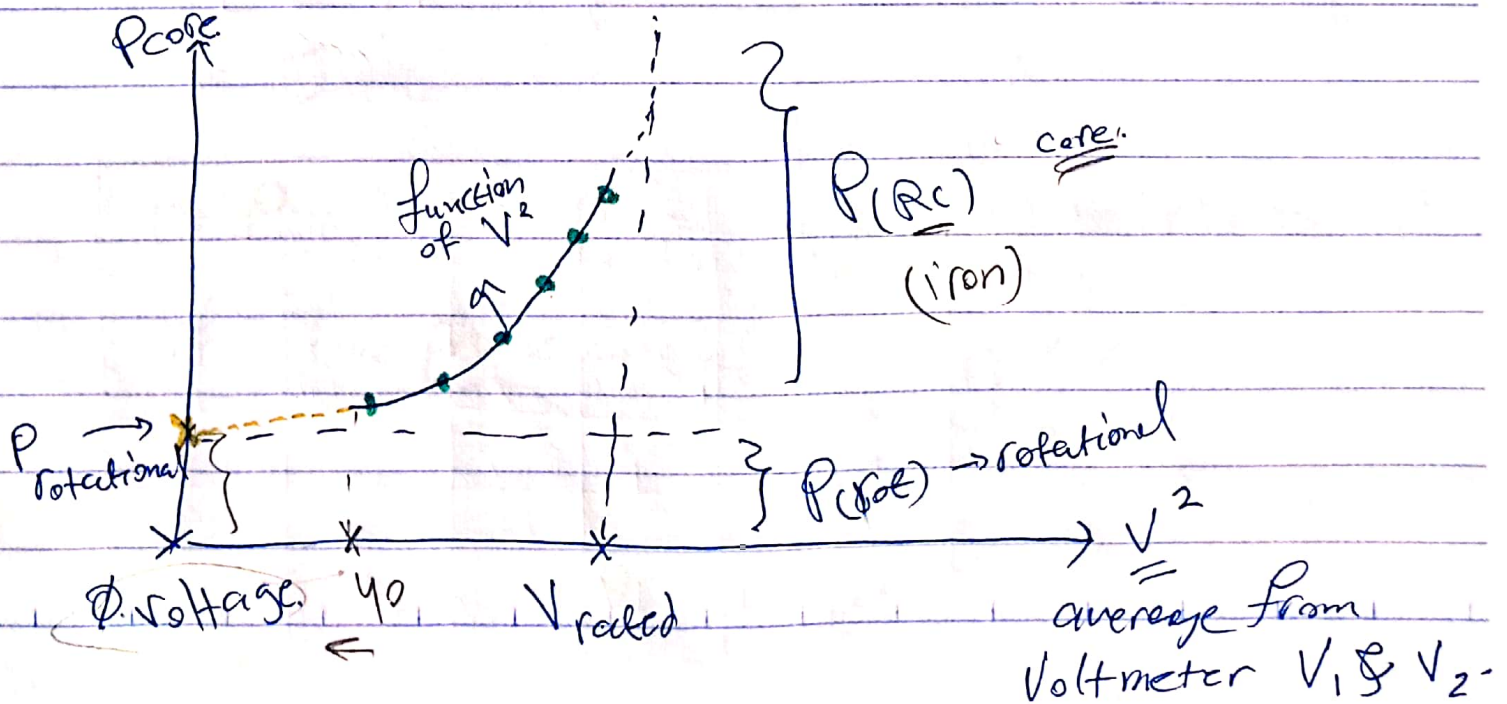• because P_{core} is speed independent unlike ($P_{rotational} \equiv$ speed dependent)



→ $\cos(\theta_{NL}) = \frac{P_{NL} - P_{rot}}{3 V_{ph} \cdot I_{ph}}$, if Δ or Y be careful.



→ $\cos(\theta_{NL}) = \frac{P_{NL} - P_{rot}}{\sqrt{3} \cdot V_L \cdot I_L}$

• $I_c = I_{NL} \cdot \cos(\theta_{NL})$

• $I_m = I_{NL} \cdot \sin(\theta_{NL})$ (or) $I_m = \sqrt{I_{NL}^2 - I_c^2}$

• $X_m = \frac{V_{ph}}{I_m(ph)}$

• $R_c = \frac{V_{ph}}{I_c(ph)}$

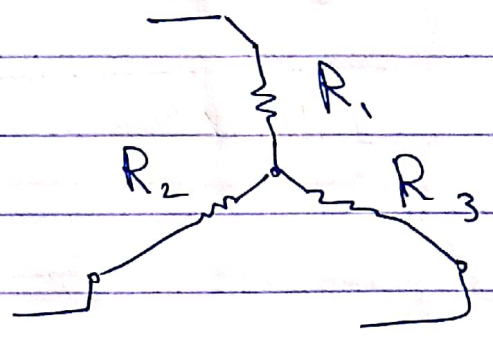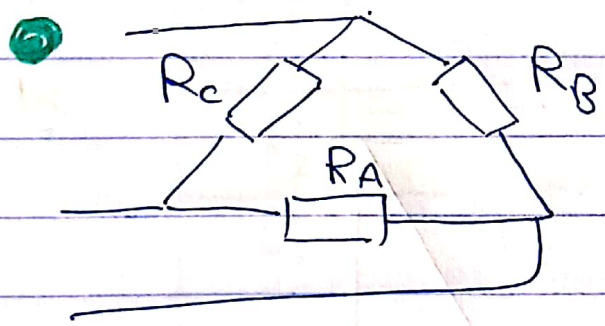

• $R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$

• $R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$

• $R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$

• $R_2 = \frac{R_C R_A}{R_A + R_B + R_C}$

• $R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$

• $R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$

Blocked Rotor test

⇒ equivalent to short circuit test.

Same wiring diagram. but

Shaft is
 $N_m = 0$
 (rotor blocked)

Wiring diagram
 بالاسلاك

→ Slip = 1 ⇒ $n_L \Rightarrow B_r$
 (بس) (تسب)

V_1	
V_2	
P_1	
P_2	
I_1	
I_2	
I_3	

$N_m = 0$

* Bonus: $\phi < 60$ or $60 < \phi$ أو $\phi < 60$ أو $60 < \phi$

→ phasor diagram

$$P = P_1 + P_2 \leftarrow$$

→ وساطة

→ 3ph-load

or

$$P_1 - P_2 \leftarrow$$

→ مؤلفات وزوايا

وتحسب الجور والركنيس

Conjugate or

Synchronous Machines (Alternators)

- pure AC machine But between Rotor & stator there is a DC supply to compensate for the losses.
- mainly used as generators. (in the power stations)
- This machine is running at fixed speed all the time. (Speed regulation = zero)
 → if a change happens to speed then it will be out of synchronization

Very large power scale

(up to 1000 MW)

- One generator power should be less than 10% of the network capacity that is required for a reliable and stable operation.

Main constructional Features

□ Stator (Armature)

→ Exactly the same features of an induction motor.

↳ where the power is generated.

→ Three (3) phase windings are distributed to develop the required Number of poles and the power needed.


[2] Rotor. (Dc Excited circuit)

(1) Salient-poles machines.

Spelling \rightarrow بارزة
pole

(2) cylindrical-rotor machines.


→ Salient-poles

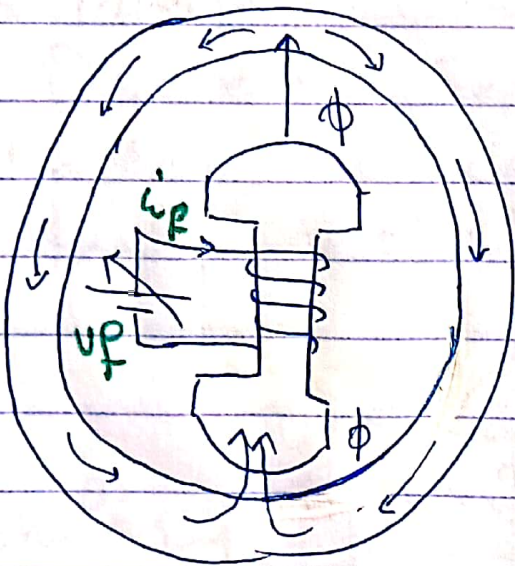

(2-poles)

$$\frac{60 f}{1} = \text{speed.}$$

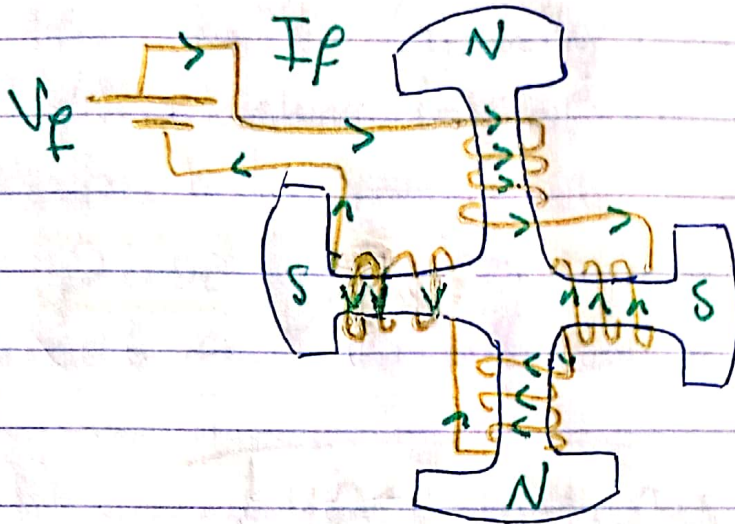- \$V_f\$: Variable.
 - \$i_f\$: also variable
- ① from a voltage divider. (to control Amplitude)
- ② controlled rectifier circuit.




(4-poles)

$$\frac{60 f}{2} = \text{speed}$$

- (two slip rings - two brushes) are required to interface between rotating rotor and DC power supply.

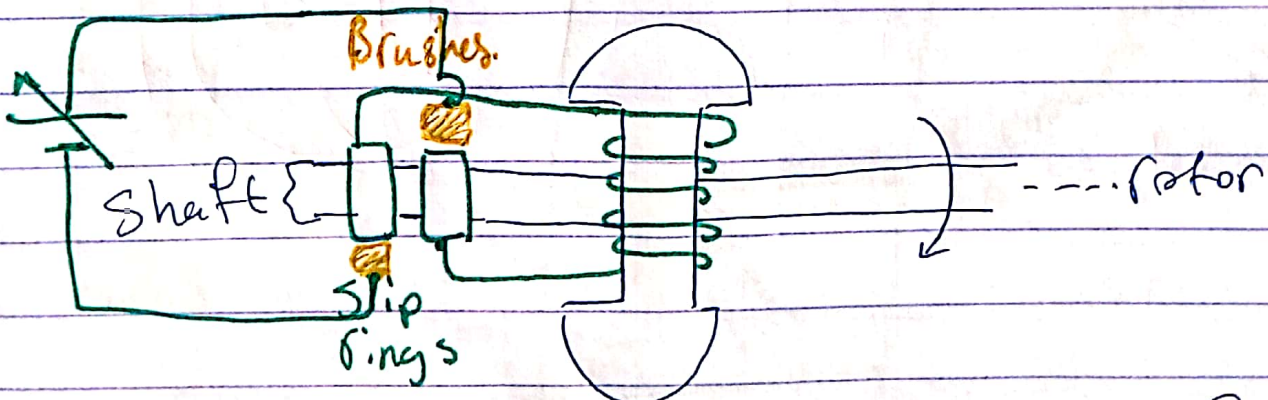- Battery or controlled rectifier are usually involved.



- two slip rings → induction motor.

- Brushless Exciter is to supply the rectifier

on the shaft (usually it takes the supply from the machine itself but at the beginning of operation)

from **Pilot Exciter**: permanent magnet: There is a field all the time.


Types in terms of prime movers.

				↳ turbine, diesel generator....
Position	Vertical			
rotor length				
rotor diameter				Power $\propto (D * L)$ diameter length
# poles	2, 4, 6, 8, 10, 12	2, 4, 6, 8, 10, 12	1500, 3000	
speed	low speed synchronous machines	high speed synchronous machines		
	Hydrolic	Thermal		

UPS

→ uninterruptable power supply

offline UPS system

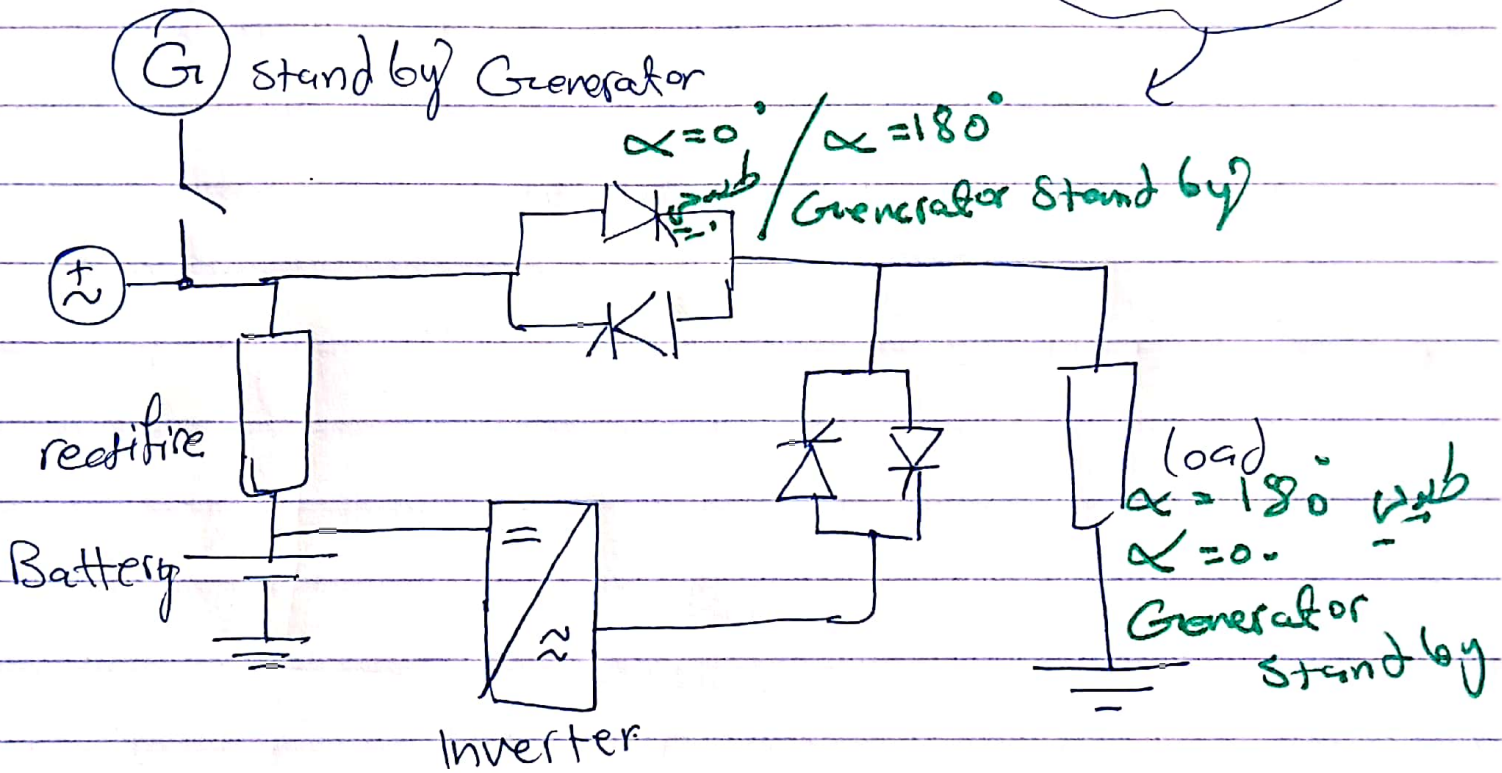

The University of Jordan
Department of Electrical Engineering
Electrical Machines (II)

A 400 V, 6-pole, 3-phase, 50 Hz, star-connected induction motor running light (no-load) at rated voltage takes 7.5 A with a power input of 700 W. When the rotor is locked and a 150 V is applied to the stator, the input current is 35 A and the input power is 4000 W. The stator and copper losses are considered equal under this condition. The standstill leakage reactance of the stator and rotor as seen from the stator are estimated to be in the ratio of 1 : 0.5.

1. Calculate the net mechanical power and torque at a slip of 4%. Use the T-equivalent circuit.
2. Calculate the motor efficiency under the above condition.
3. Repeat (a) and (b) above by shifting the excitation branch to the input terminals (L-equivalent circuit). Compare the results.
4. Repeat (a) and (b) above using Thevenin's equivalent circuit. Compare the results.

Assume the rotational losses included in the core resistance.

November 6, 2019

Homework solution.

From no-load test

7.5 A, 400 V_{L-L}, 700 W

$$P_{core} = P_{NL} - P_{cu}$$

$$700 - 3I_{oc}^2 R_1 \rightarrow P_{NL}$$

Go to blocked rotor test

$$P_{core} = 700 - 3 \times 7.5^2 \times 0.545$$

$$P_{core} = 608.03 \text{ W}$$

$$Z_{oc} = Z_{NL} = \frac{V_{NL}(\text{ph})}{I_{NL}(\text{ph})}$$

$$= \frac{400/\sqrt{3}}{7.5} = 30.79 \Omega/\text{ph}$$


608

$$\cos \theta_{NL} = \frac{P_{NL(L)}}{\sqrt{3} V_{NL(L)} I_{NL(L)}}$$

$$\cos \theta_{NL} = \frac{608/3}{\sqrt{3} \times 400/\sqrt{3} \times 7.5}$$

$$= \cos^{-1}(0.117)$$

$$\theta_{NL} = 83.3$$

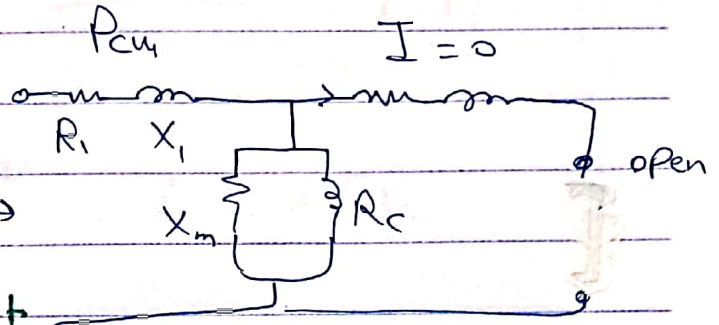


From blocked rotor test

4000 W

35 A

150 V

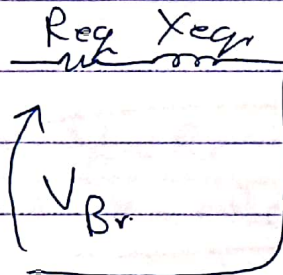

$$P_{BR} = 3 I_{BR}^2 R_{eq}$$

$$R_{eq} = \frac{4000}{3 \times 35^2}$$

$$R_{eq} = 1.09 \Omega/\text{ph}$$

$$R_{eq} = R_1 + R_2'$$

$$= 2R_1 = 2R_2'$$

$$R_1 = R_2' = R_{eq}/2$$

$$= 0.545 \Omega/\text{ph}$$

Cont. from blocked rotor test

$$Z_{eq} = \frac{V_{BR}/(\text{ph})}{I_{BR}/(\text{ph})} = \frac{150/\sqrt{5}}{35} = 2.47 \Omega/\text{ph.}$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2} = 2.22 \Omega/\text{ph.}$$

$$\frac{X_1}{X_2'} = \frac{1}{0.5} \Rightarrow X_2' = 0.5 X_1$$

$$X_{eq} = X_1 + X_2' \Rightarrow X_1 + 0.5 X_1 = 1.5 X_1$$

$$X_1 = 1.48 \Omega/\text{ph.}, \quad X_2' = 0.74 \Omega/\text{ph.}$$

$$I_c = I_{NL} \cos \theta_{NL} = 0.87775 \text{ A}$$

$$Z_{NL} = 30.7 \angle 83.33^\circ \Rightarrow$$


$$I_m = I_{NL} \sin \theta_{NL} = 7.43 \text{ A}$$

$$\boxed{\frac{X_m R_c}{X_m + R_c}}$$

$$R_c = \frac{V_{oc}(\text{ph})}{I_c} = 263.18 \Omega.$$

$$X_m = \frac{V_{oc}(\text{ph})}{I_m} = 31.0 \Omega.$$

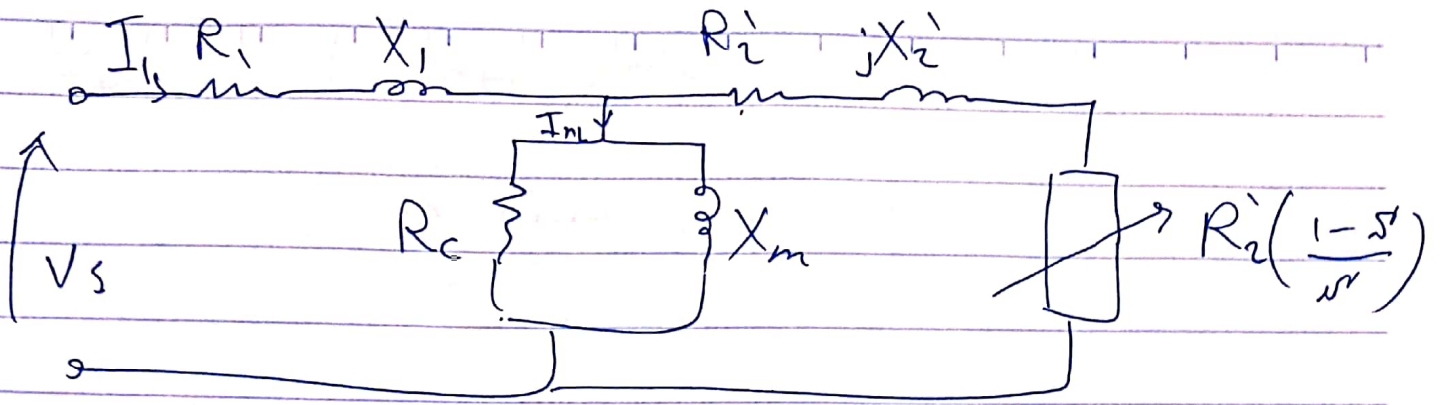, $V_{oc}(\text{ph})$ almost the same as the question given value so we substitute it.




$$Y_{nl} = \frac{1}{Z_{nl} \angle 83.33}$$

$$Y_{nl} = \left[\text{Circuit Diagram} \right] \text{Circuit Diagram}$$

$$G_c - j B_m$$
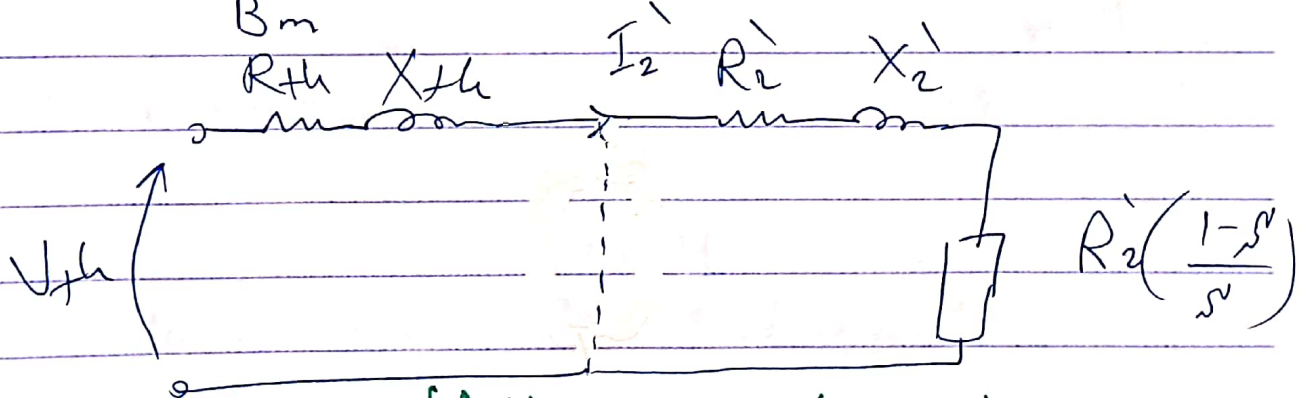
$$\frac{1}{G_c} = R_c \# \quad \frac{1}{B_m} = X_m \#$$



$$Z_{th} = Z_{nl} \parallel Z_1 \quad \text{جواب معادلہ ایستوان}$$

← حساب کنو ایستوان کی پاور اور پھر I_2' اور I_1' کا
 حساب کنو ایستوان کی پاور اور پھر Z_1 کا
 divider.

$$Z_{th} = \frac{(30.79 \angle 83.33) * (0.545 + j1.48)}{(30.79 \angle 83.33) + (0.545 + j1.48)}$$

$$Z_{th} = 1.506 \angle 70.44^\circ$$

$$= \underbrace{0.504}_{R_{th}} + j \underbrace{1.42}_{X_{th}}$$

Thevenin's Approximation

$$R_{th} = R_1 \left(\frac{X_1}{X_m + X_1} \right)^2 = 0.545 \left(\frac{1.48}{31 + 1.48} \right)^2$$

$$= 0.497 \Omega / \text{ph.}$$

$$X_{th} \approx X_1 = 1.48$$

$$\bullet \text{ error percentage} = 1.3\%$$

$$V_{th} \approx \left(\frac{X_m}{X_m + X_1} \right) V_s = \frac{31}{31 + 1.48} \times \frac{400}{\sqrt{3}}$$

$$= 220.4 \text{ V.}$$

$$\Rightarrow \text{actual } V_{th} = 220.9 \angle 0.65^\circ$$

$$I_2' = \frac{V_{th}}{Z_{th} + \frac{R_i'}{s} + jX_{i}'}$$

$$I_2' = \frac{220.9 \angle 0.65^\circ}{14.17 + j2.28} = 16.1 \text{ A}$$

$$P_{\text{mech}} = 3 * I_2'^2 * \left(\frac{1 - 0.04}{0.04} \right) * R_2'$$

$$P_{\text{in}} = 3 * 220.9 * I_2' \cos \theta_{\text{in}}$$

$$\theta_{\text{in}} = \theta_{V_{\text{th}}} - \theta_{I_2'}$$

$$\eta \% = \frac{P_o}{P_{\text{in}}} * 100\% \approx 92.6 \%$$

$$T_{\text{mech}} = \frac{P_{\text{mech}}}{(\omega_{\text{mech}})} \Rightarrow \omega_{\text{mech}} = \omega_s (1 - \delta)$$

$$\omega_s = \frac{2\pi N_s}{60}$$

$$P_d = 3 I_2'^2 \frac{R_2}{s} = P_g$$

air gap

$$T_g = \frac{P_g}{\omega_s}$$

The University of Jordan
Department of Electrical Engineering
Electrical Machines (II)

- (1) A 400 V, 6-pole, 3-phase, 50 Hz, star-connected induction motor running light (no-load) at rated voltage takes 7.5 A with a power input of 700 W. When the rotor is locked and a 150 V is applied to the stator, the input current is 35 A and the input power is 4000 W. The stator and copper losses are considered equal under this condition. The standstill leakage reactance of the stator and rotor as seen from the stator are estimated to be in the ratio of 1 : 0.5.
- (a) Calculate the net mechanical power and torque at a slip of 4%. Use the T-equivalent circuit.
 - (b) Calculate the motor efficiency under the above condition.
 - (c) Repeat (a) and (b) above by shifting the excitation branch to the input terminals (L-equivalent circuit). Compare the results.
 - (d) Repeat (a) and (b) above using Thevenin's equivalent circuit. Compare the results.

Assume the rotational losses included in the core resistance.

- (2) A 150 kW, 3000 V, 50 Hz, 6-pole star connected 3-phase induction motor has a star-connected slip-ring rotor with a transformation ratio of (stator-to-rotor) of 3.6. The rotor resistance is 0.1Ω and its per-phase leakage inductance is 3.61 mH. Stator impedance may be neglected. Calculate:
- (a) The starting current and the corresponding starting torque at rated voltage when the slip-rings are short-circuited.
 - (b) The necessary external resistance required to reduce the starting current to 30 A and the corresponding starting torque.
 - (c) The maximum torque developed in both cases and the speed at which it occurs.

(3) A certain squirrel-cage induction motor has a starting current of 600 % of the full-load current at a full-load slip of 0.05 %.

(a) Find in per-unit starting current and torque for the following methods of starting:

(1) Direct starting.

(2) Stator-resistance starting with a motor current limited to 200 %.

(3) Autotransformer starting with a motor current limited to 200 %.

(4) Star-Delta starting.

(b) What Autotransformer ratio would give 100 % starting torque?

(5) A 50 Hz, 3-phase induction motor has a rated voltage V_1 . The motor's breakdown torque at rated voltage and frequency occurs at a slip of 0.2. Stator impedance is neglected. Answer the following:

(a) If the motor runs at 60 Hz while the voltage is kept at V_1 find the ratios of starting current, starting torque and maximum torque compared to the rated ones.

(b) Find the ratio of V_1/V_2 such that the motor has the same values of starting current and torque at 50 and 60 Hz.

(c) If the motor runs at 25 Hz while the voltage V_2 is 50 % of V_1 , find the ratios of starting current, starting torque and maximum torque compared to the rated ones.

November 6, 2019

* Question

A 50 Hz, 3-ph Induction Motor has a rated voltage $V_r = V_1$, T_{max} & $T_{Break\ down}$ at the same rated V and $s = 20\%$ ($s_{T_{max}} \approx 0.2$)

$$Z = R_1 + jX_1 \rightarrow 0 \text{ (neglected)}$$

a) if the motor runs at $f_2 = 60 \text{ Hz}$ while the voltage is kept constant $V_2 = V_1$ → above rated value.

$$\Rightarrow \text{Find } \frac{I_{st}(2)}{I_{st}(1)} = ??, \frac{T_{st}(2)}{T_{st}(1)} = ??, \frac{T_{max}(2)}{T_{max}(1)} = ??$$

Sol

$$f_1 = 50 \text{ Hz} \rightarrow f_2 = 60 \text{ Hz}$$

$$V_1 = V_r \rightarrow V_2 = V_r$$

$$s_{T_{max}} = 0.2 = \frac{R_2'}{X_2'}$$

$$\sqrt{\frac{R_2'^2}{X_2'^2}} \approx \frac{R_2'}{X_2'} \Rightarrow \boxed{R_2' = 0.2 X_2'}$$

$$\boxed{X_2' @ 50 \text{ Hz}}$$

$$\begin{aligned} I_{st} &= \frac{\sqrt{3} V_{ph}}{\sqrt{R_2'^2 + X_2'^2}} = \frac{\sqrt{3} V_{ph}}{\sqrt{(0.2 X_2')^2 + X_2'^2}} \\ &= \frac{\sqrt{3} V_{ph}}{\sqrt{1.04} X_2'} \quad \left\{ \frac{V_{ph}}{1.02 X_2'} \right\} \textcircled{1} \end{aligned}$$

$$X_2'(\text{New}) = \frac{60}{50} X_2'$$

$$I_{st}' = \frac{V_{ph}}{1.02 \times 1.2 X_2'} = \frac{V_{ph}}{1.02 \times X_2'(\text{New})}$$

$$= \left[\frac{V_{ph}}{1.02 \times 1.2 X_2'} \right] \textcircled{2}$$

$$\Rightarrow \frac{I_{st}'}{I_{st}} = \frac{1.02 X_2'}{1.02 X_2' \times 1.2} = \frac{1}{1.2} = 0.83$$

Torque:

$$T_{st} = \frac{3 V_{ph}^2 R_2'}{\omega_s [R_2'^2 + X_2'^2]} \quad \text{Slip @ starting} = 1 \quad = \boxed{83\%}$$

$$T_{st} = \frac{3 V_{ph}^2 R_2'}{\omega_s [R_2'^2 + X_2'^2]} = \frac{3 V_{ph}^2 \times 0.2 \times X_2'}{\omega_s [0.04 X_2'^2 + X_2'^2]}$$

$$= \frac{3 V_{ph}^2 \times 0.2 \times X_2'}{\omega_s [1.04 X_2'^2]} = \left[\frac{3 V_{ph}^2 \times 0.2}{\omega_s [1.04 X_2']} \right] \textcircled{1}$$

$$T_{st}(\text{New}) = \frac{3 V_{ph}^2 R_2'}{\omega_s' [R_2'^2 + X_2'^2(\text{new})]}$$

$$\omega_s = \frac{2\pi f}{P}$$

$$= \frac{3 \text{ vph } R_2'}{\frac{60}{50} \times \omega_s R_2'^2 \left[1 + \frac{X_2'^2 (\text{New})}{R_2'^2} \right]}$$

$$\rightarrow X_2'^2 (\text{new}) = \left(\frac{60}{50} \right)^2 X_2'^2$$

$$= \frac{3 \text{ vph } R_2'}{\frac{60}{50} \omega_s R_2'^2 \left[1 + \frac{(1.2)^2 X_2'^2}{R_2'^2} \right]}$$

$$T_{se}' = \frac{3 \text{ vph}^2 R_2'}{\frac{60}{50} R_2'^2 \cdot \omega_s \left[1 + 1.44 \times \left(\frac{1}{0.2} \right)^2 \right]}$$


$$T_{se}' = \frac{3 \text{ vph}^2}{\omega_s R_2' \times 1.2 \times 37} \quad (2)$$

$$\bullet \frac{T_{se}'}{T_{se}} = \frac{X_2' \times 1.04}{R_2' \times 1.2 \times 37 \times 0.2}$$

$$= \frac{1.04}{0.2 \times 1.2 \times 0.2 \times 37} = 0.5855$$

1.58

Torque decreased.

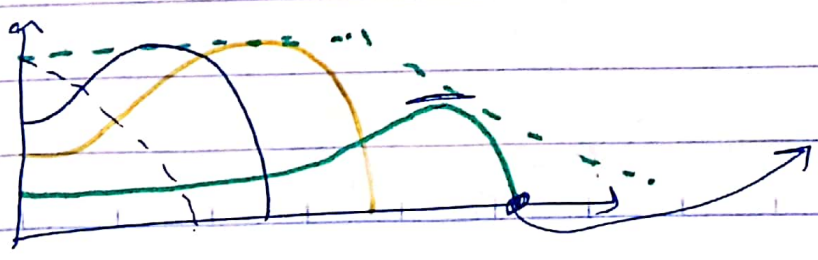

Max Torque

$$\bullet T_{\max} = \frac{3 V_{ph}^2}{2 \omega_s [X_2']^2} \rightarrow \frac{3 V_{ph}^2}{2 \omega_s \cdot [R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_2')^2}]^2}$$

$$T_{\max}' = \frac{3 V_{ph}^2}{2 \times \frac{60}{50} \omega_s \times \frac{60}{50} X_2'^2}$$

$$\sqrt{(X_2')^2} \times$$

$$\frac{T_{\max}'}{T_{\max}} = \frac{1}{\frac{60}{50} \times \frac{60}{50}} \left(\frac{50}{60}\right)^2 = 0.69$$

69%

(b) Find the ratio $\frac{V_1}{V_2} = ??$ such that the motor has the same value of starting current and starting torque. @ 50 & 60 Hz.

$$I_{st}(60) = I_{st}(50)$$

$$I_{st}' = I_{st}$$

$$\bullet I_{st} = \frac{V_{ph}(1)}{\sqrt{R_2'^2 + X_2'^2}} = \frac{V_{ph}(1)}{1.02 \times X_2'}$$

@
50
Hz

$$I_{st}' = \frac{V_{ph}(2)}{\sqrt{R_2'^2 + \left(\frac{60}{50}\right)^2 X_2'^2}} = \frac{V_{ph}(2)}{\sqrt{0.04 X_2'^2 + 1.44 X_2'^2}}$$

@
60
Hz

$$\frac{V_{ph}(2)}{\sqrt{1.48} X_2'} = \frac{V_{ph}(2)}{1.22 X_2'}$$


- $I_{st}' = I_{st}$

$$\frac{V_{ph}(2)}{1.22 X_2'} = \frac{V_{ph}(1)}{1.02 X_2'}$$

$$\Rightarrow \frac{V_{ph}(2)}{V_{ph}(1)} = \frac{1.22}{1.02} = 1.19 \approx 1.2 \text{ or}$$

120%

constant Torque.

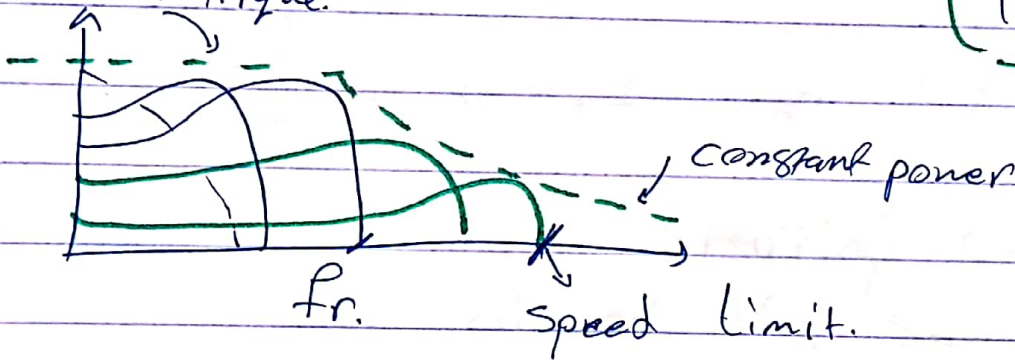

c) if $f_2 = 25 \text{ Hz}$ & $V_2 = 50\%$

$f_2 \downarrow$ 50% $V_2 \downarrow$

V/f constant

- $I_{st} = \frac{V_{ph}}{\sqrt{R_2'^2 + X_2'^2}} = \frac{V_{ph}}{1.02 X_2'}$

$$I_{st}' = \frac{0.5 \text{ Vph.}}{\sqrt{R_2'^2 + (0.5 X_2')^2}} = \frac{0.5 \text{ Vph}}{\sqrt{R_2'^2 + 0.25 X_2'^2}}$$

$$= \frac{0.5 \text{ Vph}}{\sqrt{0.04 X_2'^2 + 0.25 X_2'^2}} = \frac{0.5 \text{ Vph}}{\sqrt{0.29} X_2'}$$

$$\bullet \frac{I_{st}'}{I_{st}} = \frac{\frac{0.5 \text{ Vph.}}{\sqrt{0.29} X_2'}}{\frac{\text{Vph}}{1.02 X_2'}} = \frac{0.5 \times 1.02}{\sqrt{0.29}}$$

$$\frac{I_{st}'}{I_{st}} = 0.997 \Rightarrow 99.7\%$$

The starting current is almost the same.

Homework

$$\frac{\text{Starting } T'}{\text{Starting } T}$$

$$T_{max} = \frac{3 \text{ Vph}^2 R_2'}{2 \omega_s [X_2']} = 0.2$$

$$T_{max} = \frac{3 \text{ Vph}^2 \cdot 0.2}{2 \omega_s}$$

$$\bullet T_{max}' = \frac{3 \times 0.25 \text{ Vph}^2 R_2'}{2 \times 0.5 \omega_s \times 0.5 X_2'} = 0.2$$

$$T_{max}' = \frac{3 \times 0.25 \times 0.2 \times \text{Vph}^2}{2 \times \omega_s \times 0.5 \times 0.5}$$

$$\frac{T_{max}'}{T_{max}} = 1$$

18 // 2019

Lecture 15

- when $Z_1 = R_1 + jX_1$ are neglected
define $\lambda_f = f/f_r$

$$\lambda_v = v/v_r$$

- $$\frac{I_{se}'}{I_{st}} = \frac{\lambda_v}{\lambda_f} \sqrt{\frac{\sqrt{T_{max}^2 + 1}}{\sqrt{T_{max}^2 + \lambda_f^2}}}$$

- $$\frac{T_{st}'}{T_{st}} = \lambda_v^2 / \lambda_f \cdot \frac{\sqrt{T_{max}^2 + 1}}{\sqrt{T_{max}^2 + \lambda_f^2}}$$

- $$\frac{T_{max}'}{T_{max}} = \left(\lambda_v / \lambda_f \right)^2$$

- $$X_2(\text{new}) = \frac{f_{\text{new}}}{f_{\text{old}}} * X_2'(\text{old})$$

- $$X_2'(\text{old})_{\text{rated}} = 2\pi f \ell_2' = 2\pi \ell_2' \cdot f_{\text{rated}}(\text{old}) \rightarrow \frac{X_2'(\text{new})}{X_2'} = \dots$$

$$X_2'(\text{new}) = 2\pi \ell_2' f(\text{new}) = 2\pi \ell_2'$$

$$\frac{X_2'(\text{new})}{X_2'} = \frac{f_{\text{new}}}{f_{\text{old}}}, \quad X_2'(\text{new}) = X_2' \left(\frac{f_{\text{new}}}{f_{\text{old}}} \right)$$

- $$\omega_s(\text{new}) = \lambda_f \omega_s(\text{old})$$

$$X_2'(\text{new}) \rightarrow \lambda_f X_2(\text{old}), \quad \frac{v}{v_r} = \lambda_v$$

① Below rated speed $f < f_r \rightarrow \lambda_f < 1$ } $\frac{V}{f} = \text{constant}$
 $V < V_r \rightarrow \lambda_v < 1$ }

$$\lambda_f = \lambda_v$$


$$\frac{V}{f} = \text{constant} = 4.44 \phi_m \cdot N$$


Saturation. λ إلى λ_m

② $f > f_r \rightarrow \lambda_f > 1$
 $\lambda_v = 1$

← مفرغ الجهد
 Voltage

→ Field weakening.

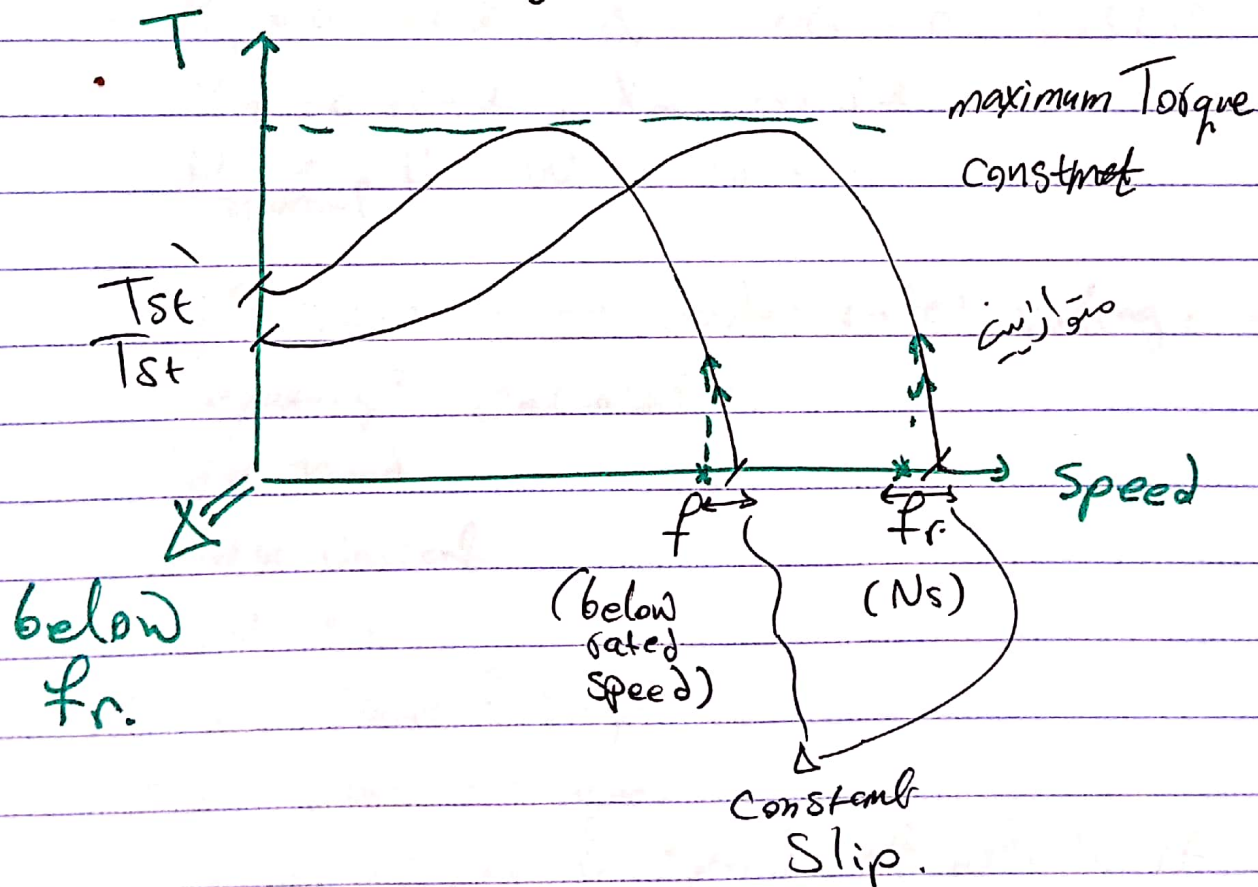

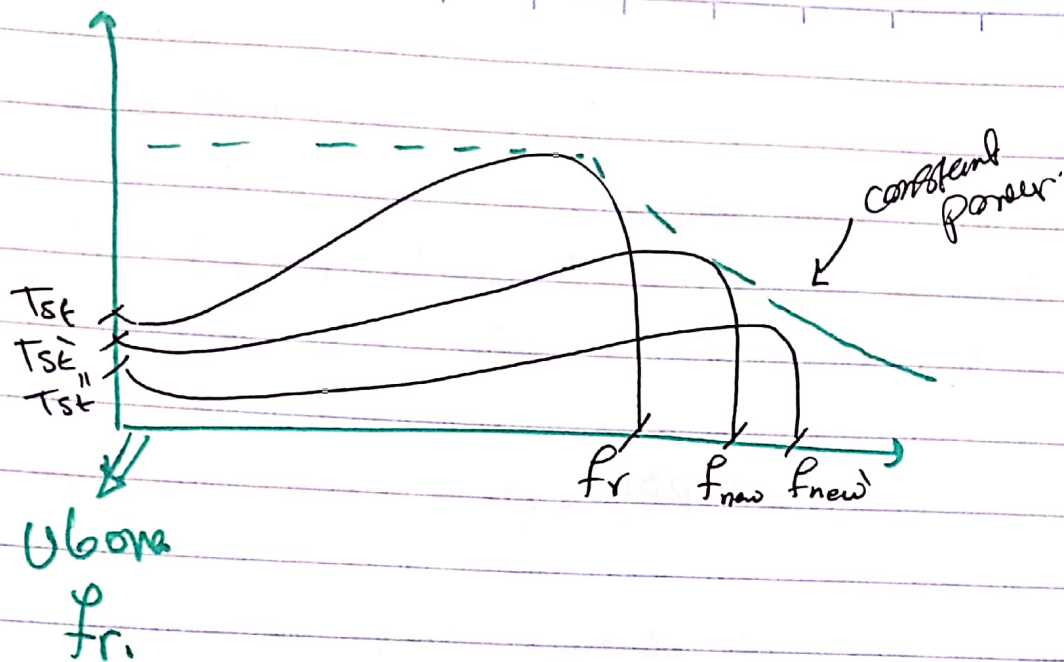

Question:- 460 V, 25 hp, 60 Hz, 4-poles
 Y-connected Induction motor.

$\rightarrow R_1 = 0.641 \Omega, X_2 = 1.106, R_2' = 0.332 \Omega$

$X_2' = 0.464 \Omega, X_m = 26.3 \Omega$

$P_{\text{rotational}} = 1100 \text{ W constant.}$

$s = 0.022 \rightarrow$ Under rated voltage and frequency. Calculate:-

- Motor speed
- Stator current
- Input PF
- air gap power & torque.
- output power & torque.
- Maximum Torque & speed at which it occurs.
- Motor efficiency.
- $\frac{I_{st}}{I_r} = ??, \frac{T_{st}}{T_r} = ??$

Solution.

$$N_s = \frac{60f}{p} = \frac{60 \times 60}{2} \rightarrow \text{pole pair (4-poles, 2-pairs)}$$


$$N_m = (1-s) N_s = 1760 \text{ RPM mechanical speed.}$$

$$\omega_s = \frac{2\pi f}{p} = \frac{2\pi \times 60}{2} = 188.5 \text{ rad/s}$$

$$\omega_m = \omega_s (1-s) = 189.4 \text{ rad/s}$$

Note:-

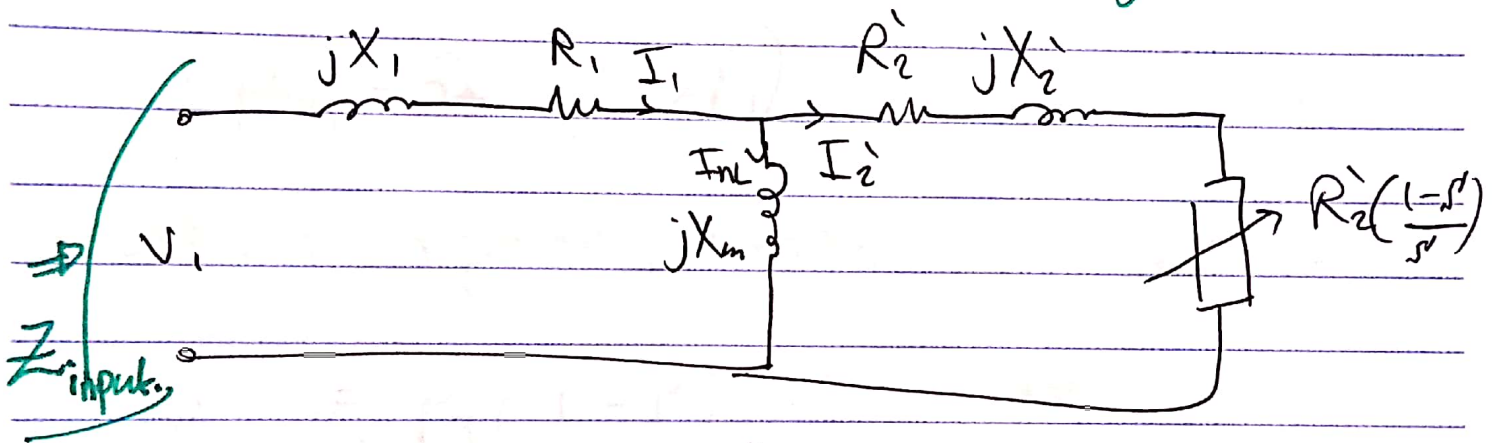R_c is not given because its value is large & when its parallel with X_m I can neglect it



$$Z_{in} = Z_{stator} + jX_m \parallel Z_{rotor}$$

$$= 0.64 + j1.106 + j26.3 * \left(\frac{0.332}{0.22} + j0.464 \right)$$

$$\frac{0.332}{0.22} + j(26.3 + 0.464)$$

$$= 14.07 \angle 33.6^\circ \text{ } \Omega/\text{ph.}$$

$$I_1 = \frac{460/\sqrt{3} \angle 0^\circ}{14.07 \angle 33.6^\circ} = 18.88 \angle -33.6^\circ \text{ A}$$

$$P_{in} = \sqrt{3} * 18.88 * 460 * \cos(\theta_{in})$$

$\sqrt{3} * I_L$ \downarrow \downarrow
 V_L, I_L Y-connected V_L

So I_L

$$P.F._{input} = \cos(0 - (-33.6^\circ)) = 0.833 \text{ (lagging)}$$

لتر الحثية

$$P_{in} = \sqrt{3} * 18.88 * 460 \frac{\cos \theta_{in}}{P.F.} = 12.53 \text{ kW.}$$

$$P_g = P_{in} - P_{cu} \Rightarrow 12.530 - 3 * 18.88^2 * 0.641$$

$$(P_{cu} = 3 * I_{ph}^2 * R_1) \Rightarrow 11845 \text{ W} = P_g$$

Note: In power we take losses per phase.

$$P_{converted} = P_g (1 - s) = 11585 \text{ W}$$

$$P_{out} = P_{shaft} = P_{converted} - P_{rotational}$$

$$11585 - 1100 = \boxed{10485 \text{ W}}$$

$$\bullet T_g = T_{ind} = T_d = P_g / \omega_2 = 62.8 \text{ Nm.}$$

$$T_{shaft} = \frac{P_{out/shaft}}{\omega_m} = 56.9 \text{ Nm.}$$

$$\eta = \frac{P_o}{P_{in}} \times 100\% = \frac{P_{sh}}{P_{in}} = 83.7\%$$

$$Z_{th} \text{ exact} = \frac{jX_m(R_1 + jX_1)}{R_1 + j(X_m + X_1)} \Rightarrow \frac{0.5908 + j1.0747}{\downarrow \quad \downarrow}$$

$R_{th} \quad X_{th}$

$$Z_{th} \text{ approximate} \Rightarrow R_{th} = R_1 \left(\frac{X_m}{X_m + X_1} \right)^2$$

$$X_{th} \approx X_1$$

So, $R_{th} = 0.59 \Omega$
 $X_{th} = 1.106$

$$\sigma_{T_{max}} = \frac{R_2'}{\sqrt{R_{th}^2 + (X_{th} + X_2')^2}} = 0.2615 \text{ (exact)}$$

$$\sigma_{T_{max}} \Rightarrow \text{maximum Torque} \Rightarrow N_m = N_s(1 - 0.2615)$$

$$V_{th} = 0.95938 \angle 1.34^\circ$$


exact

$$V_{th} \text{ approximate per phase} = V_r \text{ per phase} \cdot \frac{X_m}{X_m + X_1}$$

$$V_{th} = 0.95964$$

$$T_{max} = \frac{3 V_{th}^2}{2 \omega_s [R_{th} + \sqrt{R_{th}^2 + (X_{th} + X_i)^2}]^2} = \dots$$

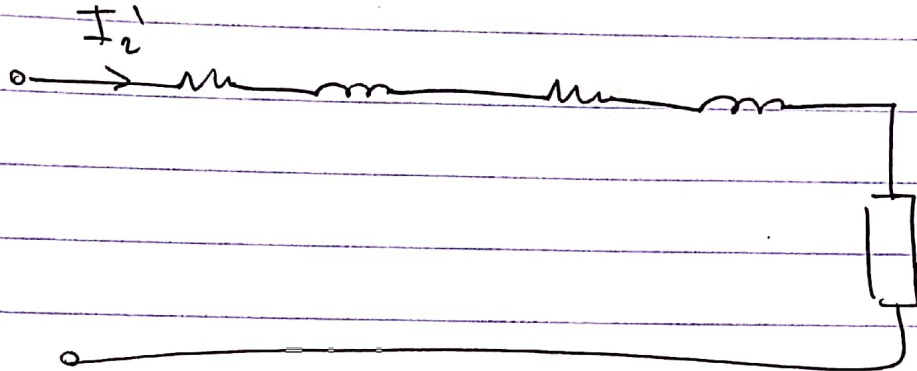for I_{st} we use Thevenin's Equivalent circuit



$$\frac{T_{se'}}{T_r} = \frac{3 I_{se}^2 R_i}{3 I_r^2 + \frac{R_i^2}{S_r}} = \frac{I_{se}^2 \times S_r}{I_r^2}$$

$$= \left[\left(\frac{I_{se}}{I_r} \right)^2 \times S_{rated} \right]$$

ex if $I_{rated} = 500\%$ or $5pu$.

$$S_r = 0.05$$

(sol)

$$\frac{T_{se}}{T_r} = 5^2 \times 0.05 = 1.25 pu$$

125%

classes starting current & Torque. Very Important
 Question in Exam \rightarrow is this motor class A, B, C or D
 Multiple choice

The University of Jordan
Department of Electrical Engineering
Electrical Machines (II)

- (1) A 400 V, 6-pole, 3-phase, 50 Hz, star-connected induction motor running light (no-load) at rated voltage takes 7.5 A with a power input of 700 W. When the rotor is locked and a 150 V is applied to the stator, the input current is 35 A and the input power is 4000 W. The stator and copper losses are considered equal under this condition. The standstill leakage reactance of the stator and rotor as seen from the stator are estimated to be in the ratio of 1 : 0.5.
- (a) Calculate the net mechanical power and torque at a slip of 4%. Use the T-equivalent circuit.
 - (b) Calculate the motor efficiency under the above condition.
 - (c) Repeat (a) and (b) above by shifting the excitation branch to the input terminals (L-equivalent circuit). Compare the results.
 - (d) Repeat (a) and (b) above using Thevenin's equivalent circuit. Compare the results.

Assume the rotational losses included in the core resistance.

- (2) A 460 V, 25 hp, 60 Hz, 4-pole, Y-connected induction motor has the following per phase equivalent circuit parameters referred to the stator circuit: $R_1 = 0.641 \Omega$, $R_2' = 0.332 \Omega$, $X_1 = 1.106 \Omega$, $X_2' = 0.464 \Omega$, $X_m = 26.3 \Omega$. The total rotational losses including the core loss are 1100 W and are assumed to be constant. For a rotor slip of 0,022 and rated voltage and frequency calculate the following:
- (a) Motor speed
 - (b) Stator current
 - (c) Input power factor
 - (d) Air-gap power and torque
 - (e) Output power and torque
 - (f) Maximum torque and speed at which it occurs
 - (g) Motor efficiency

(3) A 460 V, 25 hp, 60 Hz, 4-pole, Y-connected induction motor has the following per phase equivalent circuit parameters referred to the stator circuit: $R_1 = 0.641 \Omega$, $R_2' = 0.332 \Omega$, $X_1 = 1.106 \Omega$, $X_2' = 0.464 \Omega$, $X_m = 26.3 \Omega$. Answer the following questions:

(a) If the motor runs at 200 % of the rated frequency while the input voltage and slip are kept at their rated value, then calculate:

- (1) Motor speed
- (2) Stator current
- (3) Input power factor
- (4) Air-gap power and torque
- (5) Output power and torque
- (6) Maximum torque and speed at which it occurs
- (7) Motor efficiency

(b) If the motor runs at 50 % of the rated frequency while the input voltage is reduced such that the airgap flux is kept constant, and the slip is kept at its rated value, then calculate:

- (1) Motor speed
- (2) Stator current
- (3) Input power factor
- (4) Air-gap power and torque
- (5) Output power and torque
- (6) Maximum torque and speed at which it occurs
- (7) Motor efficiency

Comment on the above calculation results, compared to those of those obtained at rated loading conditions.

- (4) A 150 kW, 3000 V, 50 Hz, 6-pole star connected 3-phase induction motor has a star-connected slip-ring rotor with a transformation ratio of (stator-to-rotor) of 3.6. The rotor resistance is 0.1Ω and its per-phase leakage inductance is 3.61 mH. Stator impedance may be neglected. Calculate:
- The starting current and the corresponding starting torque at rated voltage when the slip-rings are short-circuited.
 - The necessary external resistance required to reduce the starting current to 30 A and the corresponding starting torque.
 - The maximum torque developed in both cases and the speed at which it occurs.
- (5) A certain squirrel-cage induction motor has a starting current of 600 % of the full-load current at a full-load slip of 0.05 %.
- Find in per-unit starting current and torque for the following methods of starting:
 - Direct starting.
 - Stator-resistance starting with a motor current limited to 200 %.
 - Autotransformer starting with a motor current limited to 200 %.
 - Star-Delta starting.
 - What Autotransformer ratio would give 100 % starting torque?
- (6) A 50 Hz, 3-phase induction motor has a rated voltage V_1 . The motor's breakdown torque at rated voltage and frequency occurs at a slip of 0.2. Stator impedance is neglected. Answer the following:
- If the motor runs at 60 Hz while the voltage is kept at V_1 find the ratios of starting current, starting torque and maximum torque compared to the rated ones.
 - Find the ratio of V_1/V_2 such that the motor has the same values of starting current and torque at 50 and 60 Hz.
 - If the motor runs at 25 Hz while the voltage V_2 is 50 % of V_1 , find the ratios of starting current, starting torque and maximum torque compared to the rated ones.

Q5)

Inuction Motor: Δ -connected.


$I_{se} = 600\%$ or 6 pu at rated Slip of 0.05 or 5%, ($s_r = 5\%$), $\frac{I_{se}}{I_{rated}} = ??$, $\frac{I_{se1}}{I_r} = ??$

→ $\frac{I_{se}}{I_r} = 6 \text{ pu}$

a) direct starting (starting at rated voltage)

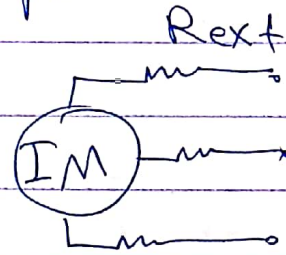b) $I_{se} = 2 \text{ pu}$. $\frac{I_{se}}{I_{rated}} = 2 \text{ pu}$.

$$I_{se} = \frac{V}{\sqrt{(R_1 + R_2)^2 + (X_1 + X_2)^2}}$$




to reduce the starting current:


→ reduce V

→ Increase R_{eq} or X_{eq} .

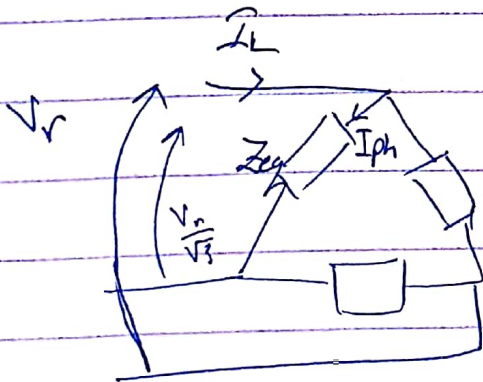Auto transformer: $a = ??$ ($\frac{I_{se1}}{I_{rated}} = 2 \text{ pu}$)




$$V_{ph} = \frac{V_r}{\sqrt{3}}$$

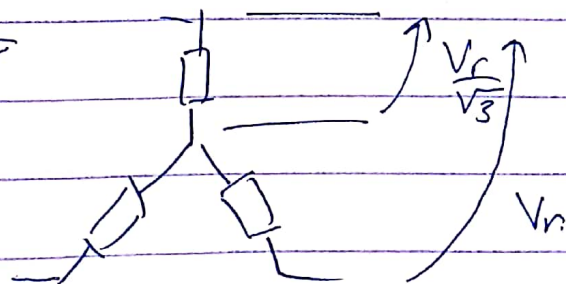

$$I_{ph} = I_L = \frac{V_r}{\sqrt{3} * Z_{eq}}$$

autotransformer

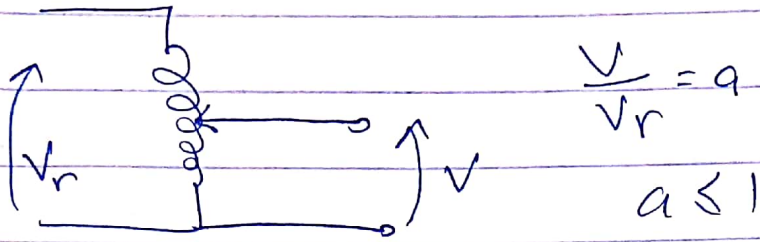

d) Y-Δ Starting.


e) $\frac{T_{se}}{T_r} = 1 \rightarrow a = ??$

Solution

$\rightarrow \frac{T_{se}}{T_r} = \left(\frac{I_{se}}{I_r}\right)^2 * \sqrt{\text{rated}}, \quad (V = V_r)$

$\frac{T_{se}}{T_r} = \frac{T_{se}'}{T_r} \dots (6)^2 * 0.05 = 1.8 \text{ pu}$

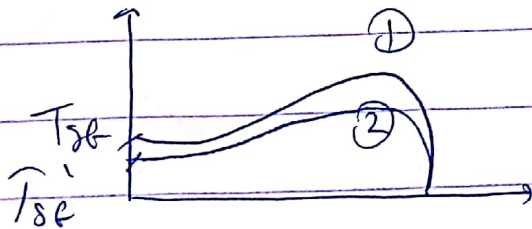$\rightarrow \frac{T_{se}}{I_r} = 2 \rightarrow \frac{T_{se}'}{T_r} = (2)^2 * 0.05 = 0.2 \text{ pu}$



$\rightarrow \frac{T_{se}'}{I_r} = ?? \quad I_{se} = \frac{V_r}{\sqrt{(R_1 + R_2)^2 + (X_1 + X_2)^2}}, \quad I_{se}' = \frac{V}{\sqrt{''}}$

$$\frac{I_{se}'}{I_{se}} = \frac{V}{V_r} = a, \quad \frac{I_{se}'}{I_{st}} = 2, \quad \frac{I_{se}'}{I_{se}} + \frac{I_{rated}}{I_{rated}} = a$$

$$\frac{I_{se}'}{I_r} = 2 = a + \frac{I_{se}}{I_r}$$

$$2 = a + 6$$

$$a = \frac{2}{6} = \frac{1}{3} \# \text{ (turns ratio / voltage reduction ratio / Transformation ratio)}$$


$$\rightarrow \frac{T_{se}'}{T_{st}} = \left(\frac{V}{V_r}\right)^2 = a^2, \quad T_{st} = \frac{3 V^2 R_i}{\omega_s \sqrt{\dots}}$$

⊗ Torque is proportional to (V^2) .

$$\text{Slip} = 1, \quad \left(\frac{1}{3}\right)^2 \rightsquigarrow \frac{1}{9} \#$$

$$\frac{I_{se}'}{I_r} = \frac{I_{se}}{I_{se}} \times \frac{I_r}{I_r} = ??, \quad \frac{I_{se}'}{I_r} = \left(\frac{1}{3}\right)^2 \times \frac{I_{st}}{I_r}$$
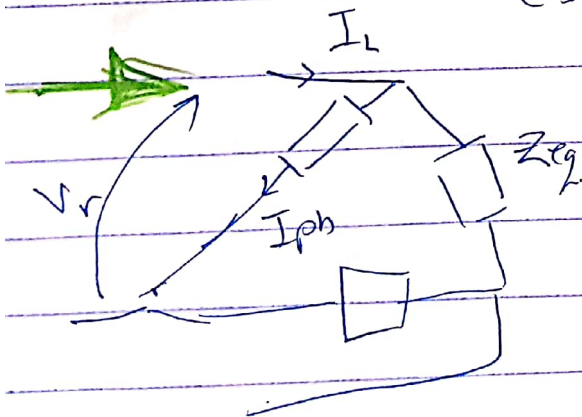
$$\left(\frac{1}{3}\right)^2 \times 1.8 = 0.2 \text{ pu}$$




$$I_{ph(st)} = \frac{V_r}{Z_{eq}} \quad \text{starting}$$

$$I_L(st) = \sqrt{3} I_{ph(st)}$$

$$I_{se} = I_L(st) = I_{ph(st)} = \frac{V_r}{\sqrt{3} * Z_{eq}}$$

$$I_L(st) = I_{ph}(st)$$

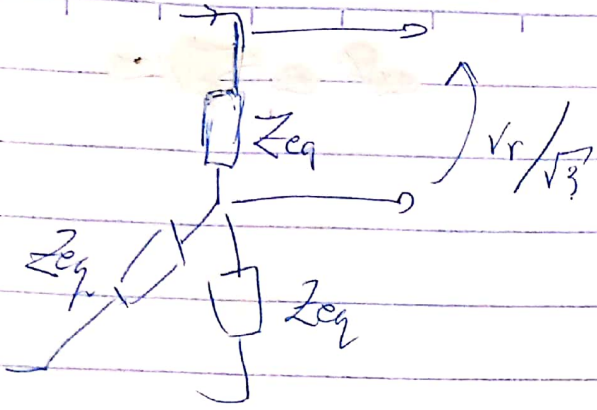

$$\frac{I_{se}'}{I_{st}} = \frac{V_n}{\sqrt{3} Z_{eq} \sqrt{3} \frac{V_r}{\sqrt{3}} Z_{eq}} = \left(\frac{1}{3}\right) \neq$$


. Δ also go, Δ also go \neq Y also go (also go), Δ also go

→ $\frac{I_{st}'}{I_r} = ??$

$$\frac{I_{st}'}{I_{st}} = \left(\frac{1}{\sqrt{3}}\right)^2 = \frac{1}{3}$$

$$\frac{I_{se}'}{I_{st}} + \frac{I_r}{I_r} = \frac{1}{3} \Rightarrow \frac{I_{se}'}{I_r} = \frac{1}{3} * \frac{I_{st}}{I_r}$$

$$\frac{1}{3} * 1.8 = 0.6 \text{ pu}$$

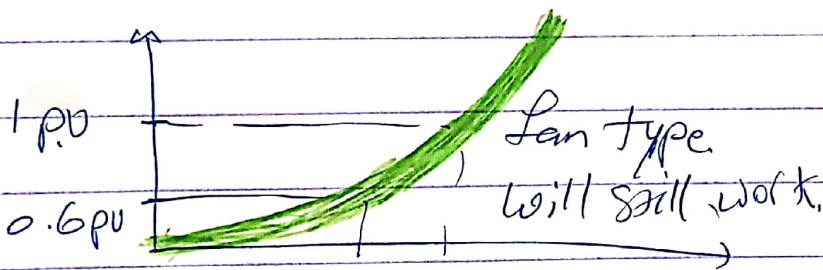

→ $a^2 = \frac{I_{st}'}{I_r} + \frac{1}{\frac{I_{st}}{I_r}}$

$$1 * \frac{1}{1.8}$$

$$a = \sqrt{\frac{1}{1.8}} = 0.745$$

Q4: Homework on notebook :- R_2 : without reflecting
 $R_2' \rightarrow * a^2$
150 W output power

(a)

$R_{ext} = 0$, Slip rings short circuited.

(b)


$$I_{sc} = \frac{V_r}{\sqrt{(R_i + R_{ext})^2 + (X_i)^2}}$$

30

$$\sqrt{(R_i + R_{ext})^2 + (X_i)^2}$$

پہلو پر

مربع

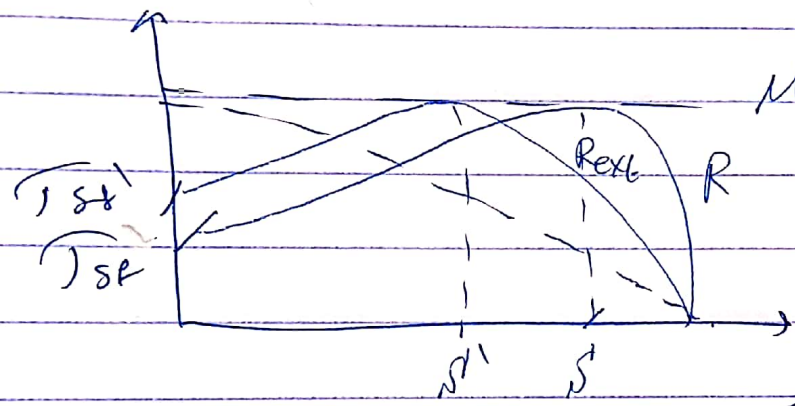

Maximum torque independent
So in both cases

پہلو پر

Slip

تحتی T_{st} و T_{st}

(c)

پہلو پر

؟



Find $R_{ext} = ?$ $\Rightarrow T_{st} = T_{max}$


$$\left(\frac{s}{s_{max}} \right)_{T_{st} = T_{max}} = 1$$

$$\frac{R_i + R_{ext}}{\sqrt{\dots}}$$

referred value


actual $\neq a^2 s_{r,sc}$

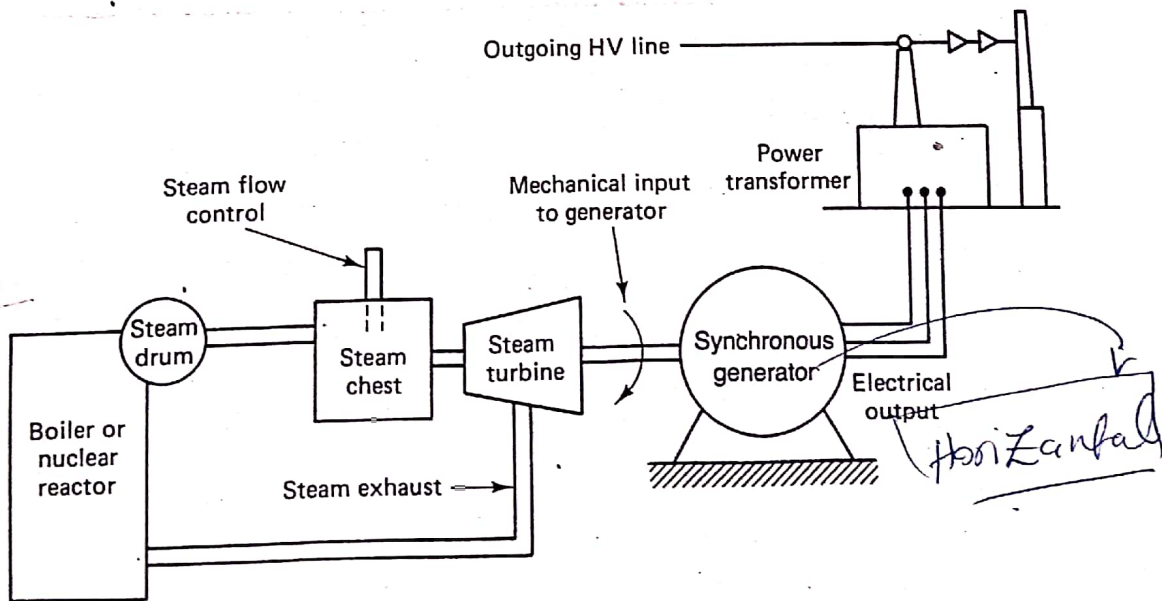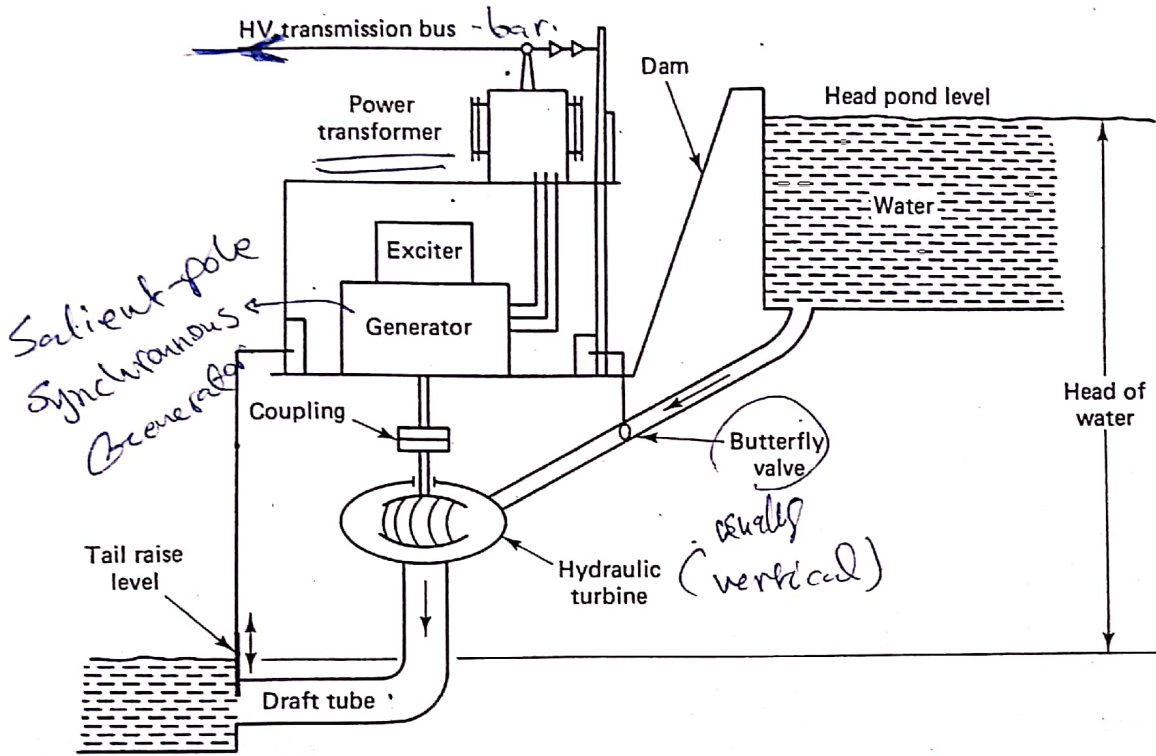

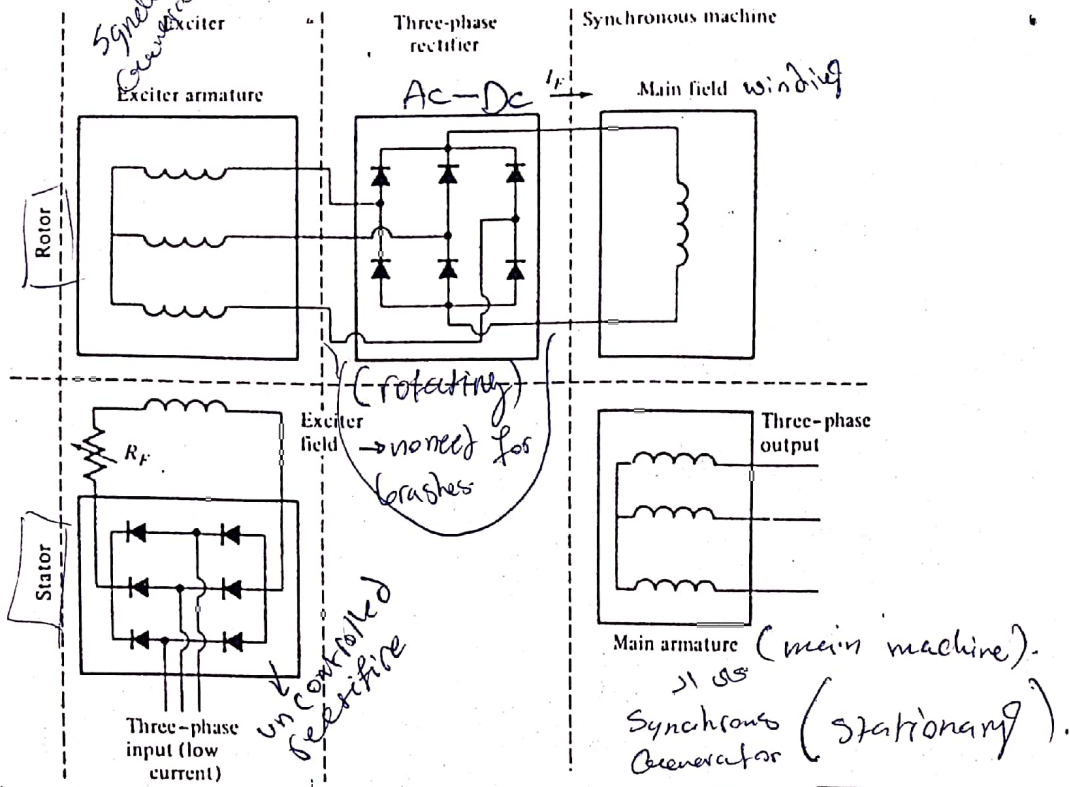

⊗ less losses → controlled rectifier without R_F .

Brushless Exciter A

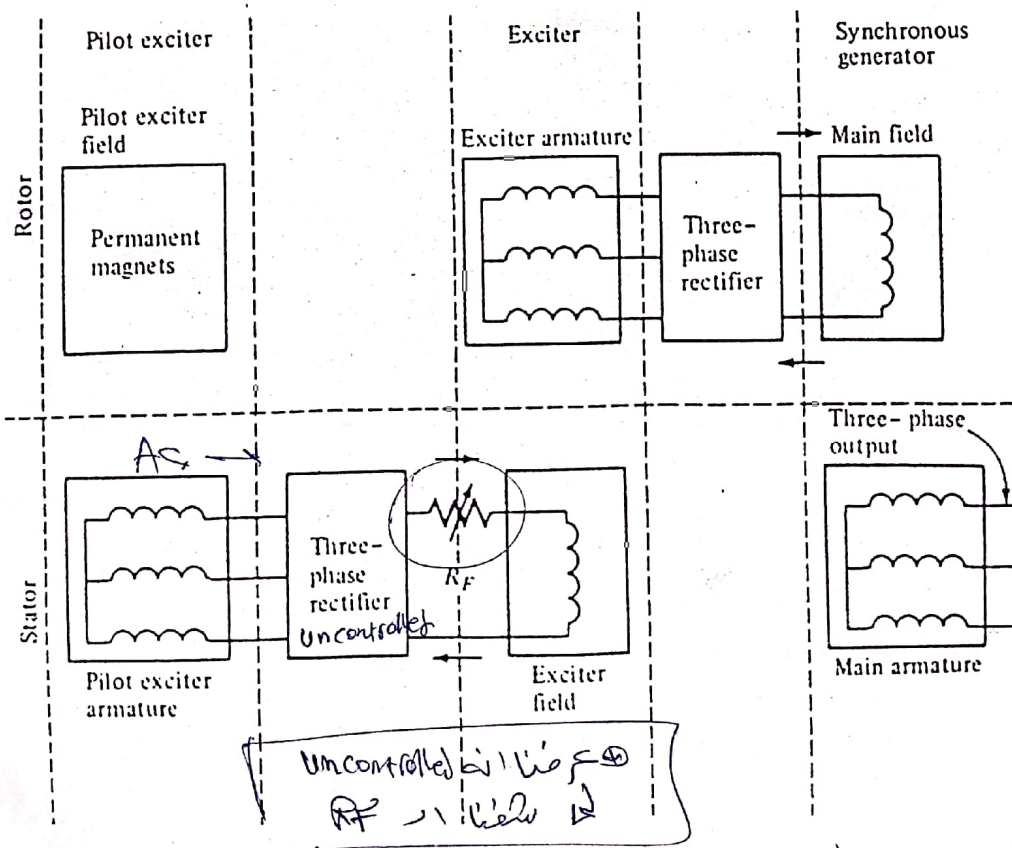

Brushless Exciter B → (Better) جيد


according to page ~~Page 1~~

Synchronous Machines

1 Salient-pole & Hydraulic Turbine, High number of poles (Low speed)

$(2p \geq 8)$
 $\rightarrow f = ??, N = \frac{60f}{p} \approx 750 \text{ RPM} \downarrow (600 \rightarrow 600)$

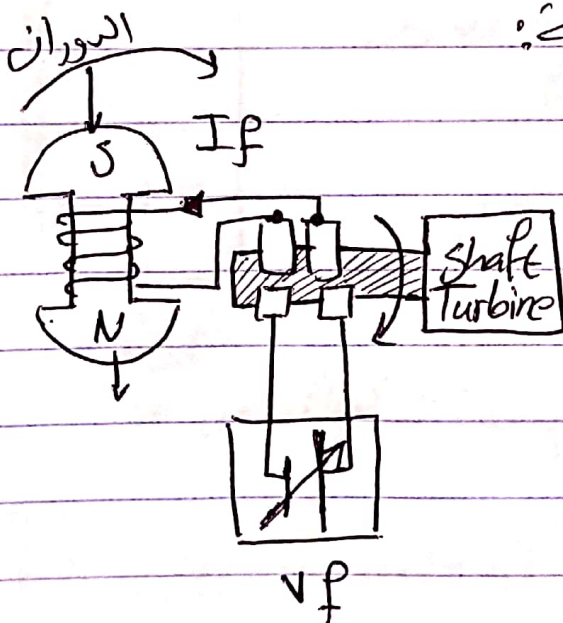⊗ Butterfly valve = directly related to power & frequency



⊙ three electrical quantities:

- ① power
- ② voltage
- ③ Frequency!

to control the Excitation ckt.


$$V_s = 4.44 \times N \times \phi \times f$$

{ Brush - excitation }


⊗ Voltage control by the field circuit and reactive power

Q

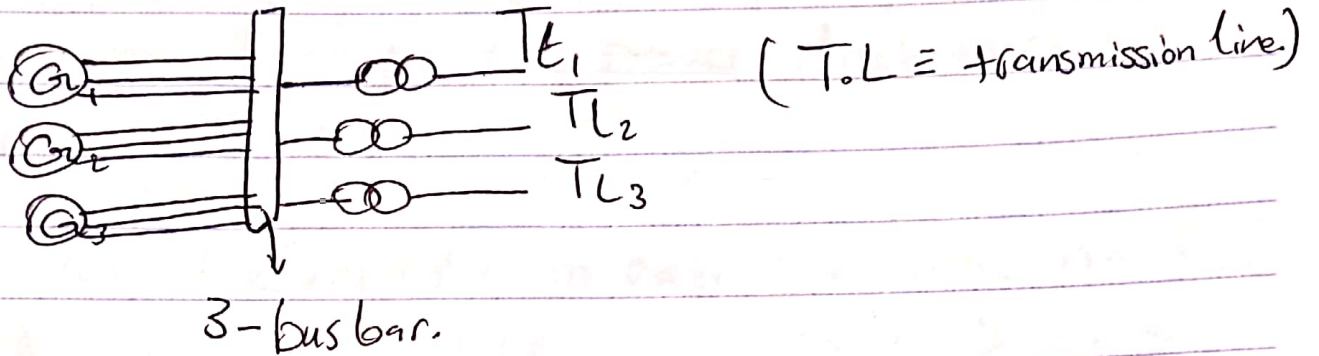- Real power and frequency are controlled by throttles in the flow path of water.




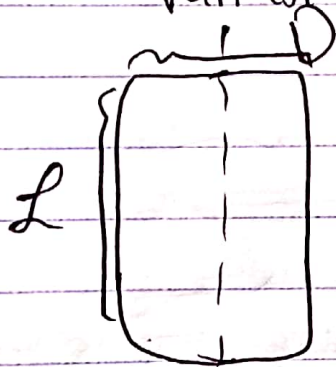- Infinite bus bar \equiv voltage & frequency of the signal are fixed irrespective of load variations.



power = $f(D, L, \dots)$
 function of \downarrow
 الابعاد

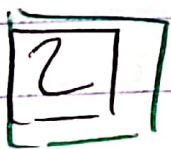- For certain power D & L are fixed.
- usually \neq large diameter D , (and length L).



Cylindrical-Rotor: Diesel, Gas, Steam turbine...

- Low number of poles 2 or 4.

So, $N_s = 1500 \rightarrow 3000$ RPM

$1800 \rightarrow 3600$ RPM

(USA)


- High speed machines. Horizontal, low Diameter, long length

Disadvantages: Brushes & slip rings.
 (before power electronics)

referring to page 2

pilot Exciter: in case there was no field at the beginning (residual flux doesn't exist)

Development of the Equivalent Circuit

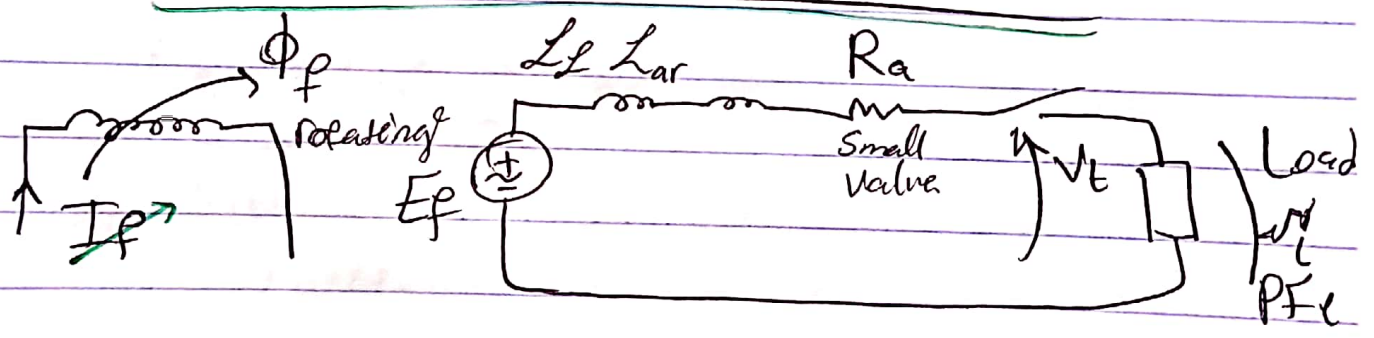

$R_a \equiv$ armature resistance (in big machines \rightarrow small value). /ph.

$L_\ell \equiv X_\ell = 2\pi f L_\ell$
 Leakage

$L_{ar} \equiv$ armature reaction from stator

$L_{ar} \gg L_\ell$
 armature reaction Leakage

or \bar{B} 's field.

• E_f : no load internal voltage

$$E_f = f \left(\underbrace{L_s}_{\text{Function of Speed of } I_f} , \underbrace{\phi_f}_{\text{or related to } I_f} \right)$$

$$I_f * K = \phi_f$$

$$E_f = (4.44 * k_w * N_{ph} * \underbrace{\phi_f}_{\text{field}} * \underbrace{f}_{\text{from speed}}) \text{ V/ph.}$$

• $E_f \Rightarrow$ open circuit test readings.

• Since L_l and L_{ar} are two series inductances in

$$L_s = L_l + L_{ar}$$


↓
Synchronous Inductance.

$$X_s = \omega * L_s$$


Synchronous reactance.

, $X_s \gg R_a$
Therefore: R_a is usually neglected

Synchronous machines

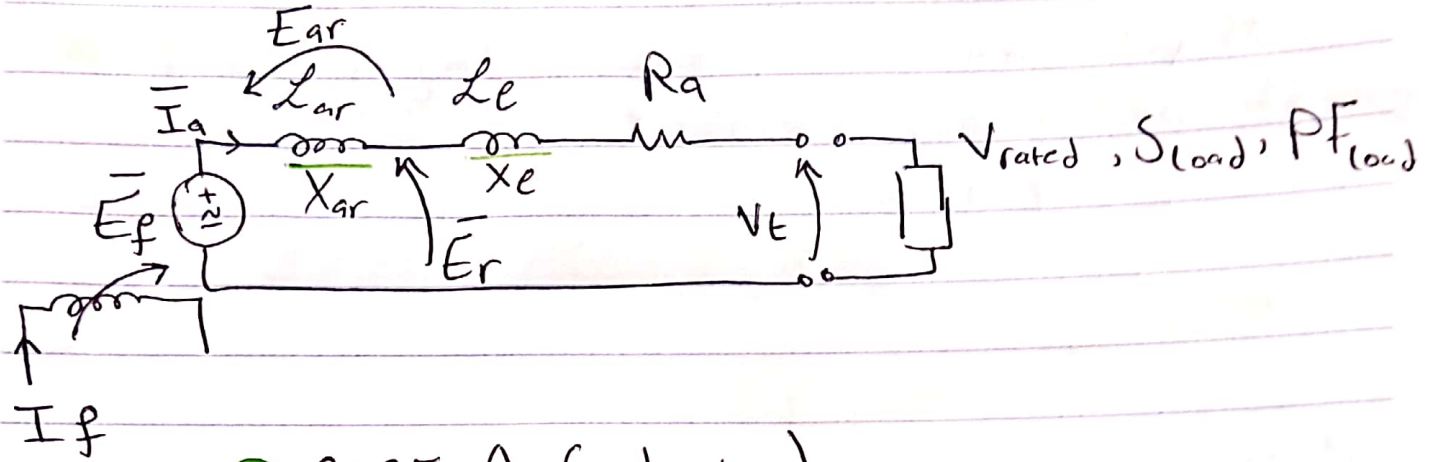

CASE A (inductive)

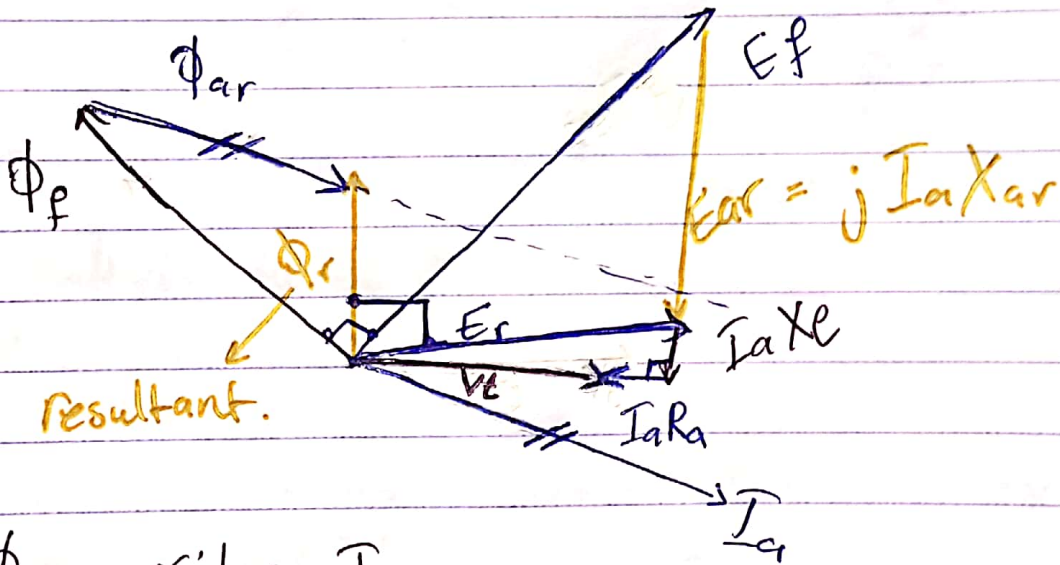

$\phi_{ar} \approx \phi_{Ia}$


$X_s = X_{ar} + X_e$
 Synchronous reactance = armature reaction + leakage

$X_{ar} \gg X_e$

$Z_s = R_a + jX_s = \sqrt{R_a^2 + X_s^2} \angle \theta_s$
 Synchronous Impedance.

• $\theta_s = \tan^{-1} \left(\frac{X_s}{R_a} \right)$, usually $R_a \ll X_s$.

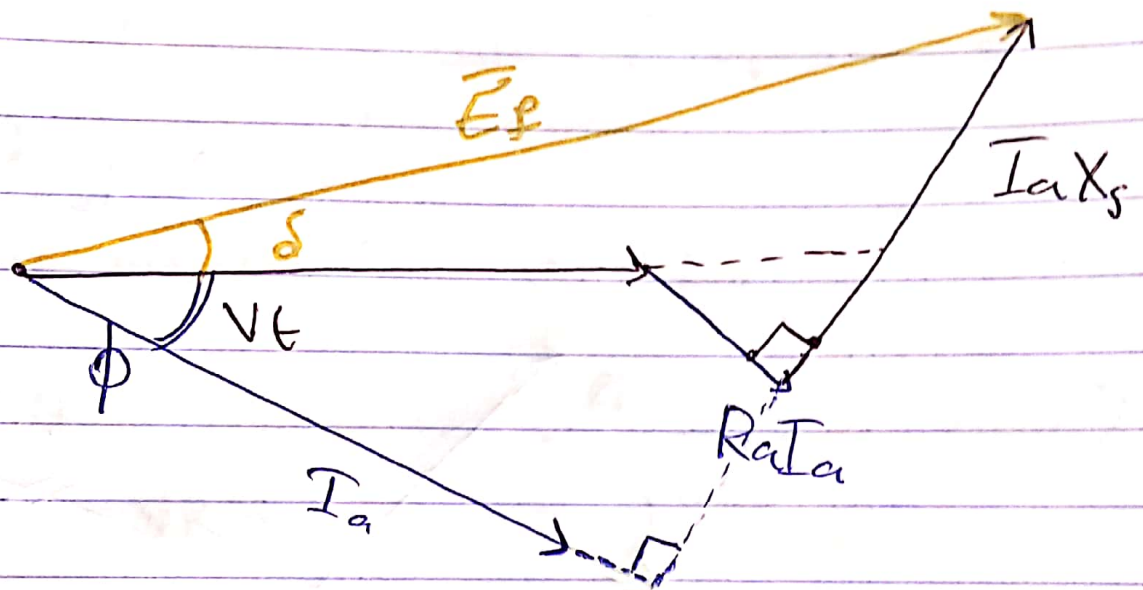• $R_a \approx \left(\frac{1}{100} \right) X_s \rightsquigarrow$ In some cases R_a is neglected, not in the efficiency calculation.




• Multiple choice:


$V_t = 11000 \angle 13^\circ \text{ V}$

$E_p = 15 \angle 46^\circ \text{ V}$

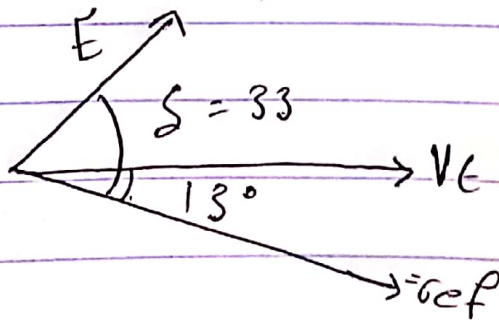is this machine a generator? motor? excited? over-excited?



CASE (c) leading PF

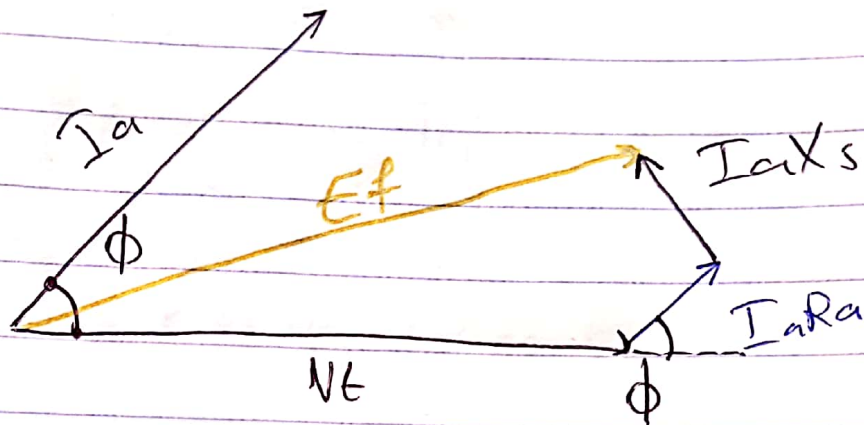

δ is positive, $E_f < V_t$, VR% is negative.

Power in Generators (δ positive $\equiv \delta > 0$)

$$\rightarrow P = 3 I_a^* \cdot \bar{V}_t$$

(conjugate)

Assume

$$\bar{V}_t = V_t \angle 0$$

$$\bar{E}_f = E_f \angle \delta$$

$$\Rightarrow \bar{I}_a = \frac{\bar{E}_f - \bar{V}_t}{Z_s \angle \theta_s} = \frac{E_f \angle \delta - V_t \angle 0}{Z_s \angle \theta_s}$$

$$= \frac{[E_f \cos \delta + j E_f \sin \delta - V_t]}{Z_s} \angle -\theta_s$$

$$\cos \theta_s - j \sin \theta_s$$

$$= \frac{[E_f \cos \delta + j E_f \sin \delta - V_t][\cos \theta_s - j \sin \theta_s]}{Z_s}$$

$$\theta_s = \begin{cases} 90^\circ, R_a \text{ neglected, } (R_a = 0) \\ 80-89, R_a \text{ considered, } (R_a \neq 0) \end{cases}$$

$$\bar{I}_a = \frac{1}{Z_s} \left[E_f \cos \delta \cos \theta_s - j E_f \cos \delta \sin \theta_s + j E_f \sin \delta \cos \theta_s \right.$$

$$\left. + E_f \sin \delta \sin \theta_s - V_t \cos \theta_s + j V_t \sin \theta_s \right]$$

$$= \frac{1}{Z_s} \left[\underbrace{E_f (\cos \delta \cos \theta_s + \sin \delta \sin \theta_s)}_{\cos(\delta - \theta_s)} - V_t \cos \theta_s \right] + \dots$$

$$\dots + j E_f \underbrace{[\sin \delta \cos \theta_s - \cos \delta \sin \theta_s]}_{\sin(\delta - \theta_s)} + j [V_t \sin \theta_s]$$

$$= \frac{1}{Z_s} \left[E_f \cos(\delta - \theta_s) - V_t \cos \theta_s \right] + j \left[E_f \sin(\delta - \theta_s) + V_t \sin \theta_s \right]$$

$$\bar{I}_a^* = \frac{1}{Z_s} \left[\underbrace{E_f \cos(\delta - \theta_s) - V_t \cos \theta_s}_{\text{Real}} - j \underbrace{[E_f \sin(\delta - \theta_s) + V_t \sin \theta_s]}_{\text{Imaginary}} \right]$$

$$S_{\text{complex power}} = \frac{3V_t}{Z_s} \left[\underbrace{E_f \cos(\delta - \theta_s) - V_t \cos \theta_s}_P - j \underbrace{[E_f \sin(\delta - \theta_s) + V_t \sin \theta_s]}_Q \right]$$

Real power including (R_a)


$$P = \frac{3V_t E_f}{Z_s} \cos(\delta - \theta_s) - \frac{3V_t^2}{Z_s} \cos \theta_s$$

approaching
 ● If $R_a \rightarrow \text{zero}$

Then $\therefore Z_s = X_s, \theta_s = 90^\circ$

$$P \Big|_{R_a=0} = \frac{3V_t E_f}{X_s} \cos(\delta - 90) - \frac{3V_t^2}{X_s} \cos 90^\circ$$

$$P \Big|_{R_a=0} = \frac{3V_t E_f}{X_s} \sin \delta$$

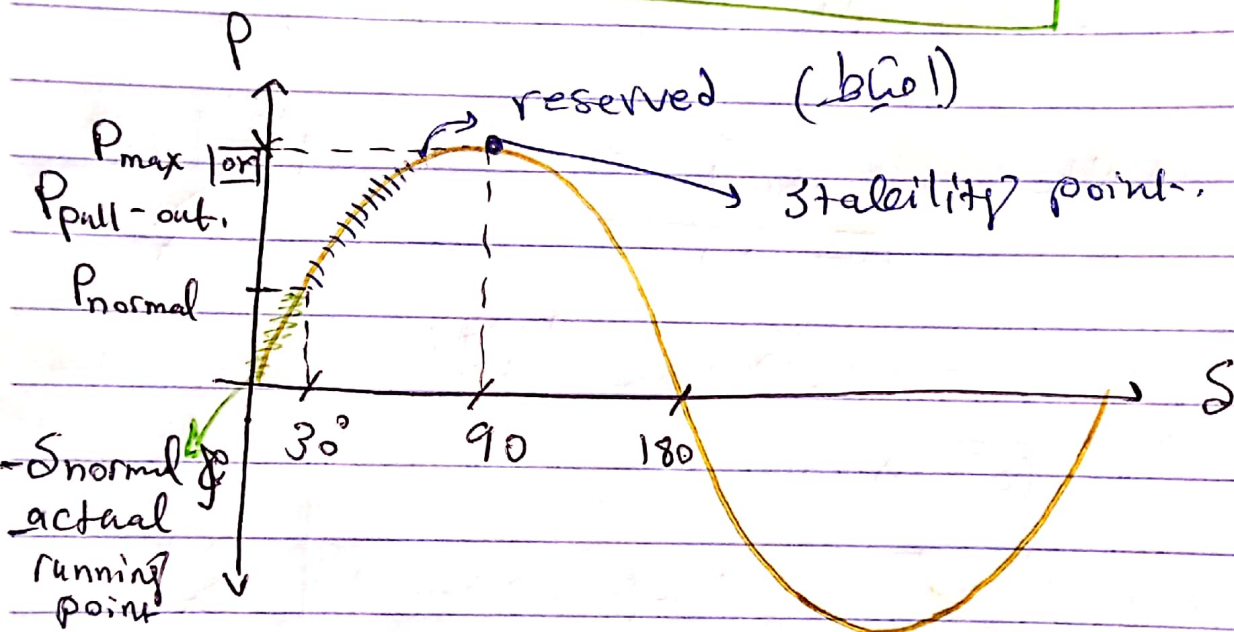


$$P \Big|_{\text{max}} \Big|_{R_a=0} = \frac{3V_t E_f}{X_s}$$

● if $R_a \neq 0$, $\delta = \theta_s$ will be $\neq 90^\circ$ for maximum power.

● Synchronous machine parameters evaluation?
 $R_a, X_a = ?!$


● SCR: Short circuit Ratio:

□ Dc test to evaluate R_a

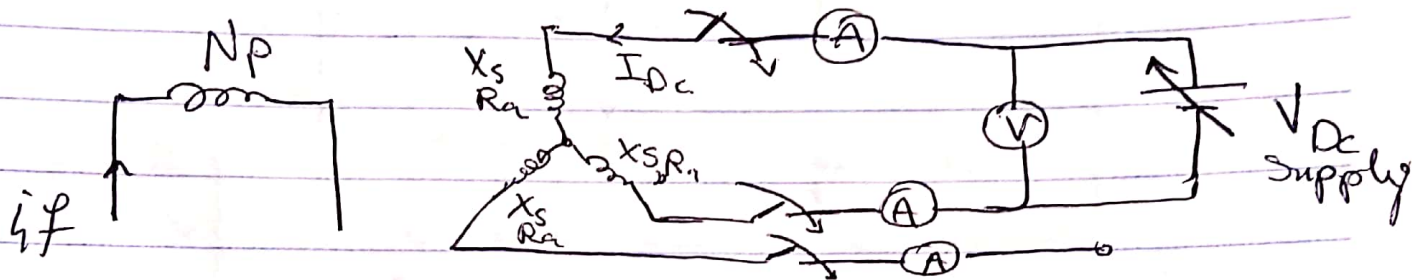

$$2R_a = \frac{V_{Dc}}{I_{Dc}} \quad | \quad Y\text{-connected}, \quad R_a = \frac{1}{2} \frac{V_{Dc}}{I_{Dc}}$$


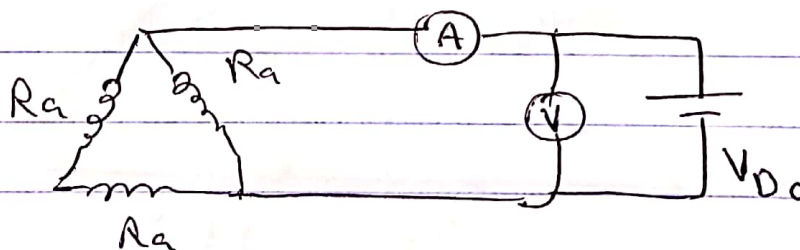
● V_{Dc} selected such that I_{Dc} is lower than that of rated value of I_a



● if Δ -connected:

$$\frac{V_{Dc}}{I_{Dc}} \quad | \quad \Delta\text{-connected} = R_a \parallel 2R_a = \frac{2R_a^2}{3R_a}$$

$$= \frac{2}{3} R_a$$

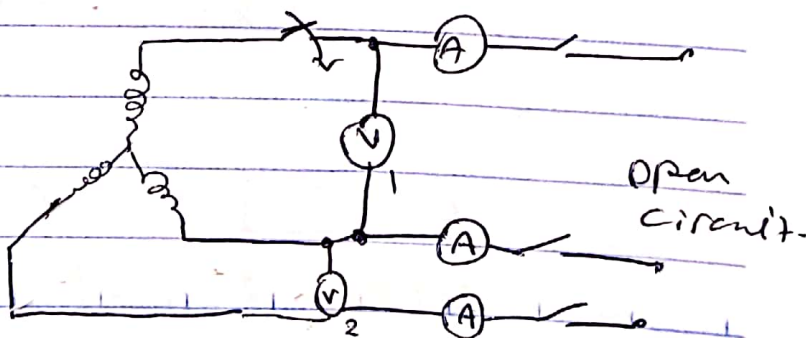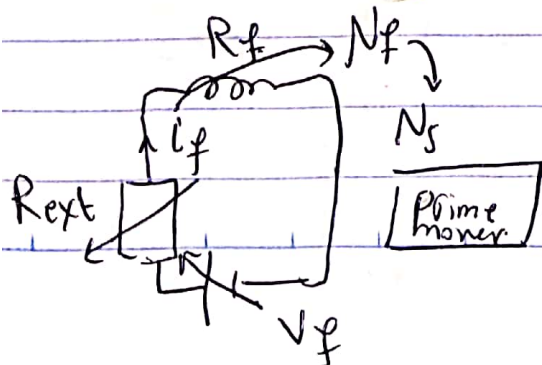

• X_s (no load - open circuit test)


- Run the motor at N_s
- Vary I_f from 0 up to $V_{oc} = 125\% V_{rated}$

SCR

res = residual

I_f	0
V_{oc}	$V_{oc, res}$	$V_{oc} = V_r$	$V_{oc} = 125\% V_r$

at $N_m = N_s = \text{constant}$

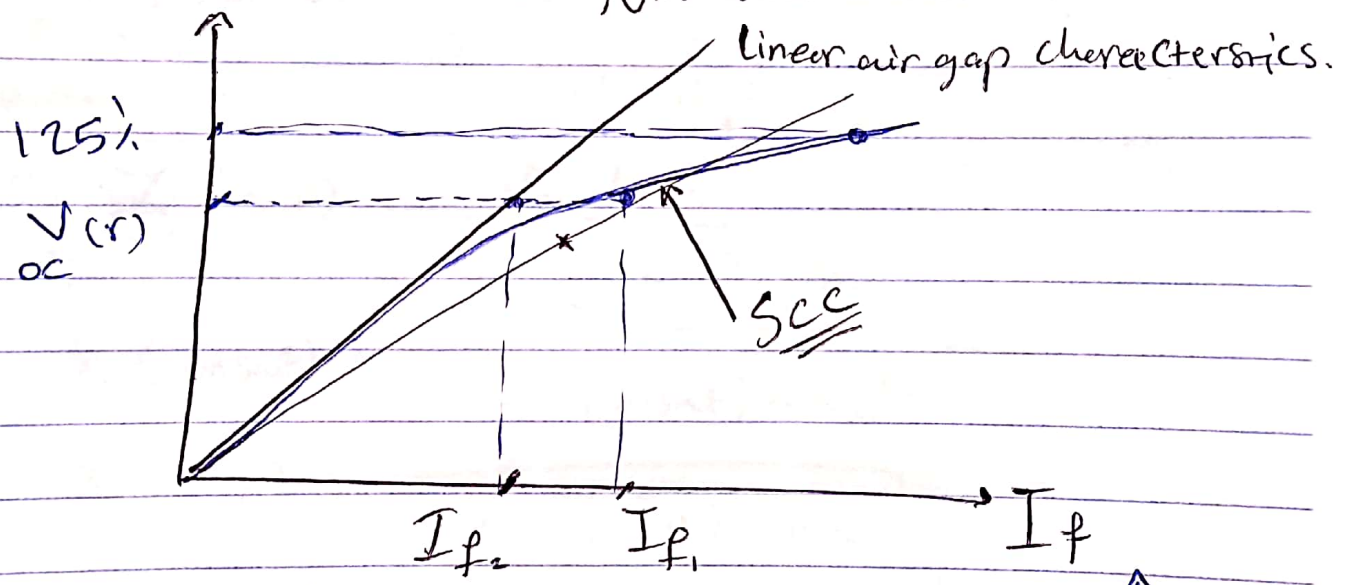

(open circuit characteristics.)


• Short circuit test: $N_m = N_s \rightarrow$ by External Model

Short with $I_f = 0$.

$I_{sc} = f(I)$ is linear.
function of f

I_f	-	+
I_{sc}	-	+	...	$I_{sc}(r)$	$125\% I_{sc}$

test can be done for this value only.

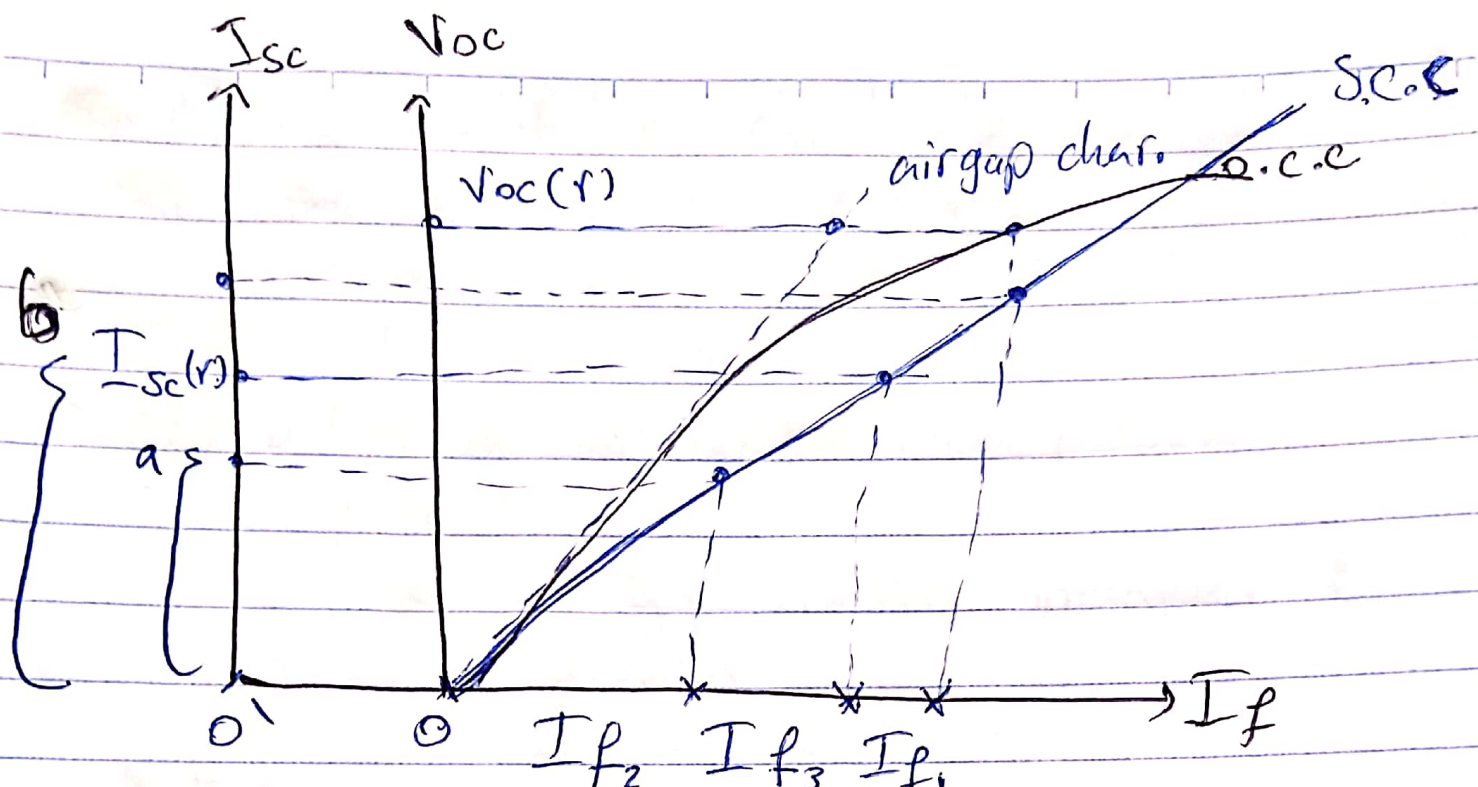

Synch. Impedance
 $Z_s(\text{unsat}) = \frac{V_{oc}/ph}{I_{sc}(\approx 0'a)/ph}$

adj. $Z_s(\text{sat}) = \frac{V_{oc}/ph}{I_{sc}(=0'b)/ph}$

$X_s(\text{unsat}) = \sqrt{Z_s^2(\text{unsat}) - R_a^2}$

$X_s(\text{sat}) = \sqrt{Z_s^2(\text{sat}) - R_a^2}$

$$SCR = \frac{I_{f1} \text{ (that gives } V_{oc}(\text{r}) \text{ at OCT)}}{I_{f3} \text{ (that gives } I_{sc} = I_a(\text{r}) \text{ from SCT)}}$$

$$= \frac{I_{f1}}{I_{f3}} \Rightarrow SCR = \frac{1}{X_s(\text{SAT}) pu}$$

rated
open ckt
test
Short ckt
test.

Behaviour of Synchronous Generator

(a) when working alone (isolated from network)

→ ~~V_t~~ ?? f ??


(b) when working parallel with infinite busbar or network.


→ V_t & f are fixed irrespective of load variations.

When working alone

* An increase in the real power in the generator leads to reduction in speed \rightarrow reduction in frequency is expected & to overcome this (increase PM speed to keep f constant)

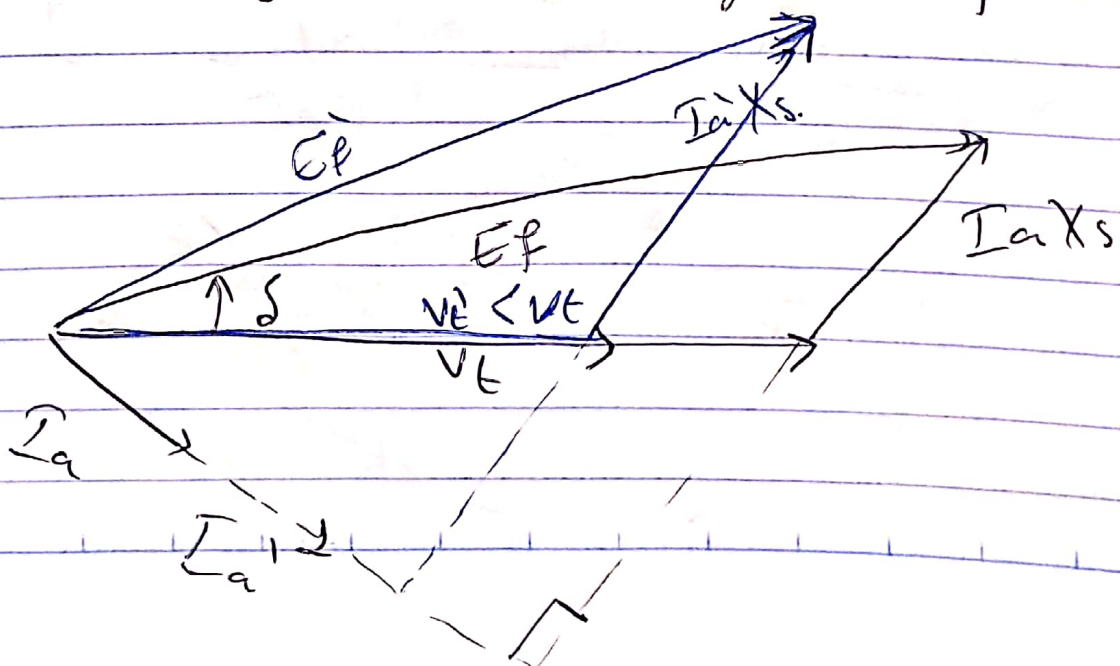* change in load power leads to change in the Arm current & terminal voltage if $I_f = \text{constant}$



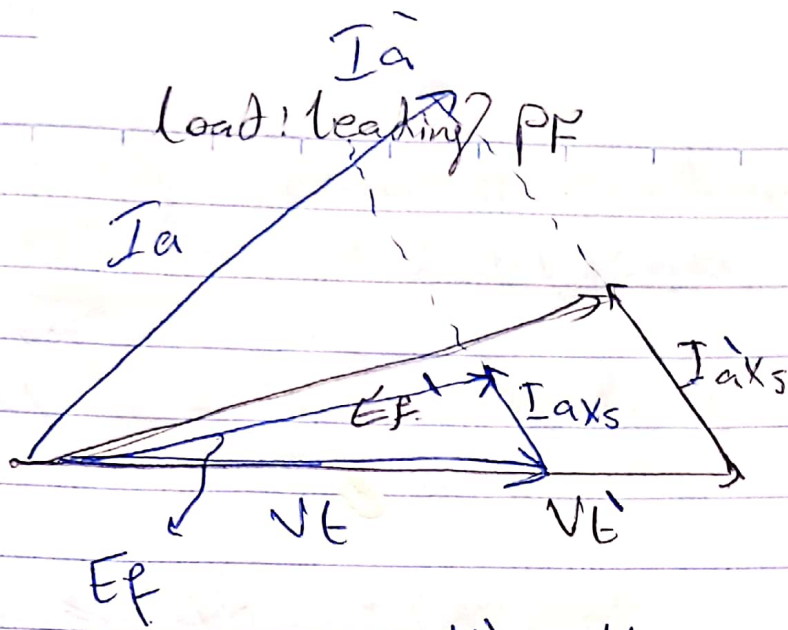


Generator working in parallel with infinite busbar/or running at constant real power (V & f are fixed)

$$P = \frac{3 V_t E_f}{X_s} \sin \delta = \text{constant} \times E_f \sin \delta$$

$$\therefore E_f \sin \delta = \text{constant}$$

$$P = 3 V_t I_a \cos \phi = \text{constant} I_a \cos \phi$$

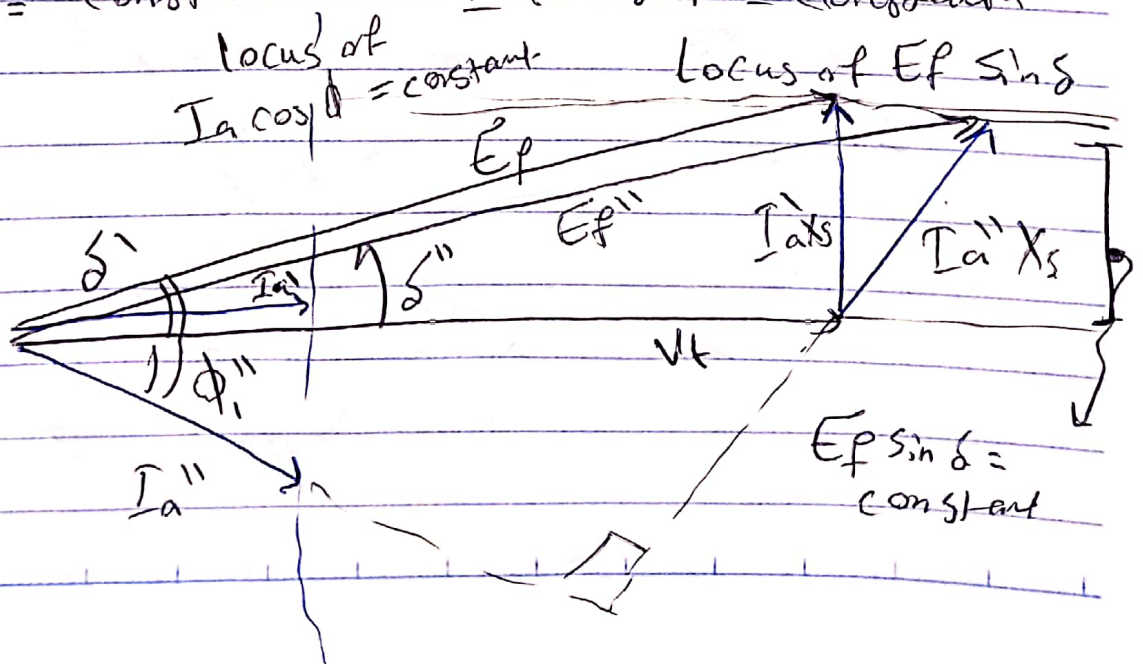
$$P = \text{constant} \rightarrow I_a \cos \phi = \text{constant}$$



Synchronous Generator Running at Constant Real Power

• $R_a \ll X_s \rightarrow R_a$ can be neglected for simplicity.

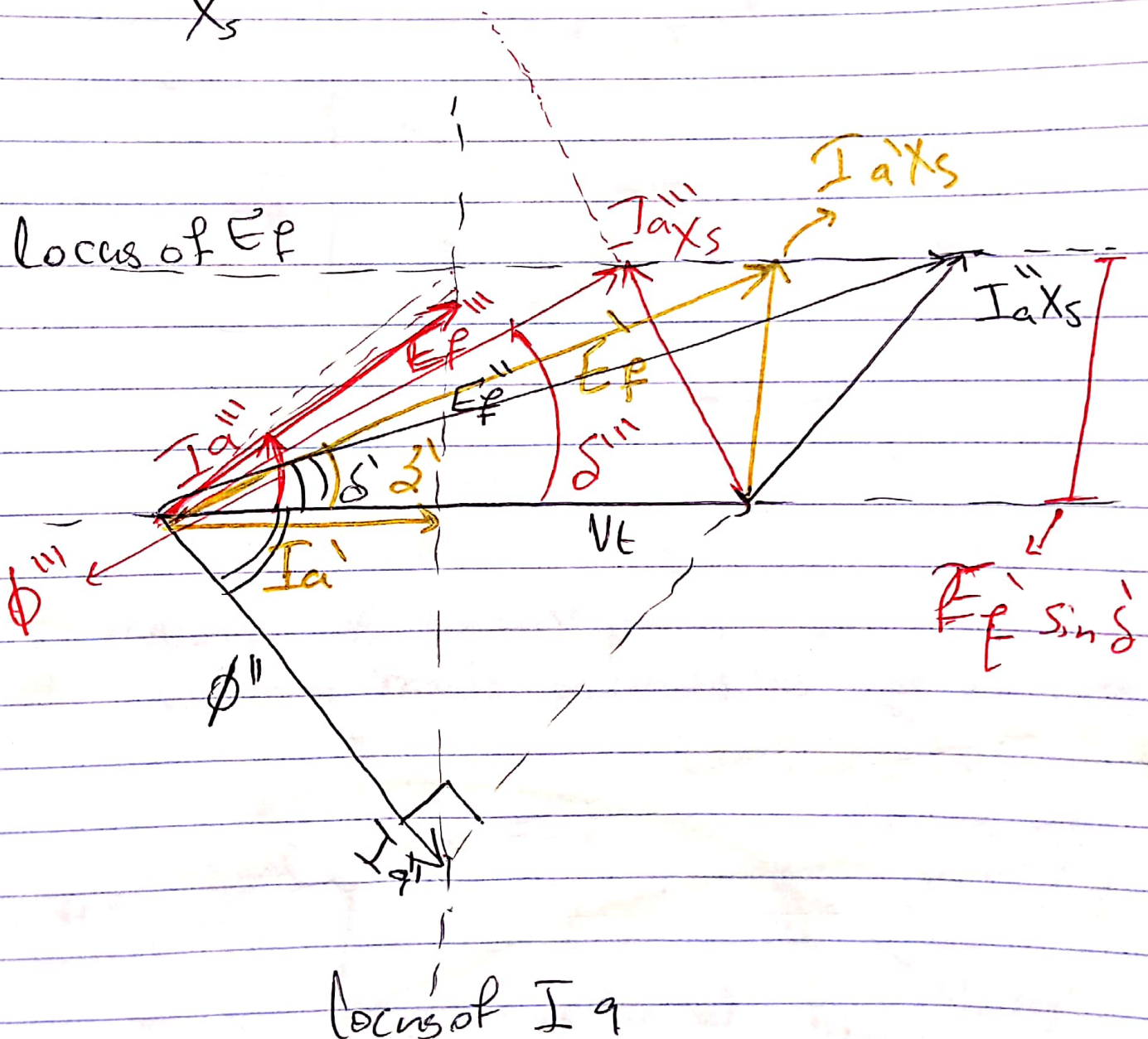
•
$$P = \frac{3VE_f \sin \delta}{X_s} = \text{constant.}$$



$$P = 3Vt \times I_a \cos\phi = \text{constant}$$


$$= I_a \cos\phi = \text{constant}$$


Maximum power generation

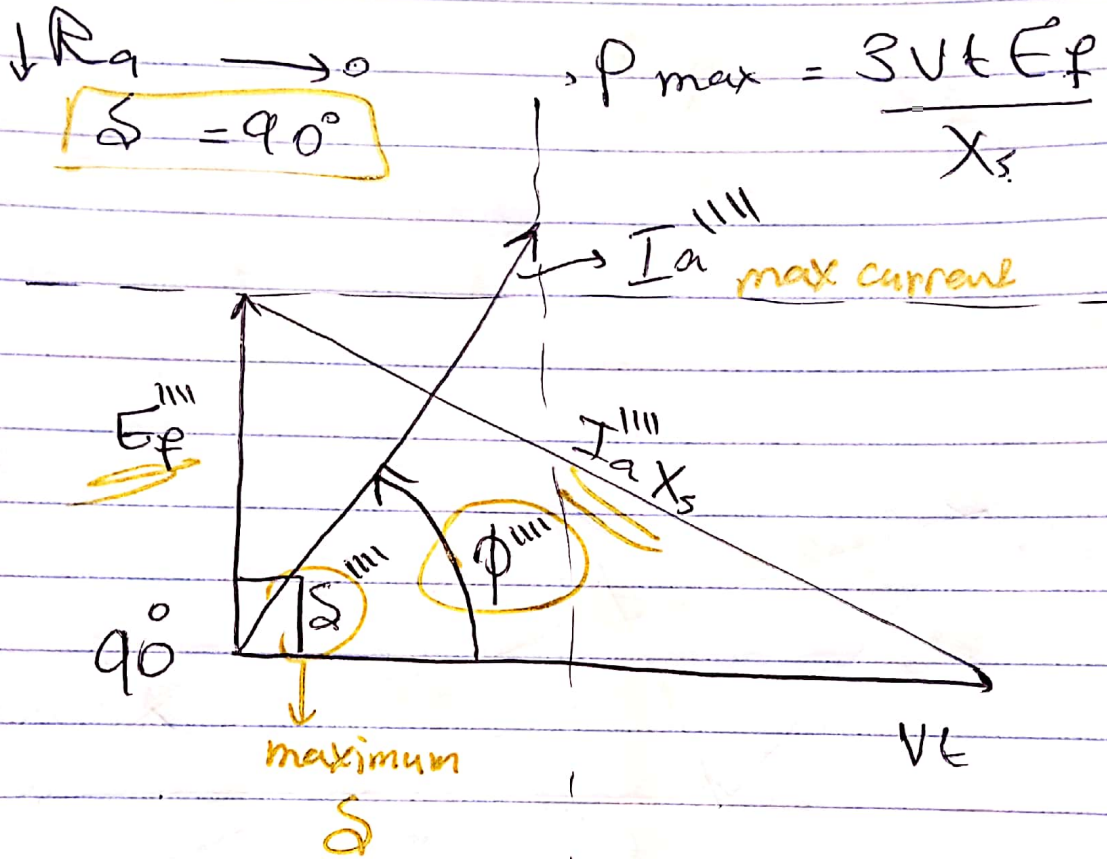

maximum at leading power factor.

Voltage regulation could be +ve or -ve

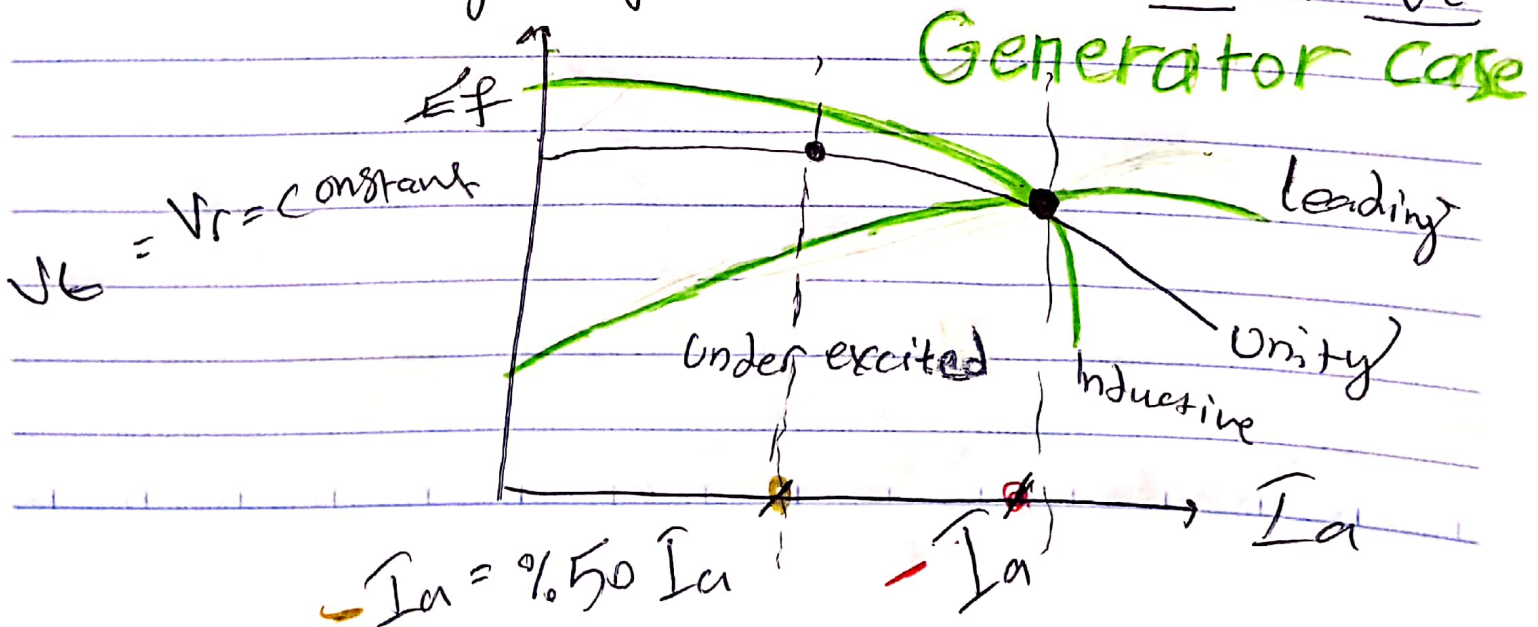

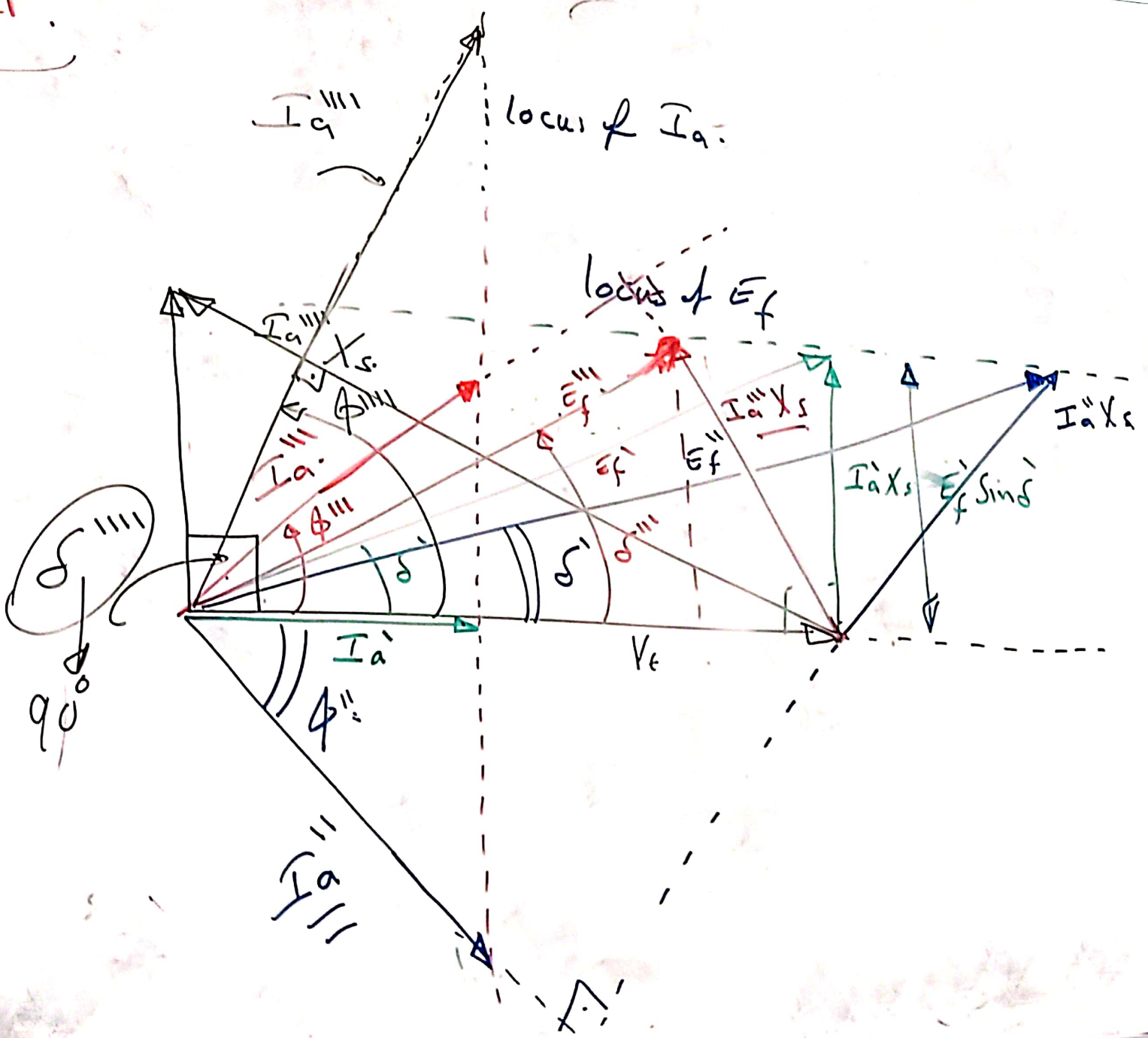

Synchronous Generator running at constant E_f


● $\bar{V}_t = \bar{E}_f - j\bar{I}_a X_s$, $\bar{I}_a = \frac{\bar{E}_f - \bar{V}_t}{jX_s}$

$\rightarrow \bar{I}_a = -j \frac{\bar{E}_f}{X_s} + j \frac{\bar{V}_t}{X_s}$

Constant


Leading V_t

90°
درجه

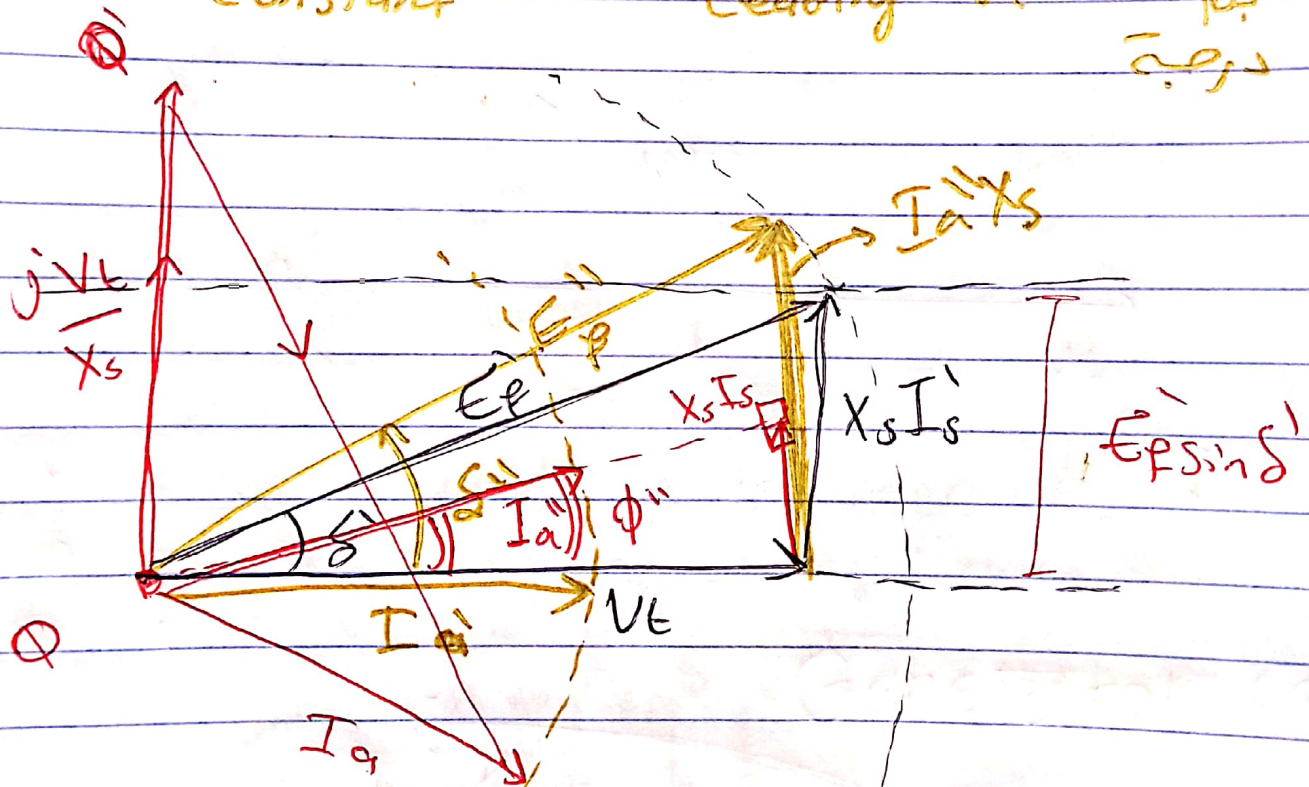


Locus of I_a

locus of $E_f = \text{constant}$

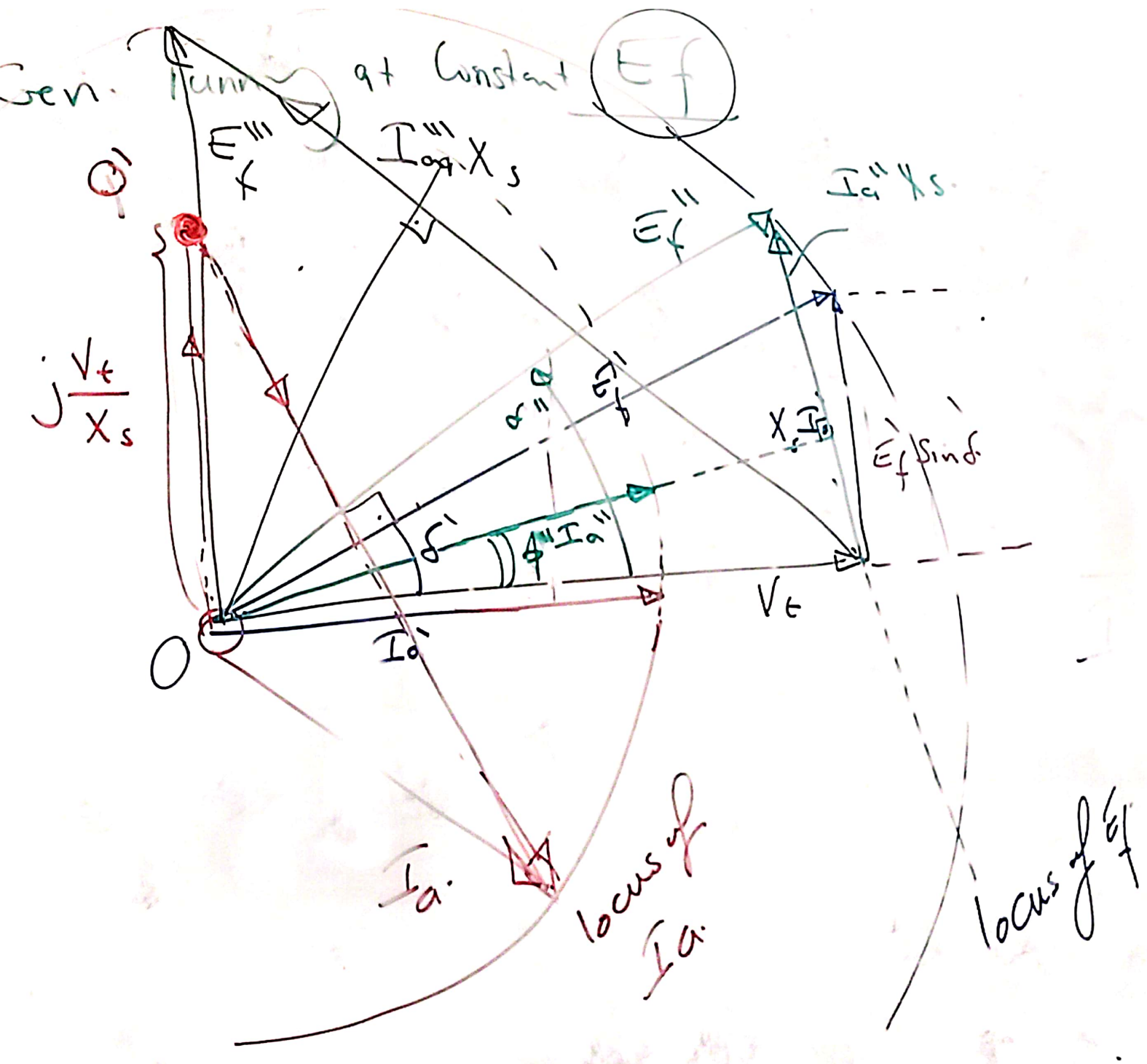


for maximum

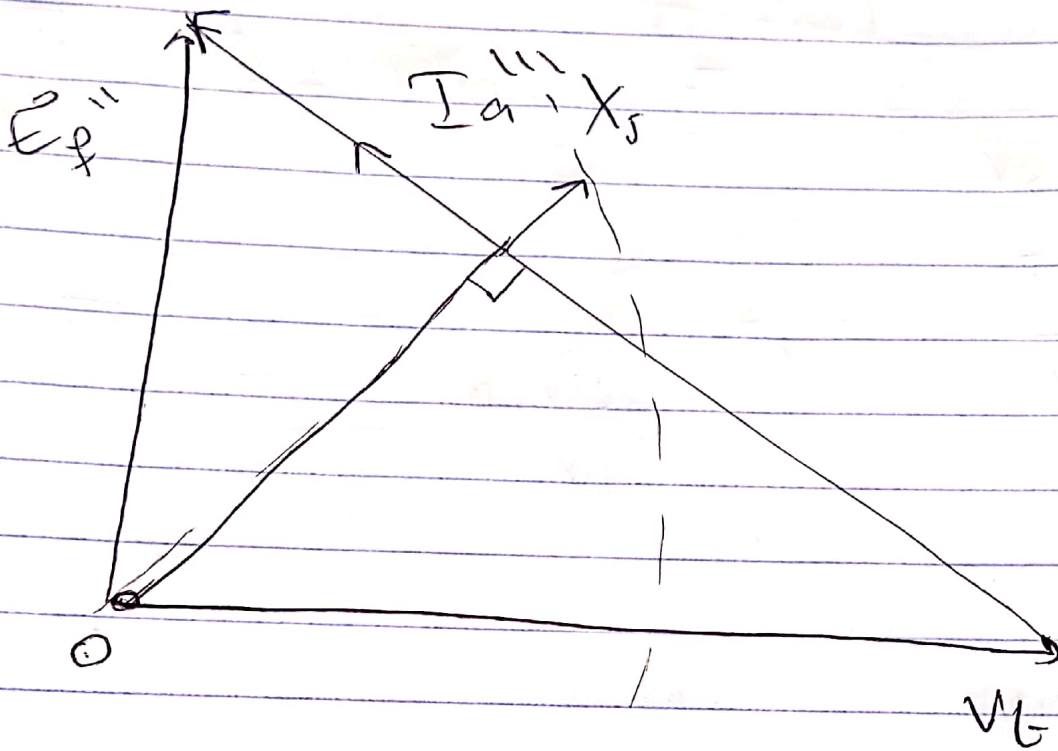

Locus of I_a

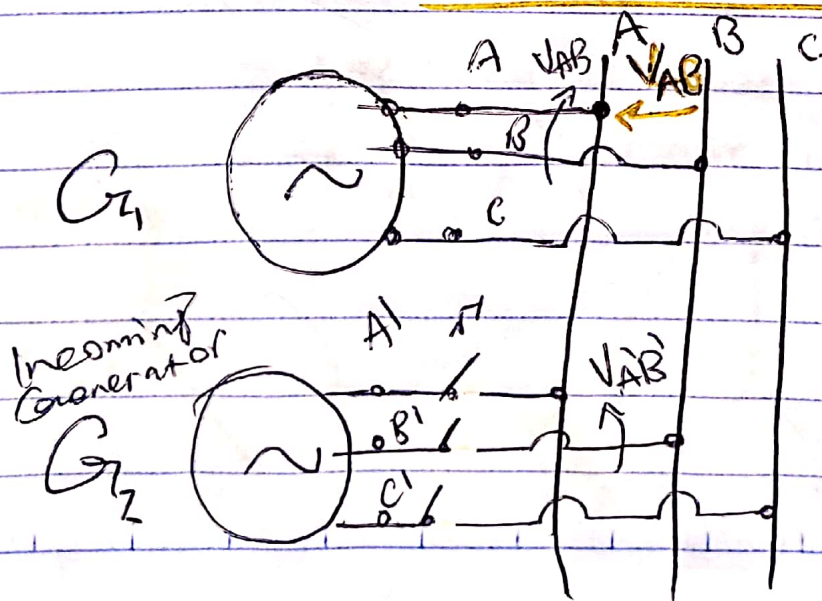Parallel operation of Synchronous Generator



while S^w Switch is open

① $V_{A'B'} = E_f = V_{AB}$

No load i_D

$I = \text{Zero}$

② Control the speed such that

$$f_{in} = f_{actual}$$

incoming generator actual


Frequency of the incoming generator is equal = Network frequency

③ phase sequence of incoming generator is same as the network


④ - V_{AB} and $V_{A'B'}$ when closing the switch should be in phase.

- V_{BC} in phase with $V_{B'C'}$


- V_{CA} in phase with $V_{C'A'}$

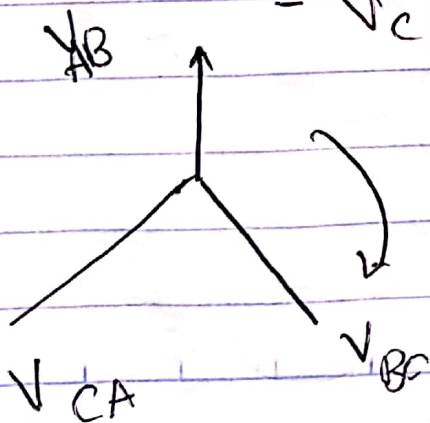


Positive Sequence

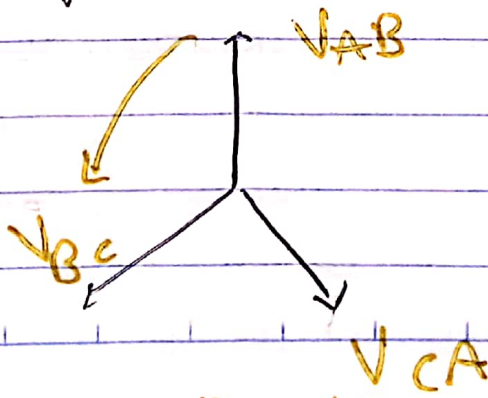

Negative Sequence

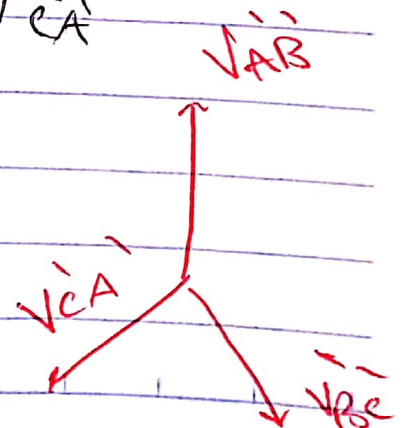



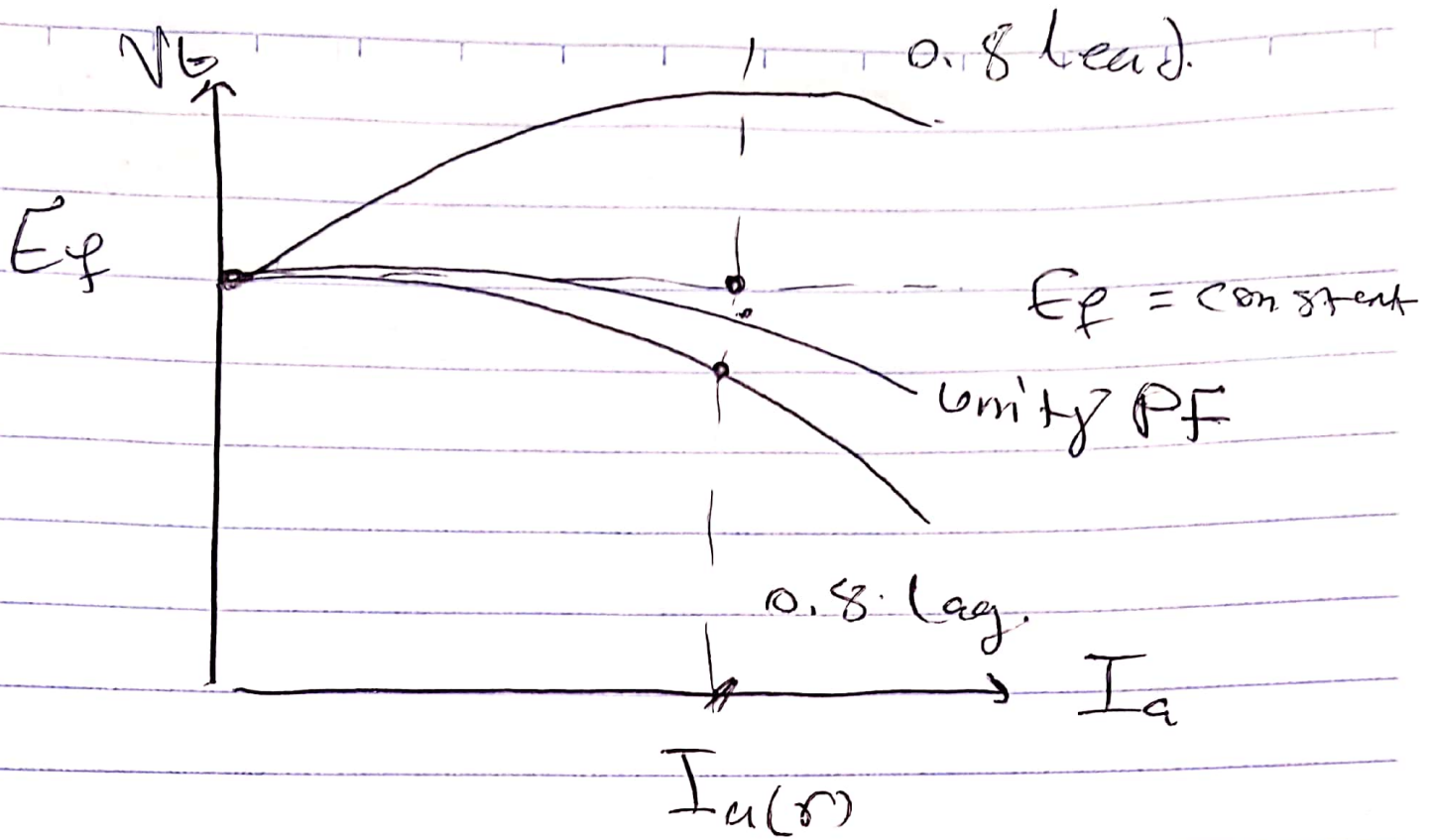


- why? parallel connection
 - more reliable systems
 - Easier Maintenance
 - Economic power distribution
 - national security.

- Conditions
 - Equal Frequency
 - Equal voltage
 - Same phase sequence
 - to be connected when line voltages are in phase.





○ Two methods to check if line voltages are in phase

I 3- extinction lamps.

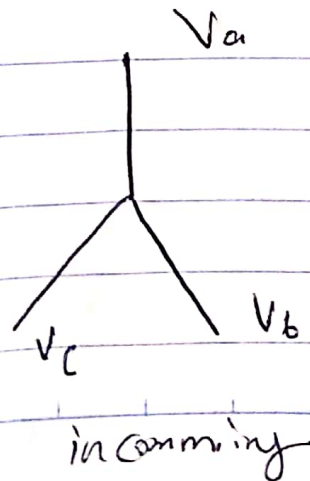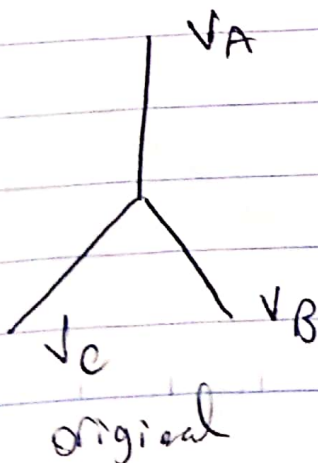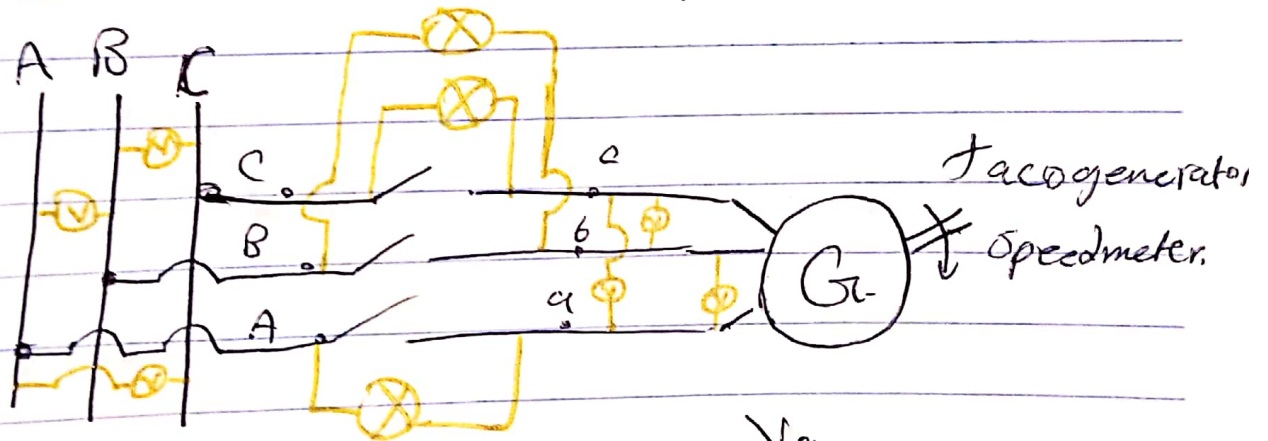

* دراسة الحالة الثانية مع مبرج الفولتية

[2] One-dark two-full bright.

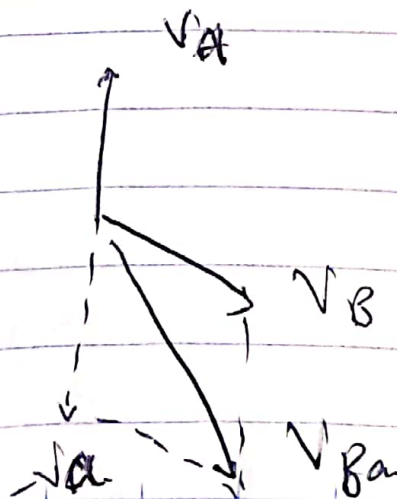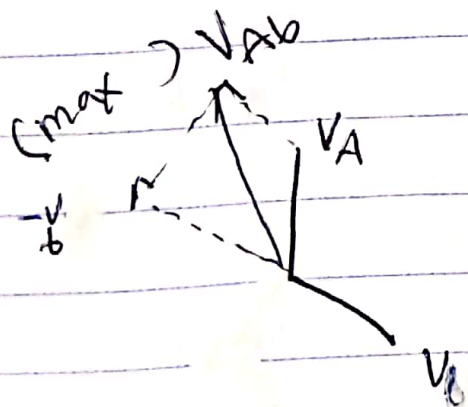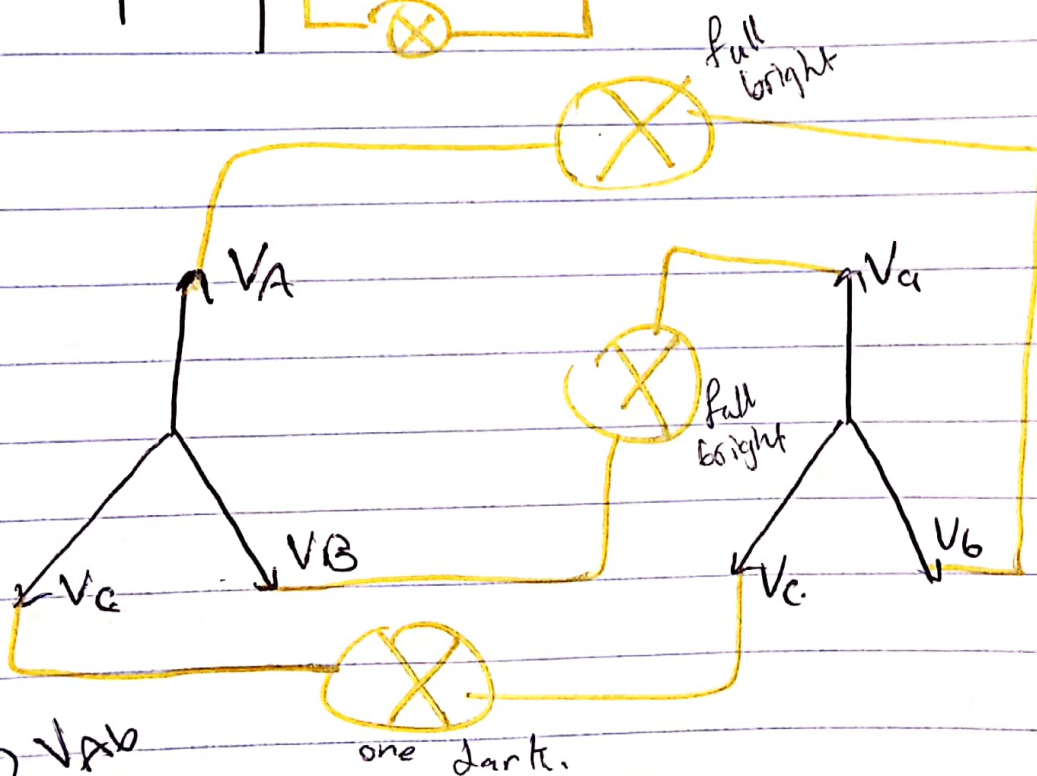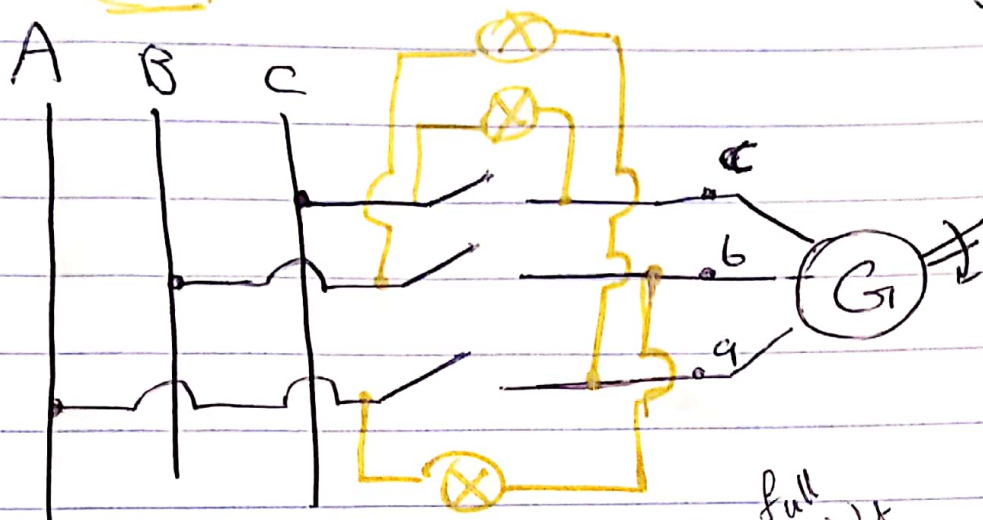


● After connection, what happens?

(A) power/frequency relationship


(B) reactive power / voltage relationship

(A)

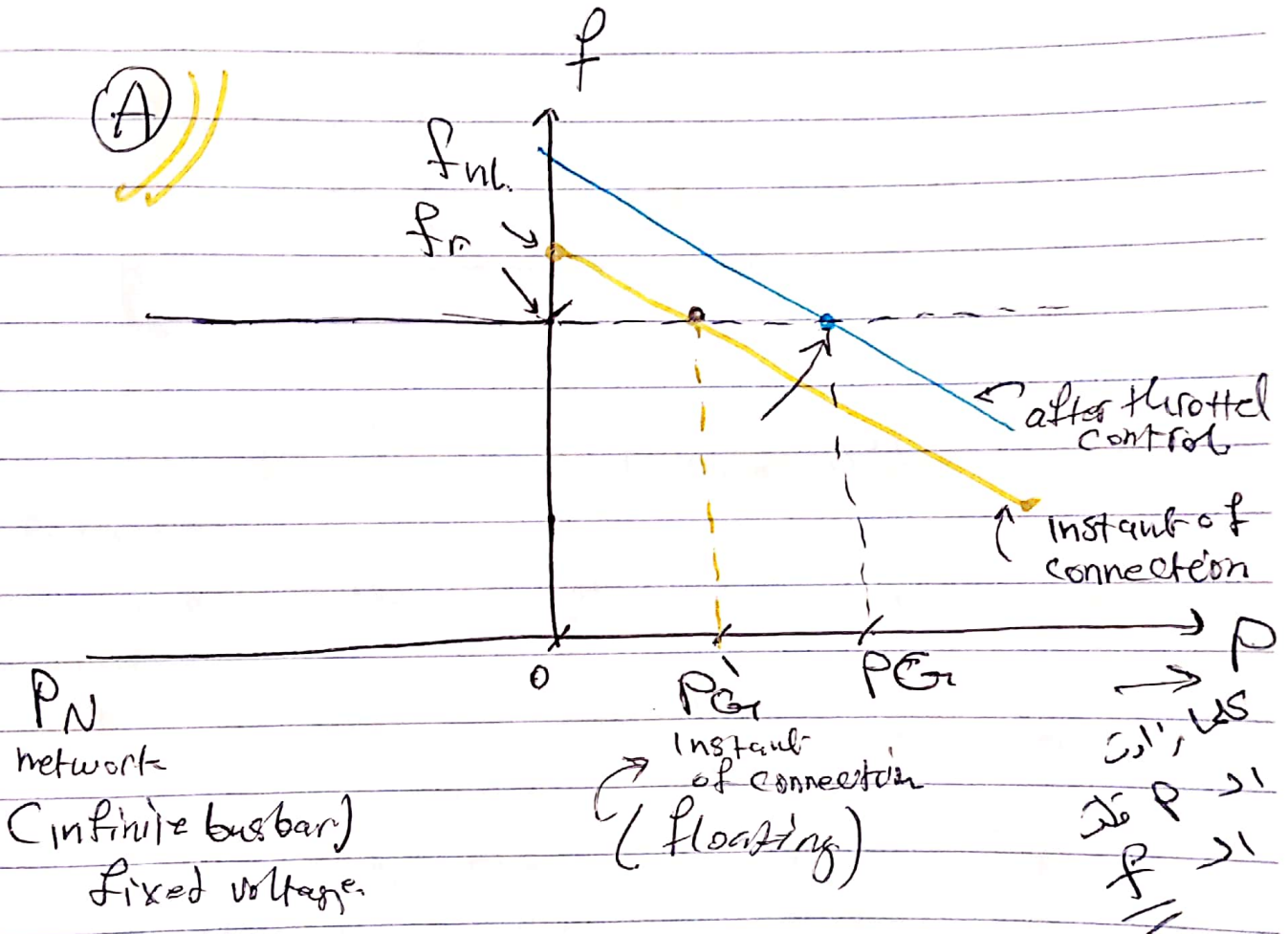

شبكة ثابتة الجهد : Fixed voltage network (A)
 → Voltage
 → Frequency

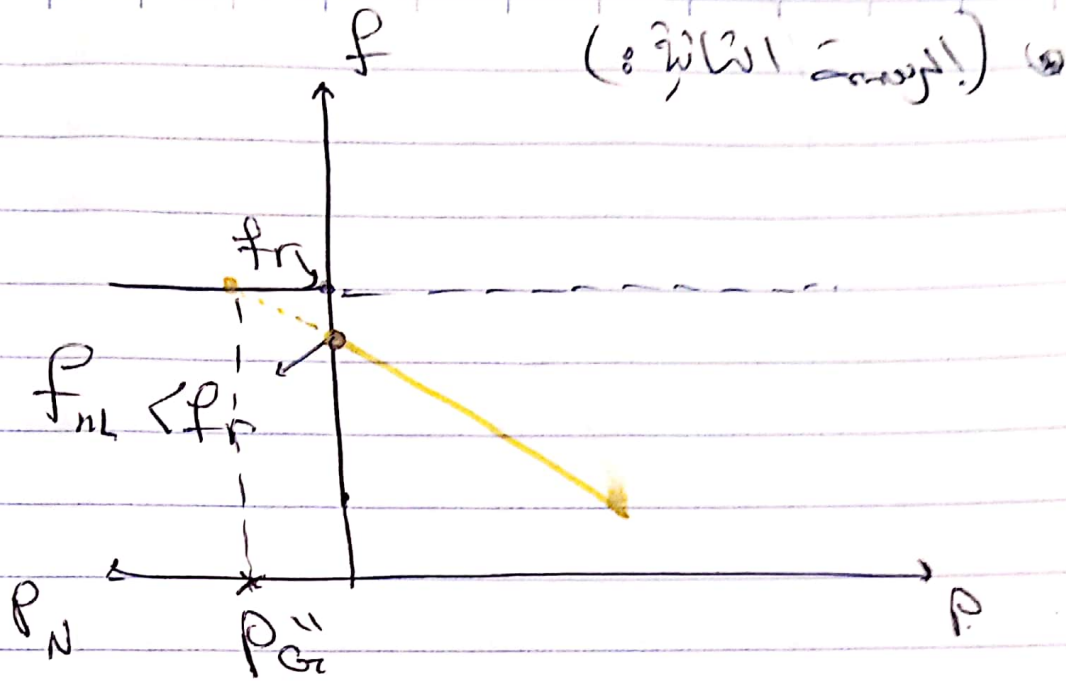Generator's frequency is fixed. (المولدات متصلة بالشبكة) $f_{network}$ is constant. Power is constant. Using throttle control.



في حالتي $f_m < f_n$ Generator لا يستطيع العمل في الشبكة

في حالتي power لا يتجاوز curve في

في حالتي $f_m < f_n$ Generator لا يستطيع العمل في Motor (load)

Incoming machine works as motor.

→ There's a certain protection against Reverse power flow. It will disconnect the incoming machine.


- connection of incoming generator to infinite busbar
- Two characteristics of interest:

① $f = f(P)$

② $V_t = f(Q)$

to describe these two characteristics:

Howsing? diagram

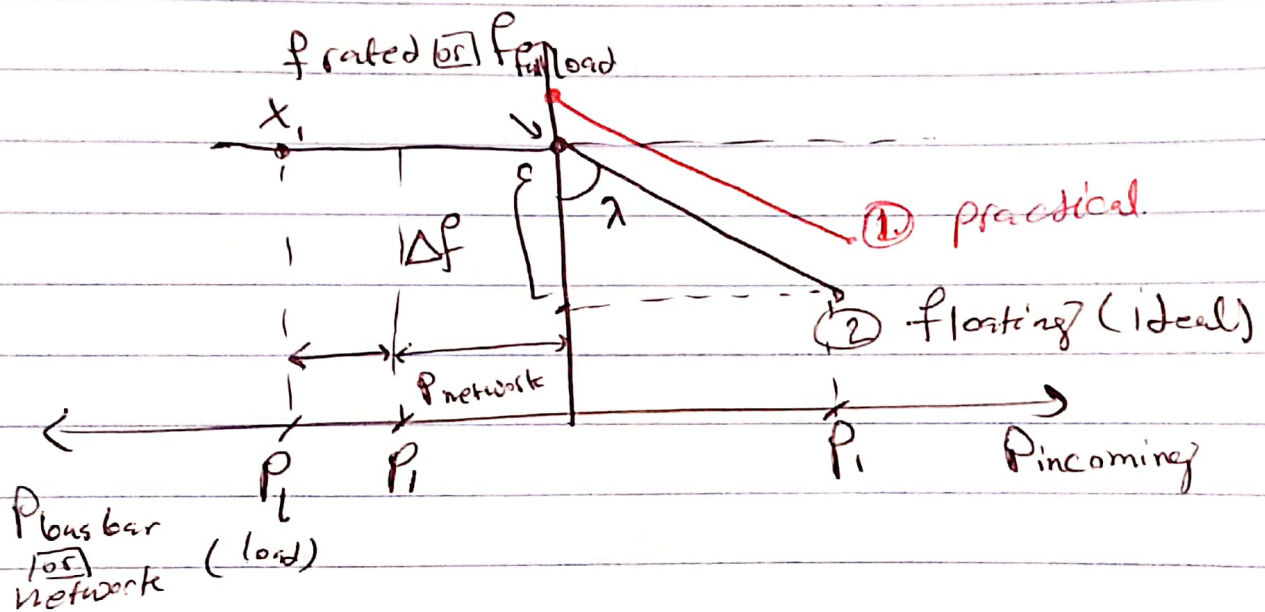

- slope of the curve = $\frac{P}{\Delta f}$

- speed drop = $\frac{f_{NL} - f_L}{f_{NL}} = \frac{N_m(nL) - N_m(L)}{N_m(L)}$
not drop!!

- If ideal floating; No power exchange occurs.

Practically: \pm N_{nL} is slightly greater than N_{rated}
 $N_{nL} > N_r$

So once it's connected, it will provide power to the network.

- P_r is provided by the incoming generator

- Load power is shared


2 If $N_{NL} < N_r$ the machine will draw power from network and work as a motor.

- Power in the reversed direction is not allowed, therefore; a protection action will disconnect the machine.


- if CASE (1) :- Generator

Load sharing can be modified by increasing the Prime mover governor set point, (PM)

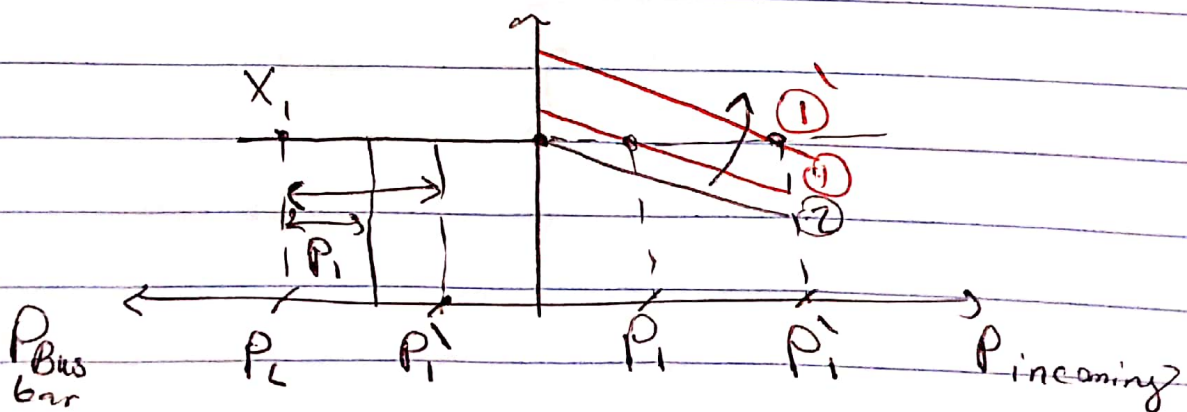→ PM is increased → no load speed is increased and the curves



$$V_t = f(Q)$$

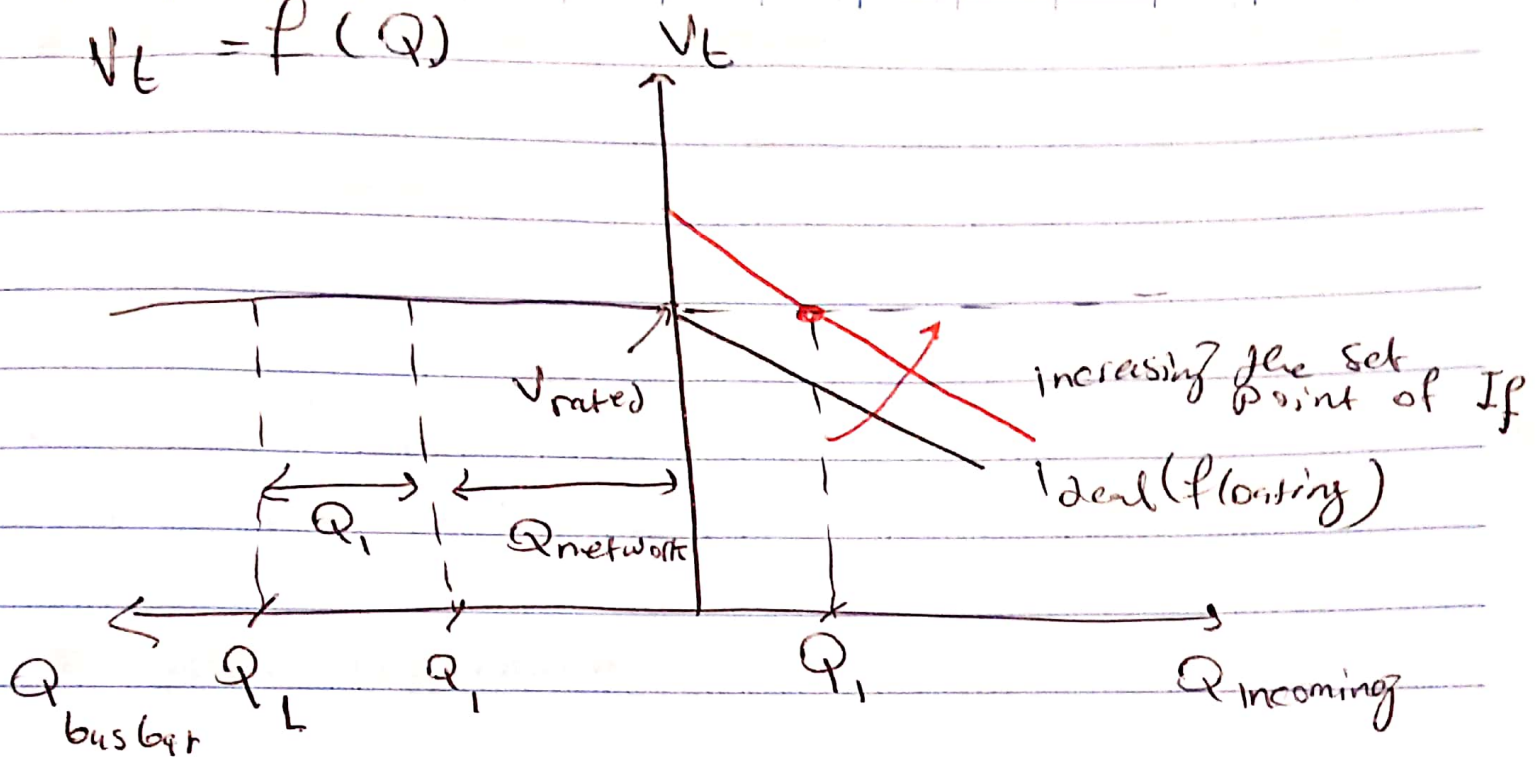


• Usually : $Q_{network} > Q_1$

• by controlling I_f , Q & PF , V_t is controlled for the incoming generator.


$$\bar{V}_t = \bar{E}_f + I \bar{Z}$$

Connection of incoming generator to another generator.

Next page

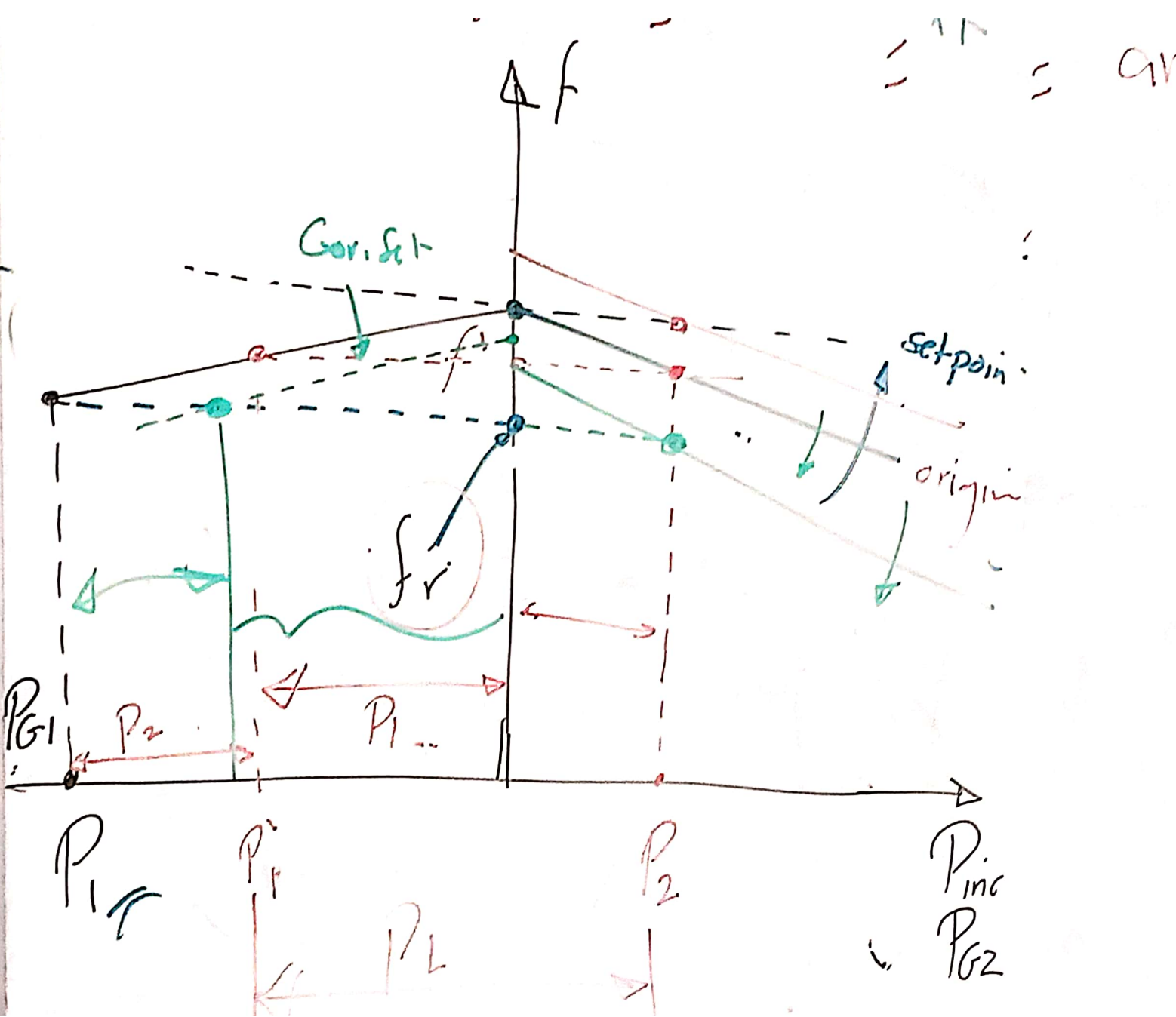

WATER COLUMN

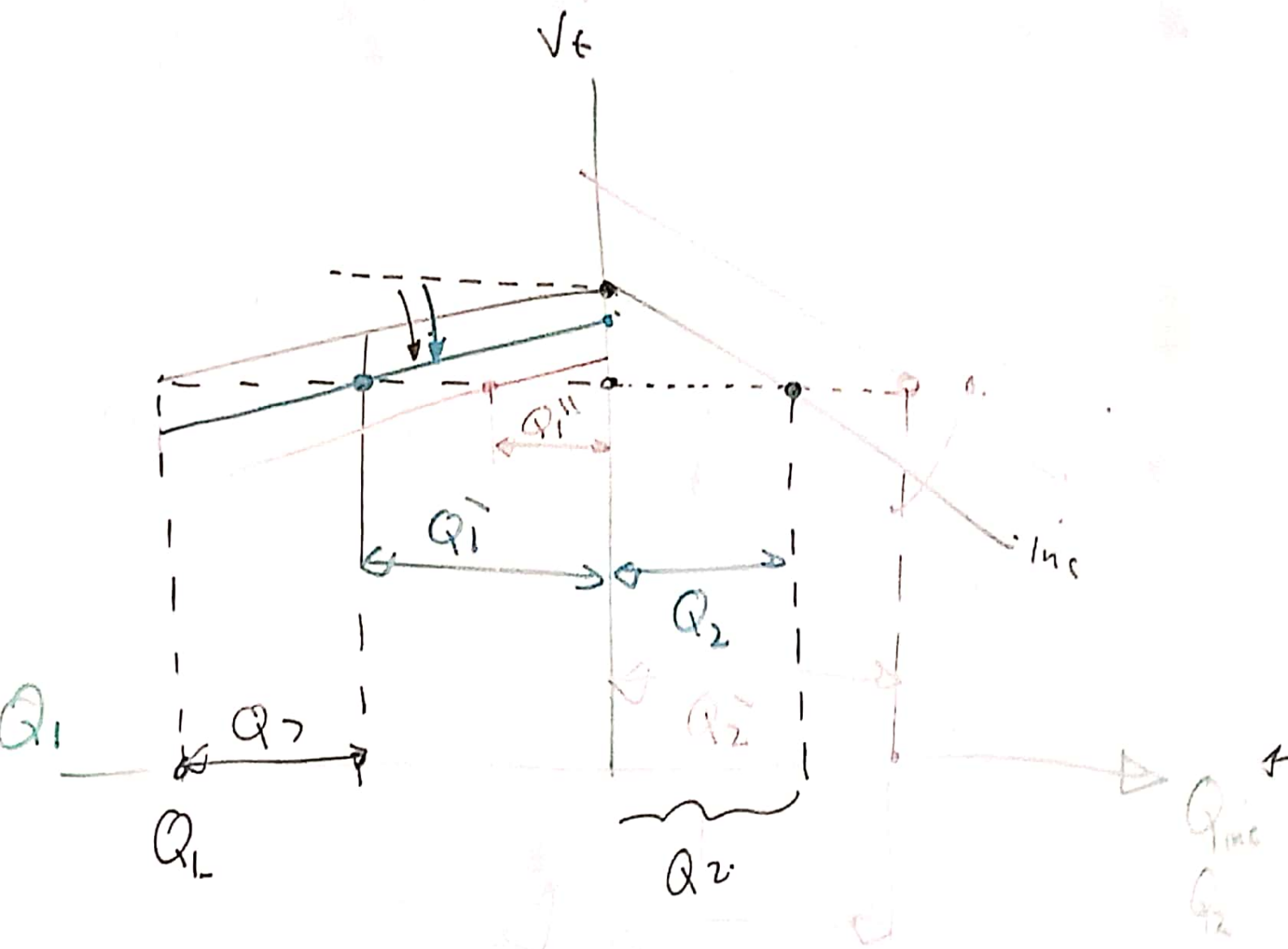


• When (3) incoming is connected, f , ϕ & V are changed and to keep them fixed at rated values, both generator set points should be controlled.

Synchronous Motor

• Special case: (rarely used), if the rotating (1) speed regulation = zero, then it is USED.

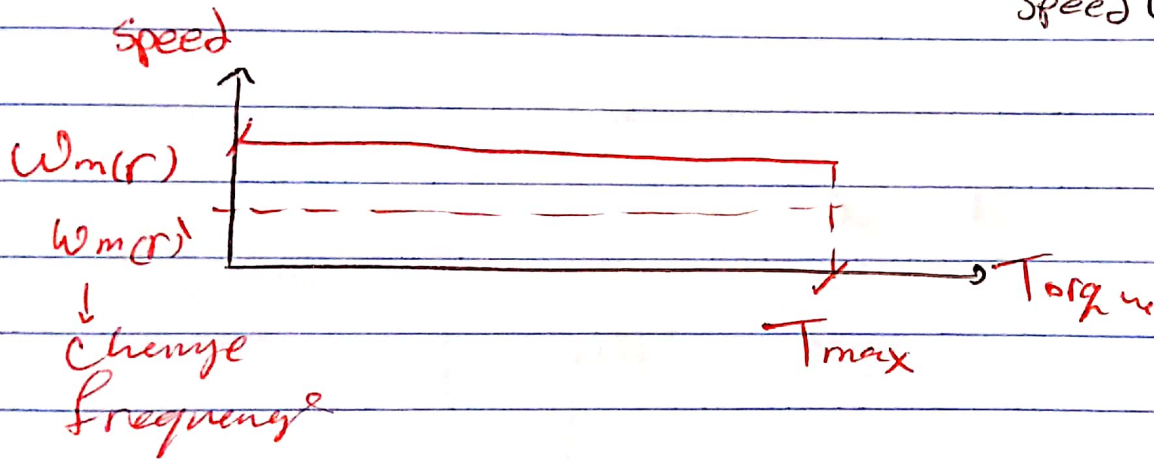• speed regulation = $\frac{\text{Speed}(nL) - \text{Speed}(L)}{\text{Speed}(L)} = 0$




• (2) USED in applications where a leading PF is required or VAR compensation is required

Three Solutions to Lagging PF


- (1) capacitor bank in parallel
- (2) Synchronous motor
- (3) power electronics

(2)

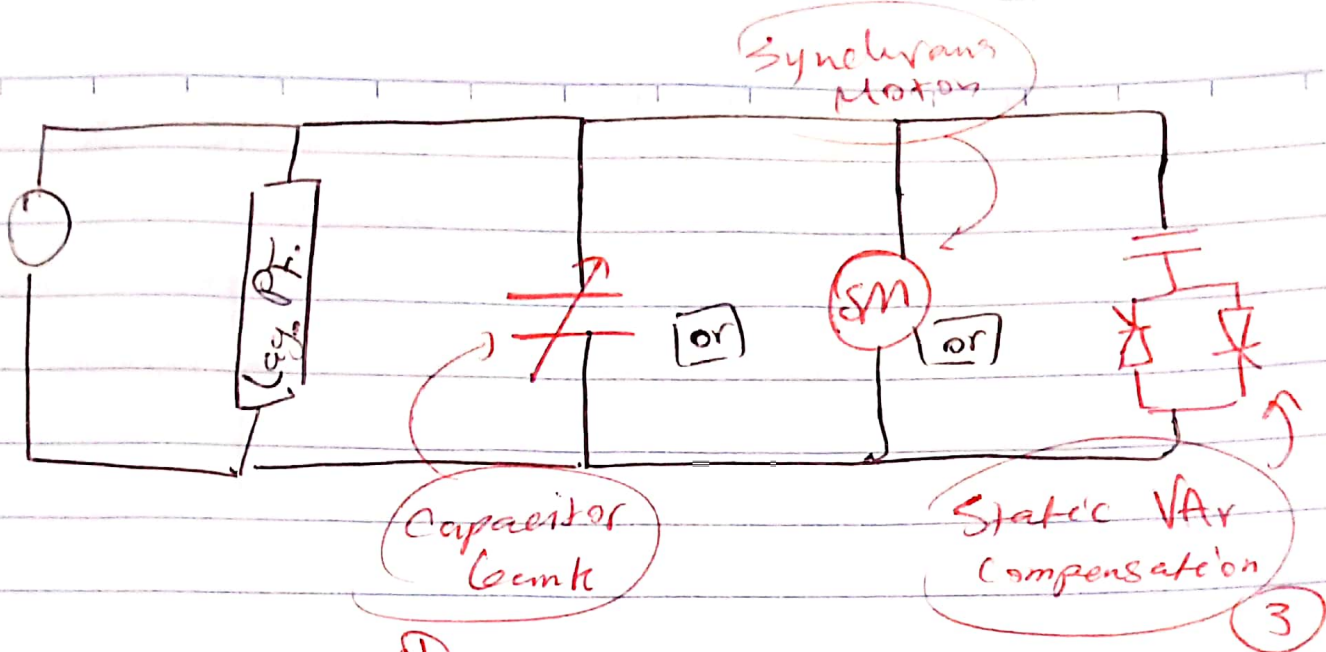

Equivalent Circuit

Same as the synchronous generator.

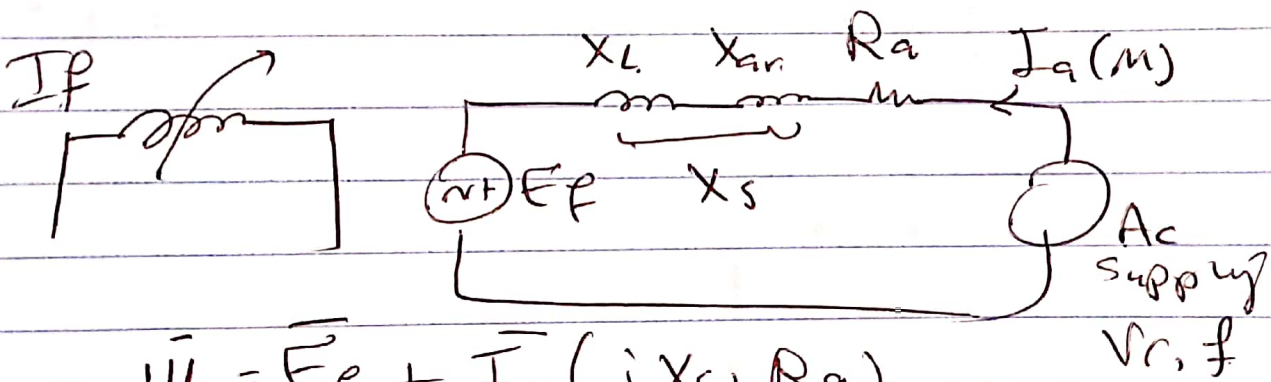


$\bullet \bar{V}_t = \bar{E}_f + \bar{I}_a (jX_s + R_a)$

$\bar{V}_t = \bar{E}_f + \bar{I}_a Z_s \angle \theta_s$

Unity? power factor

δ is always negative

$V_t > E_f$ normal Excitation.

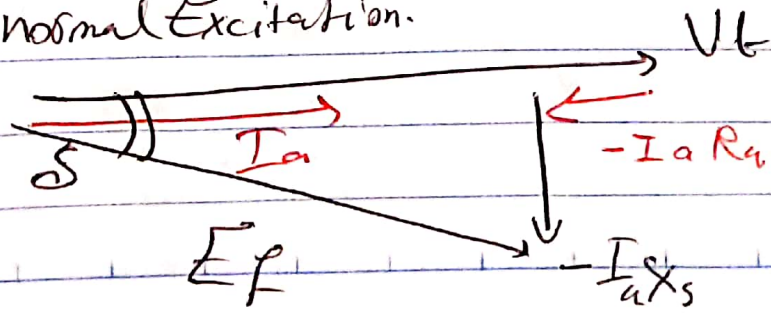


To work in a lagging PF \rightarrow run at under excited condition.

Leading PF

- δ is also negative.

$E_f > V_t$
over excited.

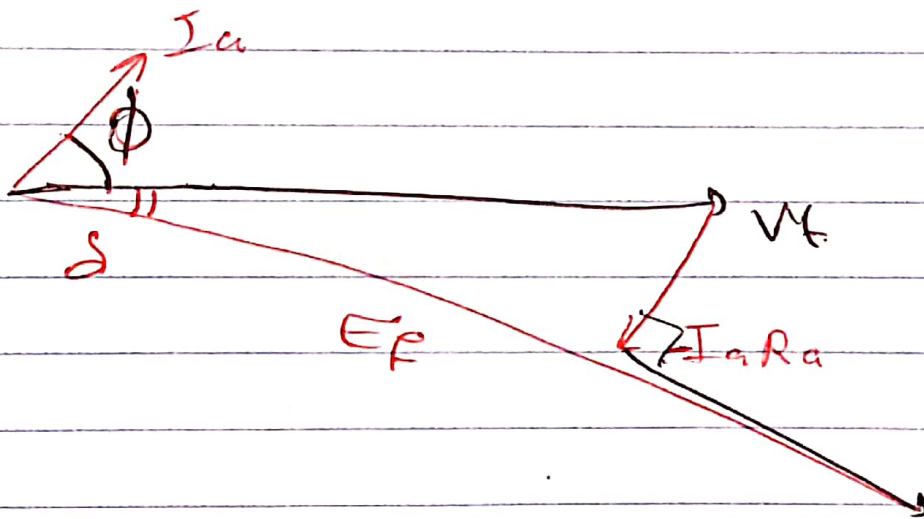So for leading power factor, over-excite the machine.



The U-curve / V-curve of the synchronous motor.

$$\vec{I}_a = \frac{\vec{V}_t - \vec{E}_f}{Z_s}$$


$$P = 3 V_t I_a \cos \phi$$

V-Curve (U-Curve) of Synchron Motor



given for constant

I_a
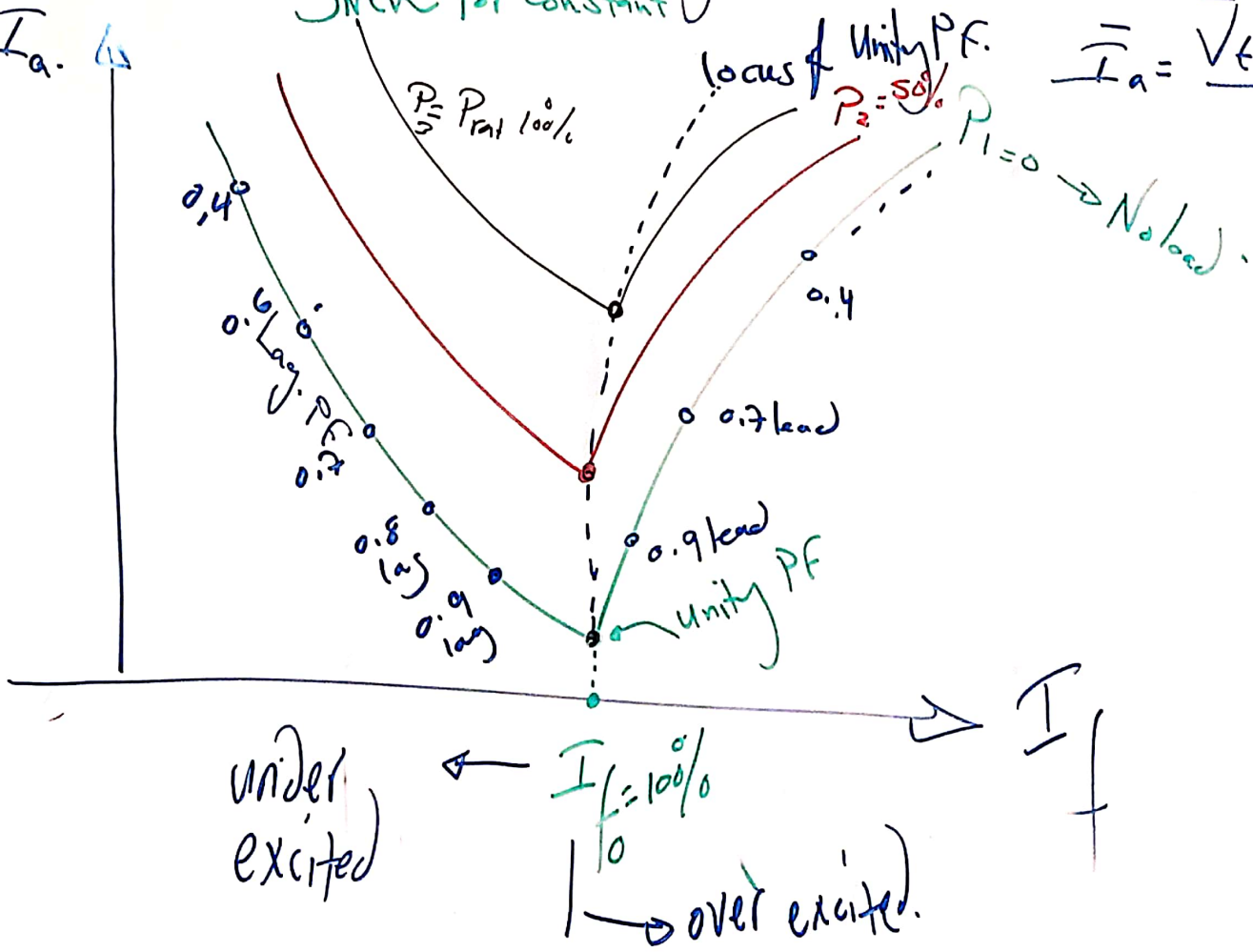
$$\bar{I}_a = \frac{\sqrt{V_t^2 - E_f^2}}{Z_s}$$



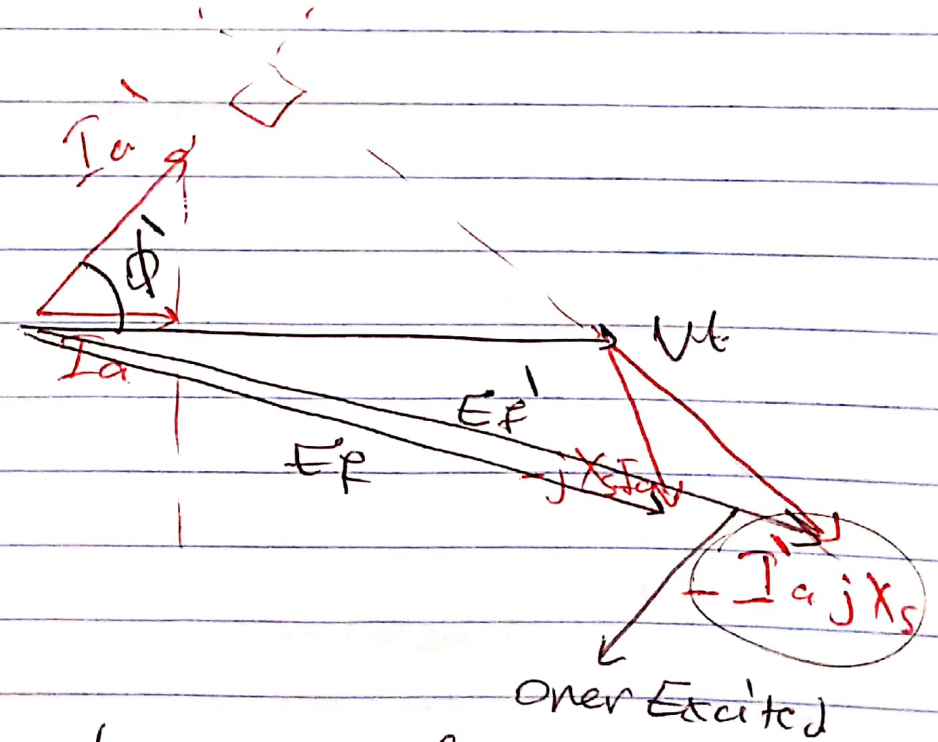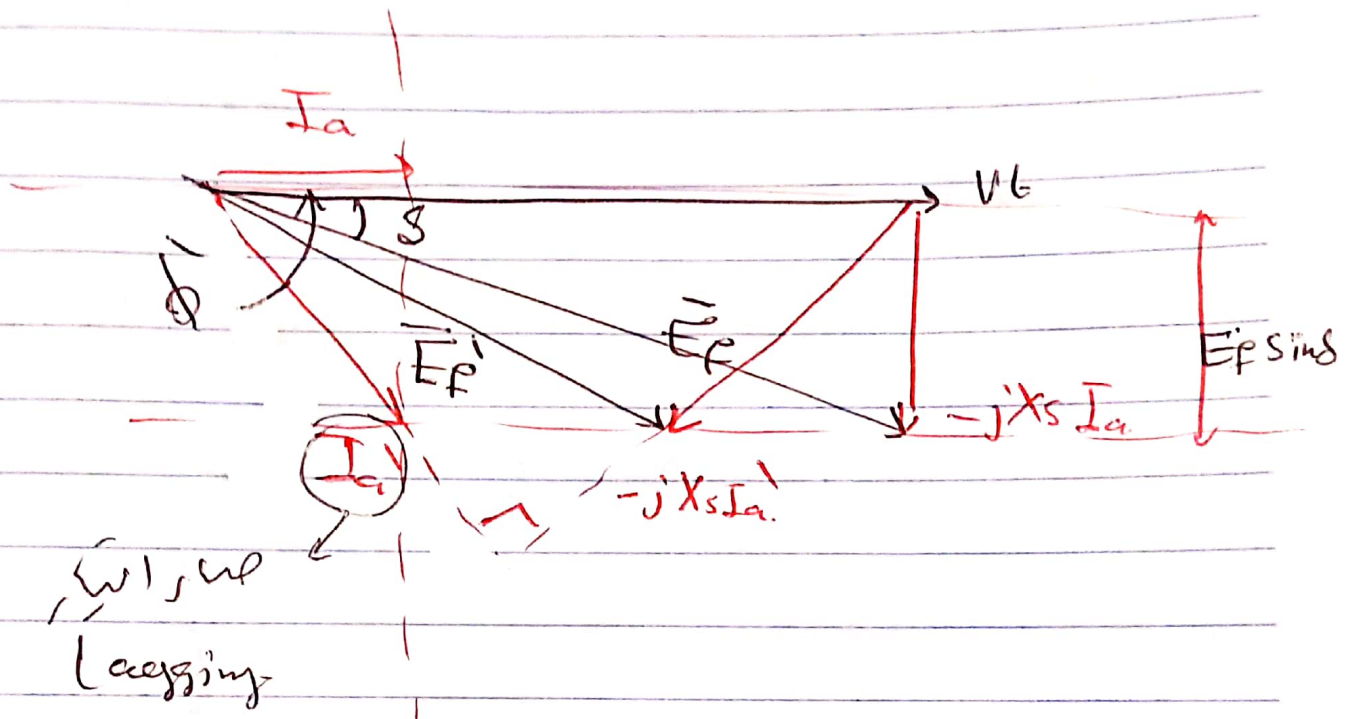Locality of I_a @ $\beta \equiv \text{constant}$.



@ $I_a \cos \phi = \text{constant}$

$E_f \sin \delta = \text{constant}$

constant power.

CASE (2) : Motor case

R_a is not neglected.

$$\bullet \bar{I}_a = \frac{\sqrt{V_t} - E_f}{Z_s \cos \theta_s} = \frac{\sqrt{V_t} \cos(\delta - \theta_s) - E_f \cos \delta}{Z_s \cos \theta_s}$$

$$\bullet \mathcal{N} = 3 \sqrt{V_t} \bar{I}_a^*$$

$$\mathcal{S} = \left(\frac{3 V_t^2 \cos \theta_s}{|Z_s|} - \frac{3 V_t E_f \cos(\delta + \theta_s)}{|Z_s|} \right) + \dots$$

$$\dots - j \left(\frac{3 V_t^2 \sin \theta_s}{|Z_s|} - \frac{3 V_t E_f \sin(\delta + \theta_s)}{|Z_s|} \right)$$

Special case if $R_a \rightarrow 0$

$$Z_s = X_s, \quad \theta_s = \tan^{-1} \left(\frac{X_s}{R_a} \right) \rightarrow 90^\circ$$

$$\mathcal{N} = \left(\frac{3 V_t E_f}{X_s} \sin \delta \right) + j \left(\frac{3 V_t^2}{X_s} - \frac{3 V_t E_f \cos \delta}{X_s} \right)$$

(P)

المتوسط

(Q)

دائماً يكون موجباً ولا يتغير أبداً

بجانب الإلكتر، فهو PP

- to start a synchronous motor → ① frequency control
- ② DC motor or

- Damper \equiv Stabilization & Damps the signal or any disturbances.

STARTING METHODS


① Use Dc prime mover.

- run the synch. machine as a generator to rated speed.
- Synchronize the generator to network.
- Switch on 3-phase supply
- Remove prime mover.

• prime mover power is much lower than that of synchronous motor since it is used to start the motor at no-load.


- Load the synchronous motor.

② Frequency control (inverter)

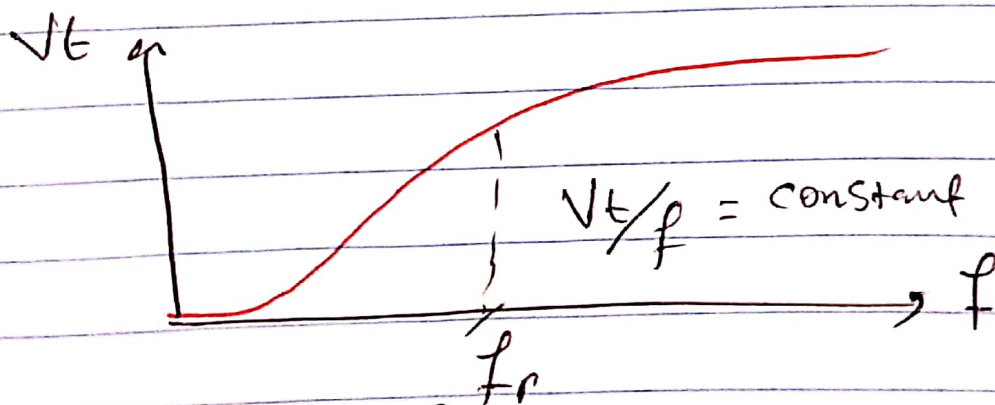

- Start at $f \leq 1 \text{ Hz}$.
- then f is increased continuously up to f_r (rated).

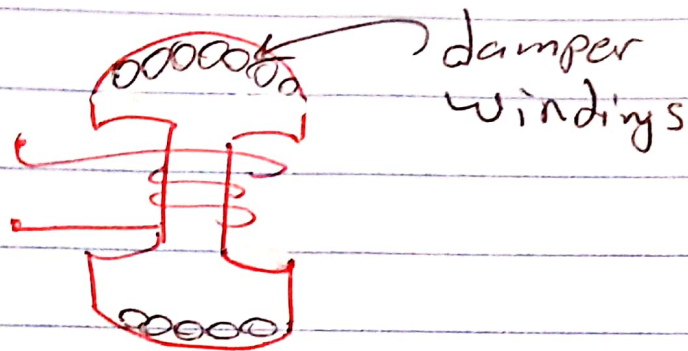③ Use Dumper winding to operate as a squirrel cage (laid on pole faces)




- These will start the motor but at synchronous speed, it has NO effect since slip = 0. It also serve as a stability means to the motor if mechanical load is changing drastically.

23/12/2019

Lecture 24

Q:- 300 kW at 60 Hz, available 50 Hz,
Motor-generator set (M-G).

How many poles?

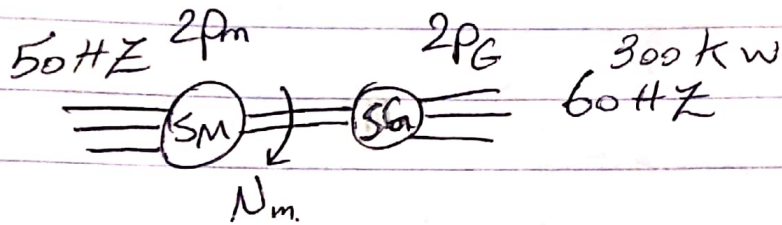

P	N_m	N_G
1	3000	3600
2	1500	1800
3	1000	1200
4	750	900
5	600	720
6	500	600

$$2P_m = 10$$

$$2P_G = 12$$



$$N_m = \frac{60f}{P}$$

Testing of synchronous


Machine

① DC test \rightarrow R_a (same as induction motor)

② No-load test
(open circuit test)

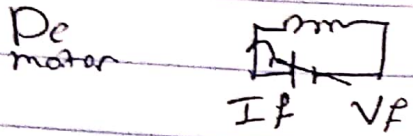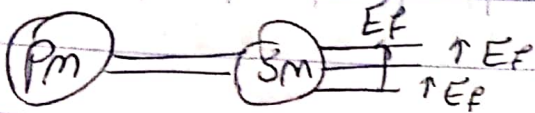


I_f	0
$V_{oc} = E_f$				
I_{sc}	0		N_r	(N_o)

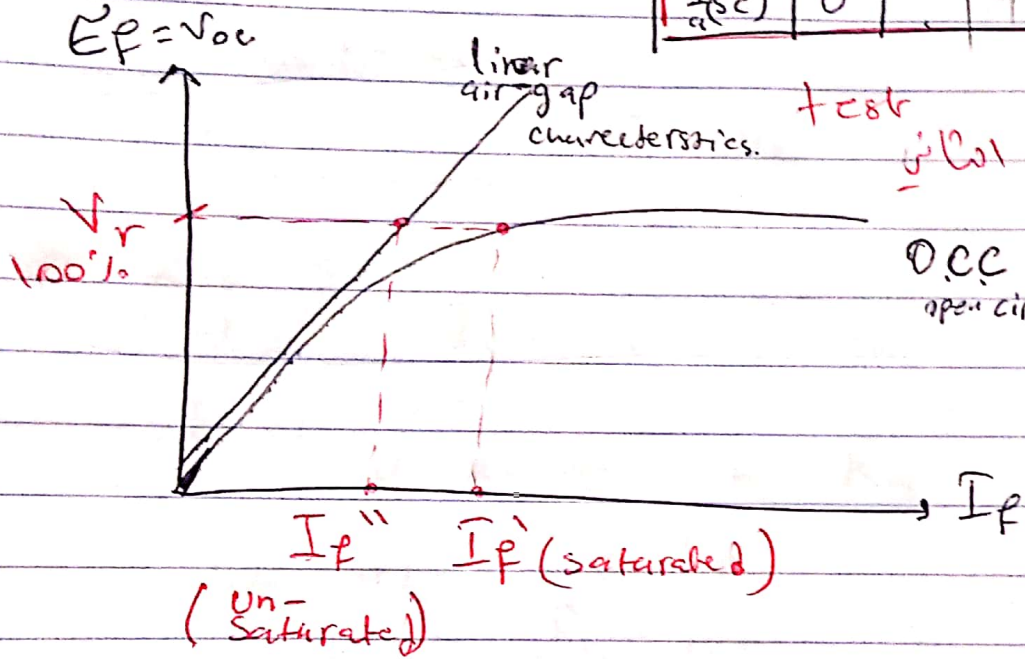

test of Col
two points are enough


Short circuit test

$N_m = N_s$


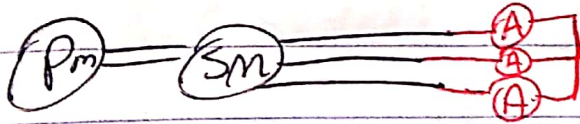


I_f is being varied & I_{sc} is recorded

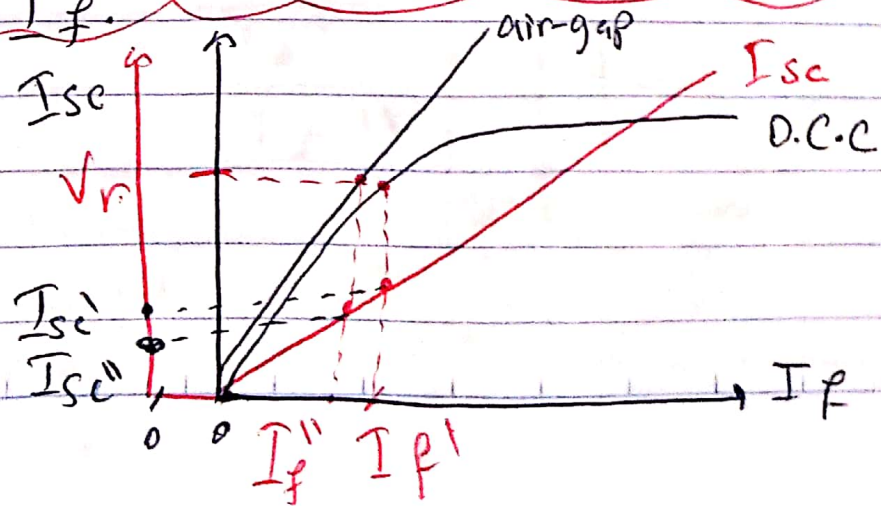Question: prove or justify that I_{sc} is linear with I_f .



Equivalent circuit

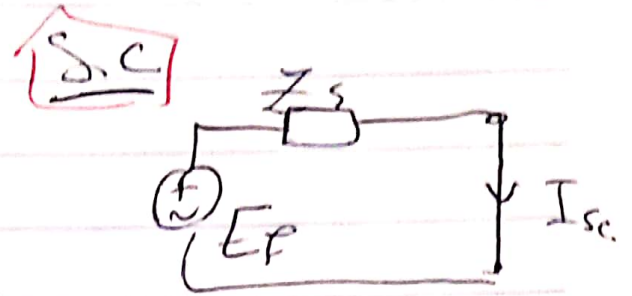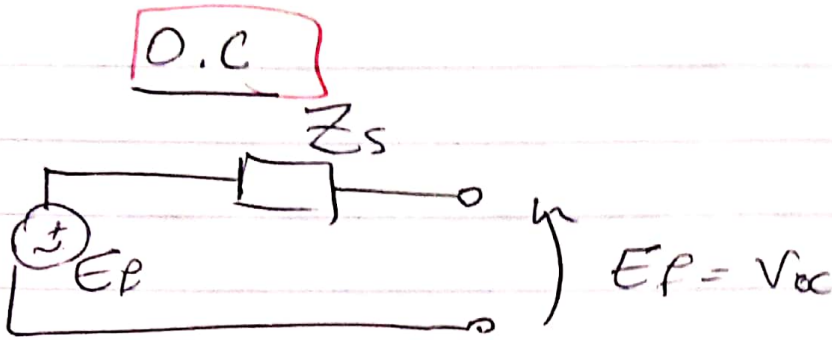

$$Z_s (sat) = \frac{V_r / ph}{I_{sc} / ph}$$

$$\rightarrow X_s (sat) = \sqrt{Z_s (sat)^2 - R_a^2}$$

$$\rightarrow Z_s (un-sat) = \frac{V_r / ph}{I_{sc}'' / ph}$$

$$Z_s (un-sat) > Z_s (sat)$$

$$\rightarrow X_s (un-sat) = \sqrt{Z_s (un-sat)^2 - R_a^2}$$


$$\rightarrow SCR = \frac{I_f \text{ at which } V_{oc} = V_r / o.c.T}{I_f \text{ at which } I_{sc} = I_{rated} / s.c.T}$$

Short circuit ratio

$$SCR = \frac{I_f'}{I_f''}$$

$$* SCR = \frac{1}{Z(sat) pu \text{ per unit.}}$$

$$\rightarrow Z_{base} = \frac{\sqrt{2}}{V}$$

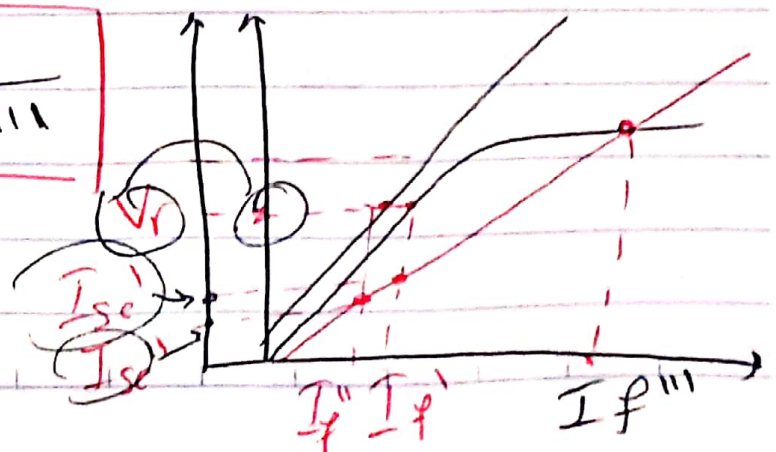

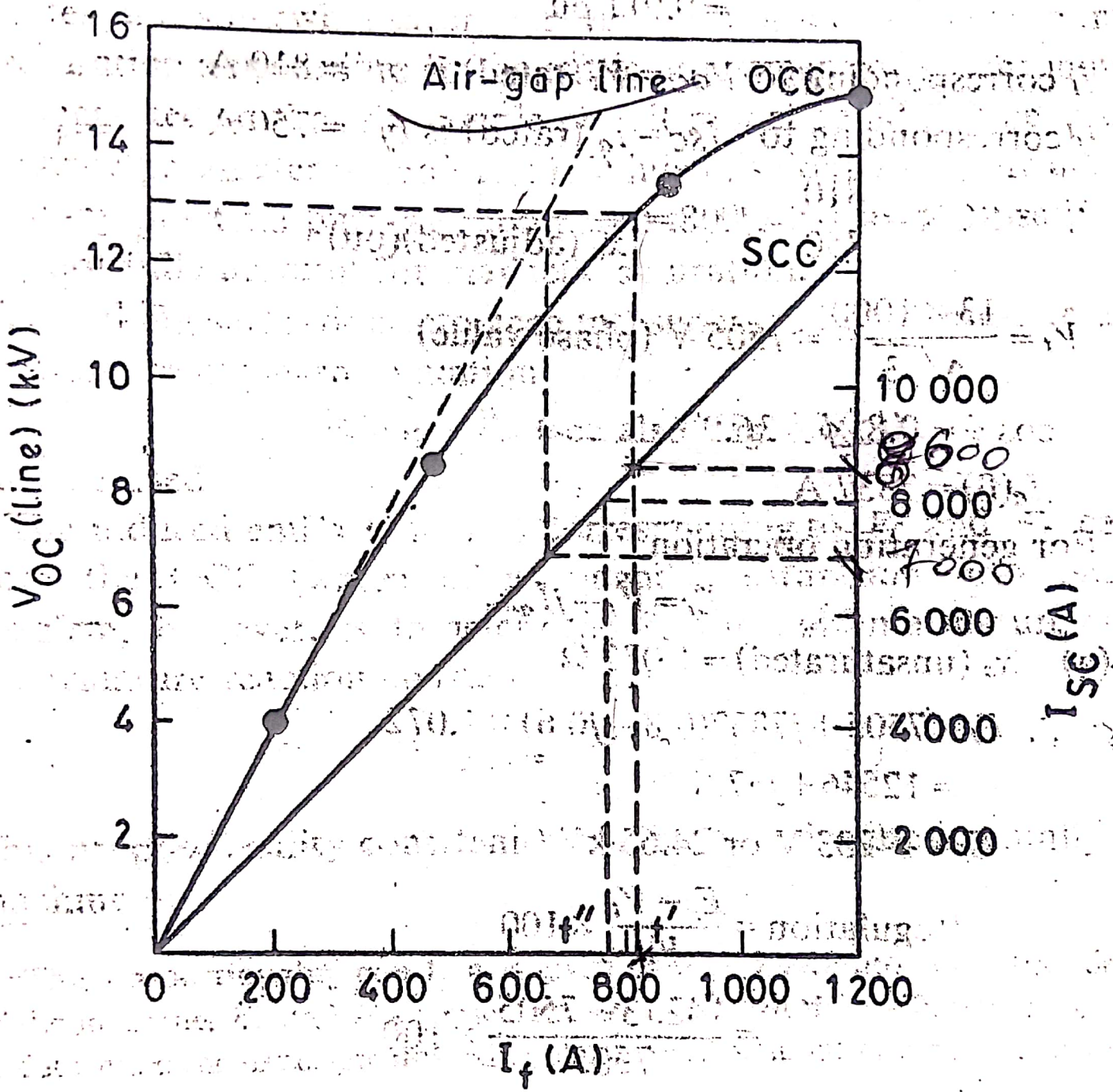


Fig. 8.15

23/12/2019

Lecture 25


ωLp1

Parameters evaluation:


Z_s, X_s, R_a (neglected in large machines), SCR.

R_a : if Y-connected:

$$2R_a = \frac{V_{Dc}}{I_{Dc}}$$

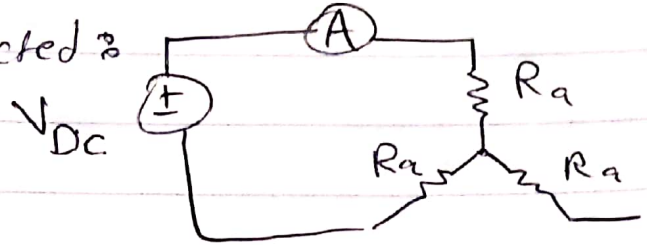

if Δ-connected:

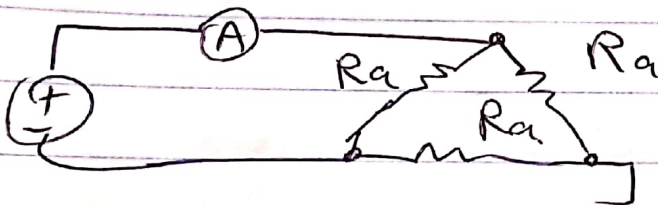

$$\frac{2R_a^2}{3R_a} = \frac{2}{3}R_a = \frac{V_{Dc}}{I_{Dc}}$$

$$R_a = \frac{3}{2} \frac{V_{Dc}}{I_{Dc}}$$

Question

No-DC test → (R_a also)

150 MW, 13 kV, 0.85 pf lagging, 50 Hz

$I_f = | 200A, 450A, 600A, 850A, 1200A$
 $E_f = | 4kV, 8.7kV, 10.8kV, 13.3kV, 15kV$

$I_{sc} @ I_f = 750A \rightsquigarrow 8000A$
 linear relation.

$I_a (r) = ??$

$$P = \sqrt{3} V_L I_L \cos \phi \rightarrow \text{PF}$$

$$S = \sqrt{3} V_L I_L \Rightarrow I_L (r) = \frac{150 \times 10^6}{\sqrt{3} \times 13 \times 10^3 \times 0.85}$$

$$\rightarrow I_{L(r)} = 7837.3 \text{ A} = I_{ph(r)} \text{ } \circ\circ \text{ Y-connected}$$

$$\rightarrow Z_{(un-sat)} = X_{(un-sat)} = \frac{13000/\sqrt{3}}{7000} \left\{ \begin{array}{l} \text{air-gap line} \\ V_{oc} = 13 \text{ kV} \\ I_a \approx 7000 \text{ A} \end{array} \right.$$

$$Z_{(un-sat)} = 1.07 \text{ } \Omega / \text{ph}$$

$$\rightarrow Z_{(sat)} = X_{(sat)} = \frac{13000/\sqrt{3}}{8600} \left\{ \begin{array}{l} \text{O.c.c.} \\ V_{oc} = 13 \text{ kV} \\ I_a = 8600 \text{ A} \end{array} \right.$$

$$Z_{(sat)} = 0.8 \text{ } \Omega / \text{ph}$$

$$\rightarrow SCR = \frac{820}{780} = \frac{I_f'}{I_f''} = 1.05 \text{ pu}$$

$$\rightarrow Z_{(base)} = \frac{\sqrt{V}^2}{\sqrt{I}^2} = \left(\frac{13000/\sqrt{3}}{\sqrt{I}} \right)^2$$

$$= \frac{13 \text{ k}^2 \text{ line}}{\sqrt{I}^2 \text{ 3-phase}} \left(\frac{\sqrt{V}}{3} \rightarrow \text{per phase} \right)$$

$$Z_{(base)} = \frac{(13000)^2}{(150 \times 10^6 / 0.85)} = 0.957 \text{ } \Omega / \text{ph}$$

$$\rightarrow Z_{(sat) \text{ in pu}} = \frac{Z_{(sat)} \text{ } \Omega}{Z_{base}} = \frac{0.8}{0.957} = 0.835 \text{ pu}$$

$$SCR = \frac{1}{Z_{(s) \text{ pu}}} = \frac{1}{0.835} = 1.19$$


Ex

Δ -connected, $Z_s = 2.5 \angle 80^\circ$

Given $E_f = 13.5 \text{ kV} \angle 15^\circ$, $V_t = 12 \text{ kV} \angle -7^\circ$


(Usually V_t is reference but in this question it is not!)

δ : between E_f & V_t

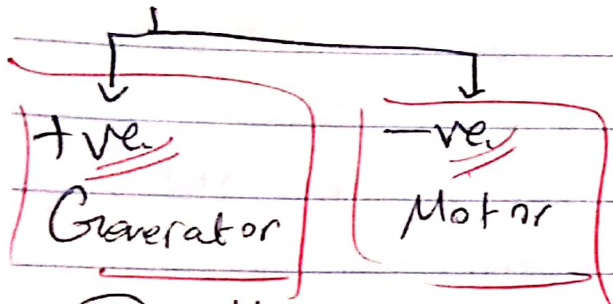


- (1) Motor or Generator ?? (2) $I_a = ??$ (3) PF = ??

Sol

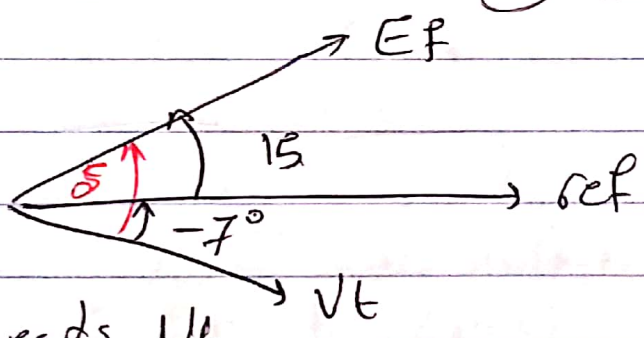

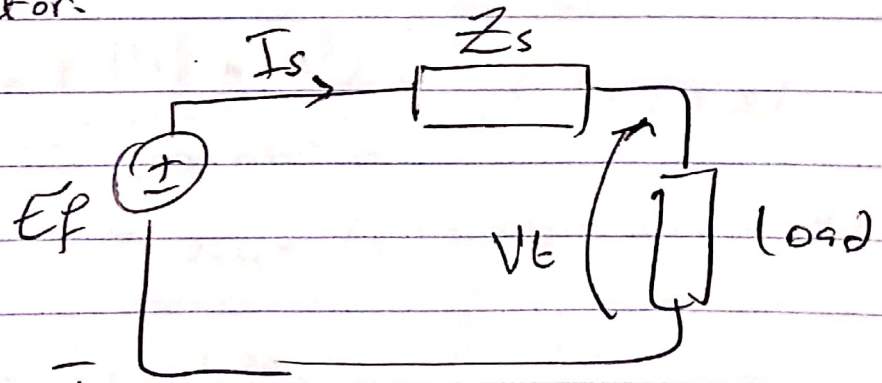$\delta = 22^\circ$
 so E_f leads V_t
 → Generator.




$$\bar{I}_a = \frac{\bar{E}_f - \bar{V}_t}{Z_s} \Rightarrow \bar{I}_a = \frac{13500 \angle 15^\circ - 12 \text{ kV} \angle -7^\circ}{2.5 \angle 80^\circ}$$

$$\bar{I}_a = 2033 \angle -2.8^\circ \text{ A}$$

$$\bar{I}_{a(U)} = 2033 \sqrt{3}$$

PF = ??

I_a leads V_t .

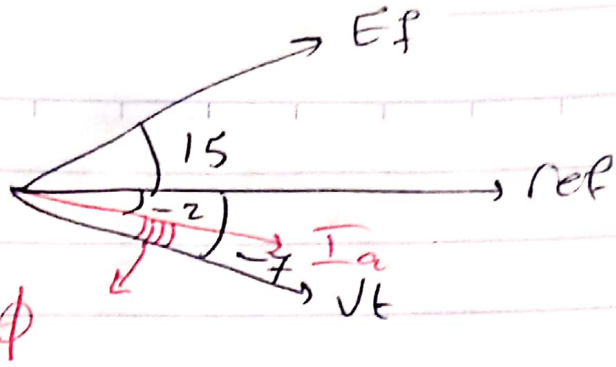

$$PF = \cos(5^\circ)$$

Question

100 MVA, 11.8 kV, 0.85 PF lagging
 50 Hz, $Z_p = 2$, Y-connected synchronous
 generator, has a pu synchronous reactance $X_s = 0.8$
 pu armature resistance $R_a = 0.012$.

X_s (sat) = ??
in Ω

R_a = ??
in Ω

E_f = ??

Torque angle
or power angle
at rated
conditions.

Sol

$P_{loss} \rightarrow 0$??
 T_{mech} to dev shift to get
 full load / rated

$$\rightarrow Z_{(base)} = \frac{(11.8 \times 10^3)^2}{100 \text{ MW}} = 1.3424 \Omega / \text{ph.}$$

$$\rightarrow X_s \text{ (sat)} = Z_{Base} \times X_s \text{ (sat) pu} = 1.3424 \times 0.8 =$$

$$\rightarrow R_a = 0.012 \times 1.3424 \quad \boxed{1.114}$$

$$= 0.0167 \Omega / \text{ph.}$$

$$\rightarrow Z_s = \sqrt{R_a^2 + X_s \text{ (sat)}^2} = 1.114 \quad \boxed{89.14}$$

$$\rightarrow I_a \text{ (rated)} = \frac{100 \text{ M}}{\sqrt{3} \times 11.8 \text{ kV}} = 4892.8 \text{ A}$$

$$\rightarrow \bar{I}_a(m) = 4892.8 \angle -31.7 \text{ lagging}$$

$$\rightarrow \bar{E}_f = \bar{V}_t + \bar{I}_a \bar{Z}_s \quad \text{per phase.}$$

$$= \left(\frac{11800}{\sqrt{3}} \angle 0^\circ \right) + \left(4892.8 \angle -31.7 \times 1114 \angle 89.14^\circ \right)$$

$$\bar{E}_f = 10779 \angle +25.2 \text{ N/ph.}$$

$$\rightarrow \bar{E}_f \text{ per line} = 10779 \times \sqrt{3}$$

$$\Rightarrow P_{in} = \frac{T_{sh}}{??} \times \omega_m \rightarrow \omega_s = \frac{2\pi f}{p} = \omega_m$$

$$\rightarrow P_{sh} = P_{in} = P_o + P_{loss} + P_{cu} \quad \Rightarrow N_s = \frac{60f}{p}$$

$$P_{sh} = P_o + P_{cu}$$

$$\omega_s = \frac{2\pi N_s}{60}$$

$$= (100M \times 0.85) + (3 \times 4892.8)^2 \times 0.96 = \frac{2\pi \times 50}{1 \text{ pole pair}} = 314 \text{ rad/s}$$

$$P_{sh} = 85M + 1.14M = 86.14MW$$

$$\rightarrow T_{shaft} = P_{sh} / \omega_m = 274 \text{ k.Nm}$$

24/12/2024

Lecture 26

in ohm

Ex) 20 MVA, 13.8 kV, 0.8 pf lagging, Y-connected, synchronous Generator has an $X_s = 0.7$ pu, $R_a \rightarrow 0$, another SG in parallel with an infinite bus-bar. ---

a) what is the armature reactance $X_s(\Omega) = ??$

b) E_a and δ at rated condition.

c) If E_a (internal EMF) is reduced by 5%, what is the new $R_a = ??$, $PF = ??$

by field current

a) $X_s(\Omega) \rightarrow X_s = X_s \text{ pu} * Z_{\text{base}}$

$$Z_{\text{base}} = \frac{V_r^2}{S_r} = \frac{(13.8 \times 10^3)^2}{20 \times 10^6} = 9.522 \Omega/\text{ph.}$$

$$X_s(\Omega) = 9.522 * 0.7 = 6.6654 \Omega/\text{ph.}$$

b) $I_a(r) = ?? \rightarrow S_n = 3 V_{\text{ph}}(r) * I_{\text{ph}}(r)$

$$I_a(\text{ph}) = \frac{20 \times 10^6}{3 * \frac{13800}{\sqrt{3}}} = 836.74 \text{ A}$$

$$I_a(\text{ph}) = 836.74 \angle -36.87^\circ$$

$$\vec{E}_a = \vec{V}_t + \vec{I}_a * \vec{Z}_s$$


by original X_s base, 1 pu
phase $V_t = 13800$

$$= \frac{18300}{\sqrt{3}} \angle 0 + 836.74 \angle -36.8 * 6.6654 \angle +90$$

$$= 12161.7 \angle +21.52^\circ \text{ A, So } \delta = 21.52^\circ$$

$$\bar{E}_a' = 0.95 \bar{E}_a \rightarrow \boxed{P = P'} \text{ constant power}$$

↑
at $\delta = 90^\circ$

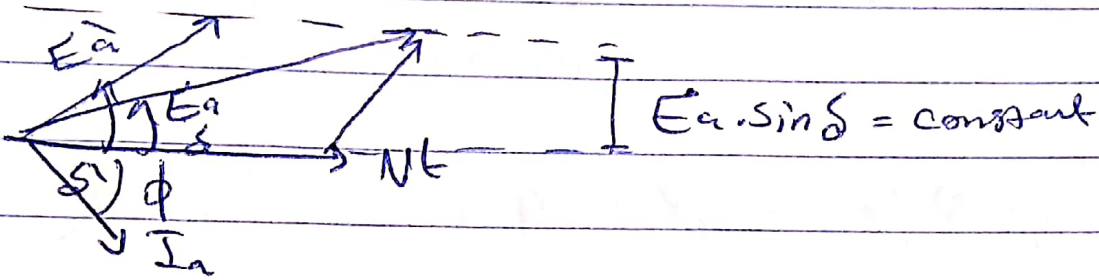

$$\bar{E}_a' \sin \delta' = \bar{E}_a \sin \delta \Rightarrow \sin \delta' = \frac{\bar{E}_a}{\bar{E}_a'} \sin \delta$$

$$= \frac{1}{0.95} \sin(21.52) \Rightarrow \delta' = \underline{22.717^\circ}$$

5) تقریباً

$$P = 3 V_t I_a \cos \phi$$


$$\rightarrow I_a(\text{new}) \Rightarrow \bar{I}_a = \frac{\bar{E}_a' - V_t L_0}{j + 6.6654}$$

$$0.95 \bar{E}_a \left[22.717 - \frac{13600}{\sqrt{3}} \frac{j X_s}{L_0} \right]$$

$$= 781.644 \angle -31^\circ$$

$(-31.08)^\circ \text{ A}$
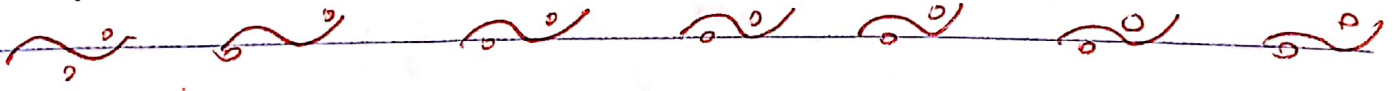
$$\ast \text{PF}' = \cos 31.08 = 0.8564 \text{ lag.}$$



Q 13.8 kV, 10 MVA, Y-connected, 0.8 PF lag
 60 Hz, 2-poles, $X_s = 18 \Omega$, $R_a = 2 \Omega$, connected
 to infinite bus-bar: a) $E_a = ??$ at rated conditions.
 b) $\delta = ??$ at rated conditions c) $I_f = \text{constant}$,
 ($E_a = \text{constant}$), what is the maximum

output power?? , How much reserved power at full load

d)) at part c)) what is $Q = ??$ (supplying or consumed?)

Sol)) a) $Z(s) = R_a + jX_s = 2 + j18 = \sqrt{2^2 + 18^2}$

$$\angle \tan^{-1} \left(\frac{18}{2} \right) \rightsquigarrow 18.1107 \angle 83.7^\circ \leftarrow \theta_s$$

$$I_a(r) = \frac{10M}{\sqrt{3} \times 13.8 \times 10^3} = 418 \angle -36.9^\circ \text{ A/ph}$$

$$\begin{aligned} \bar{E}_a &= \frac{13800}{\sqrt{3}} \angle 0 + 418 \angle -36.9^\circ \times 18.1107 \angle 83.7^\circ \\ &= 14260 \angle 22.8^\circ \text{ V} \Rightarrow \delta = 22.8^\circ \end{aligned}$$

$$E_a = 14260 \text{ V/ph.}$$

$$\Rightarrow \text{Voltage regulation} = \frac{14260 - 13800/\sqrt{3}}{13800/\sqrt{3}}$$

⊗ Maximum power.

a)) $R_a \rightarrow 0$ (neglected, $\delta = 90^\circ$)

$$(P = \frac{3 V_t E_f}{X_s} \sin \delta)$$

but b)) $R_a \neq 0 \rightarrow \delta = \theta_s = 83.7^\circ$

$$\bar{E}_a \text{ at maximum power} = 14260 \angle 83.7^\circ$$

$$I_a (\text{max. power transfer}) = \frac{E_p' - V_t}{Z_s}$$

$$= \frac{14260 \angle 83.7 - \frac{13800}{\sqrt{3}} \angle 0}{18.1107 \angle 83.7}$$

$$= 858.76 \angle 30.6 \text{ (Leading angle)}$$

115° Max

$$\rightarrow P_{\max} = \sqrt{3} V_L I_a \cos \phi = \sqrt{3} \times 13800 \times 858 \cos(30.6)$$

$$= 17.66 \text{ MW}$$

→ (another way to calculate P_{\max}):


$$P_{\max} = \frac{-3V_L^2}{Z_s} \cos \theta + \frac{3V_L E_a}{Z_s} \cos(\delta - \theta_s)$$

$$= \frac{-3 \times \left(\frac{13800}{\sqrt{3}}\right)^2}{Z_s} \cos(83.7) + \frac{3 \times 13800 + 1426}{\sqrt{3} Z_s} \cos \theta$$

$$= \frac{-13800^2}{18.1107} \cos(83.7) + \frac{3 \times 13800 + 1426}{\sqrt{3} \times 18.1107}$$

$$= 17.60 \text{ MW}$$

Q at P_{\max}

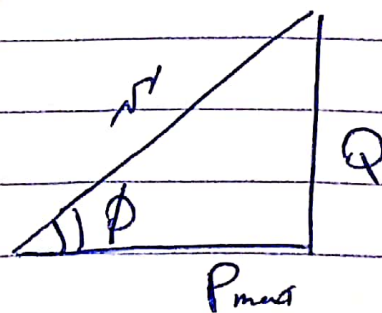


$$Q \text{ at } P_{\max} = P_{\max} \tan \phi$$


$$Q = \frac{3V_L^2}{Z_s} \sin \theta + \frac{3V_L E_a}{Z_s} \sin(\theta - \delta)$$

$$\boxed{\text{or}} \quad Q = \sqrt{3} \times 13800 \times 858.76 \times \sin [30.6^\circ]$$

$$= 10.4 \text{ M(VAR)}$$

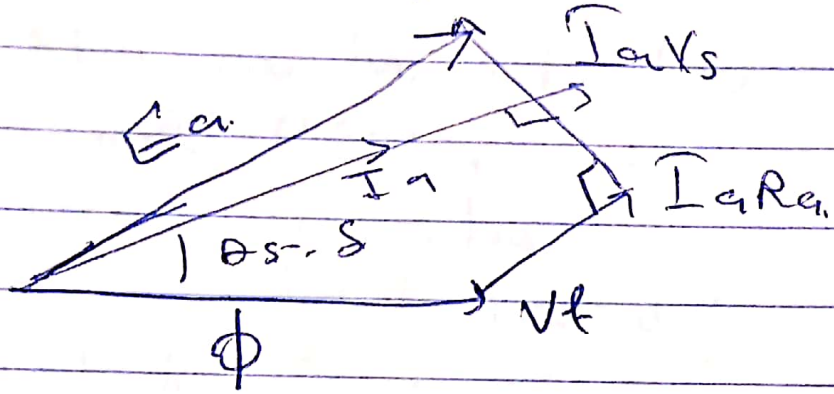

(Phasor diagram without neglecting R_a)

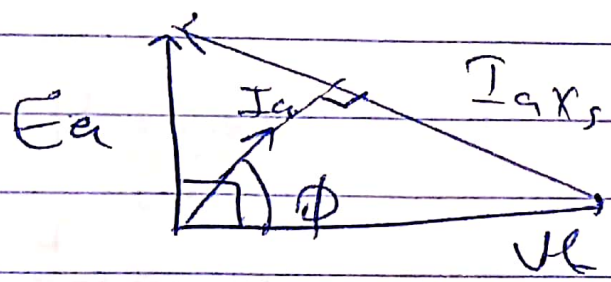

(Phasor diagram neglecting R_a)

$$\rightarrow P_{\text{reserved}} = P_{\text{max}} - P_r$$

$$= 17.66 - 8$$

$$= 9.66 \text{ MW}$$

Q) 480 V, 100 kW, two-pole, 60 Hz, 3ph SGM, its P.M has no-load speed of
 prime mover

3630 RPM and has a full-load speed = 3570 RPM

G_2 in parallel 480 V, 75 kW, 4-pole, 60 Hz Synchronous Gen. its P.M has no-load speed of 1800 RPM

also it has a full-load speed of 1785 RPM.


load = 100 kW, ($f_{system} = ?$) ($P_{G1}, P_{G2} = ?$)
 (load sharing)

$$\rightarrow \textcircled{G_1} \quad f_{NL(1)} = \frac{P \times N_m}{60} = \frac{1 \times 3600}{60} = 60 \text{ Hz}$$

$$f_{FL(1)} = \frac{P \times N_m(FL)}{60} = \frac{1 \times 3570}{60} = 59.5 \text{ Hz}$$

$$\rightarrow \textcircled{G_2} \quad f_{NL(2)} = \frac{2 \times 1800}{60} = 60 \text{ Hz}$$
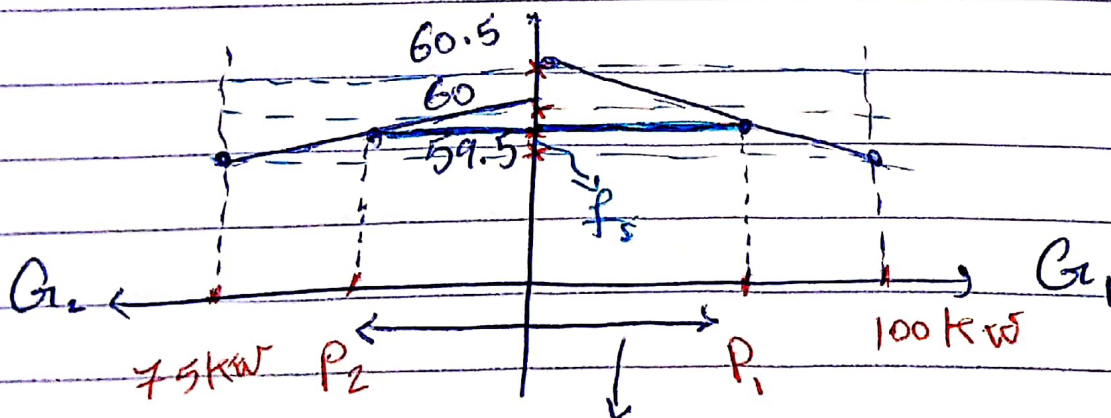
$$f_{FL(2)} = \frac{2 \times 1785}{60} = 59.5$$



$$P_1 + P_2 = 100 \text{ kW} = L$$

to find $f_s \rightsquigarrow P_L = 100(\underbrace{f_{nc(1)}}_{PG_{11}} - f_s) + 75(\underbrace{f_{nc(2)}}_{PG_{12}} - f_s)$

$$P_L = 100 \times 60.5 - 100 f_s + 75 \times 60 - 75 f_s$$

$$f_s = 59.714 \text{ Hz}$$

$$\Rightarrow PG_{11} = 100 \times (60.5 - 59.714)$$

$$PG_{12} = 75 \times (60 - 59.7)$$

$$PG_{11} = 78.6 \text{ k}, PG_{12} = 21.4 \text{ k}$$

$$PG_{11} + PG_{12} = 100 \text{ k}$$

Q) 3- Identical Synchron. Generators are connected in parallel

per line = 3 MW

3 MW, 0.7 pf lag

① $f_{NL} = 61$ Hz, speed droop = 3.4%

$$SD = \frac{f_{NL} - f_{FL}}{f_{FL}} \text{ or } SD = \frac{N_{NL} - N_{FL}}{N_{FL}}$$

$$PL = 7 \text{ MW}$$

② $f_{NL} = 61.5$ Hz, speed droop = 3%

③ $f_{NL} = 60.5$ Hz, speed droop = 2.6%
Is power sharing acceptable? why?

$$sd) \quad 7 = 3(f_{NL(1)} - f_s) + 3(f_{NL(2)} - f_s) + \dots$$

$$- 3(f_{NL(3)} - f_s)$$

$$= 3(61 - f_s) + 3(61.5 - f_s) + 3(60.5 - f_s) \Rightarrow f_s = 60.22$$

$$So \quad \begin{cases} P_1 = 3(61 - 60.22) = 2.33 \text{ MW} \\ P_2 = 3(61.5 - 60.22) = 3.8334 \text{ MW} \\ P_3 = 3(60.5 - 60.22) = 0.8334 \text{ MW} \end{cases}$$

Load sharing is not acceptable because C_{r2} is over-loaded, we must set up C_{r3} and set down C_{r2} .

Given a Synchronous motor Rating 208V, 15hp,
 0.8 pf lead, Δ -connected, 60 Hz, $R_a = 0$
 $X_s = 2.5 \Omega / \text{ph}$.


$$P_{\text{friction \& windage}} = P_{\text{mechanical}} = 15000 \text{ W}$$

$$P_{\text{core}} = 1000 \text{ W}$$


① when supplying rated power at 0.8 leading pf,

Find: (a) I_a , E_f / E_a ?

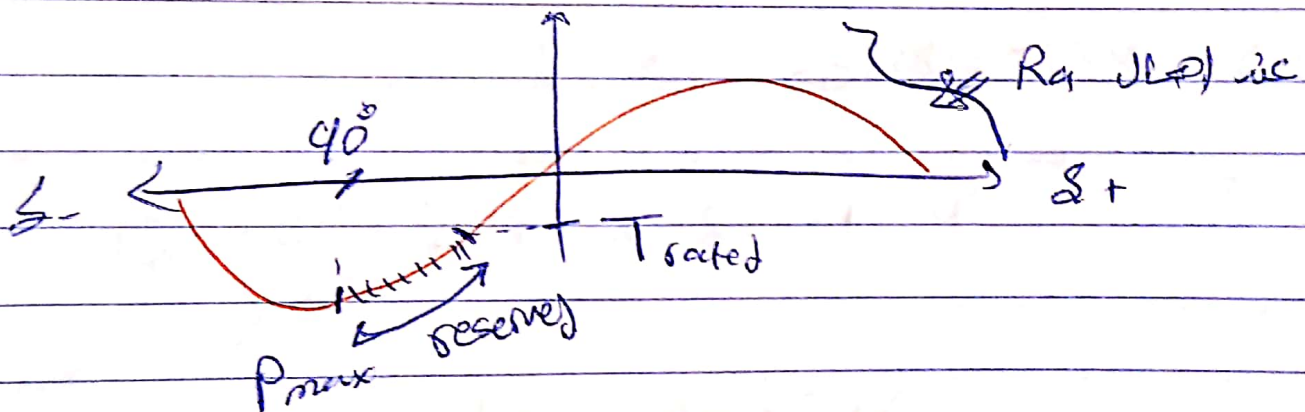(b) if supplying double rated power, repeat (a)



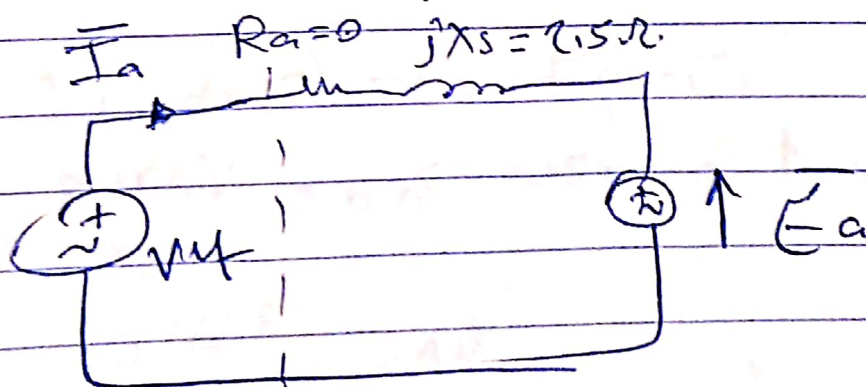\Rightarrow start by the equivalent circuit \checkmark



$\text{PF}_{\text{input}} = 0.8 \text{ leading}$

$$P_{\text{rated}} = 15 \text{ hp} \times 746 = 11190 \text{ W}$$

$$P_{\text{in}} = P_{\text{out}} + P_{\text{copper}} = P_{\text{core}} + P_{\text{mech loss}}$$

$$= 11190 + 0 + 1000 + 1500 = 13690 \text{ W}$$

③ $3 I_a^2 R_a$
3-phase power

$$I_a(\text{L}) = \frac{P_{\text{in}}}{\sqrt{3} V_{\text{L}}(\text{L}) \times \text{PF}} = \frac{13690}{\sqrt{3} \times 208 \times 0.8}$$

$$I_a(\text{L}) = 47.5 \text{ A}$$

$$\bar{I}_{\text{L(PN)}} = \frac{47.5}{\sqrt{3}} = 27.42 \angle \cos^{-1}(0.8) \text{ lead} = +36.87^\circ$$

$$\vec{E}_f = \vec{E}_a = \sqrt{3} V_{\text{L}} \angle -27.42 \angle 36.87 + Z_s$$

motor

$$\vec{E}_a = 255 \angle -12.4^\circ \quad \delta = -12.4^\circ \quad 2.5 \angle 90^\circ$$

motor and power

$$P_o = 2 \times 15 \text{ hp} = 30 \times 746$$


$$P_{\text{in}} = 30 \times 746 + 1500 + 1000 = 24880 \text{ W}$$

$$I_f' = I_f \Rightarrow E_a' = E_a = E_f' = E_f$$

$$P_1 = \frac{3 V E_f' \sin \delta}{X_s} \text{ assuming } R_a \text{ is } \hat{0}$$

$$P_2 = \frac{3 V E_f' \sin \delta'}{X_s}$$
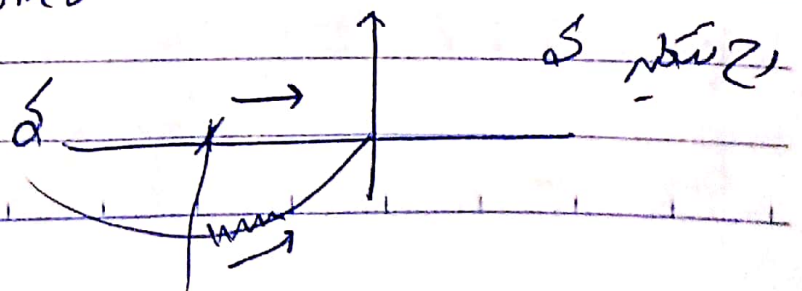
$$\frac{P_2}{P_1} = \frac{\sin \delta'}{\sin \delta}$$



$$\sin \delta' = \frac{P_2}{P_1} \sin \delta = \frac{24880}{13690} \sin(-12.4)$$


$$\delta' = -22.97^\circ$$

$$\vec{I}_a = \frac{\vec{V}_L - \vec{E}_f'}{jX_s} = \frac{208 \angle 0^\circ - 255 \angle -22.97^\circ}{2.5 \angle 90^\circ}$$

$$\vec{I}_a = 41.2 \angle 15^\circ \text{ A}$$

$$P_{cu} = P_{cu(r)} + \left(\frac{41.2}{27.4} \right)^2 \rightarrow R_a$$

$$PF = \cos(15^\circ)$$

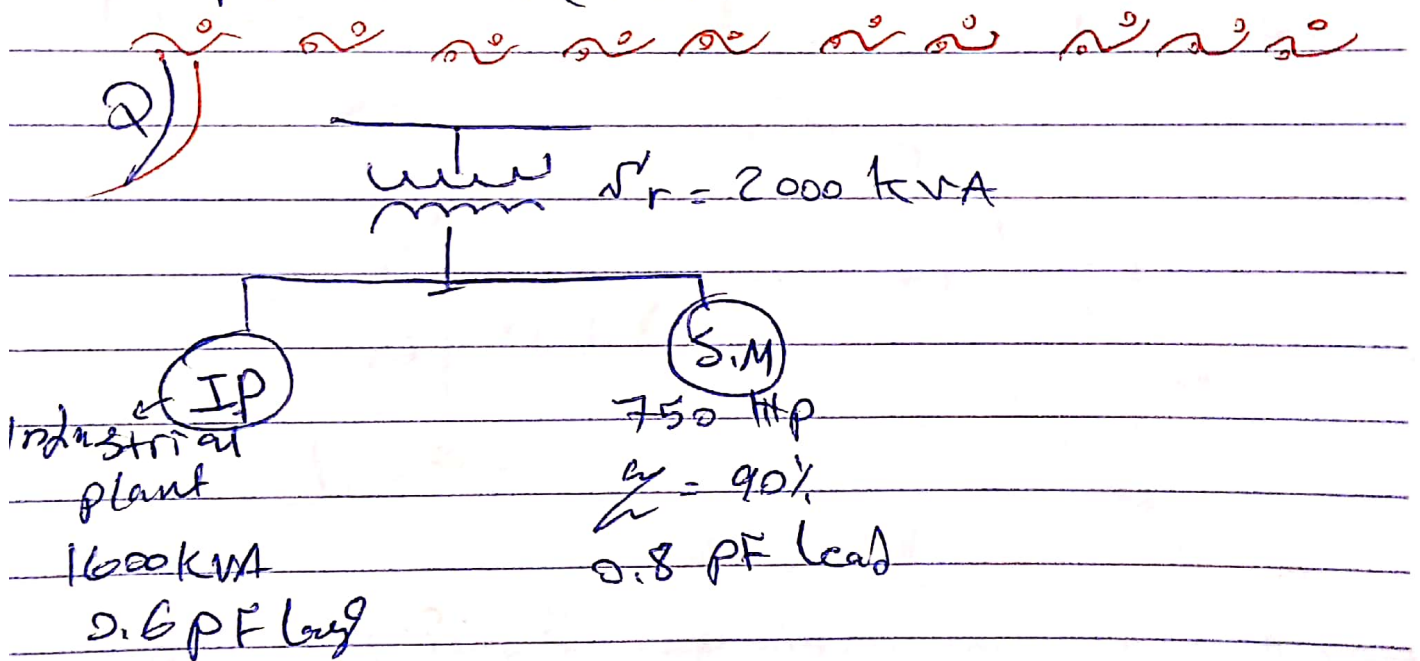

Line diagram of a transformer supplying an industrial plant of 1600 kVA, 0.6 PF lag. The transformer rating 2000 kVA it is required to add a 750 Hp, 90% efficiency, 0.8 PF lag synchronous motor in parallel. — will the addition of this load, over-load

The transformer, what will be the new PF after the addition of this load to the overall system.



Sol)

$$S_L = 1600 \times 10^3 \angle +53.13$$

$$\Rightarrow 1600 \times 10^3 \cos(53.13) + j1600 \times 10^3 \sin(53.13)$$

$$= \underbrace{960 \times 10^3}_{P_L} + j \underbrace{1280 \times 10^3}_{Q_L}$$
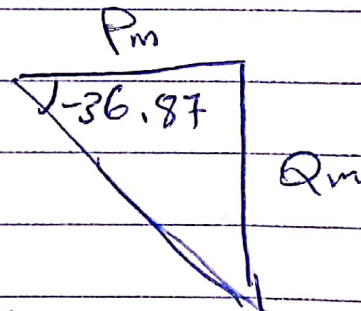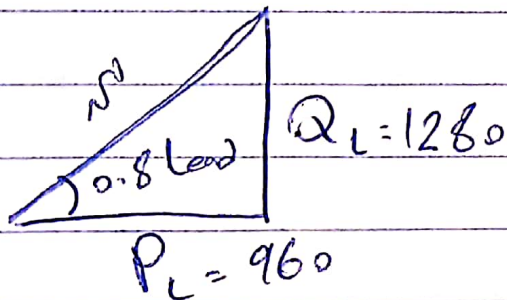
$$P_m = \frac{750 \times 746}{\cos 50.9} = \frac{P_o}{\cos 50.9} = 621.67 \text{ kW}$$



وجود انساب برای پمپ و موتور ϕ ایون جالب

$$\frac{Q_m}{P_m} = \tan(-36.87) \Rightarrow Q_m = P_m \tan(\phi) = -621.67 \times (36.87) \tan$$

$$Q_m = -466.25 \text{ kVA}$$

$$\text{overall } P_t = 960 \times 10^3 + 621.67 \times 10^3 = 1581.67 \text{ kW}$$

$$\text{but } Q_t = 1280 \times 10^3 - 466.25 \times 10^3 = 813.75 \text{ kVA}$$

$$S_t = \sqrt{P_t^2 + Q_t^2} = 1778.72 \text{ kVA}$$

$$\tan^{-1}\left(\frac{Q_t}{P_t}\right) = \angle 27.2$$

$$PF_{in} = 0.889$$

Since $S_t < S_r (Tr) \rightarrow$ no problem!

21 / 2019

Lecture 23
& Final!

(Q) $V_r = 440V$, $f = 50Hz$, $P_o = 100 \text{ hp}$, Δ -connected
 $PF = 0.8$ leading, $\eta_{FL} = 0.89$, $R_a = 0.22 \Omega/\text{ph}$

$X_s = 3 \Omega/\text{ph}$, (a) $I_a = ?$, at rated conditions
 $I_a(r) = ??$

Sol/

$$P_o(r) = 100 \times 746 = 74600 \text{ W}$$

$$P_{in}(r) = \frac{P_o(r)}{\eta_{F.L.}} = \frac{74600}{0.89} = 83820 \text{ W}$$

$$P_{in}(r) = \sqrt{3} V_L I_L \cos \phi$$

$$I_L = \frac{83820}{\sqrt{3} \times 440 \times 0.8} = 137.482 \text{ A}$$

$$I_a(r)_L = 137.482 \text{ A}$$


$$I_a(r)_{ph} = \frac{137.482}{\sqrt{3}} = 79.375 \text{ A}$$

$$I_a(r)_{ph} = 79.375 \text{ A} \quad \text{① } 36.87^\circ \text{ leading PF}$$

(b) If the field current is reduced to 90% of its original value, calculate I_a' , $PF_{in}' = ??$
 $\eta' = ??$

$$\bar{I}_a = \frac{V_t - E_a}{Z(s)}$$

We must find E_a alphan

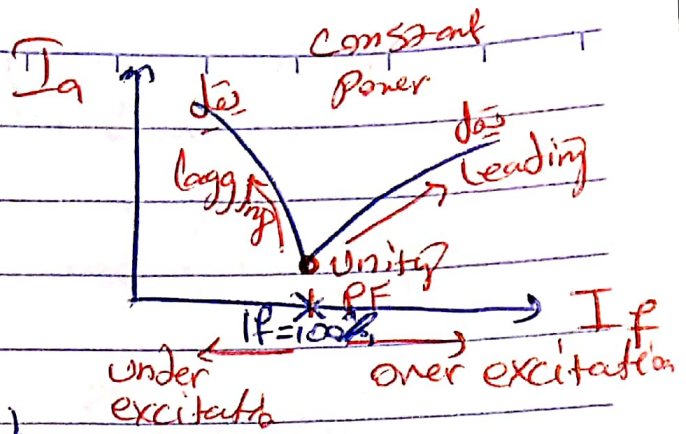

$$\bar{E}_a(r) = V_t(r) - \bar{I}_a(r)_{ph} * Z(s)$$

$$Z(s) = 0.22 + j3$$

$$= 3.008 \angle 85.8^\circ \rightarrow \theta_s$$

$$\bar{E}_a(r) = 603.34 \angle 19.46^\circ$$

$$E_a' = 0.9 E_a(r)$$

$$= 603.34 * 0.9 = 543 \angle \dots$$

$$E_a(r) \sin \delta_r = E_a' \sin \delta'$$

$$\sin \delta' = \frac{E_a(r)}{E_a'} * \sin \delta_r$$

$$= \frac{1}{0.9} \sin \delta_r \rightarrow \delta' = -21.726^\circ$$

$$\bar{E}_a' = 543 \angle -1.726$$

$$\bar{I}_a = \frac{440 \angle 0 - 543 \angle -21.726}{3.008 \angle 85.8}$$

$$\bar{I}_a = 70.35 \angle +22.42 \text{ A/ph.}$$

$$PF_{in}' = \cos 22.4 = 0.9244 \angle \text{leading}$$

$$Q = ?? \rightarrow \sqrt{3} V_L I_L \sin 22.4$$


$$= \rightarrow 3437 \text{ VAR generated (leading PF)}$$

$$P_{in} = \sqrt{3} \times 440 \times (\sqrt{3} \times 70.35) \times \cos(22.4)$$

$$P_o = P_{in} = 74600 \rightarrow \eta = \frac{P_o}{P_{in}}$$

Single-phase-Induction Motors

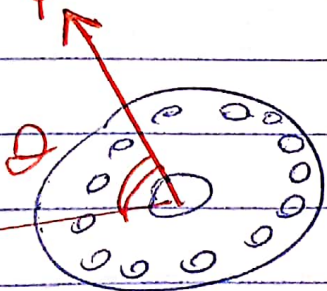- also called fractional hp motors, always squirrel
- domestic applications & low-power induction applications either Fraction hp Induction motors or DC motors.




$$i_m = N_m \cos(\omega t)$$

$$F(t) = I_m N_m \cos(\theta) \cos(\omega t)$$

N_m : main windings

field access.

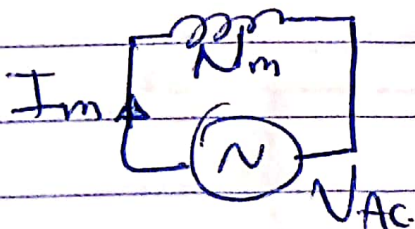

$$F(t) = F_m \cos(\theta) \cdot \cos(\omega t)$$

pulsating field


$$\vec{F}(t) = \frac{1}{2} F_m \cos(\theta + \omega_s t) + \frac{1}{2} F_m \cos(\theta - \omega_s t)$$

rotating field in the direction (Forward) rotating field in the -ve direction (backward)

$$S_f = S = \frac{N_s - N_m}{N_s}$$


$$S_b = \frac{-N_s - (N_m)}{-N_s}$$

$$= 1 - \frac{N_m}{N_s} = D(1 - s^2)$$

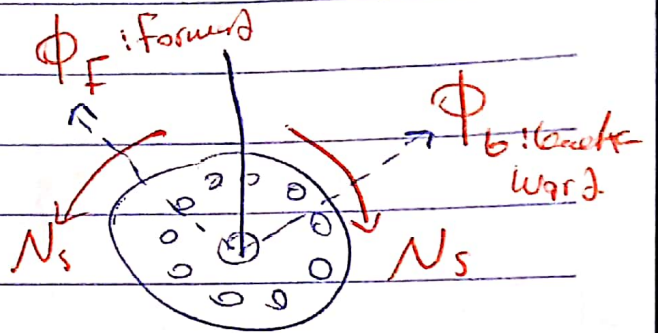

$$= D \left(1 + \frac{N_m}{N_s} \right) = 1 + (1 - S) = 2 - S$$

$$S_f = s^2, \quad S_b = 2 - S$$

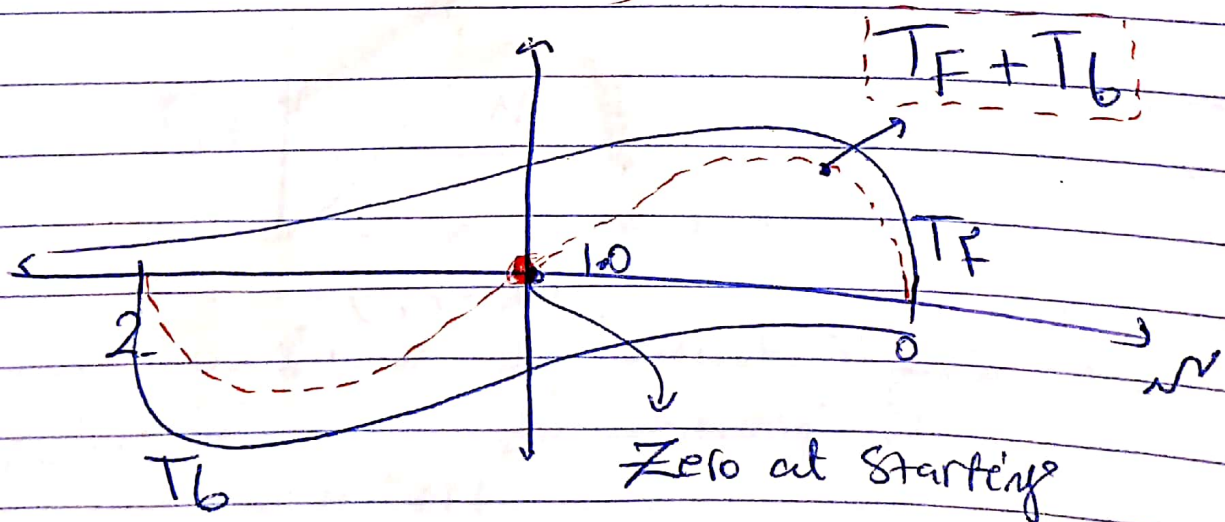


$T_{st}(F) = T_{st}(b) \rightarrow$ different ω_s signs. (+, -)


$T_g(t) = 0$ at starting
 → (Single-phase - Induction motor)
 → (non-self-starting)

①

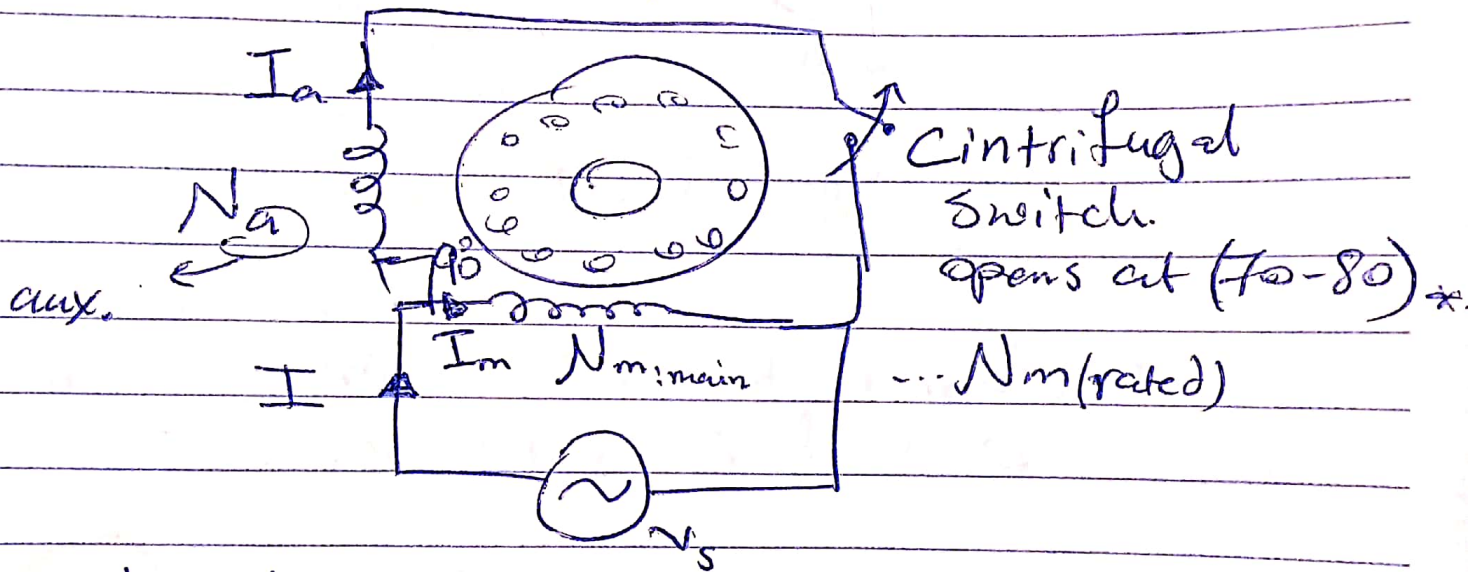Two windings motor: add auxiliary?
 field windings to the armature.




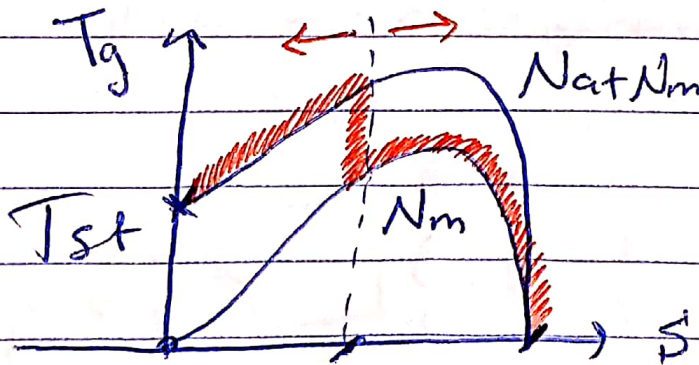$N_m, N_s \rightarrow$ results in non-zero starting



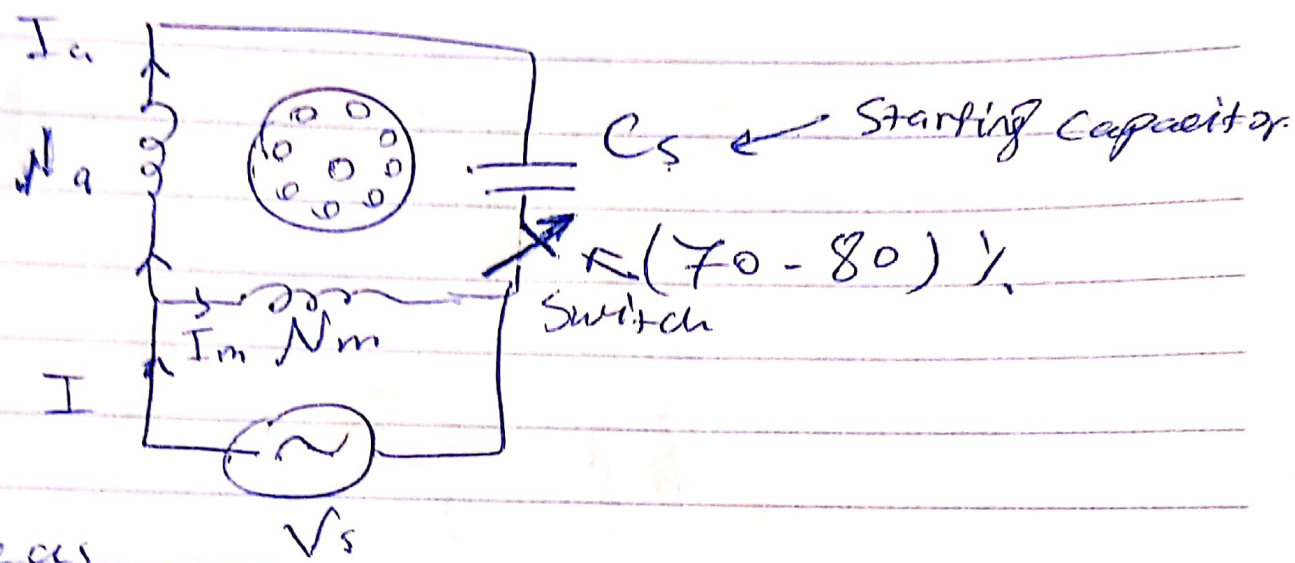
(70-80)%
 at relatively low-power factor. Switch is closed at starting T_g to N_m

2 Starting capacitor - Single Phase - Induction motor




Same as two windings but at relatively High starting torque & high starting PF.

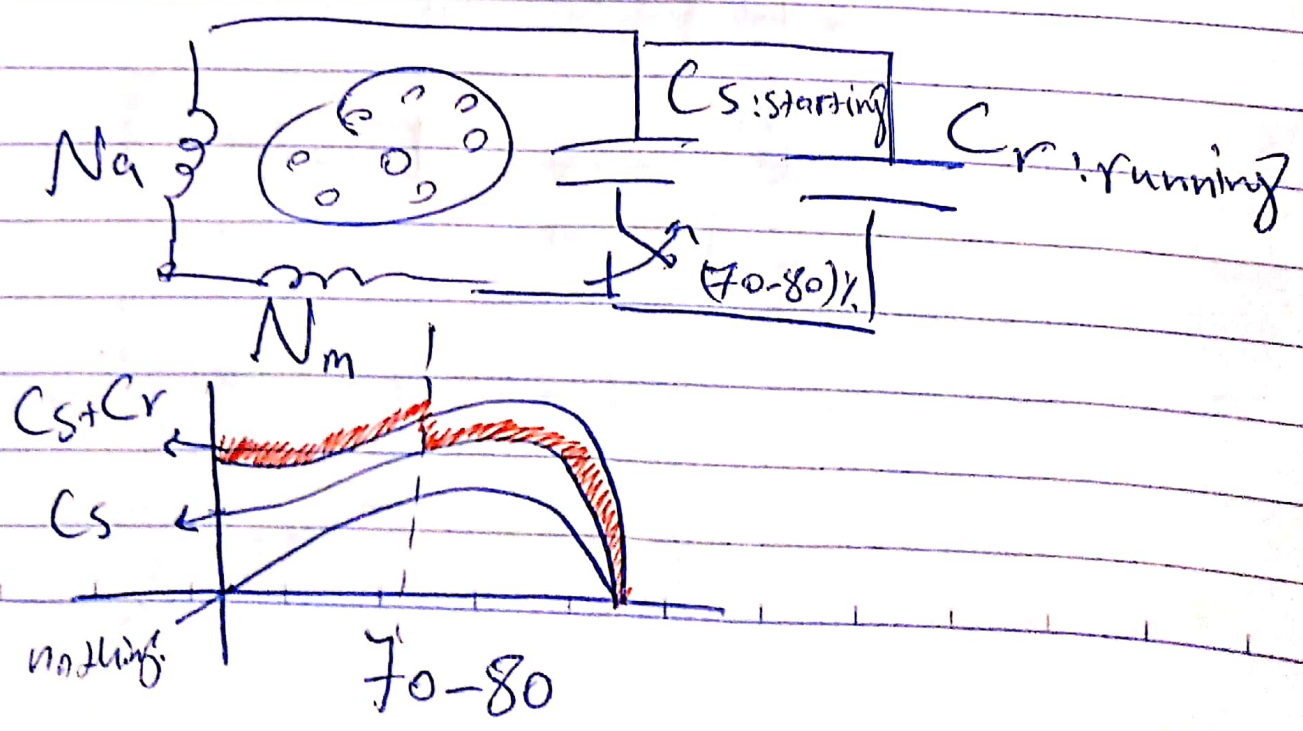3 Capacitor - starting - capacitor - running - Single phase - Induction motor



Equivalent circuit

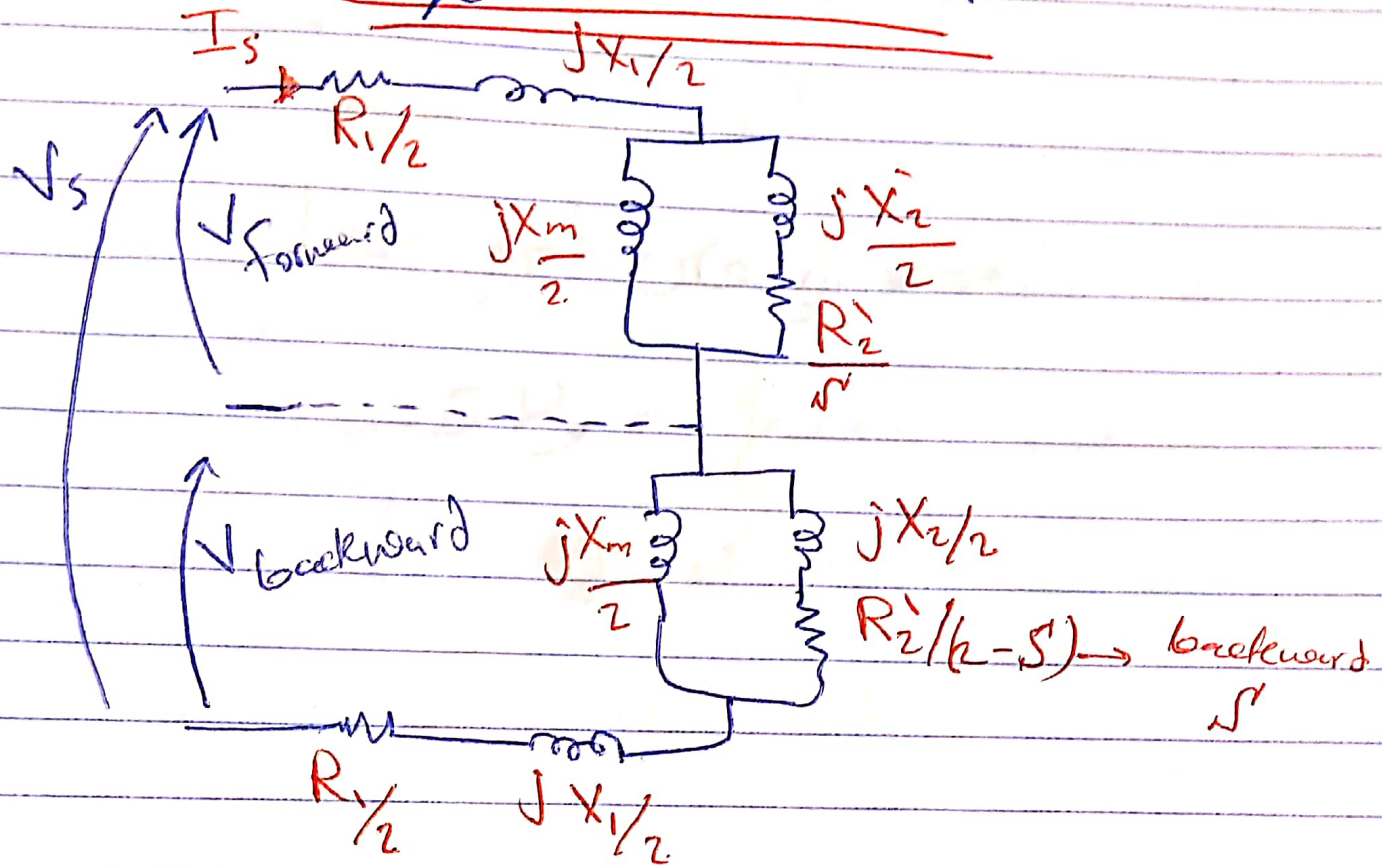

$$V_f + V_b = V_{supply}$$

$$P(f) = I_2'^2(f) \times \frac{R_2'}{s}$$

↓
circuit power

$$P(b) = I_2'^2(b) \times \frac{R_2'}{2-s}$$

$$P_{total}(t) = P(f) + P(b)$$

$$T_g(t) = T(f) - T(b)$$

↘
Waktu (G) (backward)

The End! كل التوفيق

* ساجدوني على أي فطرا ...

ادرسوا صريح ، ولا تنسوني بالديار