

power: High values of current & voltage. (power up to MWs)

- loads are: (Industrial + Transportation) drives



Electronics: High values (kA, kV).

- There is no Amplifier in power Electronics but we over drive.

- Electronic switches with high density semi-conductors.

control: using Micro-controllers to control switches

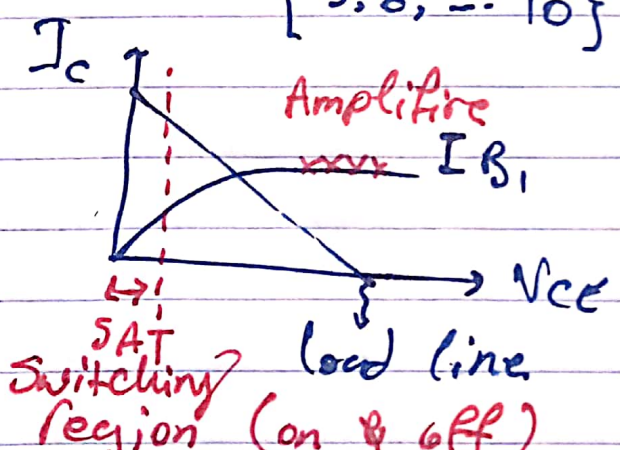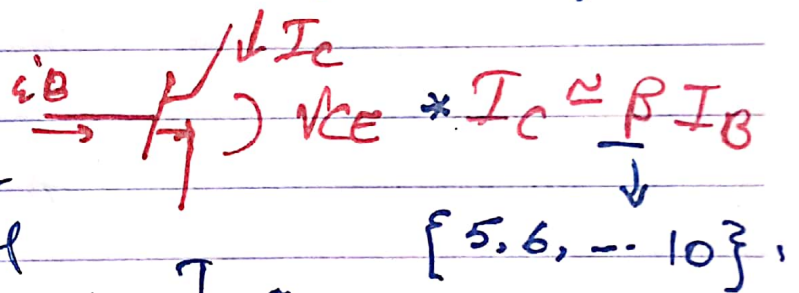
- control Topology:- could be phase delay, trigger, PWM (sin, Uniform, Multipath...)



- For High currents we use Darlington pair.

- control also mean: to apply certain control

Signal Strategy:

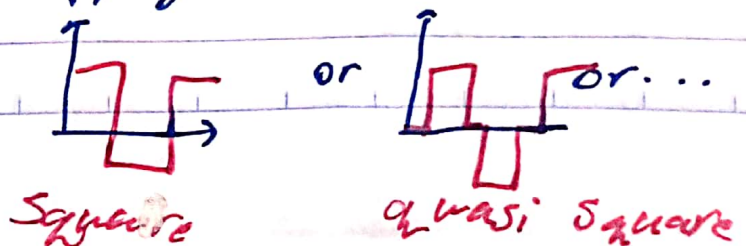

Overall, power Electronics is equivalent to
(power conditioning system)

→ control of the shape of the signal.

→ control of Amplitude

→ Dc : Average.

→ Ac : Fundamental
Component of the signal

(Signal Analysis)

Fourier

→ Frequency control.

Power electronics \equiv Electric power conditioning.

\Rightarrow The main features of the Electric conditioning are

○ Shape or nature $\left\{ \begin{array}{l} \text{Dc to Ac} \\ \text{or} \\ \text{Ac to Dc} \end{array} \right\}$

○ Amplitude $\left\{ \begin{array}{l} \text{Average for Dc \& RMS} \\ \text{fundamental for Ac.} \end{array} \right\}$

○ Power frequency control.

Power conditioning can be accomplished by

converters: Equipment that is capable of changing one or more feature of an electric signal (statically)

\hookrightarrow no rotating parts or elements.

converters are classified into 4 different categories :- (Input \rightarrow output.)


\rightarrow Rectifiers (Ac to Dc converter)

\rightarrow choppers (Dc to Dc converter)

\rightarrow Inverters (Dc to Ac converter)

\rightarrow Ac Regulators (Ac to Ac converter)

* other parameters may change.

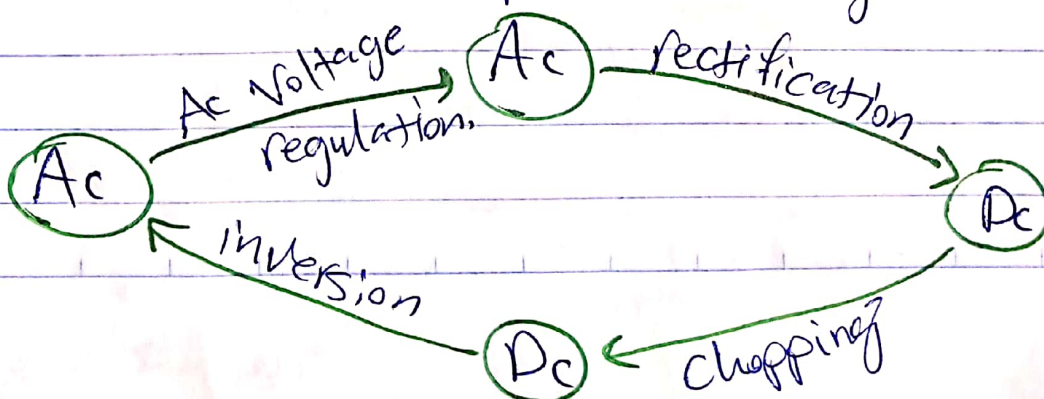

in 1 cycle of AC cycle 1/2 cycle of DC

AC → DC

• Frequency converter

Rectifier:


Required to convert AC into DC with variable amplitudes

• Control DC Motors / loads


• To control motor speed: ① Armature voltage control. \downarrow or the armature to control below rated speed

② Field weakening.

DC voltage control to change the field.

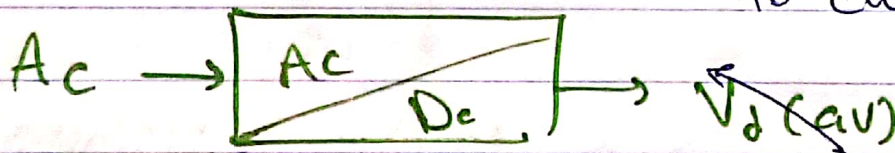

chopping:

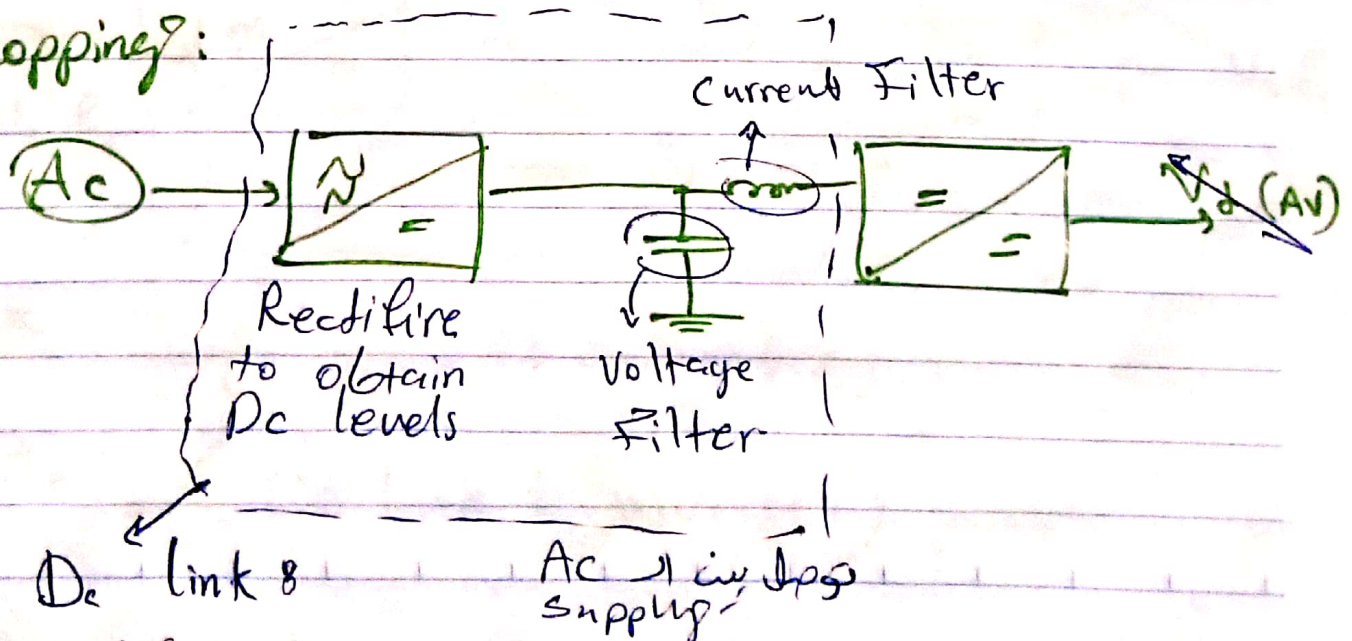

chopper DC

○ If you compare the features, harmonics and the performance; you'll find the chopper circuit with rectifier better than direct rectifier circuit.

○ Rectifier circuit → Harmonics الهارمونيات
3rd, 5th, ...

Chopper → Harmonics الهارمونيات
3rd ↓ i_{g1} 50th **Easier to filter and get rid of**

$$X_c = \frac{1}{2\pi f c}$$


$f \uparrow, c \downarrow$

الوزن والكم
والسعة اقل

$$X_L = 2\pi f L$$

$f \uparrow, L \downarrow$

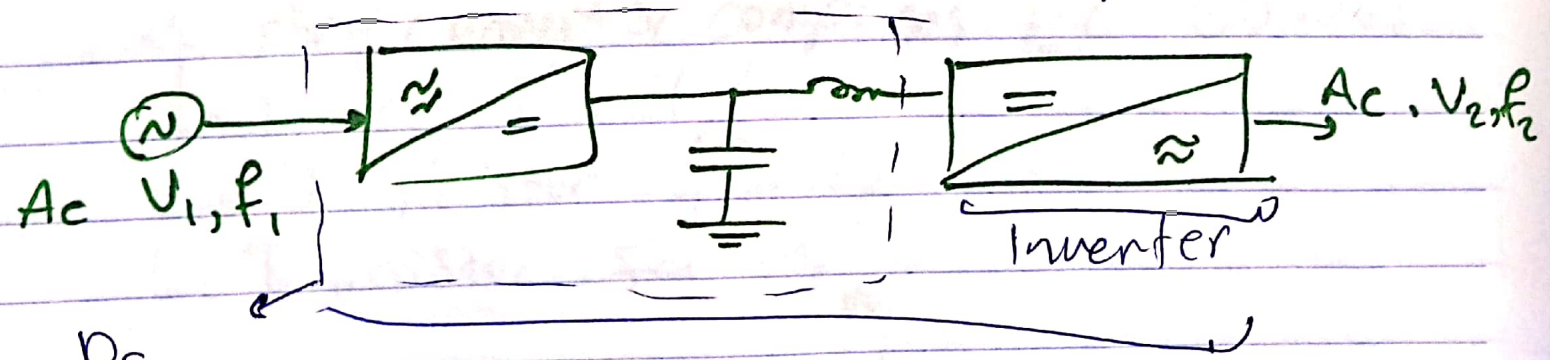Inverters: is not an exact frequency converter



Dc link.

→ frequency converter:

(Dc link + inverter)


→ Rectifiers Applications: Dc loads (Dc Motors)
+ Choppers

→ Inverters Applications: (1) Frequency control
(with Dc Link)

The speed & starting current of Ac Motors.

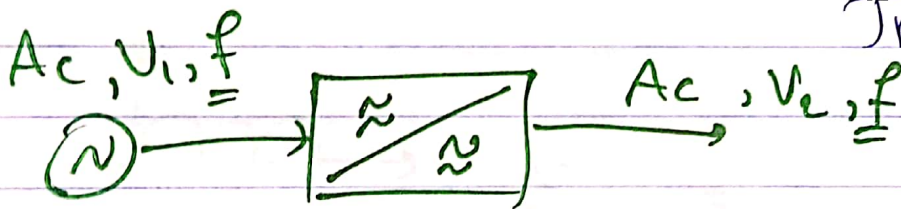
(2) PV systems: Dc (pv) → Ac (network)
کشیو اچه
آسیو اچه

Ac Voltage Regulation: (Static or Semiconductor)
Transformer
or
power Electronics
Transformer.
Without affecting the Frequency. (RMS control)



switches Any converter comprises P.E^{lectronics} switches
Diode Family
Thyristor Family
Transistor Family

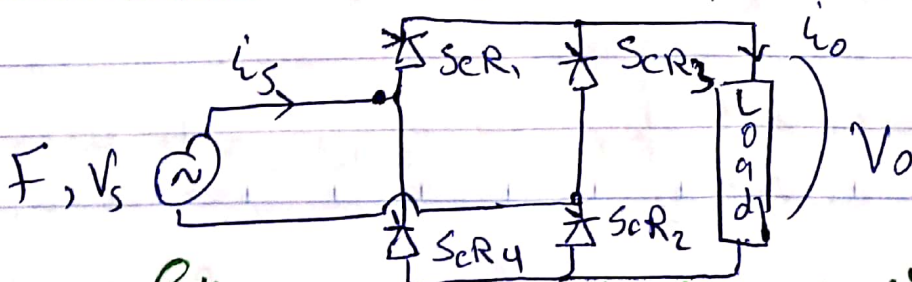
Combination of these elements means converters.



fully controlled Bridge rectifier.



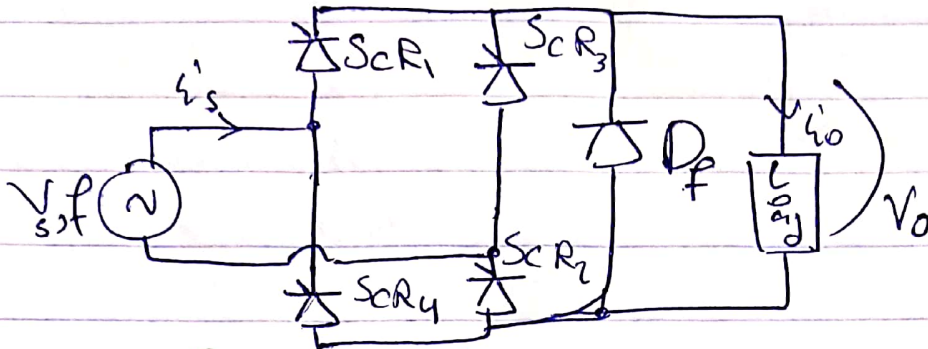
Thyristor is diode with control, silicon controlled Rectifier (SCR)




Single phase Semi-controlled bridge Rectifier.

Uncontrolled diodes as in a bridge rectifier

o Before, loads were R_L resistive load.

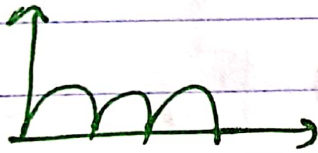

o Now, NOL Inductive load

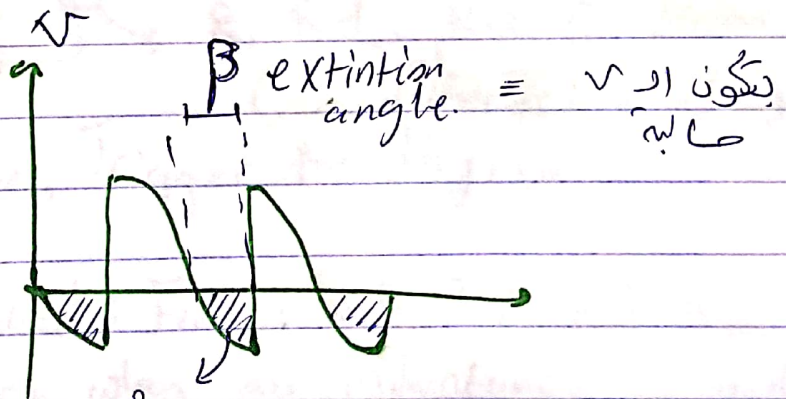

پس اس لیے (کاربی) لا اسی، تا
بصیر یگون حالت

4
F.W, running & Breaky
R.V, running & Breaky

اذا بری ری
بری اکیڑ اس لیے


وینیل اس لیے

26/9/2019

Transistors + diodes.


Lecture 5

Choppers: Basic chopper → class A.

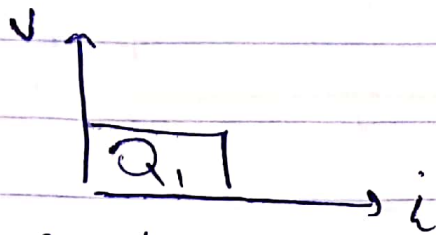

Quadrant number 1

Q₁ → class A

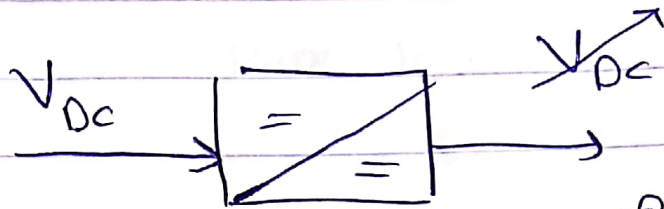

من الممكن


AV_{DC} value.

needs Dc supply

→ Batteries

→ Dc generator

→ Ac supply + Rectifier circuit

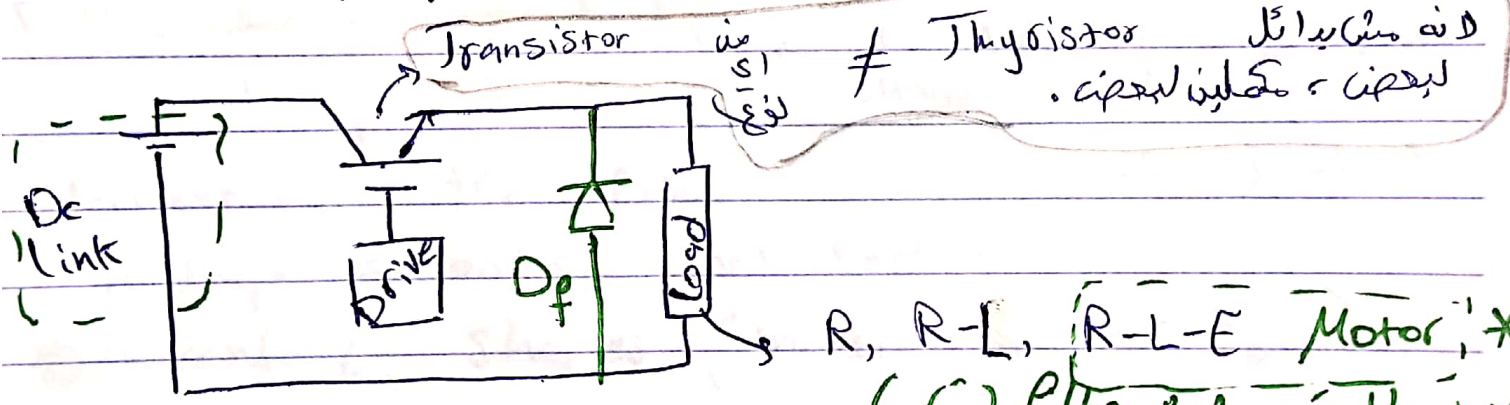


R, R-L, R-L-E Motor, *
(, ω) filter L + ωL, ωC *

Drive for transistor, Trigger for Thyristor.


Df ⇒ A must (called: Free wheeling diode) to protect the main switch when an inductance is involved in the circuit. pure resistive load لا يحتاج الى كبح

Safety & protection of the transistor and diode. destructive. لا بد من وجوده حتى لا يكون

Typical waveforms.

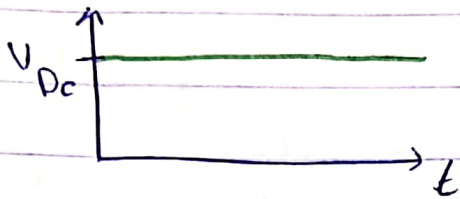


Pure dc.

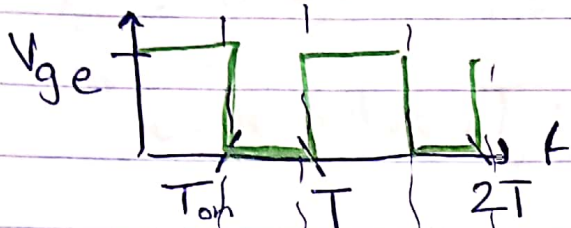

control circuit / Drive. (تدوير)

→ control signal (must be periodic)

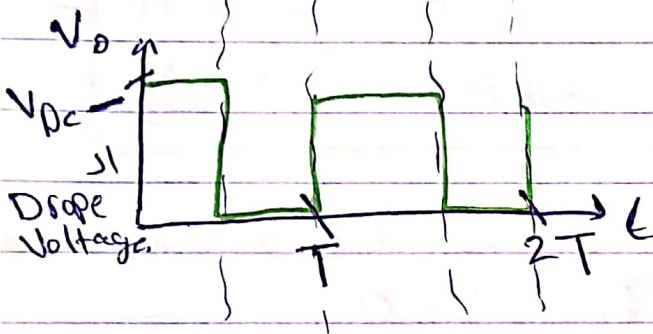ليس complex شكله اذ هو periodic في كل 1/1 ثانية





output voltage signal

• period. 1 +

In most cases the output voltage = control signal chopped.

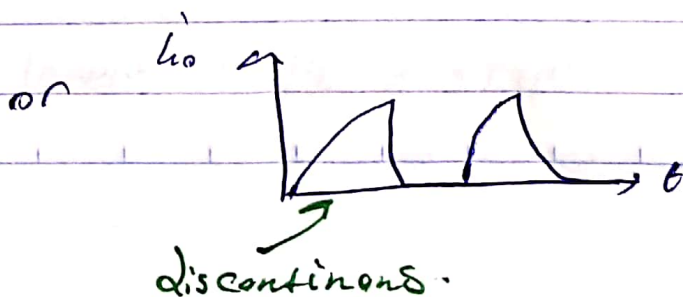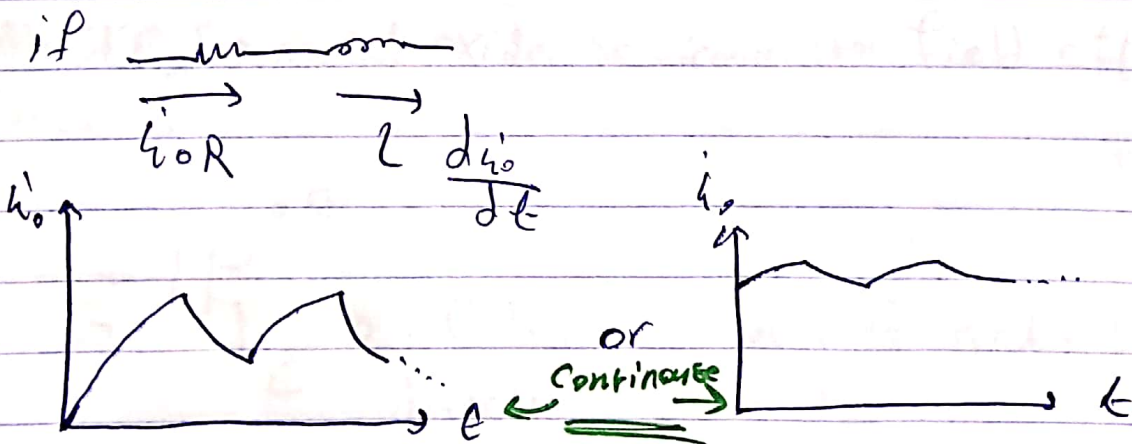⊙ Current i_o shapes: (inductivity of load) L $\frac{di_o}{dt}$



Control parameter: δ Modulation Index

$$\delta = \frac{T_{on}}{T}, \quad f_{chopper} = \frac{1}{T} \rightarrow f_{ch} : \text{chopping Frequency}$$

$$f_{ch} = 50 \text{ Hz}, \quad T = 20 \text{ msec.}$$


$$f_{ch} = 1000 \text{ Hz}, \quad T = 2 \text{ msec.}$$

period from drive circuit to decide chopping frequency.


$$\rightarrow 0 \leq \delta \leq 1$$

$$\delta * V_{DC} = \text{AVG Voltage} \rightarrow \text{we apply this variable DC-voltage}$$

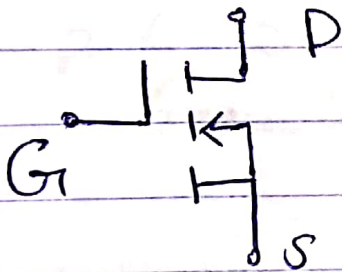o Inverters: δ is power electronics
DC-Generator.




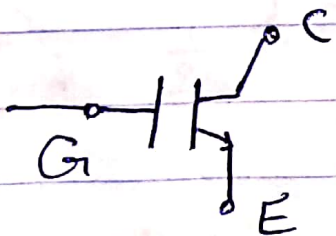o MOSFET: metal oxide semiconductor field effect Transistor.



o IGBT: Insulated gate Bipolar Junction Transistor.

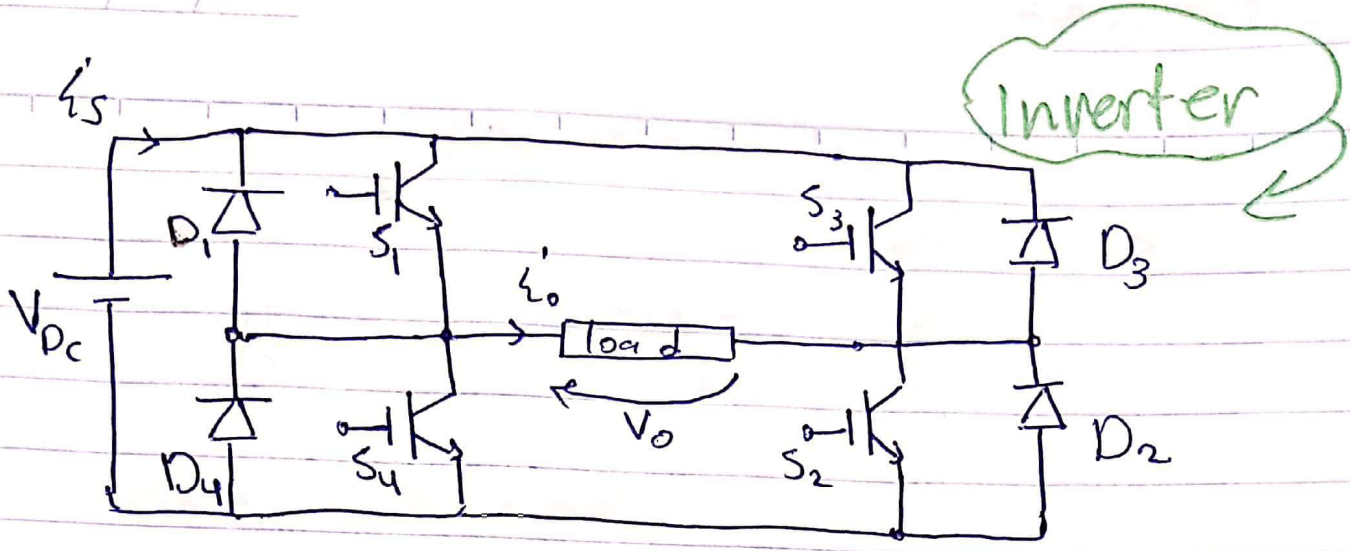o Inverter: Use any type of transistors \neq Thyristor.



Convention. all pipes are inward *

Back-to-Back Diodes *

Free wheeling diodes

Dc-supply is not diode free

or no

Feed back diodes

Supply is power is not free

→ path S₁, D₃ & load:

Free wheeling → is not free supply.

→ path D₃, Supply & D₄, load.

Feed Back.

⊗ If diodes are not included → is not free supply.

$$P_{\text{Inductor}} = \frac{1}{2} L I^2 \rightarrow$$
 is not free supply.

Transistor is not free supply.


Inverter's Applications:

① Variable Frequency. to control motors. $N_s = \frac{60 f}{P}$

② PV, UPS System uninterruptible power supply. (Fixed Frequency)

Ac Voltage Regulator.

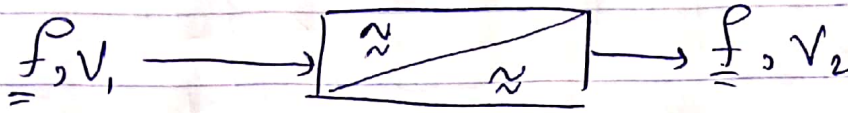
Power transformer, Static or Semiconductor Transformer



① Phase Angle Control

We change the RMS voltage at a certain frequency
Fixed


→ Ac switches are used.

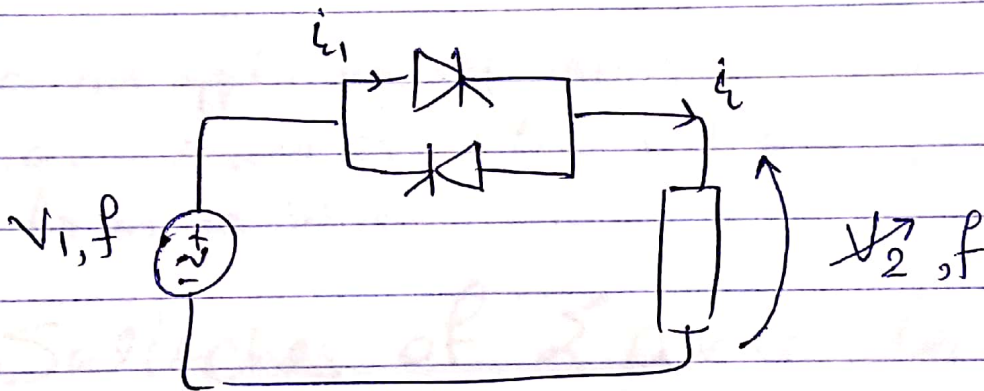


→ Full output

Zero output ←

$$0 \leq \alpha \leq 180$$

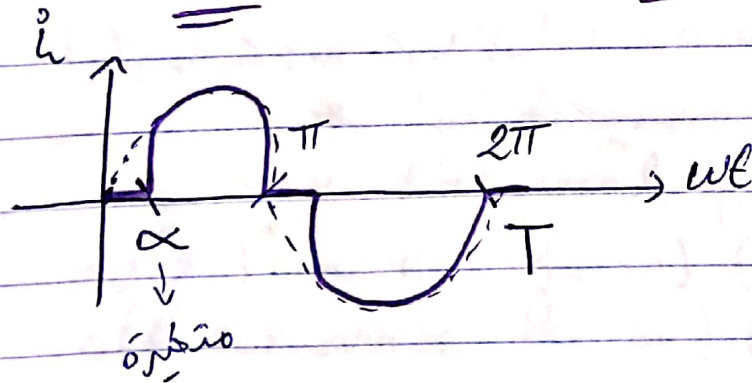

② on-off control

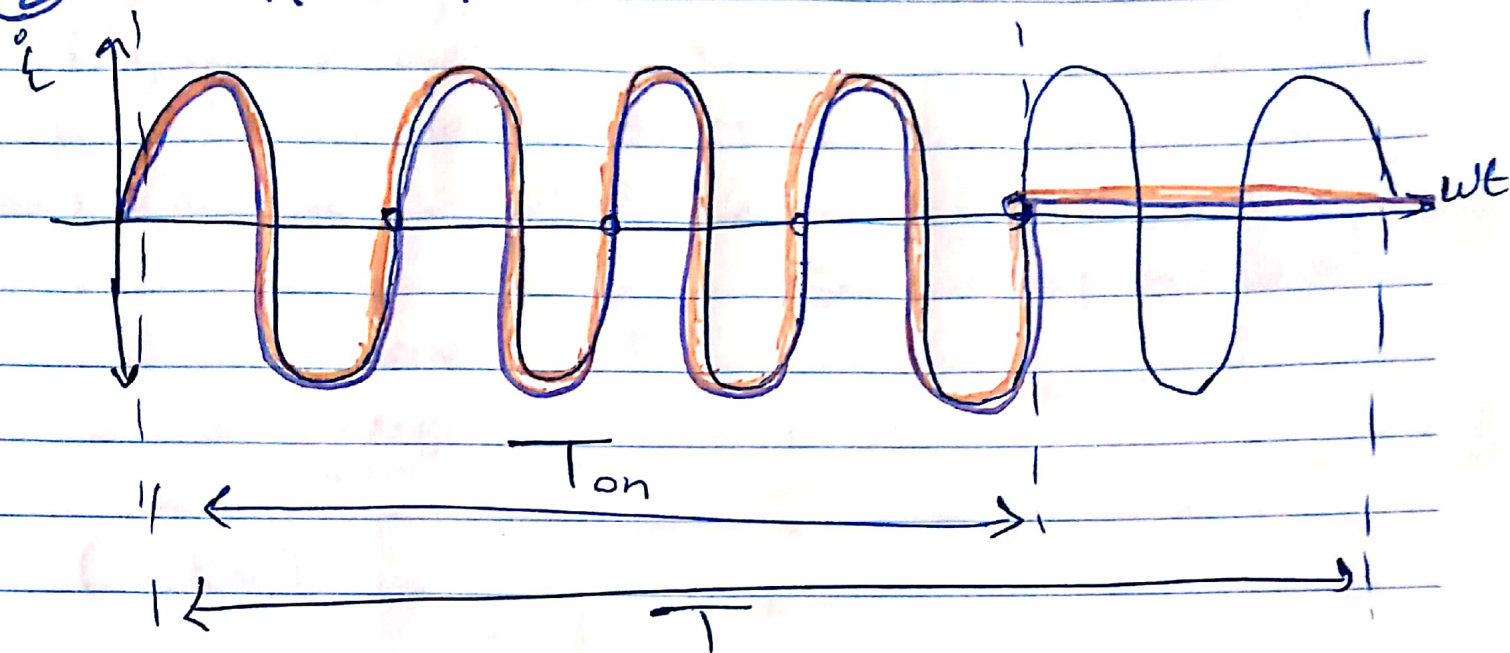


on-off control applications: Lighting, Motor limit Switch.
Triac: works on low voltage/power.
↳ an ac switch

Switches of power electronics

- ① Diodes
- ② Thyristors
- ③ Transistors.

Diodes: * switches on/off up to 400 Hz
* low frequency applications.
* General purpose diodes.


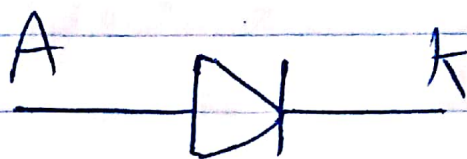
on: Forward Biased (FB)
off: Reverse Biased (RB)



* Fast recovery diodes : * Medium to high frequency applications.

(ex: choppers, inverters ---)

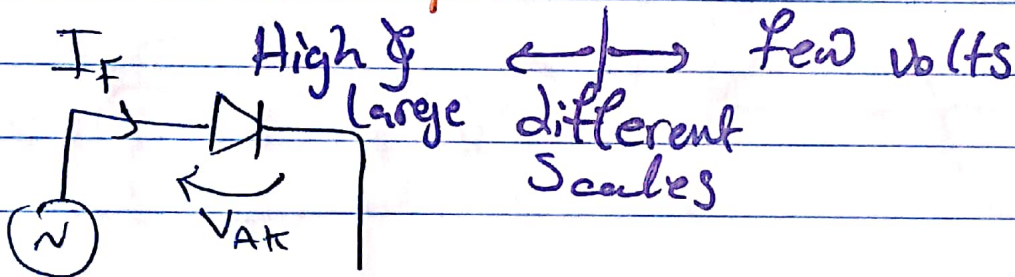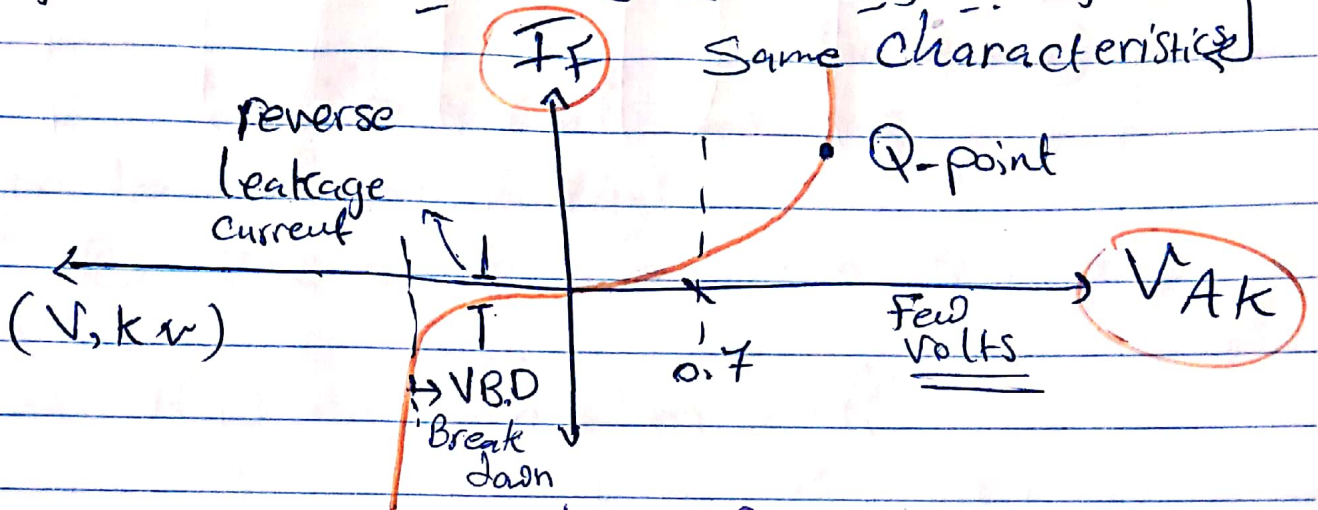... I_F V_{AK} diode ... Same characteristics



$V_s = V_m \sin(\omega t)$ usually $V_m = V_{AK}$

S.F = (2-3) * rated voltage

Safety Factor

Thyristors older than transistors (1975-2000)

- ↳ SCR (1975) Silicon controlled rectifier
- ↳ MCT (2000) Mos-controlled Thyristor


- Diodes → no control
- Thyristors → control (Ac → Ac) or (Ac → Dc)
- Transistors → control (Dc → Dc) or (Dc → Ac) From rectifier

Classifications of switches.


In terms of controllability

① Uncontrolled on, Uncontrolled off
Diodes

⇒ How to turn it on or off ...

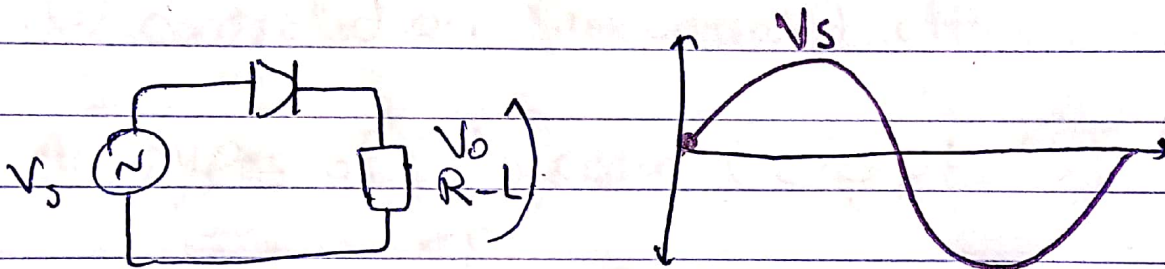

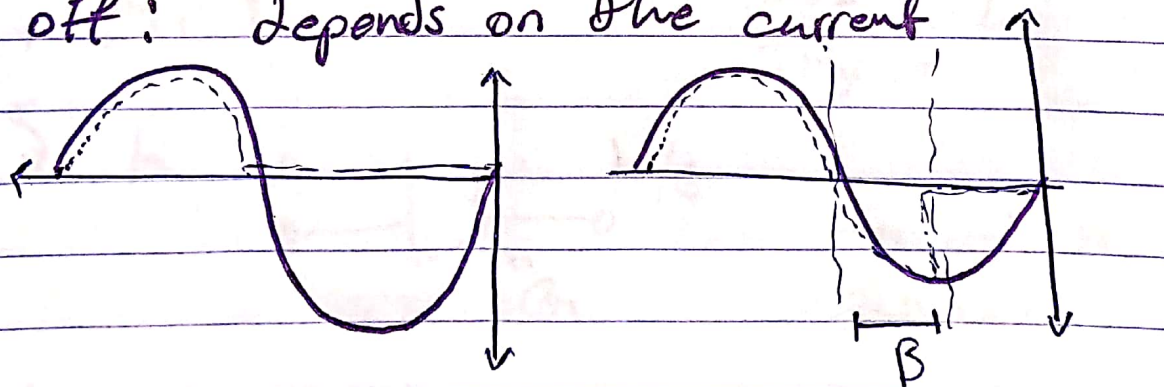on : starts when it's Forward Biased.
off : depends on the current




resistive

inductive load

Extention Angle β : depends on inductivity
 $\tau = \frac{L}{R}$

o For Thyristors α : زوایه الفی

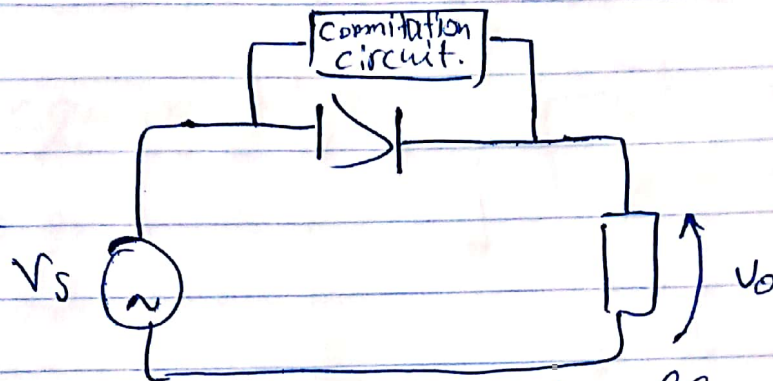To stop the diode from working, we add a commutation circuit.



ⓑ controlled on, & uncontrolled off.


All types of Thyristor (except GTO)

Thyristors


→ SCR, TRIAC, GTO, SIT, LASCR, MCT.

Static induction Thyristor
light active Silicon controlled rectifier

SCR

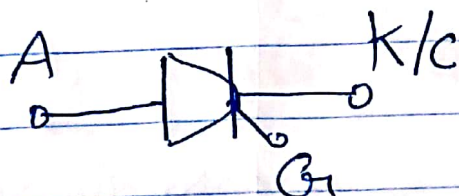


terminals 3
be use

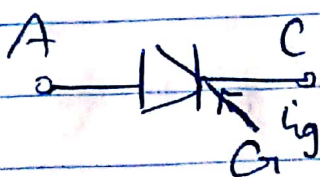


I_g : control current

(-v) feedback

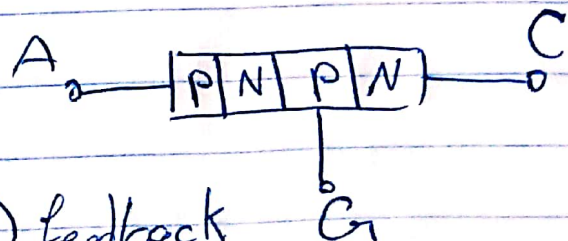


TRIAC (Ac switch) // Triode for Ac

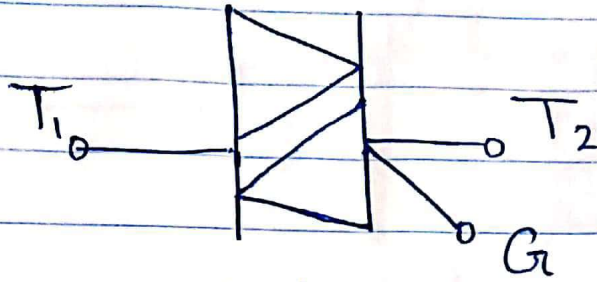

TRIAC equivalent :

↳ TRIAC البا
بجالة
Low power
Low voltage

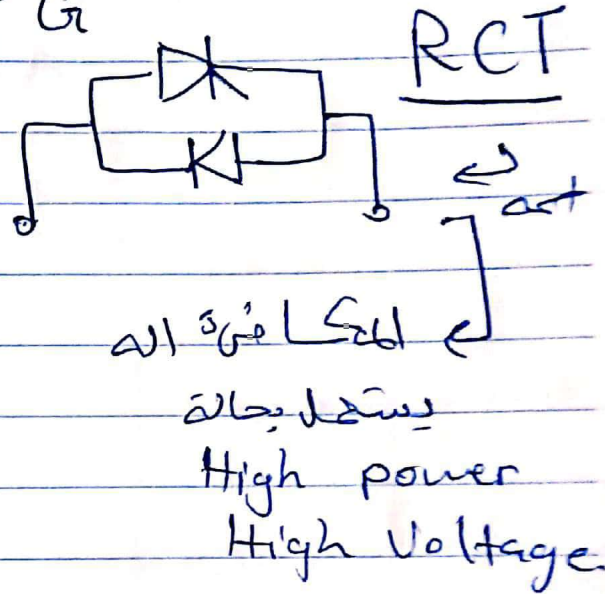



GTO gate turn-off Thyristor.
↳ for large power applications.





bidirectional

gate disadvantage → $i_g(\text{off}) \gg i_g(\text{on})$
A's mA's

o you need two control circuits. بجالة

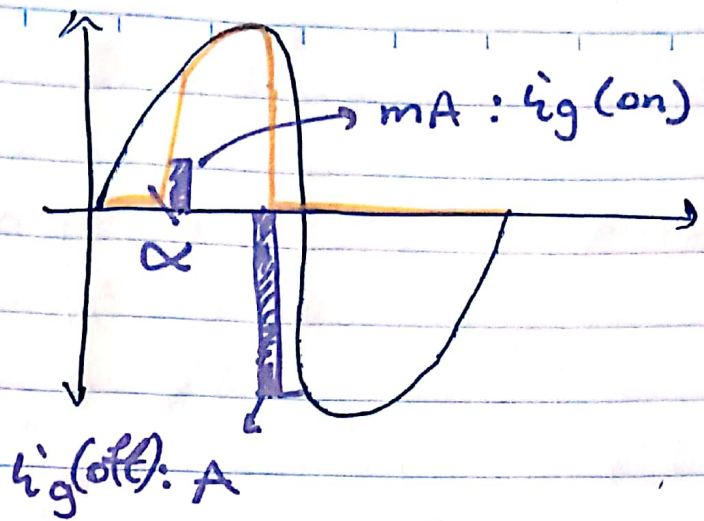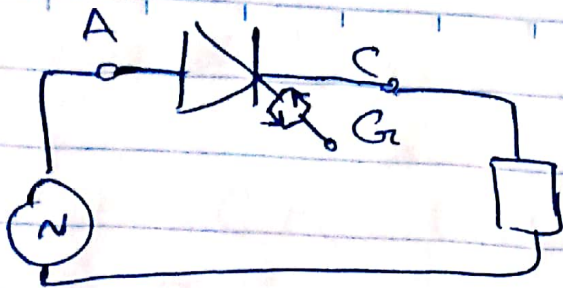

GTO vs. SCR

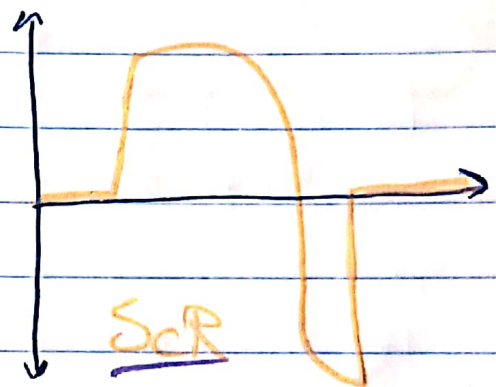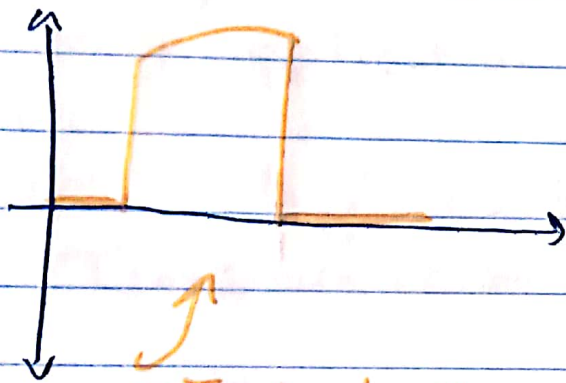


GTO is better

o Small positive gate current is required to switch GTO on

o Large negative gate current is required to switch GTO off

Controlled on, uncontrolled off

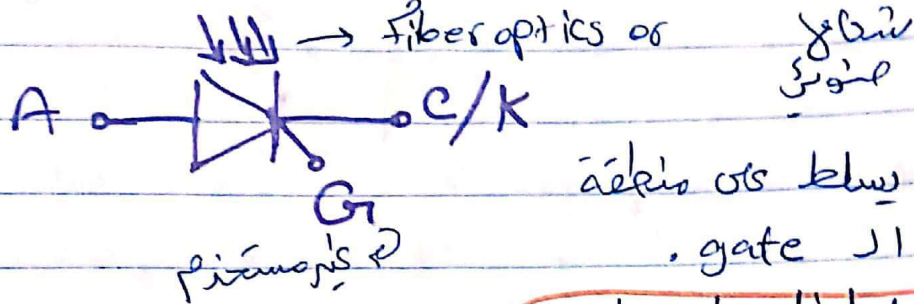
LASCR ^{Thyristor} light activated Silicon controlled rectifier.



* Very high voltage application.


excited by light not gate current.

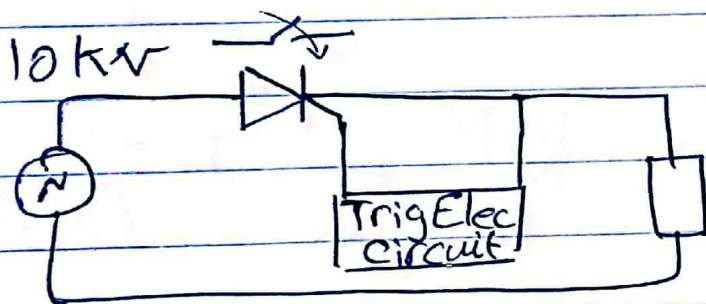HVDC T: high voltage Direct current Transmission.



10kV 11 Triggering 11 10kV electric circuit.


SITH Static Induction Thyristor.

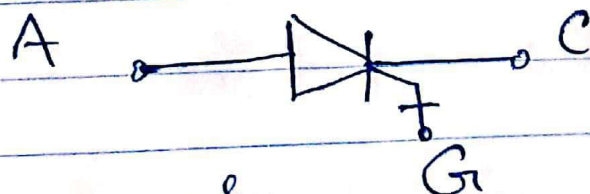

* Higher frequency applications, More than GTO or SCR → up to 50 kHz.

MCT



Mos-controlled Thyristor.

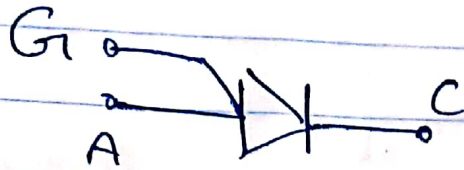

to drive this switch, we apply negative gate with respect to the anode.

charge controlled all previous Thyristors except for MCT

Voltage controlled

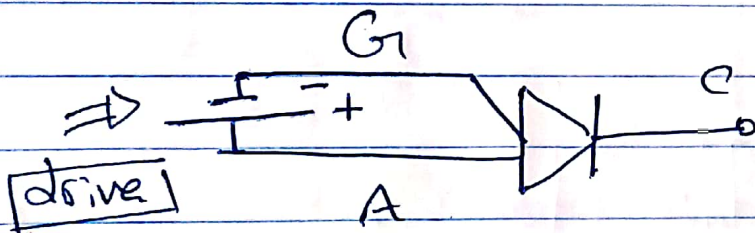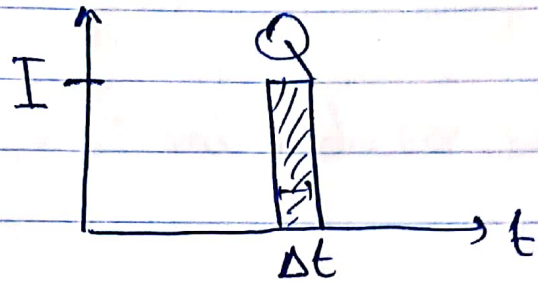


* up to 80 kHz, 2 kV, 2 kA


(c) controlled on, controlled off. (all transistors)
GTO, BJT, MOSFET, IGBT

BJT: Bipolar Junction Transistor.

↳ Base current control.

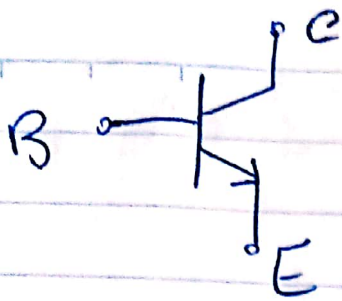

* Usually used in Darlington Form.

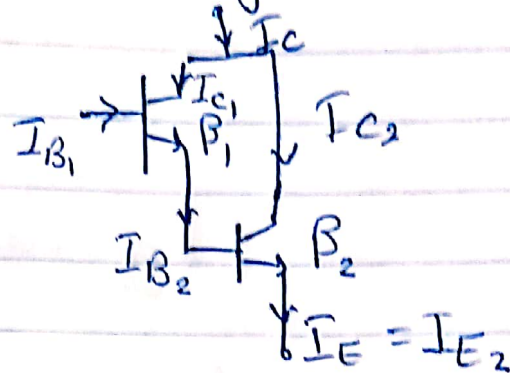


$\beta = \beta_1 \times \beta_2$
↓
in power
is $\approx 10^4$

* up to 10 kHz
(w/sg, vbi)

* up to 800V & 600A

* Disadvantage: current controlled.

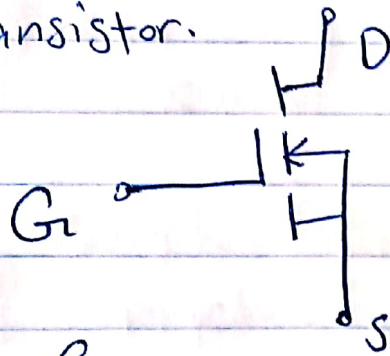
MOSFET: Metal oxide Semiconductor Field Effect Transistor.




* This is the fastest switch out there!

* Voltage controlled, up to 1 MHz, low power
~> Switching Speed $\frac{1}{\alpha}$ power capability

* up to 1200V, 800A

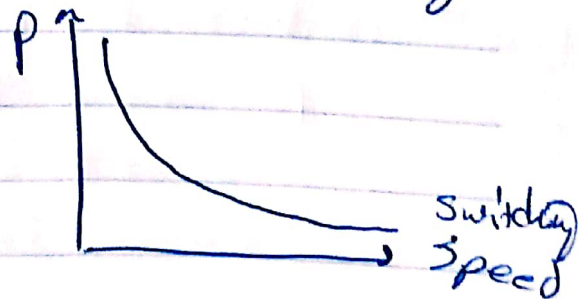

IGBT: Insulated gate Bipolar Transistor

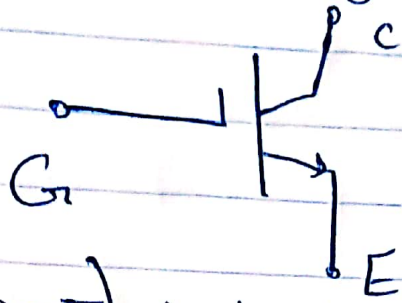

- * (MOSFET + BJT) technology.
- * voltage controlled
- * 100 kHz, 2.5 kV, 2 kA.

Classification of switches

|| In terms of the nature of the control signal.

- Ⓐ Latching switches (triggered)
- Ⓑ Continuous switches (drive)


if asked to design

- Ⓐ Rectifier: SCR
- Ⓑ Chopper/ Inverter: IGBT

Latching switches: (all Thyristors)

- small, short signal is applied to switch on or off
- when the triggering signal is removed, the switch continues conduction.

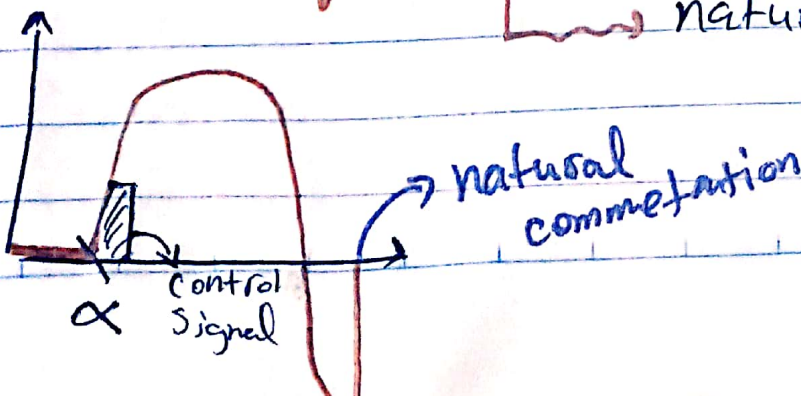Ⓐ **Switching off** → forced commutation.
→ natural commutation.



Continuous Switch. \rightarrow (all Transistors)

Drive signal:

- If on \rightarrow Switch is on.
- If off \rightarrow Switch is off.

Classification of switches

1) In terms of voltage withstanding capability \neq Amplitude.

↳ polarity of the input voltage.

① Bi-polar.

② Uni-polar.

Bipolar: Ac applications.

⊗ Rectifiers + Ac Regulators
all SCR's & Thyristors are Bipolar switches except for GTO.

↓ could be bipolar
(Special GTO)

Unipolar: used in inverters + Choppers.

↳ all Transistors.

2) In terms of current withstanding capability
↳ Direction!


① bidirectional TRIAC, RCT \neq polarity

② unidirectional all remaining switches


RCT = Reversed conducting Thyristor.
 ↳ also called: Thyristor
 (Thyristor + diode)

○ For AC Voltage control.
 (resistive loads)

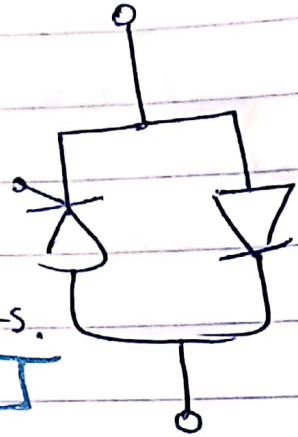
○ Unsymmetrical, cause Dc components.
 burns motors. ↴



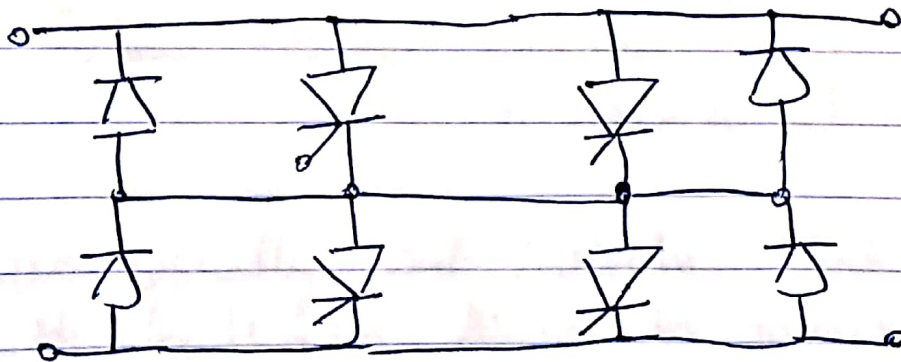⊗ Inverters ↴
 (Before power transistors)




feedback of
 freewheeling
 Diodes.

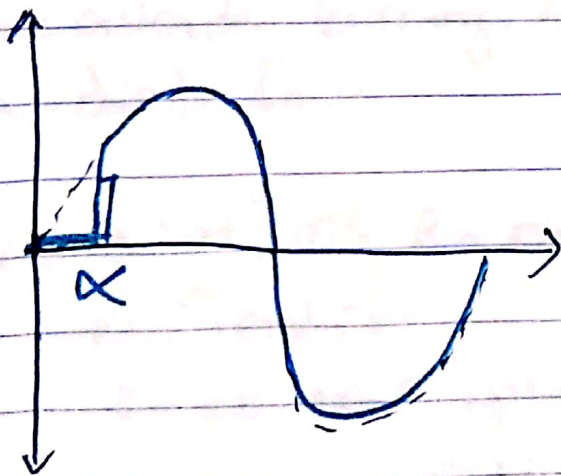

So we said that all other switches are directional ... There are Exceptions

Exception Bi-directional MOSFET

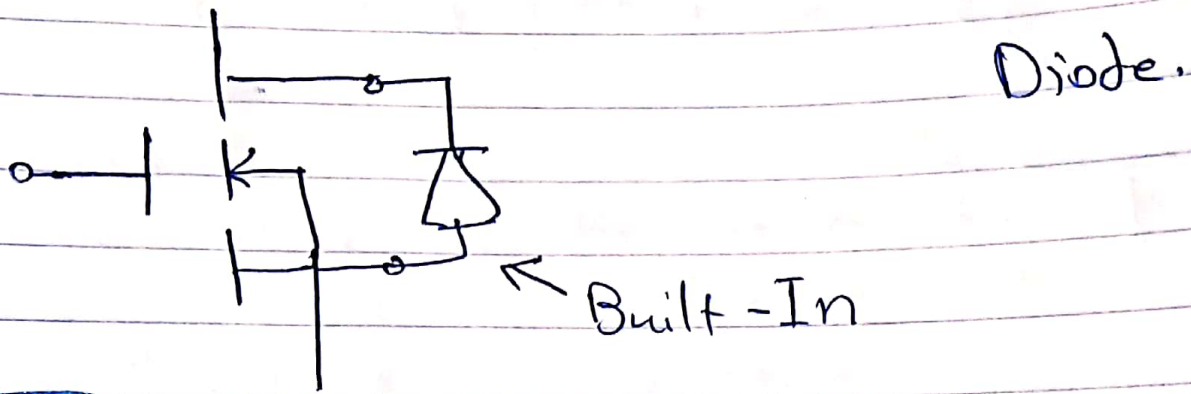⊛ this MOSFET is a module, بكونها لا يكون
 منه



Note: MOSFET Module انها لا يكون
 منه , diode انها لا يكون
 منه bi-directional.

⊛ we usually put switches that are moduled with built-in diodes in inverters (why) to avoid burning the entire inverter when a diode fails.

Applications for power electronics.

- o Services
- o Power Supplies (rectifiers + inverters + Batteries)
ex: (UPS) $\text{uninterruptable power supply}$. Used on critical loads & loads in which cannot accept any power stoppage (e.g. Data centers, hospitals, industrial...)

Power systems: (AC Voltage regulators)
ex: (SVARC): Static Var compensation.
↳ for power factor correction

ex₂: Static voltage regulators \equiv Static tap changers

ex₃: (HVDC): High Voltage DC Transmission.
(to be addressed later)

used: ↳ ● when connecting to networks with different frequencies. (eg. USA & Canada)

● When transmitting power for very long distances. (greater than 500km)

● geographical obstacles.
(eg. English channel between UK & France)

Industrial Applications:

- Industrial heating
- Electric Motor Drive: motors consume up to 70% of total power consumption.


Merits & Drawbacks

Advantages

Disadvantages.

Ex: conventional:

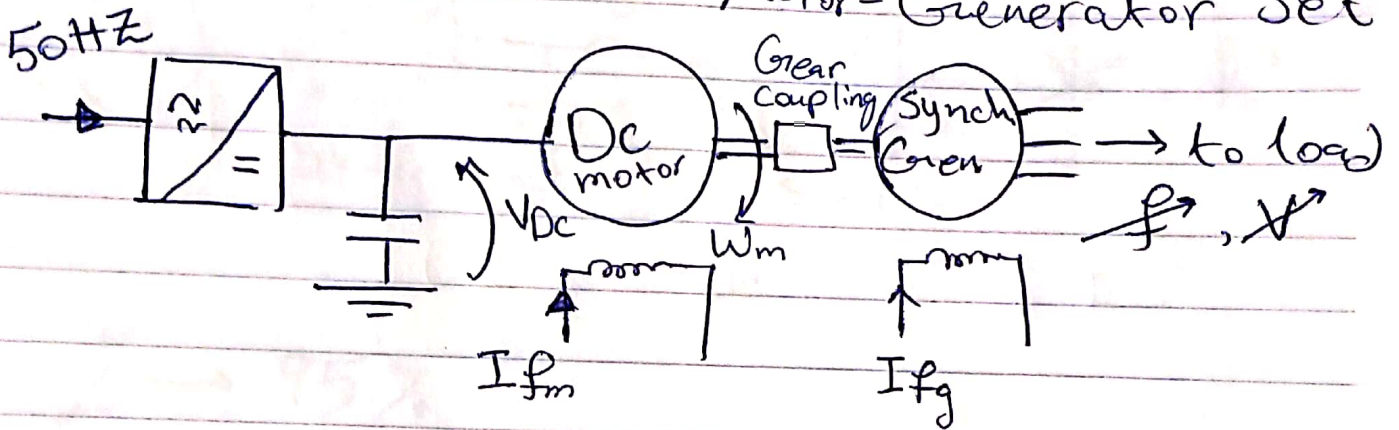To convert frequency we used (M.G) Motor-Generator Set



Frequency controlled by N_m control.

$$N_m = \frac{60f}{p} \rightarrow f = \frac{p}{60} N_m$$


N_m controlled by ① V_{dc} control
for $0 \leq N_m \leq N_m(\text{rated})$

② I_{fm} (field weakening control)
for $N_m(\text{rated}) \leq N_m \leq (2-3)(N_m \text{ rated})$
(. (10/10) 3-2))

Output Voltage controlled by controlling I_{fg} (synchronous), $V \approx 4.44 N_{ph} \cdot \phi_p \cdot f$
(Generator field)


Cont. from past lecture

⊗ Power Electronics Alternative.

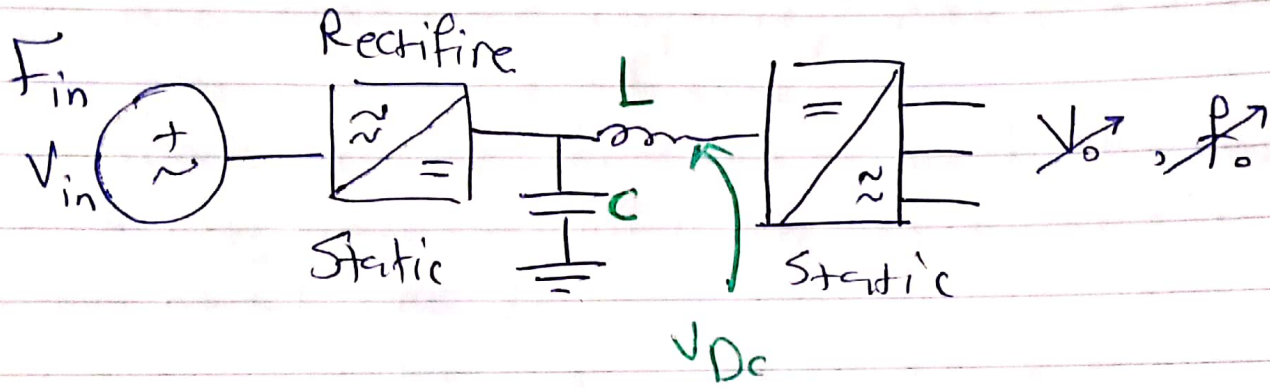

$\eta \rightarrow 95\%$

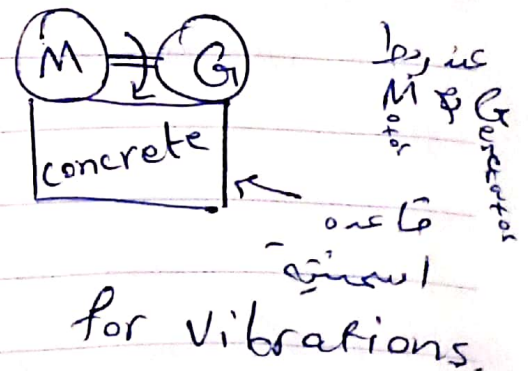- Benefits:
- 1] Much lower capital cost.
 - 2] Much higher efficiency ($\approx 95\%$ compared to $\approx 50\%$), lower running cost.
 - 3] Maintenance-Free
 - 4] Much easier control (very high controllability capabilities).
 - 5] less weight, size, and space.
 - 6] No special foundations.
 - 7] lower acoustic noise.



① Power Electronics Disadvantages (Drawbacks)

Compared to conventional counterparts.

III No over-load capacity even for a very short period of time.


Explain \rightarrow (converters are designed to match the maximum power required even if it happens for very short period of time.)

Ex


Starting a motor \rightarrow the starting current $\approx 20 I_{rated}$
So the power at the beginning is very high but the case is for a very short time, the motor will not heat up this fast. as for P.E, once a higher current value passes through \rightarrow it will burn down.

\rightarrow we must over-size the P.E
unjustified cost.

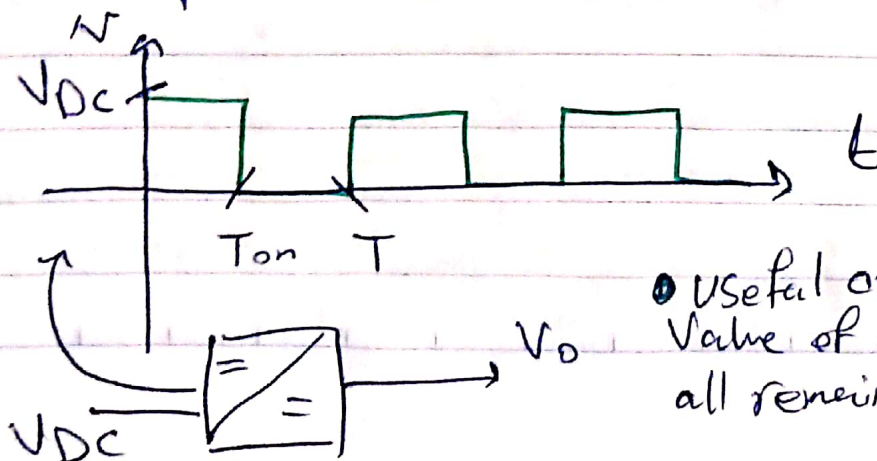② Harmonics Generation: usually voltages and currents of P.E are not ideal (not pure Dc or pure sine) \Rightarrow distorted waveforms



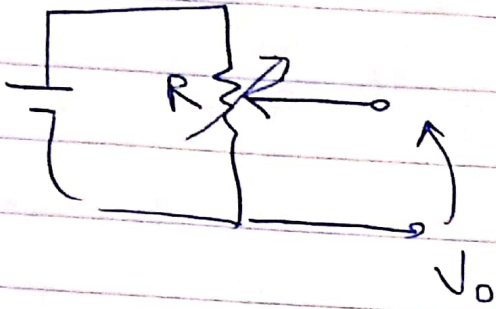• Useful component is A_{dc} (AVG) value of the signal.
all remaining are impurities.



إذا بيدي في pure ديجا
 على على على على على على
 losses)

$$V_o(t) = \begin{cases} V_{DC} & , 0 \leq t \leq T_{on} \\ 0 & , T_{on} \leq t \leq T \end{cases}$$

$$V_o(t) = \underbrace{V_{avg}}_{\text{Useful part.}} + \underbrace{\sum_{n=1,2,3,\dots}^{\infty} V_m(n) \sin(n\omega t + \psi(n))}_{\text{Impurities}}$$

$$V_{avg} = \delta \cdot V_{DC} = \left(\frac{T_{on}}{T} \right) \cdot V_{DC}$$

modulation index

(or)
 Time - to - Space Ratio
 duty cycle.



accurate.

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^{T_{on}} V_{DC}^2 dt} = \sqrt{\delta} \cdot V_{DC}$$

$$\delta < 1 \rightarrow V_{rms} > V_{avg}$$

$$V_{rms} = \sqrt{V_{avg}^2 + \sum_{n=1}^{\infty} \left(\frac{V_m(n)}{\sqrt{2}} \right)^2}$$

approximate

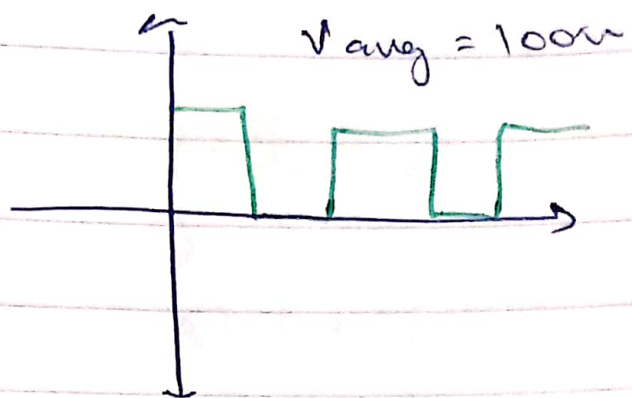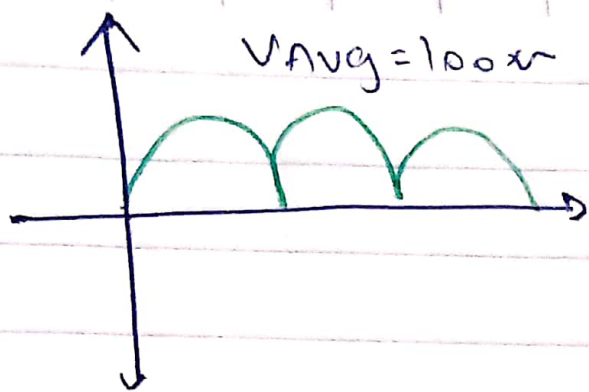


which one should we choose?


→ according to the ripple factor

Fundamental @ $n=1$ ∴ same as supply frequency
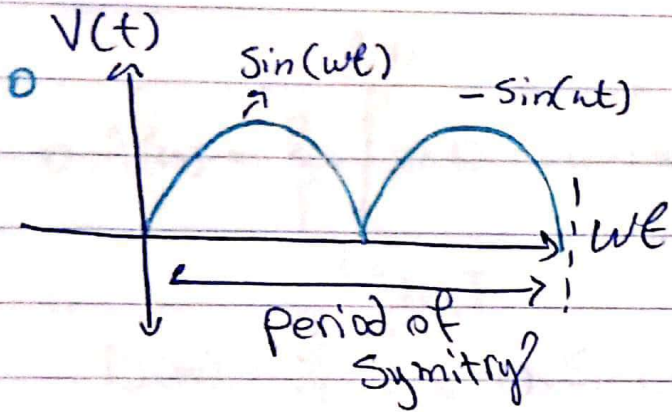
$$V(t) = V_{avg} + V_m(1) \cdot \sin(\omega t + \psi(1)) + V_m(2) \cdot \sin(\dots + 2\omega t + \psi(2)) + V_m(3) \cdot \sin(3\omega t + \psi(3)) + \dots + \dots + V_m(n) \cdot \sin(n\omega t + \psi(n)) \dots \infty$$



$$V_{avg} = A$$

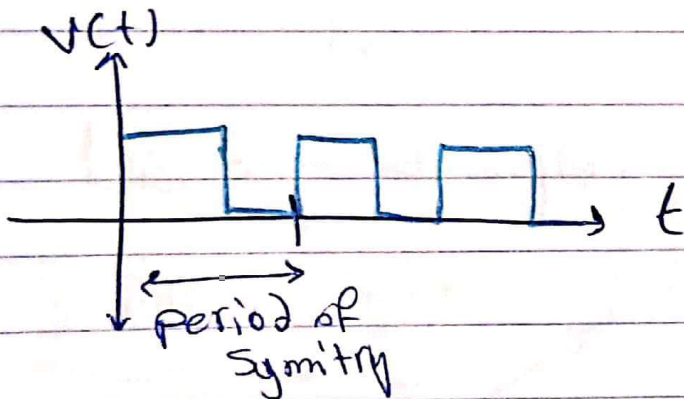


$$V_{avg} = A$$

- when our signal is sine or cosine radians. ωt or $\omega t + \psi$
- if the signal is not sine nor cosine seconds. t or $t + \psi$

period of symmetry odd (Harmonics) \rightarrow $\frac{1}{n}$ of the period of symmetry \rightarrow $\frac{1}{n}$ of the period of symmetry \rightarrow $\frac{1}{n}$ of the period of symmetry

even Harmonics.
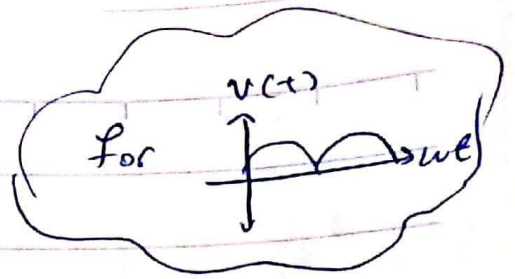
$$V_{avg} = \frac{1}{T} \int_{t_0}^{t_0+T} V(t) \cdot dt$$



$$V_m(n) = \sqrt{A(n)^2 + B(n)^2}, \text{ A \& B are Fourier coefficients}$$

$$A(n) = \frac{2}{T} \int_{t_0}^{t_0+T} V(t) \cdot \cos(n\omega t) dt$$

[or]
Euler coefficients.


$$B(n) = \frac{2}{T} \int_{t_0}^{t_0+T} V(t) \cdot \sin(n\omega t) dt$$

Displacement angle
[or]
phase shift

$$\psi(n) = \tan^{-1} \left(\frac{-B(n)}{A(n)} \right)$$

○ when $B(n) \rightarrow \sin$
 $A(n) \rightarrow \cos$
↳ $\sin/\cos \rightarrow \tan$
When $B(n) \rightarrow \cos$
 $A(n) \rightarrow \sin$
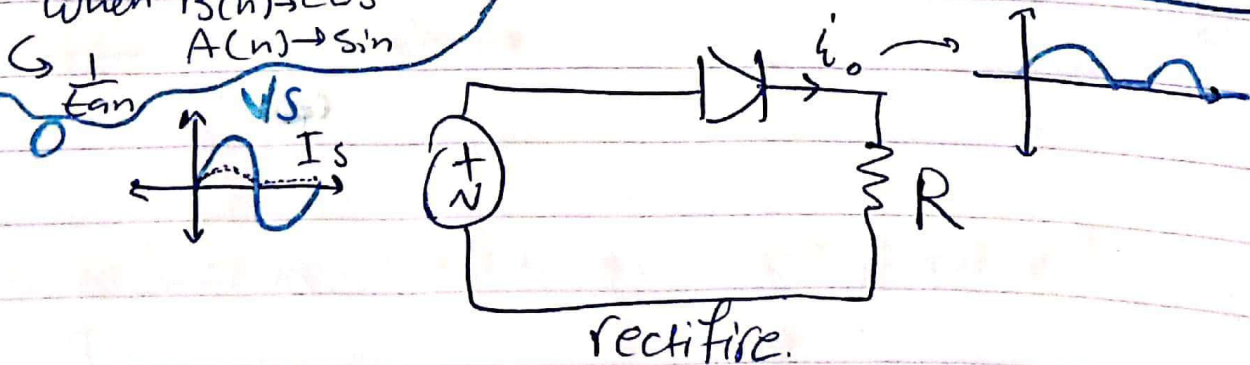
$$\psi(n) = \tan^{-1} \left(\frac{A(n)}{B(n)} \right)$$




→ Power factor & load phase angle $(\phi) = \tan^{-1} \left(\frac{\omega L}{R} \right)$

$$V_s(t) = V_m \sin(\omega t)$$



$$i_s(t) = I_{avg} + I_m(1) \cdot \sin(\omega t + \psi(1)) + I_m(2) \cdot \sin(\dots - 2\omega t + \psi(2)) + I_m(3) \cdot \sin(3\omega t + \psi(3)) + \dots$$

Original definition of power factor

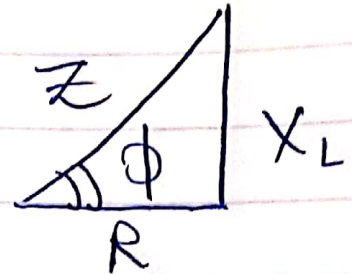


$$PF = \frac{\text{Real power supplied by the source.}}{\text{Apparent power supplied by the same source.}}$$


Resistive load power

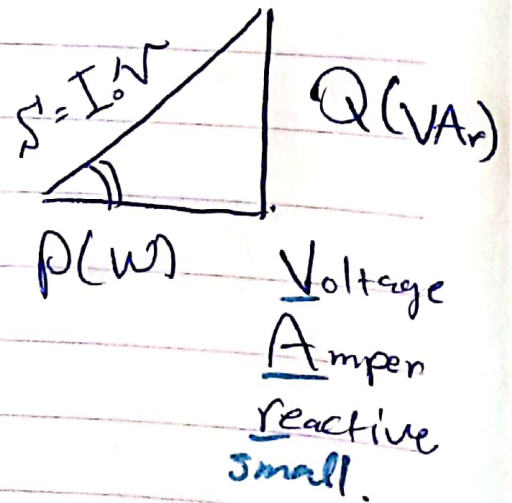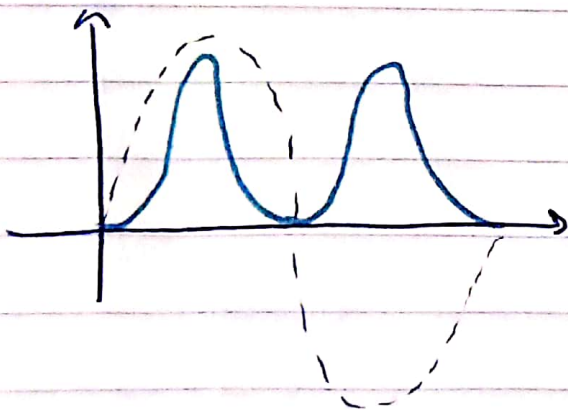


Inductive load power

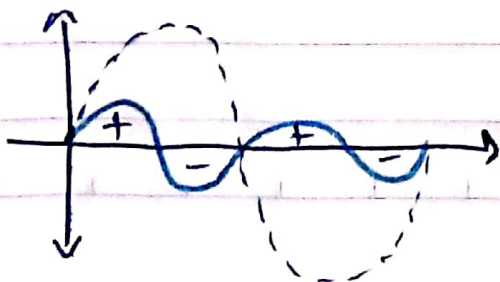

capacitive load power

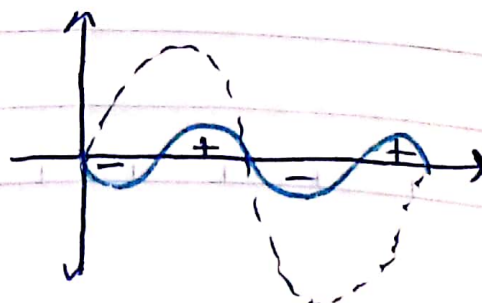


o R-L load power

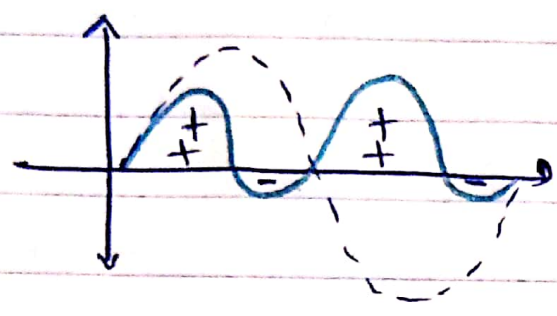

for power we use $2\omega t$
 frequency $\cos \phi$.

Special case

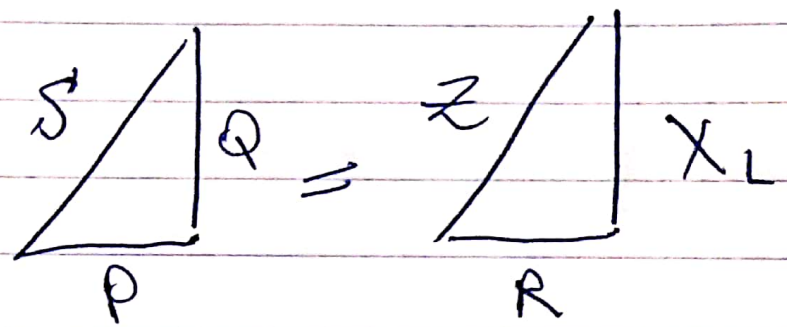

Current i , Voltage v are sinusoidal.
 pure sinusoidal.

$$\cos(\phi) = PF$$

20/10/2019

Lecture 10


$$\text{Ripple Factor} = \frac{\sqrt{V_o(\text{rms})^2 - V_o(\text{avg})^2}}{V_o(\text{avg})}, \quad 0 \leq \text{R.F.} \leq \infty$$

To compare signal 1 & signal 2, you need to find the R.F.:

ripple factor

Pure Dc signal (Best case)

approaches ∞ when the avg value of the signal = 0, (pure Ac)
 - sine wave
 - square wave

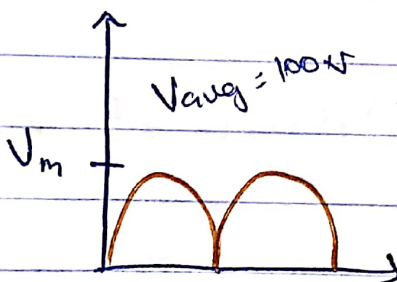

Signal 1



Signal 2

Signal 1, $V_{avg} = \frac{2 \cdot V_m}{\pi}$
 For rectified Ac, we

use $V_{RMS} = \frac{V_m}{\sqrt{2}}$ (like sine & cosine)

$$V_m = \frac{V_{avg} \cdot \pi}{2} = \frac{100 \cdot \pi}{2} = 157 \text{ V}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 111 \text{ V}$$

$$\text{RF} = \frac{\sqrt{(111)^2 - (100)^2}}{100} = 0.48 \%$$

Signal 2

$$V_{avg} = 100, \quad V_{avg} = k \cdot V_{De}, \quad V_{RMS} = \sqrt{8} \cdot V_{De}$$

If $V_{DC} = 150V$, $\delta = \frac{2}{3}$

$$V_{rms} = \sqrt{\frac{2}{3}} \cdot 150 \rightarrow 122.4$$

$$\text{So, } R.F = \frac{\sqrt{(122.4)^2 - (100)^2}}{100}$$

$$R.F = 0.7$$

The Rectified Sine is better than the chopped DC signal.

$$\text{R.F} = \frac{\sqrt{V_{rms}^2 - V_{avg}^2}}{V_{avg}}$$

$$R.F = \sqrt{\left(\frac{V_{rms}}{V_{avg}}\right)^2 - 1}$$

→ For rectified signals $FF = \frac{111}{100} = 1.11$, $FF \equiv \text{Form factor} = \frac{V_{rms}}{V_{avg}}$

shut ab, FF or RF $\sqrt{FF^2 - 1}$ is \circ
 $R.F = \sqrt{FF^2 - 1}$ is the relation



Back to Fourier:

$$V(t) = V_{avg} + V_m(1) \cdot \sin(\omega t + \psi(1)) + V_m(2) \cdot \sin(2\omega t + \psi(2)) + V_m(3) \cdot \sin(3\omega t + \psi(3)) + \dots + V_m(n) \cdot \sin(n\omega t + \psi(n)) + \dots \infty$$

→ For AC signals $V_{avg} = \text{Zero}$
 all even Harmonics = Zero in AC
 $n=1$ → fundamental component in AC & has
 the required power value.

→ $n=3$ 3rd Harmonic component
 ● pure sinusoidal \neq pure AC.

pure AC → $A_{avg} = \text{Zero}$

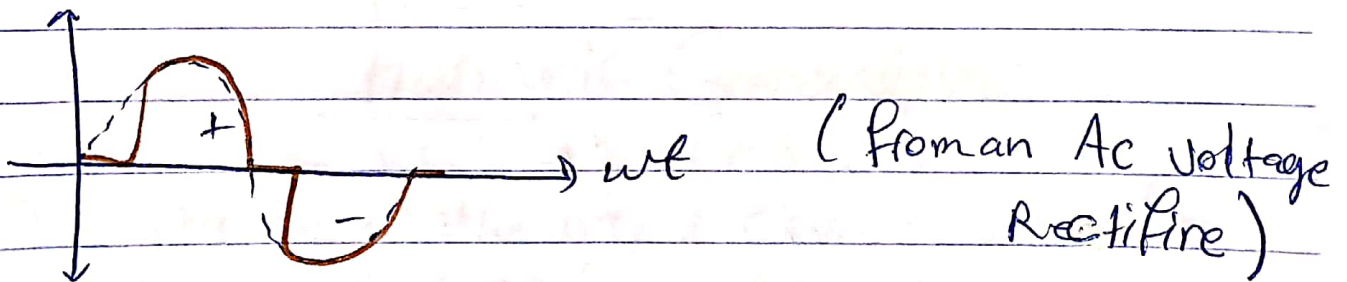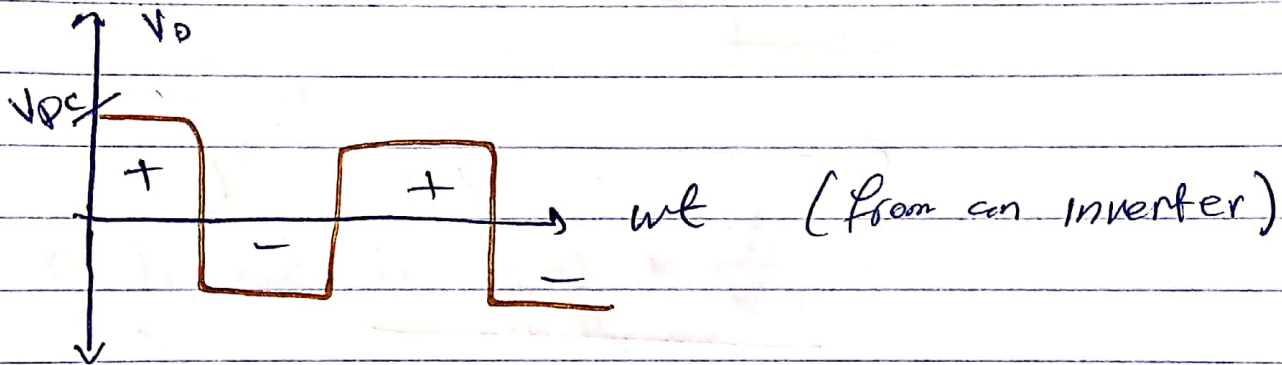

● 3rd Harmonic \equiv Heat, losses, Torque pulsation.

● To evaluate the signal:

not stable ←

Ripple factor does not work. So, we have

- Quality parameters:
- (1) Power factor (↑ better → Unity)
 - (2) Total Harmonic Distortion Factor (THDF)

$$THDF = \sqrt{V_{rms}^2 - V_{fundamental}^2} \quad (\text{Definition})$$

$$\rightarrow THDF = \sqrt{V_{rms}^2 - V_{(1)rms}^2}$$

$$0 < THDF < \infty$$

$v(t)$ is $\sin(\omega t + \psi)$
 $= V_m(t) \sin(\omega t + \psi)$
 pure sine#

approaching ∞

When the fundamental component = zero.

o If $\alpha = 0 \Rightarrow$ pure sine $\boxed{\frac{V_m}{\sqrt{2}}}$

\downarrow
 $\sin(\omega t)$ is
 $\sin(\omega t)$
 α

o To obtain $i(n) = \frac{V_m(n)}{Z(n)}$
 nth Harmonic

Harmonic Generation Impacts

① Distortion of the output signals, this leads to a load over heating (specially Motor loads).

ex: De motor

$$\rightarrow i(t) = 10 + 8 \sin(2\omega t - 30^\circ) + 5 \sin(4\omega t - 69^\circ) + \dots$$

$$\rightarrow \text{Find } I_{avg} = ? \quad 10A$$

$$\rightarrow I_m(2) = 8A$$

$$\rightarrow I_{rms}(2) = \frac{8}{\sqrt{2}} A$$

$$\rightarrow I_m(4) = 5A$$

$$\rightarrow I_{rms}(4) = \frac{5}{\sqrt{2}} A$$

for the 2nd Harmonic component.

for the 4th component.

cont...




$$I_{rms} = \sqrt{10^2 + \left(\frac{8}{\sqrt{2}}\right)^2 + \left(\frac{5}{\sqrt{2}}\right)^2 + \dots}$$

$$I_{rms} = 12 \text{ A}$$

$I_{avg} = 10 \text{ A}$, Torque is a function of current

$$\rightarrow T_{gr} = k_a \cdot \Phi \cdot i_a, \quad k_a \cdot \Phi = k$$

$$\rightarrow T_{gr} = k \cdot i_a$$

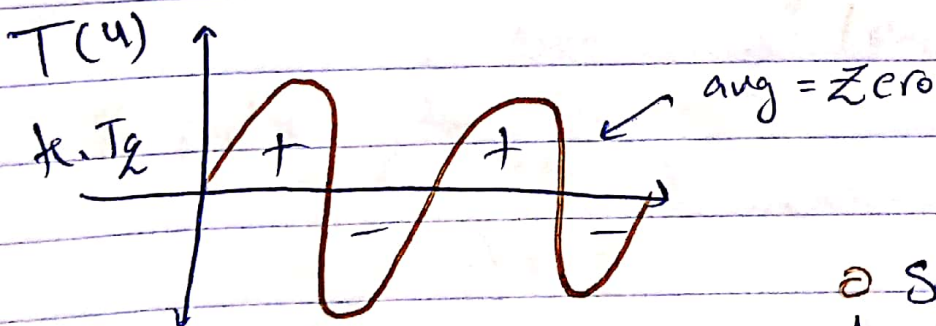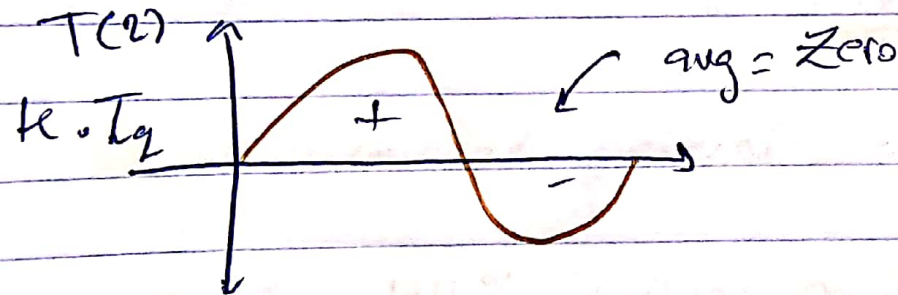
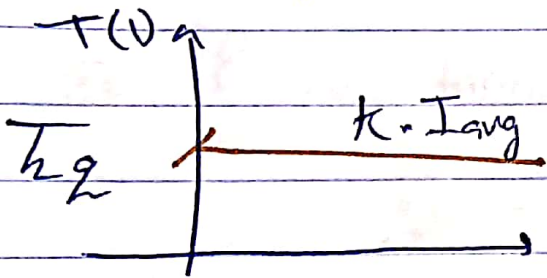


So, Torque is only developed by I_{avg}

\rightarrow Harmonics has zero avg. developed Torque \rightarrow (Torque pulsation)

Torque pulsation

CCM: continuous current mode.

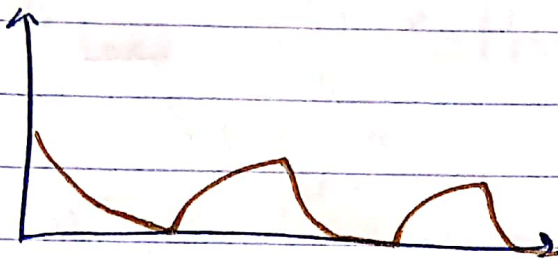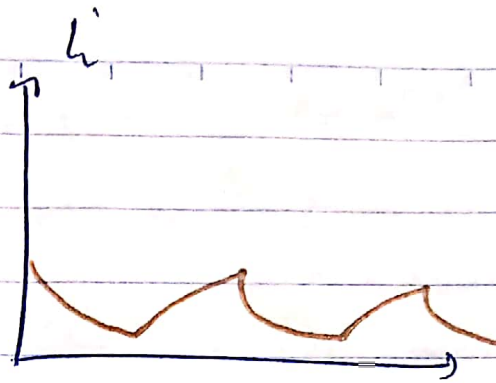

DCM: Discontinuous current mode.

⊙ If no Harmonics (pure DC): $(I_{rms} = I_{avg})$

Copper loss $\rightarrow P_{cu} = (I_{rms})^2 * R_a \rightarrow$ armature
 $= 10^2 R_a = \underline{\underline{100 R_a}}$

⊙ if Harmonics generated $= I_{rms} = \sqrt{\dots} = 12^2 R_a$
 $= \underline{\underline{144 R_a}}$

→ So 44% extra power loss → leads to overheating.

* ratio

$\left(\frac{I_{avg}}{I_{rms}} \right)$ is called Derating Factor

From the previous Example $\frac{10}{12} =$ Derating Factor

المعدل

المعدل
Derating

(يعني لازم اعدل ال Motor الى هذا الرقم
 لأن ال Power يكون اصغر)

22/10/2019

Lecture 11

Derating Factor = $\frac{I(1)_{rms}}{I_{total,rms}}$ (AC motors cause power is in the Fundamental)

Derating Factor = $\frac{I_{avg}}{I_{rms}}$ (DC motors)

$P_{load} = DF \times P_{rated}$



↓
Derating Factor

→ If the load power is not allowed to be reduced, then oversizing of the motor is required

$P'_{rated} = \frac{P_{rated}(orig)}{DF}$

DF cannot be larger than 1

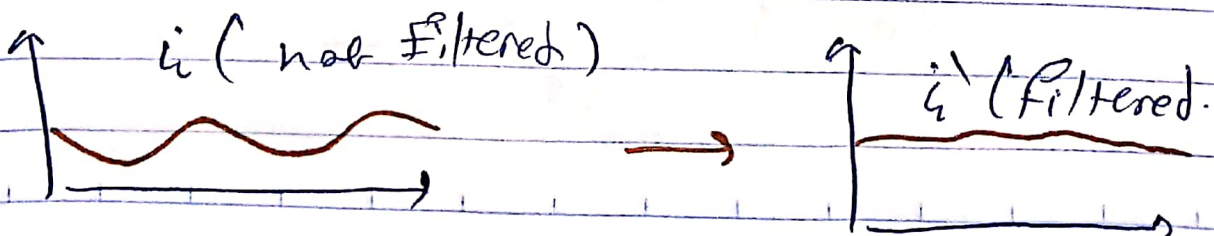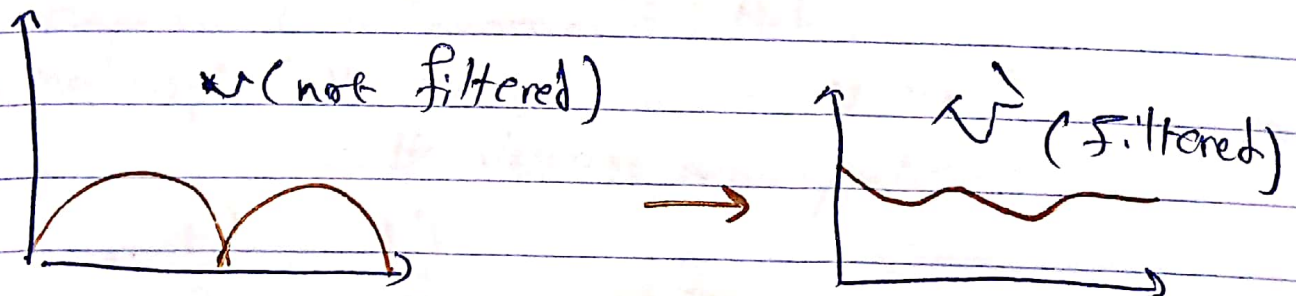
→ If no derating or over-sizing is required, then get rid of the harmonics (dominant current harmonics) by filtration.




- If capacitor $C \uparrow$ values are increased \rightarrow more filtration -
- Harmonics leads to Distortion of light currents wave forms (communication & control systems).
- Harmonics leads to Supply power factor reduction even if the load is pure resistive.

SCR

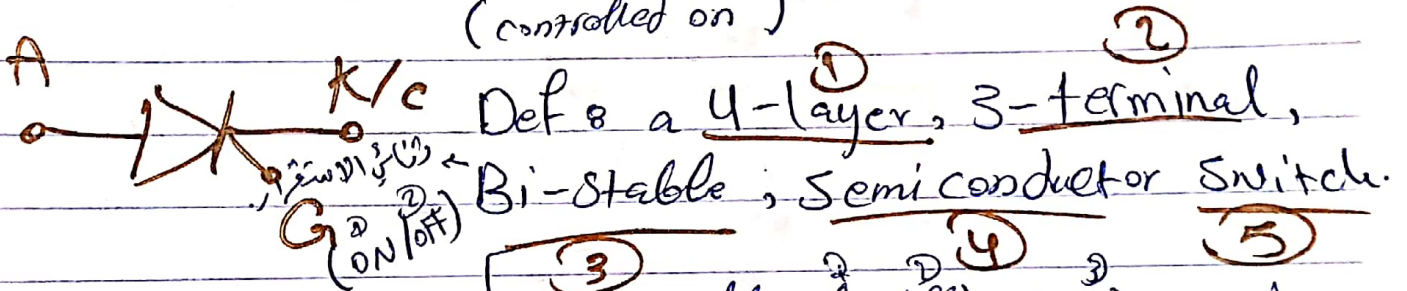Silicon controlled Rectifier.
(controlled on)




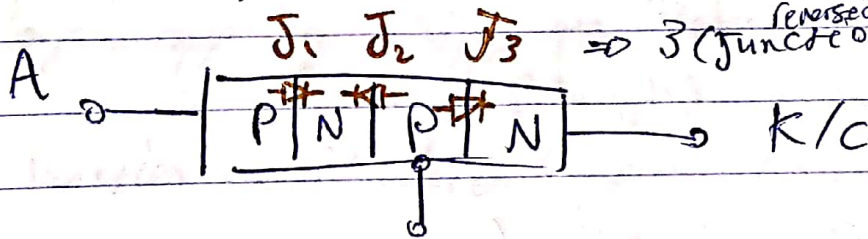4-Layers \rightarrow Tri-stable (on/off) \rightarrow (off) Forward Biased / Reverse Biased.




P: majority (+ve) charges (or) Holes.
N: majority (-ve) charges (or) electrons.


\rightarrow If voltage was applied:

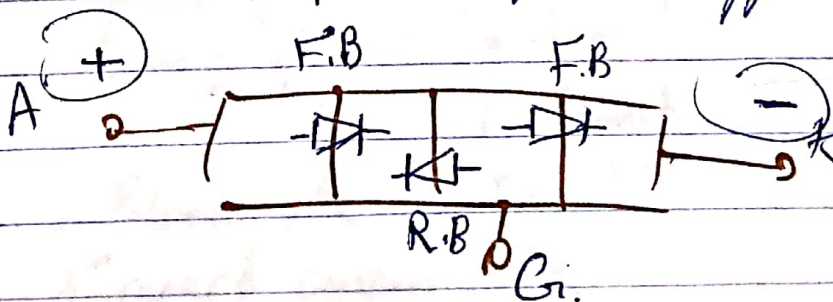

→ if voltage was applied:

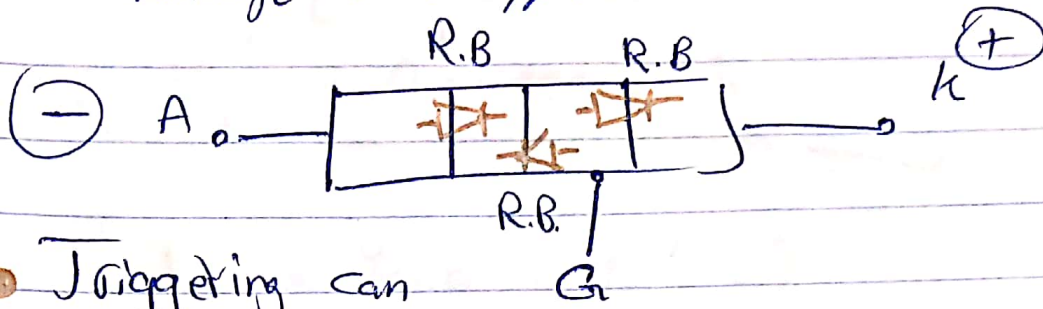


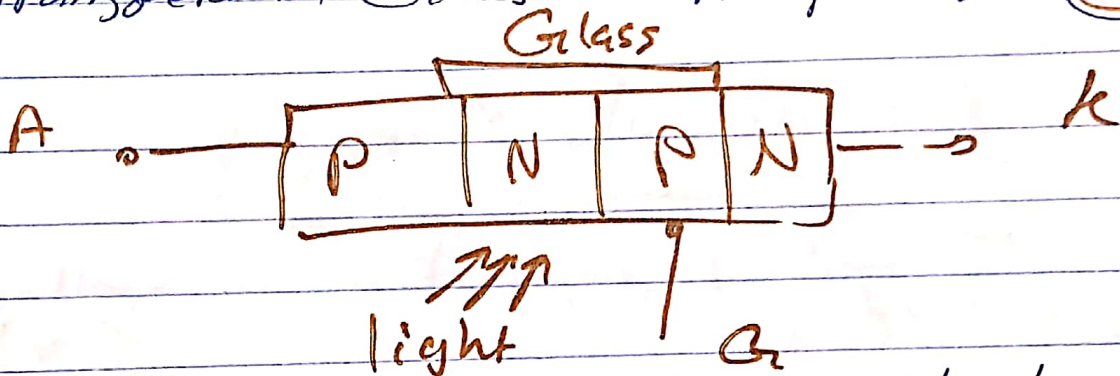- Triggering can be applied by either voltage (1) on Gate or making the [NP] junction in the middle transparent / Glass and apply light. (2)



- by applying V_{AK} (Voltage) (very high) → the barrier Junction will break and current will pass.

Layers:

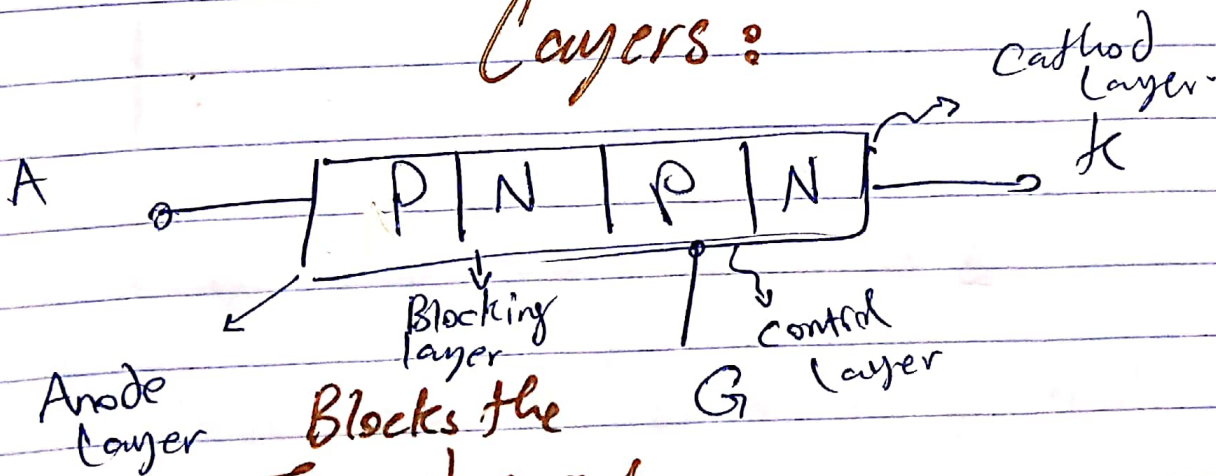

Blocks the Forward current from flowing

Static V/I characteristics → Time is embedded inside.


← (الخاصة بالتيار والجهد)

- (i) as a function of (V)
 current voltage

$$i = f(V)$$



Dynamic characteristics

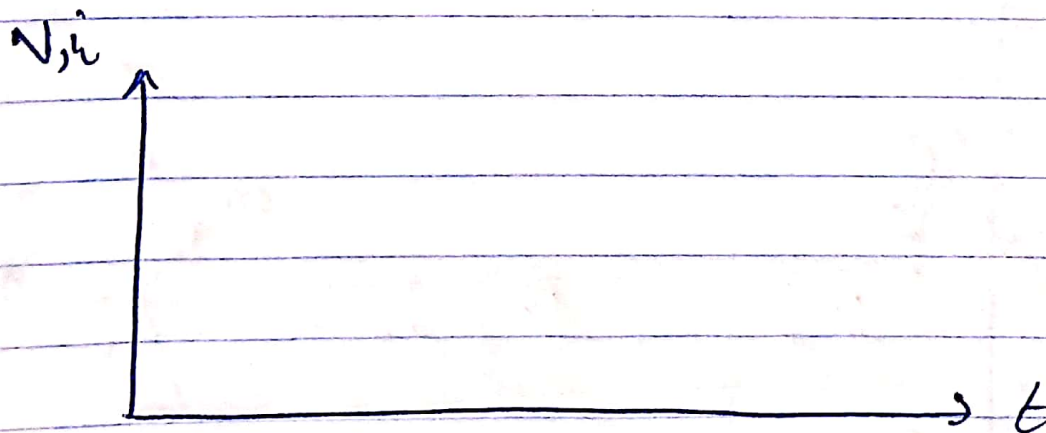- Voltage as a function of time.
 (V) (t)
 - Current as a function of time.
 (i) (t)
- } Switching on/off



area under the curve → power dissipated.

24/10/2014


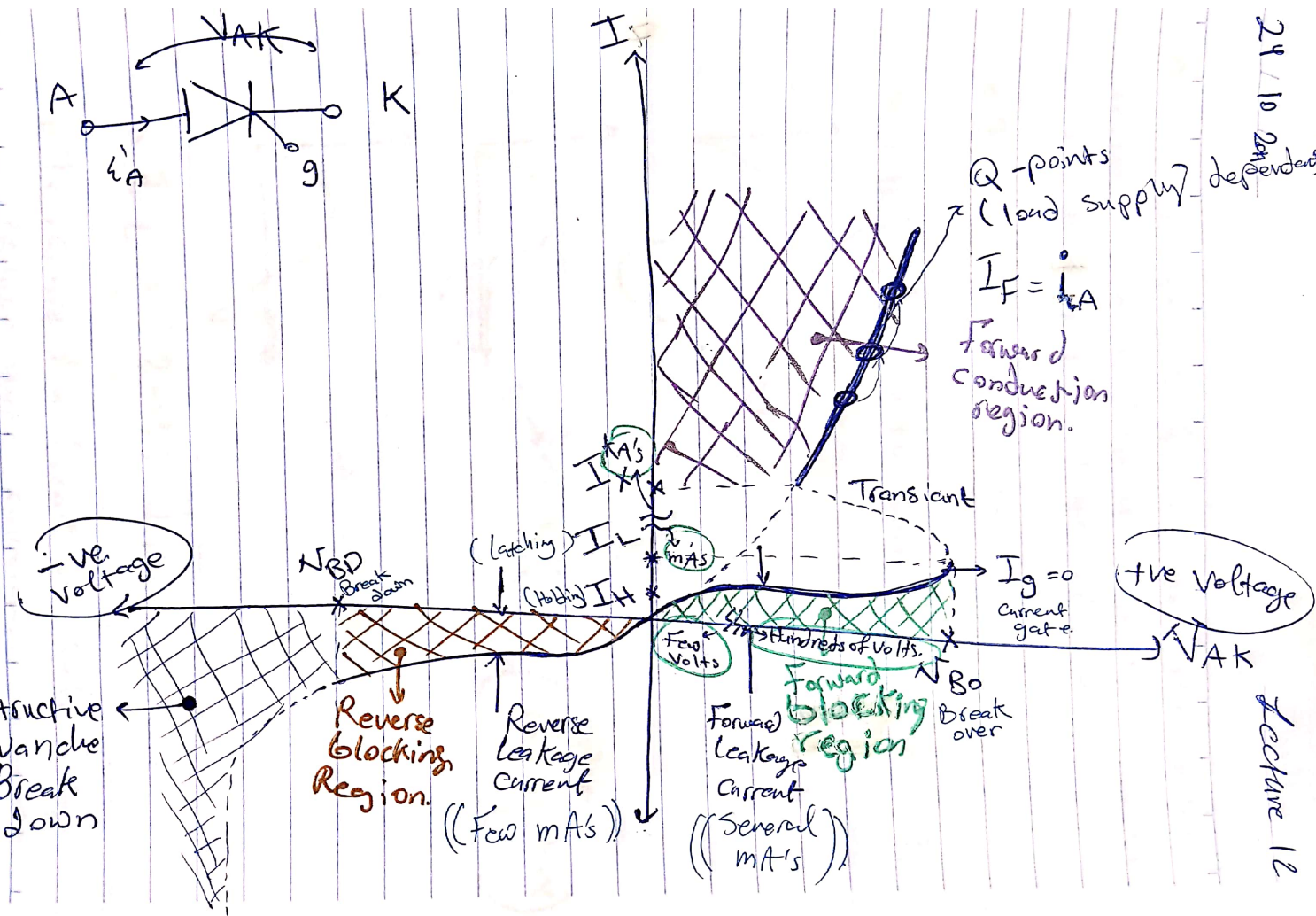
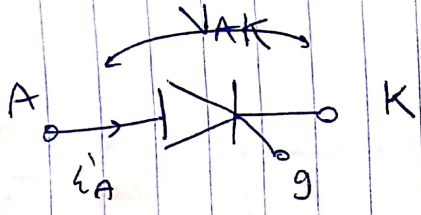


lecture 12

○ The voltage will decrease until the applied voltage on both load & Thyristor is equal to the supply voltage ((Transient))

○ $I_L < I_X$

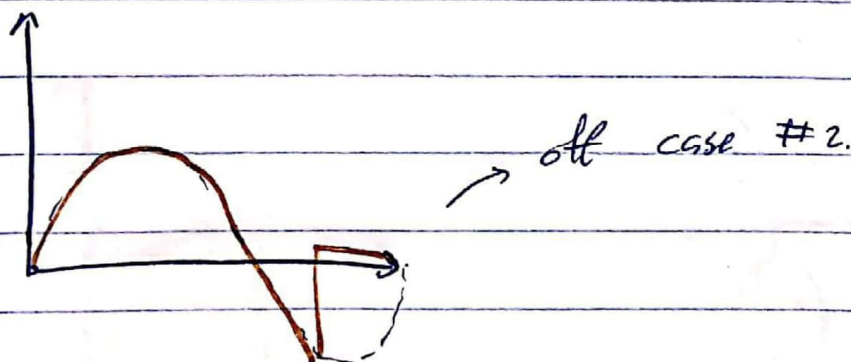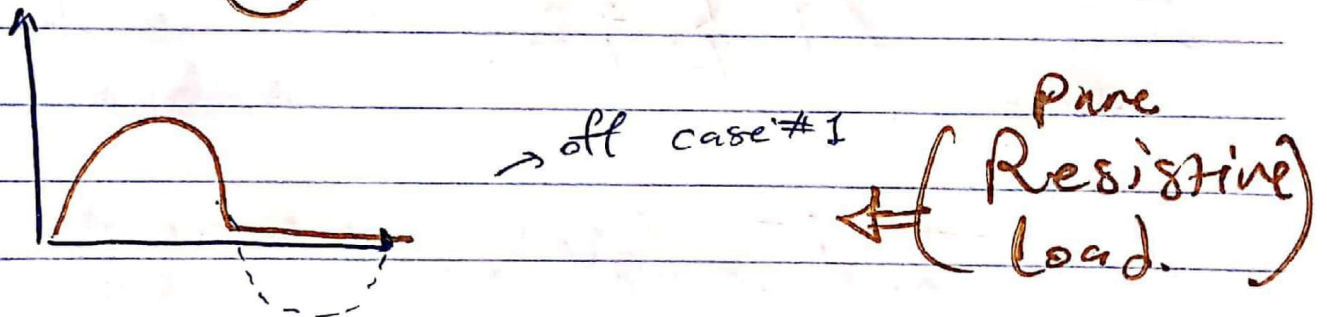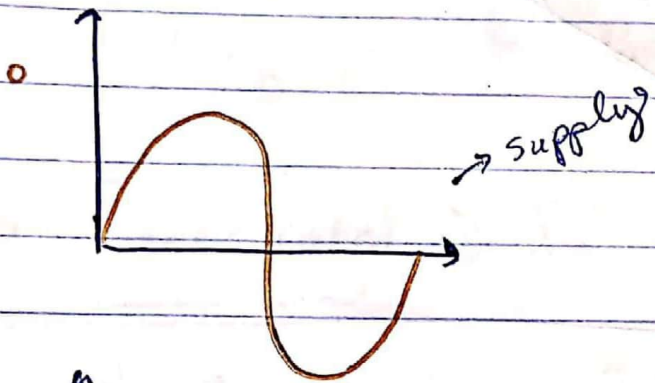○ I_H (Holding) is to switch Thyristor off.



○ $I_L = (2 \rightarrow 3) I_H$


○ To reduce the Break over voltage }
increase gate current. }

• I_L (latching) : The Minimum Forward current required to switch on a Thyristor or (SCR).

• I_H (Holding) : The Minimum Forward current required to keep an SCR on.
 → ((if $I_F < I_H$ → Switch off action occurs.))

Switch off process

in SCR's. = commutation of SCR.

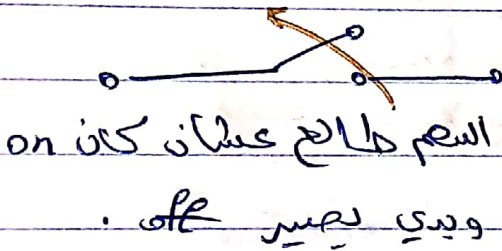


Types of commutation:

A. Natural commutation:

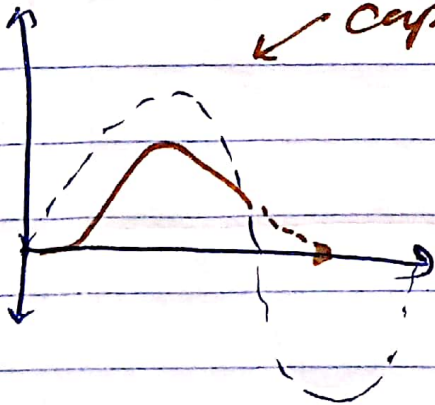1. Line commutation (Ac supply)
2. Load commutation (capacitive load)



capacitive load (i leads v).
 leading power factor.




[B.] Forced commutation

1. To switch off DC excited SCR.

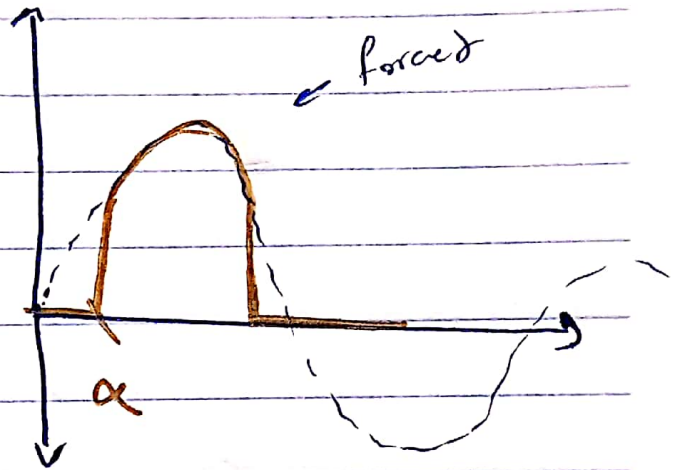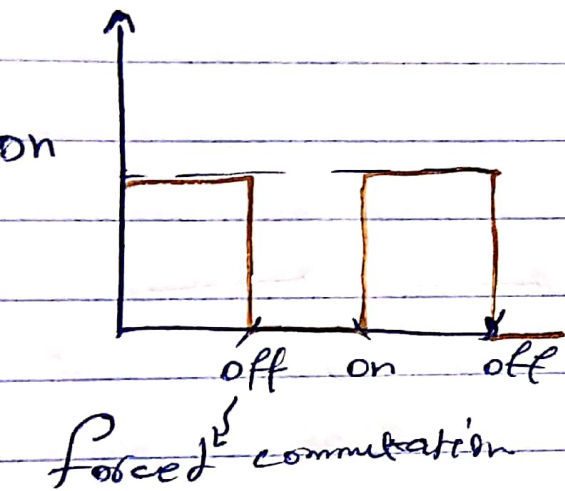2. an AC excited SCR while being forward biased.




[or]

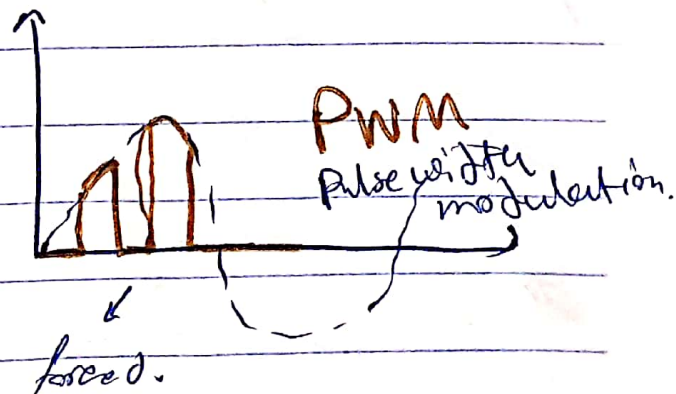

Commutation

Forced

a) Dc-Excited Systems


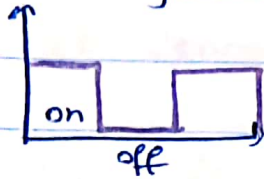


Natural

Load
for capacitive loads

Line
for Ac-Excited Systems.

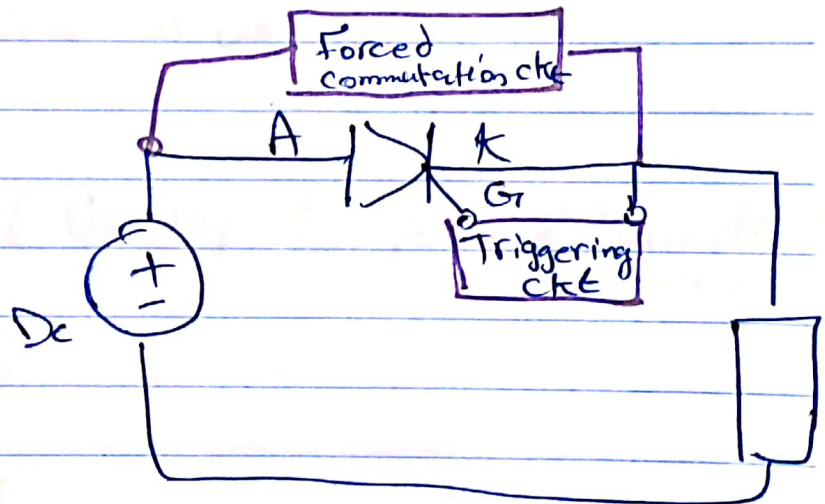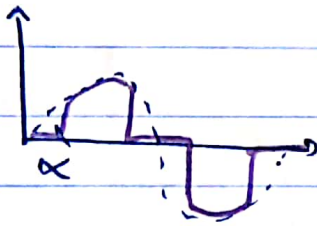b) Ac-Excited with switching off while forward biased.



① forced commutation circuit (between A & K)

→ to switch off Thyristors. (Aux SCR's, R, C, L, D)

Function: ① provides an Alternative


path for SCR forward current to decrease the current (less than I_H)

② apply Reversed Biasing to The SCR for a period slightly greater than T_{off} , where T_{off} : The →


Turn off time given by the manufacturer data sheet.

By The End of This period, The SCR is Switched off and The commutation circuit is Also Switched off. SCR will be back to conduction if triggered (not by the supply re-connection.)

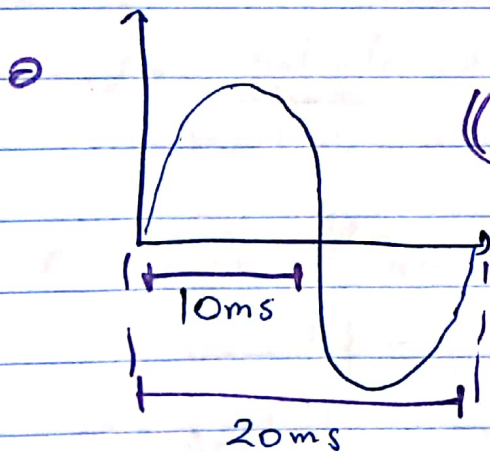- Turn off time : [P] and [N] junctions needs to recover charges (10's of μA 's)
- is, but this is "less" than "10's of μA 's"
- It is also



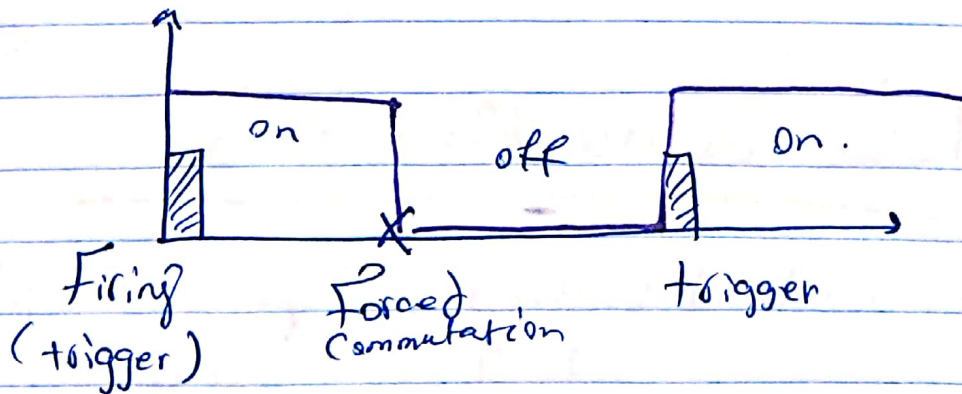((Usually T_{on} period $<$ Turn off period.))



• Data Sheet information


- Avg
- RMS
- pulse

• $V_{SCR} \text{ (rating)} = (2 \rightarrow 3) * PIV \text{ (} V_{AK} \text{)}$
 (peak inverse voltage)


Safety factor

(2 → 3)

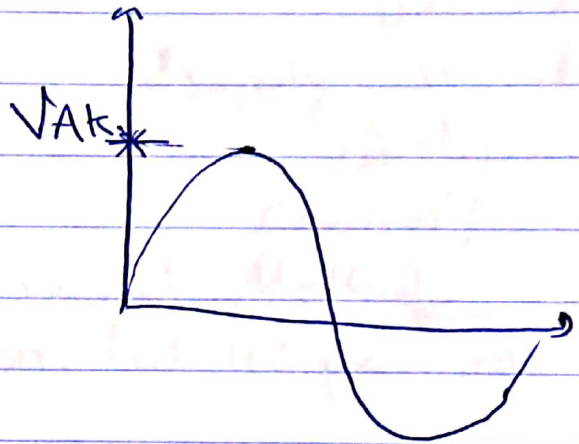لذا : 3 الى 2 ←
 لئلا α 1.4 يتجاوز
 ونسبة من choice
 لئلا نزيد ←



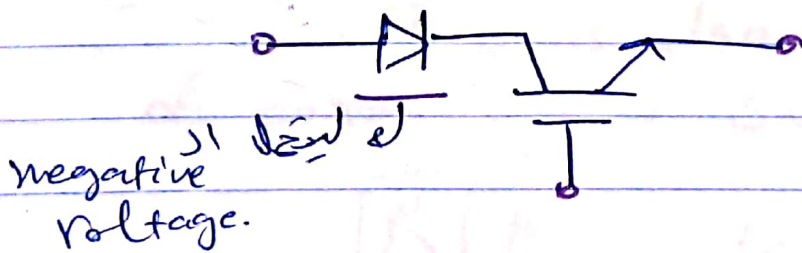• Switch off Transistor in Ac (add diode)




To switch on an SCR


A By increasing the Forward leakage current,
 This can be done by:

B apply High V_{AK} such that $V_{AK} > V_{BO}$

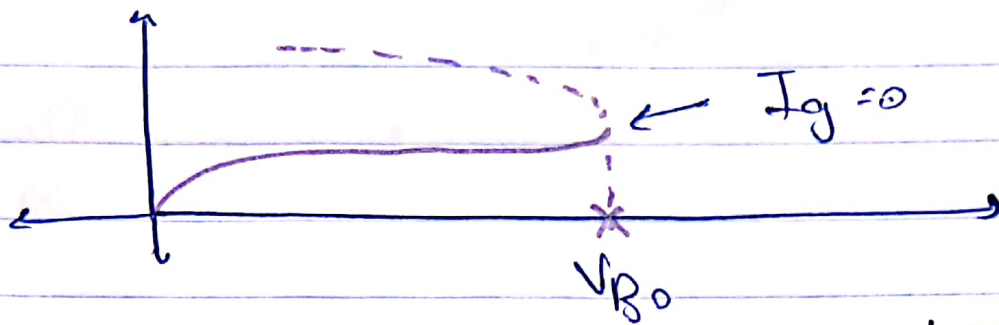تکبر اد V_{AK} اُنسبر اد $V_{Break\ over}$



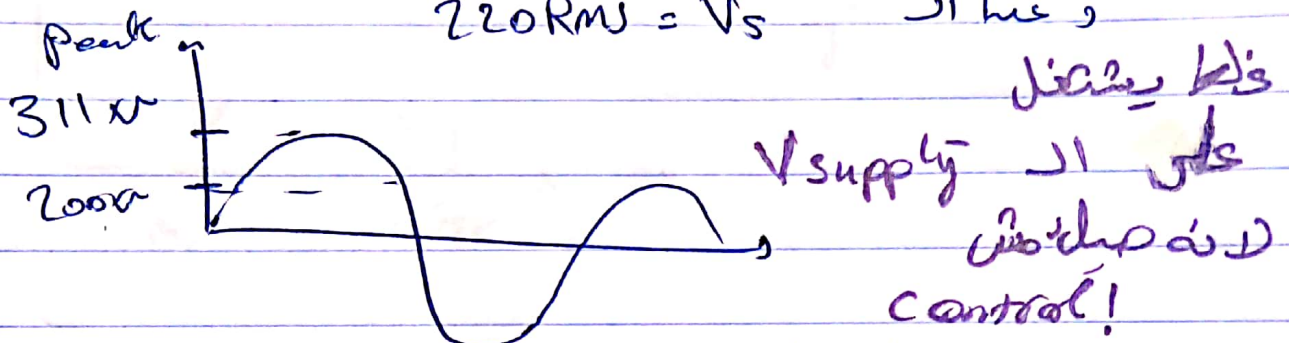* اذا انا هيا $200V = V_{BO}$ $220RMS = V_s$ $I_g = 0$ V_{supply} $control!$







→ This is not a normal Method of controlling on, but it's possible.

[2] By Increasing the Ambient Temperature (This is also not a normal method of controlling or switching on SCR on).

[B] By gate current:

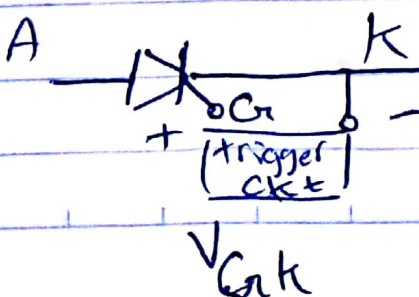* by applying a short pulse of current to the gate (I_g).



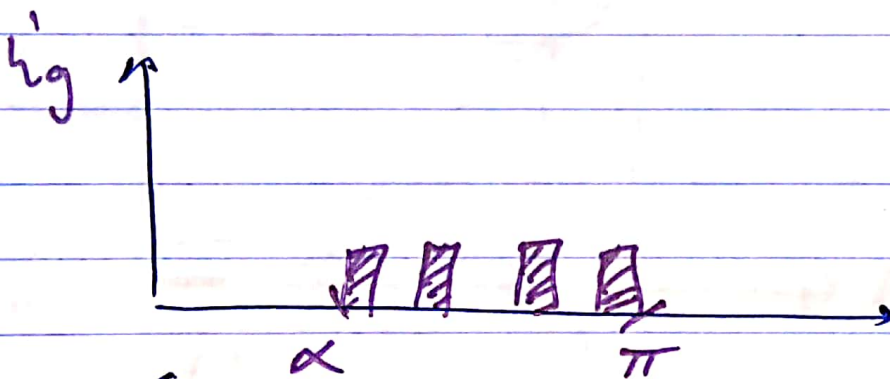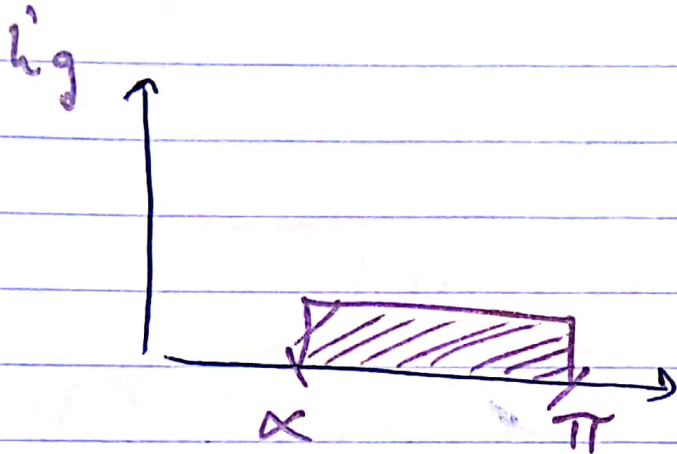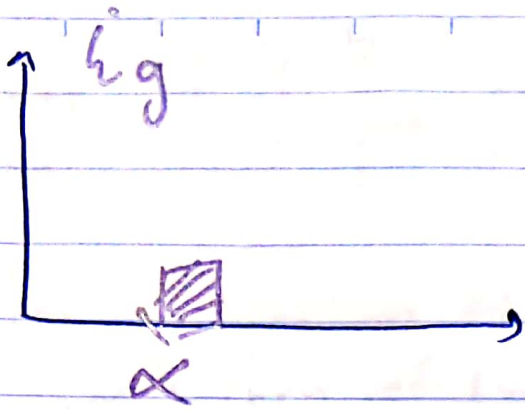


(10-20) KHZ (why?): Some loads \rightarrow High Inductive loads; The forward current takes time so Multiple pulses.

$V_{AK} = f(t)$
 $I_f = f(t)$ } → Dynamic characteristics.

T_{on} : Turn on time
 T_{off} : Turn off time.

* we want T_{on} & T_{off}
 as small as possible.
 → Fast switching?

Turn on period

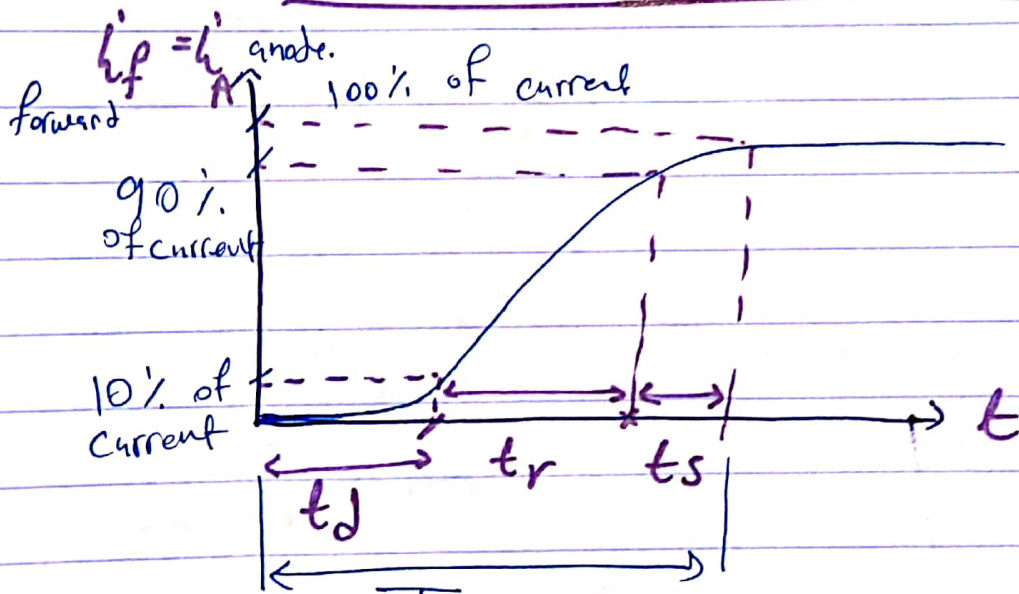


The value of

100% of current is determined by load impedance & the supply voltage.


$$T_{on} = t_d + t_r + t_s$$

delay time rise time spread time.

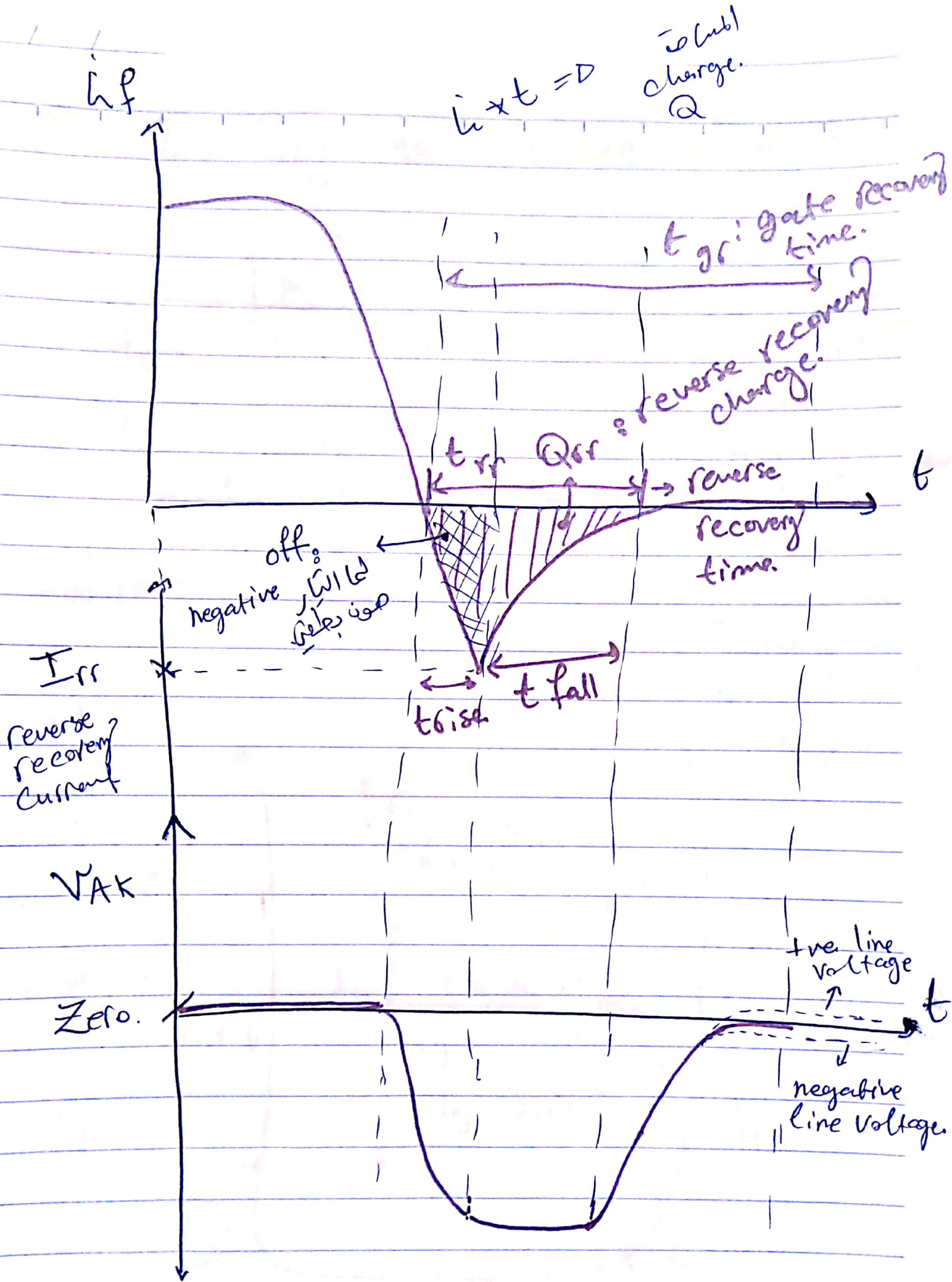


* Two-Transistor Module of an SCR

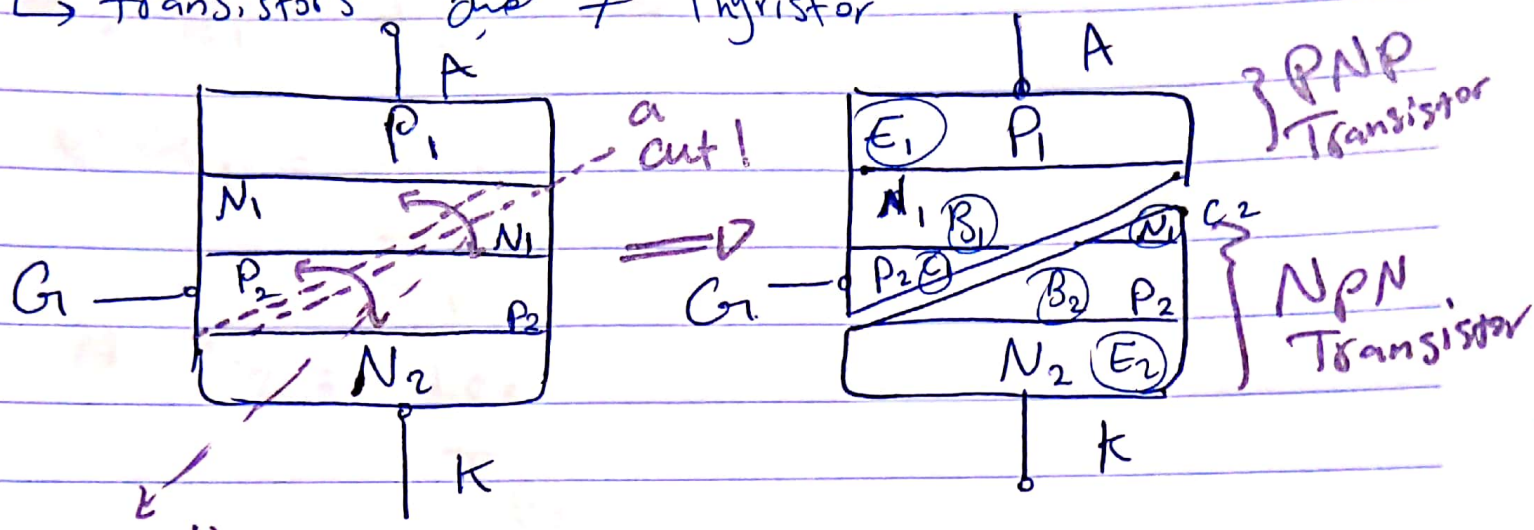SCR is a Thyristor. Thyristor is not a transistor.
 → transistors are ≠ Thyristor



connections.

E_1	Emitter	E_2
B_1	Base	B_2
C_1	collector	C_2

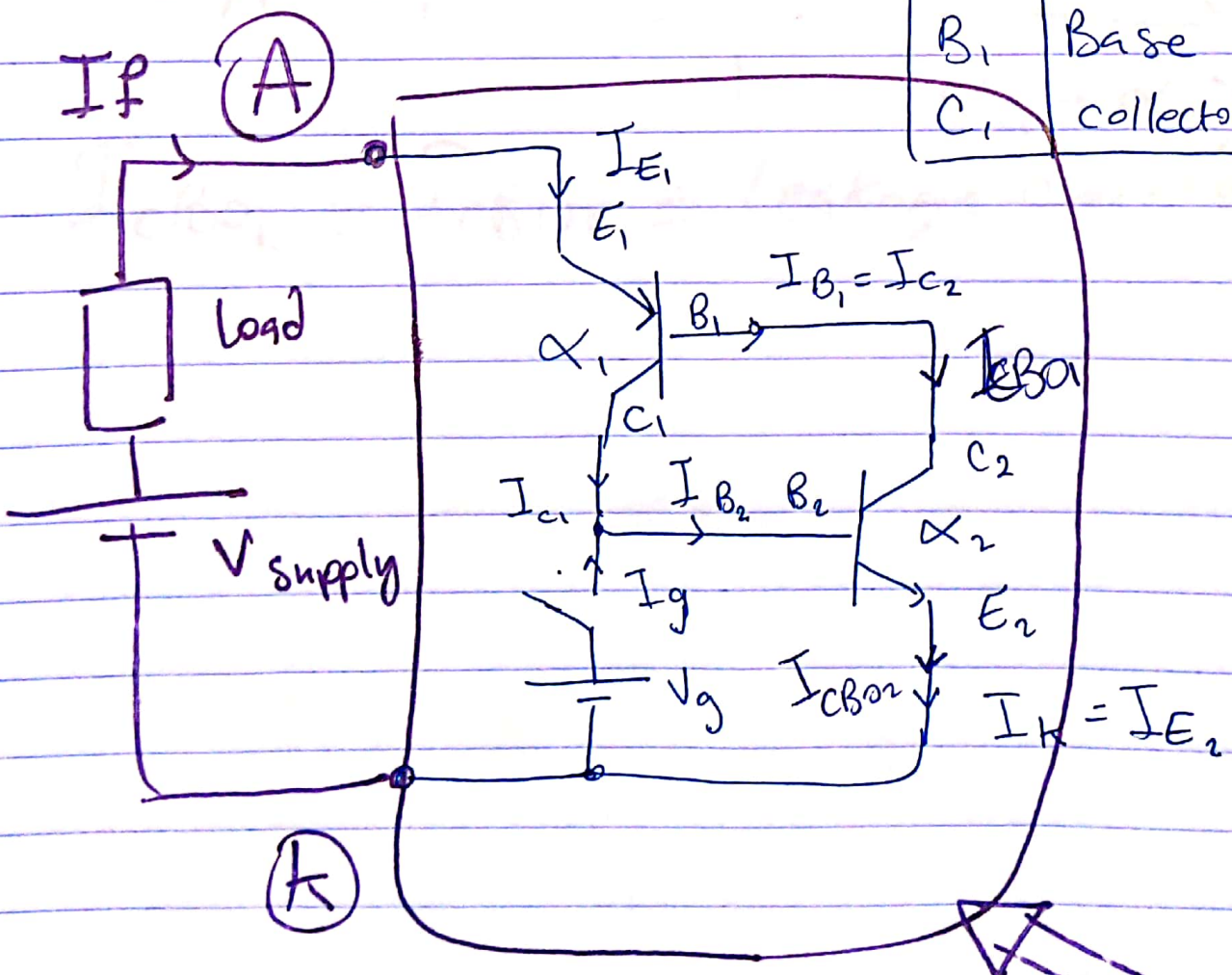

inside

$$\bullet I_{B2} = I_g + I_{c1}$$

$$\bullet I_{E1} = I_{E2} - I_g$$

$$\bullet \alpha_1 = \frac{I_{c1}}{I_{E1}}$$

$$\bullet \alpha_2 = \frac{I_{c2}}{I_{E2}}$$

$$\bullet I_A = I_F = \frac{(\alpha_2 I_G + I_{c\beta 01} + I_{c\beta 02})}{1 - (\alpha_1 + \alpha_2)}$$

$I_{c\beta 01}$ & $I_{c\beta 02} \equiv$ leakage current.

$$I_f = \frac{\alpha_2 I_g + (I_{CBO1} + I_{CBO2})}{1 - (\alpha_1 + \alpha_2)}$$
 , $I_f > I_L$ ^(latching current)
 for conduction
 Forward in Thyristor.

$\alpha_1 + \alpha_2 \lesssim 1$

To increase I_f :

- ① Increase $I_{CBO1} + I_{CBO2}$
 - By $V_{AK} \uparrow \uparrow$ } not normal.
 - or (Heat) \uparrow

② Increase I_g
 ↳ Alternative (light beams)

Back to the Ripple Factor

→ Quality parameter for Dc V, I, P .
voltage, current, power.

→ Optimum (Ideal) Dc signal:

Zero-Ripple $R.F. = 0$

Ripple, $R.F. > 0$

chopper circuit output $R.F. > 0$


by definition

$$R.F = \frac{\sqrt{V_{rms}^2 - V_{avg}^2}}{V_{avg}}$$

$0 \leq R.F < \infty$
 Pure Dc \downarrow Pure Ac
 $V_{avg} = V_{rms}$ not accepted
Ideal


Back to the Triggering circuit

Low power Electronic circuit.

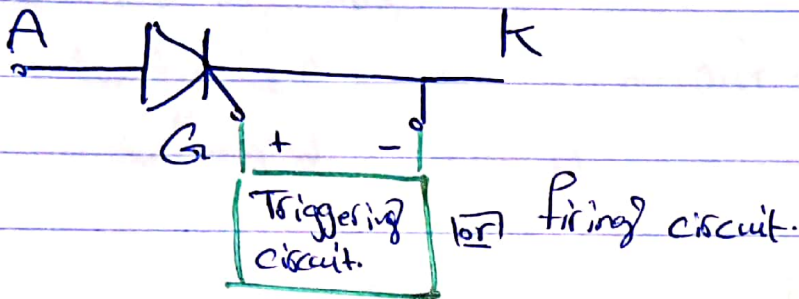

Triggering circuit should be synchronized with the AC power supply (that is supplying the converter itself).



Converter

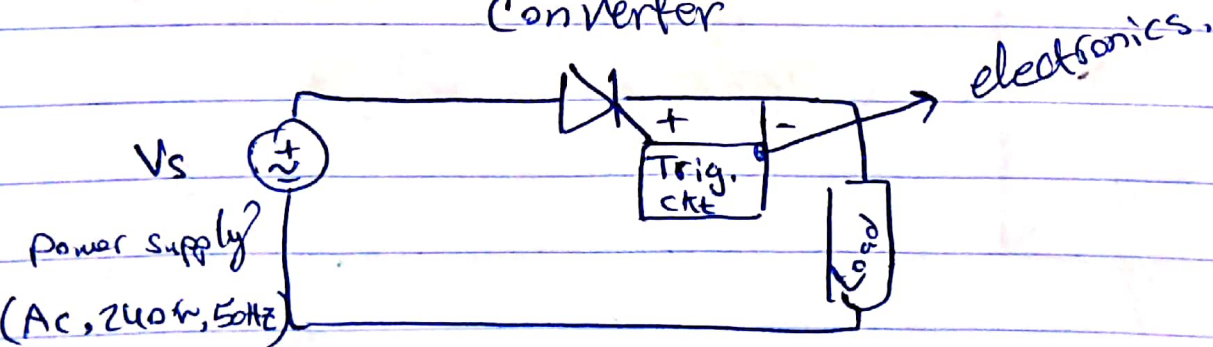


There are electronics in the triggering circuit (needs power)

Synchronization

Supply
220V, 50Hz

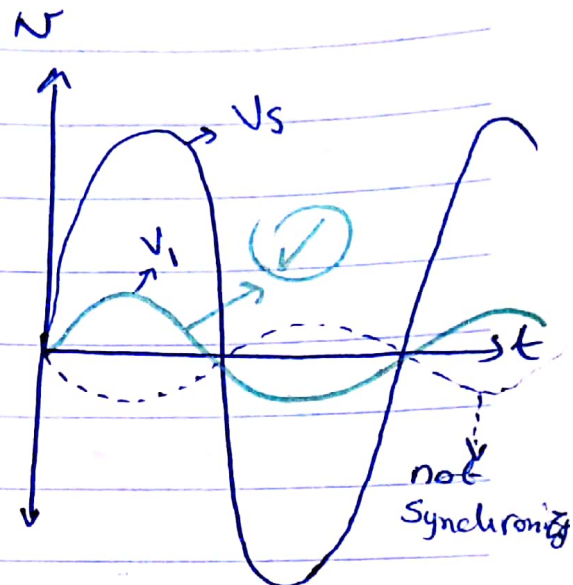
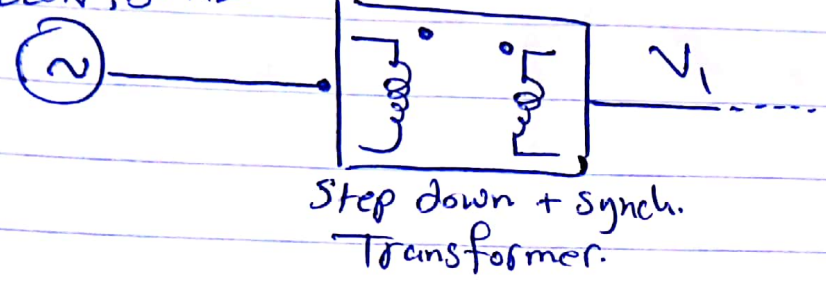


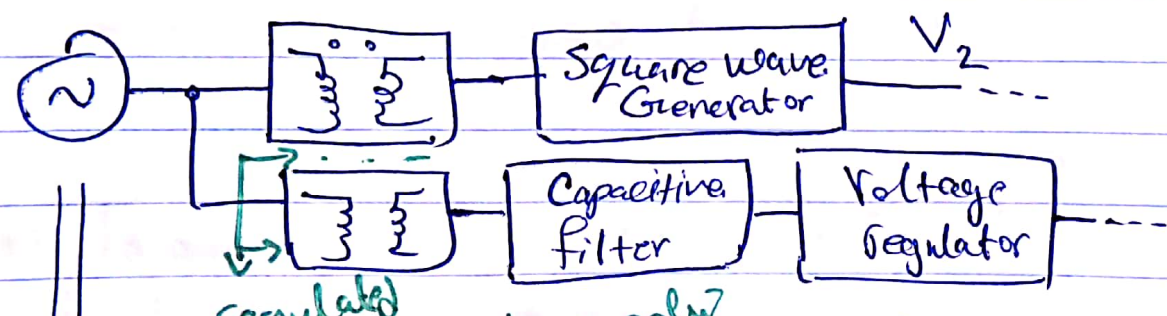- The current is in phase with the current supplying the load.
- polarity test on the Transformer to make sure it's Synchronized ((dots))




regulated DC power supply : to supply the triggering ckt.

inside a source

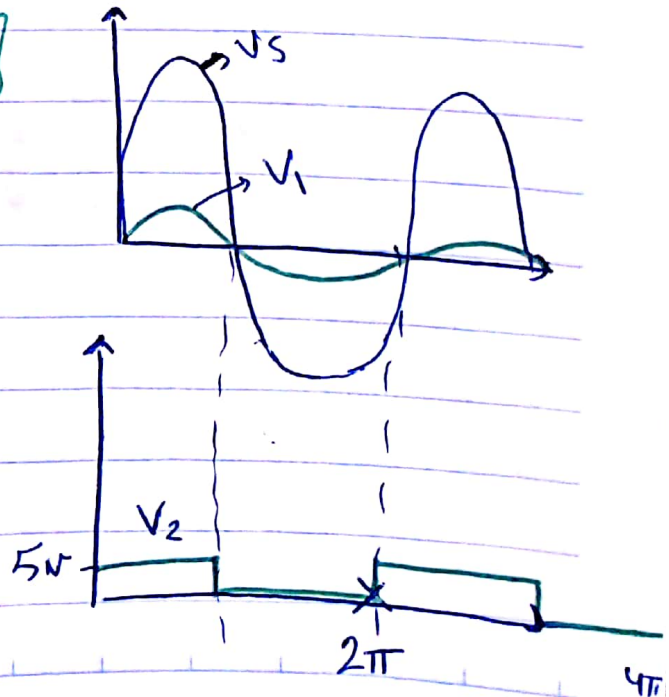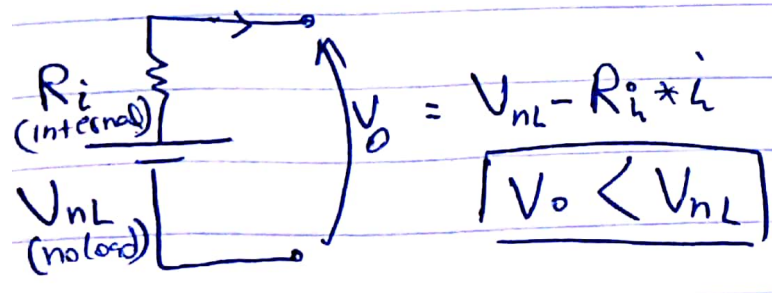

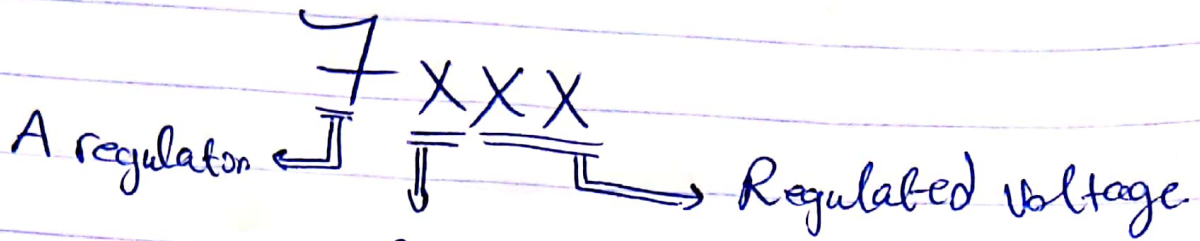● Voltage regulator: electronic element $I_c = 7XXX$




9: negative (-) 05 : 5V

8: positive (+) 09 : 9V

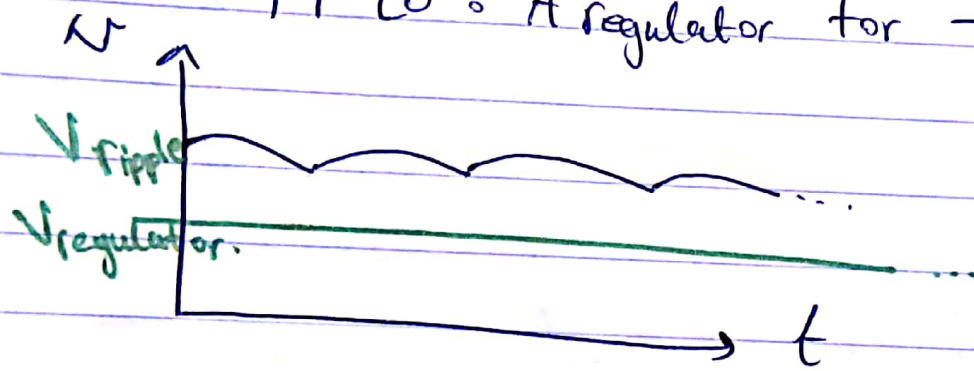12 : 12V

→ ex: 7812 : A regulator for +12V.
7920 : A regulator for -20V.




Voltage regulator level must be less than the rippled voltage.

● Triggering frequency of each switch equals that of the supply frequency.

● A regulated power supply: Zero voltage regulation (loaded or unloaded).


3 / 11 / 2019

Lecture 16

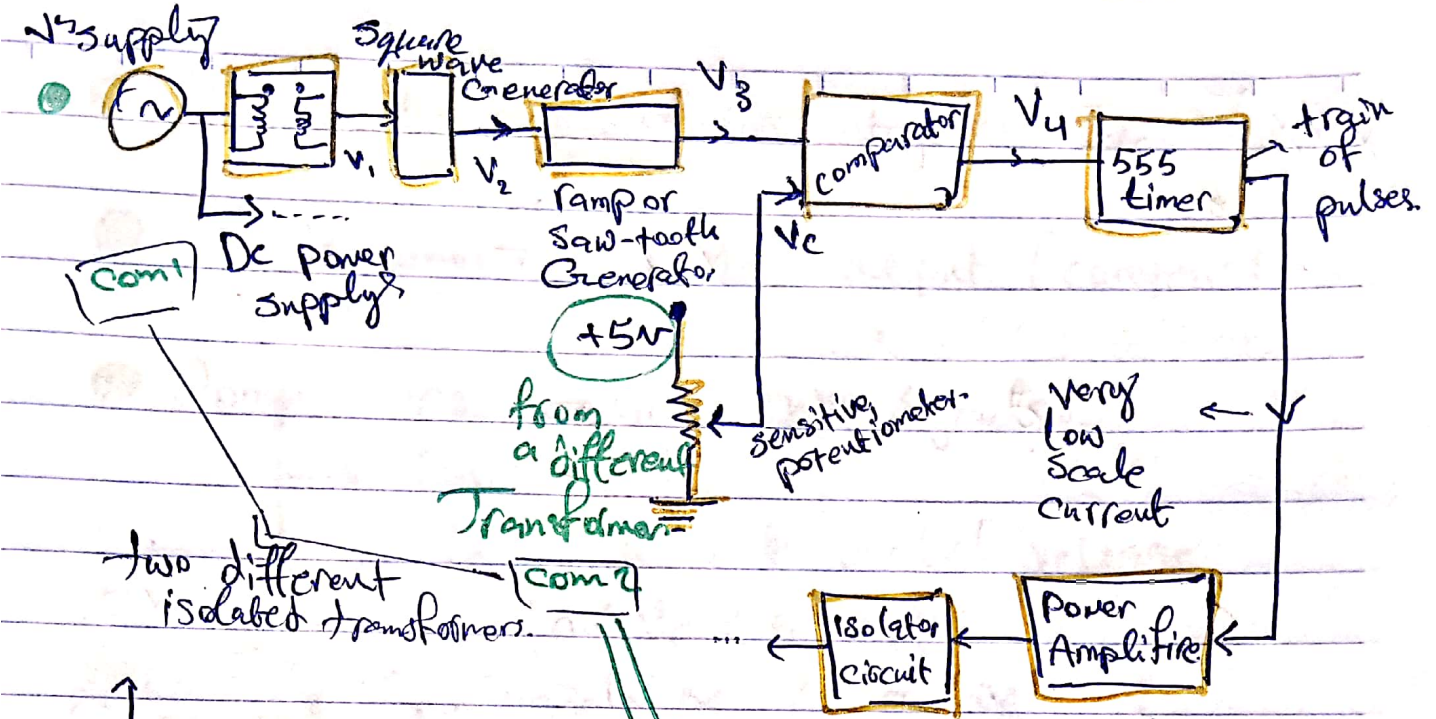

Two different isolated transformers.

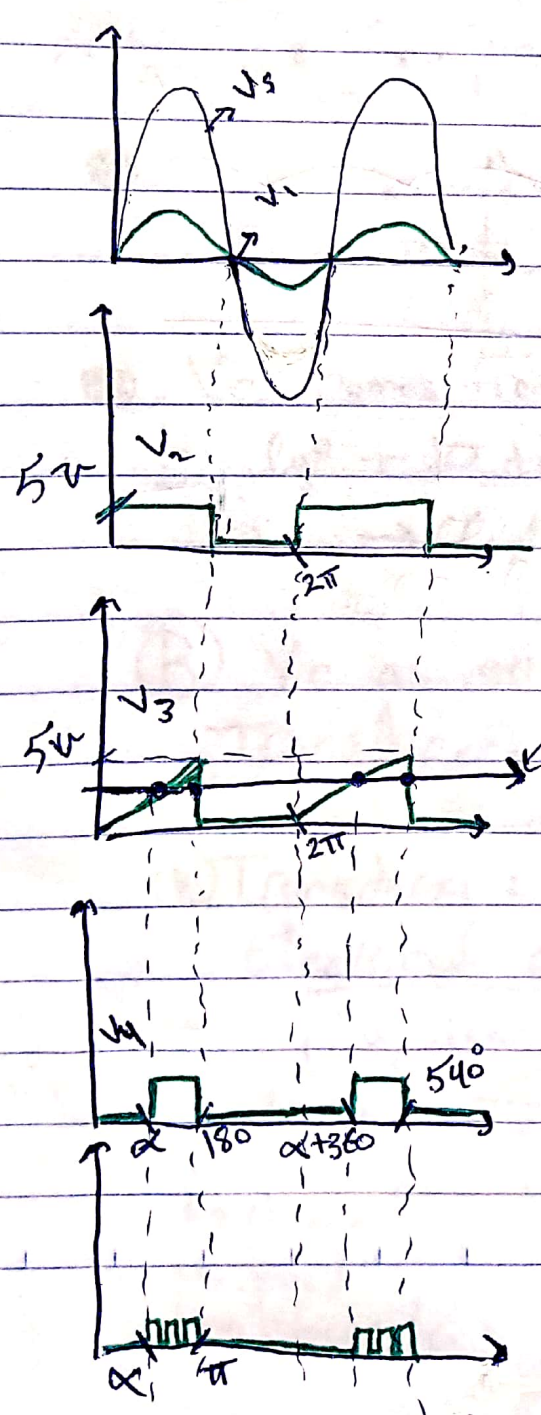we don't care if this +5V is synchronized or not.



● V_3 is the output of an Integrator Op-Amp.

● V_4 is another Op-Amp output (comparator).

● Comparators compares two signals:


→ Saw-tooth

→ V_c : Variable control voltage.

$(0 \leq V_c \leq 5)$ Volt.

* Firing angle α $0 \leq \alpha \leq 180^\circ$

●

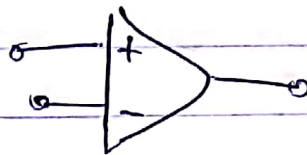

← comparator

when $\alpha = 0$
then $V_c = 0$


● V_c comes from (A) Regulated 5V Dc power supply + 10 turns potentiometer

→ ((Manual control of α))

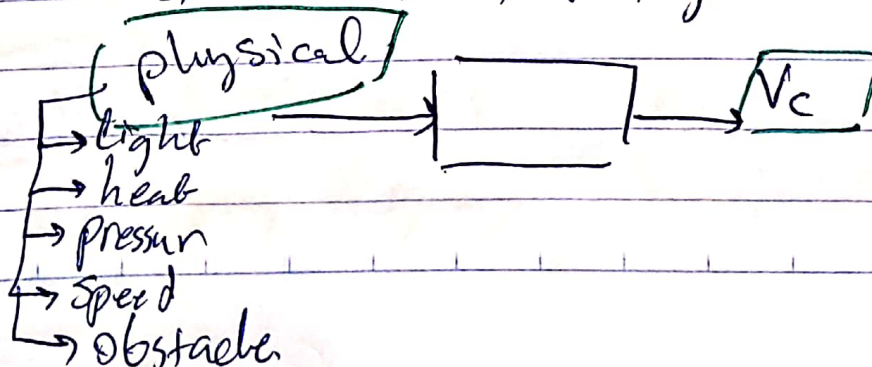
(B) V_c as an output of a certain physical Transducer.

→ ((automatic control of α))

* Transducer: physical quantity to Electrical current/voltage.



Triggering pulses

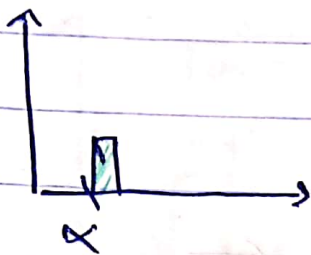


- #1 Single short pulse.
- ✓ Suitable for low inductive loads or resistive loads.

we don't prefer these two

Disadvantage → Triggering isn't ensured.


Advantage → gate losses are the lowest

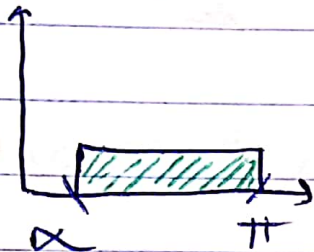

- #2 Continuous signal
- $\alpha \leq \text{Signal} \leq \pi$

Advantage → ensure triggering

Disadvantage → Highest gate losses.

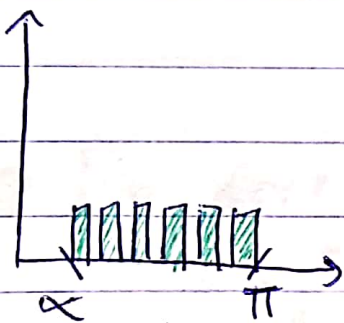

- #3 Train of pulses (10-20 kHz)
- High frequency.

to make sure that triggering occurred

to have reasonable losses values.

- ✓ → ensure triggering
- ✓ → moderate gate losses, (medium).

To obtain the schmitt trigger pulses, use 555 timer IC.


Homework

555 timer: $f = \frac{1}{T} = \frac{1}{R_1 C_1 + R_2 C_2}$

((chopping frequency low)) & ((modulation index))

← (sub index)

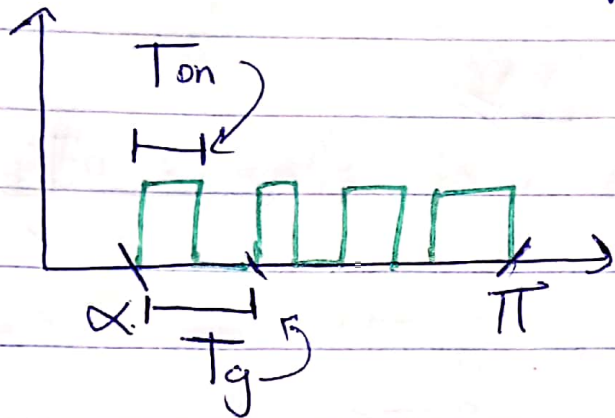● Train of pulses $\begin{cases} \rightarrow \text{period } (T_g) \\ \rightarrow \text{period } (T_{on}) \end{cases}$ ((10-20 kHz modulation frequency))



$$T_{on} = \delta \cdot T_g$$

↓
modulation index.

● power Amplifier :

Darlington \Rightarrow to Amplify the current.
 \rightarrow doesn't change the signal shape.


● Isolator : **(A)** pulse Transformer.
 (separate two different circuits).
 excellent core material such that no saturation due to the De gate pulse occurs.

\rightarrow to Isolate the electronic triggering signal from the power signal.


5 / 11 / 2019

Lecture 17

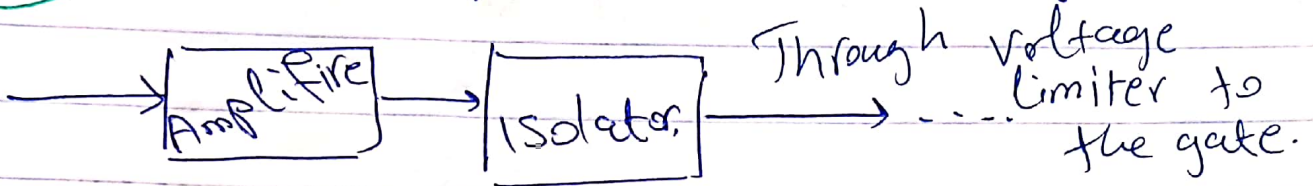② (B) Opto Coupler Isolator \rightarrow upto 2000V




Opto coupler is a light emitting diode.

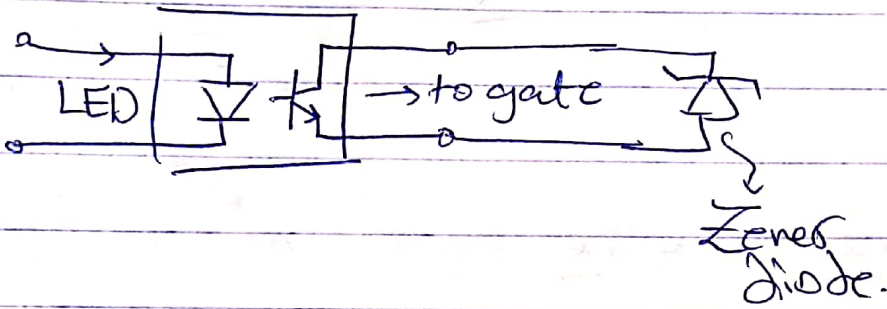


② Zener diode.

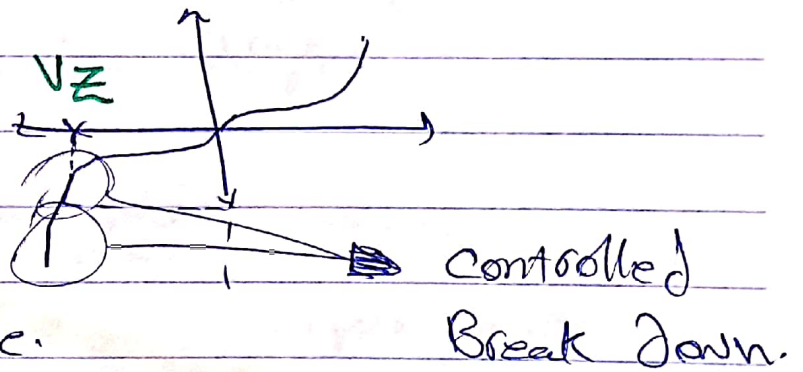
Works in the reverse & the forward biasing. to limit the voltage.



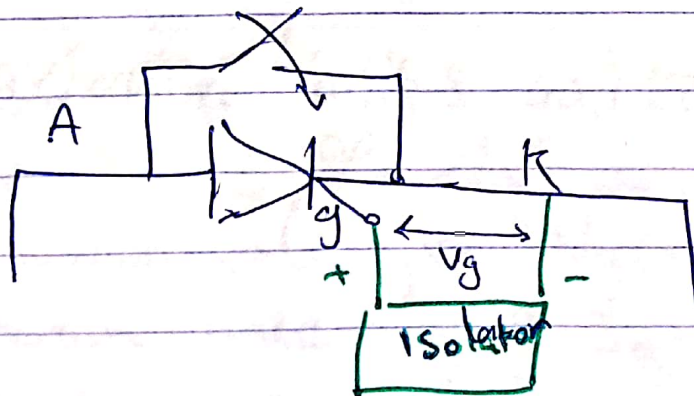
② To isolate power part of the Electronics part from each other.



① Gate characteristics

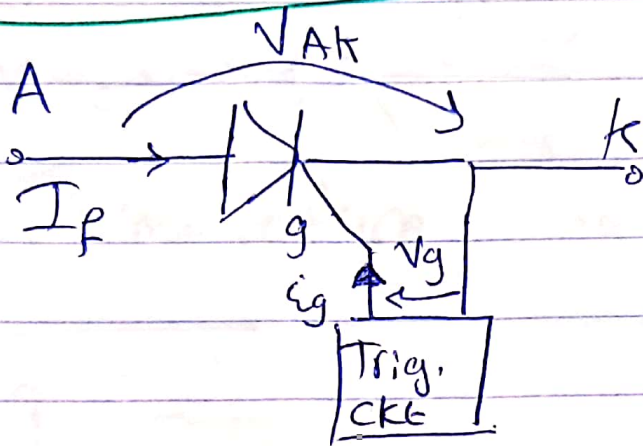

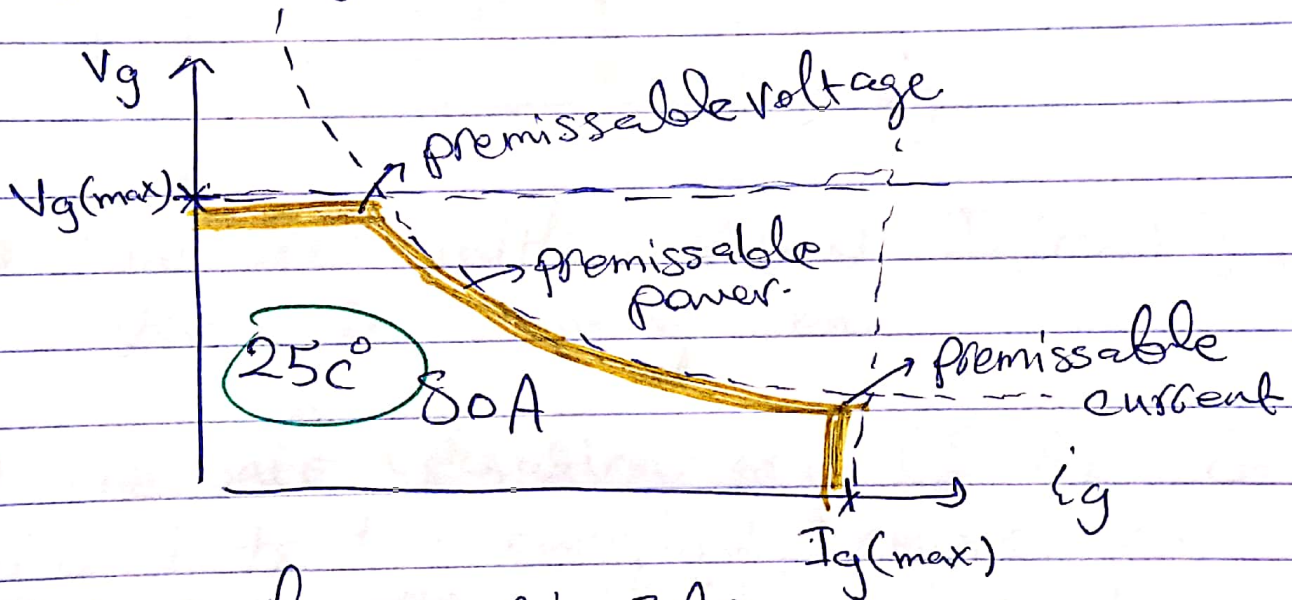● $V_g = f(I_g)$ under certain ambient temperature.



● SOA: Safe operating Area.


Maximum limits and temperature effect.

- (A) maximum voltage $V_g(\max)$.
- (B) maximum gate current $I_g(\max)$.
- (C) maximum power limits $P_g(\max)$

Power is a constant under a variable current

$$P_{max} = V_g \cdot I_g, \quad V_g = \frac{P_{max}}{I_g}$$

If Temperature changes

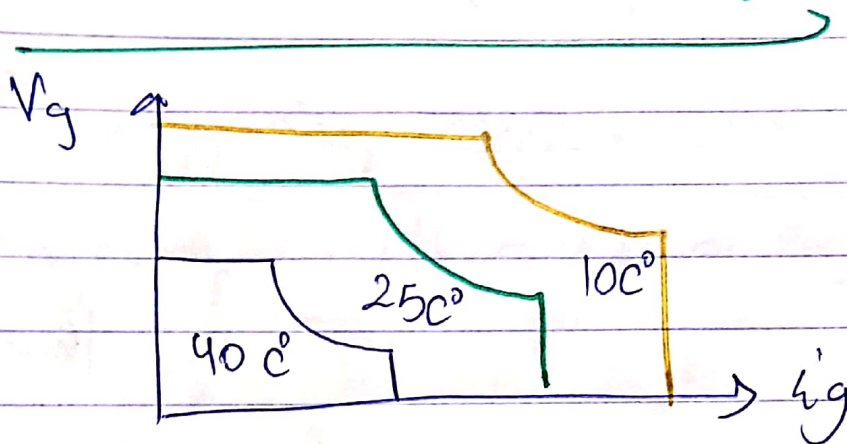

The area within $V_g(max)$, $I_g(max)$ & $P_g(max)$ is the safe operating area.


The safe operating area (SOA) is directly related to the ambient temperature.

→ SOA ↑ if $T_{ambient}$ is lower.
→ SOA ↓ if $T_{ambient}$ is higher.

SCR characteristics


manufacturer's data

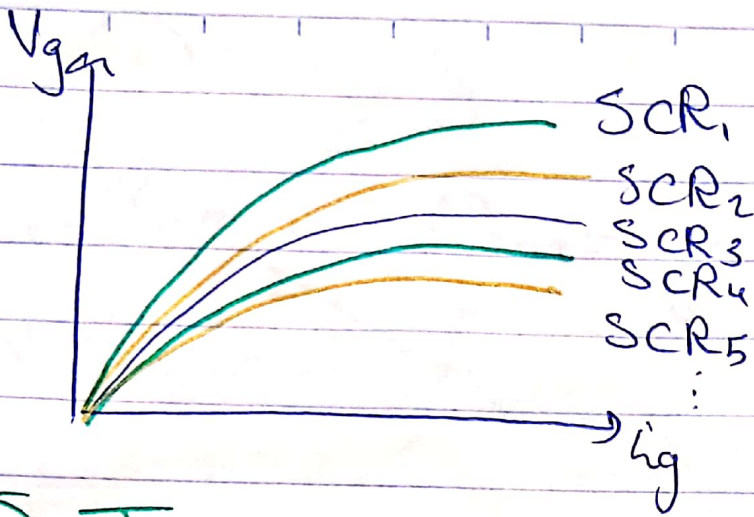→ usually a test is on a family of SCR's.




③ Triggering circuit characteristics

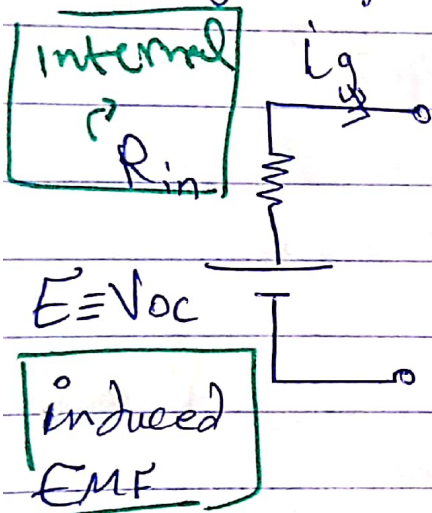Triggering circuit is a power supply.
 → (Dc power supply)



$$V_g = V_{oc} - I_g R_{in}$$

or
 open circuit

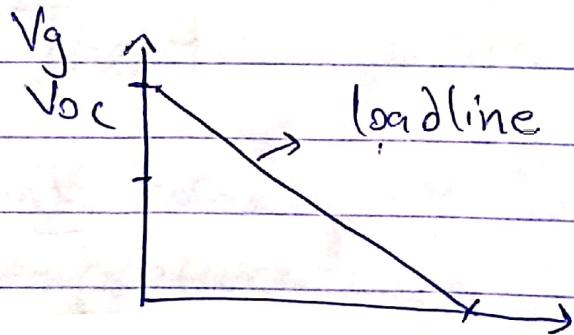


The slope is R_{in} dependent.
 (Triggering circuit design dependent)

I_{sc}
 short circuit current

- a) at no load $\rightarrow I_g = \phi$, $V_g = V_{oc}$
- b) Short circuit condition (SCC): $V_g = 0$

$$\begin{aligned} V_{oc} &= I_g * R_{in} \\ &= I_{sc} * R_{in} \Rightarrow R_{in} = \frac{V_{oc}}{I_{sc}} \end{aligned}$$

① ② & ③ Together.

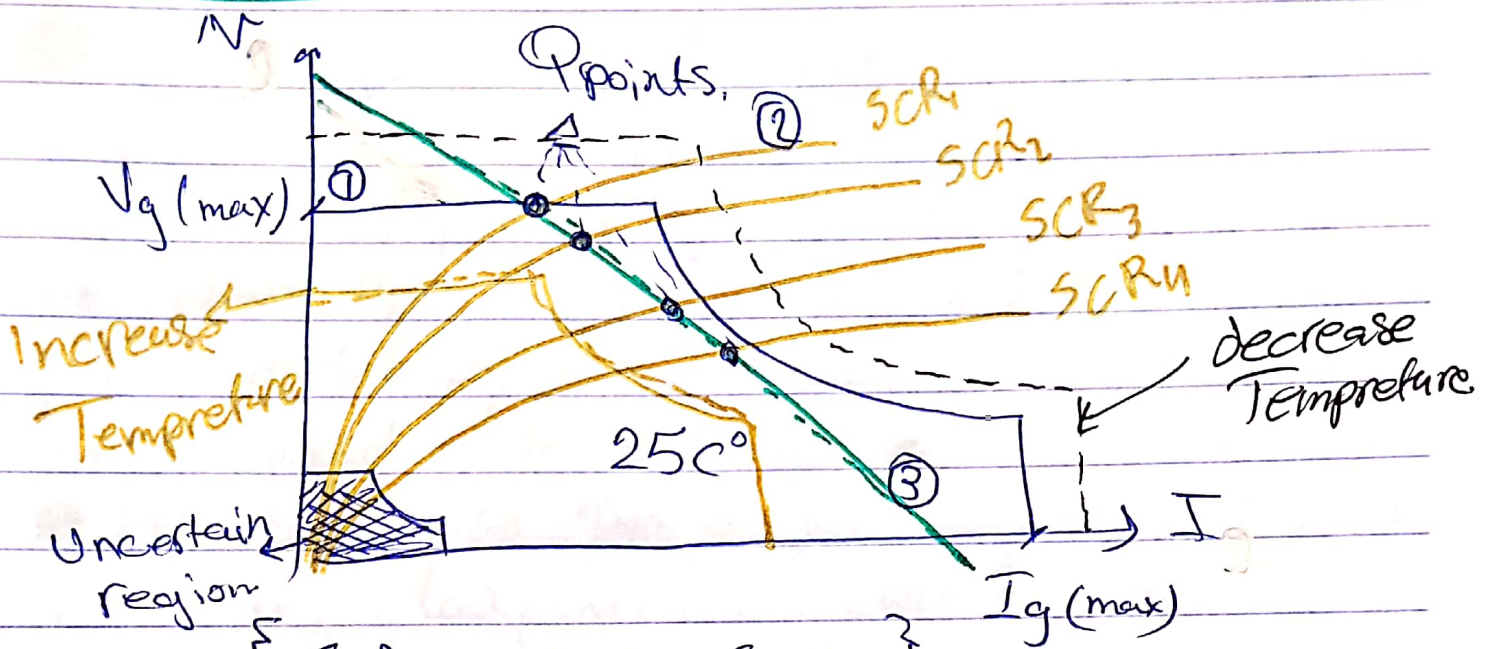

- $\{ SCR_2 - SCR_3 - SCR_4 \}$ in The SOA.

- SCR_1 on the limit (Distractive.)

- if we decrease The temperature in black •

all SCR's will work normally in SOA.

- if we increase Temperature

in yellow •

non of the SCR's will work.

→ we don't know if SCR's will work in The Uncertain region (small current values).

Duty cycle



if T_{off} long Then maximum power limits are Higher.

Analysis

* Single-phase, half wave, controlled Rectifier

→ number of phases : single phase, three phase

→ wave type : half wave, full wave


→ controllability : controlled, uncontrolled.

→ uncontrolled $\alpha = 0$, controlled α has a value.

● In practical life there is no half wave. (why?)

↳ ripples, low power, DC current in supply and harmonics.

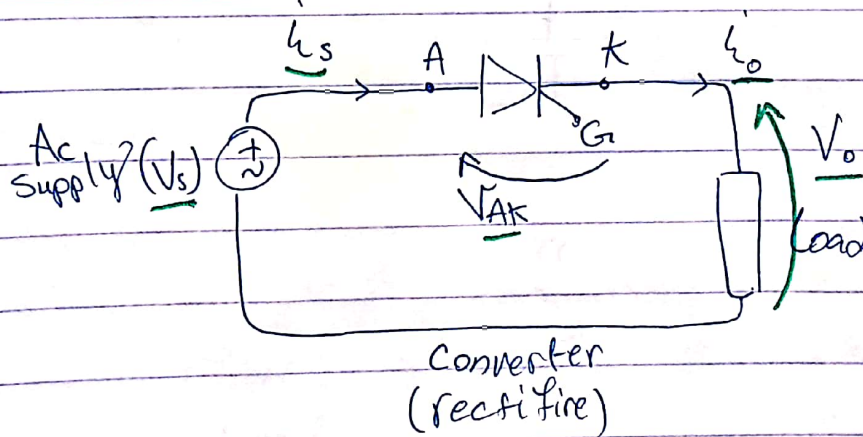power circuit (one thyristor; simplest case).




● Half-wave rectifier on a pure resistive load.

→ When choosing Thyristors

1 peak value (most important)


2 RMS value

3 AVG. value.

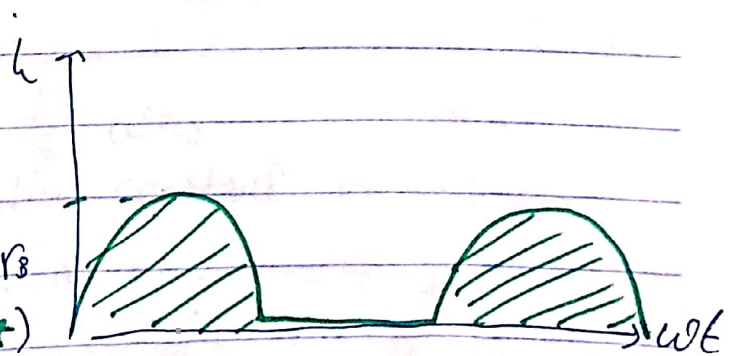


possible loads.

[1] Resistive load.

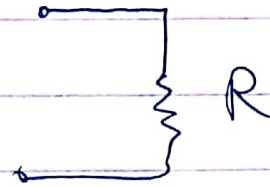


[2] R-L load.

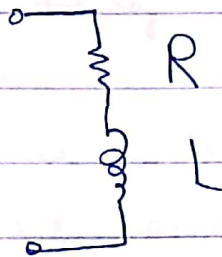


ex: • a field circuit for any machine.
• Industrial Heating System.

[3] R-E load

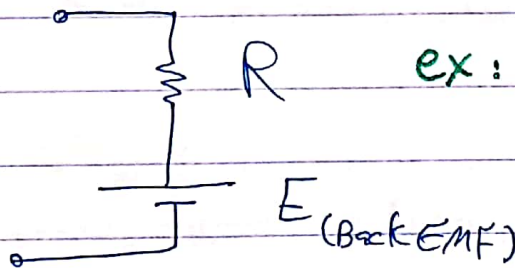



ex: Battery.

[4] R-L-E load.

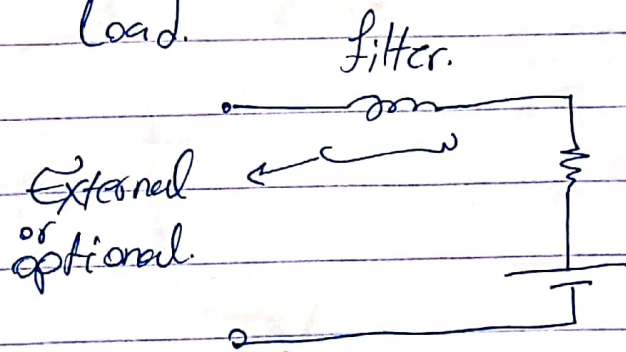

ex: • Dc motor.
• Battery with Smoothing current filter in series.

⊕ in R-L-E loads, if L was very big \Rightarrow virtually constant current.
 \rightarrow so much like a pure Dc.

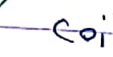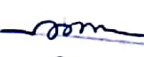we should not charge a battery coil with ripple or Pulsating current add   filter.

Expected waveforms of interest


i_s , V_s , V_{AK} , i_o , V_o .

→ Define α , the firing angle or triggering angle or phase delay angle.

→ α : the angle at which the SCR is triggered (faster), measured with respect to the zero crossing point of the supply voltage. After which; the SCR becomes forward biased.

⊗ Why do we need V_{AK} ?

→ obtain PIV: peak inverse voltage.

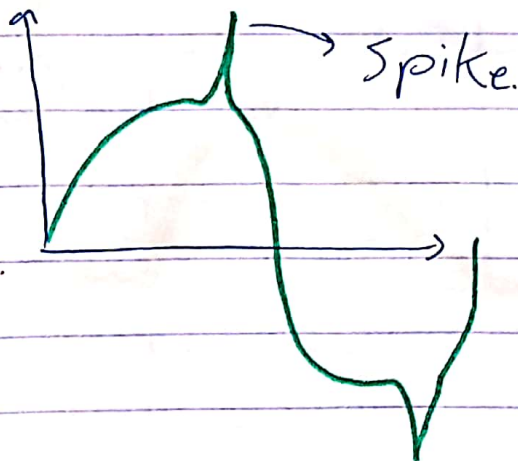

- capacitor added
- Spikes \downarrow \rightarrow i_c \downarrow i_{AK}
- The capacitor is called a snubber.





• $0 \leq \alpha \leq 180^\circ$
 uncontrolled. ↓ ↓

Zero output

(Switch off) \rightarrow if pure resistive

α : the control parameter.

Inductive load, current will lag.

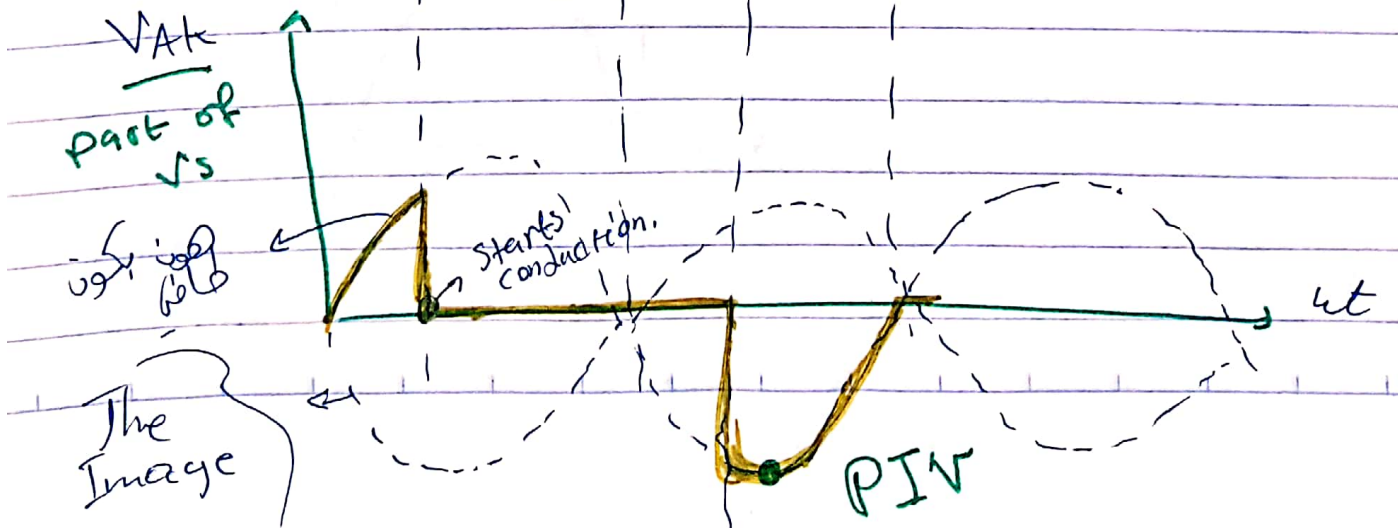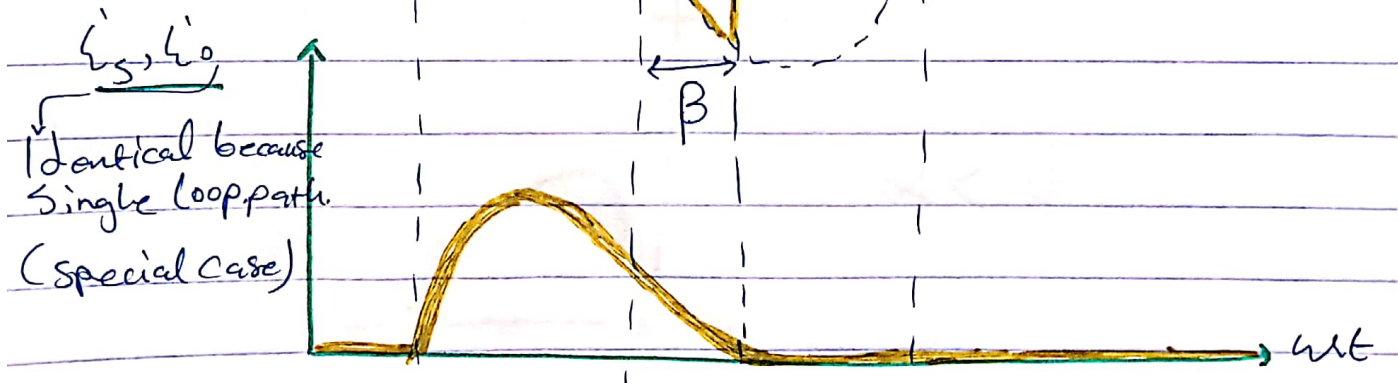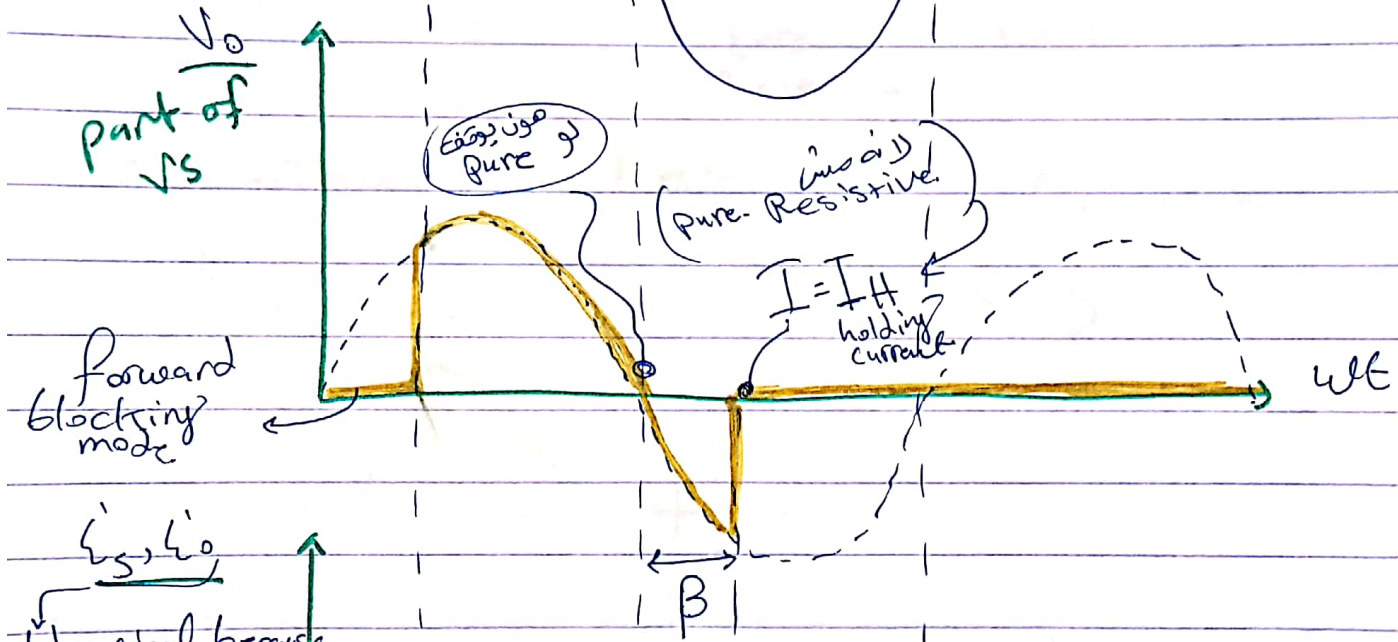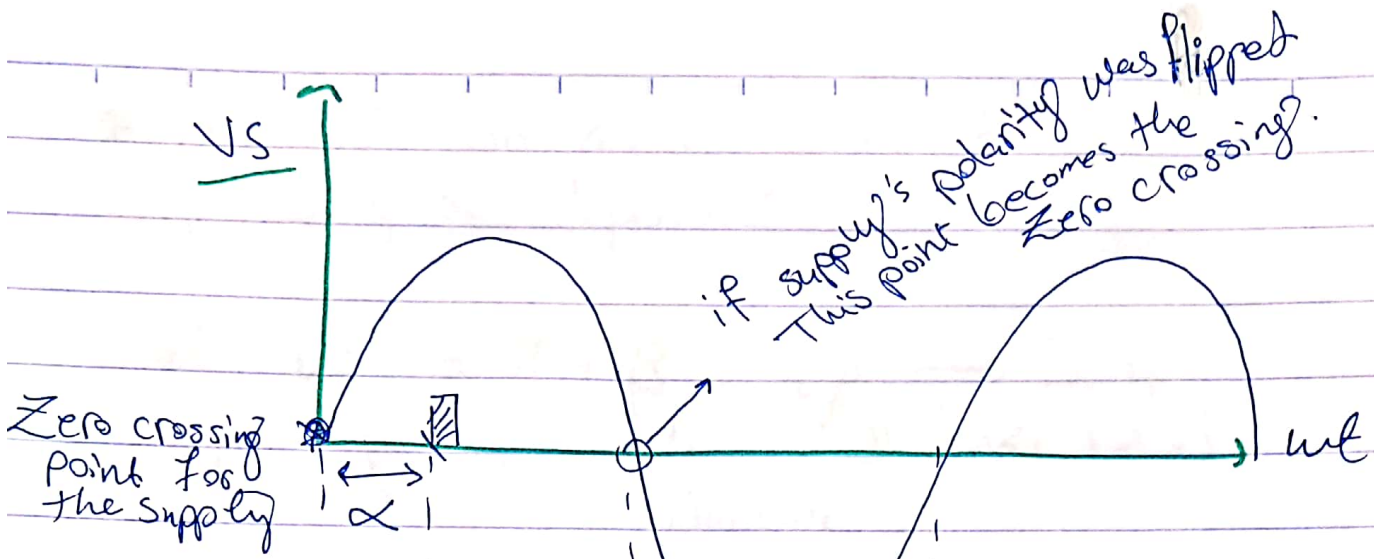


β : Extention angle. β \propto load & α dependant.


at $\omega t = \pi + \beta$, $i_f \rightarrow I_H$
 Inductive.

$\beta = 0$, pure resistive.

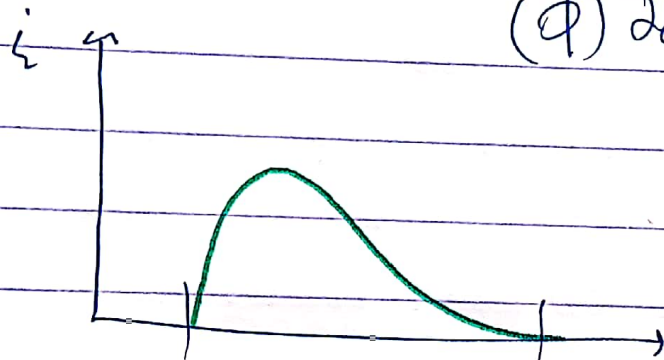• Current can be:-
 (ϕ) depends on load phase angle



$\alpha > \phi$

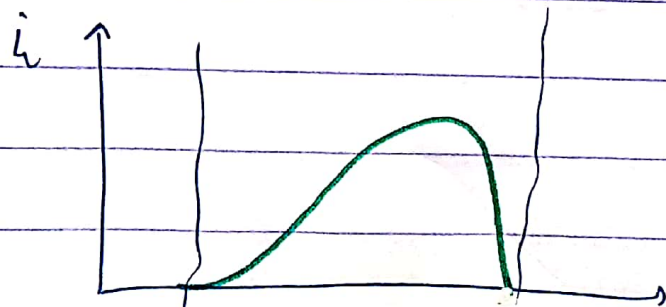

$\alpha < \phi$




$\alpha = \phi$

In order to turn off a Thyristor we want the current to be less than I_H & Reverse bias.

We have two boundary limits:


Primary α , $I = I_{\text{latching}}$ } in normal case
 Secondary β , $I = I_{\text{holding}}$ } we assume both = zero except a special case we will learn about.

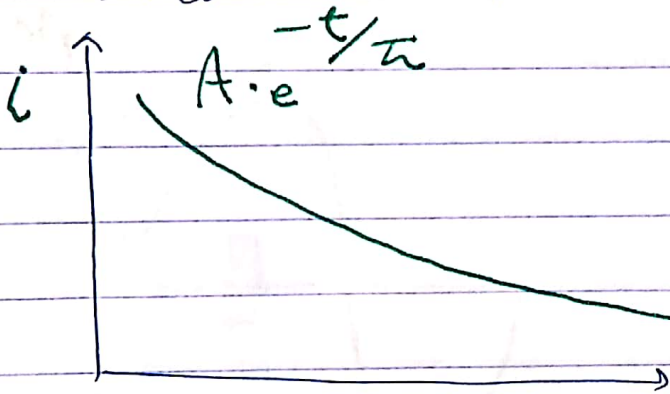if we have a natural decay without a forcing function (free wheeling)



$I_H \quad A \cdot e^{-5t}$

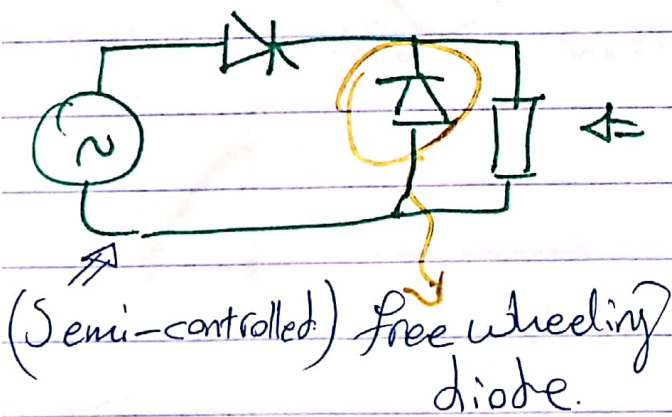
it will reach zero in ∞ but I don't have ability to reach ∞ .



having a free wheeling is going to help us turn off the Thyristor in the (no forcing function) case.

Analysis:

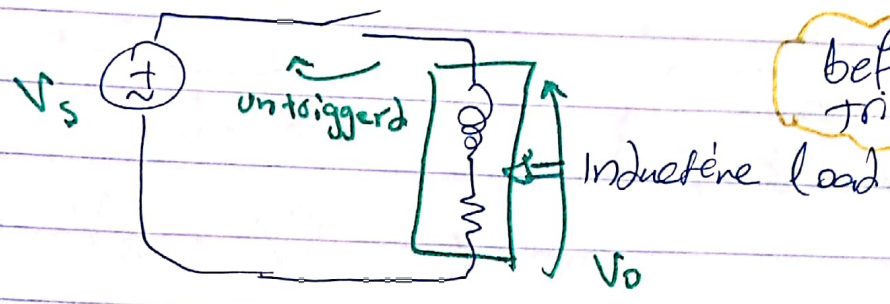half wave Rectifier
 $0 \leq \omega t < \alpha$





before α no triggering, The Thyristor is off



$i_o = 0$
 $V_o = 0$


$V_{AK} + V_o = V_s$
 Zero

$\therefore V_{AK} = V_s$

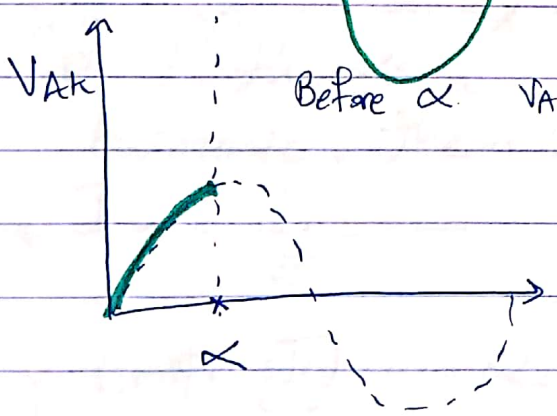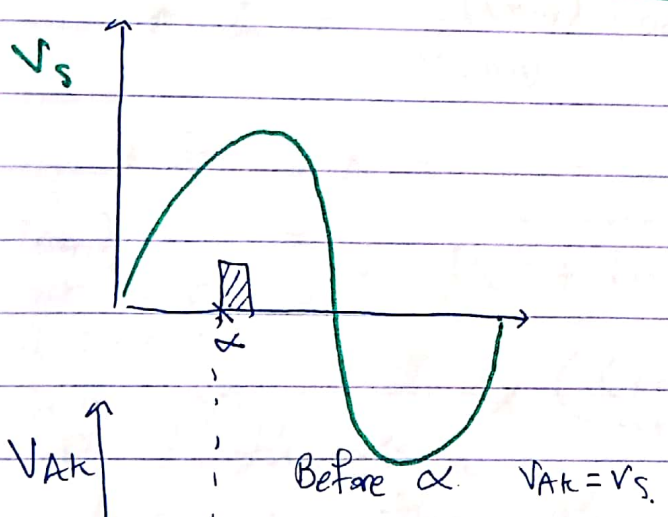

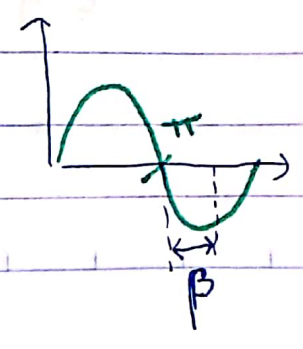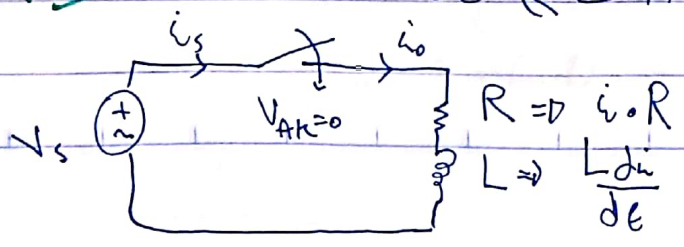[2] $\alpha \leq \omega t < [\pi + \beta]$



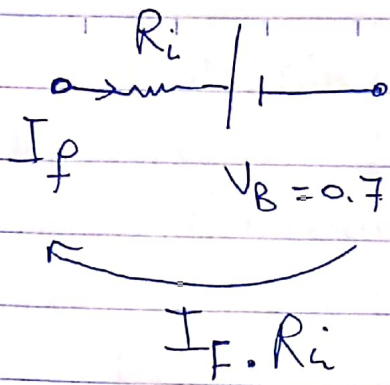

- losses. 1 (giga)
- SCR (switch)
 - ① Turn on loss.
 - ② Turn off loss.
 - ③ Steady state loss.

● $V_s - V_{AK} - V_o = 0$

$V_o = V_s$, $i_s = i_o = i$ #

Assume and define:-

→ $V_s = V_m \sin \omega t$

* $\omega = 2\pi f$ → supply frequency.

* $\tau = \frac{L \text{ (Henry)}}{R \text{ (ohm)}}$ load time constant (seconds)

* $Z = R + j\omega L$

load impedance at supply frequency. $Z = \sqrt{R^2 + (\omega L)^2} \angle \phi$, where

* (Load phase angle) $\phi = \tan^{-1} \frac{\omega L}{R}$ at supply frequency.

● If there's a Harmonic, then the impedance will change.

* $I_m = \frac{V_m}{Z}$

Cont. [2] $\alpha \leq \omega t \leq [\pi + \beta]$

→ KVL $V_s = i.R + L \frac{di}{dt}$

$V_m \sin(\omega t) = i.R + L \frac{di}{dt}$

$$V_m \sin(\omega t) = i \cdot R + L \frac{di}{dt}$$

This is a 1st order non-homogeneous Differential Equation.


$$i = i_f + i_c \quad (\text{in math})$$

Forced Response
Complementary Solution

$$i = i_s + i_n \quad (\text{in power electronics})$$

Steady state
natural

if :

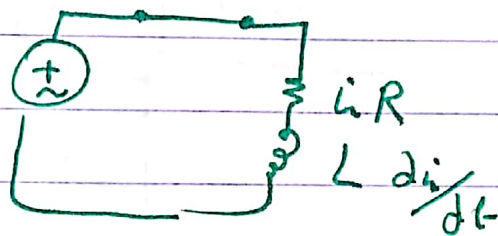

$$i = I_m \sin(\omega t - \phi) + A e^{-t/\tau}$$

Forced Function.
natural.

* A: integration constant


↳ by applying the initial current condition.



$$i = 0 \text{ at } \omega t = \alpha$$

$$0 \leq \alpha \leq 180^\circ$$

Action when triggered

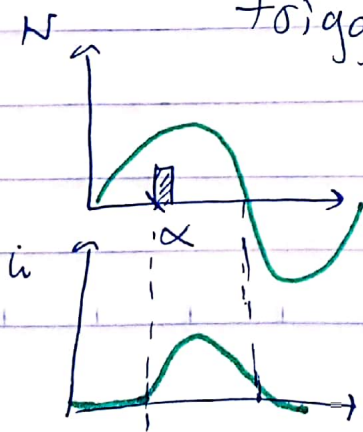

$$e^{-t/\tau} \Rightarrow e^{-t/\tau} = -\frac{t}{\tau} \cdot \omega$$

$$\boxed{e^{-\frac{R\omega t}{L}}} = \boxed{e^{\rho \omega t}} \quad \rho = -\frac{R\omega}{L}$$

$$\rho = \frac{1}{\tau \omega} \quad \tan \rho = -\cot \phi$$

e^{pwt} $\rightarrow i = I_m \sin(\omega t - \phi) + A \cdot e^{p\omega t}$

((applying The initial condition))

$0 = I_m \sin(\alpha - \phi) + A \cdot e^{p\alpha}$

$\therefore A = -I_m \sin(\alpha - \phi) \cdot e^{-p\alpha}$

$i = I_m \sin(\omega t - \phi) - \underbrace{I_m \sin(\alpha - \phi)}_A \cdot e^{p\omega t}$

• If Resistive and uncontrolled

$L = 0, \alpha = 0$





$\phi = 0$
in Resistive loads

$\dots I_m \sin(\phi) \cdot e^{p\alpha} \rightarrow I$
 $\sin(\text{Zero})$

- $i = I_m \sin(\omega t - \phi) - I_m \sin(\alpha - \phi) \cdot e^{-\rho \omega t}$

$\alpha = \phi$ special case & usually special cases are in the Exam.

- If asked to draw Typical waveforms:

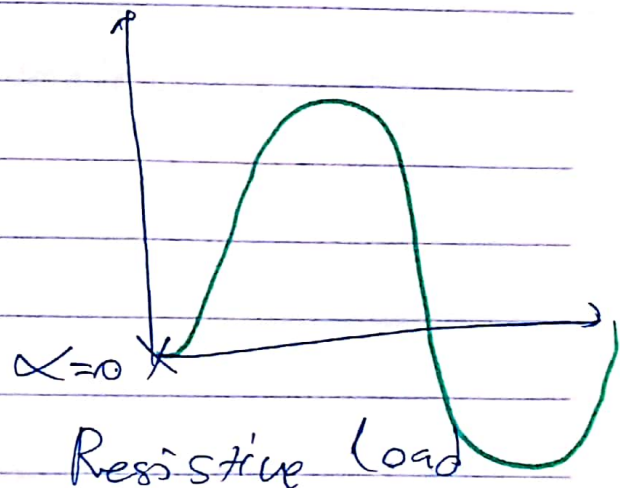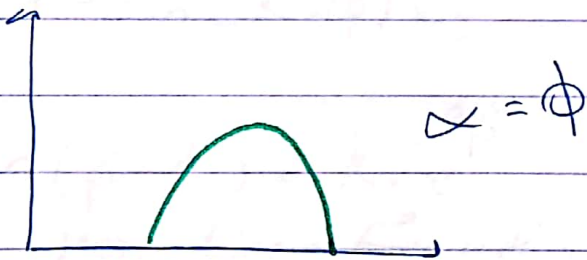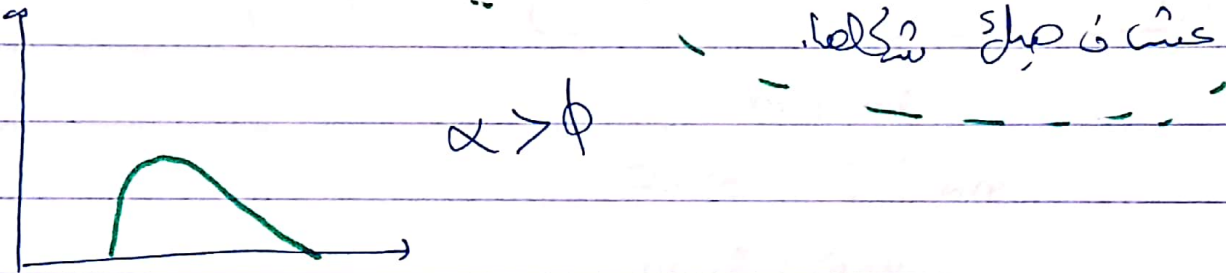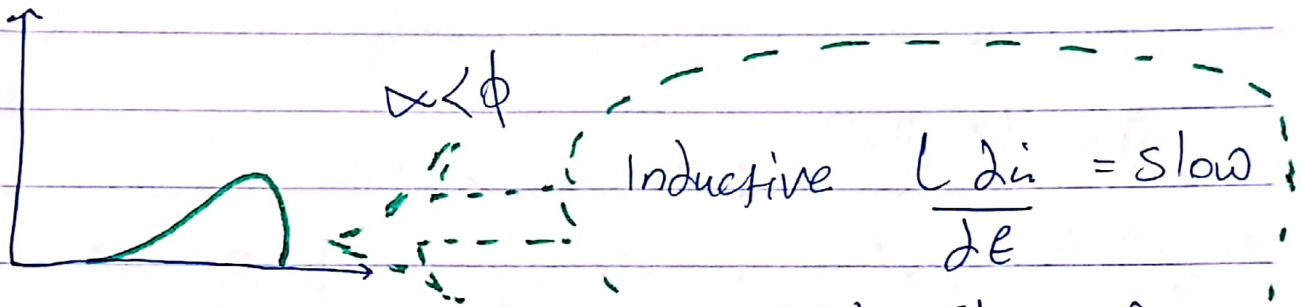

- To calculate β = Apply the final current condition where $\omega t = \pi + \beta \Rightarrow \boxed{i = 0}$

So

$$i = I_m \sin(\omega t - \phi) - I_m \sin(\alpha - \phi) \cdot e^{-\rho \alpha} \cdot e^{\rho \omega t}$$

$$\hookrightarrow 0 = I_m \sin(\pi + \beta - \phi) - I_m \sin(\alpha - \phi) \cdot e^{-\rho \alpha} \cdot e^{\rho(\pi + \beta)}$$

$$0 = -\sin(\beta - \phi) - \sin(\alpha - \phi) \cdot e^{-\rho(\pi - \alpha)} \cdot e^{\rho \beta}$$

$$\sin(\beta - \phi) = \underbrace{-\sin(\alpha - \phi) \cdot e^{-\rho(\pi - \alpha)} \cdot e^{\rho \beta}}_{\text{constant}}$$

constant

since α & ϕ are

$$k = -\sin(\alpha - \phi) \cdot e^{-\rho(\pi - \alpha)} \quad \text{usually given.}$$

$$\sin(\beta - \phi) = k \cdot e^{\rho \beta}$$

non-linear Equation = transcendental Equation.

- To evaluate β

[1] can be done [applying any Numerical Technique]

[2] Trial & Error.

[3] Graphical solution.

Graphical Solution.

Solving $\sin(\beta - \phi) = k \cdot e^{\rho\beta}$

\downarrow \downarrow \downarrow
 +ve. zero -ve

if $k=0$, β & ϕ are equal.


• In graphical solution:

$\rightarrow \sin(\beta - \phi) = f_1$ (function)

$\rightarrow k \cdot e^{\rho\beta} = f_2$ (function)

(f_1 & f_2)

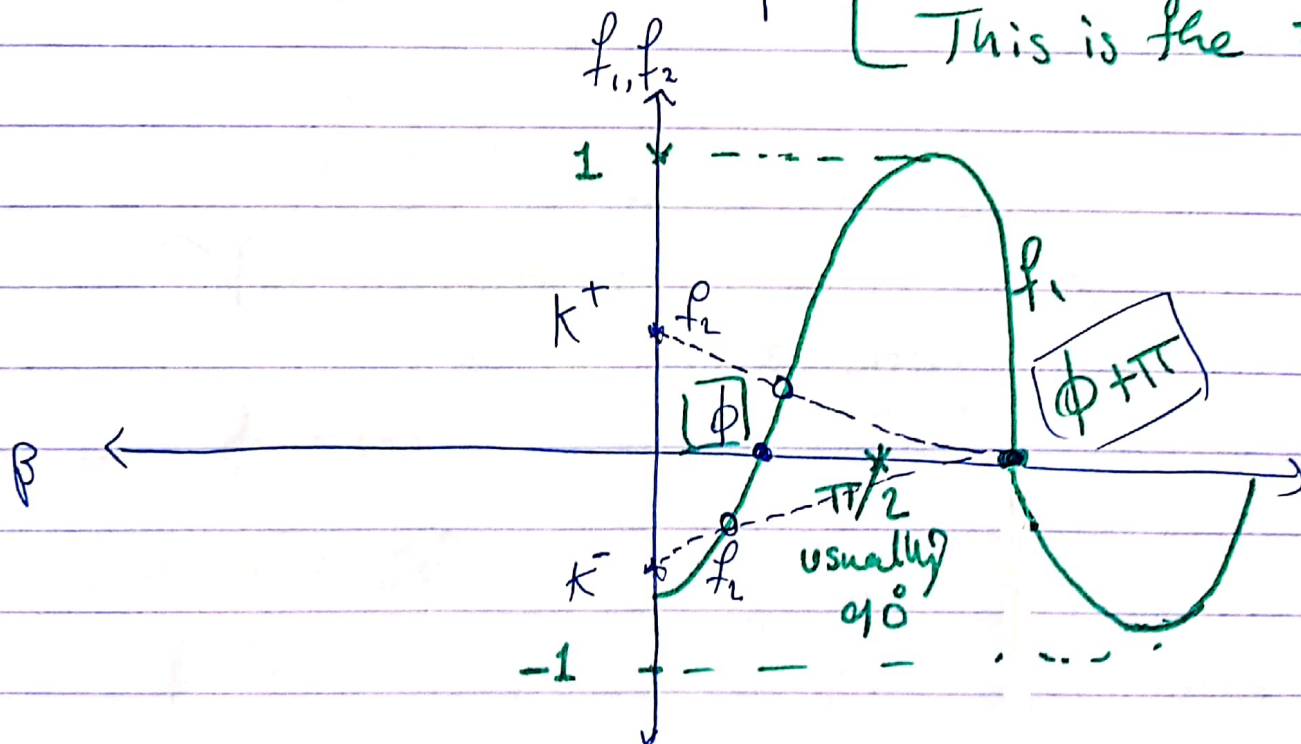Vs β . [when they intersect.]
This is the solution.]



if $\beta=0$ $f_1 = \text{exponential}$

• $k = \ominus \sin(\alpha - \phi) \cdot e^{D(\pi - \alpha)}$

always +ve.

if $\alpha > \phi \Rightarrow \sin(\alpha - \phi) \Rightarrow +ve$
 and $k = \text{negative}$

if $\alpha < \phi \Rightarrow \sin(\alpha - \phi) \Rightarrow -ve.$
 and $k = \text{positive}.$

• $f_2 \& f_1$ in case +ve (k)

The first intersect is $\beta \approx \phi$
 High inductivity.

• $f_1 \& f_2$ case -ve (k)

$\beta \approx \phi$

In Multiple choice Questions.

$\rightarrow \phi = 60^\circ$

$\rightarrow \alpha = 30^\circ$

$\beta ??$

- a) 30
- b) 60
- c) 62
- d) 58
- e) 31.5
- f) 28.7


Since
 $\alpha < \phi$
 $\phi = 60$
 62
 answer.

- once you find $\beta \Rightarrow$ calculate $V_o(\text{avg})$]
 [Integration.]

$$V_o(\text{avg}) = \frac{1}{T} \int_{t_0}^{t_0+T} V_o(t) dt.$$

$t \rightarrow$ radians (always).

- period = 2π

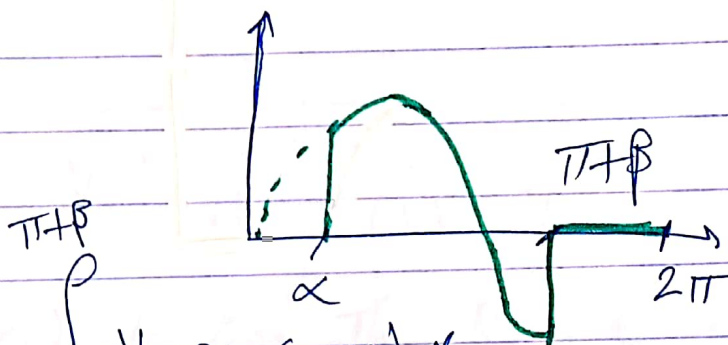

$$V_o(\text{avg}) = \frac{1}{2\pi} \int_{\alpha}^{\pi+\beta} V_m \sin(\omega t) d\omega t.$$

$$V_o(\text{avg}) = \frac{V_m}{2\pi} \left[-\cos(\omega t) \right]_{\alpha}^{\pi+\beta}$$

$$\frac{V_m}{2\pi} [-\cos(\pi+\beta) + \cos\alpha]$$

$$V_o(\text{avg}) = \frac{V_m}{2\pi} (\cos\alpha + \cos\beta)$$

$$I_o(\text{avg}) = \frac{V_o(\text{avg})}{R}$$

$$R. \Rightarrow Z = R + jX$$

only
R avg DC

$$I_o(\text{rms}) = \frac{V_o(\text{rms})}{Z}$$

30

$$V_o(\omega t) = V_o(\text{avg}) + \sum_{n=1}^{n=\infty} V_m(n) \cdot \sin(n\omega t + \psi_n)$$

ex

$$60 + 40 \sin(\omega t - 25^\circ) + 28 \sin(2\omega t - 40^\circ) + 10 \sin(3\omega t - 87^\circ)$$

$$V_o(\text{rms}) = \sqrt{60^2 + \left(\frac{40}{\sqrt{2}}\right)^2 + \left(\frac{28}{\sqrt{2}}\right)^2 + \left(\frac{10}{\sqrt{2}}\right)^2}$$

now If asked to find The Ripple Factor:-
we must find

$$\Rightarrow I_{\text{rms}}$$

$$V_o(\text{rms}) = \# \bar{V}_o$$

$$V_o(\omega t) = I_o(\text{avg}) + \sum \dots \frac{60}{R} \dots$$

cont. next lecture.

$\frac{40}{Z_1} \dots$

● Single phase Half wave controlled Rectifier

$$\rightarrow V_o(\text{avg}) = \frac{V_m}{2\pi} (\cos \alpha + \cos \beta)$$


Special case (resistive load), $\beta = 0$,

$$V_o(\text{avg}) = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$I_o(\text{avg}) = \frac{V_o(\text{avg})}{R}, \quad I_o(\text{rms}) = ??$$

HARD.
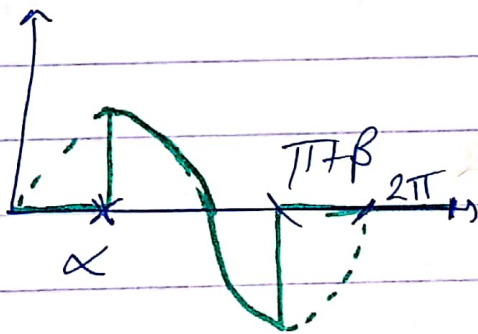
$$V_o(\text{rms}) = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi+\beta} V_m^2 \sin^2 \omega t \cdot d\omega t}$$



$$V_o(\text{rms}) = \sqrt{\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi+\beta} (1 - \cos 2\omega t) d\omega t}$$

(2)

$$= \sqrt{\frac{V_m^2}{4\pi} \left(\omega t - \frac{1}{2} \sin 2\omega t \right) \Big|_{\alpha}^{\pi+\beta}}$$

$$V_o (rms) = \sqrt{\frac{V_m^2}{4\pi} \left[\pi + \beta - \alpha - \frac{1}{2} \sin(2\beta) + \frac{1}{2} \sin(2\alpha) \right]}$$

⇒ all α values are radians.

or

$$V_o (rms) = \sqrt{V_o (avg)^2 + \sum_{n=1}^{\infty} \left(\frac{V_m(n)}{\sqrt{2}} \right)^2}$$

$$i_o (rms) = \sqrt{\left(I_o (avg) \right)^2 + \sum_{n=1}^{\infty} \left(\frac{I_m(n)}{\sqrt{2}} \right)^2}$$

$$I_m(n) = \frac{V_m(n)}{Z(n)}$$

$$Z(n) = R + j(n)\omega L$$

$$= \sqrt{R^2 + (n\omega L)^2} \left[\tan^{-1} \left(\frac{n\omega L}{R} \right) \right]$$

R.F


ripple factor.

$$= \frac{\sqrt{V_o (rms)^2 - V_o^2 (avg)}}{V_o (avg)}$$

i_s and i_o are the same.

To calculate P.F

power factor.

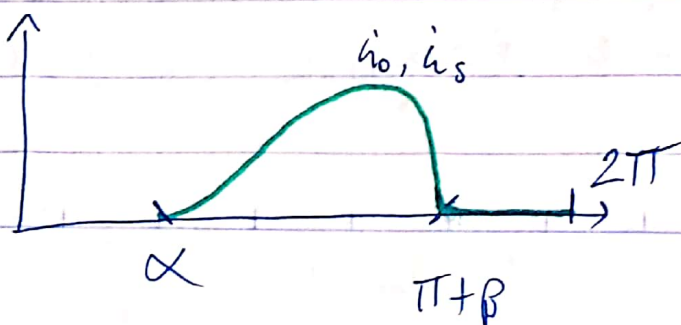

~~P.F = cos ϕ~~
not acceptable

$P.F = \cos \phi$ ^{only} The case of V_L, V_s &

Power Factor = $\frac{\text{Real power}}{\text{apparent power}}$ ^{i_L, i_s are pure sin functions.}

apparent power = $V_s \times I_s \rightarrow \text{Supply?}$
(rms) (rms)

ex::

$V_o(t) = 120 + 80 \sin(\omega t - 30^\circ) + 40 \sin(2\omega t - 60^\circ)$
 + ---- consider the first two components.

$\rightarrow i_o(t) = \frac{120}{R} + \frac{80}{Z_1} \sin(\omega t - 30 - \phi_1) + \frac{40}{Z_2} \sin(2\omega t - 60 - \phi_2)$

ϕ_1 & ϕ_2 can be found using This formula

$\phi_{(n)} = \tan^{-1} \left(\frac{n\omega L}{R} \right)$

Using Superposition ((Pout))

$V_s(t) = V_m \sin(\omega t)$

$i_o(t) = \frac{120}{R} + \frac{80}{Z_1} \sin(\omega t - 30 - \phi_1) + \frac{40}{Z_2} \sin(2\omega t - 60 - \phi_2)$

$P_{out} = P_{supply} = P_{in} = I_{s(rms)} \times V_s(rms) \times \cos(30 + \phi_{(1)})$
 Ideal Thyristor ^{pass} so ϕ losses.

[or] $\Phi_1 = \Phi_{(V_1)} - \Phi_{(I_{S1})}$

② $P_{out} = I_o^2 (rms) * R.$

P_{out} in both cases should be the same.

⇒ then we substitute in power factor formula #


Drawbacks of single phase rectifier circuit.

→ Supply current has Non-Zero average value. Destructive if a transformer is used due to a core saturation.

→ Reduced voltage & power compared to the full wave rectifier

Why didn't we say "reduced current"?

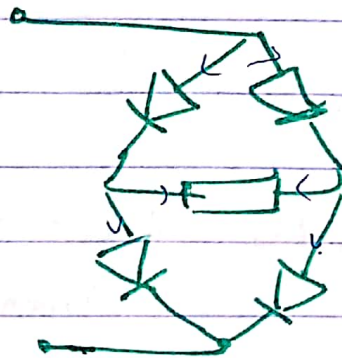لا بد من اى مرحلة من المراحل
 في دائرة الجهد و التيار
 في دائرة التردد و الجهد
 في سلسلة من
 اذا كان الجهد $\left(\frac{10}{A}\right)$
 الجهد $\left(\frac{10}{A}\right)$
 الجهد $\left(\frac{10}{A}\right)$
 الجهد $\left(\frac{10}{A}\right)$



As for voltage :- $\frac{V_m}{2\pi} (\cos\alpha + \cos\beta)$ HWR


دو طرفی
تعمیراتی $\frac{V_m}{\pi} (\cos\alpha + \cos\beta)$ FWR

due to these drawbacks,

Single phase full wave Rectifier circuit.

→ Two configurations:


- ① Bridge circuit.
- ② center tapped.

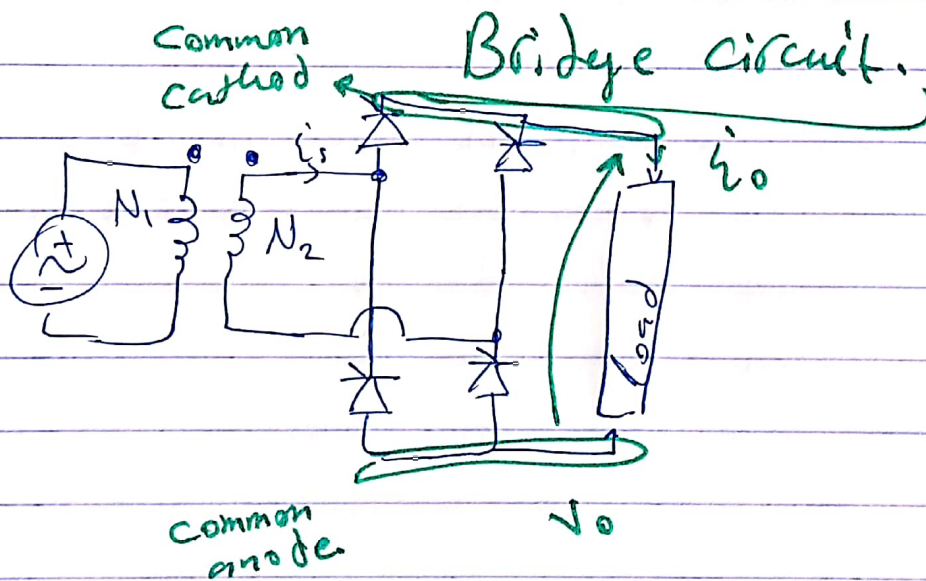

Transformer is optional ← only used to match load voltage requirements.

I_s , $S =$ if transformer exist Secondary?
if no transformer then
Supply

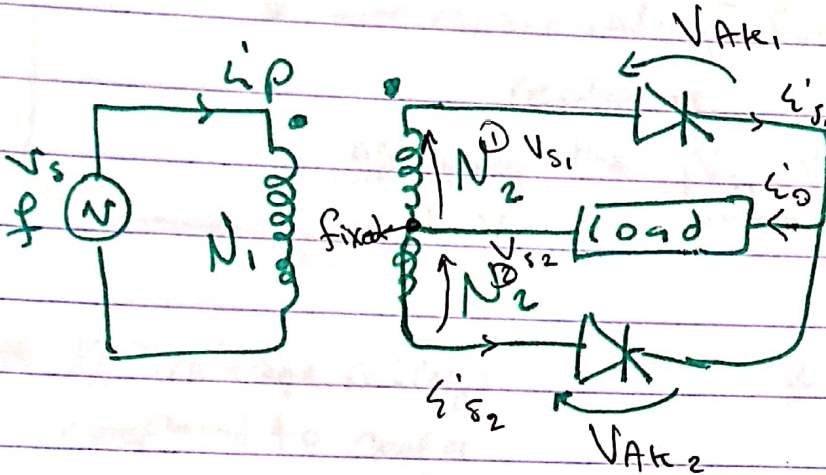- Full wave Rectifier
 - 1) Bridge Rectifier (optional Transformer)
 - 2) Center-tapped Rectifier (Transformer is a must)



not like an autotransformer.

- V_{s1} , V_{s2} have the same direction because they have the same core & are wind up with the same conductor.
- When $N_2^{(1)}$ is on, $N_2^{(2)}$ is open circuit.
- Center-tapped Rectifier has more windings, weights more & expensive compared to the bridge rectifier.
- $i_o = i_{s1}$ or i_{s2} , depending on which half cycle it's in.
- Average voltage is the same if $V_s = V_{s1} = V_{s2}$ in both cases, and that is usually the case.
So we choose bridge circuit.
Transformer.) 1 0.0g Jeds, Lo

Bridge Rectifier

* 4 - Switches.

• Same current ratings for both rectifiers.

assuming that

and V_s

$$V_{s1} = V_{s2} = V_s$$

center-tapped Rectifier

* 2 - Switches.

* $\frac{1}{2}$ Voltage ratings compared to center tapped Rectifier.

* double voltage ratings compared to bridge circuit.

* $PIV = V_m$
Peak inverse voltage

* $PIV = 2V_m$

* cheaper SCR's

* Much Expensive SCR's due to high voltage ratings.

* double DV (2 switches in series)

* Δv is half of that of bridge circuit.

* higher power loss.

* less power loss.

* more requirements and complications.

* less triggering circuit requirements.

* transformer is optional.
→ Much cheaper transformer if needed.


* Transformer is a must and it's expensive due to double secondary turns.

- The only Technical feature that is different between bridge & center tapped Rectifiers is the **PIV** every thing else is the same.

$V_{AK} \rightarrow$ Supply 11 center tapped 11

Analysis of single-phase full-wave bridge Rectifier circuit.

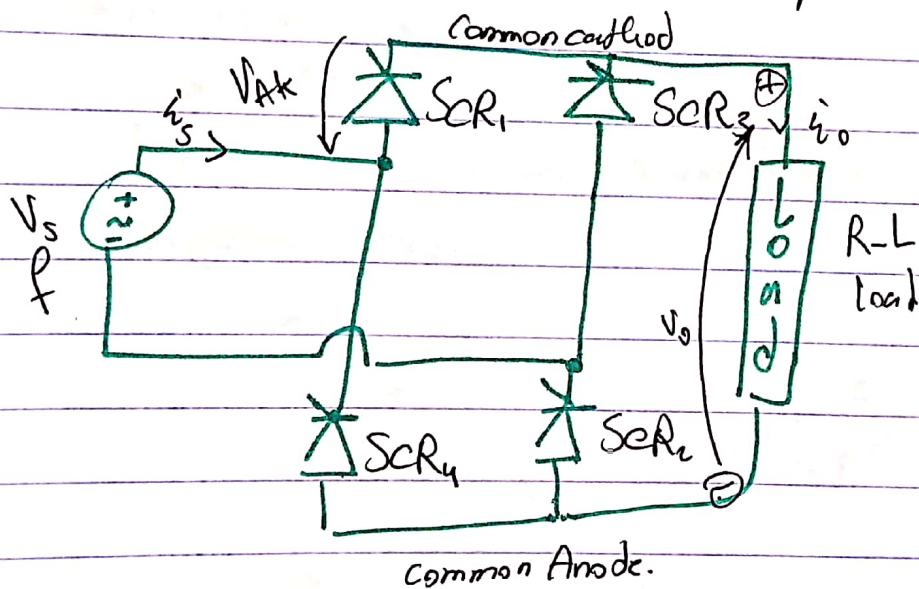
\rightarrow Exam Question: Sketch the power circuit of smth...



- $V_o = +$ number or $-$ number BUT, notation \oplus & \ominus never changes

- numbering of SCR's is very Important
 - V_{AK} is needed for calculations of PIV
 - we should trigger SCR1 & SCR2 simultaneously during positive half cycle.
- $$0 \leq \alpha \leq 180^\circ$$

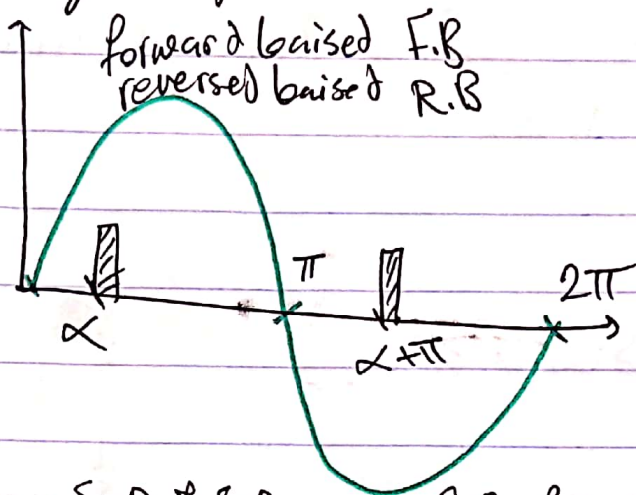
- where α is the firing angle.
at $\omega t = \alpha$



- SCR₁ & SCR₂ are F.B
- SCR₃ & SCR₄ are R.B
- SCR₃ & SCR₄ are R.B
- SCR₁ & SCR₂ are F.B

- if $\alpha + \pi$ was $\alpha + 150$?

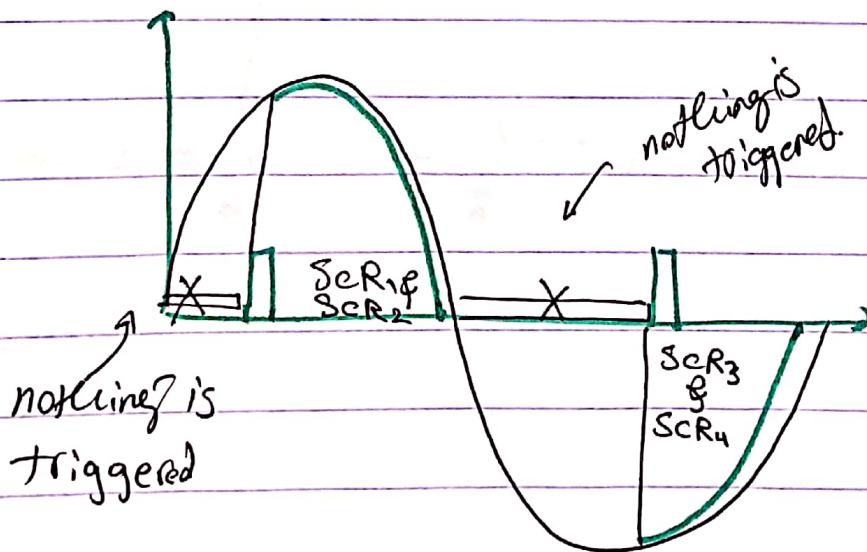Then unsymmetrical waveforms \Rightarrow Dc Avg. in the supply (BAD).




- $0 \leq \omega t \leq \alpha$, and $\pi \leq \omega t < \pi + \alpha$
all SCR's are off, $i_o = i_s = 0$, $V_o = 0$

• $\alpha \leq \omega t \leq \pi$

SCR₁, SCR₂ are triggered & F.B, SCR₃, SCR₄ still off.

• #1

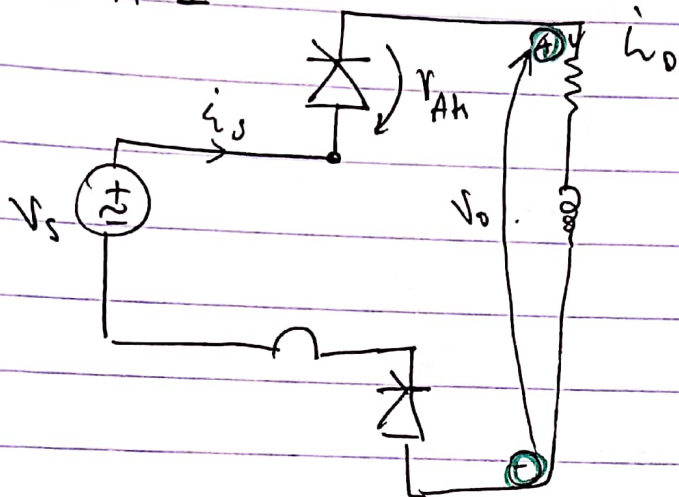


$0 \leq \omega t \leq \pi$


$$V_o \approx V_s$$

$$V_s - V_o - 2V_{AK} = 0$$


$$i_o = i_s$$

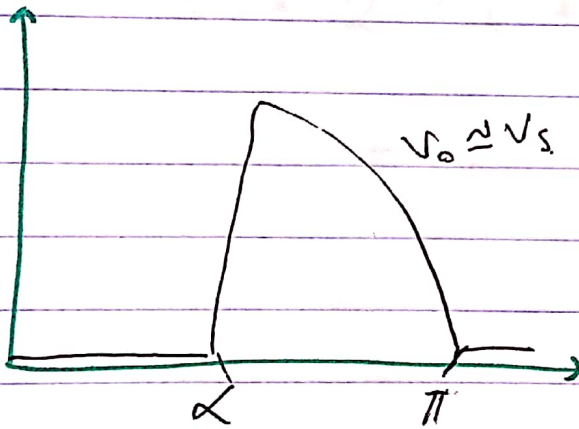

• #2

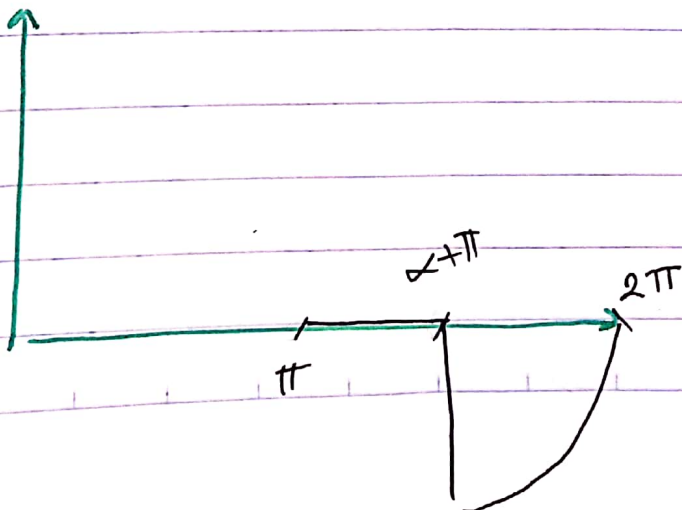



$$\pi + \pi \ll \omega t \ll 2\pi$$

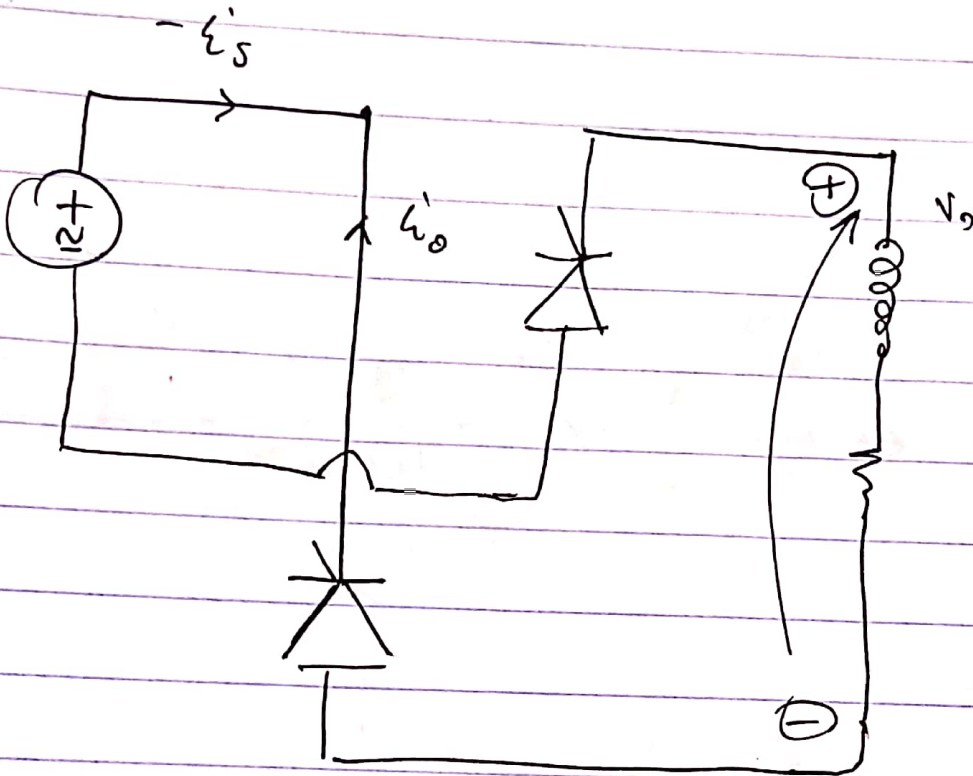



$$v_s + 2V_{AK} + v_o = 0$$

$$-v_s \approx v_o$$

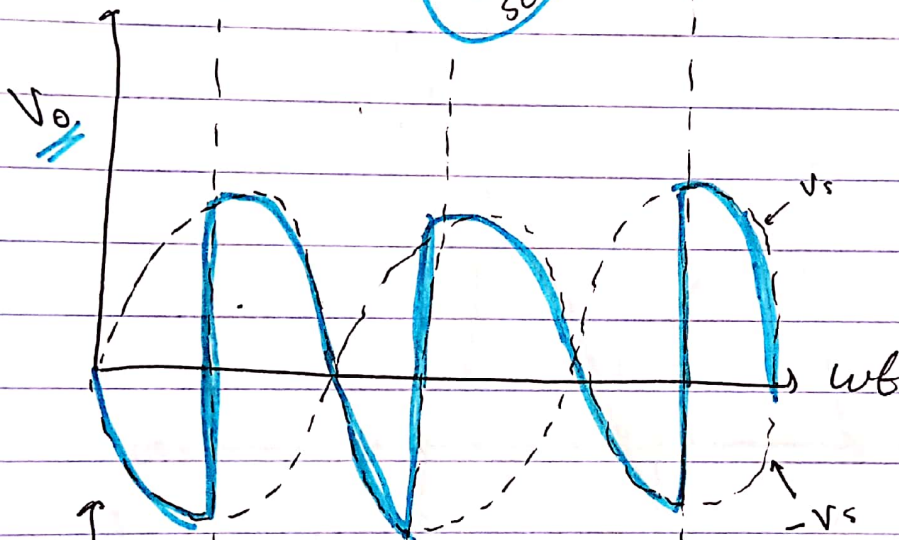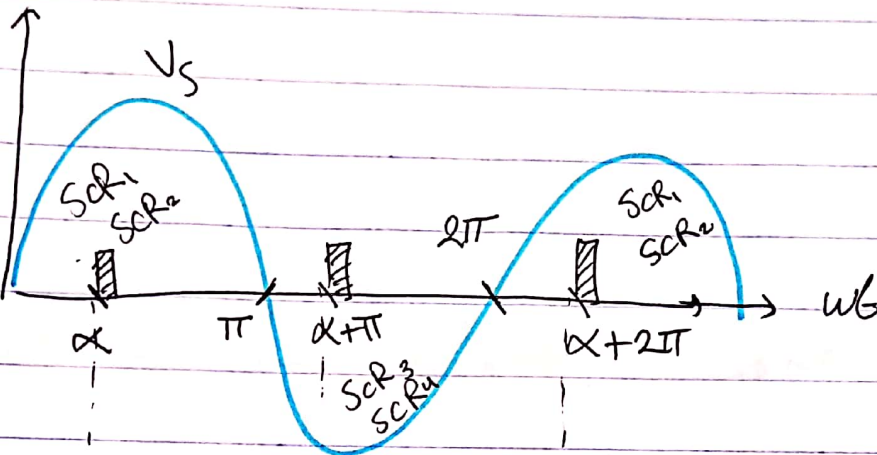● Continuous Current Mode. C.C.M
Expected waveforms




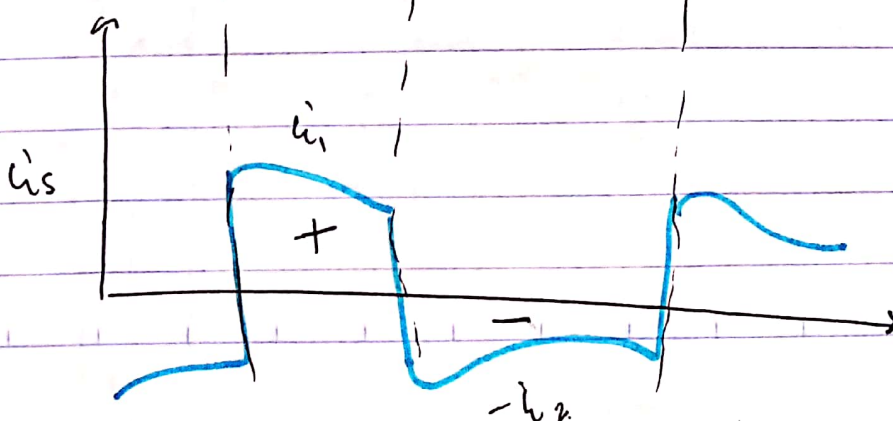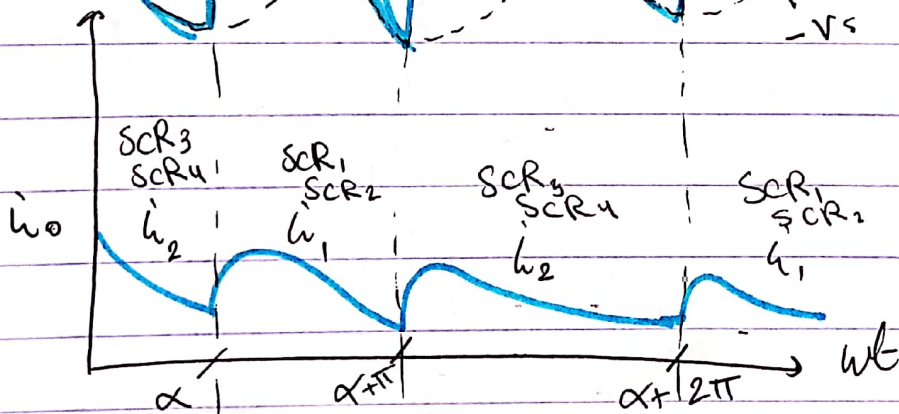- * Question in Exam:-
→ The frequency of one thyristor triggered
- ① half of frequency of supply
 - ② double of frequency of supply
 - ③ same frequency of supply
 - ④ non-of-the-above



$I_s(\text{avg}) = 0$
advantage of full wave bridge Rectifier.

Discontinuous Current mode
D.C.M

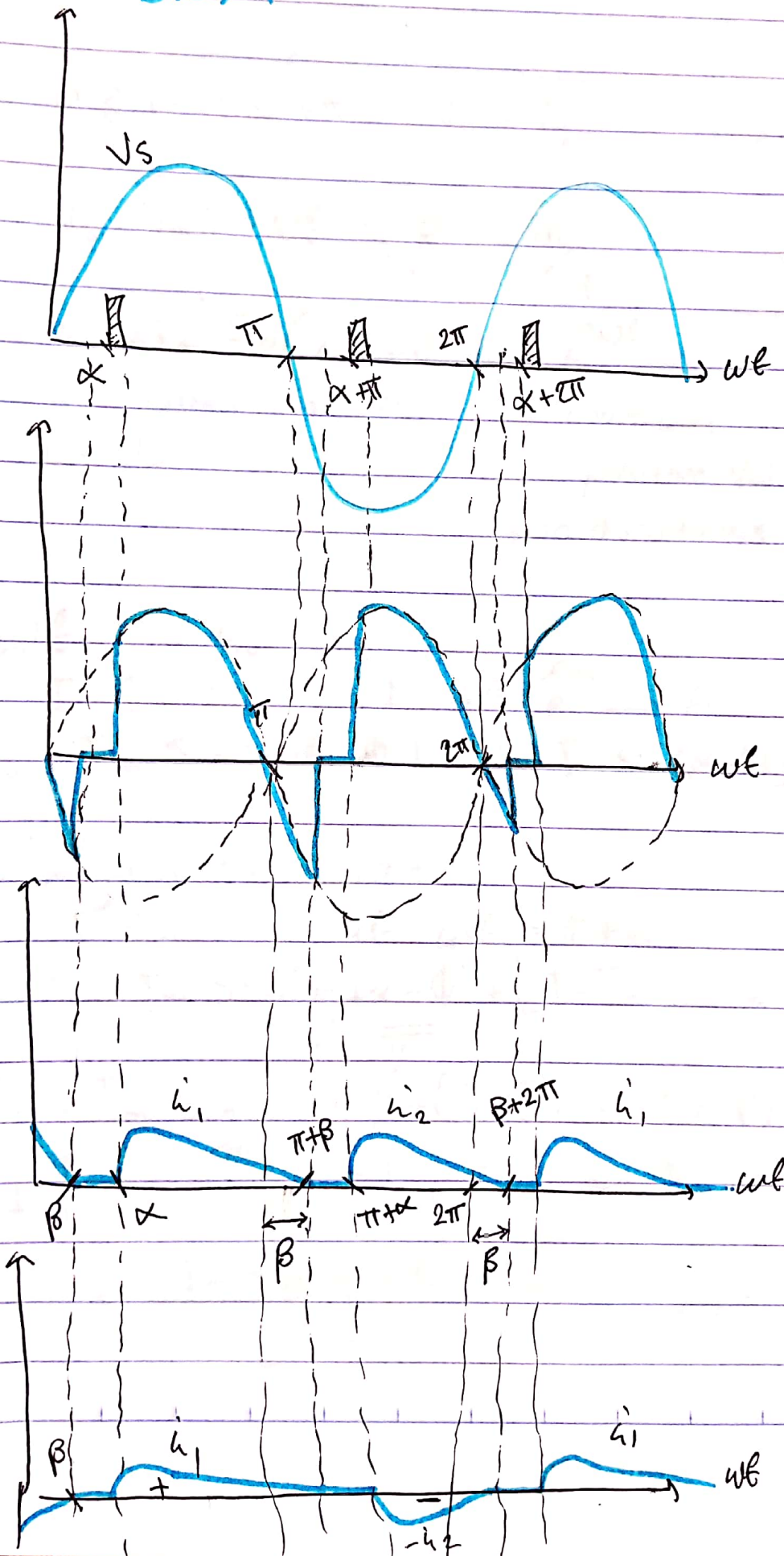


$\alpha - \beta = \delta$

hold off angle.

Analysis assuming C.C.M

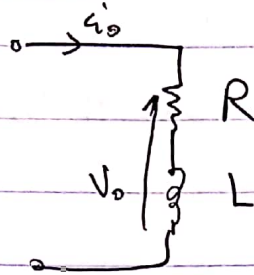• $0 \leq \alpha \leq \alpha + \pi$, $V_o = V_s$



$$V_s = V_m \sin \omega t = i R + L \frac{di}{dt}$$

$$i_o = I_m \sin(\omega t - \phi) + A \cdot e^{\rho \omega t}$$

Initial current condition : In continuous mode $I \neq 0$
I.C.C \rightarrow positive value. I.c.c
 \rightarrow in discontinuous $I = 0$.

$\omega t = \alpha$, $i_o = I$

$$I = I_m \sin(\alpha - \phi) + A \cdot e^{\rho \alpha} \rightarrow A [I - I_m \sin(\alpha - \phi)] e^{-\rho \alpha}$$

$$i_o = I_m \sin(\omega t - \phi) + \underbrace{[I - I_m \sin(\alpha - \phi)] e^{-\rho \alpha}}_A \cdot e^{\rho \omega t}$$

Final current condition.

F.C.C at $\omega t = \pi + \alpha$, $i_o = I$

$$I = I_m \sin(\pi + \alpha - \phi) + [I - I_m \sin(\alpha - \phi)] e^{-\rho \alpha} \cdot e^{\rho(\pi + \alpha)}$$

$$I = -I_m \sin(\alpha - \phi) + [I - I_m \sin(\alpha - \phi)] e^{\rho \pi}$$

$$I [1 - e^{\rho \pi}] = -I_m \sin(\alpha - \phi) [1 + e^{\rho \pi}]$$


$$I = \frac{-I_m \sin(\alpha - \phi) [1 + e^{\rho \pi}]}{[1 - e^{\rho \pi}]} \Rightarrow I = -I_m \sin(\alpha - \phi) \cdot \left(\frac{1 + e^{\rho \pi}}{1 - e^{\rho \pi}} \right)$$

when is $I=0$?

↳ if $\alpha = \phi$, this is the critical condition.

where C.C.M & D.C.M equations apply.
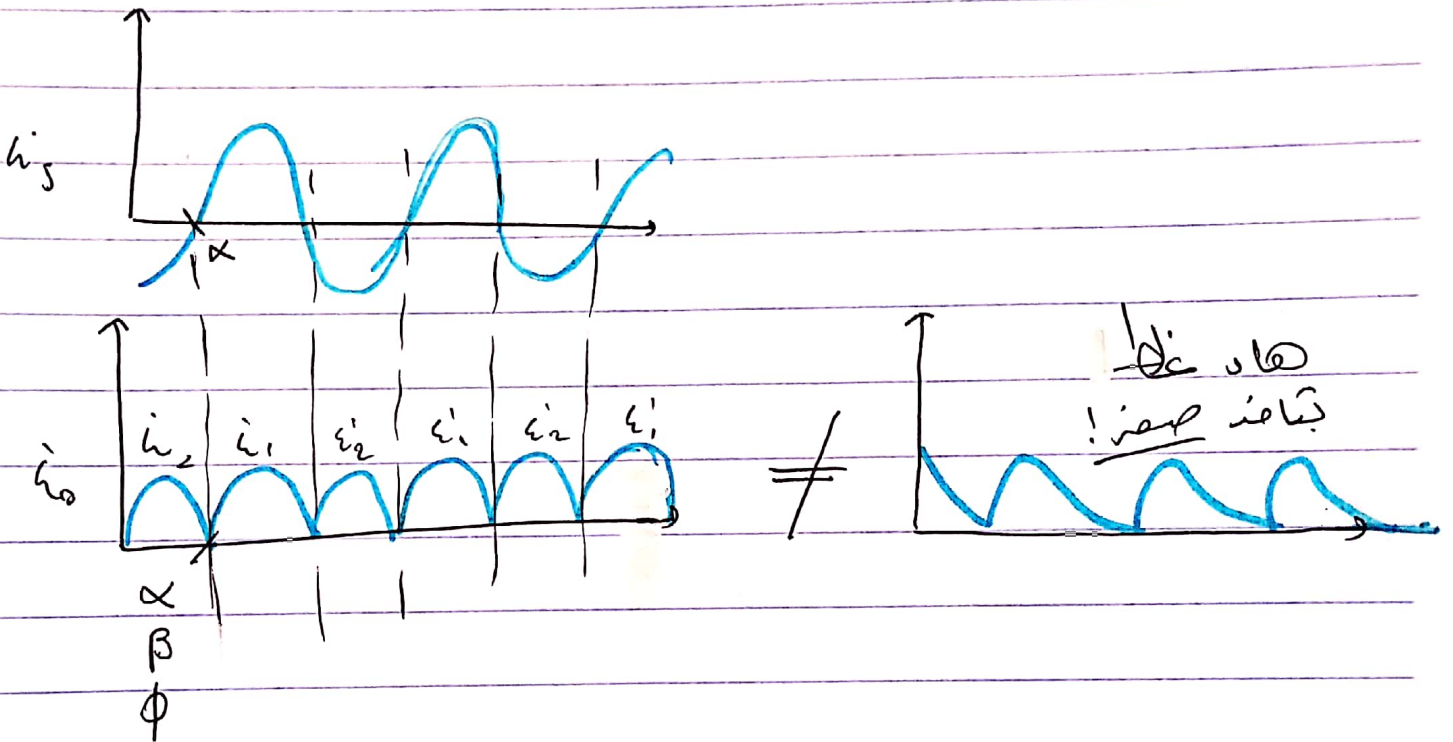
$$i_o = I_m \sin(\omega t - \phi), \quad \alpha \leq \omega t \leq \pi + \alpha$$



• $i_s = I_m \sin(\omega t - \phi) \rightarrow$ pure sinusoidal case
(total harmonic distortion = zero.)

• Voltage isn't affected.

* $I=0$ $\left\{ \begin{array}{l} I < 0, \text{ Theoretical D.C.M. } \alpha > \phi. \\ I = 0, \text{ critical case } \alpha = \phi. \\ I > 0, \text{ C.C.M } \alpha < \phi. \end{array} \right.$

$$I = -I_m \sin(\alpha - \phi) * \left(\frac{1 + e^{j\pi}}{1 - e^{j\pi}} \right)$$

• In Exam ϕ & α are given اذا اطلبنا اننا مرفوض

① $Z = 10 \angle 30^\circ \leftarrow \phi$ يكون ال 3 قيمارات انتاوية .:

② $Z = 10 + j15 \rightsquigarrow \sqrt{-} \angle \phi$


③ $R, L \rightsquigarrow X_L \rightsquigarrow 2\pi fL \rightsquigarrow Z = -j \dots$

for
load

$\sqrt{-} \angle \phi^*$

CCM $\alpha < \phi$
 $\alpha = \phi$

case $\alpha < \phi$

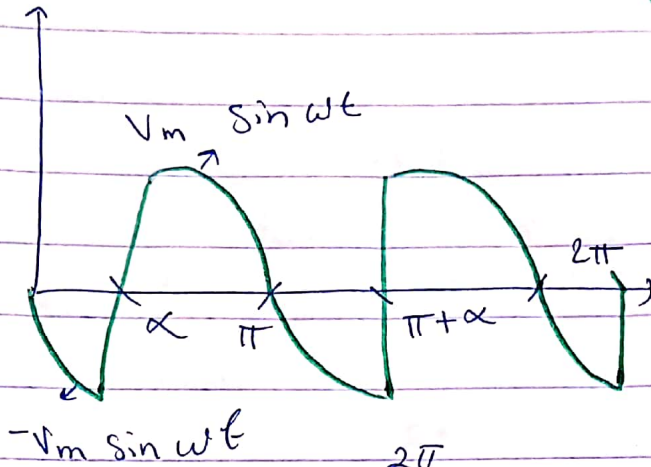

$$\rightarrow V_o(\text{avg}) = \frac{1}{2\pi} \int_0^{2\pi} v_m \sin(\omega t) d\omega t$$

$$= \frac{1}{\pi} \left[\int_0^{\alpha} -v_m \sin \omega t d\omega t + \int_{\alpha}^{\pi} v_m \sin \omega t d\omega t \right]$$

$$= \frac{1}{\pi} \int_{\alpha}^{\alpha+\pi} v_m \sin \omega t d\omega t = \frac{v_m}{\pi} [-\cos \omega t]_{\alpha}^{\pi+\alpha}$$


$$= \frac{v_m}{\pi} [-\cos(\pi+\alpha) + \cos \alpha]$$

$$V_o(\text{avg}) = \frac{2v_m \cos \alpha}{\pi}$$

CCM
 or
 CrCM

critical

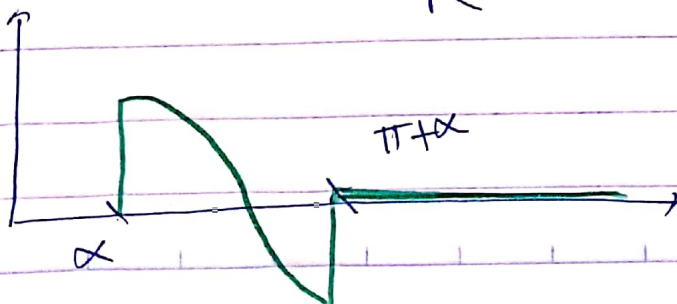
$$\text{Critical } I_o(\text{avg}) = \frac{V_o(\text{avg})}{R}, \quad I_o(\text{rms}) = ??$$



$$\rightarrow V_o(\text{rms}) = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \, d\omega t} = \boxed{\frac{V_m}{\sqrt{2}}}$$

Case $\alpha > \phi$
(DCM.)

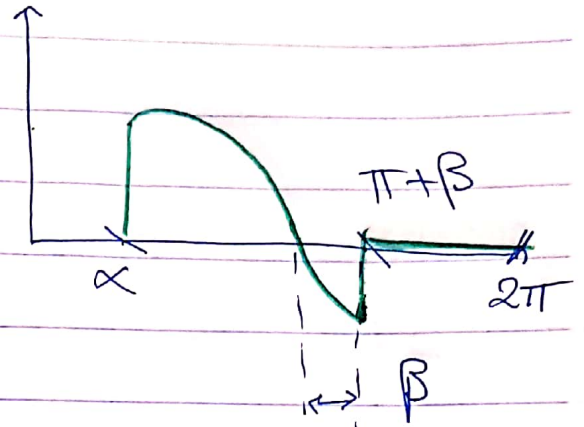
• β can be calculated using the same relationship of the HWR circuit.



$$\begin{aligned} \rightarrow V_o(\text{avg})_{\text{DCM}} &= \frac{1}{\pi} \int_{\alpha}^{\beta+\pi} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi} \left[-\cos \omega t \right]_{\alpha}^{\beta+\pi} \\ &= \frac{V_m}{\pi} [\cos \alpha + \cos \beta] \end{aligned}$$

$$\rightarrow I_o(\text{avg})_{\text{DCM}} = \frac{V_o(\text{avg})}{R}$$

In pure resistive load, $\beta = 0$

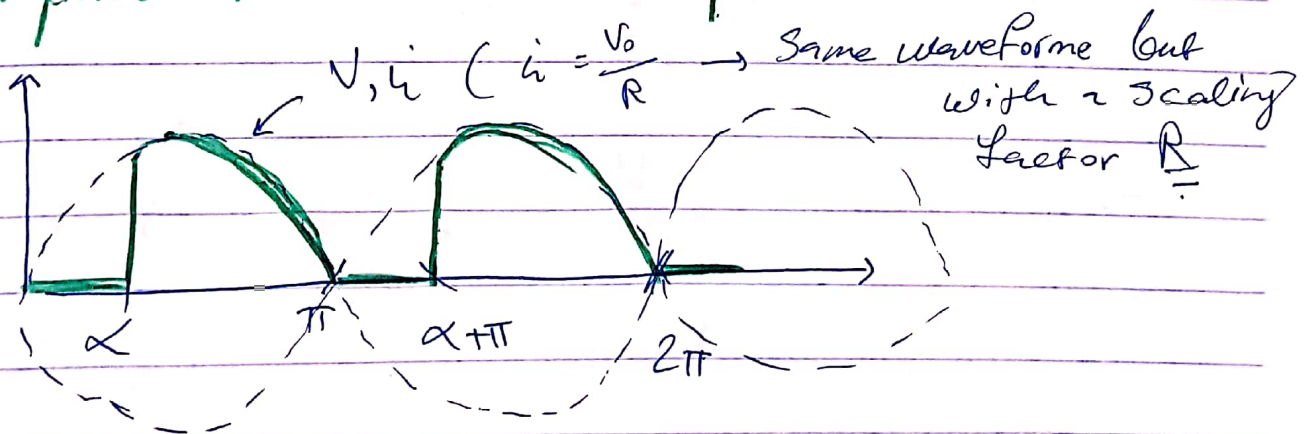

$$I_o(\text{avg}) = \frac{V_o(\text{avg})}{R}, \quad I_o(\text{rms}) = \frac{V_o(\text{rms})}{R}$$

Ex)

- Converter single phase full wave fully controlled Rectifier, 50 Hz, Sinusoidal, 240 V (rms)

$$RMS = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

- load $Z_L = 10 + j10 \Omega$

- Control parameter $\alpha = 45^\circ$

① Which mode of operation the system runs in?

② V_o (avg) = ? , RF_{V_o} = ? , RF_{I_o} = ? PF_{in} ?
THDF = ?

③ Suitable SCR ratings?

→ calculate $\phi = \tan^{-1} \frac{10}{10} = 45^\circ$

compare it with $\phi = \alpha \rightarrow$ critical mode.

calculate β if D.C.M.

→ Find avg. Voltage.

$$V_o \text{ (avg)} = \frac{2V_m}{\pi} \cos \alpha$$

$$= \frac{2 \times 240\sqrt{2}}{\pi} \cdot \cos \alpha$$

Very Important

$$V_o = 152 \text{ V}$$

→ (RMS) , $V_o \text{ (rms)} = \frac{V_m}{\sqrt{2}} = V_s \text{ (rms)} = 240 \text{ V}$


→ $RF_{V_o} = \frac{\sqrt{(240)^2 - (150)^2}}{150} = 1.24$

$$RF_{I_o} = \frac{\sqrt{I_o \text{ (rms)}^2 - I_o \text{ (avg)}^2}}{I_o \text{ (avg)}}$$

$$\rightarrow I_o(\text{avg}) = \frac{V_o(\text{avg})}{R} \Rightarrow \frac{150}{10} = 15.2 \text{ A}$$

$$\Rightarrow I_o(\text{rms}) = ?$$

Critical case

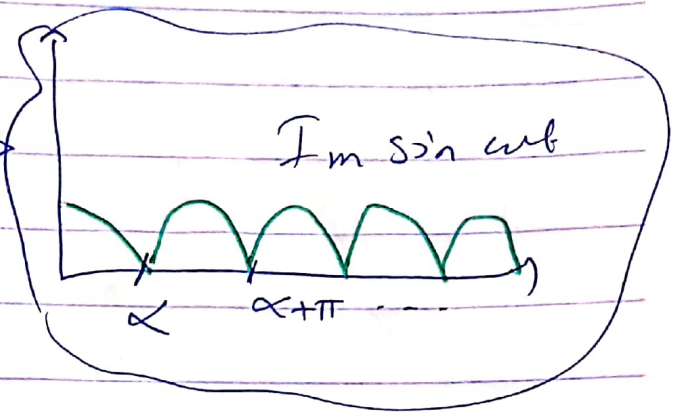

$$I_o(\text{avg}) = \frac{2I_m}{\pi}$$

because it's rectified sine.

$$I_m = \frac{V_m}{Z} \Rightarrow \frac{240 \times \sqrt{2}}{\sqrt{(40)^2 + (10)^2}} = \frac{240\sqrt{2}}{10\sqrt{2}} = 24 \text{ A}$$

$$\rightarrow I_o(\text{avg}) = \frac{2I_m}{\pi} = \frac{2 \times 24}{\pi} = 15.2 \text{ A}$$

$$I_o(\text{rms}) = \frac{I_m}{\sqrt{2}} = \frac{24}{\sqrt{2}} = 16.9 \text{ A}$$


$$\rightarrow R_{F_{i_o}} = \frac{15.2}{\sqrt{(16.9)^2 - (15.2)^2}} = 0.48$$

Current Quality is better
(Lower R.F.)
↳ inductive load $10 + j10$

Coil

as filter.

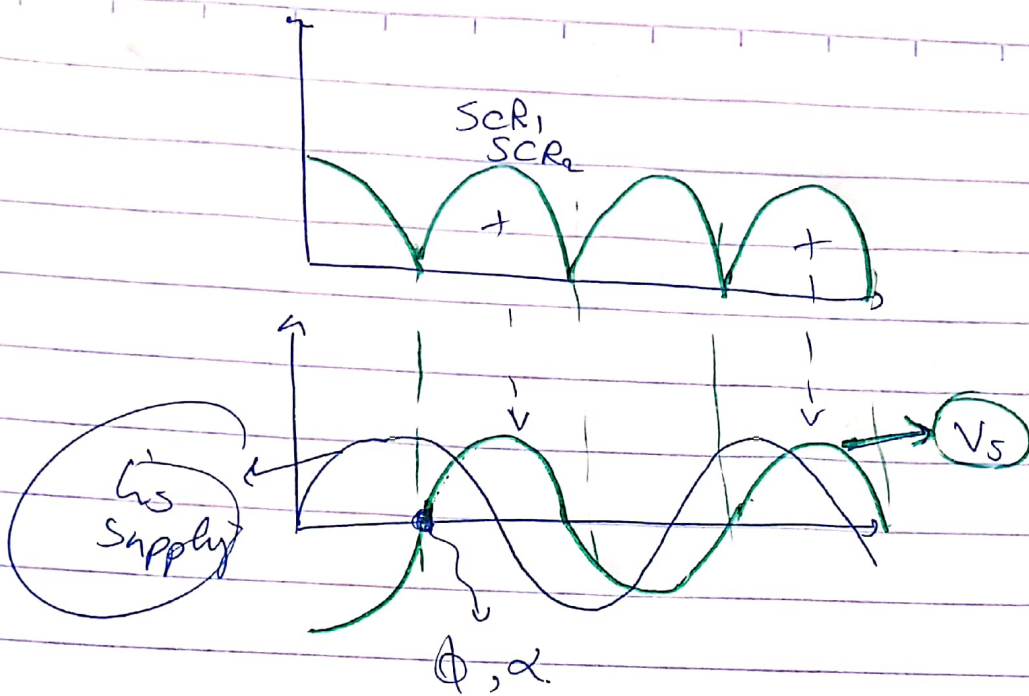→ $PF_{in} \Rightarrow$ I need to draw current in supply.



→ $PF_{in} \cos \phi = \cos \alpha = 0.707$ Lag

→ $THDF = \frac{\sqrt{I_s(rms)^2 - I_s^2(1)}}{I_s(1)}$ Fundamental

Due to sine waveform

find Fundamental

↓
 $I_s(\text{Pure sine}) \quad I_s(1) = \frac{I_m}{\sqrt{2}}$

$I_s(1) = 16.9$, $THDF = \text{Zero}$.

→ SCR current & voltage ratings:

Voltage : Safety Factor * PIV
 (2 → 3) * $(\sqrt{2} * 240)$
 V_m

Range (السعة) (المساحة)

Note: $\{Zero\}$ → Second order harmonic in supply
 { Might be in Exam }

SCR current Rating: I_m/π

$$I_{SCR} = \begin{cases} I_m(\text{peak}) = 24A \\ I_{(avg)} \geq 7.6A \text{ (half period of symmetry)} \\ I_{(rms)} = \frac{I_m}{2} \rightarrow 24/2 = 12 \end{cases}$$

add to the question

④

$V_o(\text{avg}) \rightarrow 250$ & calculate α or $\sin \alpha$

→ Solution

$$V_o(\text{avg}) = 250$$

$$250 = \frac{2V_m}{\pi} \cos \alpha \approx \frac{2 \times 240}{\pi} \sqrt{2} \cos \alpha$$

$$\cos \alpha = 1.15 !! \text{ (maximum 1!!)}$$

So this converter isn't sufficient & cannot feed the load.

$$V_o(\text{avg})_{\text{max}} = \frac{2V_m}{\pi} \cos 0^\circ = 216 \text{ V}$$

Transformer = \dots

→ Use a Transformer (step up) with

$$a = \frac{216}{250} = \frac{\text{primary V}}{\text{load Voltage}} = \text{(Maximum)}$$

Quiz:

Single phase Rectifier $V_s = 600\text{V}$, $V_{DC} = 500\text{V}$.
 is the rectifier suitable to supply
 Such load? justify.

$$\rightarrow V_o(\text{avg})_{\text{max}} = \frac{2V_m}{\pi} \rightsquigarrow \frac{2 \times 600\sqrt{2}}{\pi} = 540\text{V}$$

Since $V_o(\text{avg})_{\text{max}} > V_o(\text{avg})_{\text{Load}}$, YES!

⊗ DC link is always added before (rectifiers and filters) choppers.


⊗ To get maximum voltage (avg), in CCM not DCM that is why we use $V_o(\text{avg})$ equation CCM

SINGLE PHASE SEMI-CONTROLLED RECTIFIER


إذا كان ال Torque موجب و السرعة موجبة فيكون ال power موجب
 إذا كان ال Torque سالب و السرعة موجبة فيكون ال power سالب

$$T = K_A \phi \cdot I$$

$$EMF = K_A \phi \cdot \omega$$

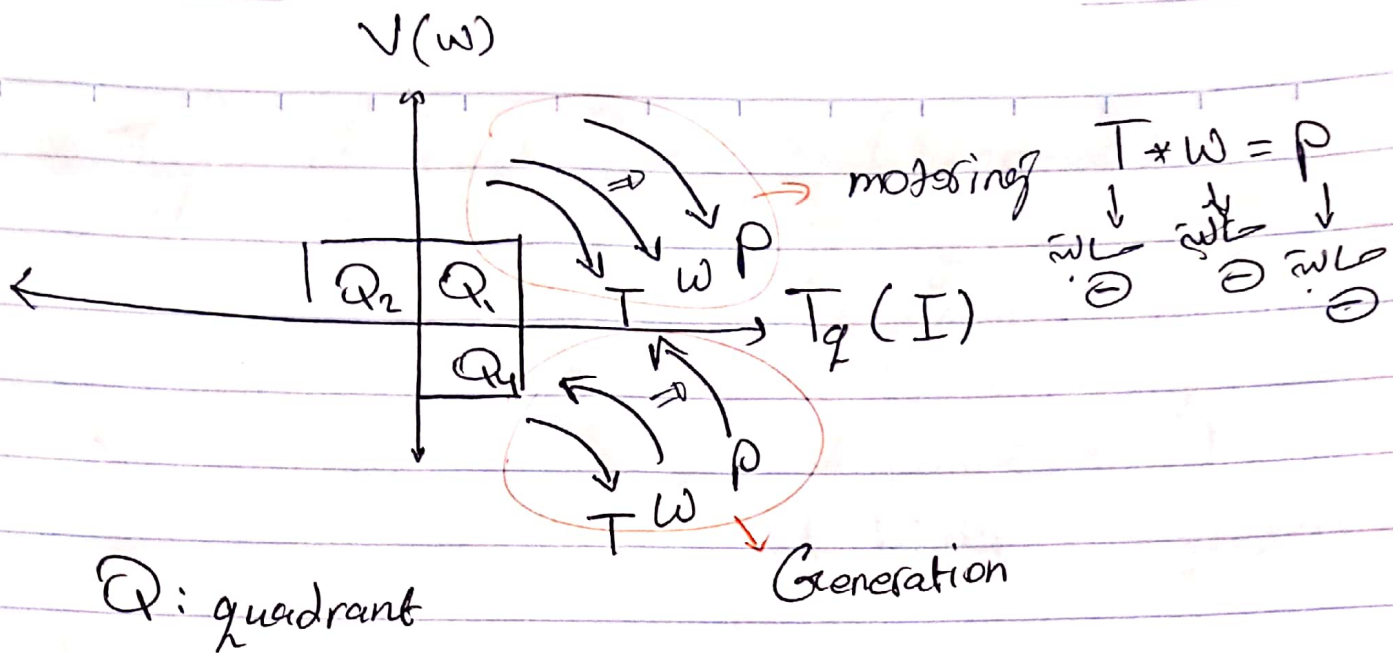

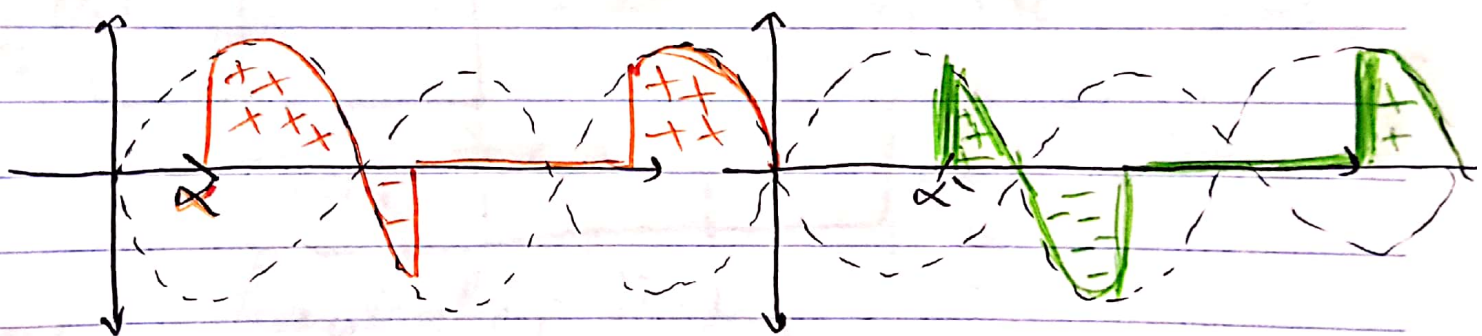ex:- عند انزال ورفع قلب اى الاداة او الاجمل ؛
 على المحرك لدرج يكون في Torque حتى ارضه
 ولما انزله ما يسقط سقوطا حرا في Torque
 عاكسا.



$V_{avg} > 0$
 لما α اقل من 90°

"الجزء الموجب اكبر"

$V_{avg} < 0$
 لما α اكبر من 90°


"الجزء السالب اكبر"

$$\alpha > 90^\circ$$

⦿ If only positive avg. voltage is required, then the negative portion of V_o should be clipped, then Semi-controlled Rectifier is the solution.


- Types of Rectifiers:
- Fully controlled
(Thyristors only)
 - Uncontrolled
(Diodes only)
 - Semi-controlled
(Diodes & Thyristors.)


Semi-controlled Rectifier power circuit.

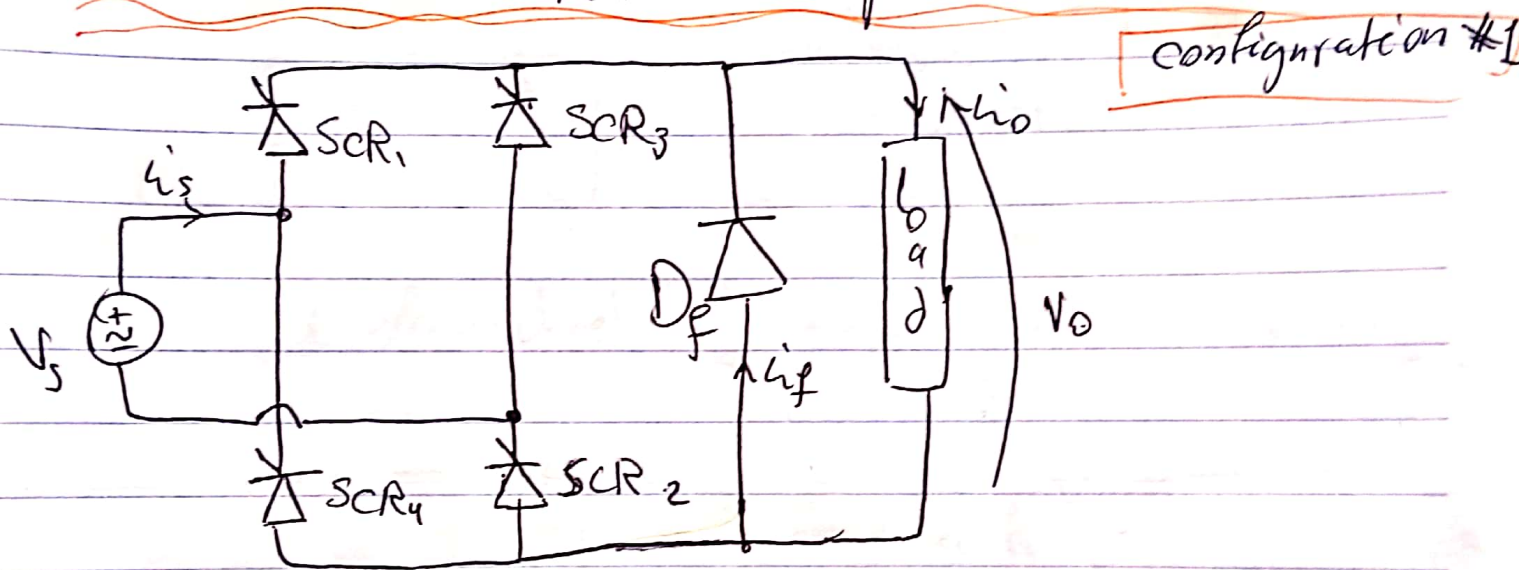


• $D_f =$ Free wheeling Diode.

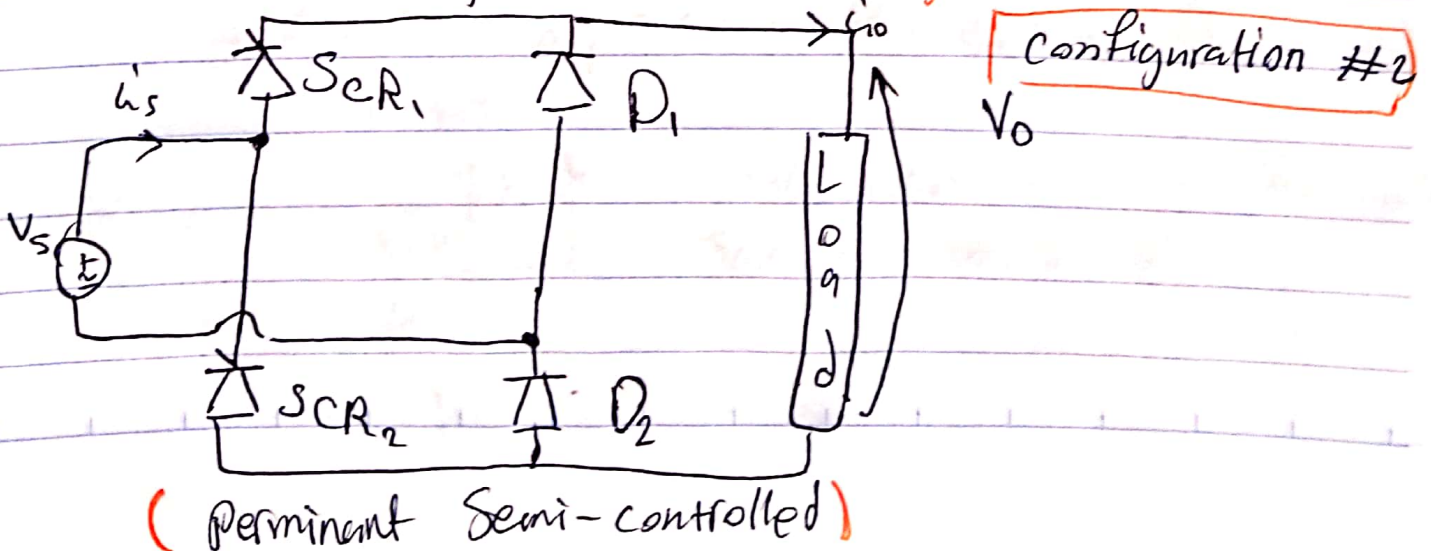(This configuration can become fully controlled if D_f was removed)



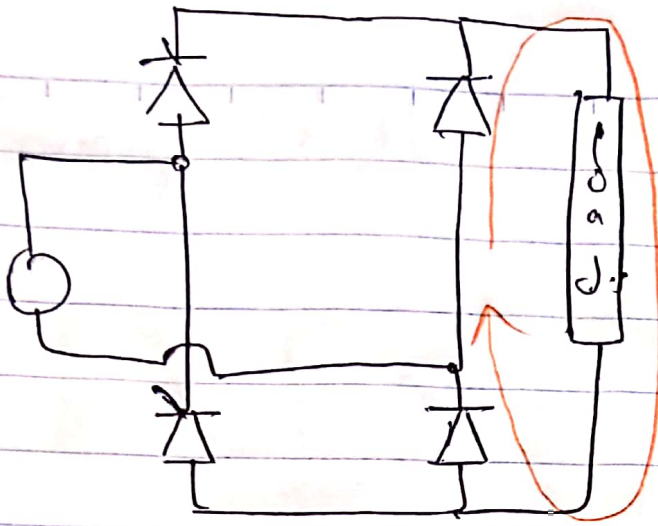


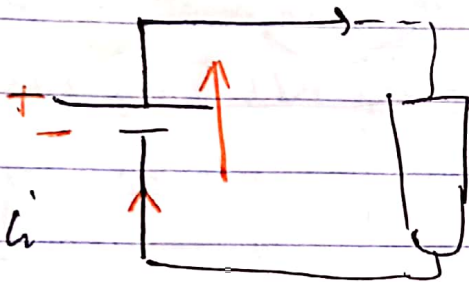اي path لا يوجد فيه
Voltage source or
a supply
Free wheeling
(Free of the source)



اي، يقوم بالسير
بطرف اتجاه الفولتية

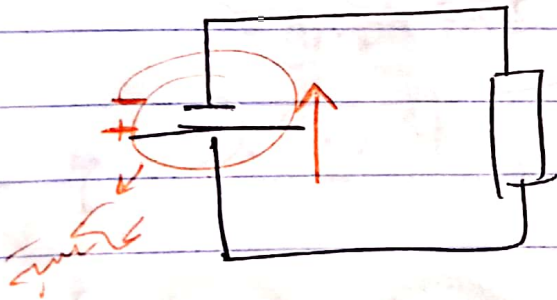
The voltage is
(Free wheeling) Supporting the current.



لما يكون التيار
عكس للفولتية
charging
The battery.


The freewheeling diode is added as
safety, to protect the circuit from
changes

ex:

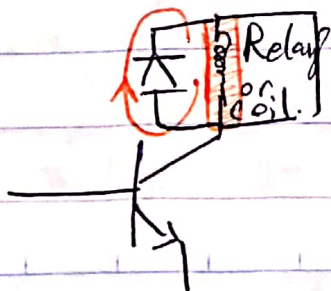


electromechanical Relays
Switch on & off.

Assuming C.C.M.

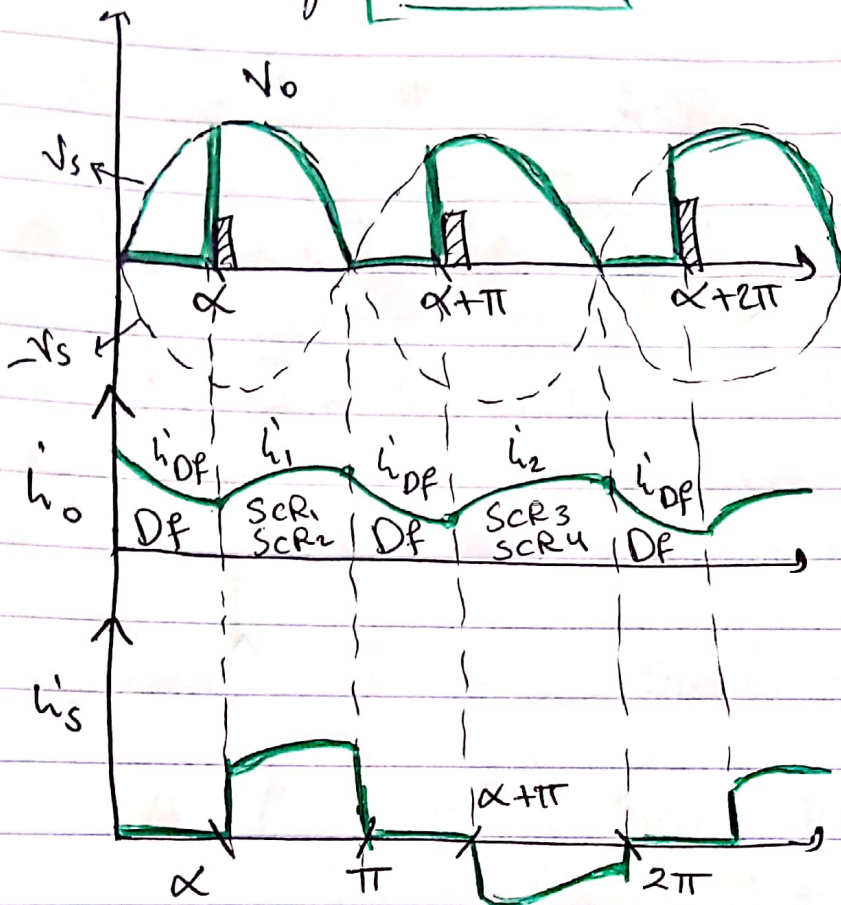

graph 1

D.C.M.

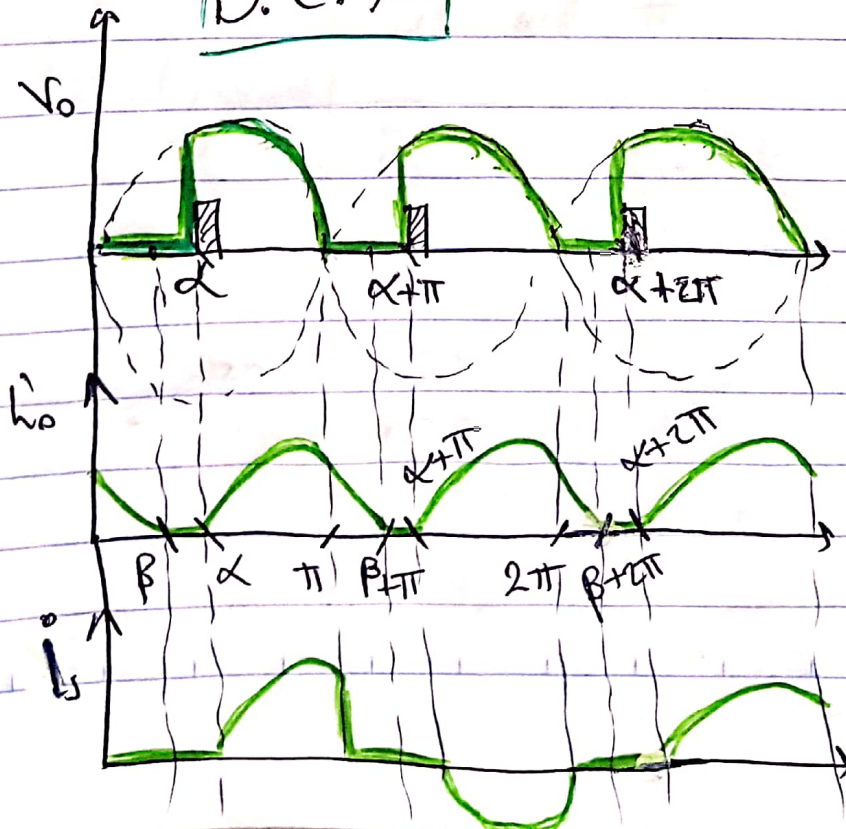

graph 2

All equations are referred to configuration #1.

$$\alpha \leq \omega t \leq \pi \rightarrow SCR_1 \& SCR_2$$

$$\otimes V_m \sin \omega t = iR + L \frac{di}{dt}$$

$$i = I_m \sin(\omega t - \phi) + A \cdot e^{\rho \omega t}$$

I.c.c
Initial
Current
condition

at $\omega t = \alpha$, $i = I_1$

$$I_1 = I_m \sin(\alpha - \phi) + A \cdot e^{\rho \alpha}$$

$$A = [I_1 - I_m \sin(\alpha - \phi)] e^{-\rho \alpha}$$

$$i = I_m \sin(\omega t - \phi) + [I_1 - I_m \sin(\alpha - \phi)] \cdot e^{-\rho \omega t} \cdot e^{\rho \omega t}$$

F.c.c
Final current
condition

at $\omega t = \pi$, $i = I_2$

two unknowns
we need another
Equation

$$I_2 = I_m \sin(\pi - \phi) + [I_1 - I_m \sin(\alpha - \phi)] \cdot e^{-\rho \alpha} \cdot e^{\rho(\pi)}$$


$$\begin{aligned} & \sin(\pi - \phi) \\ & \sin \pi \cos \phi - \cos(\pi) \sin(\phi) \\ & = \sin(\phi) \cdot \text{So, ...} \end{aligned}$$

$$I_2 = I_m \sin(\phi) + [I_1 - I_m \sin(\alpha - \phi)] e^{-\rho \alpha} e^{\rho(\pi)}$$

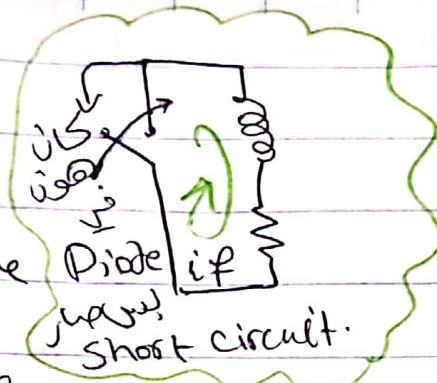(1)

① $\pi < \omega t < \pi + \alpha$

Free wheeling due to having source in the path.




② Note: all ωt 's are referred to graph ~~of I~~

→ at triggering ($\pi + \alpha$) reverse bias is applied on the diode.

→ $0 = i_f R + L \frac{di_f}{dt}$

$i_f = C \cdot e^{\rho \omega t}$

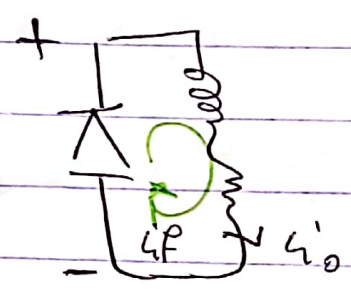

$i_f = I_2$ at $\omega t = \pi$

$I_2 = C \cdot e^{\rho \pi}$

$\therefore i_f = I_2 \cdot e^{-\rho \pi} \cdot e^{\rho \omega t}$

F.o.c.c at $\omega t = \pi + \alpha \rightsquigarrow i_f = I_1$

$I_1 = I_2 \cdot e^{-\rho \pi} \cdot e^{\rho [\pi + \alpha]}$

$I_1 = I_2 \cdot e^{\rho \alpha}$ --- ②

Substituting: ① & ② (Next page)

$I_2 = I_m \sin \phi + [I_1 - I_m \sin (\alpha - \phi)] e^{-\rho \alpha} \cdot e^{\rho \pi}$ --- ①

eq = equation!

$$I_2 = I_m \sin \phi + [I_2 e^{\rho \alpha} - I_m \sin(\alpha - \phi)] e^{\rho \pi} e^{-\rho \alpha}$$

$$I_2 [1 - e^{\rho \pi}] = I_m [\sin \phi - \sin(\alpha - \phi) \cdot e^{\rho(\pi - \alpha)}]$$

$$I_2 = \frac{I_m}{(1 - e^{\rho \pi})} [\sin \phi - \sin(\alpha - \phi) e^{\rho(\pi - \alpha)}]$$

memorize I_2 eq.

Important note & remember $\rho \Rightarrow \omega / \omega_c$

$$I_1 \rightarrow \text{input current} \quad I_1 = I_2 e^{\rho \alpha}$$

$I_1 \rightarrow$ approaching I_H , if $I_H = I_1$

Then it's the critical case.

$$I_1 \Rightarrow I_2 \cdot e^{\rho \alpha} = I_H$$

$$e^{\rho \alpha} = \frac{I_H}{I_2}, \quad \rho \alpha = \ln [I_H / I_2]$$

already calculated

$$\alpha_{cr} = \frac{1}{\rho} \cdot \ln [I_H / I_2]$$

critical

\leadsto to solve any problem \rightarrow start by I_2 to know if it's C.C.M or D.C.M

$I_2 \leadsto \alpha$
 I_H : diode (DF) holding current (positive)

If $\alpha < \alpha_{cr}$ then it's C.C.M

If $\alpha > \alpha_{cr}$ then it's D.C.M

→ analyze graph ~~2~~ ~~2~~ \rightsquigarrow find β

β should be evaluated.


DCM: to evaluate β

$$i_o = I_m \sin(\omega t - \phi) + A \cdot e^{\rho \omega t} \quad i_o$$

→ ICE at $\omega t = \alpha$, $i_o = 0$

$$0 = I_m \sin(\alpha - \phi) + A e^{\rho \alpha}$$
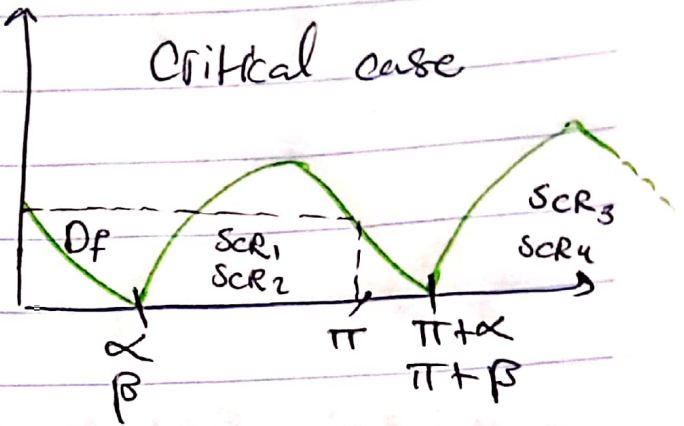
$$A = [-I_m \sin(\alpha - \phi)] \cdot e^{-\rho \alpha}$$



$$i_o = I_m \sin(\omega t - \phi) - I_m \sin(\alpha - \phi) \cdot e^{-\rho \alpha} \cdot e^{\rho \omega t}$$

→ at $\omega t = \pi \rightarrow i_o = I_2$

$$I_2 = I_m \sin(\pi - \phi) - I_m \sin(\alpha - \phi) \cdot e^{-\rho \alpha} \cdot e^{\rho \pi}$$

$$I_2 = I_m [\sin \phi - \sin(\alpha - \phi) \cdot e^{\rho(\pi - \alpha)}]$$

(DCM)

$$I_2 \gg 0$$

(DCM)

→ at $\omega t \rightarrow \pi \leq \omega t \leq \pi + \beta$ or α


$$i_o = C \cdot e^{\rho \omega t} \rightarrow \text{ICE, at } \omega t = \pi$$

$$i_o = I_2$$

(DCM)

⊙ Be careful not to find I_2 from the CCM case; I_2 must be from the DCM.

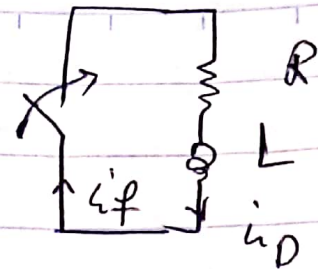$\rightarrow I_2 = C \cdot e^{\rho\pi}$ (DCM) Free-wheeling current.




$C = I_2 \cdot e^{-\rho\pi}$ (DCM)

$i_{\varphi} = I_2 \cdot e^{-\rho\pi} \cdot \rho\omega t$ (DCM)

\odot FCC at $\omega t = \pi + \beta$, $i_{\varphi} = I_H$

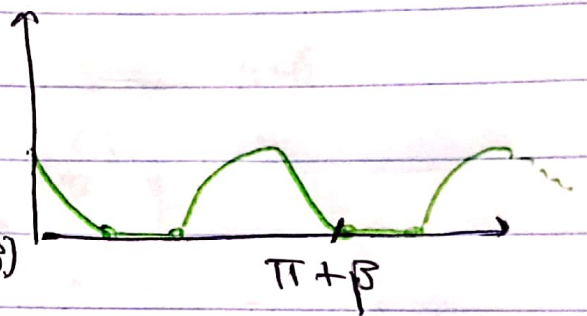The diode is turned off when the current is equal to I_H .




$\rightarrow I_H = I_2 \cdot e^{-\rho\pi} \cdot \rho(\pi + \beta)$ (DCM)

$I_H = I_2 \cdot e^{\rho\beta}$ (DCM), $e^{\rho\beta} = \frac{I_H}{I_2}$ (DCM)

So, $\rho\beta = \ln\left(\frac{I_H}{I_2}\right)$ (DCM), $\beta = \frac{1}{\rho} \ln\left(\frac{I_H}{I_2}\right)$ (DCM)

\rightarrow DCM $\rightsquigarrow \beta < \alpha$, But in critical $\beta = \alpha$ continuous

In case of Figured Question:

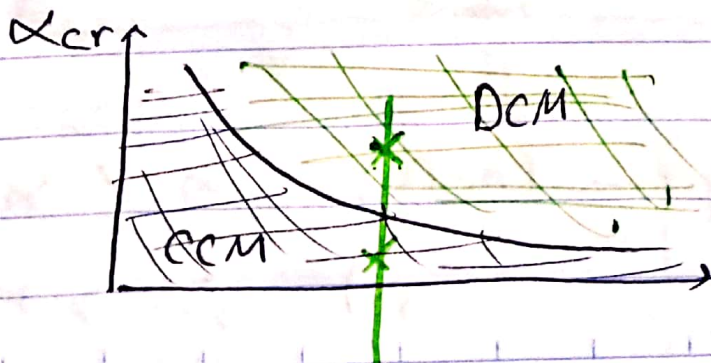

Mode \rightarrow α \rightarrow α

* Two cases: \rightarrow Case ① ($\alpha = \phi$)
 So... α \leq ϕ \rightarrow $\alpha = \phi$


\rightarrow Case ② Highly inductive load with EMF
 (special case)

Sufficiently large L such that the load current is ripple free (virtually constant)


$\rightarrow R, L, E$

① Motor.
 ② charger: { Battery + Smoothing reactor. }

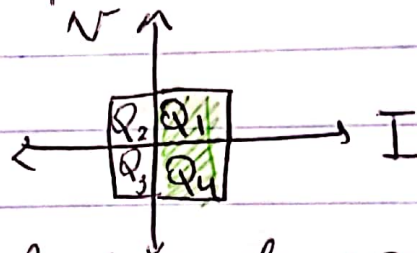
• In motor case, voltage can be positive or negative (currents always positive)



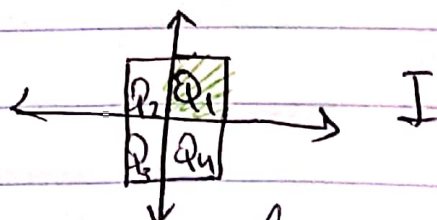• Charger case, voltage & current are negative and we don't need a fully controlled rectifier.




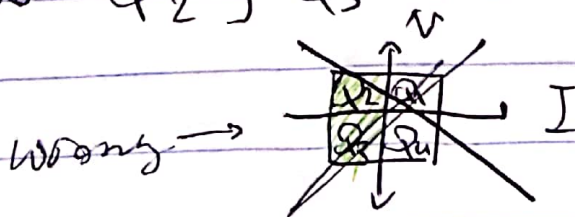Note: Since we're using rectifiers, there's no way we're negative current so Q_2 & Q_3 are not possible




• $L =$ sufficiently large, coil is to act as $\underline{100\%}$ inductor

Fully controlled rectifier

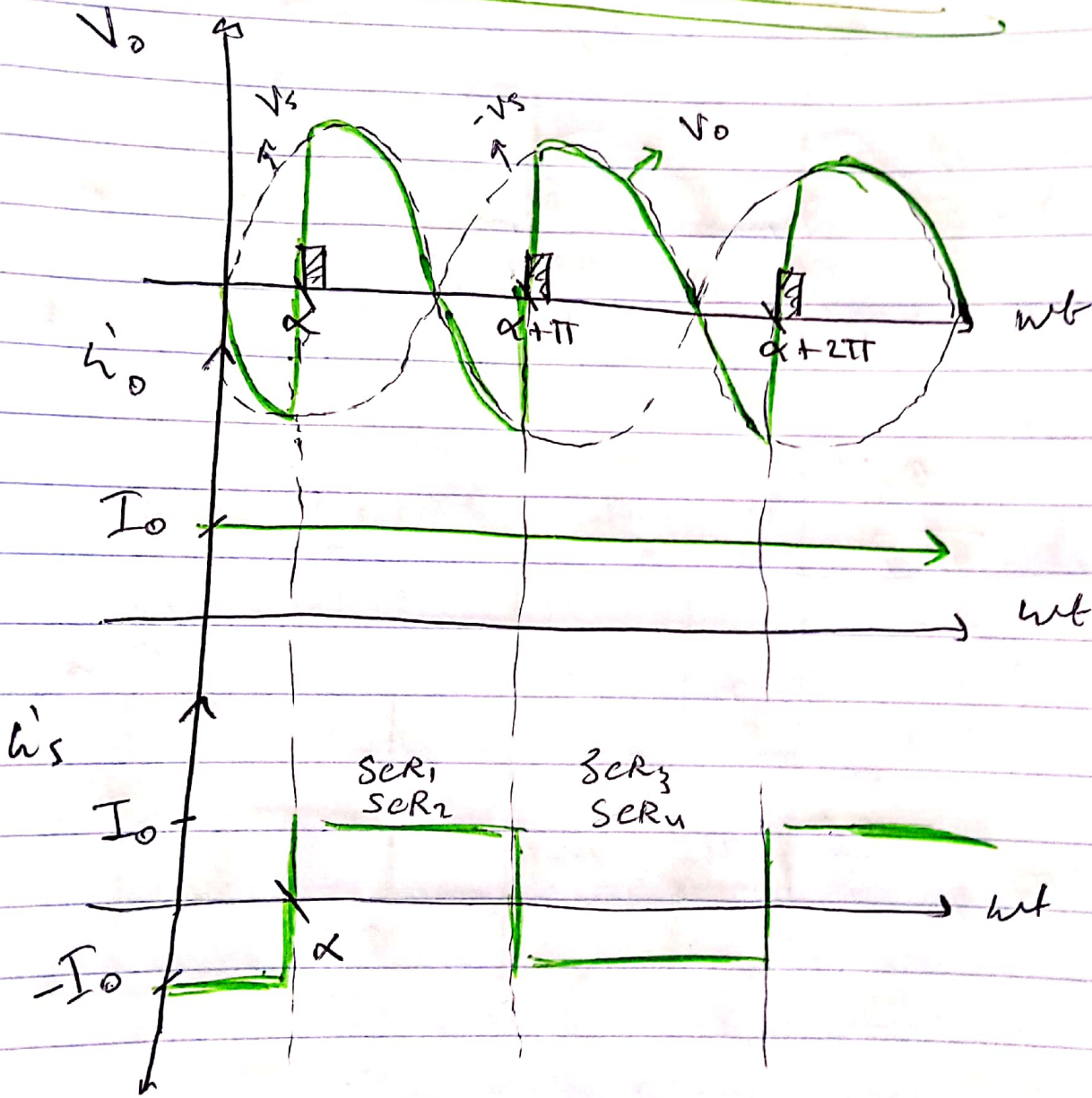

half / Semi-controlled rectifier

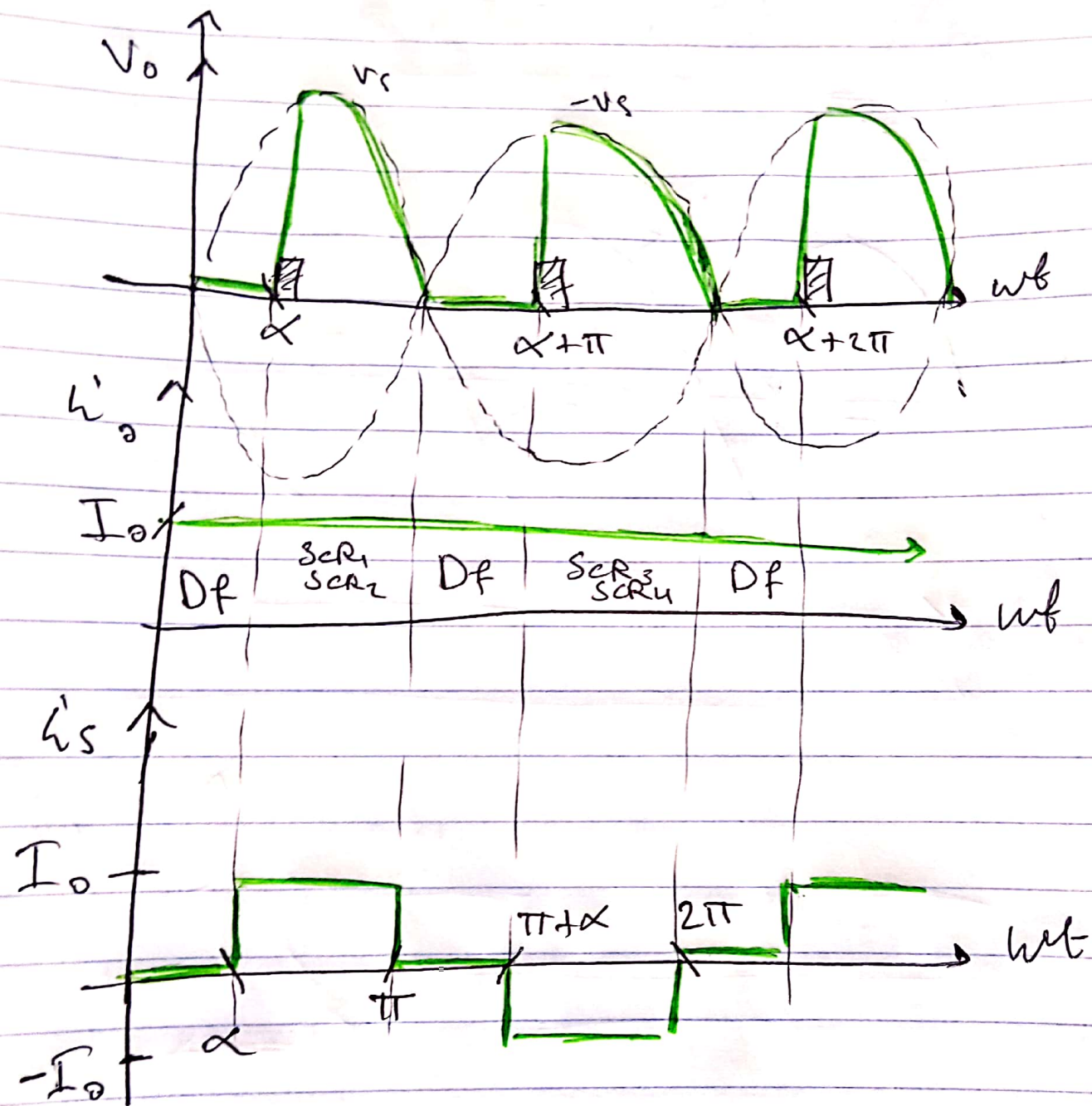

Special case 8 harmonics \rightsquigarrow Increases the current

$\rightarrow P_{cu} = R_a \times I_{avg}^2$
(rated)

$\rightarrow P_{cu}' = R_a \times I^2$

$I = \sqrt{I_{avg}^2 + \sum_{n=1}^{\infty} \left(\frac{I_m(n)}{\sqrt{2}}\right)^2}$

$P_{c(rated)} < P_{cu}'$

Torque is only produced by $I_{(avg)}$

We want a load current ripple-free (no-harmonics)

R-L-E load with (L) so large such that

the load current is ripple-free or is almost virtually constant.

R-L-E load case is always a CCM { ripple factor:

... β ... $RF < 5\%$

1 Motor with large L or external L. \therefore ripple free. \checkmark

2 Battery (charger) \rightarrow Back EMF + current smoothing coil (external)



Why do we want a ripple-free current?

to avoid over-heating & motor derating

battery charger stress.

Battery case

Motor case

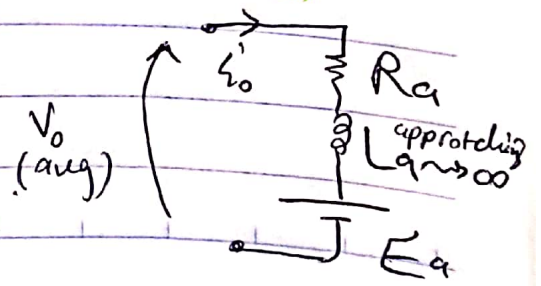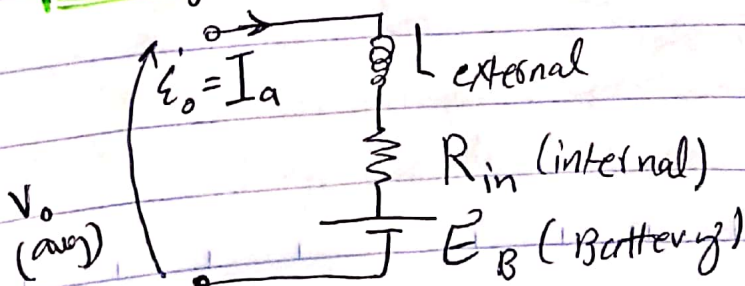

• F.C.R
Fully controlled
Rectifier

$$V_o = \frac{2V_m}{\pi} \cos(\alpha)$$

(avg)

• S.C.R
Semi-controlled
rectifier


$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

(avg)

→ Since it's ripple-free; $i_o = I_o$

$$V_o = E_a + I_a R_a$$

(avg) or E_B

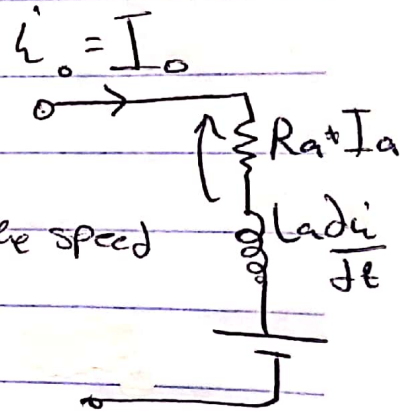

ex. for
F.C.R

$$\frac{2V_m}{\pi} \cos(\alpha) = E_a + I_a R_a$$

in motor case it depends on the speed



$$\Rightarrow k_a \phi \omega_m + \frac{T_a}{k_a \phi} R_a$$

$(L_a \frac{di}{dt} = 0)$
↓
almost virtually constant.

$$\left\{ \begin{array}{l} \underline{k_1} : \frac{k_a \phi 2\pi}{60} = k_1 \\ \underline{k_2} : \frac{R_a}{k_a \phi} = k_2 \end{array} \right.$$

$$k_1 \omega_m + k_2 T_a = \frac{2V_m}{\pi} \cos(\alpha)$$

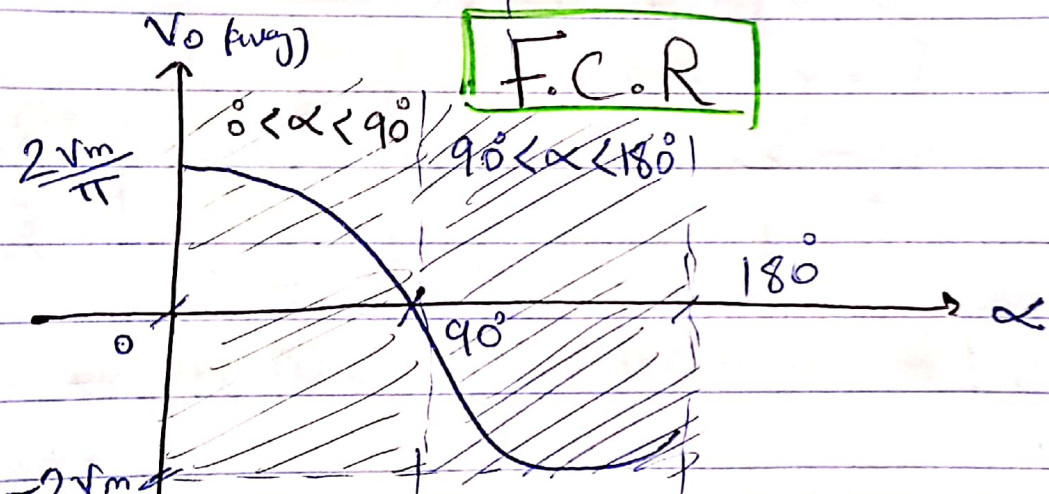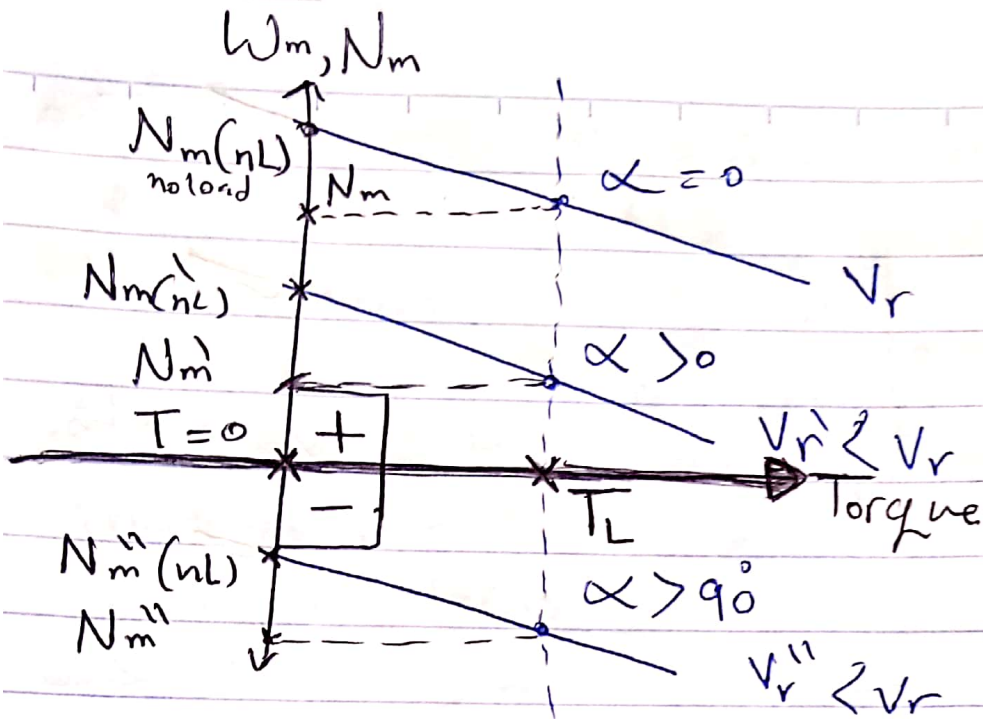k_1 : speed constant
 k_2 : torque constant
 ω_m : angular speed
 T_a : torque
 Thyristor α





* V_o (avg)	+	* V_o (avg)	-
* I_o (avg)	+	* I_o (avg)	+
* T_q	+	* T_q	+
* N_m	+	* N_m	-

$p = T_q W_m$ → motoring action (Rectification mode) → (Forward motoring)
 $-p$ → (Blugging / Braking) → (Inversion mode @ Supply Frequency) generating action.

كلاس اميز بينه
 د بين ا ر Inverter
 الاعادي

Dual Converter

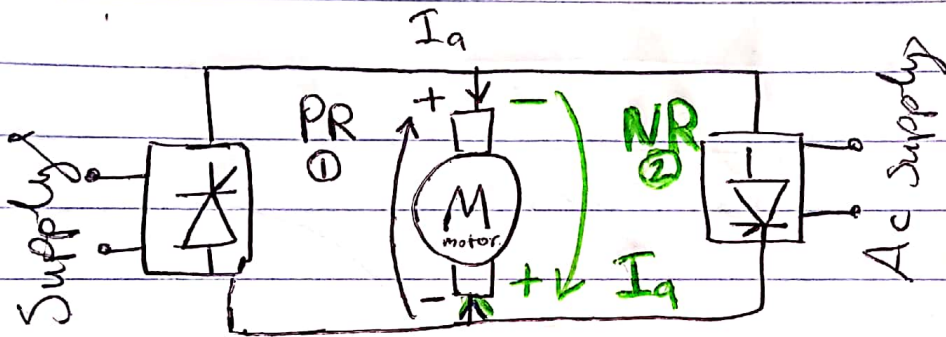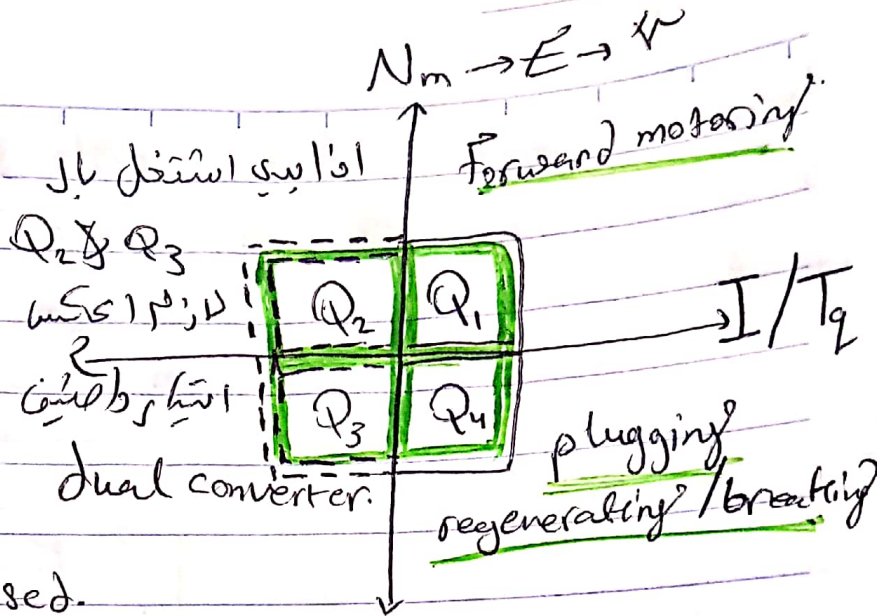- to run at all 4 Quadrants (1 → 4)
Dual converter is used.




PR ① : (positive Rectifier) → I_a direction


NR ② : (Negative Rectifier)

In dual converter one of the back-to-back connected rectifiers work. but if $\alpha_1 + \alpha_2 = 180^\circ$, then they can work together.

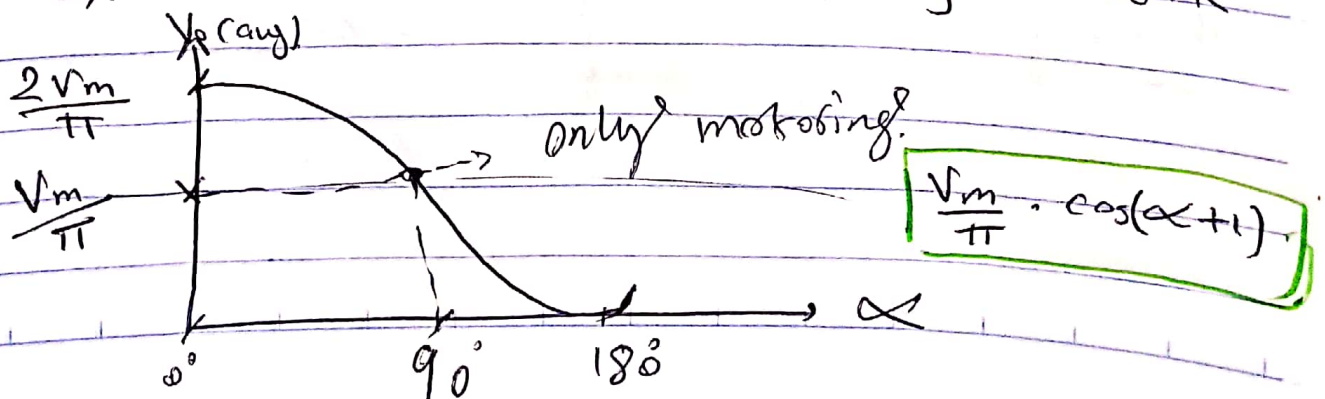ex: $\alpha_1 = 60^\circ$, $\alpha_2 = 120^\circ$. PR & NR work




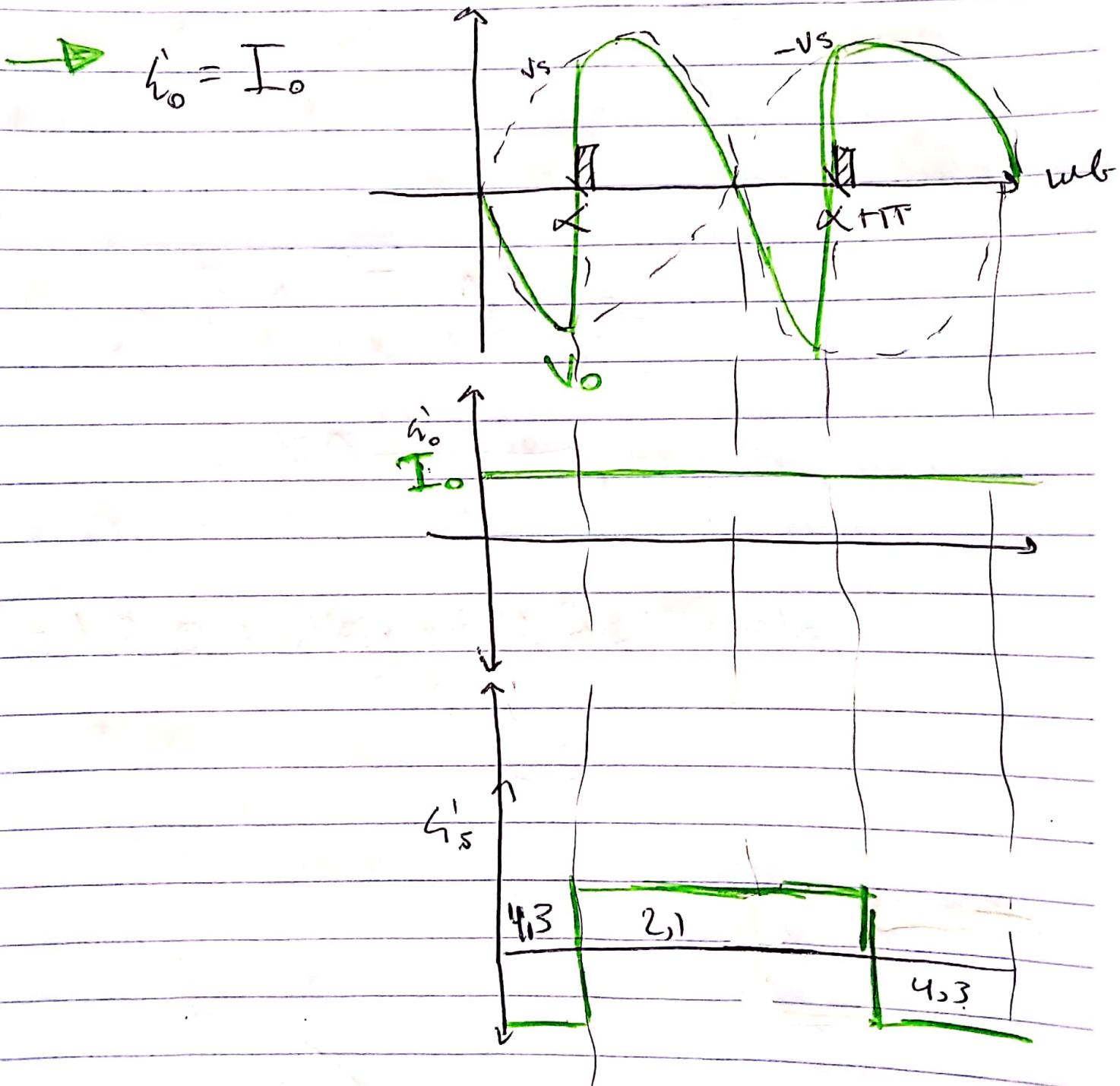Quiz : Sketch the load / supply, current and voltage waveforms for a full wave fully controlled rectifier for an L-R-E load with $L \rightarrow \infty$ (very large):



Q) controller single-phase full wave fully controlled bridge rectifier. Supply: 230 V, 50 Hz sinusoidal. load: series RLE load with R equal to 0.5Ω , $L \rightarrow \infty$,
 a) $E = +65 \text{ V}$. motoring? b) -75 V generating?

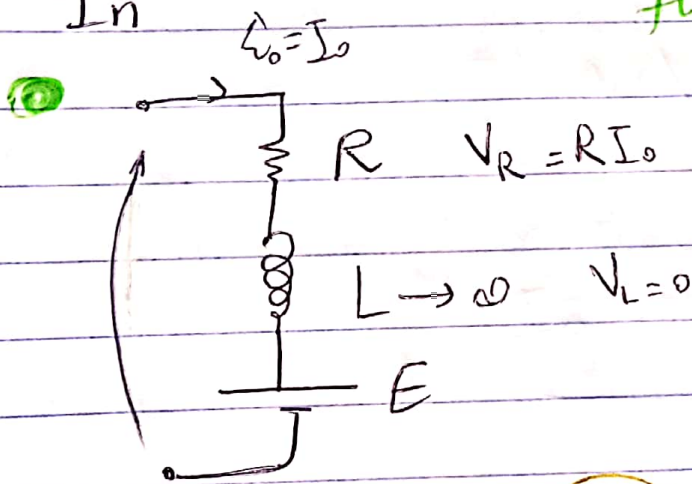For $I_o = 10 \text{ A}$, Find α , R_F , R_F , THDF, PF, I_s
note in questions like this I_o or α is given



$V_o (\text{Avg}) = I_o R + E$ → صيغة حساب الجهد المتوسط بالاعتماد من المقاومة وبتحديد E
او عند معرفة I_o بالقيمة

Continuous mode of operation $\frac{2V_m}{\pi} \cos \alpha = 10 \times 0.5 + 65$
 $\frac{2V_m}{\pi} \cos \alpha = 70 \text{ V}$

$\cos \alpha = \frac{70 \times \pi}{2(\sqrt{2}) \times 230} \Rightarrow \alpha = 70.8^\circ$

$$RF_{V_o} = \frac{\sqrt{V_{o(rms)}^2 - V_o^2(\text{avg})}}{V_o(\text{avg})} \quad , \quad V_o(\text{rms}) = V_s \text{ (PCM)}$$

$$V_o(\text{avg}) = 70 \text{ V}$$

$$\text{So, } RF = \frac{\sqrt{(230)^2 - (70)^2}}{70} = 3.1 \text{ pu}$$

or
310%

$$RF_{I_o} = \text{Zero (pure DC)}$$

THDF : HARMONIC Analysis

odd symmetry $\rightarrow n = 1, 3, 5, 7, \dots$

even symmetry $\rightarrow n = 2, 4, 6, \dots$


$$A(n) = \frac{2}{T} \int_{t_0}^{t_0+T} i_s(t) \cdot \cos(n\omega t) dt, \quad n = 1, 2, 3, 4.$$

Symmetry is being taken into consideration

$$= \frac{4}{T} \int_{t_0}^{t_0+T/2} i_s(t) \cdot \cos(n\omega t) dt, \quad n = 1, 3, 5$$

$$\frac{4}{2\pi} \int_{\alpha}^{\alpha+\pi} I_o \cos(n\omega t) d\omega t$$
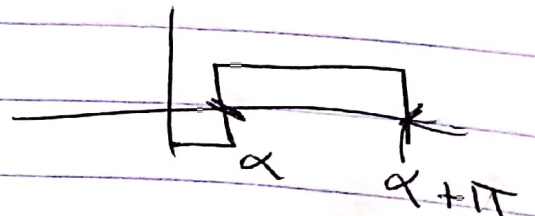
$$= \frac{4 I_o}{2\pi n} \left[\sin(n\omega t) \right]_{\alpha}^{\alpha+\pi}$$



$$= \frac{4I_0}{2n\pi} \left[\sin(n\alpha + n\pi) - \sin(n\alpha) \right]$$

$$\sin(n\alpha + n\pi) = \sin(n\alpha) \cos(n\pi) + \cos(n\alpha) \sin(n\pi)$$

$$= (-\sin n\alpha)$$

$$A(n) = \frac{-4I_0}{n\pi} \sin(n\alpha) \neq$$

$$\rightarrow B(n) = \frac{4}{2\pi} \int_{\alpha}^{\alpha+\pi} I_0 \sin(n\omega t) d\omega t$$

$$= \frac{4I_0}{2\pi n} \left[\cos(n\omega t) \right]_{\alpha}^{\alpha+\pi}$$

$$= \frac{4I_0}{2\pi n} \left[-\cos(n\alpha + n\pi) + \cos(n\alpha) \right]$$

$$-\cos(n\alpha + n\pi) = -\cos(n\alpha) \cos(n\pi) + \sin(n\alpha) \sin(n\pi)$$

$$\frac{4I_0}{n\pi} \cos n\alpha = B(n)$$

$$\rightarrow C(n) = \frac{4I_0}{n\pi} \sqrt{\sin^2(n\alpha) + \cos^2(n\alpha)}$$

$C(n) = \frac{4I_0}{n\pi}$ Peak Amplitude for n th harmonic.

$$i_c(n) = \frac{4I_0}{n\pi} \quad i_s(n) = \frac{4I_0}{n\pi} \sin(n\omega t - n\alpha)$$

* $n = 1, 3, 5, \dots$

$$i_s = \sum_{n=1,3,5,7,\dots} \frac{4I_0}{n\pi} \sin(n\omega t - n\alpha)$$

Power Factor

$$V_s = V_m \sin(\omega t)$$

$$i = \frac{4I_0}{\pi} \sin(\omega t - \alpha) + \frac{4I_0}{3\pi} \sin(3\omega t - 3\alpha) \dots$$

avg value = zero

$$\dots + \frac{4I_0}{5\pi} \sin(5\omega t - 5\alpha) + \dots$$

① $P_{in} = ??$

$$P_{(1)} = \frac{V_m}{\sqrt{2}} * \frac{4I_0}{\pi\sqrt{2}} * \cos(\omega t - \omega t + \alpha)$$

Fundamental

$$P_{(1)} = V_s(\text{rms}) * \frac{I_s(1)}{(\text{rms})} \cos(\alpha)$$

$$P_{(3)} = 0, \quad P_{(5)} = 0,$$

$$P_{in} = P_s = V_s(\text{rms}) * I_s(1)(\text{rms}) * \cos(\alpha)$$

$$PF_{in} = \frac{P_s(\text{real})}{P_r(\text{apparent})} = \frac{P_s}{\sqrt{S}}$$

$$\int_S V = V_s I_s (rms)$$

$$I_s (rms) \neq I_{s(1)} (rms)$$

$$\Rightarrow P_{in} = P_s$$

$$(V_s (rms) I_{(1)} (rms) \cos(\alpha))$$

$$P_{in} = \frac{V_s (rms) I_{s(1)} (rms) \cos(\alpha)}{V_s (rms) I_s (rms)} = \frac{I_{s(1)} (rms)}{I_s (rms)} \cos \alpha$$

$$P_{in} = DTF * DPF$$


Displacement Factor

=
cos (angle between
fundamental voltage &
fundamental current)

Distortion Factor ≠
Total harmonic
distortion
Factor.


[or] alternatively $\rightarrow P_{Fin} = \frac{P_s}{P_o} = \frac{P_o}{P_o}$

$$= \frac{I_a^2 R + (I_a E_a)}{P_o}$$

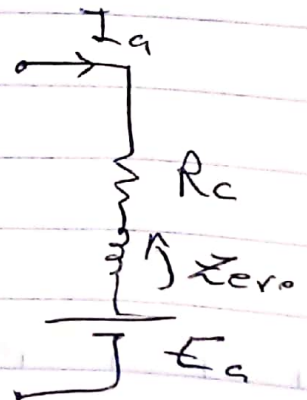


$$= \frac{I_o [E_a + I_o R]}{V_s(\text{rms}) I_s(\text{rms})} = \frac{I_o V_o(\text{avg})}{V_s(\text{rms}) I_s(\text{rms})}$$

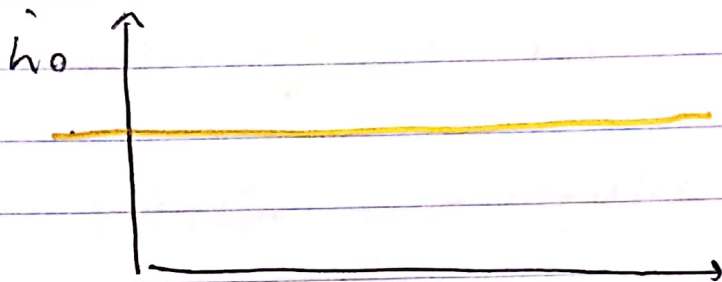Relationship between I_o & $I_s(\text{rms})$



They have same RMS Value.

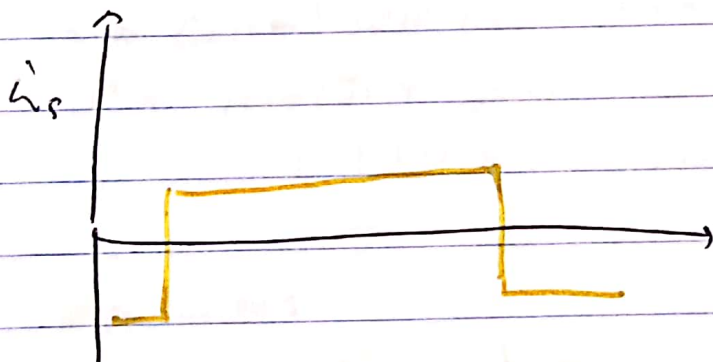

$$I_s(\text{rms}) = I_o$$

$$= \frac{I_o V_o(\text{avg})}{V_s(\text{rms}) I_s(\text{rms})} = \boxed{\frac{V_o(\text{avg})}{V_s(\text{rms})} = \text{PF}_{in}}$$

Cont. Question solution ---

$$\text{PF}_{in} = \frac{70}{230} = 0.304 \text{ (lagging)}$$

$$I_s(\text{rms}) = \frac{4 I_o}{\pi \sqrt{2}} = \frac{4 \times 10}{\pi \sqrt{2}} = 9 \text{ A}$$

$$\text{DTF} = 9/10 = 0.9$$

$$\text{DPF} = \cos \alpha = \cos(70.2) = 0.342$$

check ↗

P_{Fin} in the new way :

$$P_{Fin} = 0.9 \times 0.342 = 0.307$$

PART 2 -75 W

$E_f / E_a = -$ negative! motor is changing direction.

no current will never change direction because of the rectifier positive current (always) (blugging / breaking) case

● solution:

$$V_o(\text{avg}) = E_a + I_o R_a$$


$$= -75 + 10 \times 0.5 = -70 \text{ V}$$

$$\cos \alpha = \frac{-70 \times \pi}{2 V_m}$$

$$\alpha = 109.7^\circ$$

$$P_{Fin} = \frac{V_o(\text{avg})}{V(\text{rms})} = \frac{-70}{230} = -0.304$$

means generation

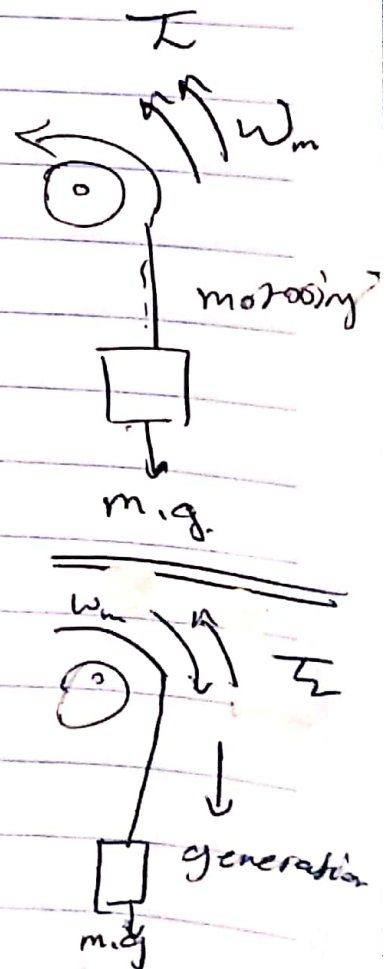

Homework 220V, 50Hz, sinusoidal, RL-series load, $R=10\Omega$, $L=55.13\text{mH}$, $\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$
 $\alpha = \phi$ critical case.

$$\alpha = 60^\circ$$

$$\omega L = 2\pi \times 50 \times 55.133 \times 10^{-3} \text{ ----}$$

Calculate all performance parameters of Load & Supply

① draw waveforms (PP) after ϕ calculation.

② Load RF_{in} , RF_{i}
Load Load

③ Supply THDF, PF_{in}
 i_s Supply

10/12/2019

- Fully controlled rectifier, supply 220, 50 Hz, sinusoidal, R-L load, $R=10$, $L=55.133 \text{ mH}$

Solution

$$V_o(\text{avg})_{\text{CCM}} = \frac{2V_m \cos \alpha}{\pi}, \quad \tan^{-1}\left(\frac{\omega L}{R}\right) = \phi$$

$$X_L = \omega L = 2\pi \times 50 \times 55.133 \times 10^{-3} = 17.3$$

$$\phi = 60^\circ \quad \text{[cr mode]}$$

$$\Rightarrow V_o(\text{avg}) = \frac{2 \times 220 \times \sqrt{2}}{\pi} \cos 60^\circ$$

$$I_o(\text{avg}) = \frac{1}{\pi} \int_{\alpha}^{\alpha+\pi} I_m \sin(\omega t) dt = \frac{V_o(\text{avg})}{R}$$


$$I_m = \frac{V_m}{Z} = \frac{220\sqrt{2}}{\sqrt{10^2 + 17.3^2}}$$

$$I_o(\text{rms}) = \frac{I_m}{\sqrt{2}}$$

$A(n), B(n) = ??$ Home-work I_o

$$i_o = I_o(\text{avg}) + \sum_{n=2,4,6,\dots} I_o(n) \cdot \sin(n\omega t + \phi(n))$$
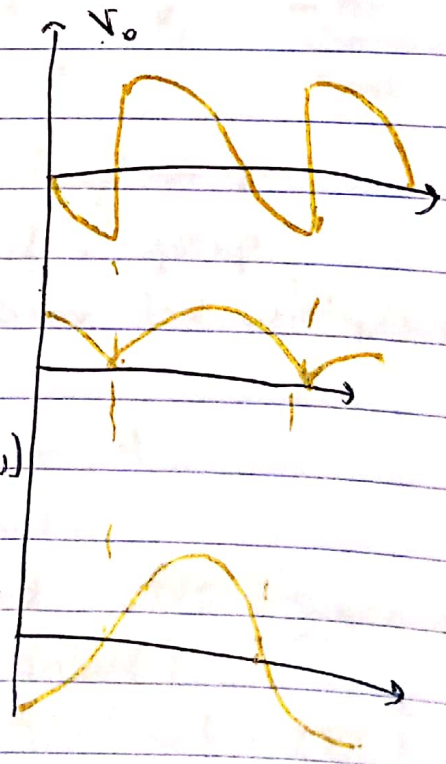
$$I_o(n) = \sqrt{A(n)^2 + B(n)^2} = C(n) \quad i_s$$




3-phase-rectifiers.

• pure resistive load: power circuit

⊗ Real numbering for later.

• Y-connected \Rightarrow avoid harmonics & circulating current.

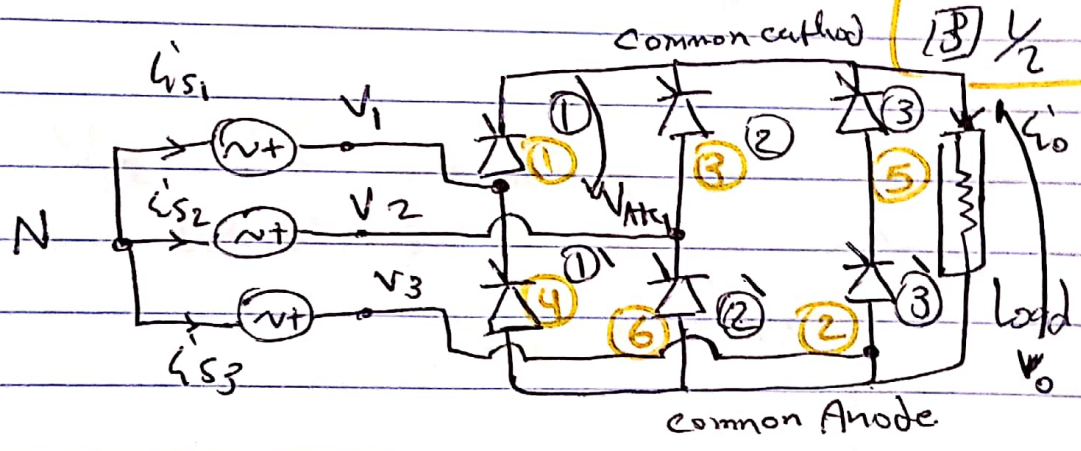- full wave
- half wave
- Disadvantages:
 - 1) Dc in supply
 - 2) low power
 - 3) $\frac{1}{2}$ voltage



- Real numbering
- non-currented numbering

⊗ Common cathode \equiv positive rectifying group.

⊗ common anode \equiv negative rectifying group

⊗ V_{AK1}, V_{AK2}, \dots are the same but with phase shift.

⊗ القضية P_{load} و I_{load} و V_{load}

• Supply (3-phase balanced (true sequence))

Reference $\rightarrow V_1 = V_m \sin(\omega t)$

$V_2 = V_m \sin(\omega t - 2\pi/3)$

$V_3 = V_m \sin(\omega t - 4\pi/3)$

\rightarrow For a balanced supply: \rightarrow




- 1] V_m 's are equal (peak)
- 2] ωt 's are equal
- 3] 120° shift between one voltage and another

● $V_{12} = V_1 - V_2 = V_m \sin \omega t - V_m \sin \omega t - \dots$


Graphically:-

$V_{12} = \sqrt{3} V_m \sin(\dots \omega t + \pi/6)$

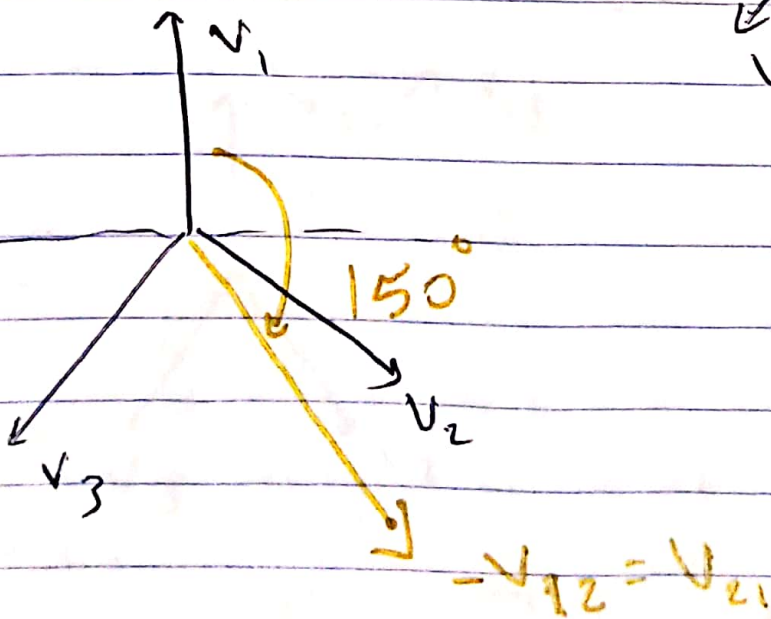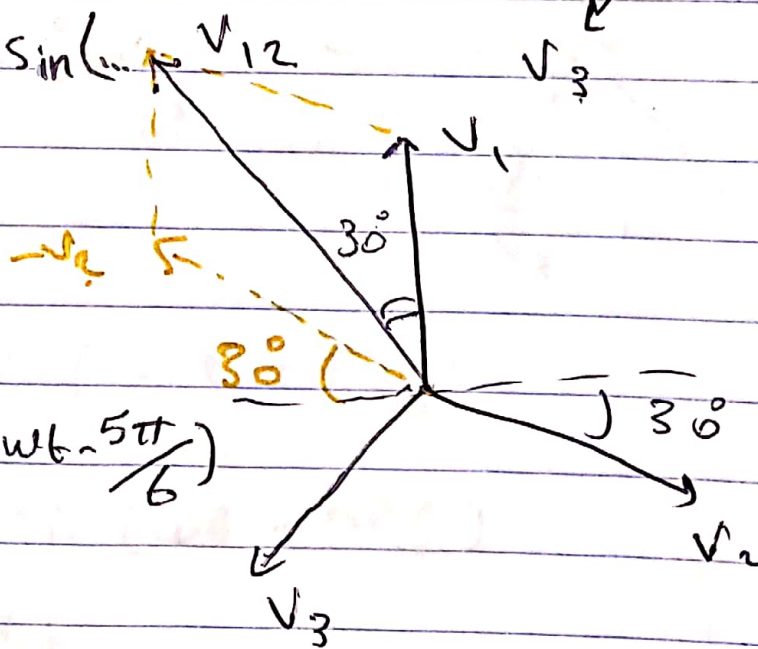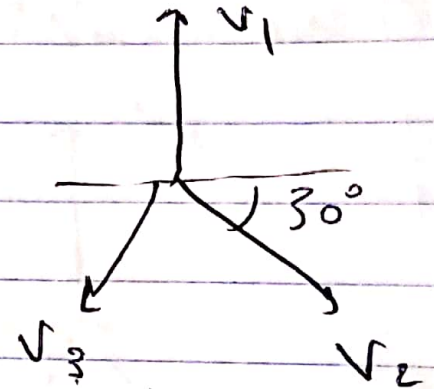
$V_{21} = \sqrt{3} V_m \sin(\omega t - 5\pi/6)$


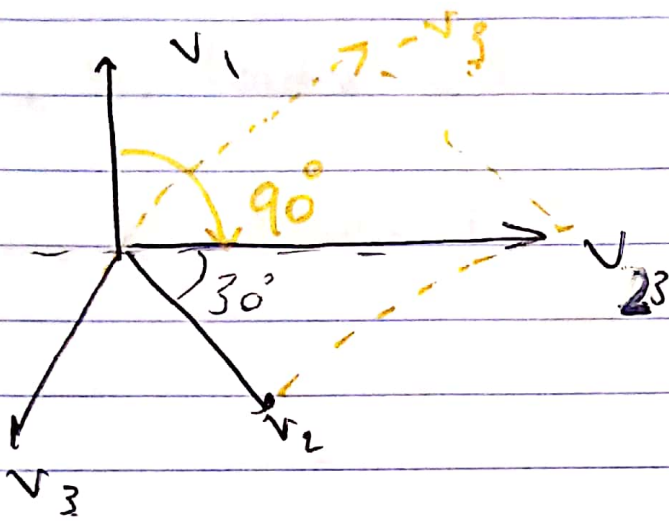
$$V_{23} = \sqrt{3} V_m \sin(\omega t - \frac{\pi}{2})$$




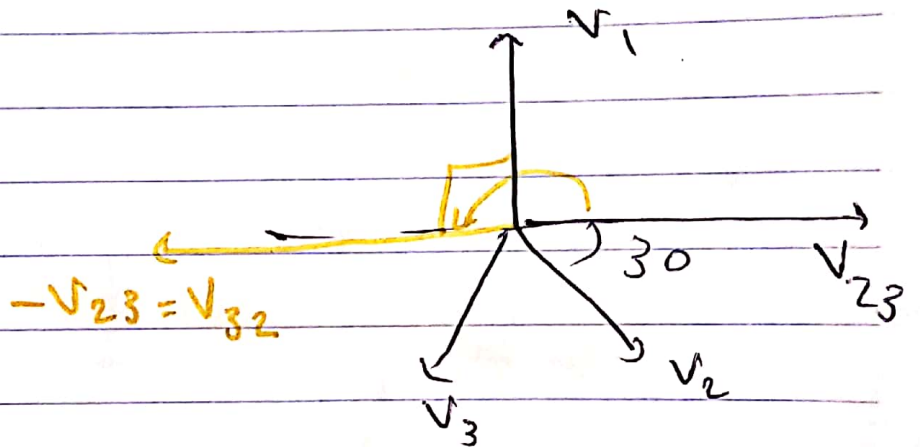
$$V_{32} = \sqrt{3} V_m \sin(\omega t + \frac{\pi}{2})$$



$$V_{31} = \sqrt{3} V_m \sin(\omega t - \frac{7\pi}{6})$$

or

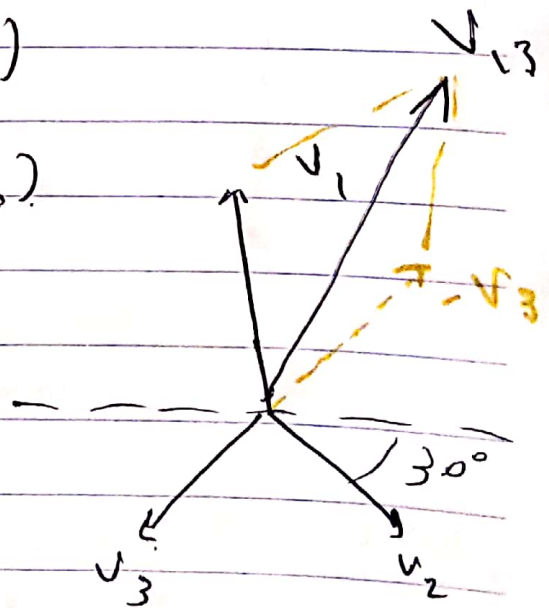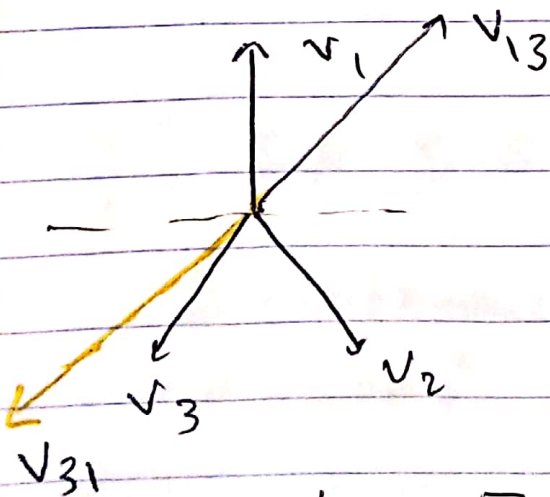
$$V_{31} = \sqrt{3} V_m \sin(\omega t + \frac{5\pi}{6})$$



$$V_{13} = \sqrt{3} V_m \sin(\omega t - \frac{\pi}{6})$$

or


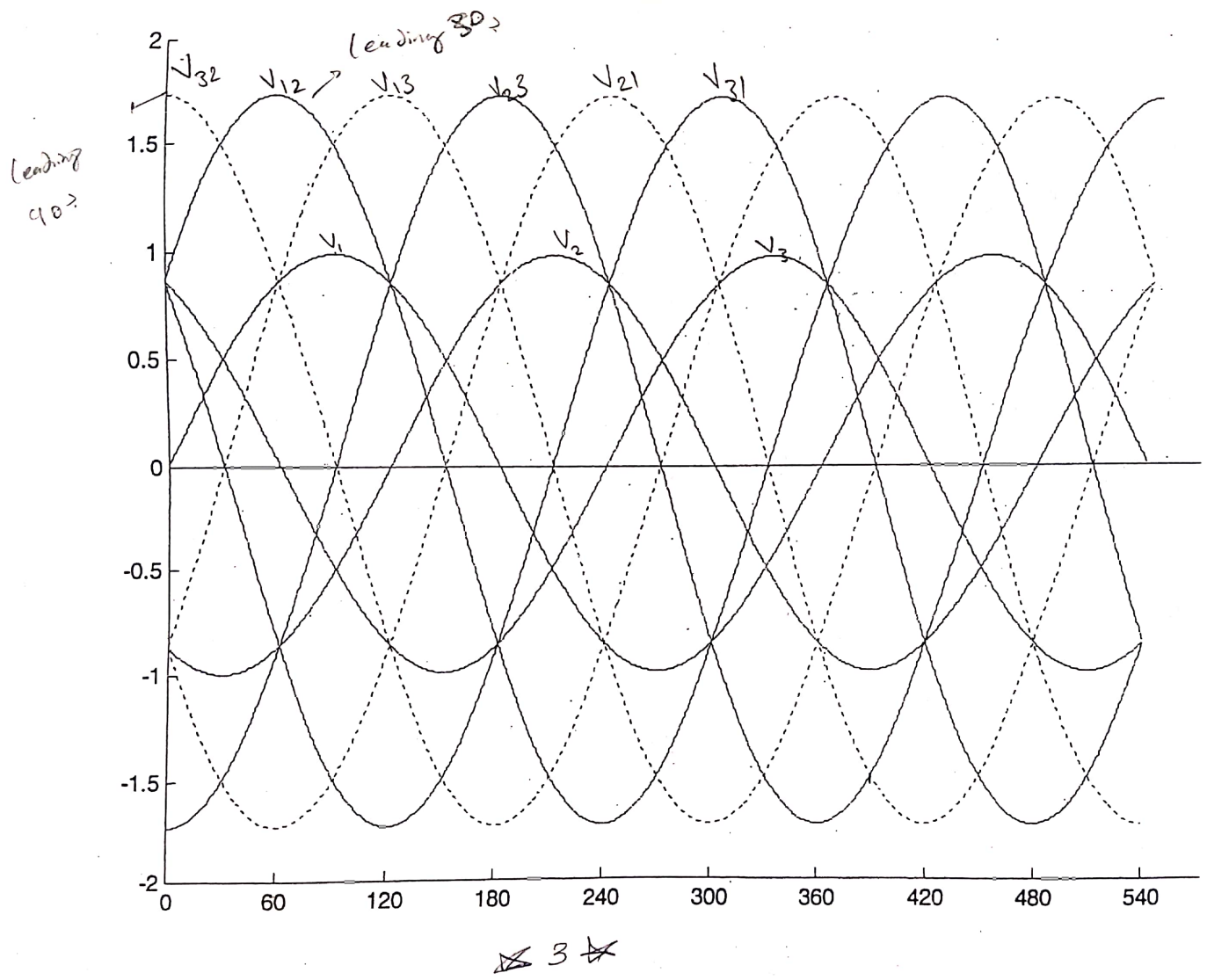
$$V_{13} = \sqrt{3} V_m \sin(\omega t + \frac{11\pi}{6})$$



referring to $\star 3\star$

$\rightarrow V_{12}$ leading by 30°

$\rightarrow V_{32}$ leading by 90°

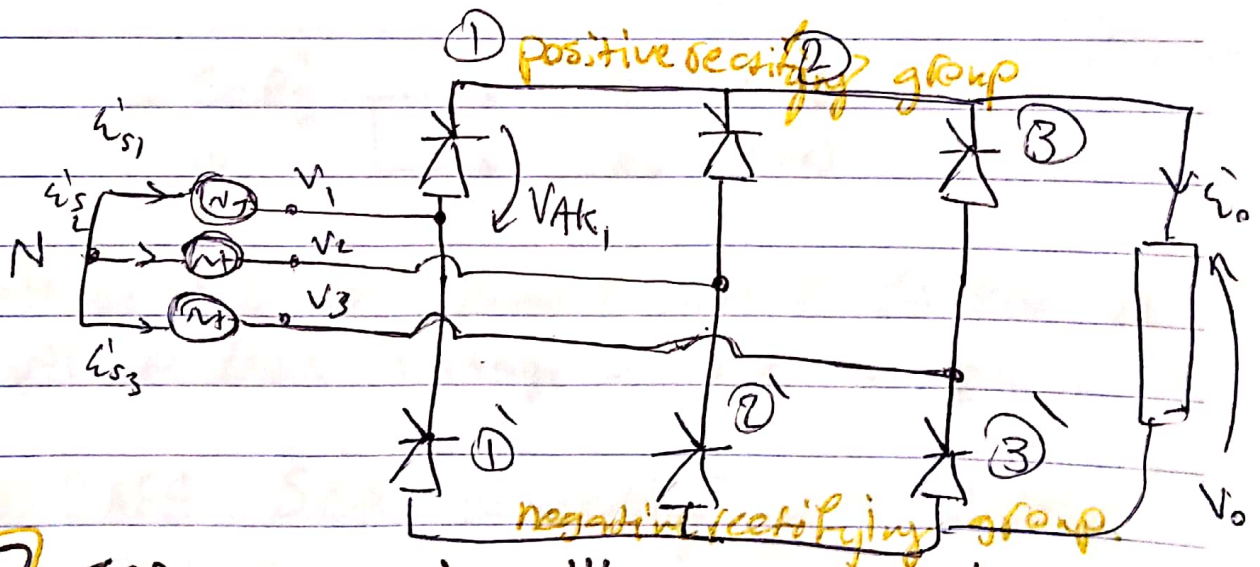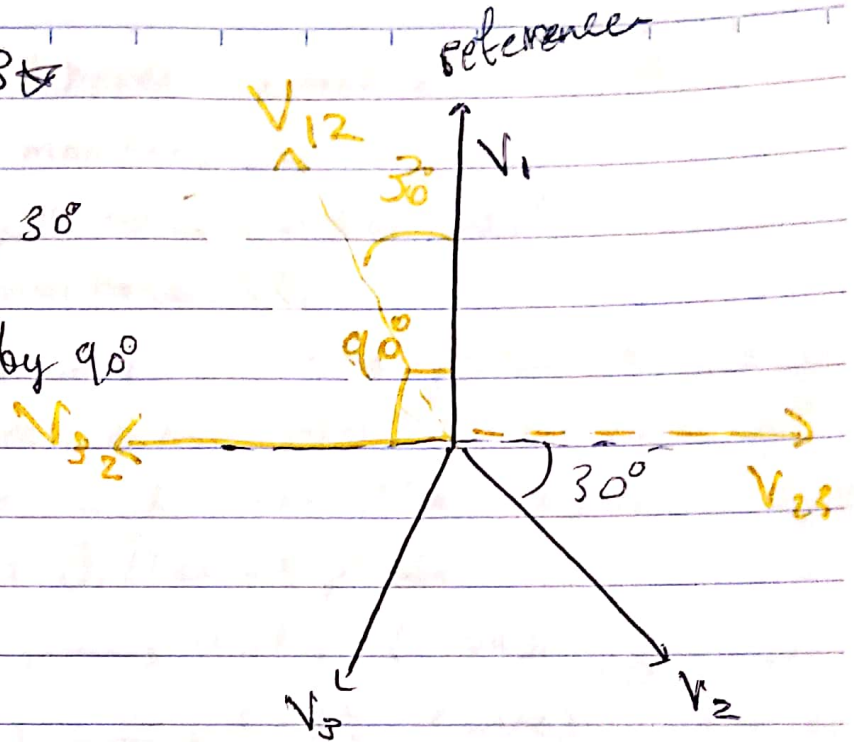

1) SCR₁ & SCR_{1'} will never conduct

Simultaneously & the same for SCR₂ and SCR_{2'}, SCR₃ and SCR_{3'}.

2) any Thyristor of the positive group will never conduct with another SCR in the same group.

eg: \therefore SCR(1) will never conduct with SCR(2) or SCR(3) simultaneously.

+ SCR(1) will never conduct with SCR(1) or SCR(3) simultaneously.


[3] any Thyristor at the positive group should share conduction simultaneously with another SCR from the negative group but belongs to different phase.

eg: + SCR₁ (+ve) $\begin{cases} \rightarrow \text{SCR}_2 (-ve) \\ \rightarrow \text{SCR}_3 (-ve) \end{cases} \neq \text{SCR}_1$
Some phase!

+ SCR₂ (-ve) $\begin{cases} \rightarrow \text{SCR}_1 (+ve) \\ \rightarrow \text{SCR}_3 (+ve) \end{cases}$


6. Voltage ال حساب؟ $V_1 - V_0 - V_2 = 0$
 $V_0 = V_{12}$

⊙ CASE SCR₁ conducting with SCR₂

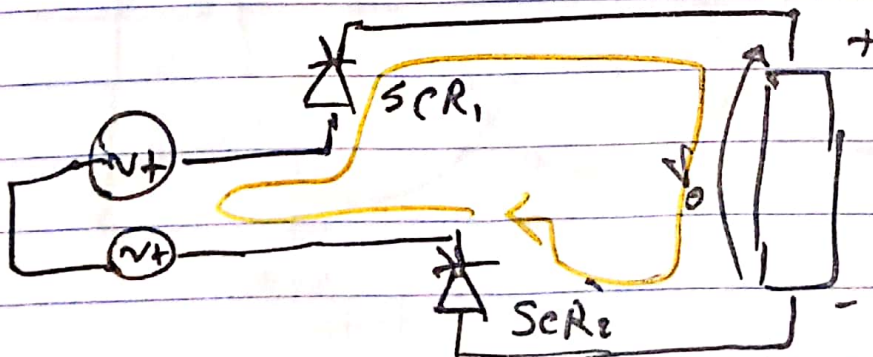

• $V_1 - V_0 - V_2 = 0$
 $V_0 = V_{12}$


CASE SCR₁ conducting with SCR₃

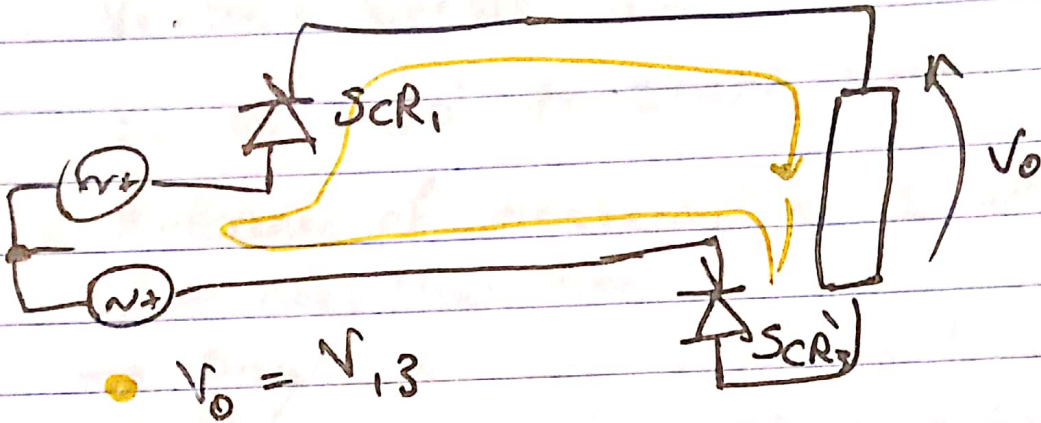

The voltage across the Load is parts of the line voltages, not the (phase) voltages

e.g. :- $V_{12}, V_{23}, V_{32}, V_{21}, \dots$

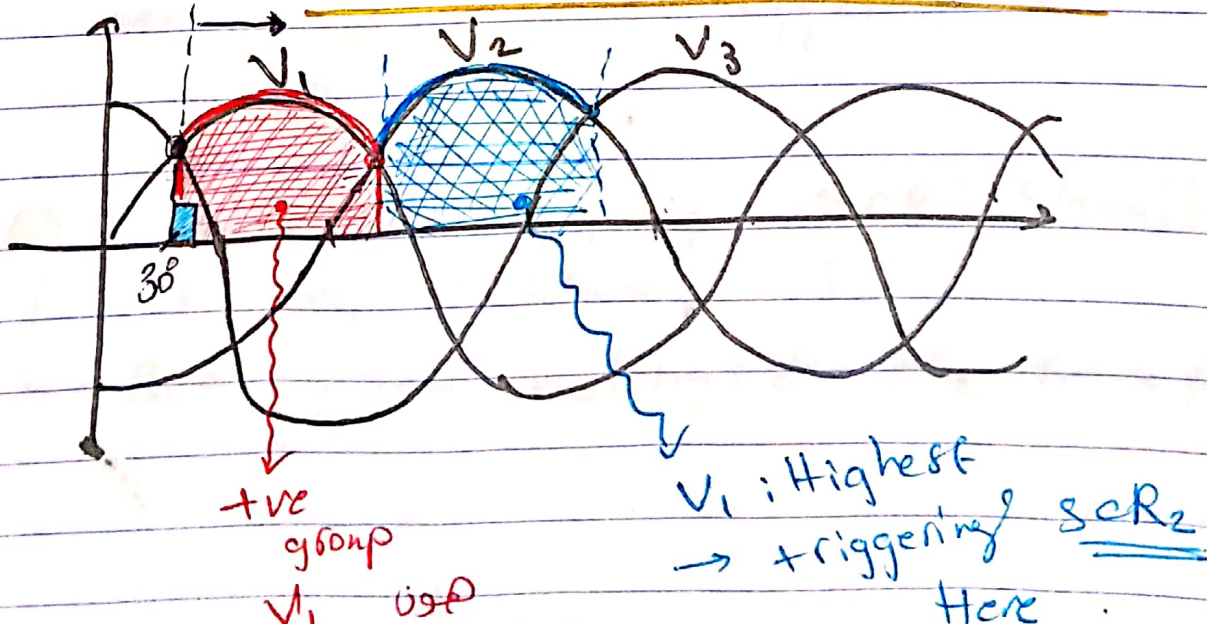$\omega t = \frac{\pi}{6} = 30^\circ$
Reference of measuring α



Highest in polarity
 SCR₁ is first, then SCR₂ is
 - then to SCR₃ *

● $0^\circ \rightarrow 30^\circ$, we can't conduct SCR,
because V_1 isn't the highest in
voltage before 30° .

so $\alpha = 30^\circ$ to start SCR,

* Reference of measuring α is $\omega t = \pi/6$,
what does that mean?

→ say $\alpha = 30^\circ$, SCR₁ is triggered at
 $\omega t = ??$ $60^\circ = \omega t \rightarrow \alpha = 30^\circ$

● Each SCR is capable of conducting
 120° at maximum.

- If SCR₁ is triggered at $\omega t = X$, SCR₂
should be triggered at $\omega t = X + 120^\circ$
and SCR₃ will be triggered at
 $\omega t = X + 240^\circ$



● For the negative group, SCR_{1'} should be
triggered at $\omega t = X + 180^\circ$
↳ SCR₁ & SCR_{1'} belongs to the same phase.



3-phase Rectifiers



Waveform construction.

$\alpha = 0 \rightarrow$ equivalent to uncontrolled rectifier.



<u>SCR No.</u>	<u>Starts conduction at $\omega t =$</u>	<u>Ends conduction at $\omega t =$</u>
<u>1</u>	<u>$\alpha + 30$</u>	$(\alpha + 30) + 120 =$ <u>$\alpha + 150$</u>
<u>1'</u>	$(\alpha + 30) + 180 =$ <u>$\alpha + 210$</u>	$\alpha + 210 + 120 =$ <u>$\alpha + 330$</u>
<u>2</u>	$(\alpha + 30) + 120 =$ <u>$\alpha + 150$</u>	$\alpha + 150 + 120 =$ <u>$\alpha + 270$</u>
<u>2'</u>	$(\alpha + 150) + 180 =$ <u>$\alpha + 330$</u>	$\alpha + 330 + 120 =$ <u>$\alpha + 450$</u> $\swarrow \quad \searrow$ <u>$\alpha + 360$</u> $0 \rightarrow 90^\circ$
<u>3</u>	$(\alpha + 150) + 120 =$ <u>$\alpha + 270$</u>	$\alpha + 270 + 120 =$ <u>$\alpha + 390$</u> $\swarrow \quad \searrow$ <u>$\alpha + 360$</u> $0 \rightarrow 30^\circ$
<u>3'</u>	$\alpha + 270 + 180 =$ $= \alpha + 450$ $90^\circ \swarrow$	$\alpha + 90 + 120 =$ <u>$\alpha + 210$</u>

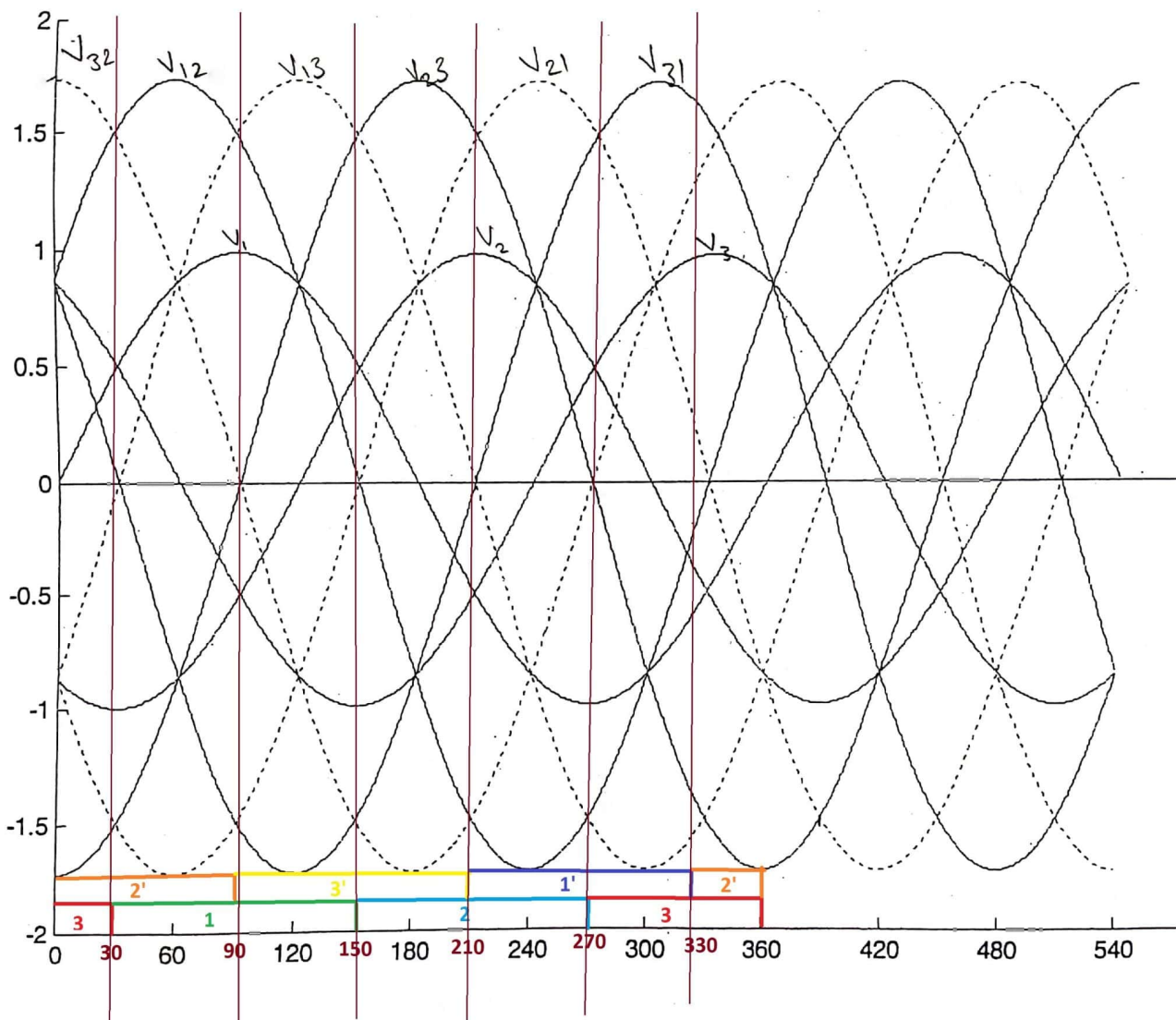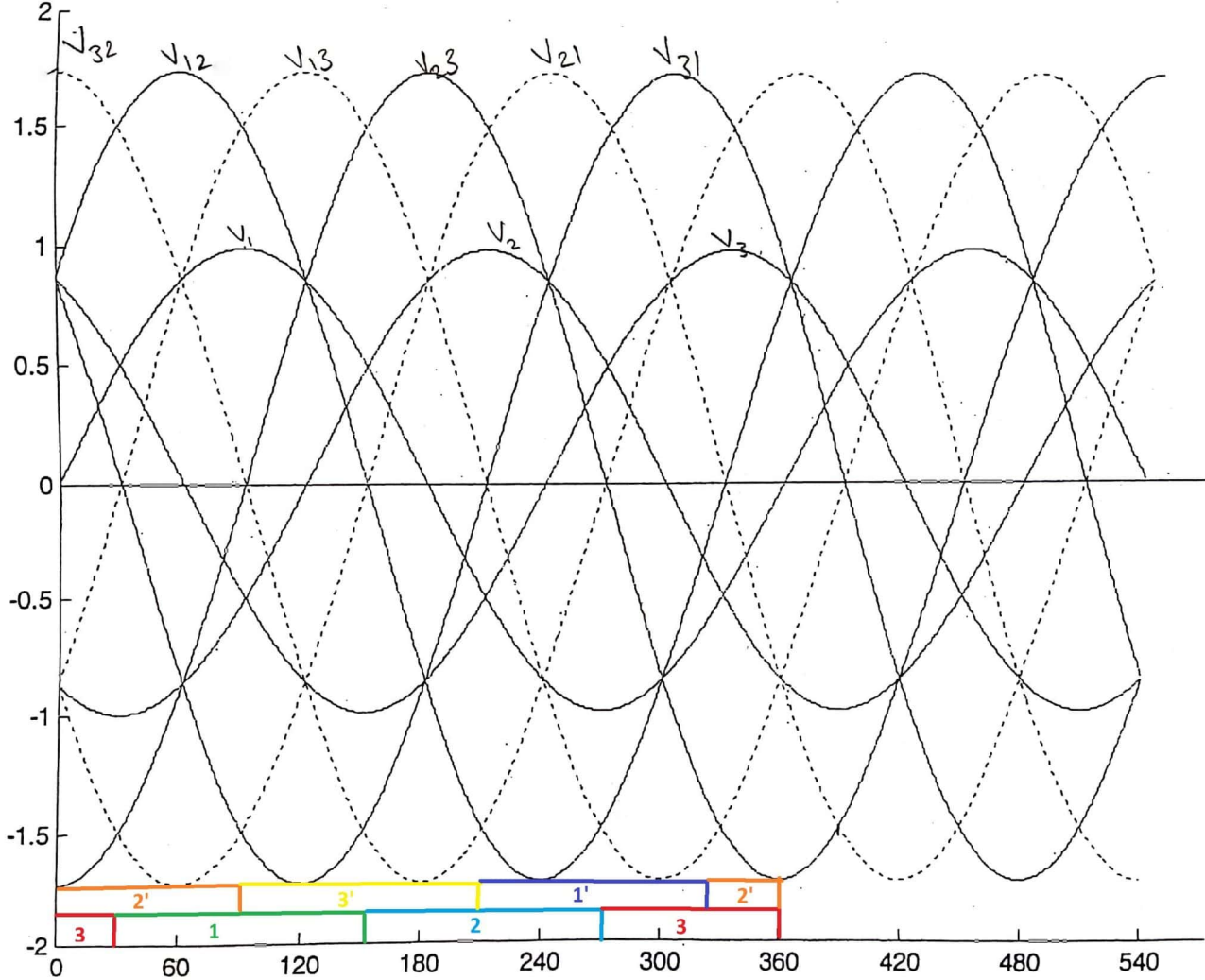

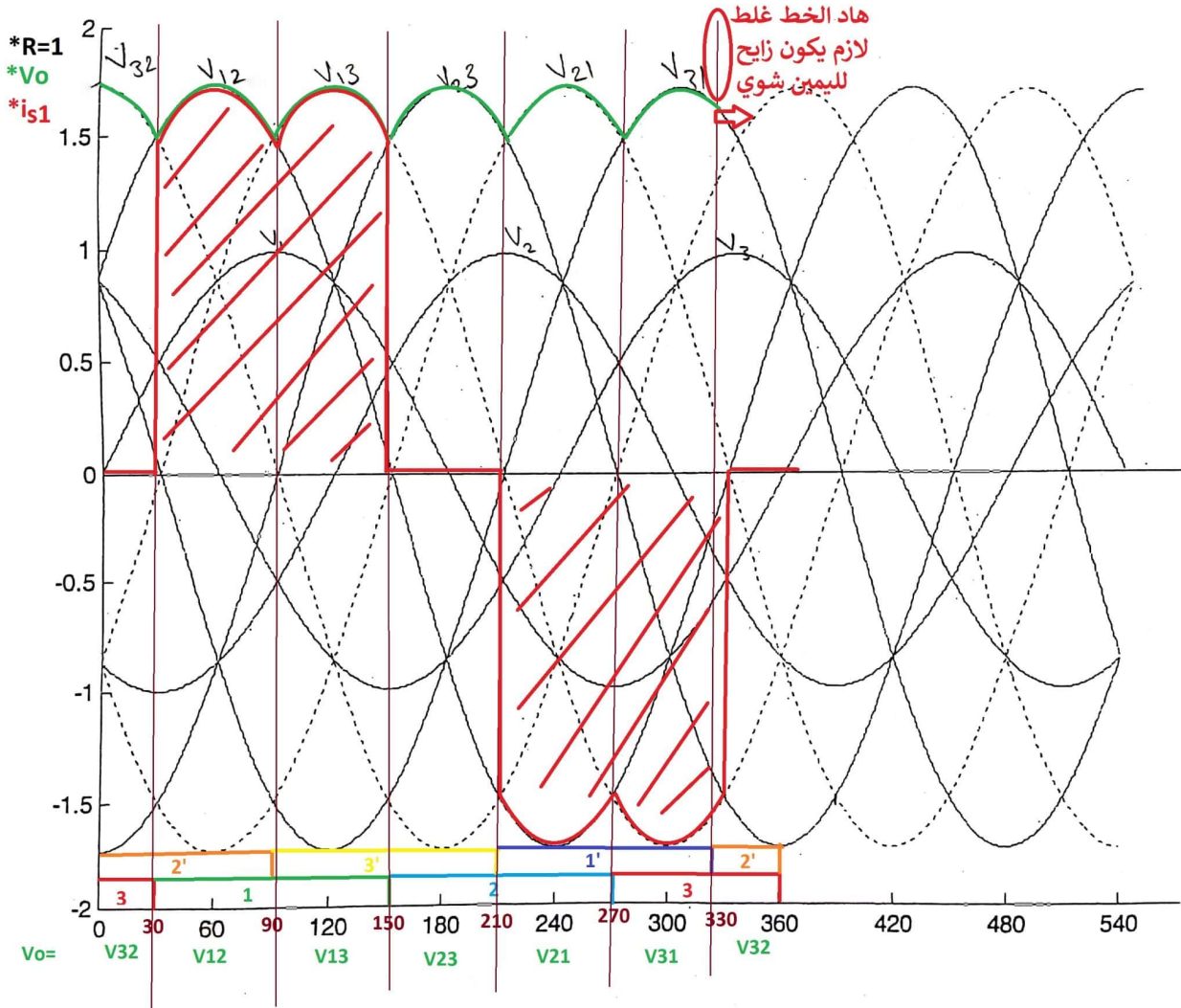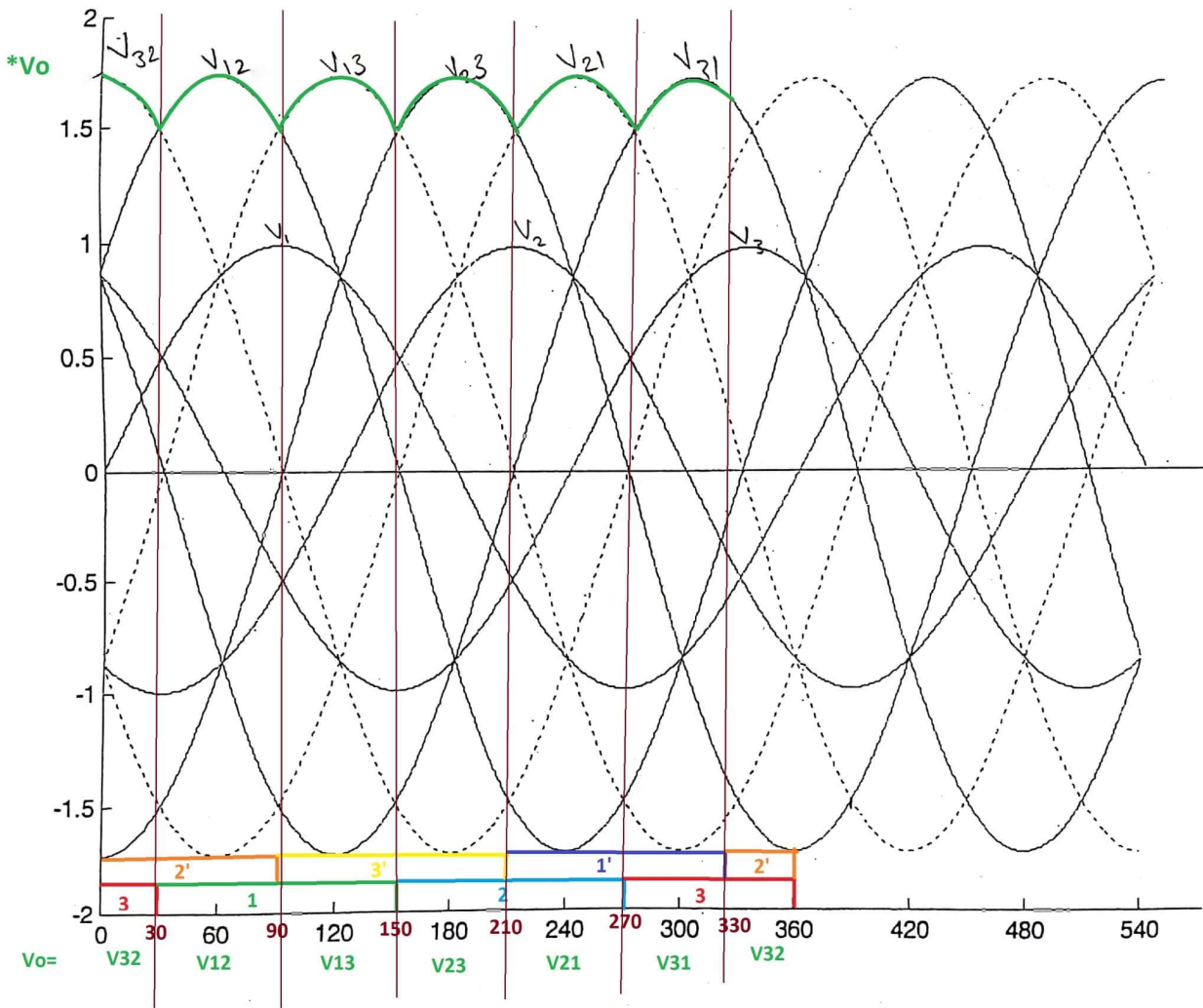

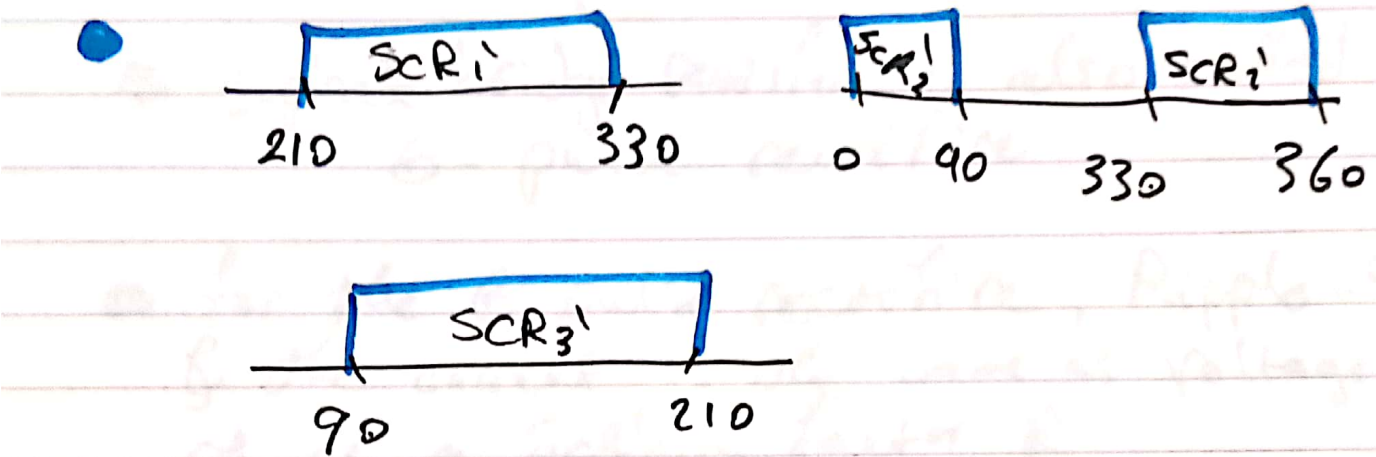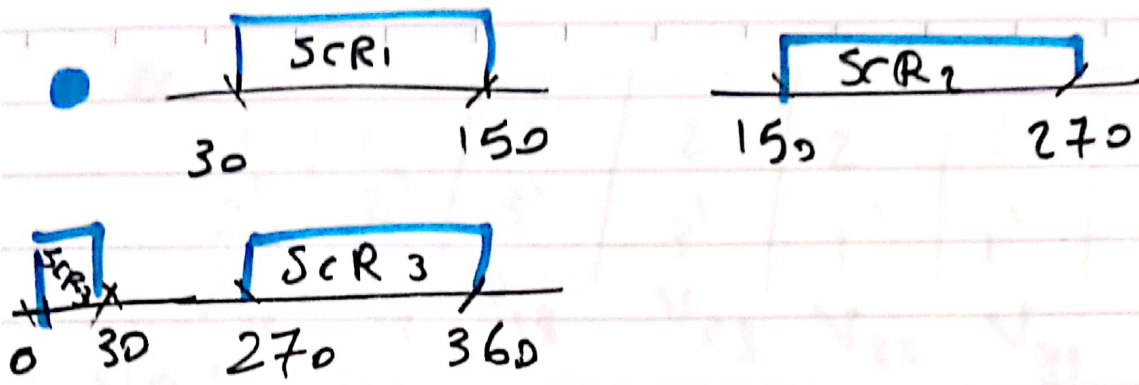


conventional numbering (fig)

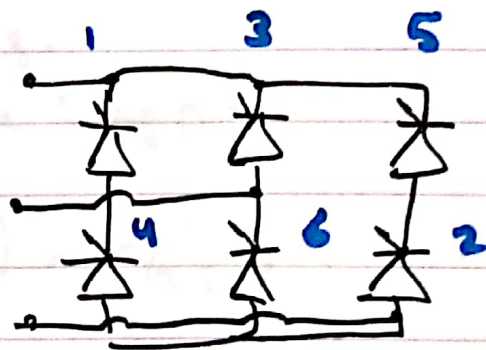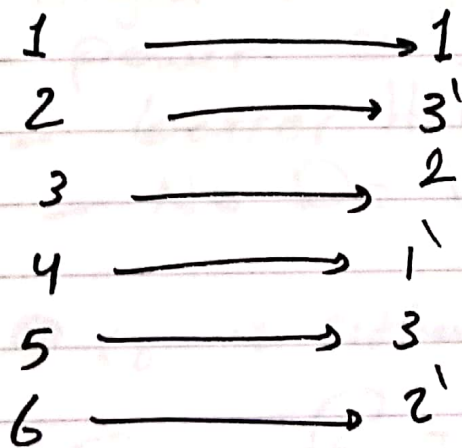

numbering according to the sequence of triggering/switching.

$$\rightarrow V_o = \sqrt{3} V_m \left[\frac{3}{2} \right], V_o = V_{13} \left[\frac{3}{3'} \right]$$
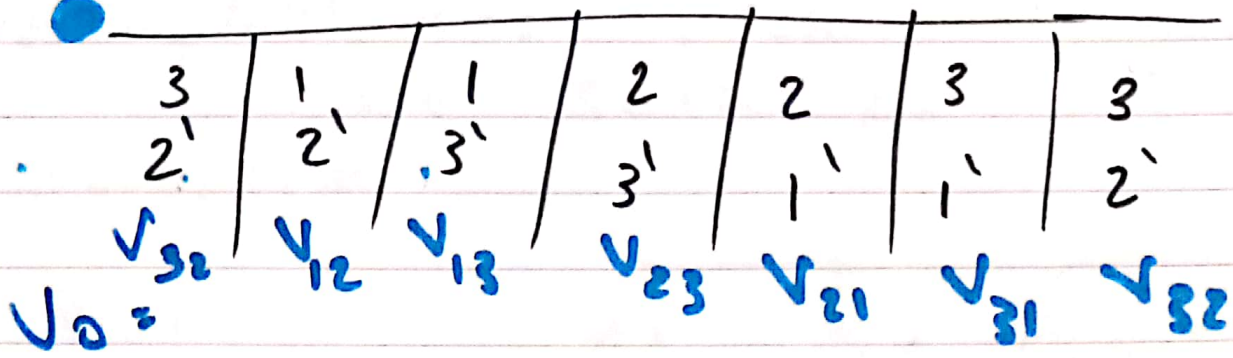
$$V_o = \sqrt{3} V_m \left[\frac{1}{2} \right]$$



● 3-phase bridge rectifier is also called 6-pulse rectifier

● For the 6-pulse rectifier, Ripple = 4% & the current is the same as voltage except a scaling factor \underline{R}


● 3-phase rectifier advantages:

- Higher voltage $\approx 3 \times V$ (cable/w)
- Power $\approx 3 \times P$ (cable/w)
- better Harmonics.
- No DC in the supply

● i_o is either (i_{s1}) or $(-i_{s2})$


$$I_{s1} = \sqrt{\frac{2}{3}} I_o(\text{rms})$$

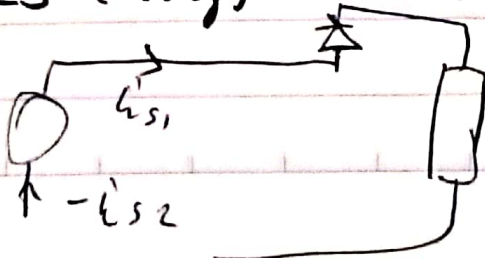$I_s(\text{avg}) = 0 \Rightarrow$ Zero always in supply.



Example ①, $\alpha = 30^\circ$, SCR is triggered at
 $\omega t = 30 + \alpha = \underline{60^\circ}$

Mode: CCM.

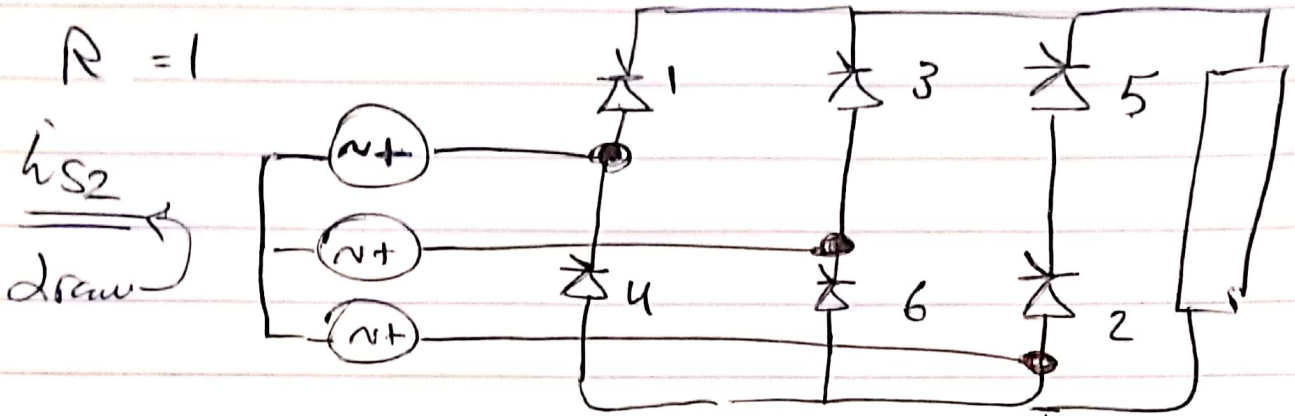

check Example 1
 Solution. in
 Next
 pages))

Example ② $\alpha = 60^\circ$ single phase
 resistive load $\alpha_{cr} = 0$

$$\phi = \alpha_{cr} = 0$$



$$\omega t = 30 + 60 = 120 \text{ (starts SCR}_1\text{)}$$



conducts 1. $90 \rightarrow 120$

1.5A



check solution in
 The next pages.

Example 1

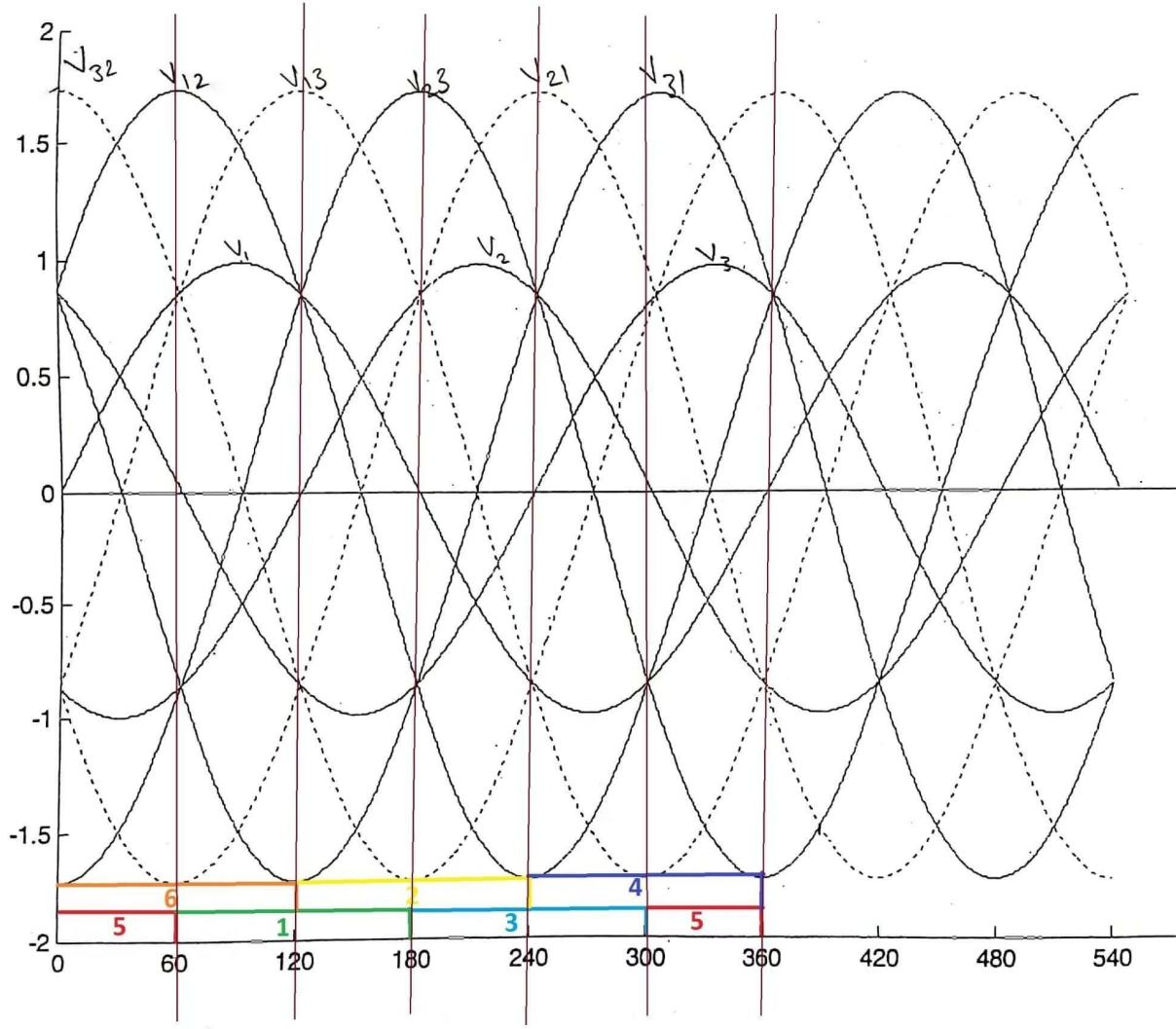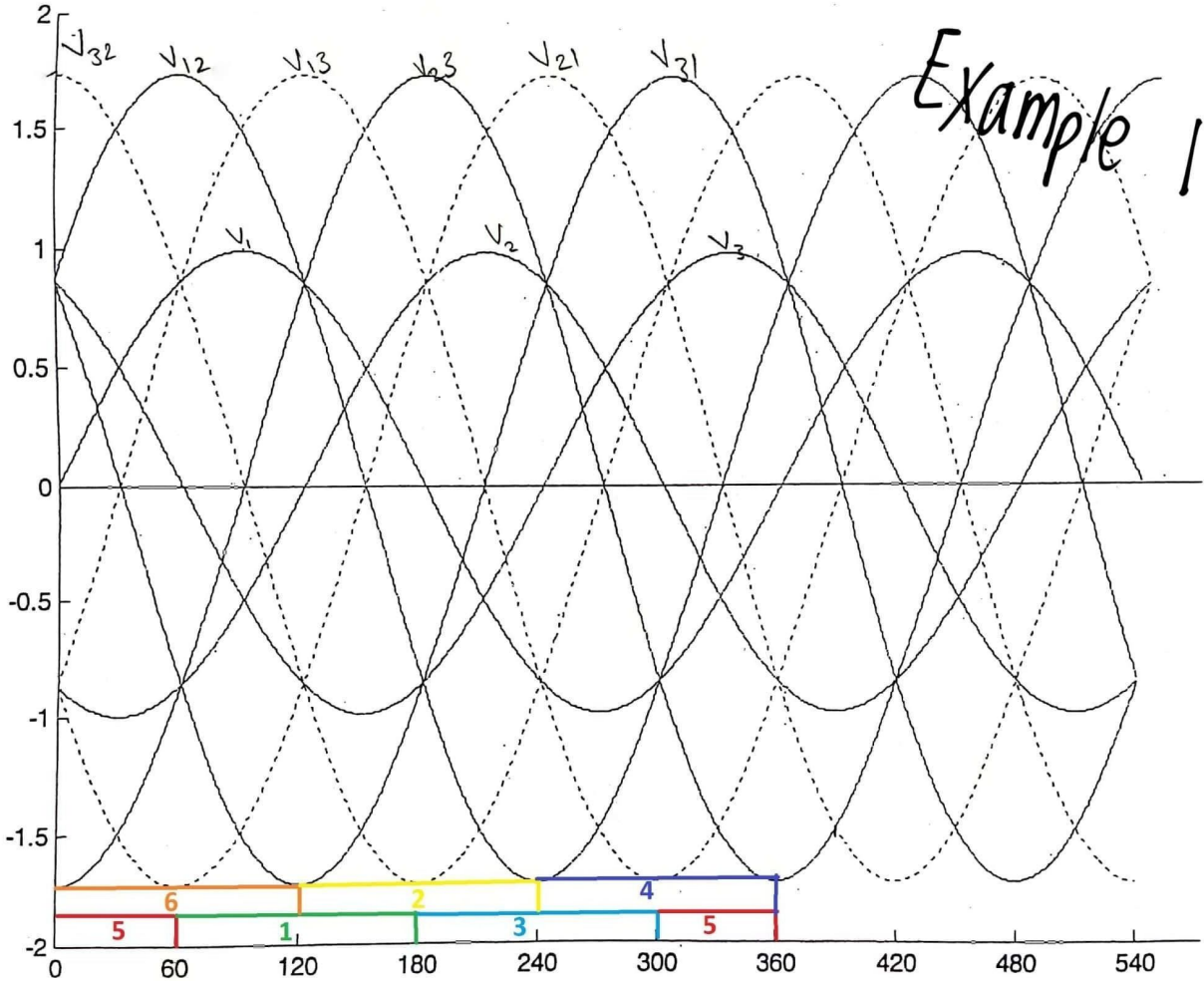

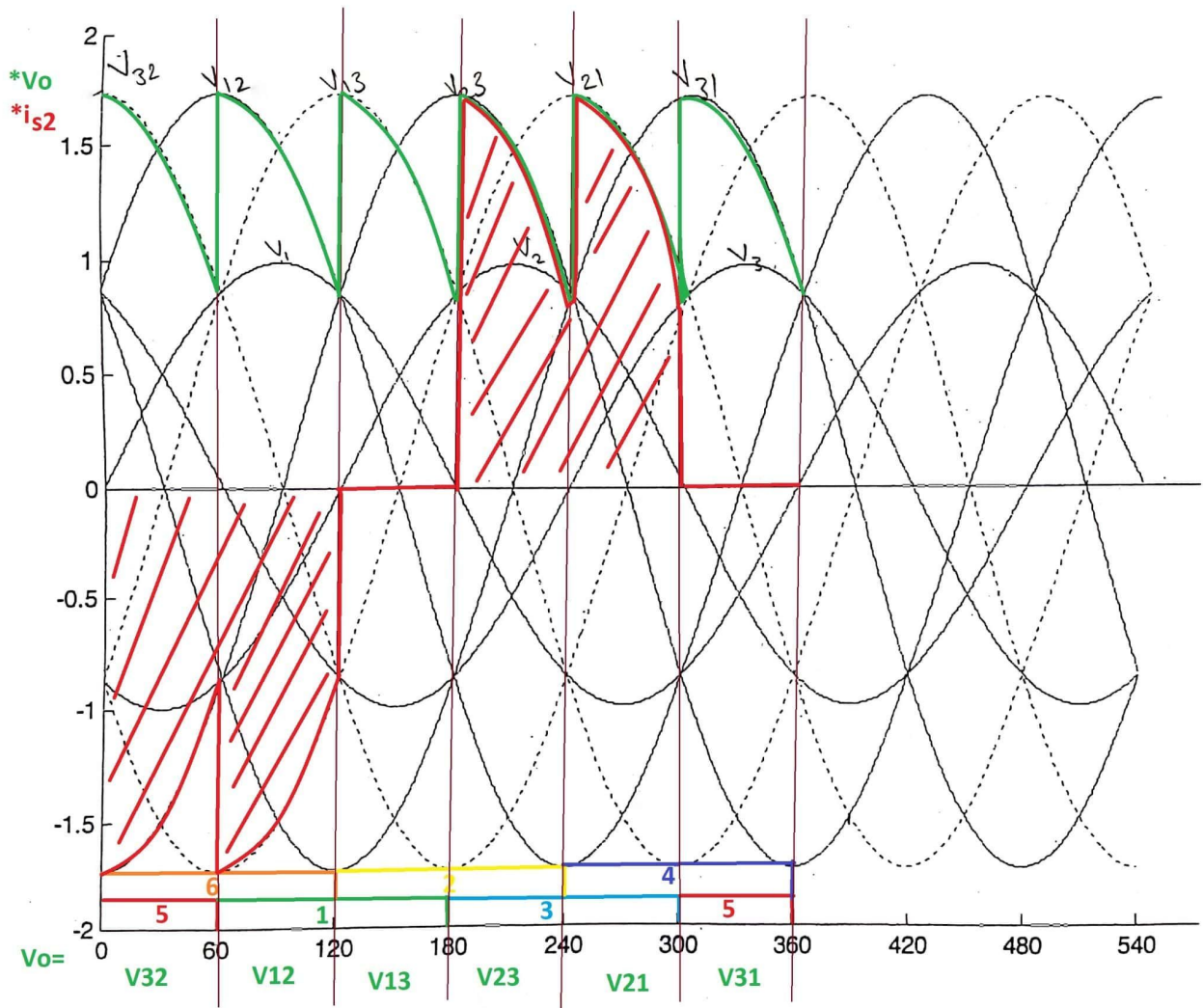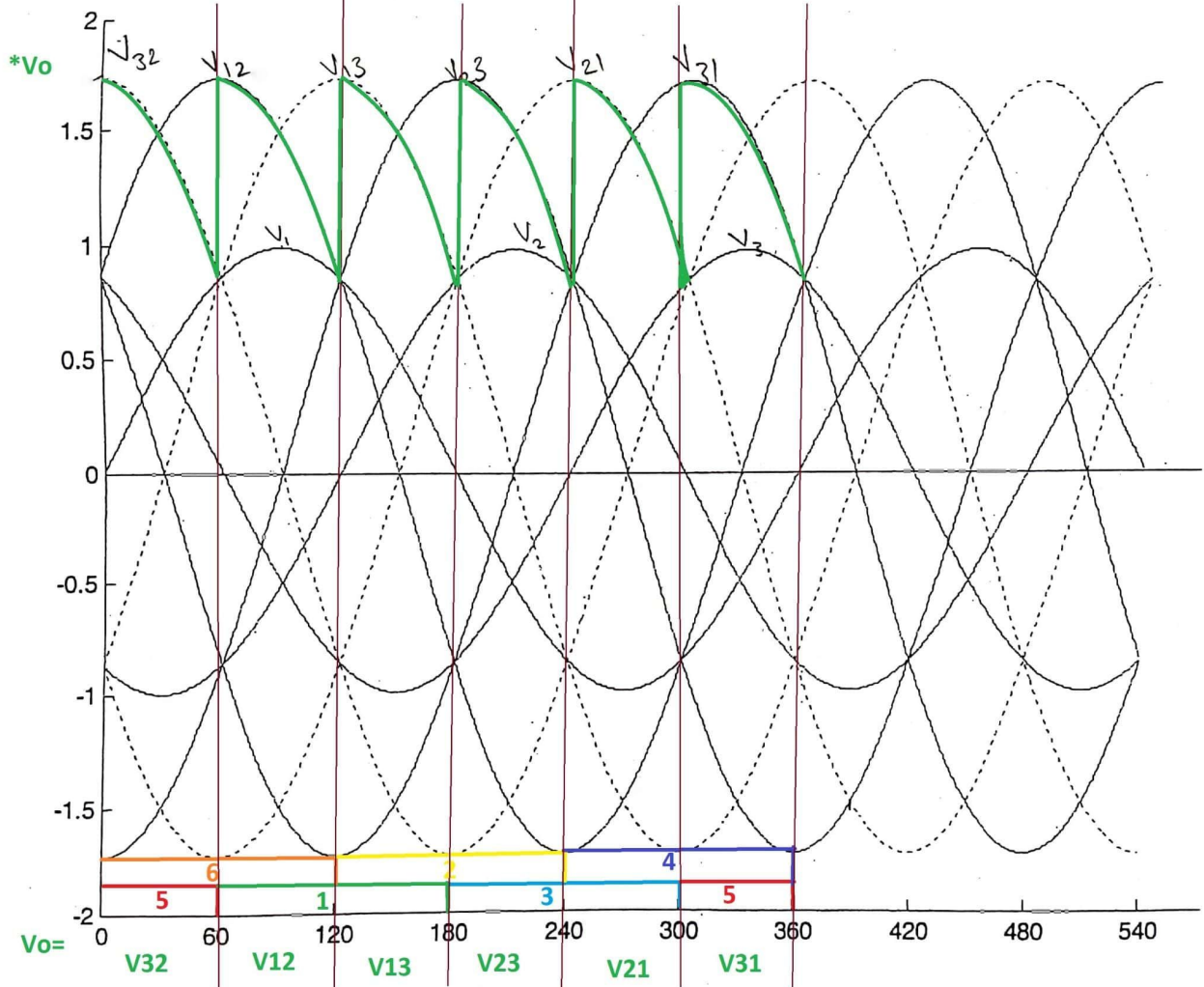

Example 2

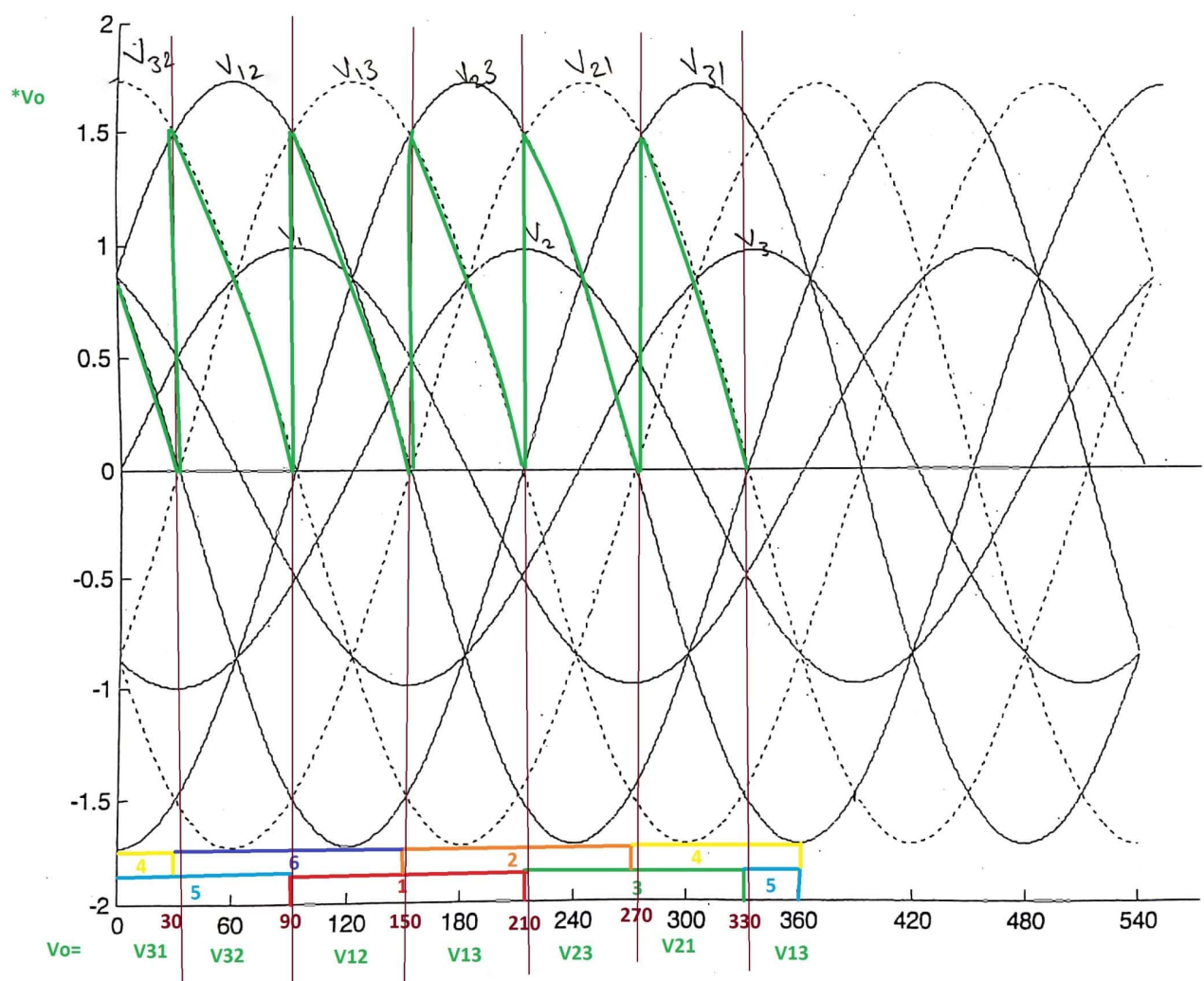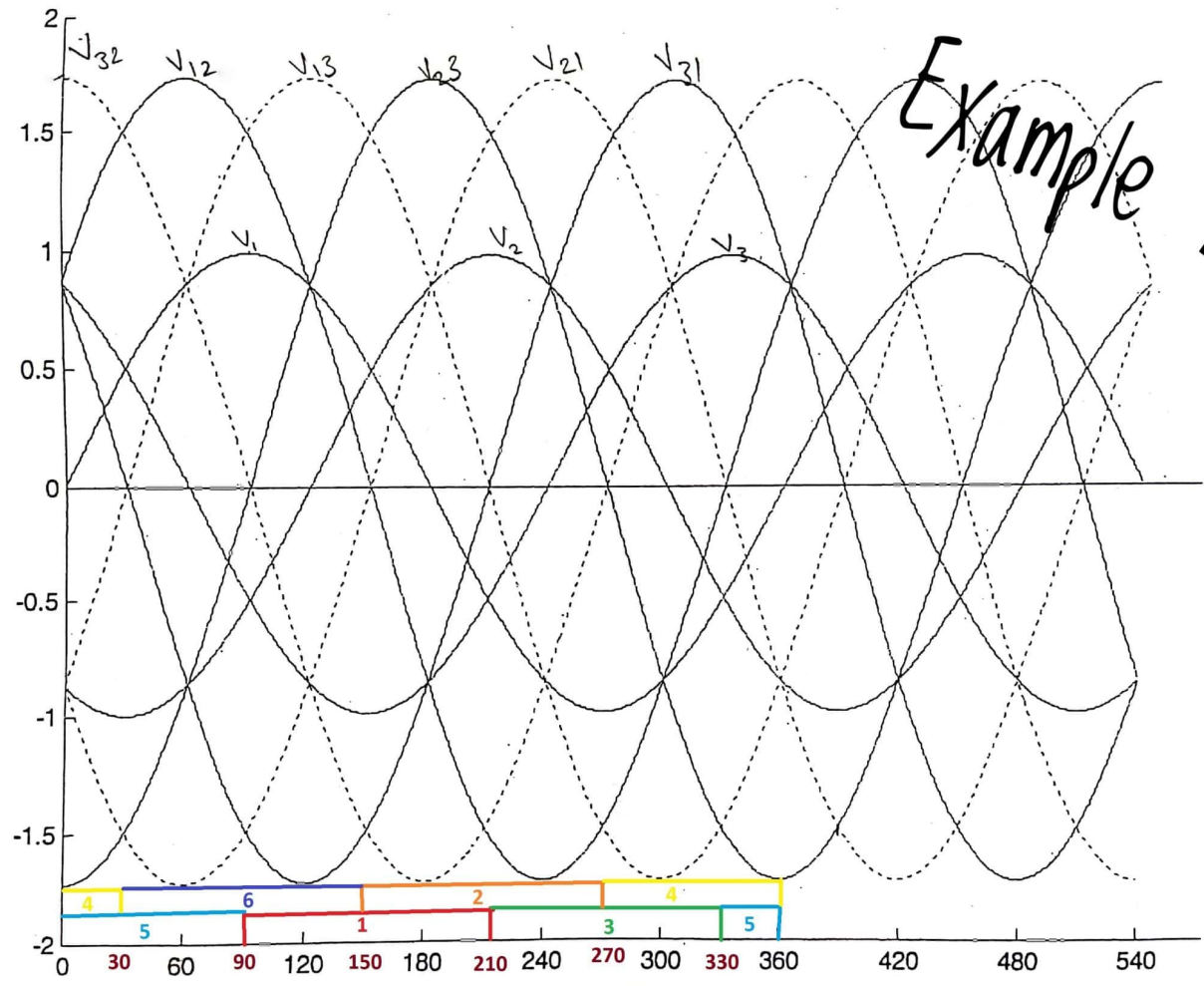

Homework Find V_o & i_s for $\alpha = 45^\circ$

Example 3

$$\alpha = 90^\circ$$


$$SCR_1 \rightarrow \omega t = 30^\circ + 90^\circ = 120^\circ \rightarrow 240^\circ$$

conduction


Mode: DCM

⊗ Check solution in next pages ---


○ if $\alpha < 90^\circ$

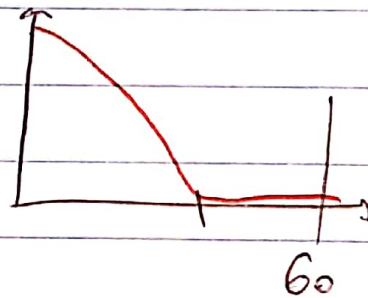



if $\alpha > 90^\circ$

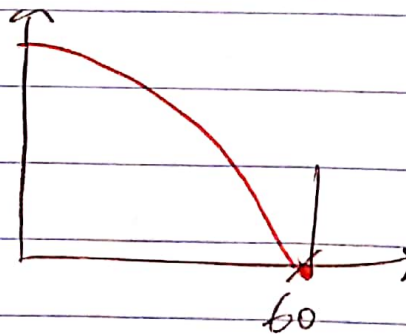

if $90^\circ < \alpha < 120^\circ$

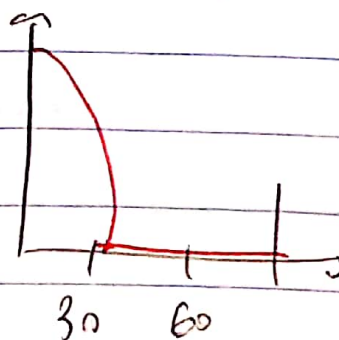

Example 3

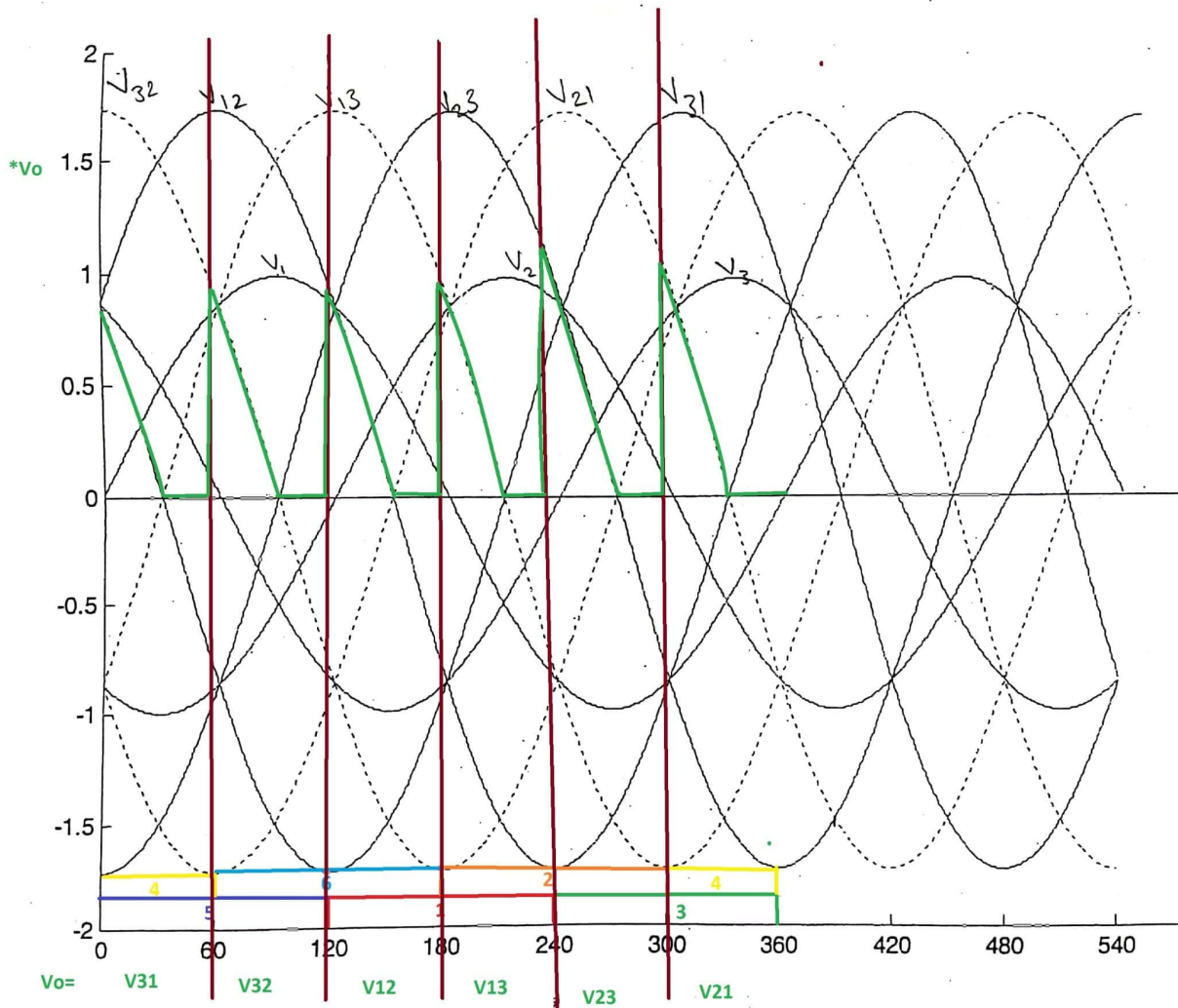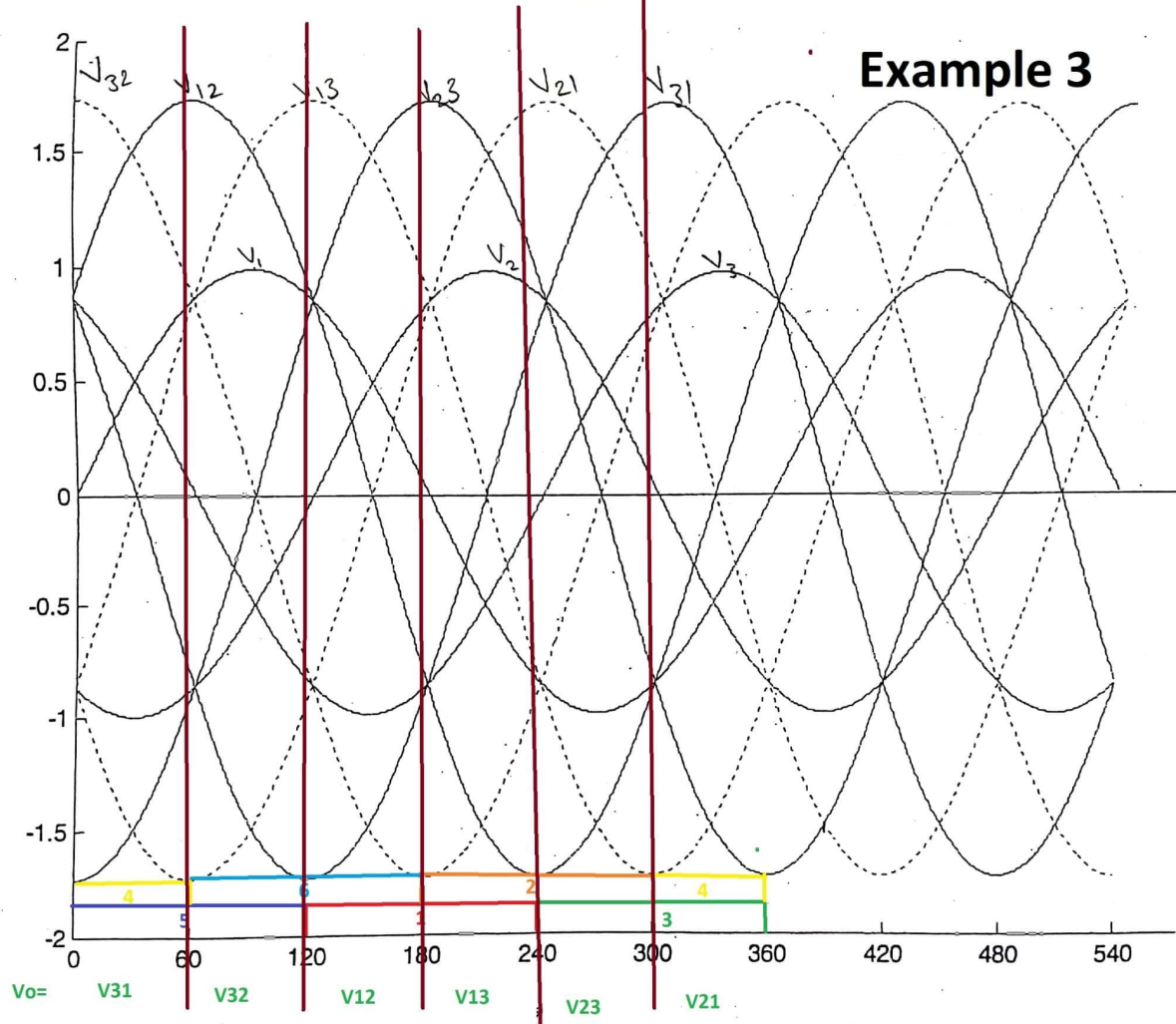

• In DCM CASE:

SCR_i must be triggered twice → @ 30° & 60°
 or else it won't re-conduct ⇒ **HWR**

- This doesn't happen in CCM.

• To avoid error in the output signal, each SCR should be triggered twice:

- SCR₁ (30+α) & (30+α)+60
- SCR₂ (30+α+60) & (30+α+60)+60
- SCR₃ (30+α+120) & (30+α+120)+60

⋮
 & so on

* Exam Question:

α = 75°, SCR₂ is triggered at ωt = ??

Sol:

$$\text{SCR}_2 (30 + 75 + 60) = 165^\circ$$

$$((30 + 75 + 60) + 60) = 225^\circ$$

answer: at 165° and 225°.


• V_o(avg) = ??

two modes of operation. CCM & DCM

CCM:- (0 ≤ α ≤ 60) ⇒ critical mode included.

$$V_o(\text{avg})_{\text{CCM}} = \frac{1}{2\pi/6} \int_{(\alpha + \pi/6)}^{(\alpha + \pi/6) + (\pi/3)} V_{12} \cdot d\omega t$$

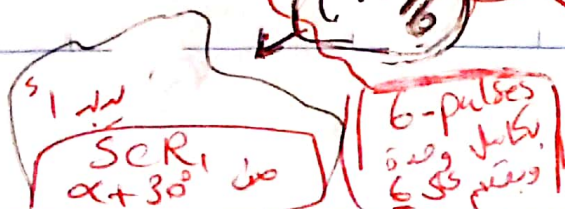نطاقات إشارات pulse هو الفرق بين البداية ونهاية



اول pulse بالترتيب ((Curves))

6-pulses بكل وحدة وتسمى SS


So,

$$\left(\alpha + \frac{\pi}{6} + \frac{\pi}{3}\right) \Rightarrow \frac{\pi}{2}$$

$$V_o(\text{avg})_{\text{CCM}} = \frac{1}{(2\pi/6)} \int_{\alpha + \pi/6}^{\alpha + \pi/2} V_{12} \cdot d\omega t = \frac{3}{\pi} \int_{\alpha + \pi/6}^{\alpha + \pi/2} \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6}) d\omega t$$

$$= \frac{3\sqrt{3} V_m}{\pi} \left[-\cos(\omega t + \frac{\pi}{6}) \right]$$
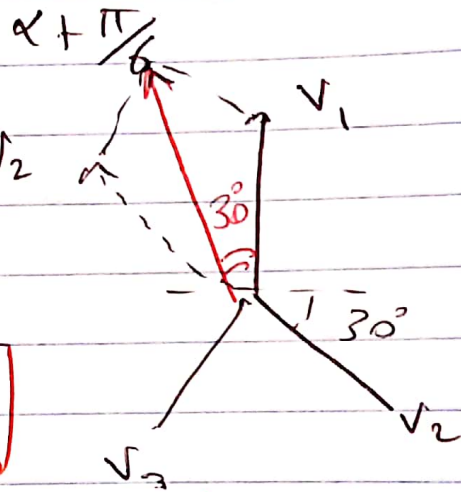
$$= \frac{3\sqrt{3} V_m}{\pi} \left[-\cos(\alpha + 120^\circ) + \dots - \cos(\alpha + 60^\circ) \right]$$



$$V_o(\text{avg})_{\text{CCM}} = \frac{3\sqrt{3} V_m \cos \alpha}{\pi}$$

Peak value of the phase voltage.

NOT the line voltage.

$$= 1.65 V_m \cos \alpha$$

→ compared to single phase

$$V_o(\text{avg}) = \frac{2V_m}{\pi} \cos \alpha \Rightarrow 0.63 V_m \cos \alpha$$

1.65 V_m cos alpha 3phase 31 cèlèlèl "تقریباً"

DCM!

$(5\pi/6) \rightarrow 150^\circ$ is not a function of α .

$$V_o(\text{avg})_{\text{DCM}} = \frac{1}{(2\pi/6)} \int_{\alpha + \pi/6}^{\dots} V_{12} d\omega t$$

• V_{12} always ends conduction at 150° (fixed)

$$\Rightarrow V_{o(\text{avg})}^{\text{DCM}} = \int_{\alpha + \pi/6}^{5\pi/6} \sqrt{3} V_m \sin(\omega t + \pi/6) d\omega t.$$

$$= \frac{3\sqrt{3}}{\pi} V_m \left[-\cos(\omega t + \pi/6) \right]_{\alpha + \pi/6}^{5\pi/6}$$

$$= \frac{3\sqrt{3}}{\pi} V_m \left[-\cos(\pi) + \cos(\alpha + \pi/3) \right]$$

$$V_{o(\text{avg})}^{\text{DCM}} = \frac{3\sqrt{3}}{\pi} V_m \left[1 + \cos(\alpha + \pi/3) \right]$$

• $V_{o(\text{avg})}^{\text{DCM}} = 1.65 V_m \left[1 + \cos(\alpha + \pi/3) \right]$

For critical case.

- $V_{o(\text{avg})}^{\text{er Mode}} = \frac{3\sqrt{3}}{\pi} V_m \cos(60^\circ) = \frac{3\sqrt{3}}{2\pi} V_m$

(or)

- $\frac{3\sqrt{3}}{\pi} V_m \left[1 + \cos(120^\circ) \right] = \frac{3\sqrt{3}}{2\pi} V_m$

SAME \rightarrow DCM equations

* If asked for a certain Voltage value is which mode to choose?

• Calculate the critical mode then.

→ if $V_o(avg) > V_o(avg)_{Cr}$ → CCM


→ if $V_o(avg) < V_o(avg)_{Cr}$ → DCM.

To calculate & draw the current wave form.

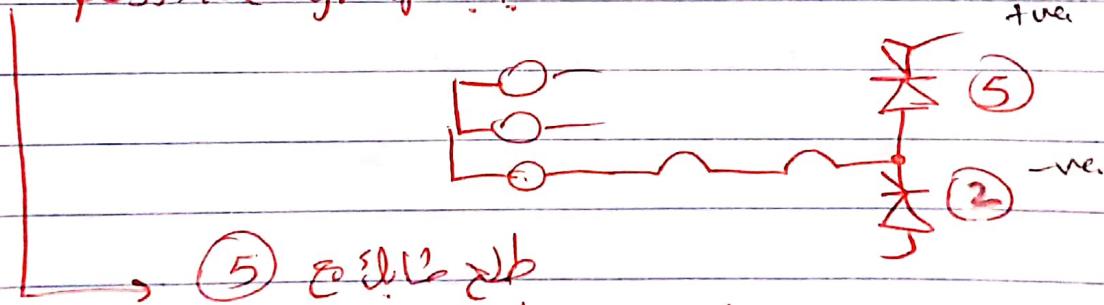Example 3 والتالي (L_s) هو يظهر


→ draw L_{s3}

by SCR و يسأل (V_{s3}) هل هو مجموعة
positive group??



→ (5) هو مجموعة
So, back to the graph → و يظهر
(0 → 120°) ≠ SCR 5 و ...

Check solution
in next page

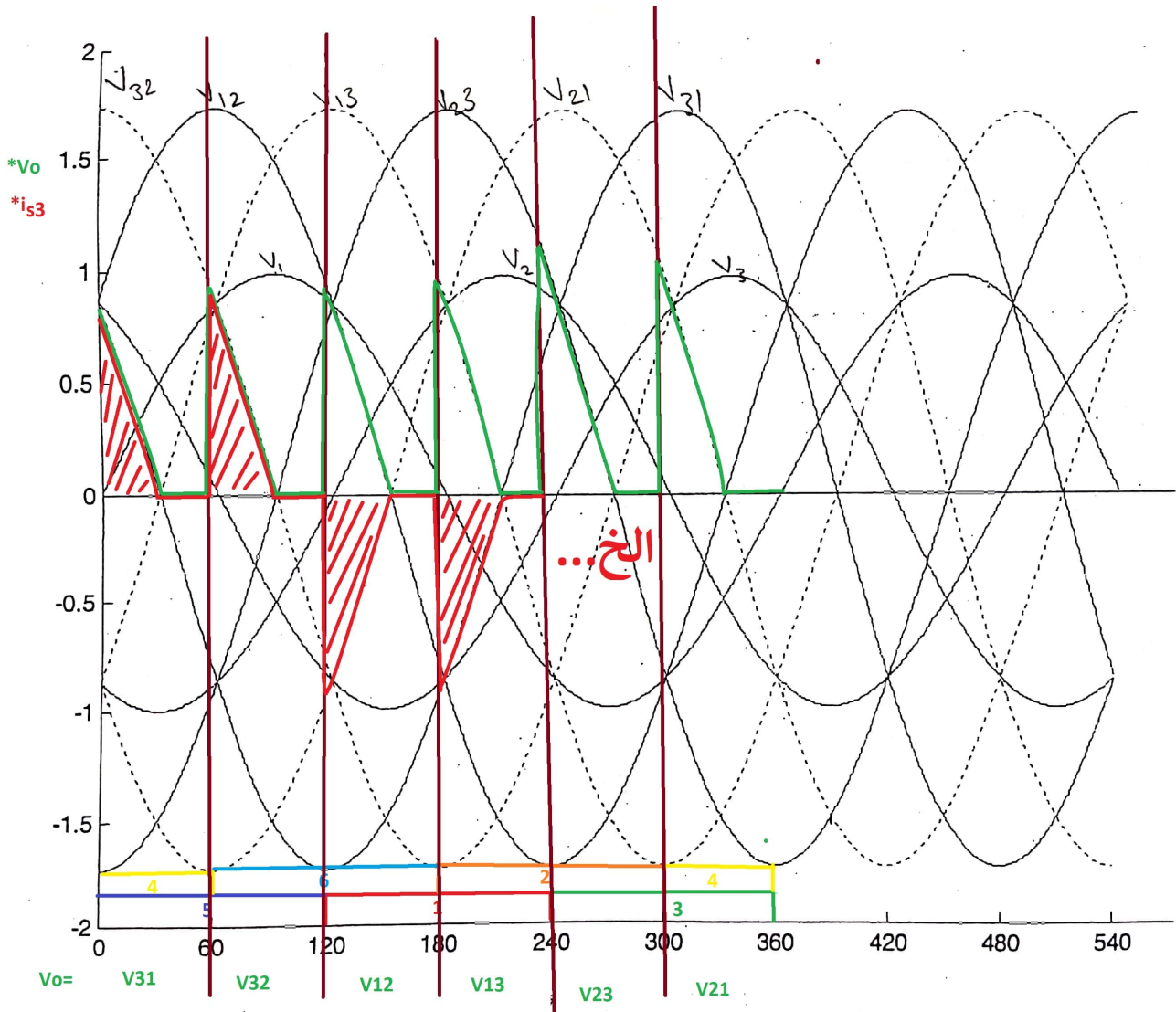

• $\alpha_{max} = ??$

For both CCM & DCM. but we calculate from DCM because small avg. voltage values are in the DCM.

→ When $V_o(avg) = Zero$, $\alpha = max$

$$So, \quad 0 = \frac{3\sqrt{3} V_m}{\pi} \left[1 + \cos\left(\alpha_{max} + \frac{\pi}{3}\right) \right]$$

$$\left[1 + \cos\left(\alpha_{max} + \frac{\pi}{3}\right) \right] = 0$$

$$\cos\left(\alpha_{max} + \frac{\pi}{3}\right) = -1$$


180° = π; ∴ $\alpha_{max} + \frac{\pi}{3} = \pi$

$$\alpha_{max} + \frac{\pi}{3} = \pi$$

$$\alpha_{max} = \frac{2\pi}{3} \quad \text{or} \quad 120^\circ \quad \#$$

Choppers : classifications (A) in terms of $V_o : V_i$

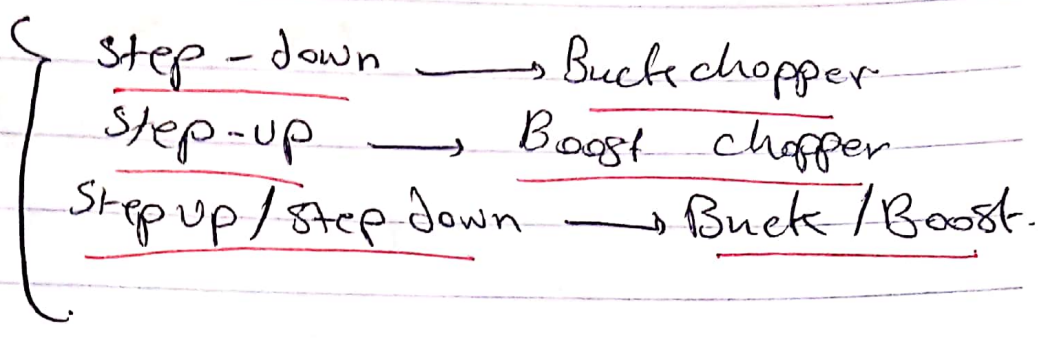
mainly needed for Regulated Dc power Supplies



(Variable Voltage power supply)

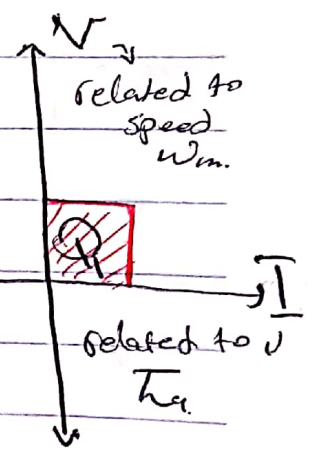
(B) In terms of polarity of V and direction of I
 4-types:-

Class A chopper Positive I & V (Q_1)
 - direction:- drive in forward




Class B chopper

V positive & I negative.

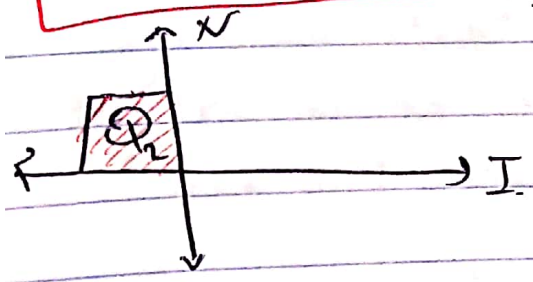

- Ex:-

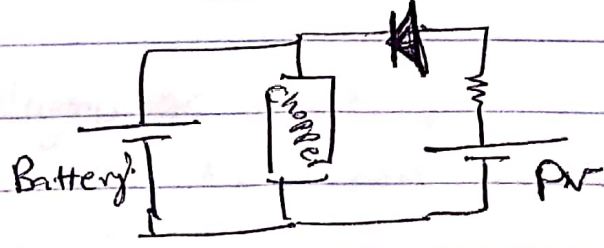
(1) solar cells \rightarrow charging battery



(2) motor \rightarrow Generator or Braking action.

Class C chopper

- Positive v & (+ve and -ve current)

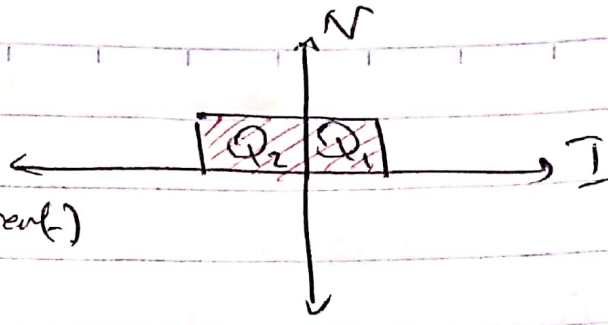


- Q_2 & Q_1
Braking, F.W motoring

- Drive (motoring & Braking (regeneration action))

$\Rightarrow Q_3 \equiv Q_1$

Class D chopper

positive current & (-ve and +ve voltage)

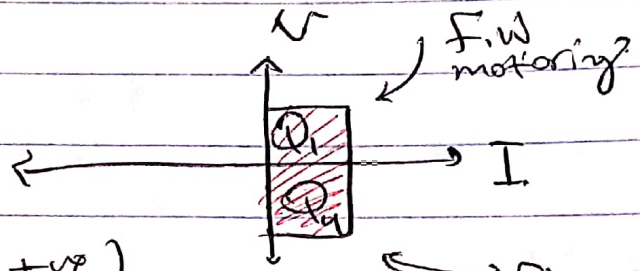


F.W motoring

Blugging
Braking

Class E chopper

* Does everything,
In sha Allah!

* (+ve and -ve I) &
(+ve and -ve v)

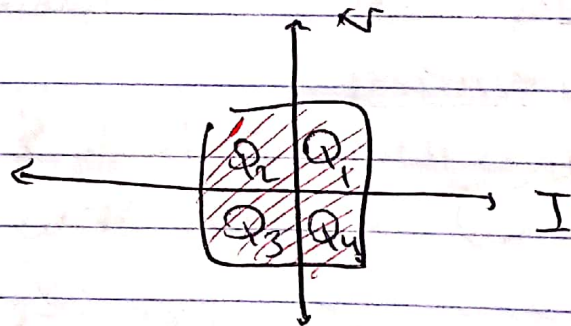


Blugging & Braking

is equivalent to Full wave rectifier when

$$\alpha > 90^\circ \quad \therefore Q_4$$

$$\alpha < 90^\circ \quad \therefore Q_1$$

ex :

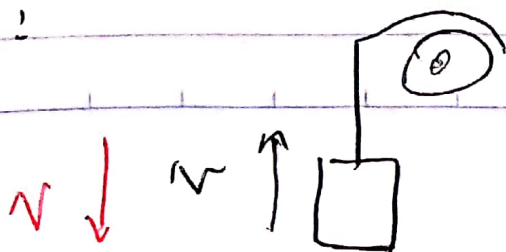


T_2 Bulk \downarrow T_1 Bulk \uparrow

Class A chopper

We use transistors, not thyristors (why?)

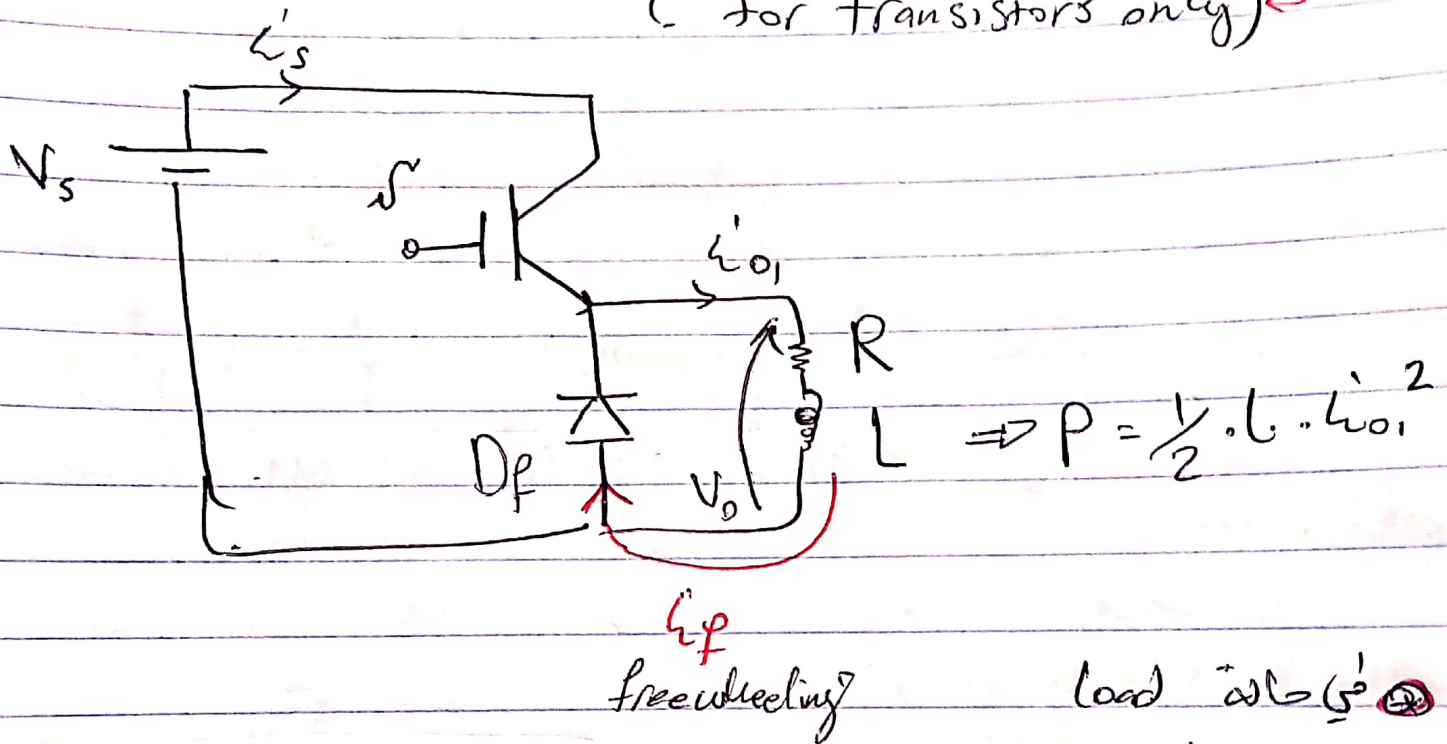- ① The input is Dc.
- ② Thyristors needs forced commutation.
- ③ we need driving circuit. (For transistors only)



freewheeling load i_o i_L
resistive load


④ D_f : Nothing to do with resistive loads.

Question in Exam: Freewheeling Diode D_f is Very Important in Dc \rightarrow Dc converters irrespective of load; The above statement is ...

\rightarrow Incorrect / wrong, since D_f is only active when the load is inductive, otherwise no current runs in it.

Control Topology


① pulse width Modulation (PWM)

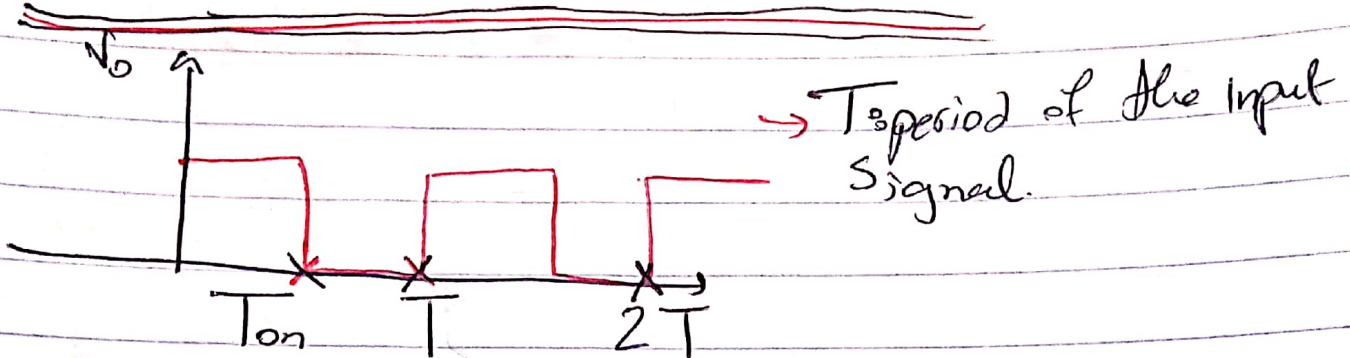

→ $f_{ch} = \frac{1}{T}$; chopping frequency or f_m (modulation)
 ↳ up to 1 MHz (10^6) ⇒ MOSFET

- * High switching frequency
- * Less harmonics
- * Small size (without current filter)

frequency / power

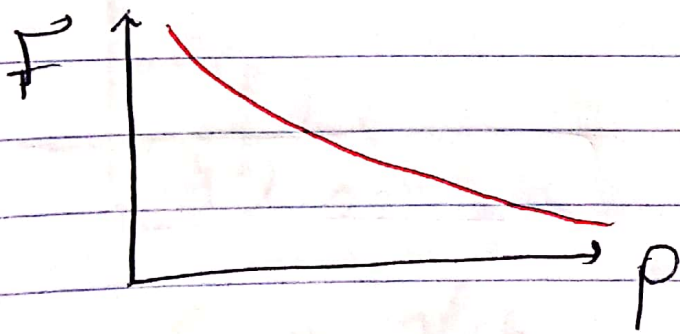

Inversely proportional
 to avoid large switching losses.



$$V_o \text{ (avg)} = \left(\frac{T_{on}}{T} \right) \cdot V_s, \quad \delta \cdot V_s.$$

δ : modulation index, $\delta \leq 1$ → $T_{on} = T$ Pure DC.
 Transistor is not active.

$$I_{(avg)} = \frac{V_{(avg)}}{R}$$


② Frequency Modulation (FM)

$$f_{ch} = \frac{1}{T}$$

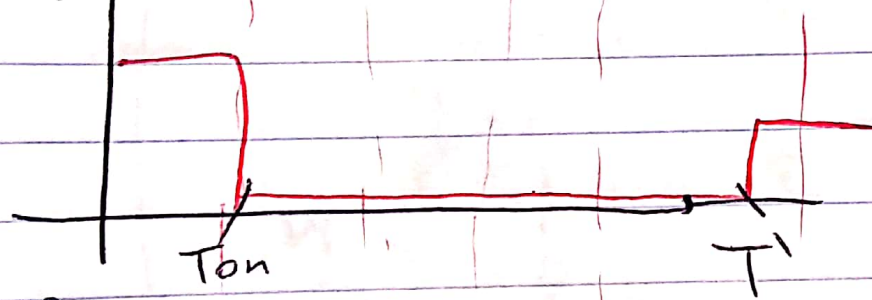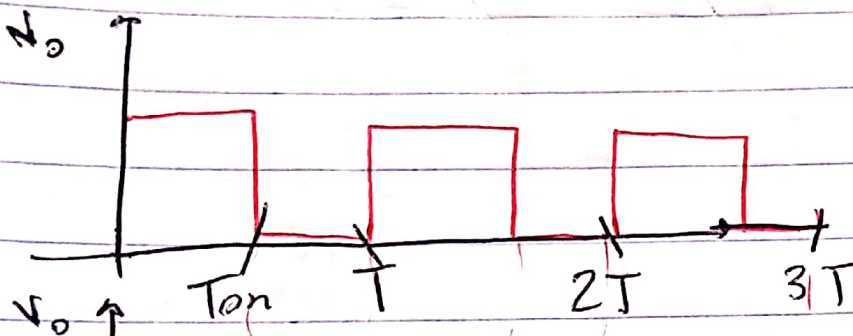

$$f_{ch}' = \frac{1}{T}$$

$$f_{ch}'' = \frac{f_{ch}}{3}$$

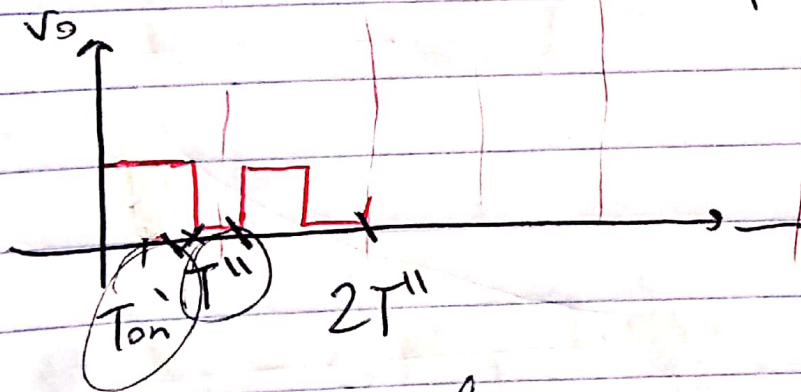

Frequency Modulation
when T_{on} is fixed.


$$f_{ch}'' = 2f_{ch}$$

Usually, PWM + FM are used Simultaneously
for advanced control.




Analysis assuming C.C.M.:-

$V_g (-20 \rightarrow +20)$

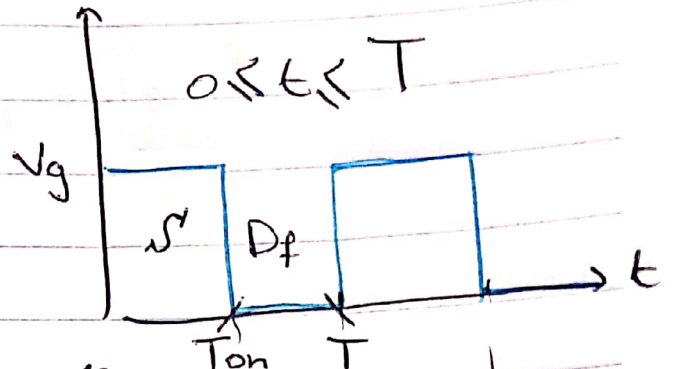$\delta = \frac{T_o}{T}, \frac{1}{f_{ch}} = T = \frac{1}{f_m}$



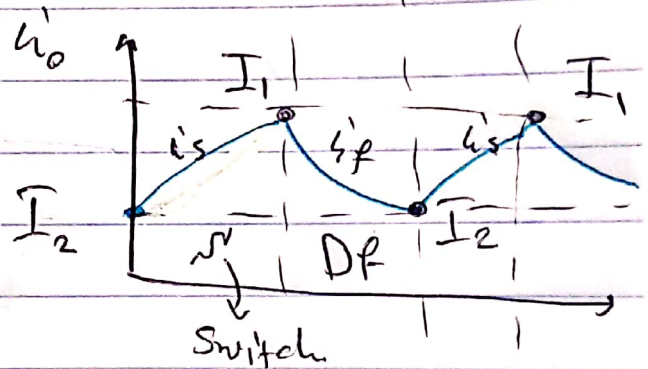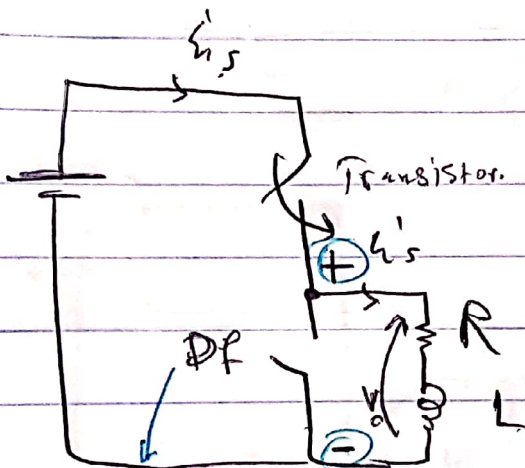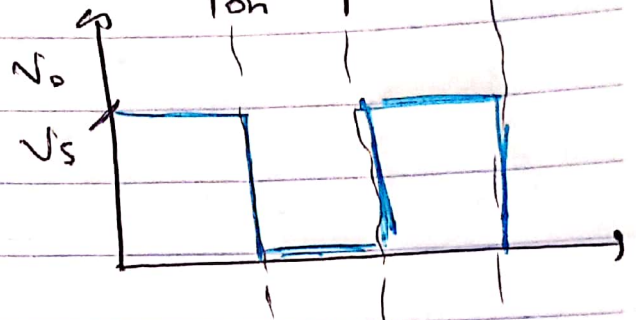$0 \leq \delta \leq 1$
 Zero output \rightarrow
 \uparrow
 Full output



open circuit
 (reversed
 biased)

$V_s = i_s R + L \frac{di_s}{dt}$

$i_s = \frac{V_s}{R} + A \cdot e^{-t/\tau}$

Steady State
 current
 (fixed)

so, $\frac{V_s}{R} = I_s$

⊗ I.C.C at $t=0$, $i_s' = I_2$

$$I_2 = I_s + A \cdot e^{-t/\tau}$$


$$A = I_2 - I_s \longrightarrow i_s' = I_s + (I_2 - I_s) \cdot e^{-t/\tau}$$

$$= I_s (1 - e^{-t/\tau}) + I_2 \cdot e^{-t/\tau}$$

⊗ F.C.C at $t = T_{on}$, $i_s' = I_1$

$$I_1 = I_s (1 - e^{-T_{on}/\tau}) + I_2 \cdot e^{-T_{on}/\tau} \quad \text{①}$$

$$T_{on} \ll t \ll T$$

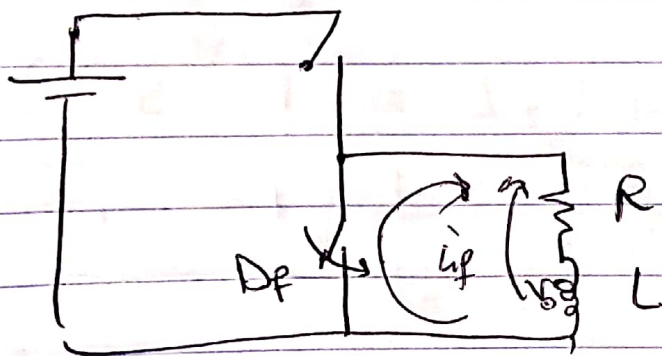

$$\Rightarrow 0 = i_L R + L \frac{di_L}{dt}$$

$$i_L = B \cdot e^{-t/\tau}$$

I.C.C at $t = T_{on} \longrightarrow i_L = I_1$

$$I_1 = B \cdot e^{-T_{on}/\tau}$$

$$\therefore i_L = (I_1 \cdot e^{T_{on}/\tau}) \cdot e^{-t/\tau}$$

$$I_1 = B \cdot e^{-T_{on}/\tau} \rightarrow B = I_1 \cdot e^{T_{on}/\tau}$$

$$\therefore i_p = (I_1 \cdot e^{T_{on}/\tau}) \cdot e^{-t/\tau}$$

F.C.C at $t = T$, $i_p = I_2$

$$I_2 = I_1 \cdot e^{T_{on}/\tau} \cdot e^{-T/\tau} \quad (2)$$

From (1) & (2) $\rightarrow I_1 = I_s (1 - e^{-T_{on}/\tau}) + I_1 e^{T_{on}/\tau} \cdot e^{-T/\tau}$

$$I_1 = I_s (1 - e^{-T_{on}/\tau}) + (I_1 e^{T_{on}/\tau} \cdot e^{-T/\tau}) \cdot e^{-T_{on}/\tau}$$

$$I_1 (1 - e^{-T/\tau}) = I_s (1 - e^{-T_{on}/\tau})$$

$$I_1 = I_s \left[\frac{1 - e^{-T_{on}/\tau}}{1 - e^{-T/\tau}} \right]$$

I_1 is always positive

$$I_2 = I_s \left[\frac{1 - e^{-T_{on}/\tau}}{1 - e^{-T/\tau}} \right] \cdot e^{T_{on}/\tau} \cdot e^{-T/\tau}$$

$$I_2 = I_s \left[\frac{1 - e^{-T_{on}/\tau}}{1 - e^{-T/\tau}} \right] \cdot \frac{e^{T_{on}/\tau}}{e^{T/\tau}}$$




$$I_2 = I_s \left[\frac{e^{T_{on}/\tau} - 1}{e^{T/\tau} - 1} \right]$$

$$I_2 = I_s \left[\frac{1 - e^{-T/\tau}}{1 - e^{-T_{on}/\tau}} \right]$$

could be +ve
or
-ve.

critical case

CCM \rightarrow DCM, $I_2 = 0$

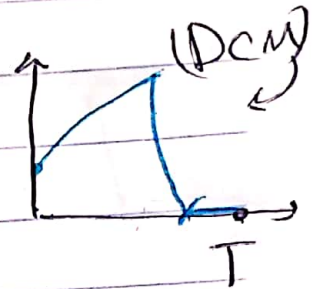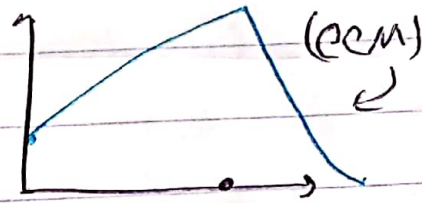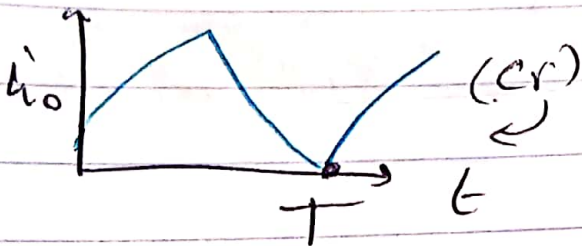

$$I_2 = I_{H(DC)} = I_s \left[\frac{1 - e^{-T/\tau}}{1 - e^{-T_{on}/\tau}} \right]$$

$$\frac{I_{H(DC)}}{I_s} (1 - e^{-T/\tau}) = 1 - e^{-T_{on}/\tau}$$

$$e^{-T_{on}/\tau} = \left[1 - \frac{I_{H(DC)}}{I_s} (1 - e^{-T/\tau}) \right]$$

$$\frac{T_{on}}{\tau} = \ln \left[1 - \frac{I_{H(DC)}}{I_s} (1 - e^{-T/\tau}) \right]$$

$$T_{on (cr)} = \tau \cdot \ln \left[1 - \frac{I_{H(DC)}}{I_s} (1 - e^{-T/\tau}) \right]$$

load time constant

exy

$\phi = 0.5$??

or $\phi = 1$??



$$\phi_{cr} = \frac{T_{on (cr)}}{T}$$

continuous or Discontinuous?

find $\phi (cr)$
 $\phi_{cr} < \phi$ CCM
 $\phi_{cr} > \phi$ DCM

DCM

$T_m = ??$

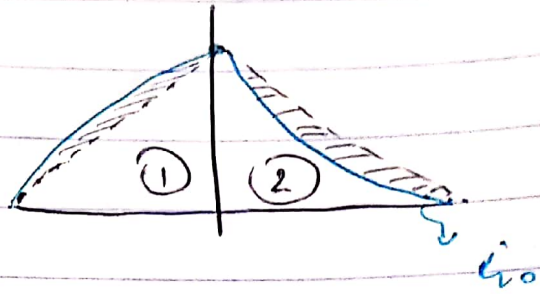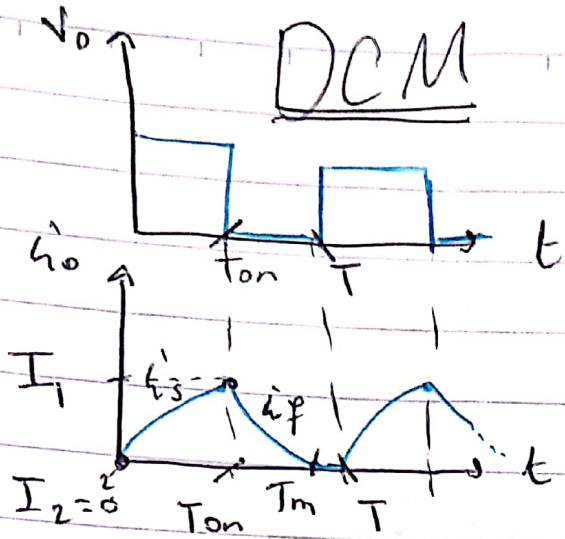

{ الزيادة في ① = التيار
في ② من كذا كذا
في ③ كذا كذا }

$i_p \rightarrow I_H$ at $t = T_m$

$$i_s = I_s + A \cdot e^{-t/\tau}, \quad t=0 \rightarrow \boxed{i_s = 0}$$

$$0 = I_s + A \rightarrow A = -I_s$$

$$i_s = I_s - I_s e^{-t/\tau} = I_s [1 - e^{-t/\tau}]$$

$$i_p = B \cdot e^{-t/\tau}$$

F.C.C. at $T = T_{on}$, $\boxed{i_s = I_2}$

$$I_1 = I_s (1 - e^{-T_{on}/\tau})$$

$$i_p = B \cdot e^{-t/\tau}$$

I.C.C. at T_{on} , $\boxed{i_p = I_1}$

$$I_1 = B \cdot e^{-T_{on}/\tau} \rightarrow B = I_1 \cdot e^{T_{on}/\tau}$$

$$i_p = I_1 \cdot e^{T_{on}/\tau} \cdot e^{-t/\tau}$$

$$t = T_m \rightarrow \frac{1}{2} p = I_H$$

$$I_H = I_1 \cdot e^{\frac{T_{on}}{\tau}} \cdot e^{-\frac{T_m}{\tau}}$$

$$e^{-\frac{T_m}{\tau}} = \frac{I_H}{I_1} \cdot e^{-\frac{T_{on}}{\tau}}$$

$$-\frac{T_m}{\tau} = \ln \left(\frac{I_H \cdot e^{\frac{T_{on}}{\tau}}}{I_1 (DCM)} \right)$$

$$T_m = -\tau \cdot \ln \left[\frac{I_H \cdot e^{\frac{T_{on}}{\tau}}}{I_1 (DCM)} \right]$$

$$\bullet V_o \text{ (avg)} = \frac{1}{T} \int_0^{T_{on}} v_s \cdot dt \Rightarrow \boxed{\delta \cdot v_s = V_o \text{ (avg)}}$$

$$\bullet V_o \text{ (rms)} = \sqrt{\frac{1}{T} \int_0^{T_{on}} v_s^2 \cdot dt} \Rightarrow V_o \text{ (rms)} = \sqrt{\delta} \cdot v_s$$

$$\bullet RF = \frac{\sqrt{\delta v_s^2 - \delta^2 v_s^2}}{\delta \cdot v_s} \Rightarrow RF = \sqrt{\frac{1}{\delta} - 1}$$

Voltage Harmonics $\phi(n) = \frac{\pi}{2} - n\pi\delta$

$$\rightarrow A(n) = \frac{2}{T} \int_0^{T_{on}} v_s \cdot \cos n\omega t \cdot dt = \frac{2v_s}{T} \cdot \frac{1}{n\omega} \sin(n\omega t) \Big|_0^{T_{on}}$$

$$\rightarrow B(n) = \frac{2}{T} \int_0^{T_{on}} v_s \cdot \sin n\omega t \cdot dt \dots$$

$$\rightarrow C(n) = \frac{2v_s}{n\pi} \cdot \sin(n\pi\delta) \dots$$

ex: $\delta = 1$, fundamental $\rightarrow 0$
 $\delta = 0.5$, fundamental $\rightarrow \text{MAX}$.

The previous $A(n)$, $B(n)$, $C(n)$ Equations are for both \rightarrow OCM & PCM.



- $I_{avg} = \frac{V_{avg}}{R}$

- $f_{ch} \uparrow \rightarrow$ Harmonics \downarrow

- $L \uparrow \rightarrow$ Harmonics \downarrow


Chopper's disadvantages \rightarrow more switching losses.

Inverters

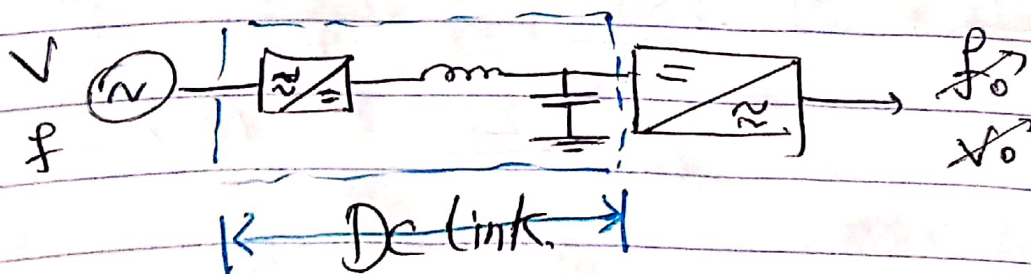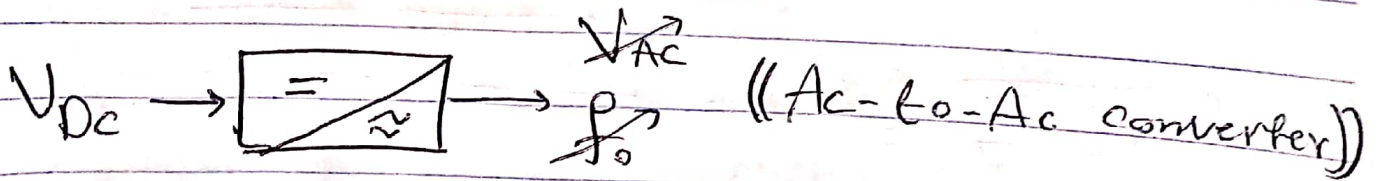


- The Best switching elements are Transistors. To avoid forced commutation of SCR's.
- Transistors + fast recovery Diodes.

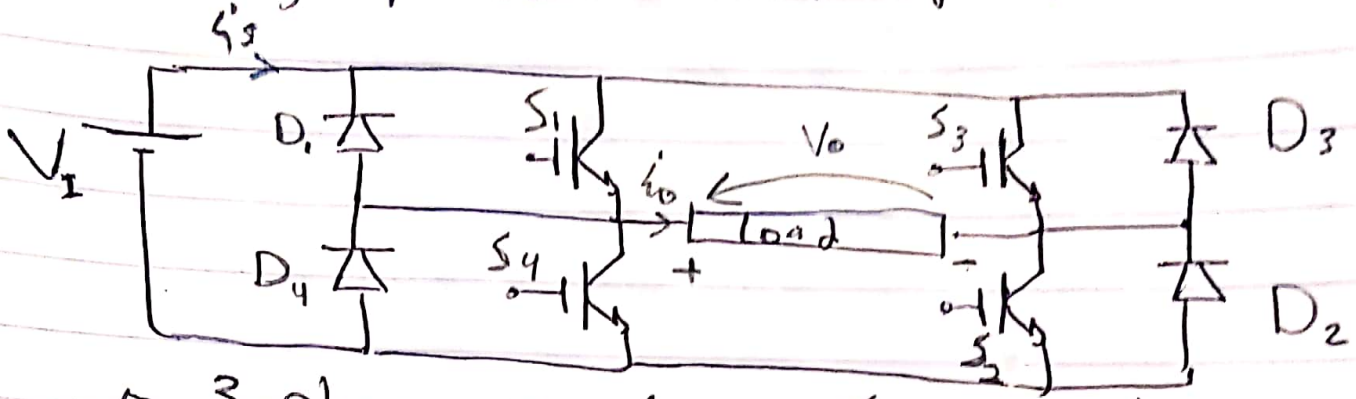• Single phase - Inverter (power circuit).



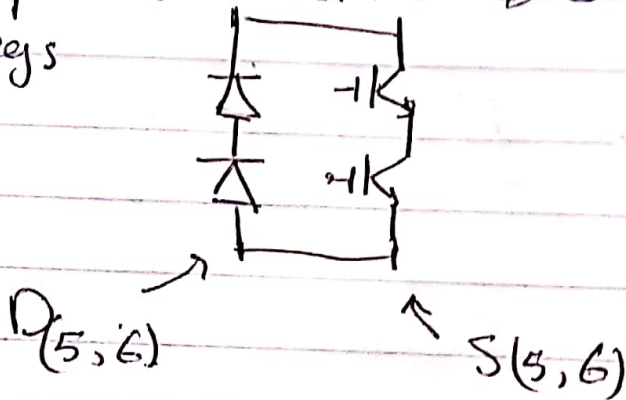⇒ 3-phase - Inverter ⇒ Same + two new legs





Control Topology

① Square-wave Inverter


$f_o = \frac{1}{T}$

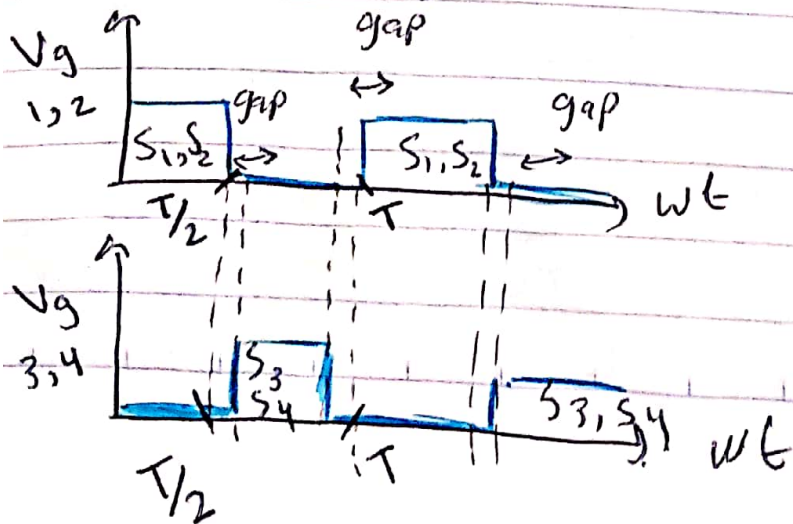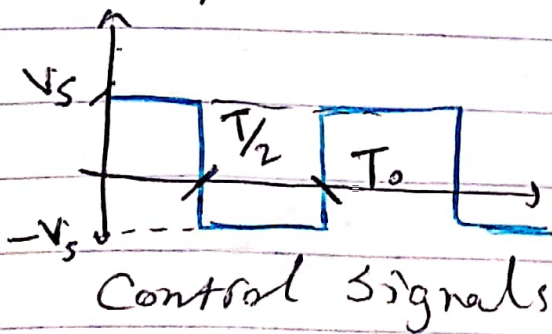⇒ Control T by a microcontroller to obtain the required frequency.



• We keep a gap (delay) to prevent short circuiting the 4-transistors when over-lapping


29/12/2019

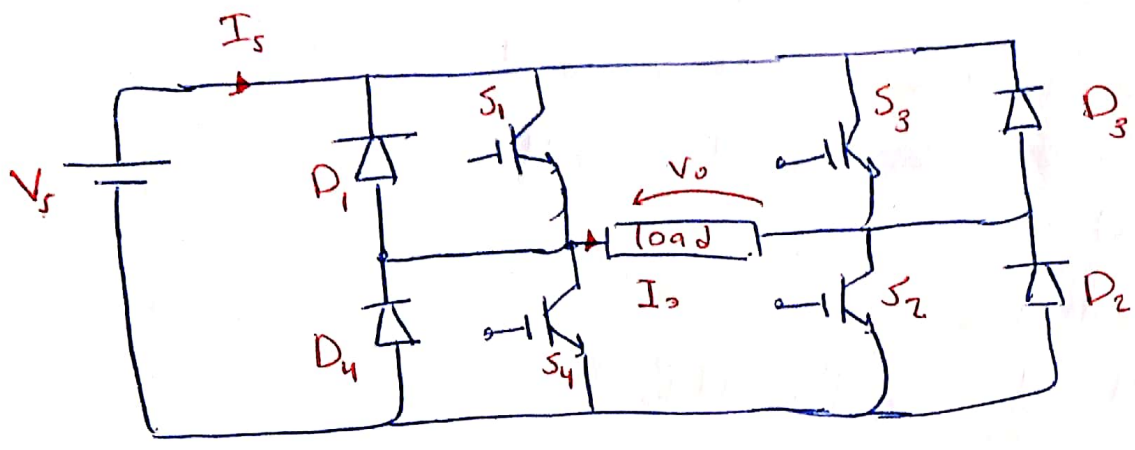


Control topology

① Square-wave

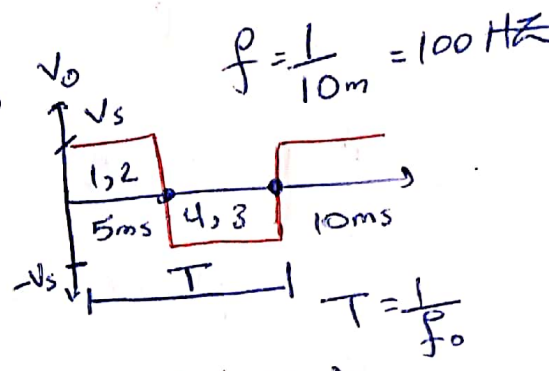- f_o controlled by selection of switching times of the inverter switches
- V_o controlled by V_s , Dc link with controlled rectifier



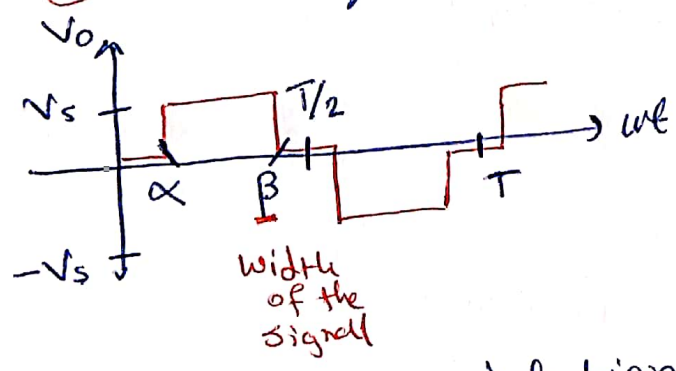
② Quasi-Square-wave (single pulse-width modulation)



- V_o controlled by the inverter switching action

③ Pulse width modulation (PWM) → Sinusoidal PWM
→ Uniform PWM.

④ Uniform PWM

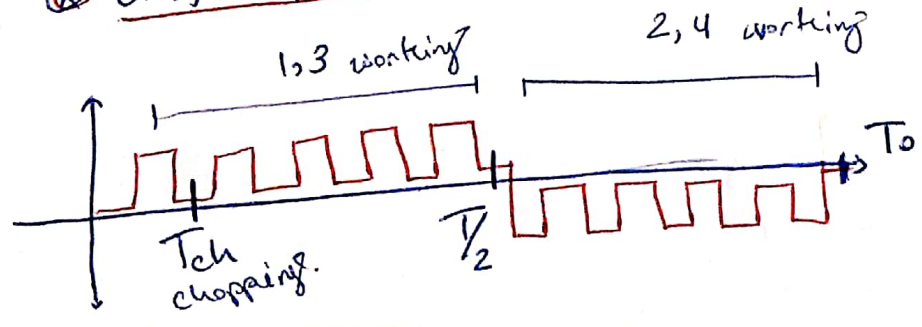

$$4\text{PWM}, f_{ch} = \frac{1}{T_{ch}}$$

$$f_o = f(f_{ch})$$

① Number of pulses per half cycle N .

② Number of pulses per full cycle M .

$$M = 2N$$

$$T_o = M \times T_{ch}$$

$$\frac{1}{f_{ch}} \times M = \frac{1}{f_o} \Rightarrow f_{ch} = M f_o$$

$$= 2N f_o$$

Question in Exam


→ Pulse width modulation Technique, $f_{ch} = \dots$ Hz, pulse # = \dots No.
 Find power frequency $f_o = ??$

(ex) Microcontroller:-


$f_{ch} = 5000$ Hz, $f_o = 100$ Hz \rightarrow find # of pulses, $\frac{5000}{100} = 5$ pulses
 each half cycle = 25 pulses

\rightarrow is $10\text{ms} = \frac{1}{100} \rightarrow$ each pulse $\frac{10\text{ms}}{25} =$ time for
 each pulse.....

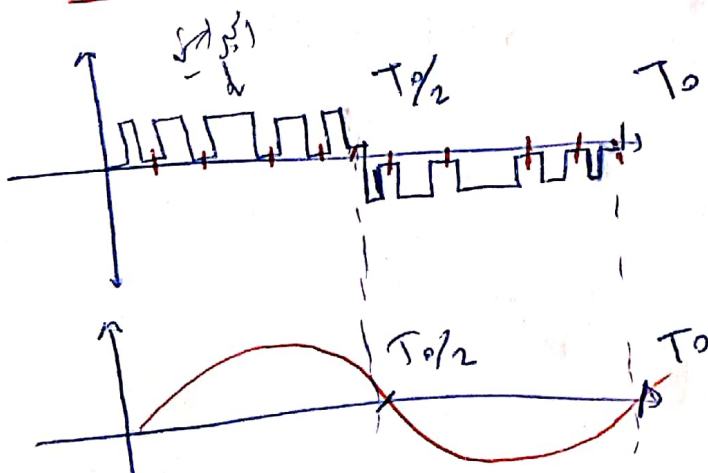⊗ Sinusoidal PWM : for better performance.




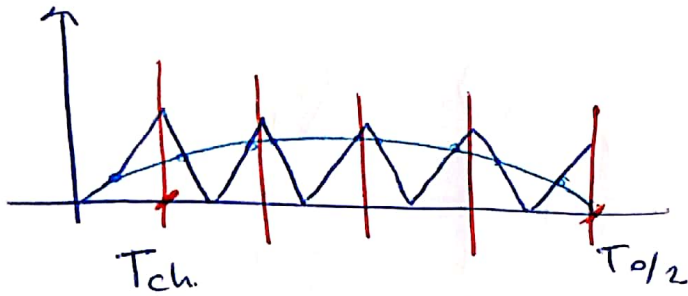③ in microcontroller I generate triangular signal then we get Dc modulation signal and compare it :-



④ Multilevel Voltage Source Inverter :-

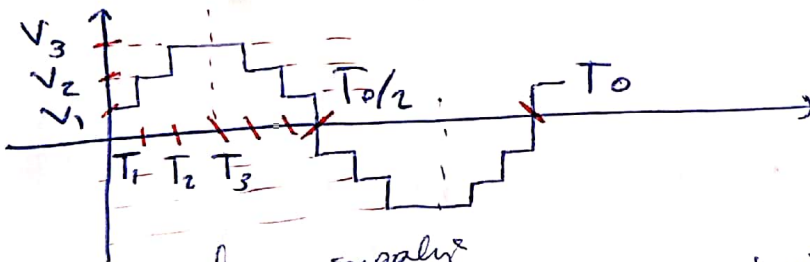→ complex in design & more expensive but
Great performance.



fundamental supply
 $V(1) = 240 \text{ RMS}$

$$V(3) = 0$$


$$V(5) = 0$$

$$V(7) = 0$$




} → sitting in
computer to generate
equations.

31/12/2019

Lecture 40

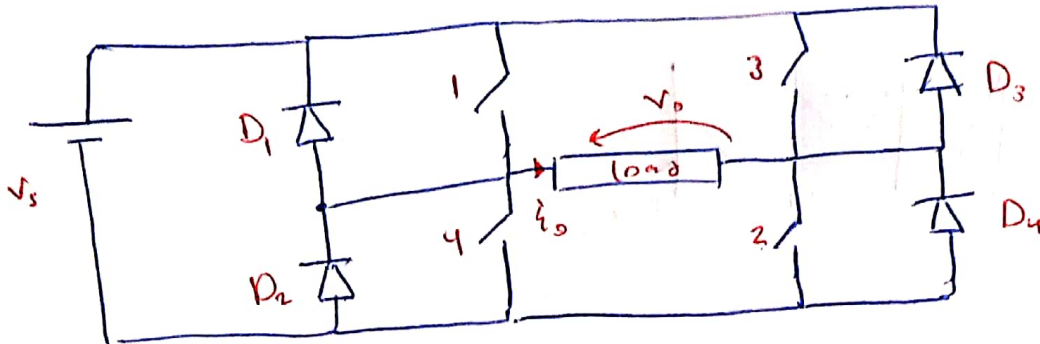

Square-Wave Inverter

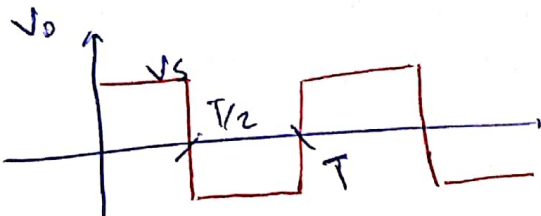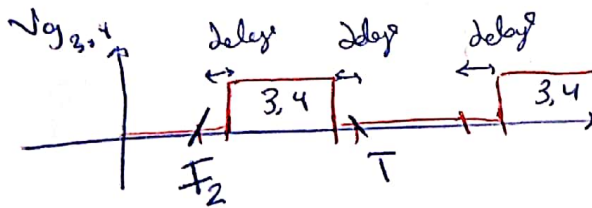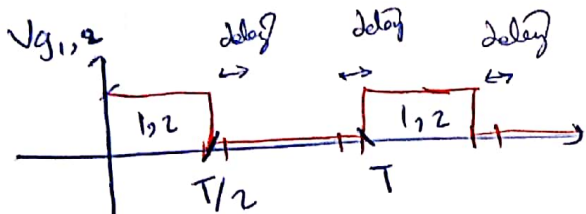


T is decided by f_0

(ex) $500 \text{ Hz} = f_0$

$$T = \frac{1}{500} = 2 \text{ msec}$$

→ each switch will work for 1 msec.


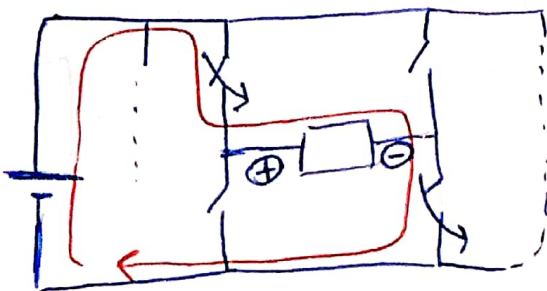
When SCR₁ & SCR₂ are on, $V_s = i_o R + L \frac{di_o}{dt} \Rightarrow \omega_s \omega_c$ (chopper)



$$0 \leq t \leq T/2$$

In the second cycle

في دورة الثانية *

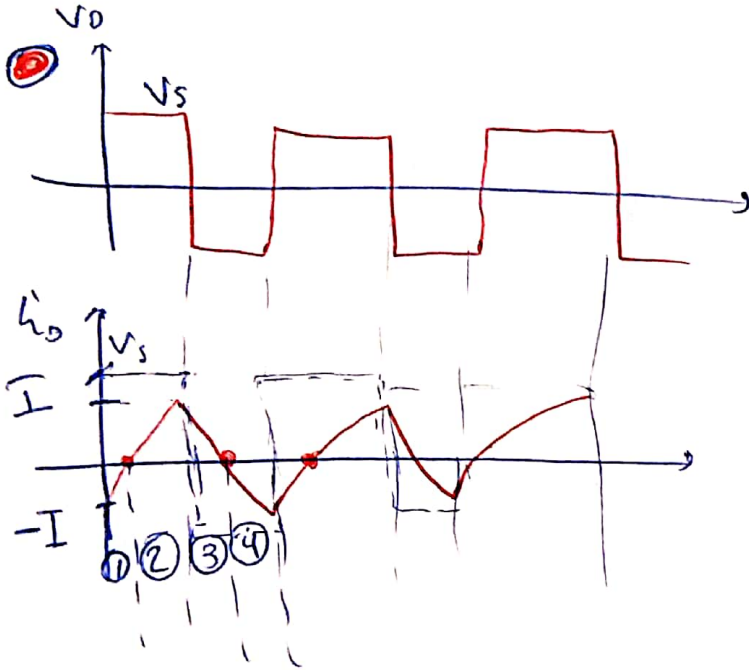
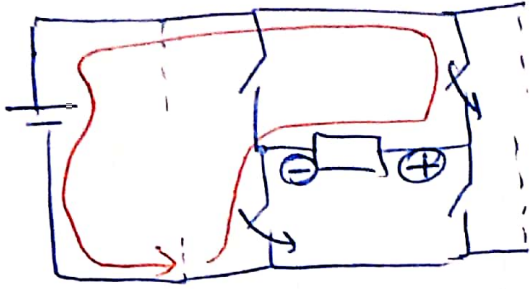


- (F.B)
- ①: D_1 & D_2 , V_o^+ , I_o^-
 - ②: S_1 , S_2 , V_o^+ , I_o^+
 - ③: V_o^- , I_o^+ , D_3 & D_4 (F.B)
 - ④: S_3 , S_4 , V_o^- , I_o^-

• Power $\equiv \frac{1}{2} I^2 L$ يترجع
 Feedback الى Supply الى Diodes.

Question in the Exam: In Square-wave Inverters, Diodes are used for feedback or free wheeling? (A) feedback.

To Force Zero Voltage:

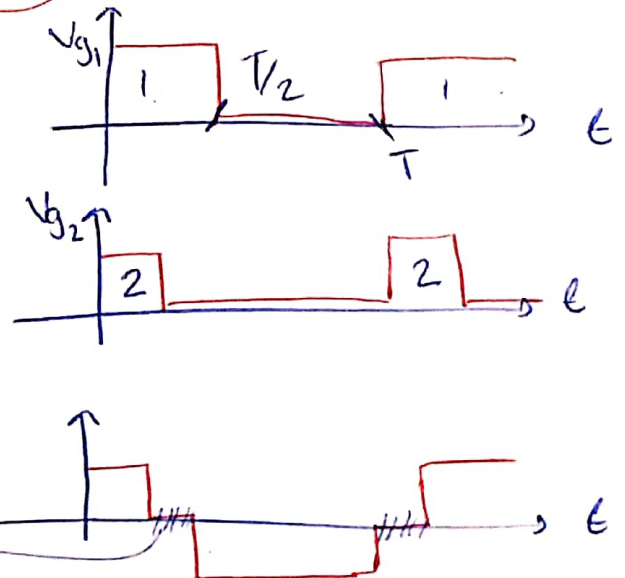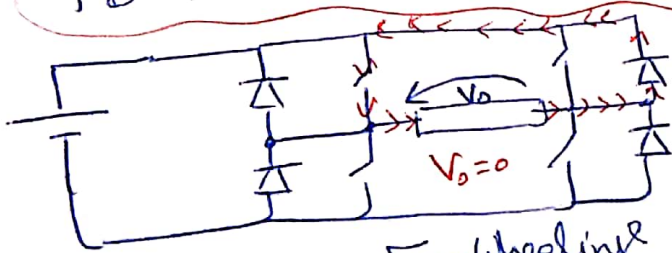

• in PWM Techniques (including quasi-square-wave)

⇒ $D_1 \rightarrow D_4 \rightarrow$ Free Wheeling / Feed back Diodes
(work as both F.B & F.W!)

2/1/2020

Lecture 41

3-ph Rectifier (Questions in Exam)

ex) Waveform construction (V_o, I_s)
given $\alpha \rightarrow$ SCR 4 triggered at 45°

$$1 \rightarrow \alpha + 30 = 75$$

$$2 \rightarrow 135$$

$120^\circ, \dots$

ex) given $\omega t = 240$ SCR₃ triggered at $\alpha = ??$

$$3 \rightarrow 240$$

$$\downarrow$$
$$2 \rightarrow 180$$

$$\downarrow$$
$$1 \rightarrow 120 \rightsquigarrow 120 = \alpha + 30, \alpha = 90^\circ$$

ex) $V_s = \sqrt{L} / V_{ph}$, 3ph-supply, given $\alpha \rightarrow$ find :-
380/220

$RF_{vo}, i_o, PF_{in} = ??$

Q) 3ph Rectifier, $V_{ph} = 220V, V_L = 380V, f = 50Hz$

$R_L = 10\Omega, RF_{vo} = ??, PF_{in} = ??$ at $\alpha = 0$
 $\alpha = 30^\circ \rightarrow CCM$

Sol) $\alpha = 30^\circ \quad \alpha < \alpha_{cr} \rightarrow CCM. \quad \alpha = 90^\circ \rightarrow DCM$

$$V_o (avg) = \frac{3\sqrt{3} V_m \cos \alpha}{\pi} = \frac{3 \times \sqrt{3} \times \sqrt{2} \times 220}{\pi} \cos(30^\circ)$$

$$V_o (avg) = 445.656V$$

$$\underline{V_o (rms)} = \sqrt{\frac{1}{2\pi/6} \int_{\alpha+\pi/6}^{\alpha+\pi/2} [\sqrt{3} \cdot V_m \sin(\omega t + \pi/6)]^2 dt}$$

X Don't Do This!!
Jokes time ...

$$V_o(\text{rms}) = 3V_m \left[\frac{1}{6} + \frac{\sqrt{3}}{4\pi} \cos 2\alpha \right]^{1/2} \#$$

$$\Rightarrow V_o(\text{rms}) = 453.034 \text{ V} > V_o(\text{avg})$$

$$R_F = \sqrt{V_{\text{rms}}^2 - V_{\text{avg}}^2} = 18.27 \%$$

$$PF_{\text{in}} = \frac{P_{\text{in}}(\text{W})}{\sqrt{S_{\text{in}}(\text{VA})}} = \frac{P_o(\text{W})}{\sqrt{S_{\text{in}}(\text{VA})}} \leftarrow \begin{matrix} \text{no. of} \\ \text{Losses.} \end{matrix}$$

$$P_o(\text{W}) = I_o(\text{rms})^2 * R \rightarrow \text{given.}$$

$$I_o(\text{rms}) = \frac{V_o(\text{avg})}{R} \Rightarrow \text{only for resistive loads}$$

$$I_o(\text{avg}) = \frac{V_o(\text{avg})}{R}$$

$$\sqrt{S_{\text{in}}(\text{VA})} = 3V_{S(\text{ph})} * I_{S(\text{ph})}$$

$$3 * 220 * \dots$$

$$I_{S(\text{ph})} = \sqrt{\frac{240^2}{360}} + I_o(\text{rms})$$

$$= \sqrt{\frac{2}{3}} + I_o(\text{rms})$$

$$I_{S(\text{avg})} = ?? \rightsquigarrow \text{Zero } \& \text{ the } \alpha \text{ is } \text{ve}$$

$$I_o(\text{rms}) = 45.3034 \text{ A}$$

$$I_{S(\text{rms})} = 36.99 \text{ A}$$

$$P_{\text{in}} = P_o = 20524 \text{ W}$$

$$\sqrt{S_{\text{in}}} = 24413.4 \text{ VA}$$

$$PF = 0.8407 \text{ lag}$$

→ when $\alpha = 90^\circ$

$\alpha > 60^\circ \rightarrow$ DCM.

$$V_o(\text{avg}) = \frac{3\sqrt{3}V_m}{\pi} (1 + \cos(\alpha + \pi/3))$$

$$V_o(\text{avg}) = 68.94 \text{ V}$$

$$V_o(\text{rms}) = 3V_m \left[\frac{1}{3} - \frac{\alpha}{2\pi} + \frac{1}{4\pi} \sin(2\alpha + \frac{2\pi}{2}) \right]^{1/2}$$

must be in radians! $\frac{\pi}{180}$

$$V_o(\text{rms}) = 112.07 \text{ V}$$

$$RF_{V_o} = 128.16\%$$

$$I_s(\text{rms}) = 9.1507 \text{ A}$$

$$PF_{in} = 0.208 \text{ lag}$$

OK!

PIV in 3-ph rectifiers = $\sqrt{3} V_m$
Peak inverse voltage

PIV, Single phase - half wave = V_m

PIV, Single phase - full wave $\left\{ \begin{array}{l} \text{Bridge} = V_m \\ \text{Center tapped} = 2V_m \end{array} \right.$

$$\text{Voltage rating} = \text{PIV} * (2-3)$$

min
max

PIV

2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 21, 22, 23, 24, 25, 26, 27, 28, 29, 30, 31, 32, 33, 34, 35, 36, 37, 38, 39, 40, 41, 42, 43, 44, 45, 46, 47, 48, 49, 50, 51, 52, 53, 54, 55, 56, 57, 58, 59, 60, 61, 62, 63, 64, 65, 66, 67, 68, 69, 70, 71, 72, 73, 74, 75, 76, 77, 78, 79, 80, 81, 82, 83, 84, 85, 86, 87, 88, 89, 90, 91, 92, 93, 94, 95, 96, 97, 98, 99, 100

Single ph - Rectifier

① R-L-load \rightsquigarrow critical case:-

$$\boxed{\alpha = \phi}$$

② $\alpha \neq \phi \rightarrow \phi = 60, \alpha = 30 \rightsquigarrow$ Find $R, V_o = ??$

$$Z = 10 + j10 \Omega \rightsquigarrow \text{(rectangular form)}$$

$$\text{or } R = \text{--- and } X = \text{---}$$

$$\text{or } Z = 10\sqrt{2} \angle 45^\circ \Omega \text{ (polar form)}$$


CCM :- $\phi = \tan^{-1}\left(\frac{X}{R}\right)$

$$- V_o = \frac{2V_m}{\pi} \cos(\alpha)$$

$$- V_{rms} = V_s (rms) = \frac{V_m}{\sqrt{2}}$$

$$- R_F V_o = \frac{\sqrt{V_o^2 - V_{avg}^2}}{V_{avg}}$$

$$- I_o (avg) = ?? \rightarrow \frac{V_o (avg)}{R}$$

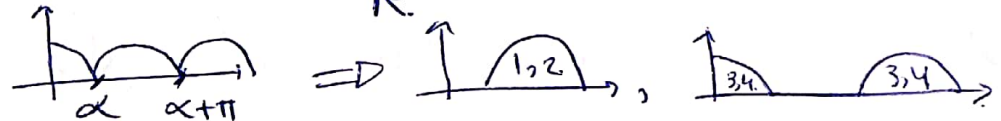- critical \Rightarrow 

$$\begin{cases} I_{avg}(SCR) = \frac{1}{2} I_{(avg)} \\ I_{rms}(SCR) = \frac{I_o (rms)}{\sqrt{2}} \\ I_{peak}(SCR) = I_m = \frac{V_m}{2} \end{cases}$$

\Leftarrow Current ratings of SCR.

\rightsquigarrow choose Peak, (\rightarrow hold)



What is the (avg) of the SCR (Question in Exam \rightarrow)

ans \rightarrow (Load avg / 2)

\rightsquigarrow Rms?? (Load RMS / 2)

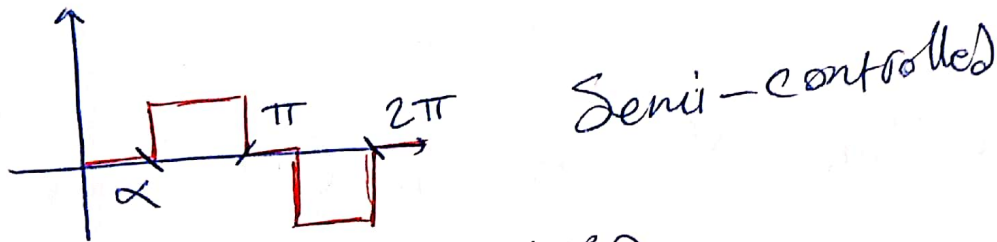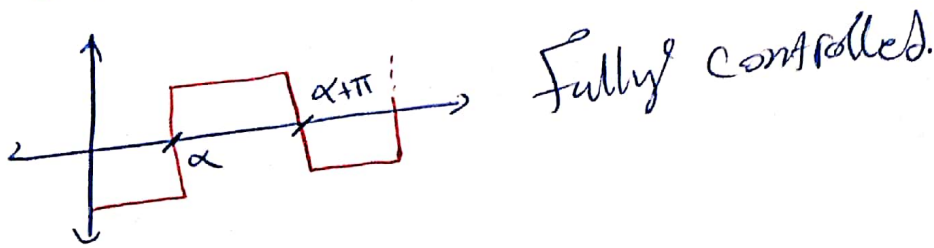Questions can also be:

- R-L-E, L so large such that I_o is ripple free. -




• IN FULLY CONTROLLED:

$R_{FI} = \text{Zero}$, $V_s = \sum_{1,3,5,\dots} \frac{4I_o}{n\pi} \sin(n\omega t - n\alpha)$ $\psi = n\alpha$
 has harmonics \rightarrow peak value.

$\rightarrow I_1(\text{rms}) = \frac{4I_o}{\pi\sqrt{2}}$ (fundamental)

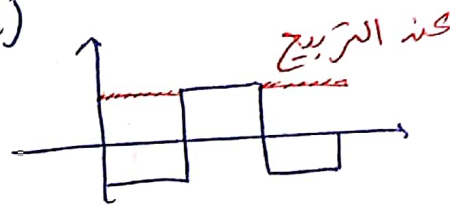$I_s(\text{rms}) = I_o = I_o(\text{rms})$



• IN SEMI-CONTROLLED:

$I_s(\text{rms}) = I_o(\text{rms}) * \sqrt{\frac{180 - \alpha}{180}}$

α in degrees or 180 by π less radians.


$V_s = \sum_{1,3,5,\dots} \frac{4I_o}{n\pi} \cos\left(\frac{n\alpha}{2}\right) \sin\left(n\omega t - \frac{n\alpha}{2}\right)$

Question in the Exam Find:


R_{FI} , PF_{in} , THDF = ?? then add a freewheeling diode \rightarrow connected to the load
 Recalculate them then compare the results.

\rightarrow Draw α vs. $V_o(\text{avg})$ for the previous two cases \rightarrow

Case 1)) Fully controlled rectifier, $V_o(\text{avg}) = \frac{2V_m}{\pi} \cos \alpha$

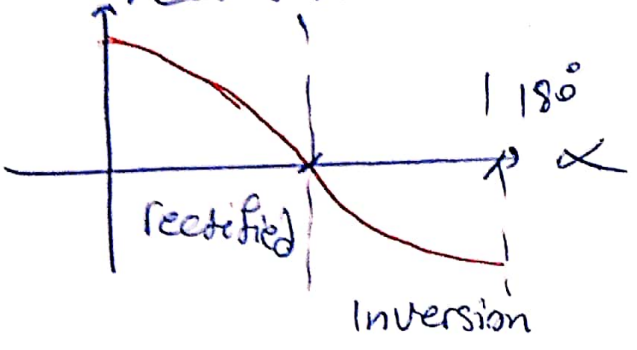

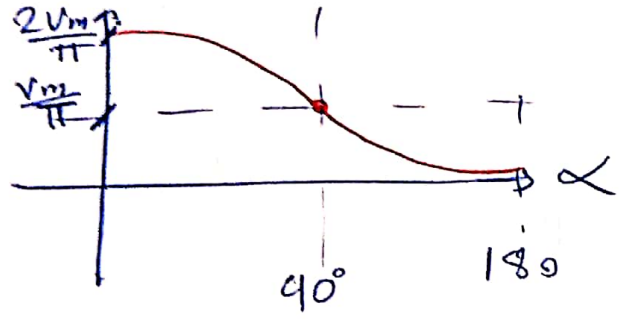
Case 2)) Semi-controlled rectifier, $V_o(\text{avg}) = \frac{V_m}{\pi} (1 + \cos \alpha)$



another Question: Semi-controlled R-L-Load, is it CCM or DCM??
 $\rightarrow I_1$ & I_2 for CCM & DCM, you should know them
 $I_1 > 0 \rightarrow$ CCM, $I_1 < 0 \rightarrow$ DCM.

Choppers

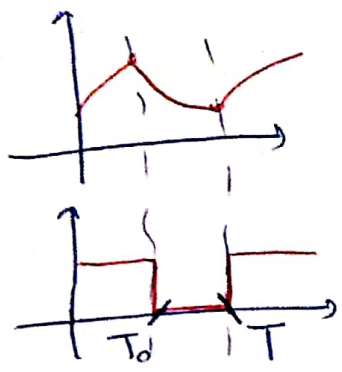R-L-load, $f_{ch} (f_m)$, $V_s (DC)$, δ given, or, $V_o(\text{avg})$
 \rightarrow Find $RfV_o = ??$ CCM/DCM = ??




$\delta = T_0/T$, $\delta_{cr} = ??$ you must find it
 $\delta_{cr} < \delta \Rightarrow$ CCM.
 $\delta_{cr} > \delta \Rightarrow$ DCM.

$$V_o(\text{avg}) = \delta \cdot V_s$$

$$V_o(\text{rms}) = \sqrt{\delta} \cdot V_s$$

$I_1, I_2 \rightarrow$ Sketch to scale

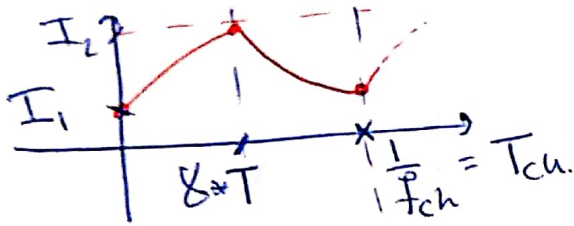

$$R_F i_o = ??$$

Harmonics \rightarrow as ω increases
 (line) \rightarrow ω period \rightarrow $\frac{1}{f}$ \rightarrow ω

$$i_o = I_o(\text{avg}) + \sum_{n=1,2,3,\dots} \frac{2V_s}{n\pi} \cdot \sin(2\pi n \delta) \sin(n\omega t - \frac{\pi}{2} + n\pi \delta)$$

$$\psi(n) = \frac{\pi}{2} - n\pi \delta$$

if $n=1$, find i_o or $n \rightarrow 3$ ----


$$1^{\text{st}} \text{ RMS value} \rightsquigarrow \frac{2V_s}{\pi\sqrt{2}} = I_1(\text{rms})$$

$$2^{\text{nd}} \text{ RMS value} \rightsquigarrow \frac{2V_s}{2\pi\sqrt{2}}$$

$$V_o = V_o(\text{avg}) + \sum_{n=1,2,3,\dots} \frac{2V_s}{n\pi} \cdot \sin(2\pi n \delta) \sin(n\omega t - \frac{\pi}{2} + n\pi \delta)$$

INVERTER

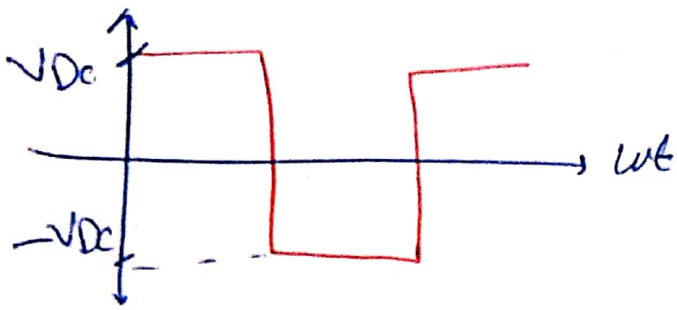- Questions:
- Power circuit - PWM, F_m & f_o relations.
 - typical waveforms
 - conduction pattern: where SCR 1, 2, 3, ... &
 - control signal ? \rightarrow $D_{1,2,3,\dots}$




$$V_0 = \begin{cases} +V_{DC}, & 0 \leq \omega t \leq 180^\circ \\ -V_{DC}, & 180^\circ \leq \omega t \leq 360^\circ \end{cases}$$

$$V_0(t)_{(avg)} = \sum_{n=1,3,5,\dots} \frac{4V_{DC}}{n\pi} \sin(n\omega t)$$

$$\psi(n) = 0$$

$$i_0(t) = \sum_{n=1,3,5,\dots} \frac{4V_{DC}}{n\pi Z(n)} \sin(n\omega t)$$


$$V_0(rms) = V_{DC}$$

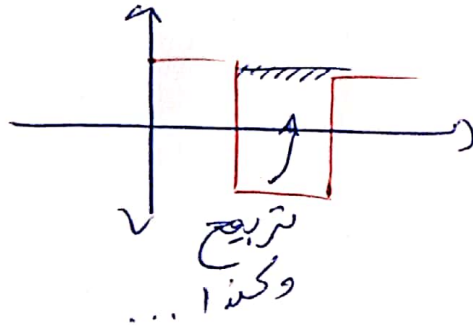

Q) Find V_{DC} such that $V_{0_1}(rms) = 240V$??
Fundamental \rightarrow ω

$$V_{0_1}(rms) = \frac{4V_{DC}}{\pi\sqrt{2}} \Rightarrow 240 = \frac{4V_{DC}}{\pi\sqrt{2}}, \quad V_{DC} = ??$$

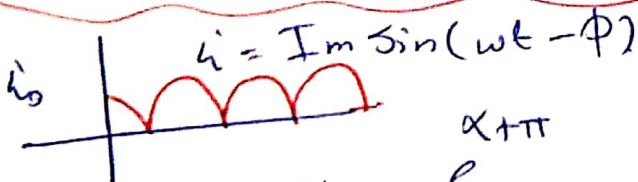Homework: كان لا يمكن من تحديد الزمان ω (أحد) \rightarrow C.R. case:-



$$R_{F_{i_0}} = ??, \quad I_0(rms) = \frac{I_m}{\sqrt{2}}, \quad I_0(avg) = \frac{2I_m}{\pi}$$

$$A(n) = \frac{4}{2\pi} \int_{\alpha}^{\alpha+\pi} I_m \sin(\omega t - \phi) \cos(n\omega t) dt$$

يحول \rightarrow $\sin(X) \cdot \cos(Y)$

$$= \frac{1}{2} \left[\dots \right]$$