

Electrical Drive

(electrical machines drive)

Involved: ① Electrical machines

- DC motors (precise control), have more features than AC
- AC motors (inspecific: induction motor)


up to 90% of the market of DRIVE.

↳ very hard to control.

Series Compound Shunt

HINT: adding a resistor (R_m) to rotor would: ① reduce the starting current (I_{st})

② increase the starting Torque (T_{st})

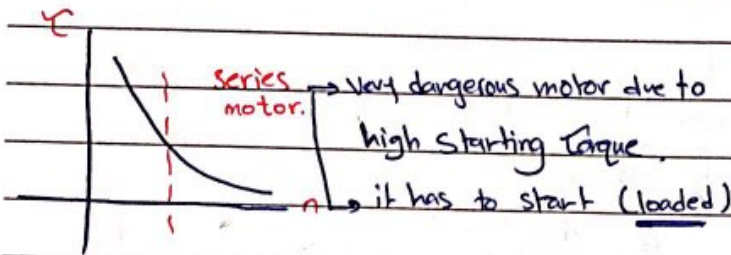


• Spark in commutation circuit:
brush + commutator
Produce sparks because of current break down.
(armature reaction)

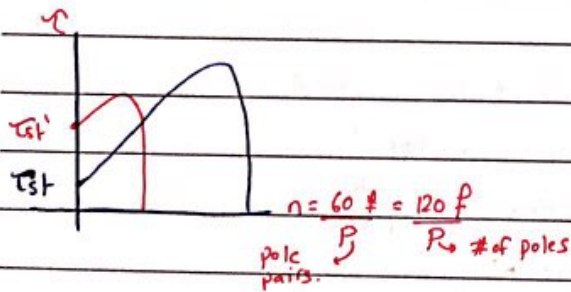Question to wonder !!

Why is low frequency (500 Hz) is enough in power applications??

For the speed of the mechanical machine to be able to tolerate, it will add up to 10 times.




• vuvf: variable voltage, variable frequency.

② Power electronics (Power conditioning)

* DC machines are controlled through M-G set

↳ DC motor + synchronous generator.

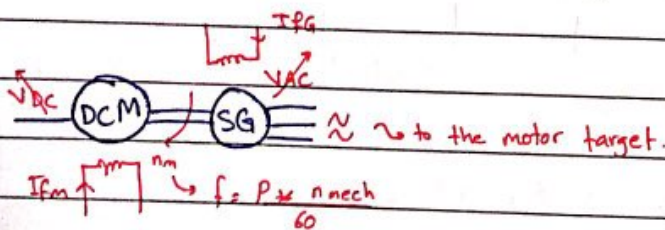

* Speed is controlled from the Prime mover.

$$E_{mf} = 4.44 k \cdot W \times \phi \cdot f \cdot N$$

↳ related to I_{fg}

* Problems of power electronics:

- ① Harmonics.
- ② PF reduction
- ③ Torque pulsation.
- ④ over heating.

$$I_{rms} = \sqrt{I_{av}^2 + I_{harmonics}^2}$$

↳ high value means more losses ($I^2 \times R$)

ie → 20% higher I_{rms} → 44% over heating.

* over-heating is fatal to electrical machines.

* Insulation classes (A, B, C, ... F) ^{155°C}
 ↳ doesn't get deteriorated.

• Most important features in a motor ^{Power}
^{frequency}
^{voltage}
^{speed}
 ↳ Insulation class → heat v. imp

Tuesday 24/9/2019


* Basic Drive system features:

- ① controller
- ② converter
- ③ Motor
- ④ Mechanical load

↳ feedback to control

at least one PE

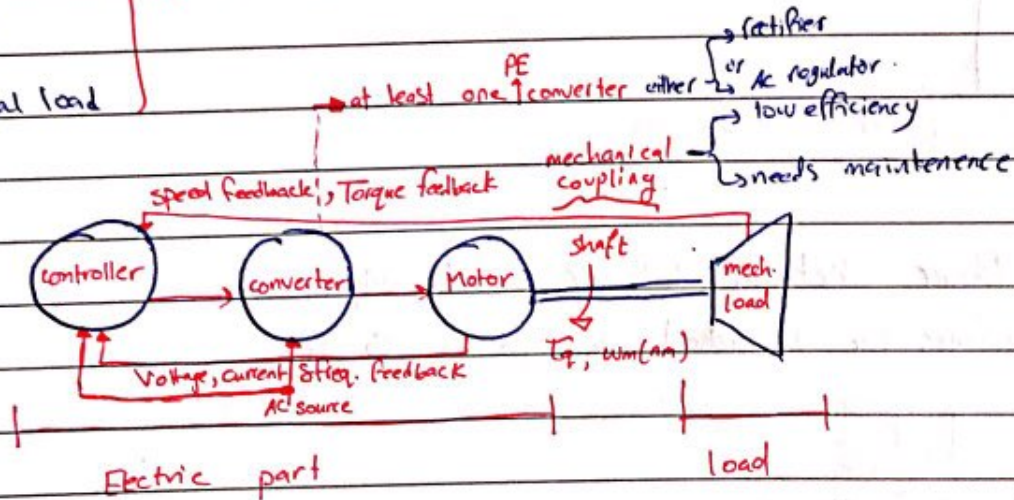converter either ^{rectifier} or AC regulator.
 ↳ low efficiency
 ↳ needs maintenance



what goes from the controller to the converter is pure power electronics.

• Controller

Electronic circuitries (from basic diode to micro-controller)

ex: Triggering circuit of SCRs

Drive circuit of Power transistors.

• Trigger → pulse & then the signal vanishes & the thyristor is still ON.
 • Drive → Signal must remain to keep the transistor ON.

• Converter: (piece of equipment which does electric power conditioning)

Power conditioning: (shape (Wave), Amplitude (average for DC, RMS, Fundamental), Frequency)

- Rectifiers
- choppers
- Inverters.
- AC regulators.

• Motor

→ DC Motors (recently limited for precise control applications & certain loading conditions). 10%

→ AC Motors (90% of Drive systems & mainly induction motors & rarely synchronous motors).

Thursday 26/9/2019


* Torque / Speed characteristics:

• Load Requirements & Motor capability.

- Torque value
- Speed value
- direction of rotating.
- Braking.


- Torque (value & direction)
 - Speed (value & direction)

to match the load's requirements.

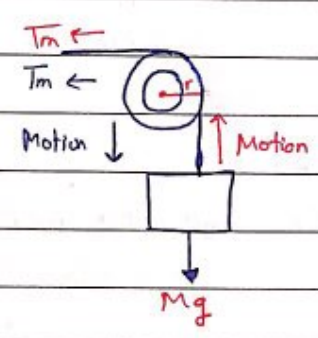


direction of Torque doesn't change even if the direction of motion changes.

Hint:

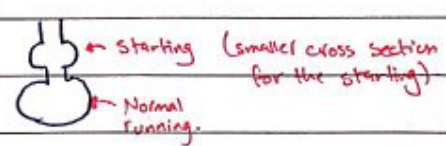



* Power = $T \omega$

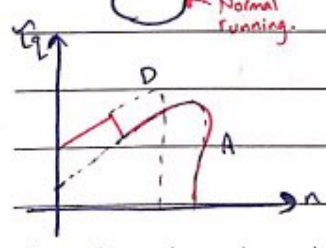• Motor with -ve power means it's a generator.



the motor has become a generator.

$-T_g$

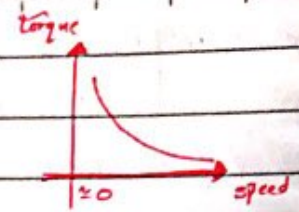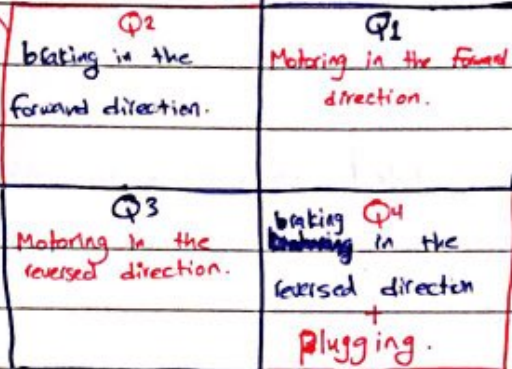

∴ if P is -ve then it's braking.

• Quadrant 1:

Motor running at certain direction to drive mechanical load.

Both Torque & speed are considered positive.

$$P = T_g * \omega_m (+)$$

• Quadrant 3:

Motor running in the opposite direction to drive mechanical load.

Both Torque & speed are considered negative.

$$P = -\omega_m * (-T_g) (+)$$

• Quadrant 2:

Negative Torque but positive speed.

$P = (-T_g) * \omega_m (-)$; the motor is running in the opposite direction as a generator to brake the load.

• Quadrant 4:

case ①: the machine is running as a generator to brake the load in the reversed direction.

$$P = (-\omega_m) * T_g (-)$$

case ②: a type of braking referred to as Plugging.

$$\tau_q \oplus \rightarrow \omega_m (-)$$

$$P \rightarrow -ve$$

$$P = -(\omega_m) \times \tau_q \quad (-)$$

* why do we need braking?


- energy saving/efficiency.
- precise precision control. (that's why electrical cars are easy & simple to brake)

Sunday 29/9/2019

* Types of loads:

① Friction

$$T_F = T_V + T_C$$

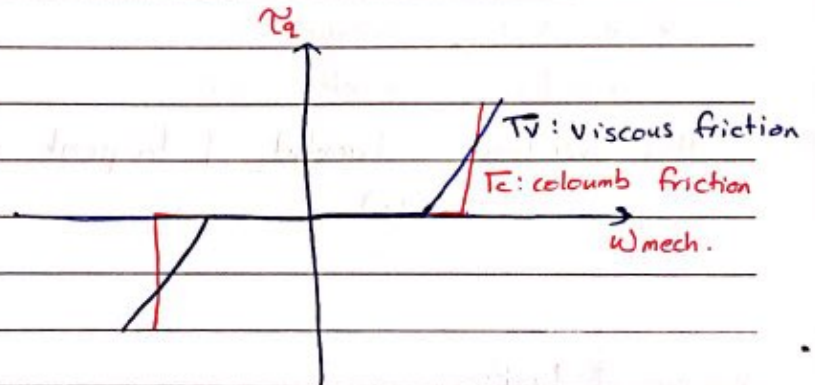

② Acceleration / Deceleration.

$$T_{acc} = J \cdot \frac{d\omega_{mech}}{dt}$$


↳ moment of Inertia (kg.m²)

- a. for positioning systems (i.e.: PV array movement, Antenna movement)
- b. starting of a certain load (Motor/load)
- c. braking (Deceleration).

③ Windage.

Torque required to move the air surrounding the rotational elements.

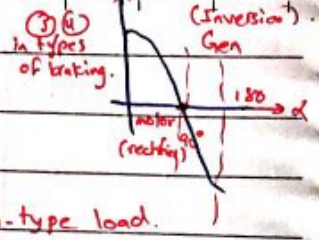• motor \rightarrow generator
(reverse the direction of the field)



④ Mechanical load Torque.

$T_L = f(\omega_{mech})$

$T_L = T_f + T_w + T_{acc.} + T_{mech.}$

$T_{motor} (shaft) = T_L$

$T_{motor} (shaft) = T_d - \text{Losses (motor)}$
 \rightarrow developed torque.

$T_{motor} (shaft)_{rated} = T_{load} \rightarrow$ the motor is fully-loaded ($T_g = \frac{P}{\omega_{mech.}}$)

* the motor can be over-loaded for short periods of time.

- ex: at starting (acceleration).
- at braking (desceleration).

this overload is harmful if frequent starting/braking is applied.
(i.e: lifts).

Tuesday 1/10/2019


* Types of braking:

① conventional mechanical braking.

kinetic energy dissipated as heat (loss).

② Eddy-current braking.

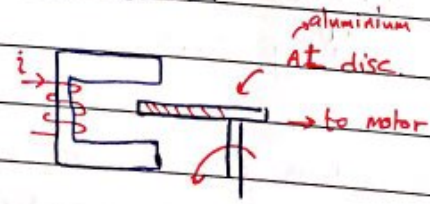- usually used in machine labs for testing purposes.



- kinetic energy is dissipated as heat.

$P_e \rightarrow f(Bm^2)$
 $P_h \rightarrow f(Bm^2) \rightarrow 1.5 - 2.5$


③ Dynamic braking.

The motor is controlled to run as a generator.

The generated power is locally used for other purposes (water heating, air conditioning).

④ Re-generative braking:

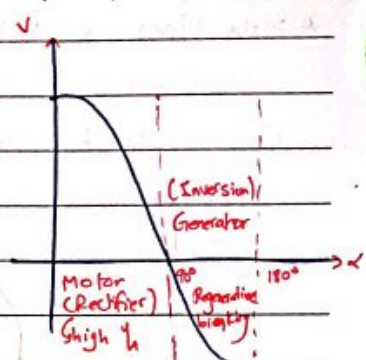The motor is controlled to run as a generator.
The generated power is pumped back to supply.




HINT: efficiency is a very big advantage in power electronics.

* Mechanical coupling (between motor's shaft and mechanical load's shaft):

- ① Gearing - Coupling. } speed & Torque transformation. (+J)
- ② Belt-coupling. } Inertia.

① # of teeth in the disc.

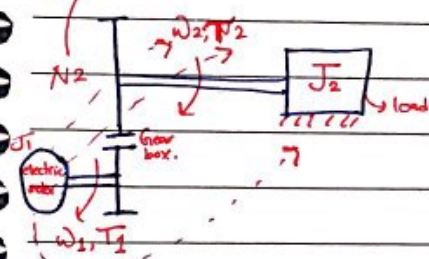

$T_2 \rightarrow V$ (transformer)
 $\omega \rightarrow I$ (transformer)
 $J \rightarrow Z$ (transformer).

each load has a specific inertia
acceleration braking.

$$T = J \frac{d\omega_{mech}}{dt}$$

$$T = \frac{J}{r} \cdot \frac{dv}{dt} \text{ (linear motion)}$$

v : linear speed.

$$\frac{T_1}{T_2} = \frac{N_1}{N_2} = a$$

$P = T \cdot \omega$


$$\frac{\omega_1}{\omega_2} = \frac{N_2}{N_1}$$

$v = \omega \cdot r$
(rotational & linear relation).

$$T_1 = T_2' = T_2 \frac{N_1}{N_2} = a T_2$$

$$J_2' = \left(\frac{N_1}{N_2}\right)^2 J_2$$

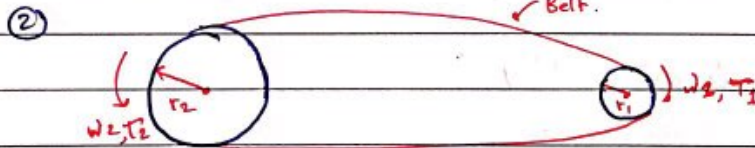* the only problem in Gear-coupling is its losses.



low radius is usually at the motor side.

Motor { high speed.
low torque.

$$\frac{T_1}{T_2} = \frac{r_1}{r_2} = \frac{D_1}{D_2}$$

* the problem of belt-coupling is its elasticity, vibration, slippage.

$$\frac{\omega_1}{\omega_2} = \frac{r_2}{r_1}, \quad J_2' = \left(\frac{r_1}{r_2}\right)^2 \cdot J_2$$


to avoid slippage: use toothed belt.

Thursday 3/10/2019

* Main types of mechanical loads:

① compressors.

T_L is almost independent of speed.

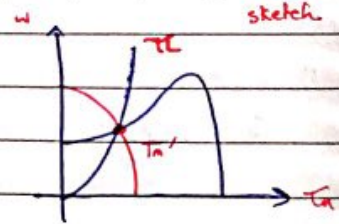

(linearized to be constant)
practically.


• this load is unidirectional & works in Q_1, Q_3 only. (cannot be reversed).

(Zero speed / high torque for compressors).

② Fan-type load.

$$T_L = f(\omega^2) = k\omega^2$$

ω function.

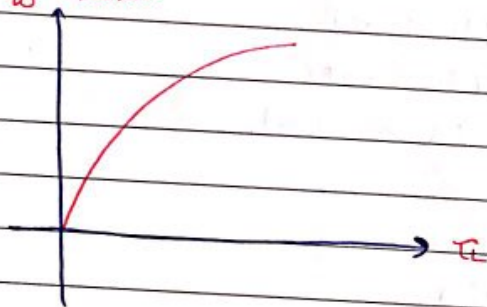


starting Torque = 0

$$P = k \cdot \omega^3$$

(works in Q_1, Q_3 only).

③ constant Power load.

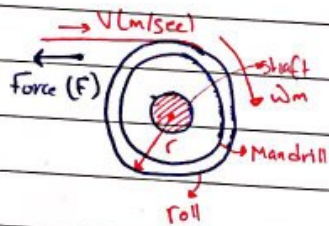


$$T_L = F \cdot r$$

$$\omega_m = \frac{V}{r}, \quad r = \frac{V}{\omega_m} \quad \therefore T_L = F \cdot \frac{V}{\omega_m}$$

$$(T_L \times \omega_m) = F \cdot V$$

Power

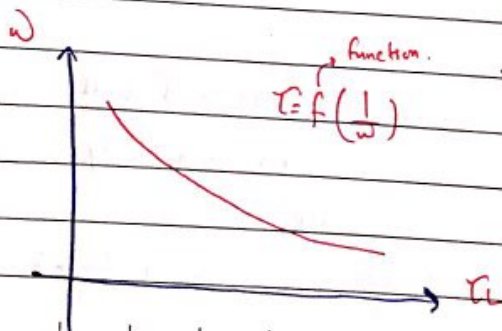



$$T_L = f\left(\frac{1}{\omega}\right)$$

$$\therefore P = T_L \times \omega_m = F \cdot V \equiv \text{constant}$$

must be constants


④ Transportation loads

- Subway trains
- street cars

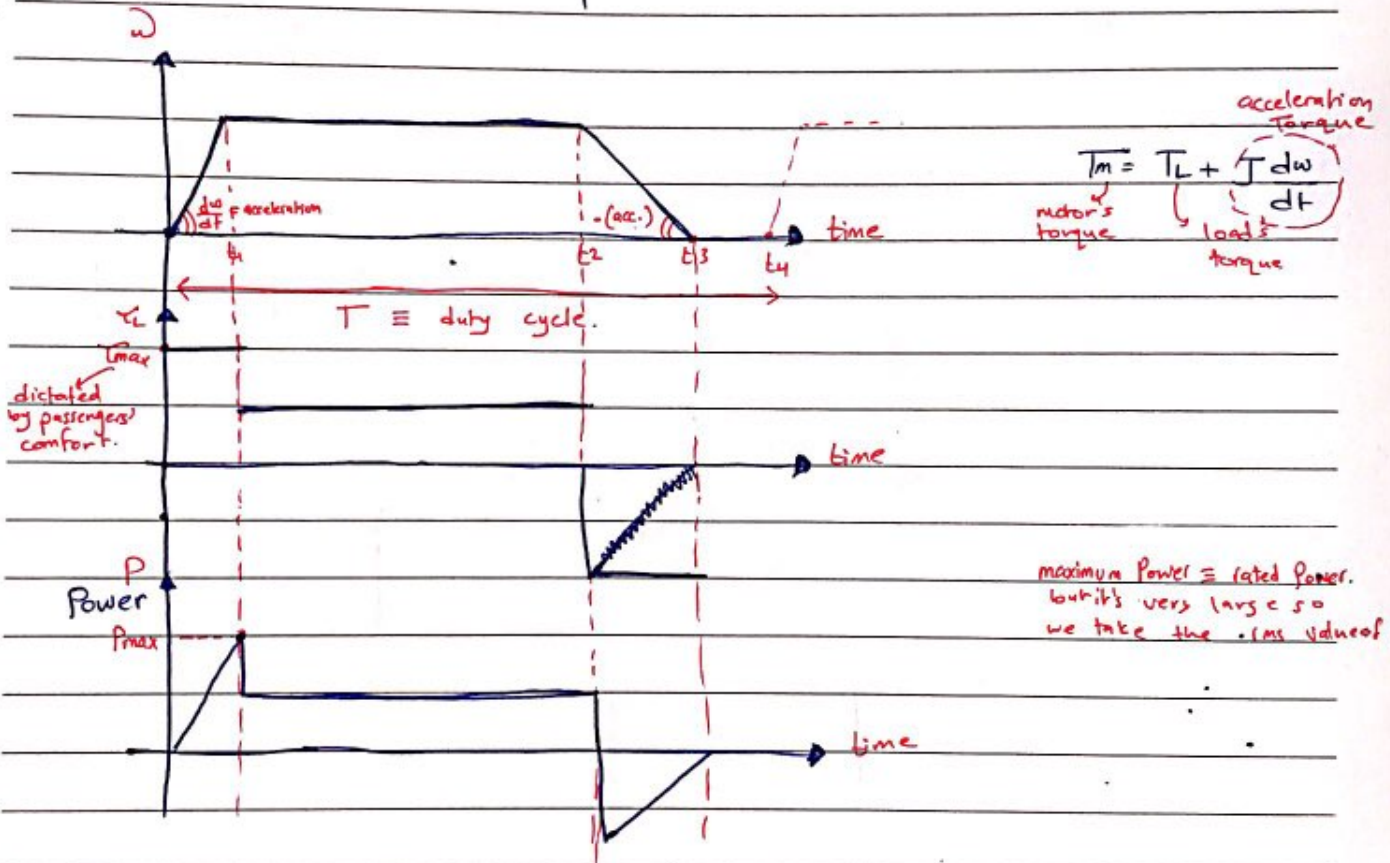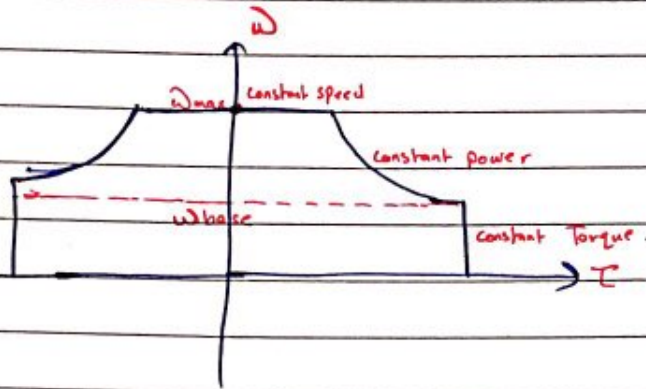

* Transportation

① Torque - Speed Limits

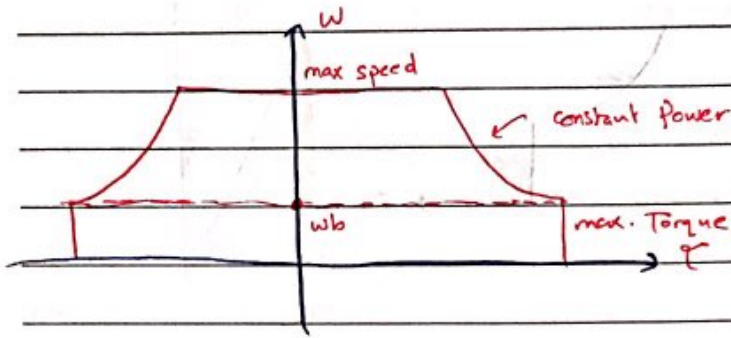

$\omega_b \triangleq$ base speed

Max speed: load max. limits.

Max Torque: Max. motor Torque during acceleration.

$$T_{motor} = T_{load}(\text{constant speed})$$

$$+ J \cdot \frac{d\omega}{dt}$$

$$T_{motor} = T_l + T_{acc.}$$

$J(\text{transportation}) \geq 20$ (normal loads) or Motor

• power limits:

Limits of the supply and converter.

* Station-to-station duty cycle:

$$\omega = f(t), \tau = f(t), P = f(t)$$

$$\omega = \frac{v}{r}$$


Linear acceleration $a = \frac{dv}{dt} \text{ (m/s}^2\text{)}$

$$\theta = \frac{d\omega}{dt} \text{ (rad/s)}$$

$$\theta = \frac{d(v/r)}{dt} = \frac{1}{r} \frac{dv}{dt} = \frac{a}{r}$$


angular acceleration $\theta = \frac{a}{r}$

r: wheel's radius.

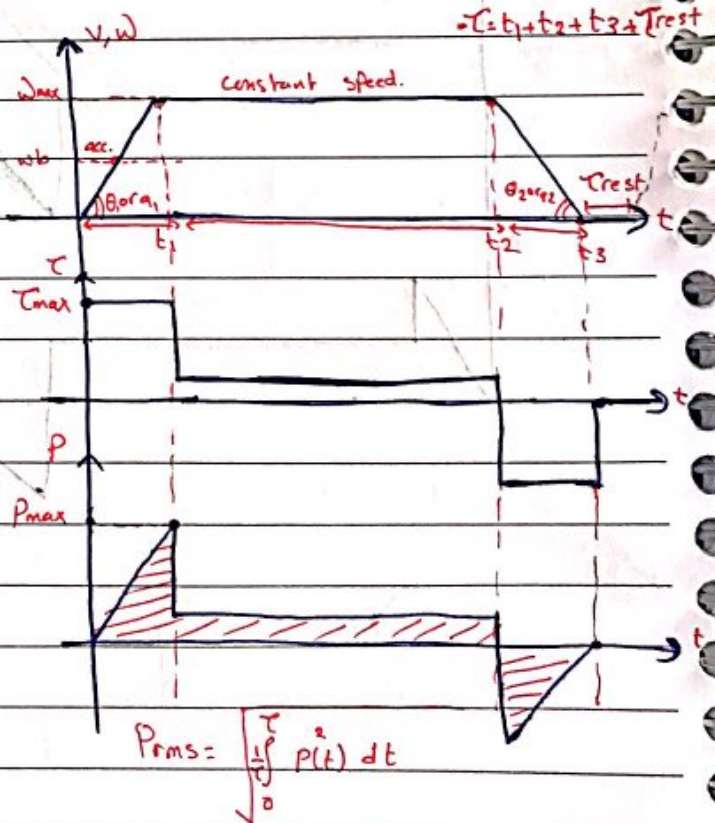

$$P_{rms} = \sqrt{\frac{1}{t} \int_0^t P^2(t) dt}$$

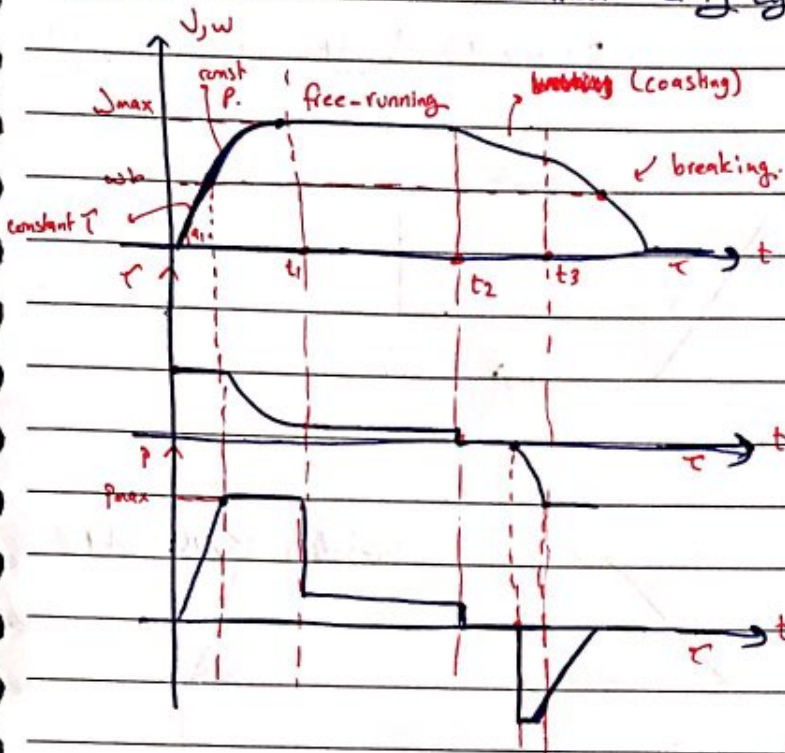* Modified Station-to-Station duty cycle. → for power to be less than the maximum scale.




* the aim of modified version:


to reduce the maximum power limit of the converter/supply → and motor.

(acceleration at max torque only up to the base speed).

* Speed/Time Trapezoidal envelope

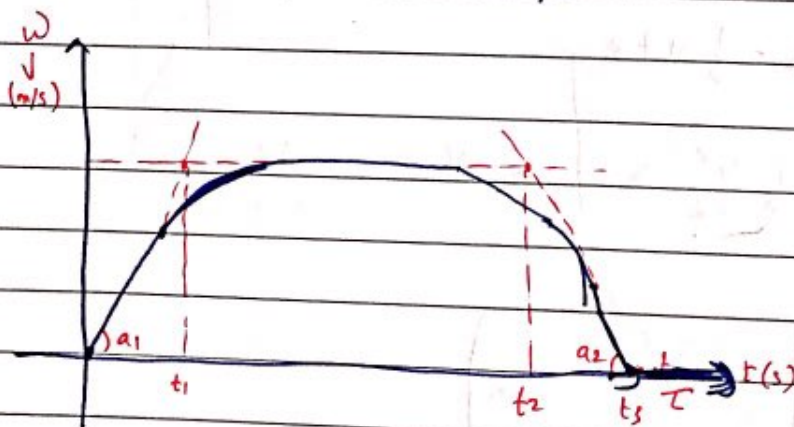

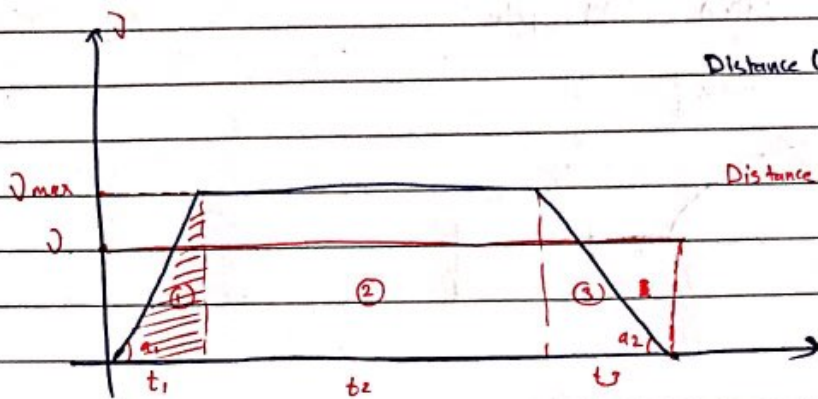
$$v_{avg} = \frac{\text{Distance}}{(t_1 + t_2 + t_3)}$$



$$\text{Distance (D)} = \frac{1}{2} v t_1 + v_{\max} t_2 + \frac{1}{2} v t_3$$

$$\text{Distance (D)} = (t_1 + t_2 + t_3) \times v_{\max} - \frac{1}{2} \frac{v_{\max}^2}{a_1} - \frac{1}{2} \frac{v_{\max}^2}{a_2}$$

Tuesday 15/10/2019

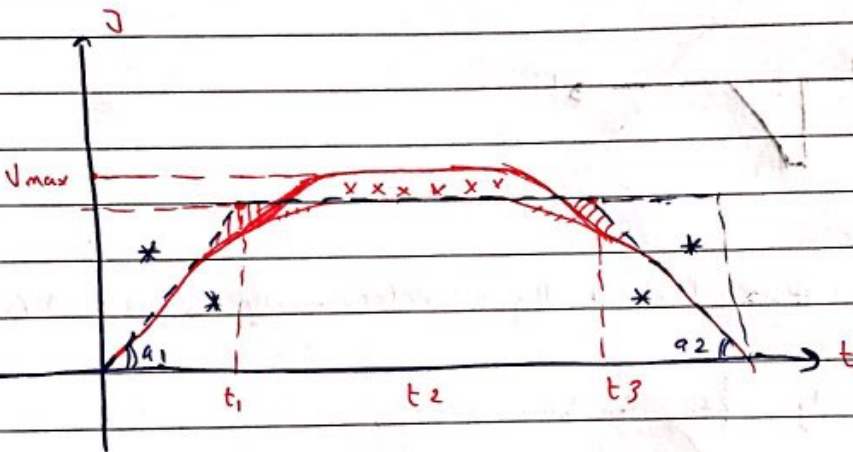


Distance :

$$D = (t_1 + t_2 + t_3) \times v - \frac{1}{2} v t_1 - \frac{1}{2} v t_3$$

$$D = (t_1 + t_2) \times v + \frac{1}{2} \frac{v^2}{a_1} + \frac{1}{2} \frac{v^2}{a_2}$$
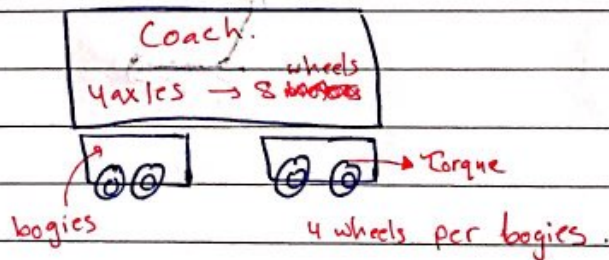
$$\therefore \text{Vav.} = \frac{D}{t_1 + t_2 + t_3}$$



$n =$ gear ratios


$n_1 =$ # of motors

$n_2 =$ # of wheels

$J_w =$ Inertia for one wheel

$J_w = \frac{1}{2} m r^2$  wheel

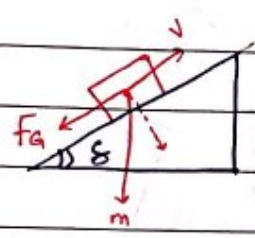$J_m = \frac{1}{2} m a^2$
 \hookrightarrow armature of the motor's radius.



$\sin \theta = G =$ Gradient
 $\sin \theta \leq 0.05$
 $F_g = mg \sin \theta$
 $T = mg \cdot r$

* Required Torques during acceleration:

acceleration rate (a_1 acc, a_2 dec)

① $T_{acc} = m \cdot a \cdot r \cdot n$ (for all motors)
 \hookrightarrow to refer to the motor side.

Acceleration (+, -) Torque.

② Torques to accelerate the rotating elements

a) wheels ; $T = J_w \times \frac{dw}{dt} = J_w \times r \frac{d\theta}{dt} = J_w \times \left(\frac{a}{r}\right)$ θ : Rotational (angular) acc.

$T_w = J_w \cdot \frac{a}{r} \cdot n_2 \cdot n$; for all motors.

b) $T_{motor (acc)} = J_m \cdot \frac{a}{r}$; for one motor $T_{motor (acc)} = J_m \cdot \frac{a}{r} \cdot n_1$; for all motors.

③ Gradient Torque.

$T_G = m \cdot g \cdot r \cdot \sin \theta \cdot n$; for all motors.


④ Resistance to motion (Friction + windage) during acceleration.

Assume to be : 20 Newton/Tonne $\cdot 1000 \text{ kg} \rightarrow 20 \text{ Newton}$.

$T_R = \frac{20 \times m}{1000} \cdot r \cdot n$; for all motors.

* $T_{shaft} = T_{acc} + T_w + T_R + T_{max (acc.)}$

Sunday 20/10/2019

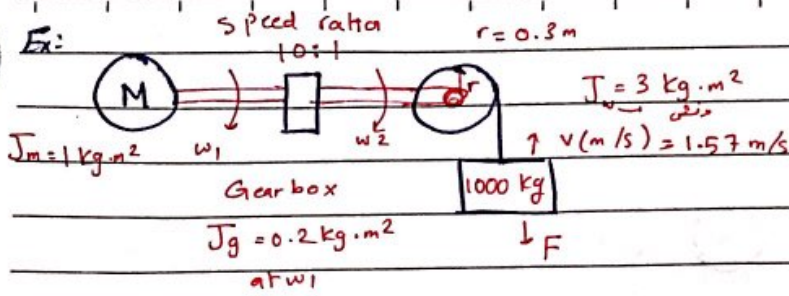

(a) Calculate Equivalent Inertia in motor side.

(b) Select suitable motor ratings ($P_r, w_m(r) \rightarrow N_m(r)$), Assume 100% efficiency for all system's elements.

Sol:

$$\frac{N_1}{N_2} = \frac{1}{10} = n$$

$$\frac{w_1}{w_2} = \frac{1}{n} = 10$$

$$\frac{T_1}{T_2} = n = \frac{1}{10}, \quad \frac{J_1}{J_2} = n^2$$

(a) $J_{\text{equ. (m. side)}} = J_m + J_g + J_w' + J_L'$

$$J_w' = n^2 J_w = \frac{1}{10^2} \times 3 = 0.03 \text{ kg}\cdot\text{m}^2$$

$$J_L = m \cdot r^2 \quad \text{when linear; but when circular } \frac{1}{2} m r^2$$

$$J_L = 1000 \times (0.3)^2 = 90 \text{ kg}\cdot\text{m}^2$$

$$J_L' = n^2 \times J_L$$

$$= \left(\frac{1}{10}\right)^2 \times 90 = 0.9 \text{ kg}\cdot\text{m}^2$$

$$J_{\text{equ}} = 1.0 + 0.2 + 0.03 + 0.9 = 2.13 \text{ kg}\cdot\text{m}^2$$

$$J_L = J_L \cdot \theta = J_L \cdot \frac{q_L}{r}$$

$$J_L = T_r \cdot \frac{r}{a_L}$$

$$= F \cdot r \cdot \frac{r}{a_L}$$

$$= \frac{m \cdot g \cdot r \cdot r}{a_L} = m \cdot r^2$$

3000 rpm
1500 rpm → synch.
motor

1410 rpm → Induction
2820 rpm → Ac motors.

$$F_L = m \cdot g = 1000 \times 9.81 = 9810 \text{ N}$$

$$\textcircled{b} \omega_2 = \frac{v}{r} = \frac{1.57}{0.3} = 5.236 \text{ rad/s}$$

$$\omega_1 = \frac{\omega_2}{a} = \frac{5.236}{0.1} = 52.36 \text{ rad/sec.}$$

$$N_m (\text{motor}) = \frac{60 \times \omega_m}{2\pi} = \frac{60 \times 52.36}{2\pi} = 500 \text{ rpm}$$

$$\Rightarrow \frac{T}{r} \cdot v = T \cdot \omega = J_{\text{equ.}}$$

$$P_L = F \cdot v = \omega \times T$$

$$T = F \cdot r$$

$$F = \frac{T}{r}$$

$$P_L = F \cdot v = \omega \times T = 9810 \times 1.57 = 15401.6 \text{ W}$$

$$P_L = \frac{15401.6}{746} = 20.3 \text{ hp}$$

$$\omega_2 = 52.36 \times a = 5236$$

$$P_L = T_L \times \omega_2 = 15401 \text{ W}$$

$$\hookrightarrow F \cdot r = 9810 \times 0.3$$


* if η was given in the question, we must divide the power by the η each shaft, but don't divide the motor's η unless we want to know the input power of the motor, as the output power is the considered one here. (Previous ex assumed all 100% η).

* Ex:

Motor is required to drive stop roll on a plastic strip line, the mandril which the strip is wound ($r_m = 5\text{cm}$), the strip emerges from the line at $v = 20\text{m/sec}$, strip tension = 10kg ; the motor is coupled to the mandril by

$\rightarrow 10 \times 9.81\text{N}$.

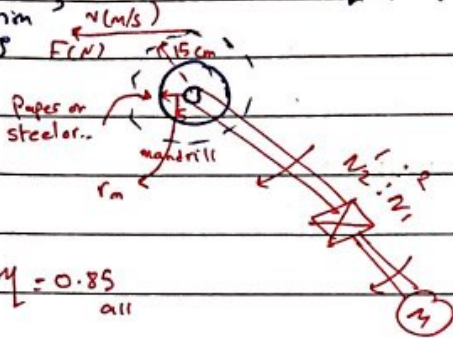1:2 reduction gearing $\eta = 0.85$ at all speeds.



find speed & power ratings of the motor required for this system?

$a = \frac{N_1}{N_2} = 2$

$\eta = 0.85$
all

→ the strip's builds up to a roll of (30 cm) diameter.

Sol:

$F = m \times g = 10 \times 9.81 = 98.1\text{ N}$.

$P = F \cdot v$
 $P = 98.1 \times 20 = 1962\text{ watts}$

$P_{\text{motor}} = \frac{P_{\text{load}}}{\eta} = \frac{1962}{0.85} = 2308.23\text{ Watts}$

at starting of rolling:

$\omega_2 = \frac{v}{r_m} = \frac{20}{5 \times 10^{-2}} = 400\text{ rad/s}$

$\omega_1 = \frac{\omega_2}{2} = 200\text{ rad/s}$

motor side

$N_{\text{motor}} (\text{rpm}) = \frac{60 \times \omega_1}{2\pi} = \frac{60 \times 200}{2\pi} = 1910.8\text{ rpm}$

$T = F \cdot r$ (load) $\neq P$

$= 98.1 \times 5 \times 10^{-2}$

$= 4.9\text{ N.m}$

$T_m = 2 \times 4.9 = \frac{9.8}{0.85}\text{ N.m}$ (motor) $\neq P$

or $T = \frac{P_{\text{motor}}}{\omega_{\text{motor}}} = \frac{2308}{200}$

at the end of rolling:

$$\omega_2 = \frac{20}{15 \times 10^{-2}} = 133.33 \text{ rad/s}$$

$$\omega_{\text{motor}} = \frac{\omega_2}{2} = \frac{133.33}{2} = 66.665 \text{ rad/s} \rightarrow \frac{60 \times 66.665}{2\pi} = 985.4 \text{ rpm} = N_m \text{ (rpm)}$$

$$P_{\text{motor}} = 2308 \text{ watts}, \quad T_{\text{end}} = \frac{2308}{66.665}$$

• Motor ratings (2308 W, 1910 RPM)

$0 \leq N_{\text{motor}} \leq N_{\text{motor (rated)}} \Rightarrow$ Armature voltage control.


$N_{\text{motor}} > N_{\text{motor (rated)}} \Rightarrow$ Field-weakening voltage control.

} DC-motor.


$0 \leq N_{\text{motor}} \leq N_{\text{motor (rated)}} \Rightarrow$ VVUF

$N_{\text{motor}} > N_{\text{motor (rated)}} \Rightarrow$ voltage control (above) only \rightarrow field weakening.

} AC-motor

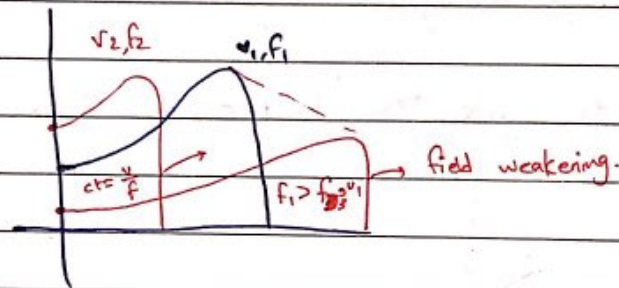

* Ex:

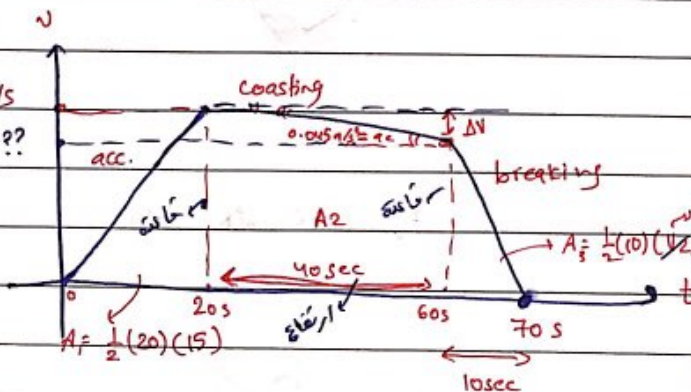

ac: a coasting.

find the average speed?

$$a_c = \frac{\Delta v}{40} \rightarrow \Delta v = 40 \times 0.045 = 1.8 \text{ m/s}$$

$$v_2 = 15 - 1.8 = 13.2 \text{ m/s}$$

$$a_{\text{deceleration rate}} = \frac{v_2}{10} = \frac{13.2}{10} = 1.32 \text{ m/s}^2$$

$$a_{\text{acceleration rate}} = \frac{15}{20} = 0.75 \text{ m/s}^2$$

$$\text{Sol: } v_{\text{avg}} = \frac{D \text{ (m)}}{70 \text{ sec}}$$

$$A_1 = \frac{1}{2} (15)(20) = 150 \text{ m}$$

$$A_2 = \frac{(15 + 13.2) \times 40}{2} = 564 \text{ m}$$

$$A_3 = \frac{1}{2} (10)(13.2) = 66 \text{ m}$$

$$\hat{D} = A_1 + A_2 + A_3 = 780 \text{ m} \Rightarrow v_{\text{avg}} = \frac{780}{70} = 11.14 \text{ m/sec}$$

$$v \left(\frac{\text{km}}{\text{hr}} \right) = \frac{11.14 \times 3600}{1000} = 40.1 \text{ km/hr}$$

Five Apple

* Example:

(gear)

Train with $m = 96 \times 10^3 \text{ kg}$, n_c : # of coaches = 3; each coach has 3 bogies, each bogie has 2 axles

(# of axles = 12, # of wheels =


$m_w = 455 \text{ kg}$; $r_w = 0.54 \text{ m}$

$m_{ar} = 502 \text{ kg}$, $r_a = 0.225 \text{ m}$

- Train operates between two stations / 500 apart.
- between two stations a uniform gradient of 1 in 80
- scheduled average speed is 20 m/s up the gradient.
- scheduled average speed is 22.5 m/s down the gradient
- Control setting of acceleration on a level track = 1.25 m/sec²
- Control setting of deceleration on a level track = 1.5 m/sec²
- Regenerative braking is used
- Train resistance during acc/dec = 20 N/1000 kg.


• Required:

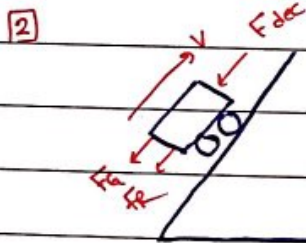① draw, to scale, the trapezoidal v/t curve.




braking upward.

$$F_t = F_{dec} + F_R + F_G$$

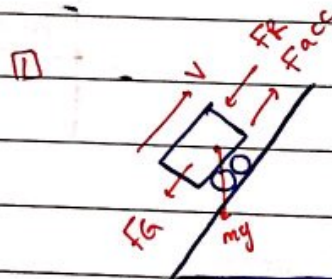


accelerates upward.

$$F_t = F_{acc} - F_R - F_G$$

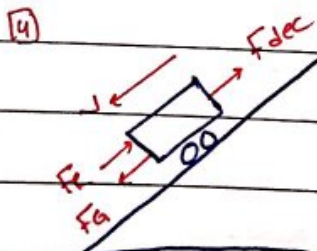

$$F_t = F_{dec} + F_R - F_G$$

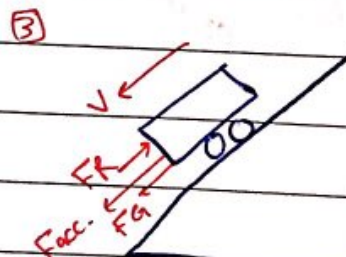

$$F_t = F_{acc} + F_G - F_R$$


$F_{acc.} \rightarrow \frac{1}{8}$
 $F_{dec.} \rightarrow \frac{1}{8}$

→ we have to convert the mass first:

$$m_{acc} = m + m_{eq.(\omega)} + m_{eq.(a_r)}$$

* Note: acceleration on Linear

↳ equivalent (Fictions)

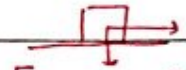

Force = $m \cdot a$ → in case Linear.

$$m_{eq.(\omega)} = m + \frac{J_{\omega} * n_{\omega}}{r_{\omega}^2} + \frac{J_{a_r} * n_m}{r_{a_r}^2 * n^2} \quad \# \text{ of motors.}$$

$$m_{eq.(\omega)} = ?$$

* Note: $F = m a$

$$\rightarrow J_{\omega} = \frac{1}{2} r_{\omega}^2 m$$

$$\frac{J}{r} = m a$$

$$= \frac{1}{2} * 455 * 0.54^2 = 66.34 \text{ kg} \cdot \text{m}^2$$

$$\frac{J}{r} \frac{d\omega}{dt} = m a$$

$$\frac{J}{r r} \frac{d\omega}{dt} = m a$$

$$\rightarrow J_{a_r} = \frac{1}{2} * r_{a_r}^2 * m$$

$$\frac{J a}{r^2} = m a$$

$$= \frac{1}{2} * 502 * 0.225^2 = 12.707 \text{ kg} \cdot \text{m}^2$$

$$m = \frac{J}{r^2}$$

$$\rightarrow m_{eq.(\omega)} = \frac{66.34 * 24}{0.54^2} = 5.46 \text{ kg}$$

$$\rightarrow m_{eq.(a_r)} = \frac{12.707 * 12}{0.225^2 * 0.356^2} = 4.126 \text{ kg}$$

$$\therefore m_{acc} (eq) = 96 * 10^3 + 5.46 * 10^3 + 4.126 * 10^3 = 105.59 * 10^3 \text{ kg.}$$

$m_{acc} * a$


$$\rightarrow F_{acc} = 105.59 * 10^3 * 1.25 = 132 \text{ kN}$$

↳ eq. (acc).


$$\rightarrow F_{dec} = 105.59 * 10^3 * 1.5 = 158.4 \text{ kN}$$

Sunday 27/10/2019

Complete the example:

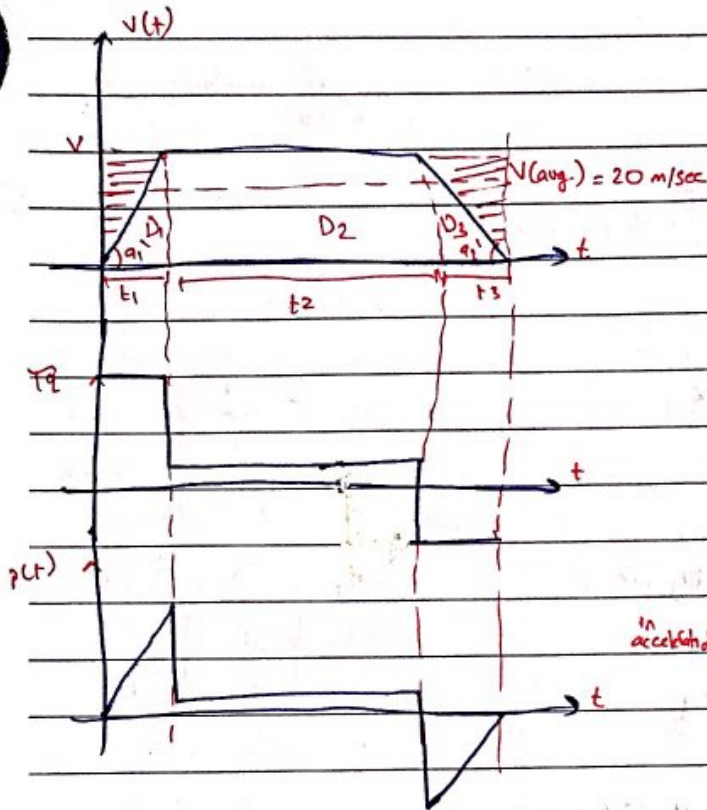

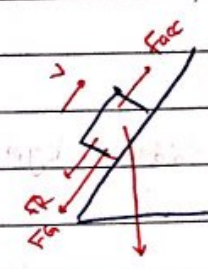* equivalent acceleration rate a_1' } upward motion
 * equivalent deceleration rate a_2'




$$F_t^{(acc)} = F_{acc} - F_R - F_G$$

$$F_t = (131.98 - 142 - 11.772) \times 10^3$$

$$F_t = 118.29 \times 10^3 \text{ N}$$

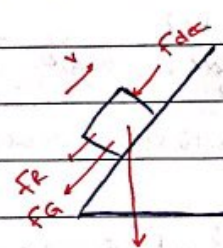in acceleration, $a_1' = \frac{F_t^{(acc)}}{\text{mass}} = \frac{118.29 \times 10^3}{105.6} = 1.12 \text{ m/s}^2$; $v_{avg} = 20 \text{ m/sec}$
 $a_2' = ??$; $D = 1500 \text{ m}$
 $\therefore T = \frac{1500 - 75}{20}$



$$F_t^{(dec)} = F_{dec} + F_R + F_G$$

$$F_t = 172.071 \times 10^3 \text{ N}$$

$$a_2' = \frac{F_t^{(dec)}}{105.6} = 1.63 \text{ m/s}^2 >> 1.5$$

* upward motion $\left(\begin{matrix} \text{sol} \\ \text{basic} \end{matrix} \right)$ $\left(\begin{matrix} \text{sol} \\ \text{basic} \end{matrix} \right)$

$$D = 1500 = v \cdot T - \frac{1}{2} a_1' v^2 - \frac{1}{2} a_2' v^2$$

$$1500 = 75v - \frac{1}{2} v^2 \left(\frac{1}{1.12} + \frac{1}{1.63} \right)$$

$$v^2 - 99.6v + 1991.7 = 0$$

$v = 71.9 \text{ m/sec}$; 27.71 m/sec ; $v_{avg} = 20 \text{ m/sec}$
 \therefore we'll take $v = 27.71 \text{ m/sec}$
 X neglected.

$$D_1 = \frac{v_1^2}{2a_1} = \frac{1}{2} \times \frac{27.71^2}{1.12} = 342.7 \text{ m}$$

$$D_3 = \frac{1}{2} \frac{v^2}{a_2} = \frac{1}{2} \times \frac{27.71^2}{1.65} = 235.6 \text{ m}$$

$$D_2 = D - D_1 - D_3 = \underline{921.7 \text{ m}}$$

$$t_1, t_2, t_3 \Rightarrow t_2 = \frac{D_2}{v} = \frac{921.7}{27.71} = 33.26 \text{ sec.}$$

$$\text{to find } t_1 \Rightarrow D_1 = \frac{1}{2} v t_1 = \frac{1}{2} \times 27.71 \times t_1$$

$$\therefore t_1 = 24.73 \text{ sec.}$$

$$t_3 = \frac{2D_3}{v} = \frac{2 \times 235}{27.71} = 17 \text{ sec.}$$

or $75 - (t_1 + t_2)$

* Downward motion:

$$a_1'' \quad a_2'' \quad ??$$

downward acceleration ↓ down ward deceleration

$$a_1'' = \frac{F_{acc} + F_G - F_R}{m_{acc}} = 1.343 \text{ m/sec}^2$$

$$a_2'' = \frac{F_{dec} - F_G + F_R}{m_{dec}} = 1.407 \text{ m/sec}^2$$

$$T_{dec} = \frac{D}{v_{avg(dec)}} = \frac{1500}{22.5} = 66.67 \text{ sec.}$$

$$v_{dec} \times T_{dec} = -\frac{v_{dec}^2}{2} \left(\frac{1}{a_1''} + \frac{1}{a_2''} \right) = 1560$$

$$\frac{v_{dec}^2}{2} - 91.62 v_{dec} + 2061.4 = 0$$

$$v_{dec} = 51.9 \text{ m/sec} \quad ; \quad 39.72 \text{ m/sec}$$

neglected

$$v_{avg(dec)} = 22.5 \text{ m/s}$$

$$\therefore v = 39.72 \text{ m/sec}$$

$$D_1 + D_2 + D_3 = 1500 \text{ m}$$

$$D_1 = 587.23 \text{ m} \quad ; \quad D_2 = 352 \text{ m} \quad ; \quad D_3 = 560.8 \text{ m}$$

$$t_1 = 29.57 \text{ sec} \quad ; \quad t_2 = 8.861 \text{ sec} \quad ; \quad t_3 = 28.24 \text{ sec}$$

$$t_1 + t_2 + t_3 = 66.67$$

$$\omega_{\text{max (Load)}} = ?? \quad \frac{v}{r} = \frac{27.71}{0.54} =$$

$$\omega_{\text{max (motor)}} = \omega_{\text{max (load)}} = \boxed{144.146 \text{ rad/sec.}} \quad \text{to find Power}$$

n
(transf. ratio)

$$N_{\text{motor}} = \frac{144.146 \times 60}{2\pi} = 1376 \text{ RPM} \quad (\text{looks like AC induction motor})$$

rating: 1500 assuming 50 Hz frequency.

~~slip~~ slip ≈ 8.1

D-class motors, τ_{max} very high
slip $> 5\%$

(8% \rightarrow 12%) D class
losses $\propto \omega^2$

Tuesday 29/10/2019

* Torque/Power versus time curves.


* Forces in the following cases:

(A) upward motion:

- 1) During acceleration
- 2) constant speed running
- 3) Deceleration

(B) downward motion:

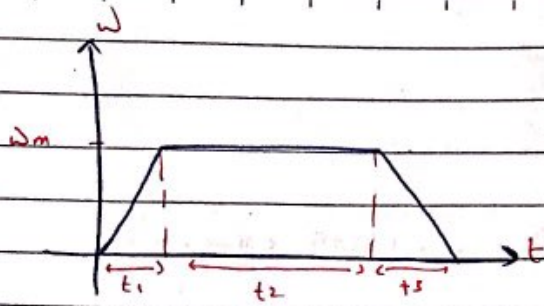- 1) acceleration
- 2) constant speed
- 3) deceleration



$$A_1 = F_{acc} + F_G + F_R$$

$$A_2 = 0 + F_G + F_R'$$

↳ Acc running.

F_R' : Resistance to motion force during constant speed running.

$$F_R' = m(4.1 + 0.123v) \times 10^{-3} + A_c \cdot v^2 [151 \text{ K} + 2.16 \text{ nc} \cdot L_c] \times 10$$

v \equiv speed m/sec


A \equiv Area of the front edge of the first coach.

K \equiv shape of the front edge.

nc \equiv # of coaches

L_c \equiv length of each coach.
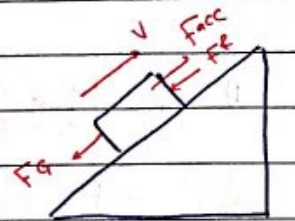
$$m = 96 \times 10^3 \text{ kg}, k=1, nc=3, A_c = 11.5 \text{ m}^2, L_c = 23 \text{ m}$$



$$F_G = m \cdot g \cdot \frac{1}{80}$$

$$\times F_G = 11.772 \text{ kN}$$

$$\times F_R = 20 \times 96 = 1.92 \text{ kN}$$

$$F_R' (\text{upward}) = 3.37 \text{ kN}$$

$$F_R' (\text{downward}) = 6.306 \text{ kN}$$

upward case

$$F_{\text{motor}} (\text{upward-acc.}) = (131.98 + 11.772 + 1.92) \text{ kN} = 145.6745 \text{ kN} \text{ (Motoring action)}$$

[all motors]

$$T_{\text{motor}} (\text{upward-acc.}) = \frac{F \cdot r \cdot \eta}{n_1} = \frac{145.6745 \times 0.54 \times 0.356}{12} = 2.333, 707 \text{ kNm}$$


[Per-motor]

$$\omega = \frac{v_{\text{upward}}}{r \cdot n} = \frac{27.71}{0.57 \times 0.35} = 144.15 \text{ rad/sec}$$

$$P_{\text{max}} = T_{\text{m}} \times \omega_{\text{max}} (\text{upward})$$

[motor]
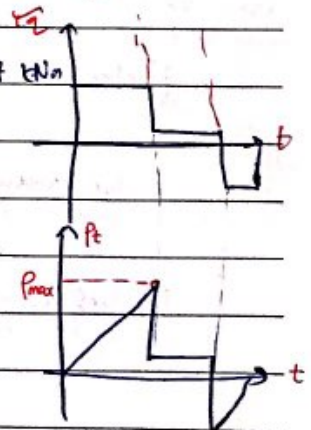
$$P_{\text{max}} = 2.333 \times 10^3 \times 144.15 = 336.4 \text{ Kw/motor}$$



either design on P_{max} or P_{avg} .

$$F_{\text{motor}} (\text{up-ward}) = 0 + F_G + F_R = 15.142 \text{ kN}$$

constant speed

$$T_{\text{motor}} (\text{constant speed}) = \frac{15.142 \times 0.54 \times 0.35}{12} = 242.58 \text{ Nm/motor}$$

[Per-motor]

$$P_{\text{motor}} (\text{constant speed}) = 242.58 \times 144.15 = 34.967 \text{ Kw}$$

Five Apple

$$F_{\text{motor (upward-dec)}} = -F_{\text{acc}} + F_R + F_G$$

deceleration

$$= -144.6787 \text{ KN}$$

Generation of power.

$$T_{\text{motor (upward-dec)}} = \frac{-144.687 \times 0.54 \times 0.35}{12} = -2.217885 \text{ KNm}$$

[per-motor]

$$P_{\text{max (upward-dec)}} = -2.217885 \times 10^3 \times 144.15$$

$$P_{\text{max}} = -334.11 \text{ KW}$$

to find the energy:

$$W(\text{up}) = \left[\frac{1}{2} \times P_{\text{max (acc)}} \times t_1 \right] + [t_1 \times P] + \left[-\frac{1}{2} \times P_{\text{max (dec)}} \times t_2 \right]$$

$$= \left[\frac{1}{2} \times 336.4 \times 24.7 \right] + [24.7 \times 33.26] + \left[-\frac{1}{2} \times 334.11 \times 17 \dots \right] = 29.9721 \text{ MJ for all motors.}$$

$49.923 \times 10^6 \text{ J}$ $13.9567 \times 10^4 \text{ J}$ $-34.087 \times 10^6 \text{ J}$

define specific energy factor:

$$\text{SEF (upward)} = \frac{W_t (\text{Joule})}{m (\text{kg}) \times D (\text{m})} = \frac{49.923 + 13.9567 - 34.087}{96 \times 10^3 \times 1500} = 0.2069 \frac{\text{J}}{\text{kg.m}}$$

كل ما كان اقل يكون اقل وهو العنبر
بين قسط وقسط
downward case:

$$F_{\text{motor (downward-acc)}} = F_{\text{acc}} + F_R - F_G$$

$$F_{\text{motor (downward-constant speed)}} = 0 + F_R - F_G$$

$$F_{\text{motor (downward-dec)}} = -F_{\text{dec}} + F_R - F_G$$

Thursday 31/10/2019

completing downward motion:

A) acceleration:

$$T = 1.9565 \text{ kNm/motor}$$

$$P_{max} = 404.25 \text{ kW/motor}$$

$$W = 71.72 \text{ MJ}$$

$$F = 122.13 \text{ kW}$$

B) Constant speed:

$$F = -5.466 \text{ kN}$$

$$T = -87.56 \text{ kN.m/motor}$$

$$P = -18.09 \text{ kW}$$

$$W = -1.924 \text{ MJ}$$

C) deceleration:

$$F = -148.527 \text{ kN}$$

$$T = -2379.4 \text{ N.m}$$

$$P_{max} = -491.624 \text{ kW}$$

$$W = -83.29 \text{ MJ}$$

$$W_{tot} (\text{run down}) = -13.4946 \text{ MJ}$$

$$S.P. E = \frac{-13.4946 \times 10^6}{1500 \times 96 \times 10^3} = -0.0937 \text{ J/Kg.m}$$

توضیح

* RMS kW rating of the motor:


$$Kw_{(rms)} = \sqrt{\frac{1}{T} \int_0^T P^2(t) dt}$$

كنبه اللفه كالم واللفه كالم
وعجيره متقار، كرتم الازكر




* Drive system:

1. Load
2. Motors
3. converters


MOTORS

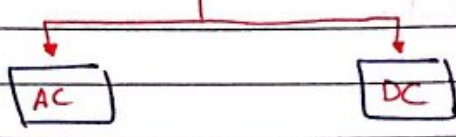

DC MOTORS

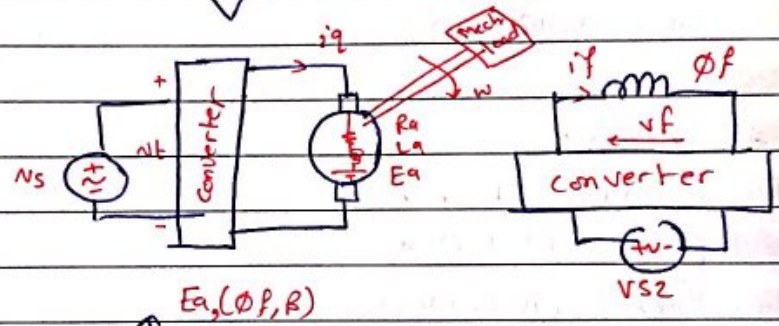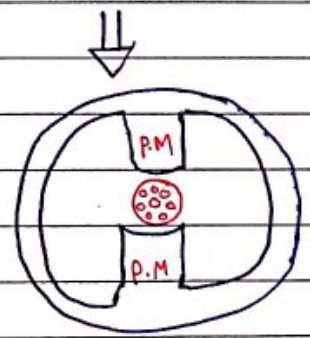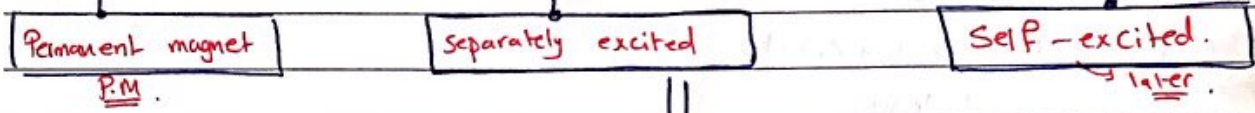

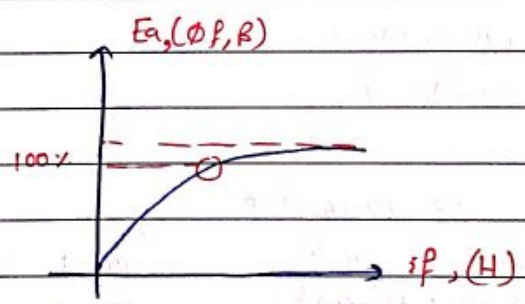- * up to 1 kW power.
- * more reliable.
- * no field winding
- * very expensive
- * servo systems.



B/H curve, no load characteristics;
in BH curve \rightarrow Slope = μ

$$e = k_a \times \phi \times \omega$$

$$k_a \equiv \text{design constant} = \frac{Z}{\pi} \times \frac{P}{n}$$

$A = 2 \rightarrow$ wave winding

$A = 2P \rightarrow$ lap winding

$(\lambda, i_f) \rightarrow$ slope = L

completely separately excited:

$A = 2$	wave winding	high voltage low current
$A = 2p$	Lap winding	low-medium voltage medium-high current

$$\text{motor time constant} = \tau = \frac{L_a}{R_a}$$

high $\tau \rightarrow$ higher inductance

advantage \rightarrow better current filtration
(converter controlled systems)

disadvantage \rightarrow lower response to control command.

high $T \rightarrow$ higher inductance
 advantage \rightarrow better current filtration
 (converter controlled systems)
 disadvantage \rightarrow lower response to control command.

Sunday 3/11/2019


* motors with rapid speed change:-

J : moment of inertia

$$J = \frac{1}{2} m r^2$$

power rating of a motor is a function of (mass, r , l_r)

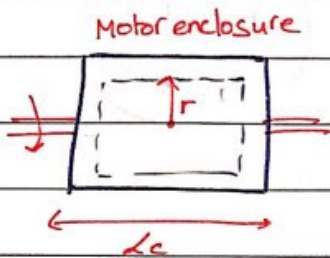
rotor's radius \leftarrow armature's & rotor's length
 \downarrow
 in DC mech. stator.



Fast response: low inertia leading to low (r) design
 \Rightarrow to keep the power unaffected, the length of the rotor (l_r) should be higher to compensate.

inertia is for the rotating elements, so it's less for the rotor in motors.

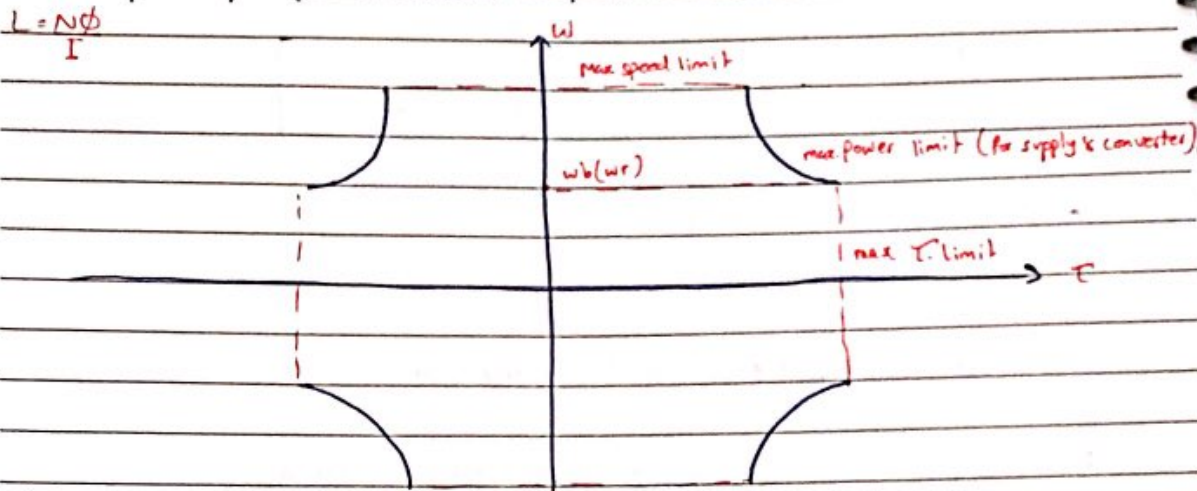* Envelope of T/w characteristic of the motor :-



w_b : linear speed to w_b & then constant Torque.

* Speed Limits :-


① Mechanical design.

② Air-gap length : should be as small as possible.

with air gap larger MMF is needed to create same flux.



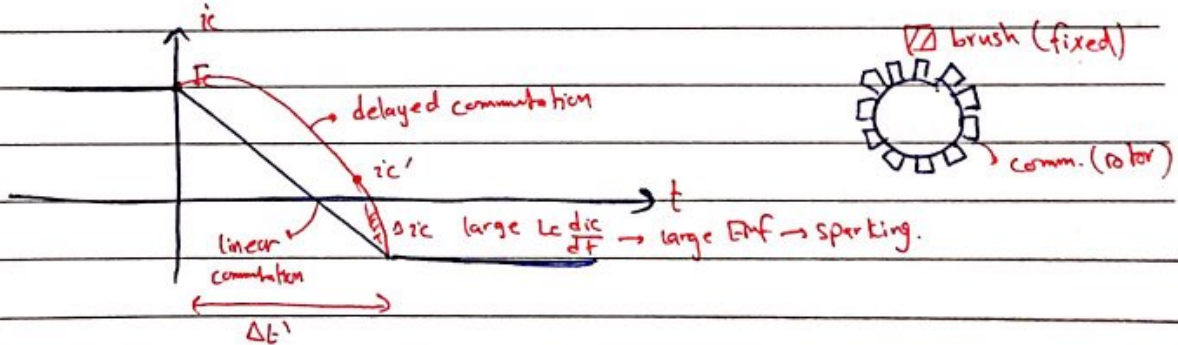③ Armature reaction + commutation (sparkling between the brushes and commutator segments).



* higher rotor speeds leads to higher change in $\tau_c \rightarrow k_c \frac{dx}{dt}$
 \rightarrow large \rightarrow sparking


* ϕ over brushes isn't zero by the effect of Armature reaction.

$$w_m \leq (2 \rightarrow 3) w_m(\text{rated})$$

$w_m(\text{base})$

Tuesday 5/11/2019

* overloading

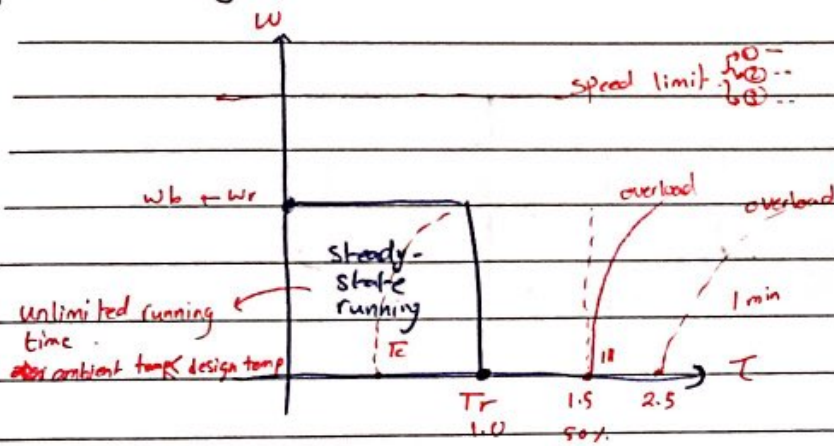

① Steady-state:

can run 24-H a day without overheating, assuming that:


- a) No current harmonics
- b) The ambient temperature is below design value.

limits \rightarrow Rated Torque / rated speed

② over-loading: restricted with the required time of overloading.

over-loading includes: load Torque overload & harmonics overload. % overheating
 \hookrightarrow caused by harmonics.
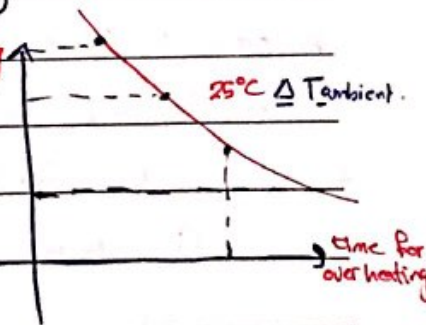
$$I_{\text{harmonics}} = \sqrt{I_{\text{av}}^2 + \sum_{n=1}^{\infty} I_{\text{rms}}^2(n)}$$



Solution ?? For continuous running \Rightarrow oversize the motor.


Hint:
When do we do intentional over-load??

i.e: bridges (machines which work periodically).


designed by humans for low power rated motors.

(سواء بس ما يتجوز في السرعة الزمنية، أو ما يتجوز في الأحمال)

better economics \checkmark

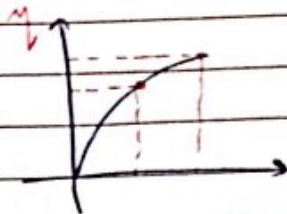

* DC-Motor modeling so

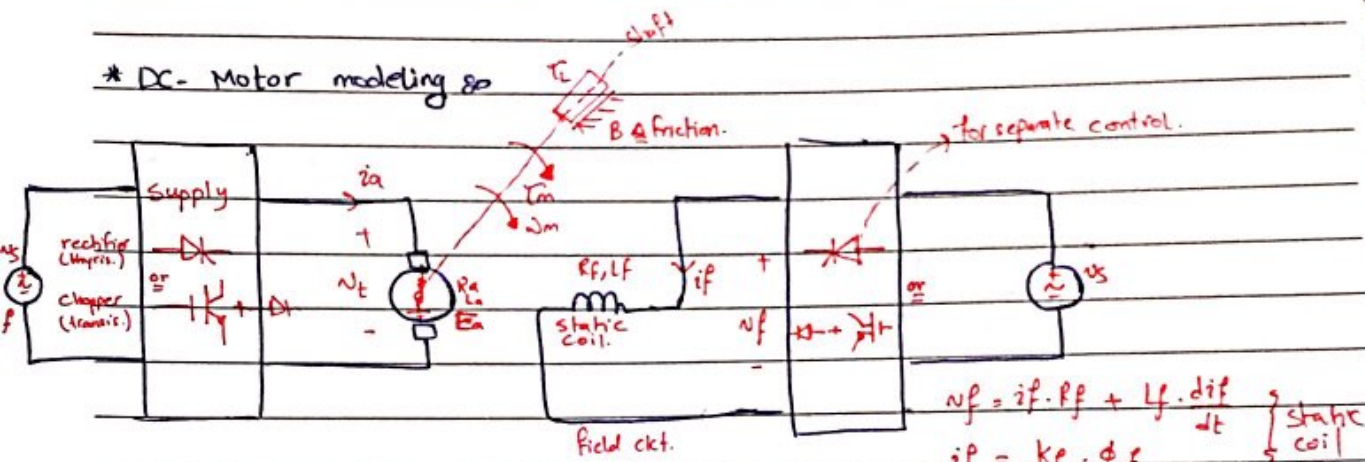

$$n_f = i_f \cdot R_f + L_f \cdot \frac{di_f}{dt}$$

$$i_f = k_f \cdot \phi_f$$

} static coil
} Now
} Magnetization curve.


E_a or $e_a = k_a \cdot \phi \cdot \omega$ (Induced emf).

$T_m = k_a \cdot \phi \cdot i_a$

\hookrightarrow design parameter

$v_t = i_a \cdot R_a + L_a \frac{di_a}{dt} + k_a \cdot \phi \cdot \omega$

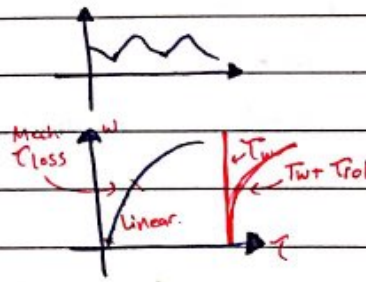$T_m = k_a \cdot \phi \cdot i_a = T_L + B \cdot \omega$



* $E_a = k_a \cdot \phi_f \cdot \omega$ under steady state conditions, with no harmonics.

* $T_m = k_a \cdot \phi_f \cdot I_a$ "

* $v_t = I_a R_a + k_a \phi_f \cdot \omega$ =

* $T_m = T_L + B \cdot \omega$ "

* $v_f = I_f R_f$ "

$\therefore E_a = V_t - R_a I_a$

$k_a \phi \cdot \omega = V_t - R_a I_a \frac{I_a}{k_a \phi}$

$(k_a \phi)^2 \omega = k_a \phi V_t - R_a (\tau_l + B \cdot \omega)$

$\omega ((k_a \phi)^2 + R_a \cdot B) = k_a \phi V_t - R_a \tau_l$


$\omega = \frac{k_a \phi V_t - R_a \tau_l}{(k_a \phi)^2 + R_a \cdot B}$

(*) very important

$\omega = \frac{k_a \phi V_t}{(k_a \phi)^2} = \frac{V_t}{k_a \phi}$ if we neglect viscous friction

* Methods of speed control:



1) Armature resistance control. (R_a)

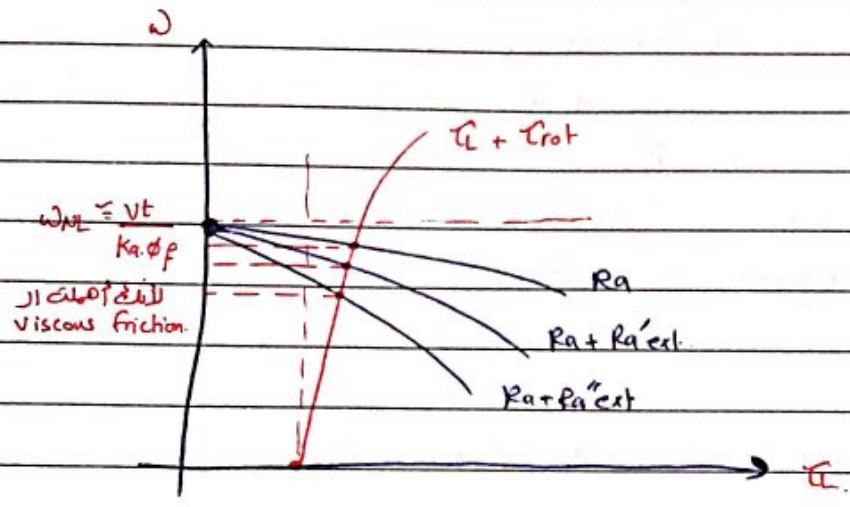

range of speed control:
 $0 \leq \omega \leq \omega_{rated}$

Thursday 7/11/2019


2) Armature voltage control

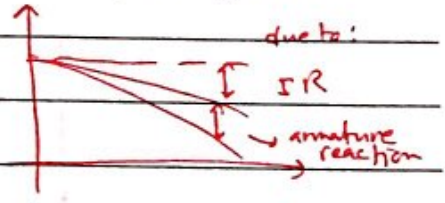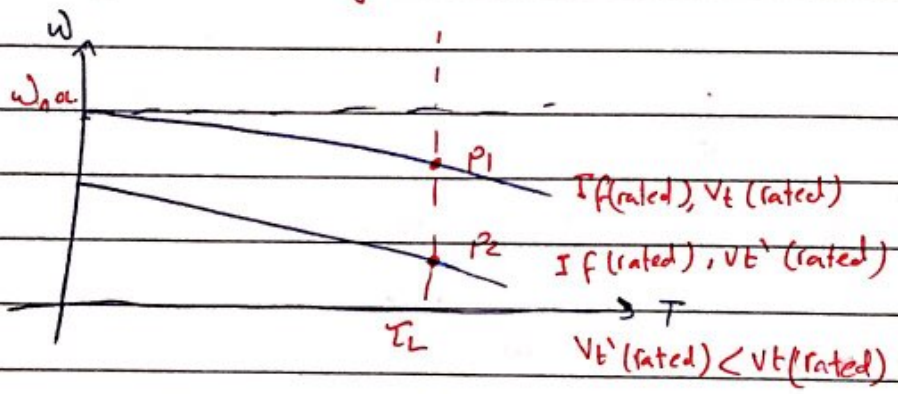

$\omega_{nl} = \frac{V_t}{k_a \phi}$ neglect B at no load

$= \frac{V_t}{k_a \cdot k_f \cdot I_f}$

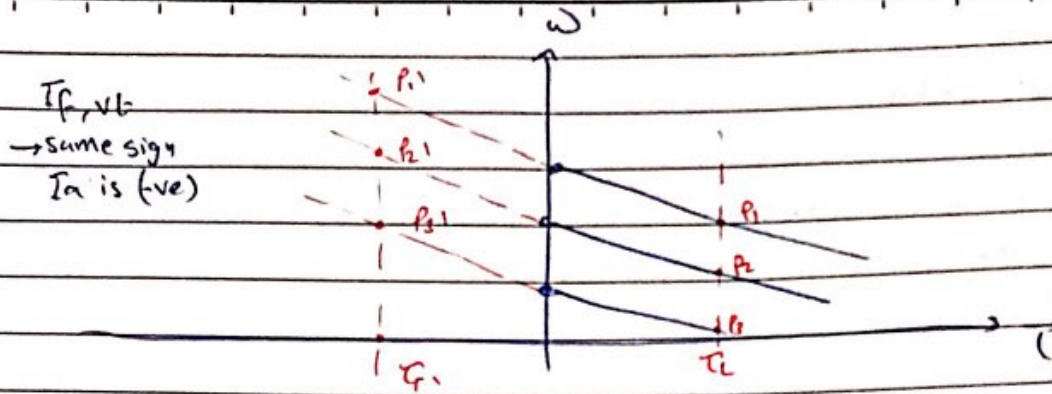$0 \leq V_t \leq V_t(rated)$
 $0 < \omega_m \leq \omega_m(rated)$



* with variable v_t , speed varies below rated value.

* curves are almost parallel with v_t variations.

* if the torque has a negative sign (accelerating), then, speed increased in the second quadrant assuming v_t & I_f are unchanged in polarity.


In this case (T_a) is changing direction.

P is (-ve). this is regeneration process.

[3] Field weakening control.


I_f can only be controlled below its rated value.

$$I_f \leq I_f(\text{rated})$$

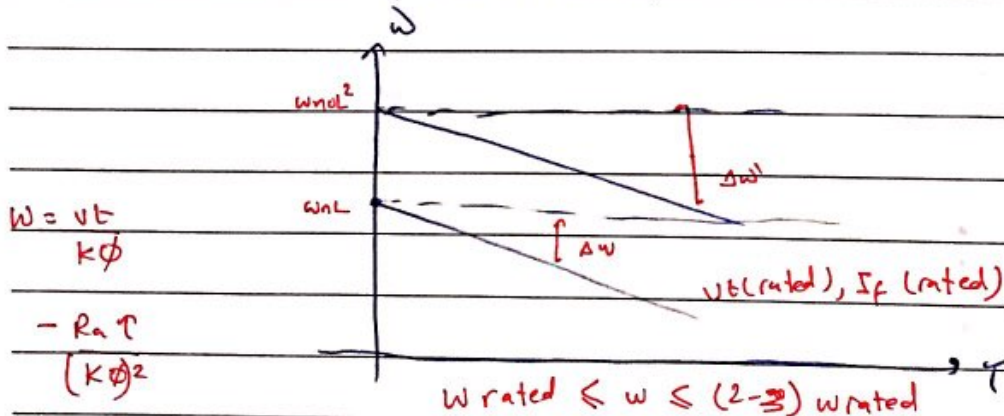

operation is constant power profile
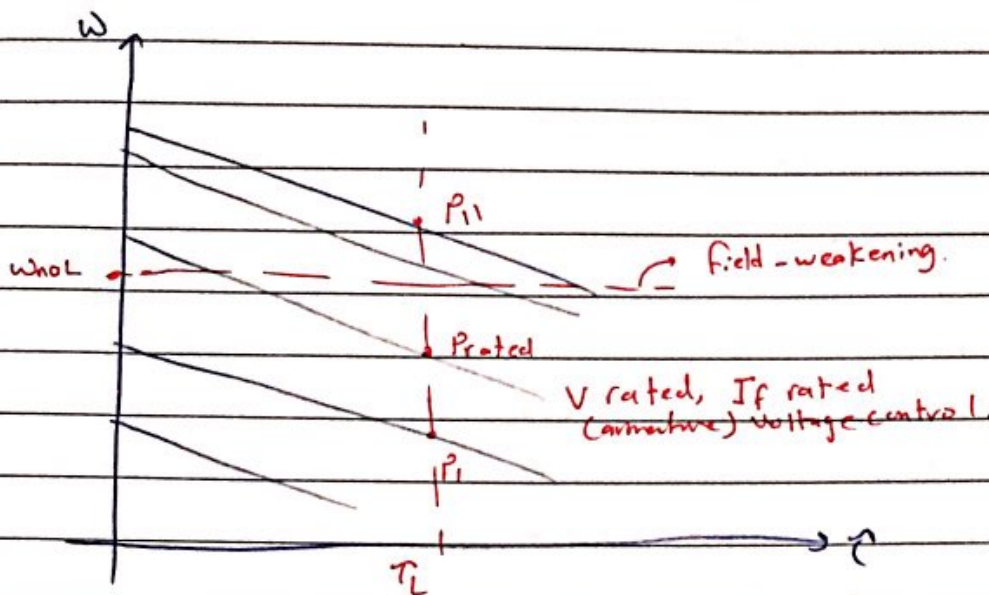
$$P = \tau \omega, \quad \omega \uparrow \rightarrow \tau \downarrow$$



Q) Supply: $0 < V_c < 600V$

to supply a motor when $V_t = 600V \Rightarrow 1600 \text{ RPM}$

a) load torque 420 Nm , calculate I_a ??

b) Field weakening is applied such that the power is constant, calculate the torque, if speed is 4000 RPM

c) Power rating of the supply.

Sol: a) $P = \omega \cdot T = VI$

b) $V_t = I_a = T \cdot \omega$

c) $P = I_a \times V \rightarrow (100)$

Sunday 10/11/2019

Solution:

$$P = W \times T = V_t \cdot I_a$$

$V_{rated} = 600V$, $N_r = 1600 \text{ rpm}$ neglect losses.

$$T_d = 420 \text{ Nm} \rightarrow I_a = ??$$

$$W_m = \frac{2\pi \times 1600}{60} \rightarrow P_d = V_t \cdot I_a$$

$$P_d = T_d \times W_m = 420 \times \frac{2\pi \times 1600}{60} = V_t \cdot I_a$$

$$I_a = 117.3 \text{ A}$$

Field weakening \rightarrow constant power


$$P_d = 600 \times 117.3 = W_m' \times T' = \frac{2\pi \times 4000}{60} \times T_d'$$

$$T_d' = 168 \text{ Nm}$$

$$\frac{168}{420} = \frac{1600}{4000}$$

• if P_{rot} were given $\rightarrow P_{rot} = k \cdot W_m \rightarrow$ calculate k

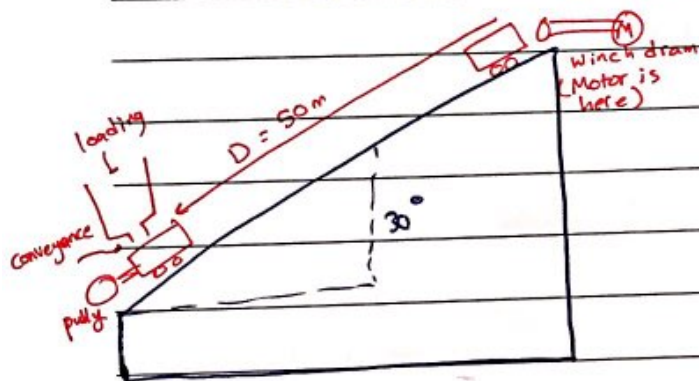$T_w = T_w' \rightarrow$ can use this when there's no rotational losses.



empty convey = 400 kg

load = 1600 kg

$$\eta = 2u = \frac{W_m}{W_L}$$

$$V_{up} = 5 \text{ m/sec}$$

$$V_{down} = 10 \text{ m/sec}$$

DC Motor :

230 V

$$I_a(r) = 2460 \text{ A}$$

75 HP

115 rpm

$$J_m = 1.94 \text{ kg}\cdot\text{m}^2$$

$L = 2 \text{ m}^4$

$$R_a = 0.0237 \Omega$$

Motor's preparation :-

T_{max} (and $I_a(max)$) is limited to 200%. (during acceleration).

Solution:

$$E_a = V_t - I_a R_a \quad \text{and} \quad q^2 T_L = T_L' \text{ (referred)} = J_m = 1.94$$

$$k = \frac{E_a}{\omega_m(r)}$$

$$J_L = 1.94 \times \frac{24^2}{n^2}$$

$$T_d = k \cdot I_a(r) = 464.7 \text{ Nm}$$


$$T_d(r) = T_{sh} = \frac{P_o(r)}{\omega_m(r)}$$

$$T_{motor}(\max) = 2 \times 464.7 = 929.4 \text{ Nm}$$

$$T_{load}(\max) = 24 \times 929.4 = 22305.6 \text{ Nm}$$

$$F_{load}(\max) = \frac{T_L(\max)}{r} = 23205.6 \text{ N}$$

$$I_a = \frac{T_a}{k}$$

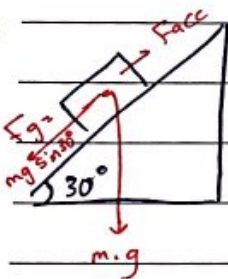

$$F_g = (1600 + 400) \times 9.81 \times \sin 30^\circ = 9810 \text{ N}$$

$$T_g = F_g \cdot r = 9810 \times 1 = 9810 \text{ Nm}$$

$$P_g = F_g \times v = 9810 \times 5 = 49050 \text{ W}$$

$$P(\text{Hp}) = \frac{49050}{746} = 765.75 \text{ hp} \rightarrow \text{Selected } P(\text{hp}) = 75 \text{ hp}$$

$$\omega_m(L) = \frac{v}{r} = \frac{5}{1} = 5 \text{ rad/sec}$$

$$\omega_m(\text{motor}) = 24 \times 5 = 120 \text{ rad/sec}$$

$$N_{\text{motor}(\text{rated})} = \frac{120 \times 60}{2\pi} = 1150 \text{ rpm}$$

Tuesday 12/11/2019

$$F_{\max} = 22305.6 \text{ N}$$

$$T_{\max} = 22305.6 \text{ Nm}$$

$$T_{\text{acc (motor)}} = 2 J_m \frac{d\omega_{\text{Motor}}}{dt} = 2 J_m \cdot d = 2 J_m \times \frac{n}{r} \frac{dv}{dt} = \frac{2n}{r} J_m \cdot a$$

$$= \frac{2 \times 24}{1} \times 1.94 \times a = 9312.9$$

$$\rightarrow \omega_{\text{motor}} = n \times \omega_{\text{tot}}$$

$$= n \times \frac{v}{r}$$

$$= 24 \times \frac{v}{r}$$

Load side:

$$T_{\text{acc (load)}} = n \times T_{\text{acc (motor)}} = 24 \times 9312.9$$


$$= 2234.889 \rightarrow \text{for rotating elements (not the train's pulley)}$$

$$F_{\text{acc}} = \frac{2234.88}{1} = T_{\text{acc (load)}} = 2234.889$$

upward Journey $\rightarrow m = 1600 + 400 = 2000$

a) acceleration:

$$F_t = F_{\text{acc}} + F_g$$

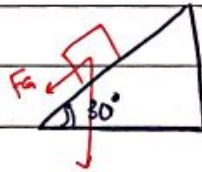

$$F_g = m \cdot g \cdot \sin 30^\circ$$

$$= 2000 \times 9.81 \times \frac{1}{2} = 9810 \text{ N}$$

$$F_t = (m \cdot a + 2234.889) + 9810$$

\downarrow
 f_{\max}

\leftarrow
 F_{acc}

$$22305.6 = (2000 a + 2234.889) + 9810$$

$$a = \frac{12495.6}{4234.88} = 2.95 \text{ m/sec}^2$$

$$t_{\text{acc(up)}} = \frac{v}{a} = \frac{5}{2.95} = 1.694 \text{ sec}$$

$$D_{\text{acc(up)}} = \frac{1}{2} \cdot a \cdot t_{\text{acc(up)}}^2 = \frac{1}{2} \times 2.95 \times 1.694^2 = 4.236 \text{ m}$$

$$P_{\text{motor}} = \left(\frac{22305.6}{24} \right) \times \underset{W_{\text{mot}}}{120.4} = 111899 \text{ W} \approx 150 \text{ hp}$$

b) constant speed (No. acceleration)

$$F_t = F_g = 9810 \text{ N}$$

D zero acc ?

$$P_m = \left(\frac{9810 \times r}{n} \right) \times \frac{120.4}{0.746} = 65.75 \text{ hp}$$

↳ upward journey (Dec)

c) $F_t = -F_{\text{acc}} - F_g$ (deceleration upward motion)

$$22305.6 = -(2000a + 2234.88a) - 9810$$

$$a = \left(\frac{22305.6 + 9810}{4234.88} \right) = -7.5836 \text{ m/sec} \rightarrow \text{dec.}$$

$t_{\text{dec(up)}} = ??$

$$v_f = v_i - a \times t_{\text{dec(up)}}$$

0 ↑ 5 m/sec

$$a = \frac{v_i}{t_{\text{dec(up)}}$$

$$t_{\text{dec(up)}} = \frac{v_i}{a} = \frac{5}{7.5836} = 0.66 \text{ sec}$$

$$D_{\text{dec(up)}} = \frac{1}{2} \cdot a \cdot t_{\text{dec(up)}}^2 = 1.65 \text{ meter}$$

$$D_{\text{constant speed}} = 50 - 4.236 - 1.65 = 44.118$$

downward journey:

$$F_t = F_{acc} - F_g$$

field weakening \rightarrow constant power profile

$$T = k \cdot \phi \cdot I$$

200% \downarrow 80%
0.5

$$W_m(\text{down}) =$$

$$V_{\text{down}} = 10 \text{ m/sec}$$

$$W_m(\text{down}) = 2 \times 120.4 = 240.4 \text{ rad/sec}$$

$$P = W \cdot T$$

200% \downarrow 100%
Constant

nsf, current \downarrow 50%

$$T_{\text{max down}} = \frac{2230.6}{2} = 1115.28 \text{ N.m}$$

$$F_{\text{max down}} = \frac{T_{\text{max down}}}{r} = 1115.28$$

$$m = 400 \text{ kg} \rightarrow F_g = 400 \times 9.81 \times \frac{1}{2} = 1962 \text{ N}$$

* Downward:

(a) Acceleration:

$$F_t = F_{acc} - F_g$$

$$11152.8 = 9 \times 400 + 2234.88 \times 9 - 1962$$

$$a = 4.977 \text{ m/s}^2$$

$$t^1 = \frac{V}{a} = \frac{10}{4.977} = 2.018 \text{ sec}$$

$$D_1 = \frac{1}{2} a t^2 = 10.05 \text{ m}$$

(b) Deceleration:

$$F_t = F_{acc} + F_g$$

$$11152.8 = -(9 \times 400 + 2234.88 a) + 1962$$

$$a = -3.488 \text{ m/sec}^2$$

$$t^2 = \frac{V}{a} = \frac{10}{3.488} = 2.867 \text{ sec.}$$

$$D_2 = \frac{1}{2} a t^2 = 14.34 \text{ m}$$

(c) Constant speed:


$$F_t = F_g$$

$$D_3 = D - D_1 - D_2$$

$$= 50 - 14.34 - 10.05 = 25.61 \text{ m}$$

$$t_{\text{correspond}} = \frac{25.61}{10} = 2.561 \text{ sec}$$

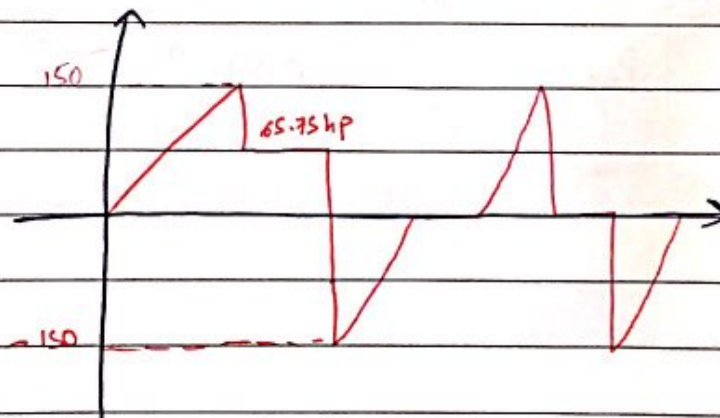
$$P_m = F \times V = 1962 \times 10 = 19.62 \text{ kw} \rightarrow 26.3 \text{ hp}$$



* RMS Horse Power


RMS : kW

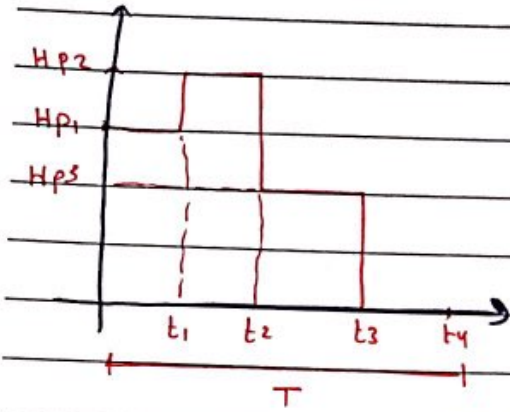Assume power duty cycle of the shape below



$$\text{RMS (HP)} = \sqrt{\frac{t_1 \text{HP}_1^2 + (t_2 - t_1) \text{HP}_2^2 + (t_3 - t_2) \text{HP}_3^2 + (t_4 - t_3) \times 0 + \dots}{t_3 + (t_4 - t_3)k}}$$

k: related to ventilation ; $k \geq 1$

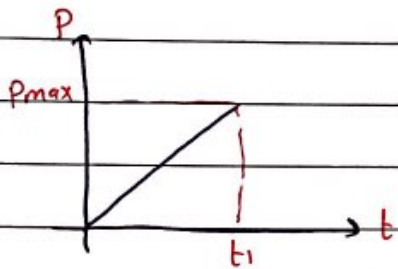

$$P(t) = P_{\max} \frac{t}{t_1}$$


RMS HP = ?!

$$\begin{aligned} P_{\text{rms}} &= \sqrt{\frac{1}{t_1} \int_0^{t_1} P_{\max}^2 \cdot \left(\frac{t}{t_1}\right)^2 dt} \\ &= \sqrt{\frac{P_{\max}^2}{t_1^3} \left[\frac{t^3}{3} \right]_0^{t_1}} \\ &= \sqrt{\frac{P_{\max}^2 \cdot t_1^3}{3 t_1^3}} \end{aligned}$$

$$P_{\text{rms}} = \frac{P_{\max}}{\sqrt{3}} = 0.577 P_{\max}$$

Case	hp	time	hp ² × t	rms hp = $\sqrt{\frac{\sum P^2(n) t_n}{T}}$
up acceleration	150	1.694		
up constant speed	65.75	8.823		
up deceleration	150	0.659		
unloading		5		
down acceleration	26.3	2.01		
down constant speed	150	2.561		
down deceleration		2.868		

* Converters:

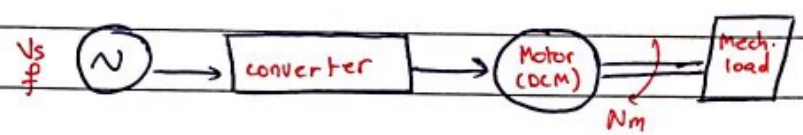

• Supply ⇒

- Vs & f are fixed
- 240 V/ph 50 Hz
- 110 V/ph 60 Hz

Motor V_{rated} 400 V

Supply 240 V_{rms}, 50 Hz

converter rectifier / single Ph or 3-phase.

Single phase rectifier:

$$V_{av}(\text{Max}) = \frac{2V_m \cos 0^\circ}{\pi} = \frac{2 \sqrt{2} \times 260}{\pi} = 216 \text{ V}$$

(α=0°)

3 phase rectifier:

$$V_{av}(\text{max}) = \frac{3 \sqrt{3} V_m \cos \alpha}{\pi} = \frac{3 \times \sqrt{3} \times \cos 0}{\pi} \times 240 \sqrt{2} = 561.3 \text{ V.}$$

a transformer is needed to transform 216 V to 400 V.

Sunday 17/11/2019

Converters for DC Drive:

(A) Rectifiers (controlled)

single phase or 3 ϕ .

(B) choppers (DC to DC)

of phases: (load power)

① $P_o < 2 \text{ kW}$ \rightarrow single-ph is almost a must.
 \downarrow
load power

② $2 \text{ kW} < P_o < 5 \text{ kW}$ \rightarrow Preferred to be 3-ph, but single phase is possible.

③ $P_o > 5 \text{ kW}$ \rightarrow 3-ph is almost a must.

* supply / load voltage.

$$V_o(\text{av}) = f(V_s) = \frac{2V_m}{\pi} = \frac{2\sqrt{2}}{\pi} V_s(\text{rms}) \approx 200 \text{ V}$$

$$V_o(\text{av})_{3\text{ph}} = \frac{3\sqrt{3}\sqrt{2} V_s(\text{rms})}{\pi} = \frac{3\sqrt{6}}{\pi} V_s(\text{rms}) / \text{ph} = 500$$

$V_s(\text{rms})$: per phase.

$$I = \frac{P}{V_{\text{av}}} = \frac{2000}{200} = 10 \text{ A}$$

$$I_{\text{single}} = \frac{5000}{200} = 25 \text{ A}$$

$$I_{3\text{ph}} = \frac{5000}{500} = 10 \text{ A}$$

DRIVE

@ load voltage

ex: $V_{rated(DC) motor} = 230V$

$V_o(av)_{1\phi} = 200 \rightarrow$ not sufficient

solution: ① use step up transformer $a = 200/230$

② 3-ph rectifier

$V_o(av) = 514 \approx 500$

This voltage is sufficient but a rectifier should run at high firing angle that generates 230V, the system will suffer from the harmonics and ripple and power factor.

$\propto \uparrow$ PF \downarrow

\rightarrow in this case ($V_{load} \ll V_o(av)_{max. rectifier}$) , use a step-up transformer.

- about 20% tolerance is acceptable.

* Converter Selection:

Selected type of converter.

if DC voltage is available : use choppers.

ex: existed DC generator or PU systems.

if not \rightarrow $\begin{cases} \text{choppers} \\ \text{controlled rectifier.} \end{cases}$


Tuesday 19/11/2019

* Converter Selection:

Controlled rectifiers or choppers.

Voltage & power capability are both in favor of rectifiers (using SCRs) rather than choppers (using transistors).

* The type & requirements of load:

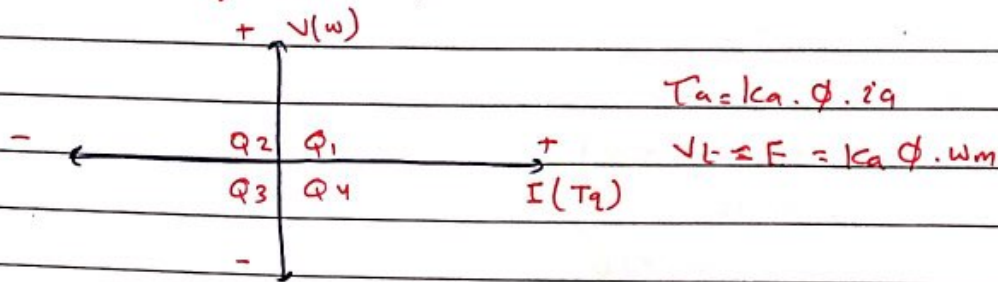

of quadrants:

- (a) $V^+, I^+ \rightarrow Q1$
- (b) $V^+, I^- \rightarrow Q2$
- (c) $V^-, I^- \rightarrow Q3$
- (d) $V^-, I^+ \rightarrow Q4$

* Can a single rectifier work in Q1? yes.

" " " " " " = Q2? Never, thyristors can't have a reversed current.


" " " " " " = Q3? Never runs at negative voltage when $\alpha > 90^\circ$, but current negative no.

" " " " " " = Q4? yes, $\alpha > 90^\circ$.


* for running in 4 quadrants, we need another converter that is possible to run in Q2, Q3.

when the two converters are connected to run together, the equivalent converter is known as the Dual converter.

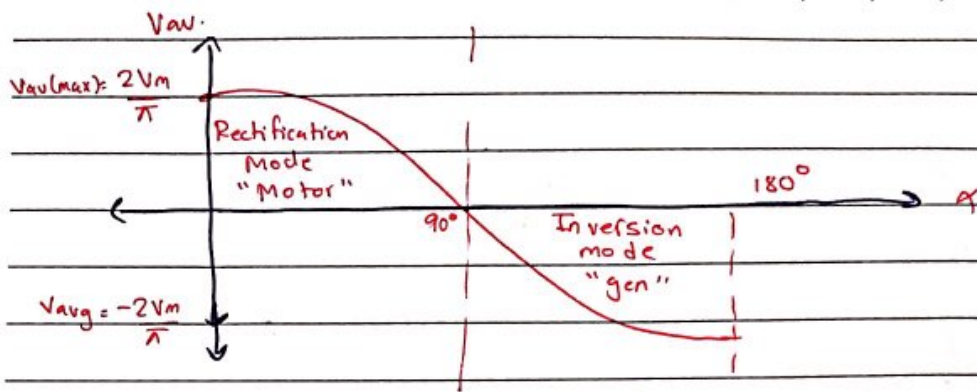* A single converter (rectifier) can run in Q1 & Q4 in a drive system.
↖ for motoring
↘ for plugging.



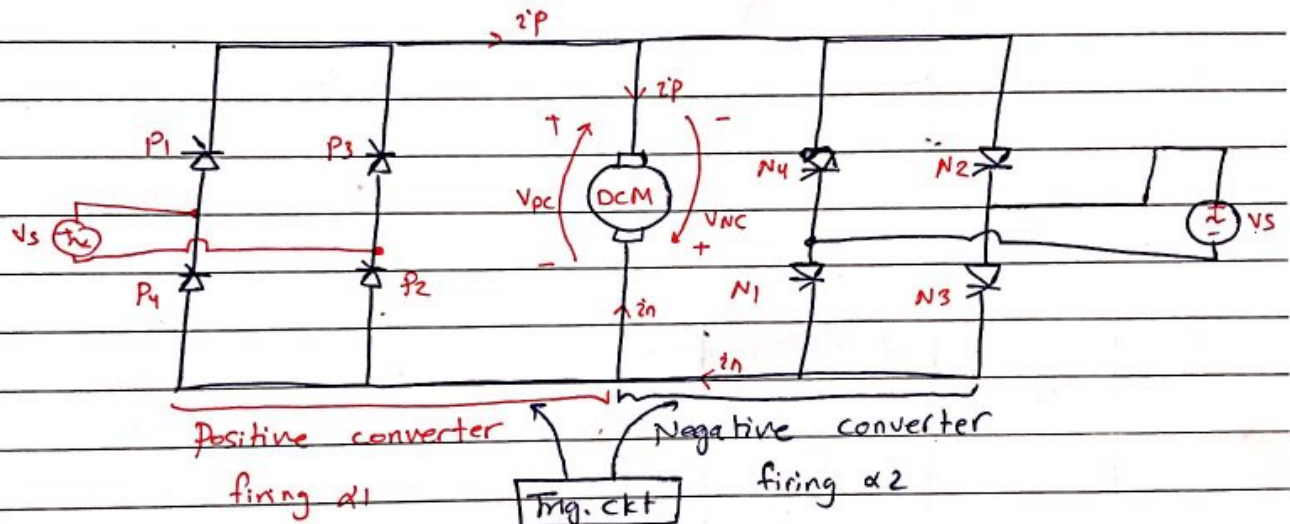Dual converters are required for reversible variable-speed DC Drive.



$$V_{avg} = \frac{2V_m}{\pi} \cos \alpha$$

$$PC: \alpha = \alpha_1$$

$$NC: \alpha = \alpha_2$$


$$V_{pc} = \frac{2V_m}{\pi} \cos \alpha_1$$

$$V_{nc} = \frac{2V_m}{\pi} \cos \alpha_2$$


$$V_{PC} = -V_{NC}$$

$$\frac{2V_m}{\pi} \cos \alpha_1 = -\frac{2V_m}{\pi} \cos \alpha_2$$


$$\alpha_1 + \alpha_2 = 180^\circ$$

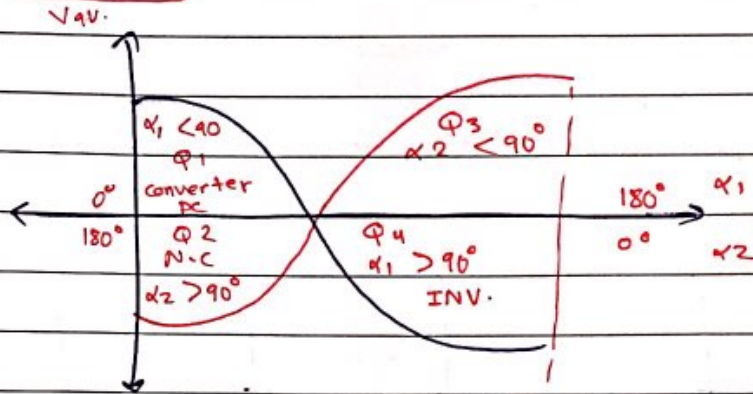

Thursday 21/11/2019

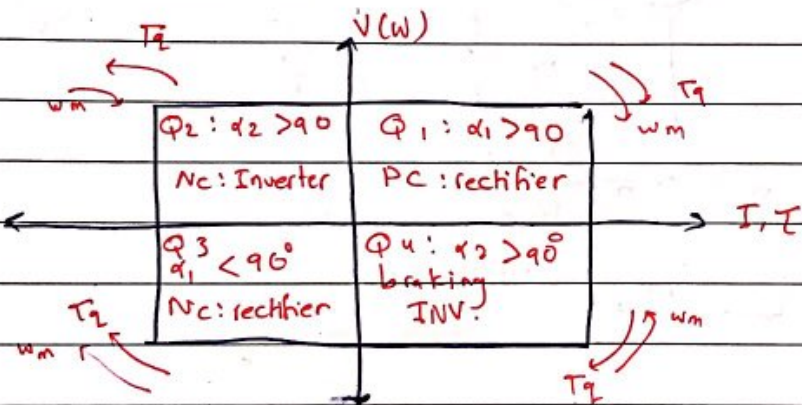

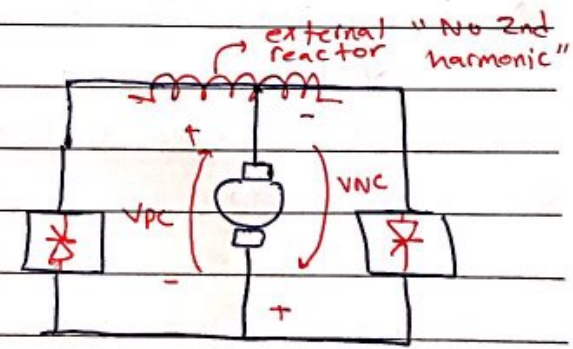- Q1: motoring action
- Q2: Inversion Act generation Act
- Q3: motoring action
- Q4: braking inversion




* Dual converters Modes!

- ① without circulating current.
- ② with circulating current

$$\alpha_1 + \alpha_2 = 180$$

$$V_{o1}(\text{avg}) = -V_{o2}(\text{avg})$$
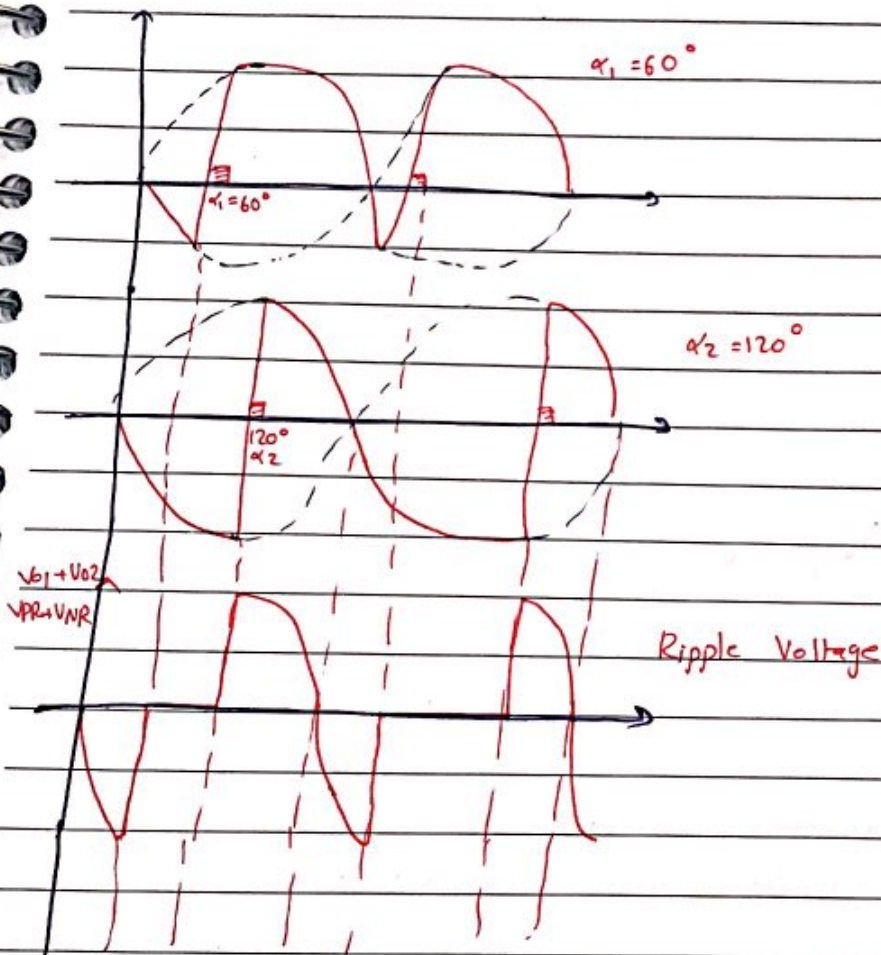
$$\alpha_1 = 60^\circ, \quad \alpha_2 = 120^\circ$$



* So an external reactor is added in case of circulating current mode.

① without circulating current:

a) The triggering of PC SCRs & NC SCRs are separate (No overlapping) with a separation time of (10-20)msec. when PC SCRs are triggered, NC SCRs aren't triggered.

Result : No circulating current.

b) one single triggering circuit is enough to control both converters.

② with circulating current:

Ⓐ both converters are simultaneously triggered but with $\alpha_1 + \alpha_2 = 180^\circ$.

which implies that two separate triggering circuits are required.

Ⓑ a circulating current flows between the two converters due to the ripple voltage. To reduce this current an external reactor is added to the system, this will add to the cost, PF, η , weight of the system.

↳ more expensive ↳ lower PF ↳ lower η ↳ more weight & space requirements.

Ⓒ advantage: No current cut-off, simpler control circuit (not cheaper).

* To select proper converter (In terms of controllability -- uncontrolled, fully controlled, semi controlled).

uncontrolled: just to run a motor at a certain fixed loading condition. (No braking, No speed control, No direction) reversing.

fully-controlled: when 4-quadrant or two quadrant operation is required, speed control, direction control, --- Reg braking.

semi-controlled: only positive voltage (rectified) is possible so; No regenerative braking, a speed control is possible in one quadrant.

→ better harmonics on load.

→ better load current waveform.

Sunday 24/11/2019

Semi-controlled \rightarrow only V^+ , only I^+ \rightarrow $\phi 1$


Semi-controlled dual converter $\rightarrow V^+$ only $\rightarrow I^+, I^- \rightarrow \phi 4, \phi 2$


In all rectifier circuits, I_{load} (motor current) is assumed to be ripple free.

L_a is large enough (either by motor design or by adding external L in series with motor armature)
(Assuming that response speed isn't critical)

In this case, the system always operates in CCM.


(a) Single phase F.W.R fully controlled.

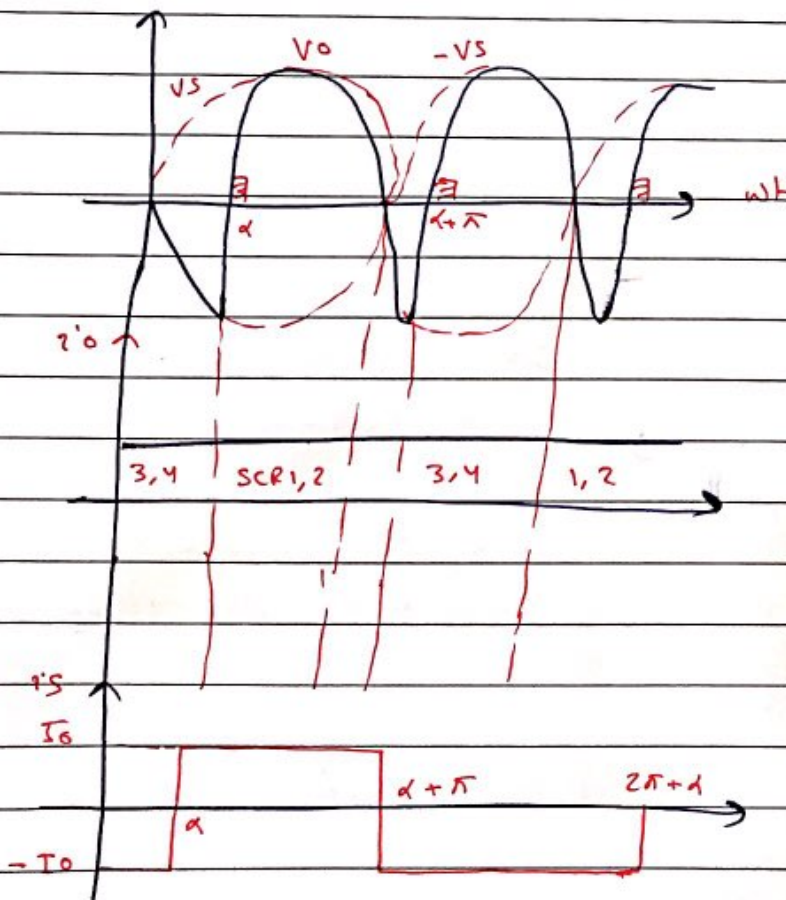

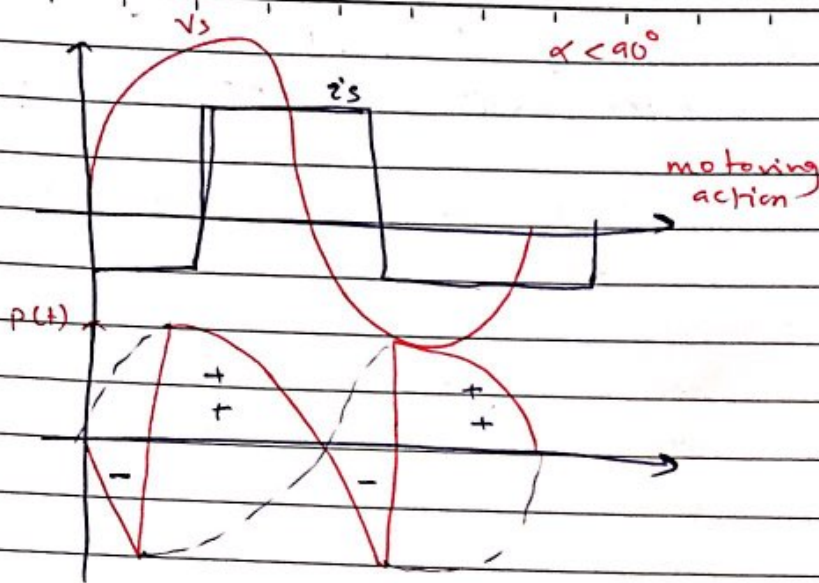


$$V_o(\text{avg}) = \frac{2V_m \cos \alpha}{\pi}$$

$$P_{in}(\text{avg}) = +$$

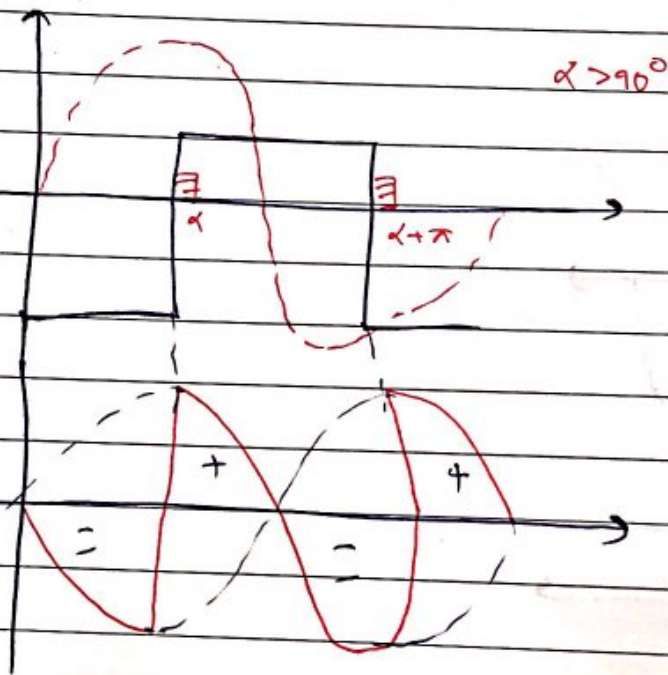


④ $V_o(\text{avg})$ is neg
 $P(\text{avg}) = -$

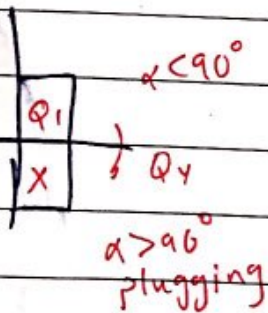
Drive with plugging: only two modes (Q) \rightarrow (Q₁, Q₄)




(b) Semi-controlled f.w.R

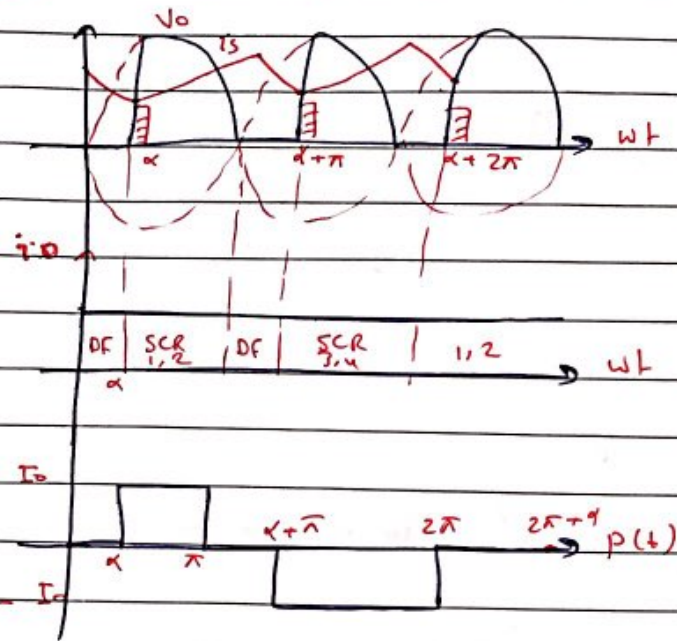

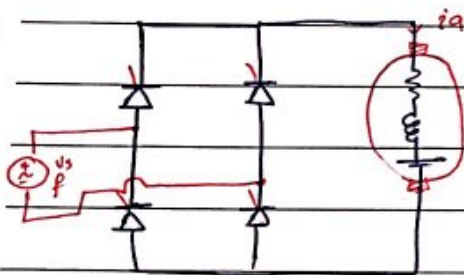H.W: 2φ Rectifier $L_a \rightarrow \infty$, $\alpha > 90$, $\alpha < 90$
 v_o , i_u , i_n , i_c



Tuesday 26/11/2019

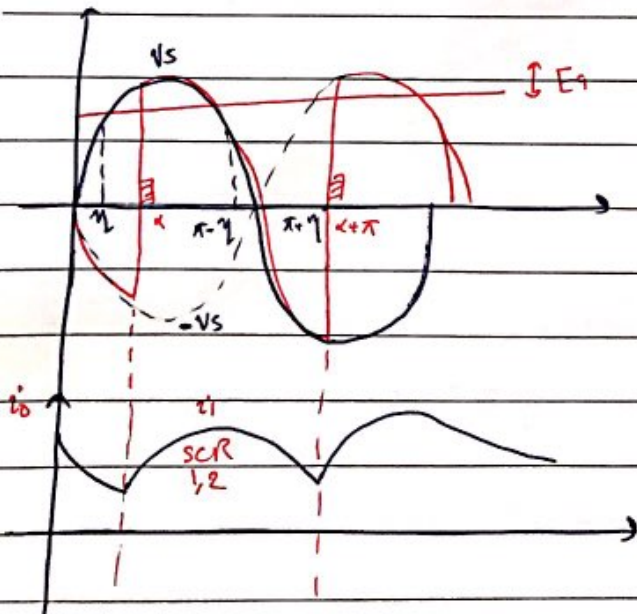

$$E_a = k_a \cdot \phi \cdot \omega_m$$

to find $\mu \rightarrow$

$$E_a = V_m \sin \mu$$

$$\mu = \sin^{-1} \frac{E_a}{V_m}$$

$$V_s = E_a + i \cdot R + L \frac{di}{dt}$$

$$i = I_m \sin(\omega t - \phi) - \frac{E_a}{R} + A e^{\rho \omega t}$$

Icc at $\omega t = \alpha$, $i_1 =$

$$I_1 = I_m \sin(\alpha - \phi) - \frac{E_a}{R} + A e^{-\rho \alpha}$$

$$A = \left[I_1 + \frac{E_a}{R} - I_m \sin(\alpha - \phi) \right] e^{-\rho \alpha}$$

$$i = I_m \sin(\omega t - \phi) - \frac{E_a}{R} \left[I_1 + \frac{E_a}{R} - I_m \sin(\alpha - \phi) \right] e^{-\rho \alpha} \cdot e^{-\rho \omega t}$$

Fcc at $\omega t = \alpha + \pi$, $i_1 = I_1$

$$I_1 = I_m \sin(\pi + \alpha - \phi) - \frac{E_a}{R_a} + \left[I_1 + \frac{E_a}{R_a} - I_m \sin(\alpha - \phi) \right] e^{-\rho \alpha} e^{\rho(\pi + \alpha)}$$

$$I_1 - I_1 e^{\rho \pi} = -I_m \sin(\alpha - \phi) - \frac{E_a}{R_a} + \frac{E_a}{R_a} e^{\rho \pi} - I_m \sin(\alpha - \phi) e^{\rho \pi}$$

$$I_1 (1 - e^{\rho \pi}) = -\frac{E_a}{R_a} (1 - e^{\rho \pi}) - I_m \sin(\alpha - \phi) [1 + e^{\rho \pi}]$$

$$I_1 = -\frac{E_a}{R_a} - I_m \sin(\alpha - \phi) \cdot \left[\frac{1 + e^{\rho \pi}}{1 - e^{\rho \pi}} \right] \quad \text{--- } \otimes$$

given $N_a \rightarrow \omega_m = \frac{2\pi N_a}{60}$

$$E_a = k \cdot \omega_m$$

$$k = \frac{E_a \text{ (rated)}}{\omega_m \text{ (rated)}}$$

$$I_m = \frac{V_m}{Z}$$


$$Z = \sqrt{R_a^2 + \omega L_a^2} \quad \text{--- } \otimes$$

$$\phi = \tan^{-1} \frac{\omega L_a}{R_a}$$

$$\rho = -\frac{1}{\tan \phi} = -\cot \phi \rightarrow -\frac{R_a}{\omega L_a}$$

* critical operation between CCM & DCM, $I_1 = 0$

Write a report:

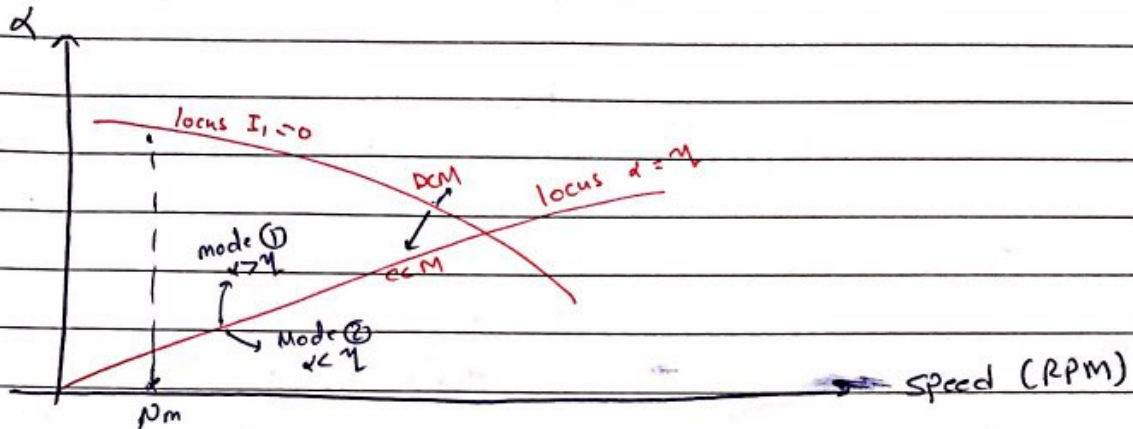

change speed & find α value from I_1 equation (*)

$$V_o(av) = \frac{2V_m}{\pi} \cos \alpha$$

$$I_o(av) = \frac{V_o(av) - E_a}{R}$$

$$I_o(av)_{st} = \frac{V_o(av) - 0}{R_a} = \frac{V_o(av)}{R_a} \text{ direct}$$

to start at $I_{st} \approx 200\% I_{rated}$


$$I_{st} = 2 I_{rated} \frac{V_o'(av)}{R_a}$$

& we find d_{st}
 speed $\uparrow \rightarrow \alpha \downarrow$

Thursday 28/11/2019

Ex: H.W: $V_o(av) = 3 \sqrt{3} V_m \cos \alpha$
 sol. ccm. I_a is ripple free.

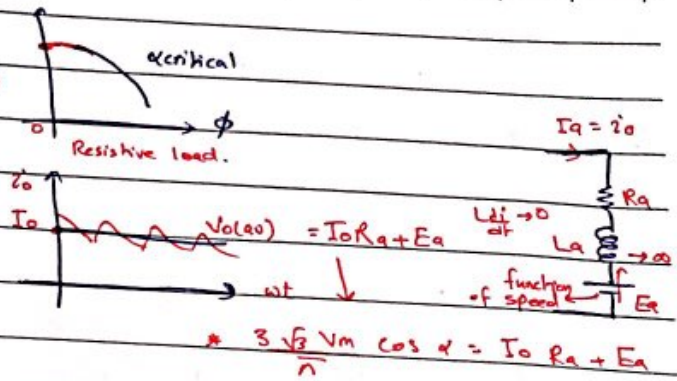$\alpha > 90^\circ \rightarrow -$
 $\alpha < 90^\circ \rightarrow +$



$\omega_m = \frac{2\pi \times \text{rpm}}{60}$ rad/sec

$V_r = (E_a(r) + I_a(r) \times R_a)$

$E_a(r) = V_r - I_a(r) \times R_a$

$K_a \cdot \phi = E_a(r) \rightarrow \text{rated}$

$\omega_{mech}(r)$

at any speed $\omega_m \rightarrow E_a = K\phi \times \omega_m$

$T_d = K_a \cdot \phi \times I_a(av)$


$T_d = T_{\text{shaft}} + T_{\text{rotational losses}}$

Quiz on Sunday.

$P_{fin} = I_o^2 R_a + I_o E_g$

3 Vs ph (rms) & Is ph (rms)

$I_o \sqrt{\frac{2}{3}}$ Peak/phase

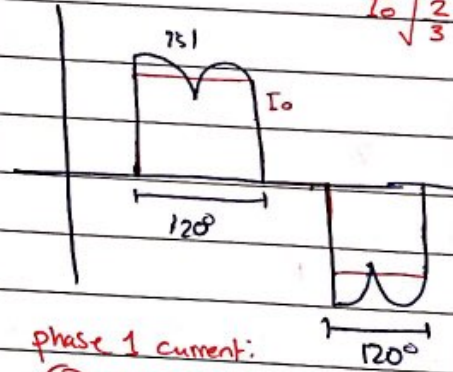

phase 1 current:

⊕ when SCR1 running.

⊖ when SCR4 running.

#1 Solution: $\alpha = 60^\circ, \alpha < 90^\circ$

SCR1 $\rightarrow 30 + 60 = 90^\circ \xrightarrow{+120^\circ} 210^\circ$


2 $\xrightarrow{+60^\circ} 150^\circ \rightarrow 270^\circ$

3 $210^\circ \rightarrow 330^\circ$

4 $270^\circ \rightarrow 390^\circ \rightarrow 30^\circ$

5 $330^\circ \rightarrow 480^\circ \rightarrow 90^\circ$

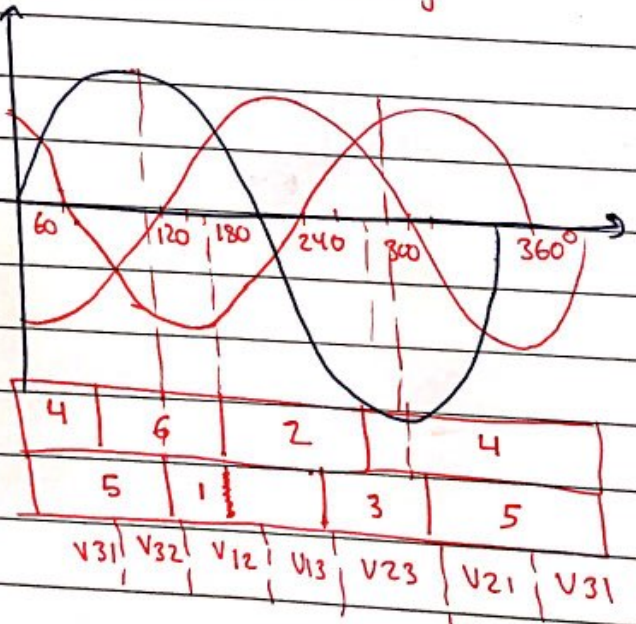6 $390^\circ \rightarrow 30^\circ \rightarrow 150^\circ$



Tuesday 3/12/2019

* Motor 230V, 5 Hp, 850 RPM, 20A, $R_a = 1.19 \Omega$, $L \rightarrow \infty$, $P_{rot} = \text{function of sp speed}$
 Supply: 240V, 50 Hz, 1 ϕ converter: 1 ϕ fully controlled rectifier (Linear (dctm))

Q1: does the supply's converter capable of supplying the motor at rated conditions?


$$V_{o(av)} = \frac{2 V_m \cos \alpha}{\pi} = \frac{(2 \times 240 \sqrt{2})}{\pi} \cos 0^\circ = 216.076 \text{ V}$$

$\hookrightarrow \alpha = 0^\circ$ (to get max. possible voltage).

Since $V_{o(av)}(\text{load } 230\text{V}) > V_{o(av)}(\text{max } 216.076)$

\therefore the supply's converter isn't capable of supplying the motor at rated conditions.

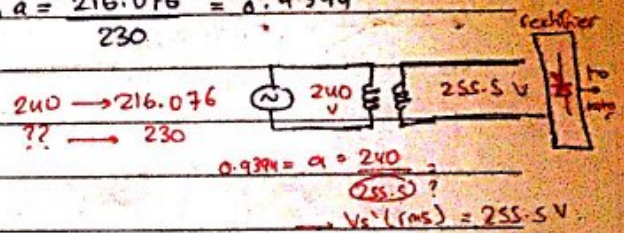Solution: use a transformer (step-up); $a = \frac{216.076}{230} = 0.9394$



^{rated}
 $E_a(r) = V_t(r) - I_a(r) \times R_a$
 $= 230 - 20 \times 1.19 = 206.2 \text{ V}$

$$k_a \phi = \frac{E_a(r)}{\omega_m(r)} = \frac{206.2}{\frac{2\pi \times 850}{60}} = 89.01 \text{ rad/sec}$$

$$\therefore \frac{E_a(r)}{\omega_m(r)} = \frac{206.2}{89.01} = 2.3 \text{ V}\cdot\text{sec/rad}$$

$T_{d1} = k_t \phi \cdot I_a(r) = 2.3 \times 20 = 46 \text{ Nm}$ } 2 ways to find developed torque.

$$T_{d1}(r) = \frac{E_a(r)}{\omega_m(r)} \times I_a(r) = \frac{206.2}{89.01} \times 20 = 46 \text{ Nm}$$

$P_{out} = P_{developed} - [P_{rotational}] \rightarrow P_{rot}(r) = (206.2 \times 20) - 3730 = 394 \text{ W}$
 \hookrightarrow rated speed only = 850 RPM

$$P_o = 5 \times 746 = 3730 \text{ W}$$

$$P_{rot}(\omega_m) = P_{rot}(850) \times \frac{N_m}{N_m(r) \text{ or } \omega_m}$$


Q2:

How much power can the motor supply at rated speed without transformer?

$$V_t = 216.076 = \omega_m(r) \times K_a \phi + \frac{E_a(r)}{K_a \phi} R_a$$

↳ V_t (AV) without transformer.
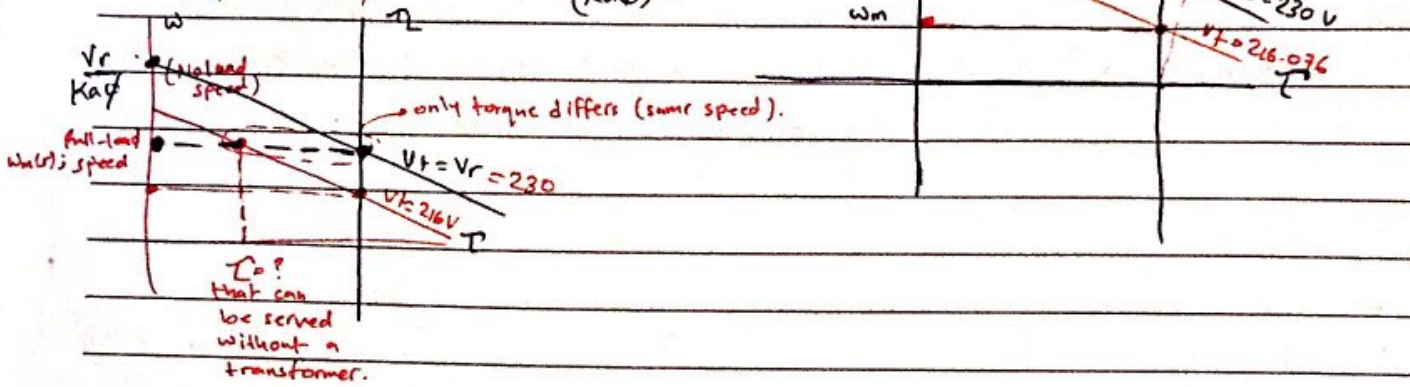
$$\omega_m = \frac{V_r}{K_a \phi} - \frac{I_a R_a}{K_a \phi} = \frac{V_r}{K_a \phi} - \frac{R_a}{(K_a \phi)^2} T_a$$



$$216.076 = 206.2 + I_a R_a + 1.19 I_a$$

$$I_a = 8.3 \text{ A} \text{ instead of } 20 \text{ A}$$

$$P_a = P_d = K_a \phi \times I_a = 2.3 \times 8.3 = 19.09 \text{ Nm}$$

$$P_a = T_a \cdot \omega_m(r) = 1711.3 \text{ Watts}$$

$$P_{rot} = P_{rot}(850) = 394$$

$$P_{out} = 1711.3 - 394 = 1317.3 \text{ Watt} = 1.7658 \text{ hp}$$



$$\text{loading ratio} = \frac{1.7658}{5 \text{ hp}} = 35.3\%$$

Q3: if running at rated conditions, (transformer is used).


$$V_{supply} = 255.5 \text{ V rms}$$

$$V_t = V_r = 230 \text{ V}$$

$$230 = \frac{2V_m}{\pi} \cos \alpha$$

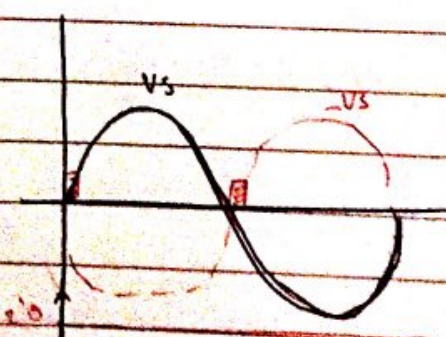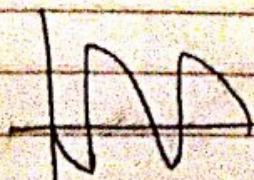

No -ve part cause $\alpha = 0^\circ$.

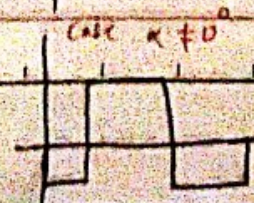

to a + losses

Ripple factor (RF) [V_o] = 48.43%

R.F (i_o) = 0

THDF (i_o) = 48.43%

P_{Fin} = DPF x DTF

= $\frac{V_o(\text{avg})}{V_o(\text{rms})} = 0.9 \text{ lag.}$


Qn: we need to do plugging.

Emf should be negative

$E_a \rightarrow I_a R_a \rightarrow V_t(r) \rightarrow \alpha$

$\omega_m = \frac{V_t}{k_a \phi} = \frac{I_a R_a}{k_a \phi}$ to find new speed


So we find above

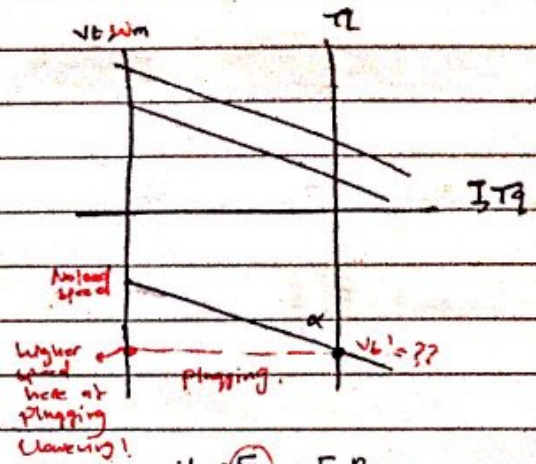

$V_t = E_a + I_a R_a$

$\downarrow -E_a$

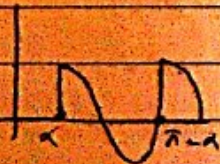$\therefore I_a \therefore \frac{2V_m \cos(\alpha)}{\pi} \rightarrow \alpha > 90^\circ$



to find ripple factor from α.



to find total harmonic distortion factor

$P_{Fin} = DTF \times DPF$ (General)

$\frac{I_2(\text{rms})}{I_1(\text{rms})}$

$\cos \phi_2$

↳ us & i fundamental.

$P_{Fin} = \frac{V_o(\text{avg})}{V_s(\text{rms})}$

(Special case of pure DC current).

inversion mode of operation (-ve Emf).

Thursday 5/12/2019

Starting of Antenna

↳ Discontinuous mode.

$$\omega_m = 0 \rightarrow E_a = 0$$

$$\therefore v_b = E_a + I_a R_a$$

↳ very low values.

$$V_{av}(\text{critical}) = \frac{2V_m \cos \phi}{\pi}$$

$$T_{\text{motor}} = \underbrace{J \frac{d\omega_m}{dt}}_{T_{\text{acc}}} + \text{Losses} + T_{\text{load}} \quad ; \quad J_{\text{total}} = J_{\text{motor}} + J_{\text{load}}$$

↳ $2J_{\text{motor}}$

$$P_{\text{rotational}} = P_{\text{in}} - P_o = P_{\text{cu}}$$

↳ $I_a^2 R_a$

$$T_{\text{rotational}} = \frac{P_{\text{rot}}}{\omega_m} \quad ; \quad T_{\text{rot}} = k \cdot \omega_m$$

↳ rotational losses
↳ viscous friction.

Past paper: Adding an external inductor to certain DC motors → comment on the statement.

go back to power electronics for relations & graphs.

$$c(n) = \frac{4 I_o \sin(-n\alpha)}{n\pi}$$


go back to check its square wave.

find rms value kw of motor.

↳ DCM relation with given α & β find $V_o(\text{avg.})$.


Final material.

* DC-to-DC (choppers) controlled Drive.

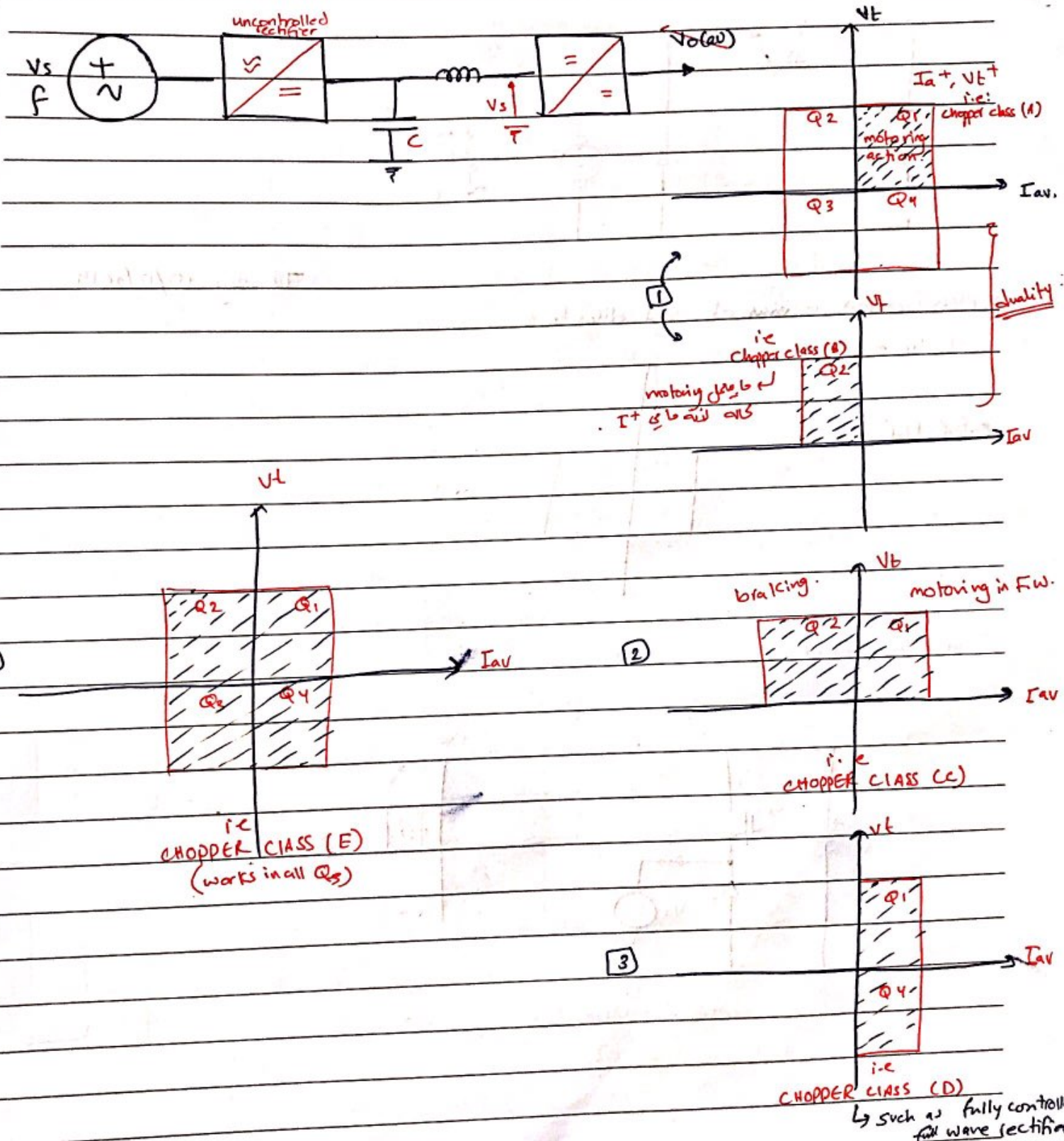

Chopper, Inverter → only transistors not thyristors.

* Chopper class (A) :

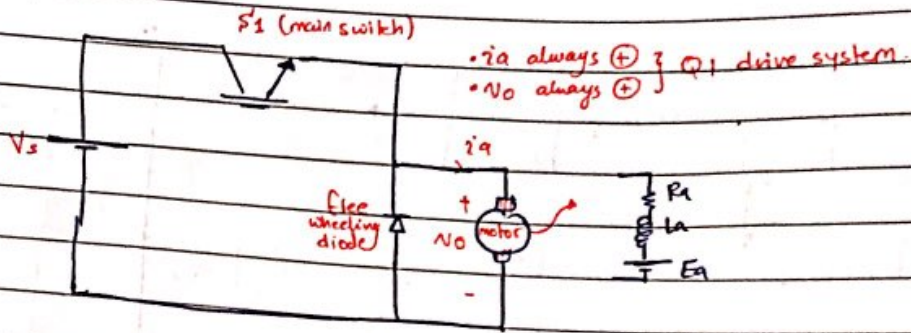


Tuesday 10/12/2019


* classification in terms of V, I directions:

4-types:

A, B, C, D, E

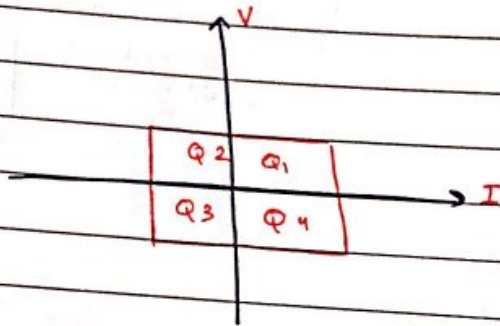


1) Type 'A' chopper.

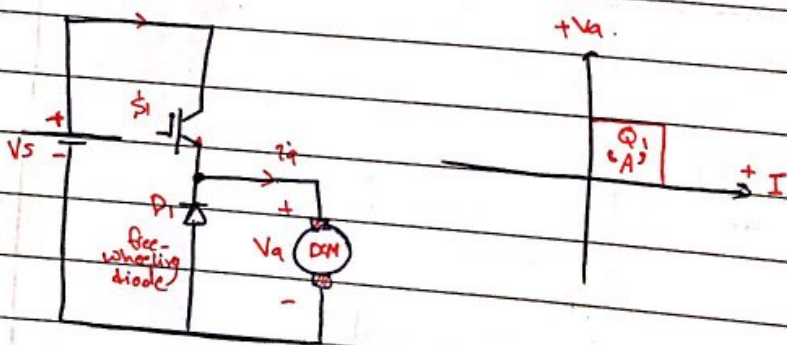

$V_a = V_t$
armature terminal

[discharging → +ve I]

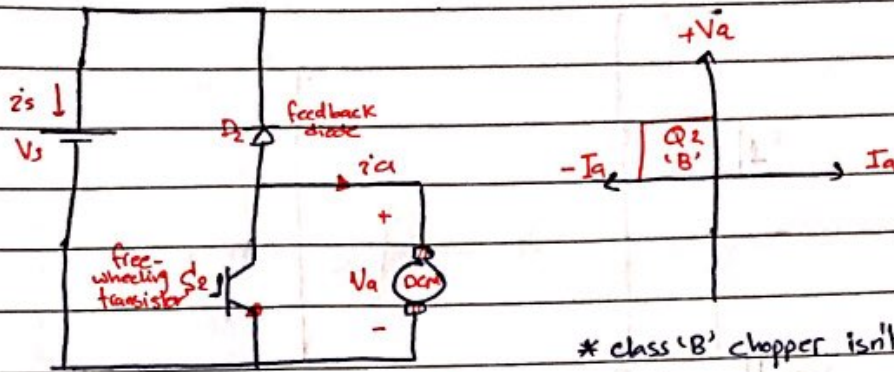② Type 'B' chopper. → it does braking so it doesn't work alone.




* class 'B' chopper isn't existing alone.

(the current will be negative)

[charging]

③ Type 'C' chopper.

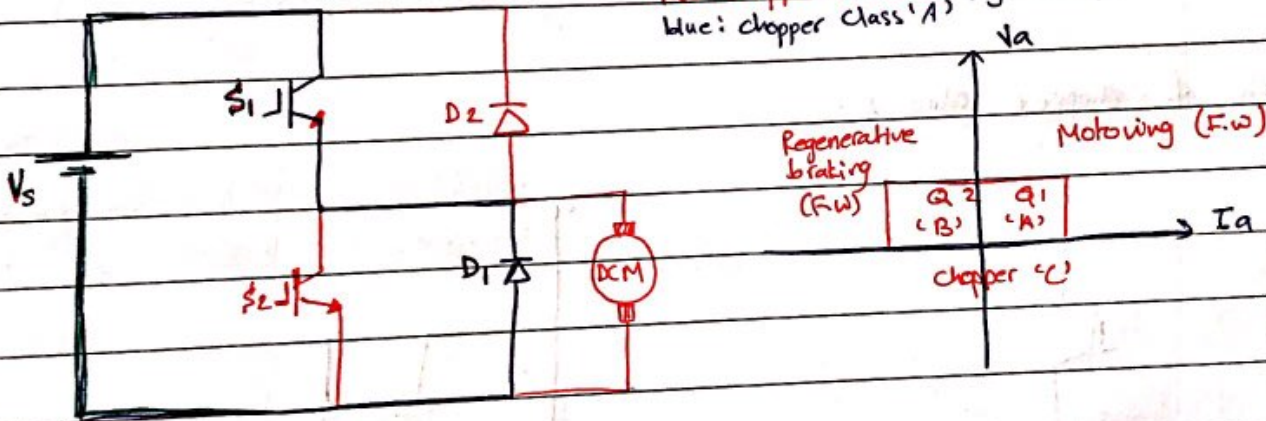


Red: chopper class 'B' + 3
Blue: chopper class 'A' + 3

Regenerative braking (F.W)


Motoring (F.W)

chopper 'C'

④ Type 'D' chopper.

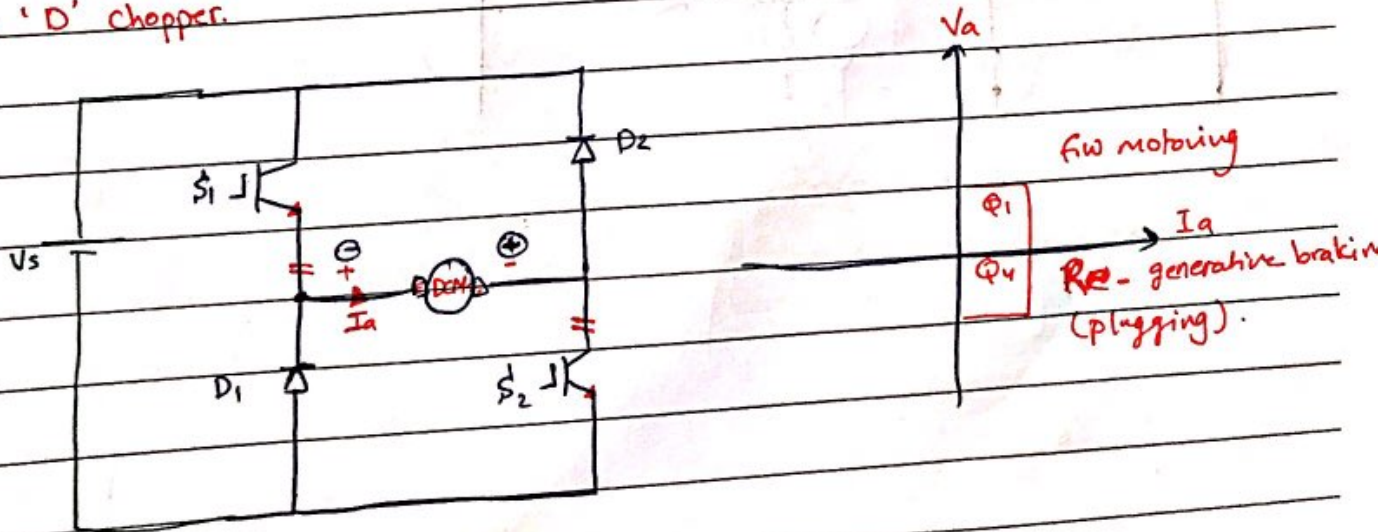



5) Type 'E' Chopper.

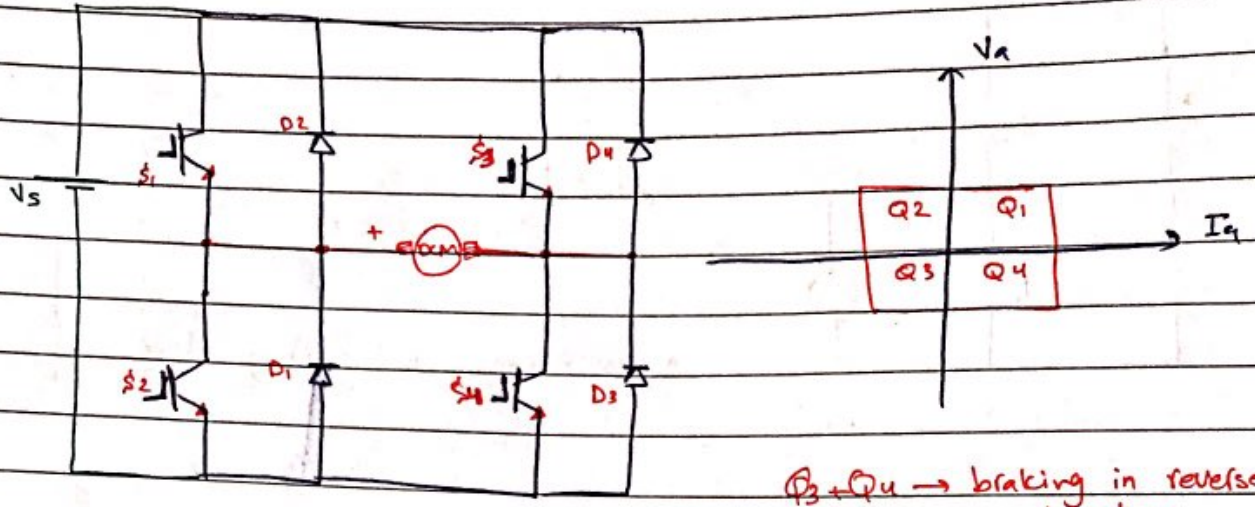

$\Phi_3 + \Phi_4 \rightarrow$ braking in reversed direction.

$\Phi_2 + \Phi_3 \rightarrow$ plugging in reversed direction.

* Analysis of chopper class A:

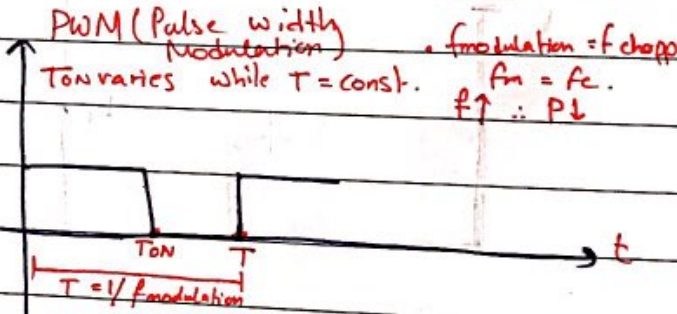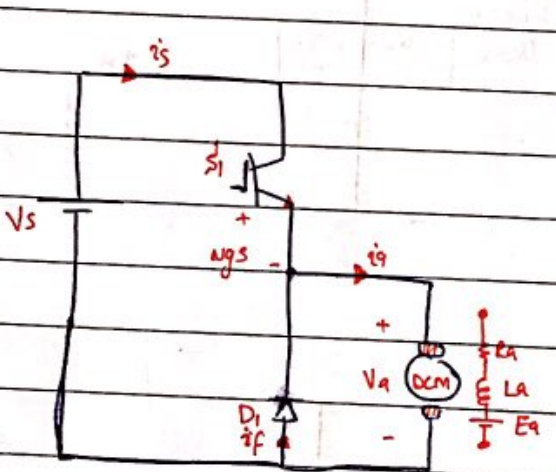



* (A) very large if we don't care about the system's control.

$\delta = \frac{T_{on}}{T} \rightarrow \delta$: modulation index

$0 \leq \delta \leq 1$
 $V_o = 0 \leftarrow \delta = 0 \quad \rightarrow \delta = 1 \leftarrow V_o = V_s$



* chopper class 'A'

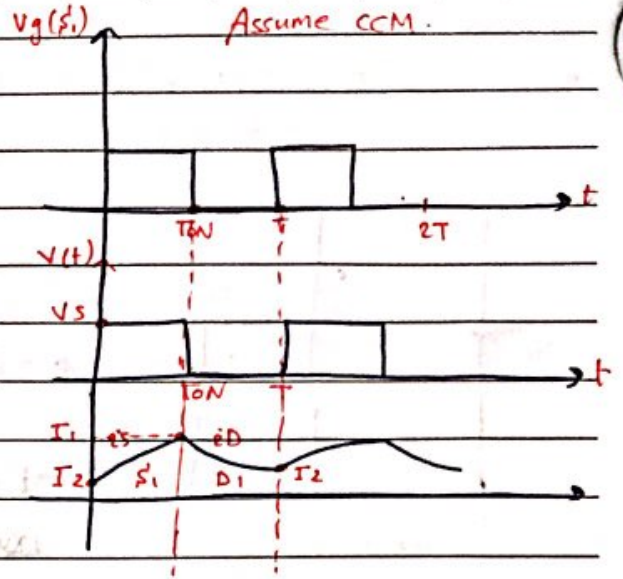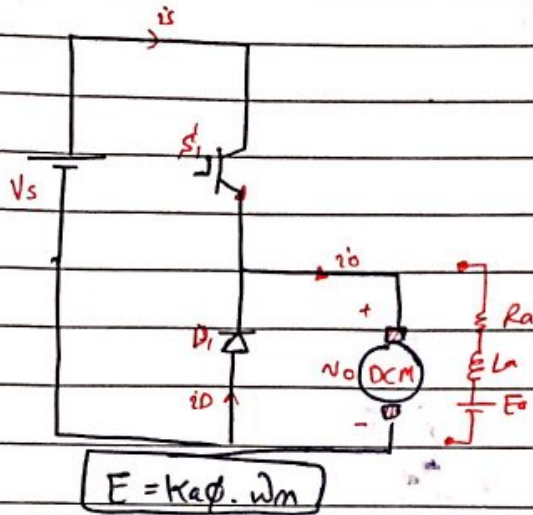

Assume CCM.

$$T = \frac{1}{f_m} = \frac{1}{f_{chopping}}$$

Assume CCM

T_{ON} → Variable

$$\delta: \text{Modulation index} = \frac{T_{ON}}{T}$$

$$0 \leq \delta \leq 1$$

$$V_o = 0 \quad \text{and} \quad L_s V_o = V_s$$

• beginning of Analysis:

$$0 \leq t \leq T_{ON}$$

$$\tau = L/R$$

$$V_o = V_s$$

$$V_s = iR + L \frac{di}{dt} + E$$

$$V_s - E = iR + L \frac{di}{dt}$$

$$i = \frac{V_s - E}{R} + A e^{-t/\tau}$$


→ A = ?? I_{cc} : where at $t=0, i = I_2$

$$I_2 = I_s - I_E + A e^{-0/\tau}$$

$$A = I_2 - I_s + I_E$$

$$i = I_s - I_E + I_2 e^{-t/\tau} - I_s e^{-t/\tau} + I_E e^{-t/\tau}$$
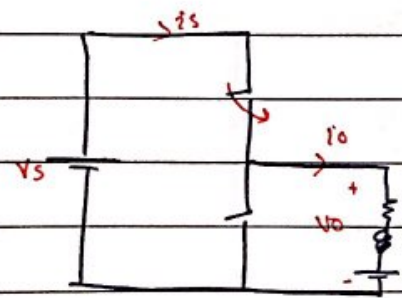
$$i_s = I_2 e^{-t/\tau} + I_s (1 - e^{-t/\tau}) - I_E (1 - e^{-t/\tau})$$




$$i_D = 0, \quad i_o = i_s$$

Fcc at $t = T_{ON}$, $i = I_1$

$$I_1 = I_s e^{-\frac{T_{ON}}{\tau}} + I_s (1 - e^{-\frac{T_{ON}}{\tau}}) - I_E (1 - e^{-\frac{T_{ON}}{\tau}}) \quad \text{--- (1)}$$

$T_{ON} = \delta \cdot T$

two unknowns, I_1 & I_2 .

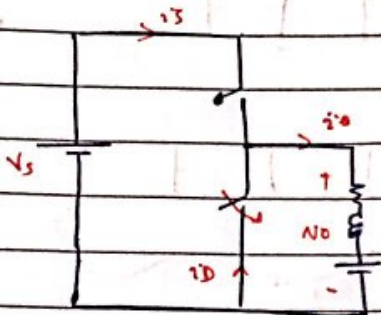

$$i_s = 0$$

$$i_o = i_D$$

$$0 = iR + L \frac{di}{dt} + E$$

$$-E = iR + L \frac{di}{dt}$$

$$i_D = -IE + Be^{-t/\tau}$$

$$\text{at } t = T_{ON} \text{ fcc. } \rightarrow i_D = I_1$$

$$I_1 = -IE + Be^{-\frac{T_{ON}}{\tau}} \Rightarrow B = (I_1 + IE) e^{\frac{T_{ON}}{\tau}}$$

$$\therefore i_D = -IE + (I_1 + IE) \cdot e^{-\frac{T_{ON}}{\tau}} \cdot e^{-\frac{t}{\tau}}$$

Fcc at $t = T$, $i_D = I_2$

$$I_2 = -IE + (I_1 + IE) e^{-\frac{T_{ON}}{\tau}} \cdot e^{-\frac{T}{\tau}} \quad \text{--- (2)}$$

Conclusion:

$$I_1 = I_s \left[\frac{1 - e^{-\frac{T_{ON}}{\tau}}}{1 - e^{-\frac{T}{\tau}}} \right] - IE$$

$$I_2 = I_s \left[\frac{1 - e^{-\frac{T_{ON}}{\tau}}}{1 - e^{-\frac{T}{\tau}}} \right] - IE$$

Critical condition:

$$I_2 = 0$$

$$T_{ON}(cr.) = \tau \ln \left[1 + \frac{IE}{I_s} (e^{\frac{T}{\tau}} - 1) \right] \quad *$$



$$\delta(cr.) = \frac{T_{ON}(cr.)}{T} \quad *$$

T_m ?? in DCM next lecture.

Sunday 15/12/2019

* DCM for chopper class 'A'

• class 'c' never works in DCM.

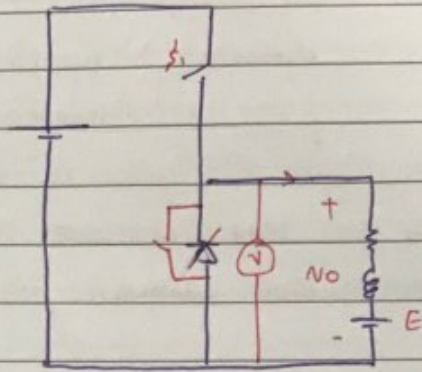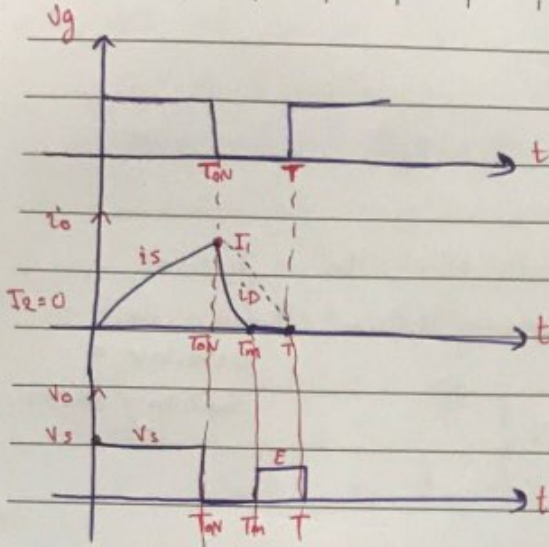

$$T_m = -T \ln \left[\frac{IE}{(IE + I_1)} \cdot e^{-\frac{T_{on}}{T}} \right] \oplus$$

Tcr ?

$$V_o(av) = \delta V_s$$

$$V_o(av)_{DCM} = \frac{1}{T} \int_0^{T_{on}} [V_s dt] + \frac{1}{T} \int_{T_{on}}^T [E dt] = \delta V_s + E(1 - \delta_m)$$

• where $\delta_m = \frac{T_m}{T}$

Voltage harmonics:

• $c(n) = \frac{2V_s}{n\pi} \sin(n\delta\pi)$; $n=1, 2, 3, \dots$ [peak amplitude for nth harmonic]

• $\phi(n) = \frac{\pi}{2} - n\delta\pi$ [displacement angle for nth harmonic]

$$V_o(t) = \delta V_s + \sum_{n=1,2,3,4,\dots} \frac{2V_s}{n\pi} \sin(n\delta\pi) \cdot \sin(n\omega t + \frac{\pi}{2} - n\delta\pi) \oplus$$

$$\phi(n) = \tan^{-1} \left(\frac{2\pi n f_{ch} L_a}{R} \right)$$

$$i_o(t) = \frac{\delta V_s - E}{R} + \sum_{n=1,2,3,\dots} \frac{2V_s}{n\pi Z(n)} \sin(n\delta\pi) \sin(n\omega t + \frac{\pi}{2} - n\delta\pi - \phi(n))$$

$$Z(n) = R + j \frac{2\pi n f_{ch} L_a}{\omega}$$

• $f_{ch} = f_m$


$$V_o(rms) = \sqrt{V_o^2(av) + \sum_{n=1,2,3,\dots} \left(\frac{2V_s}{\sqrt{2}n\pi} \right)^2 \sin^2(n\delta\pi)}$$

$$I_o(rms) = \sqrt{I_o^2(av) + \sum_{n=1,2,3,\dots} \left(\frac{2V_s}{\sqrt{2}n\pi Z(n)} \right)^2 \sin^2(n\delta\pi)}$$

* advantages:

- Much simpler analysis.
- harmonics elimination is possible & simple.
 - ↳ reduction.
- extra degree of freedom to reduce the harmonics effect, that is besides to the load inductance, the chopping frequency (up to a certain level) is an excellent solution.
 - ↳ because of switching losses.

* Chopper class 'B':

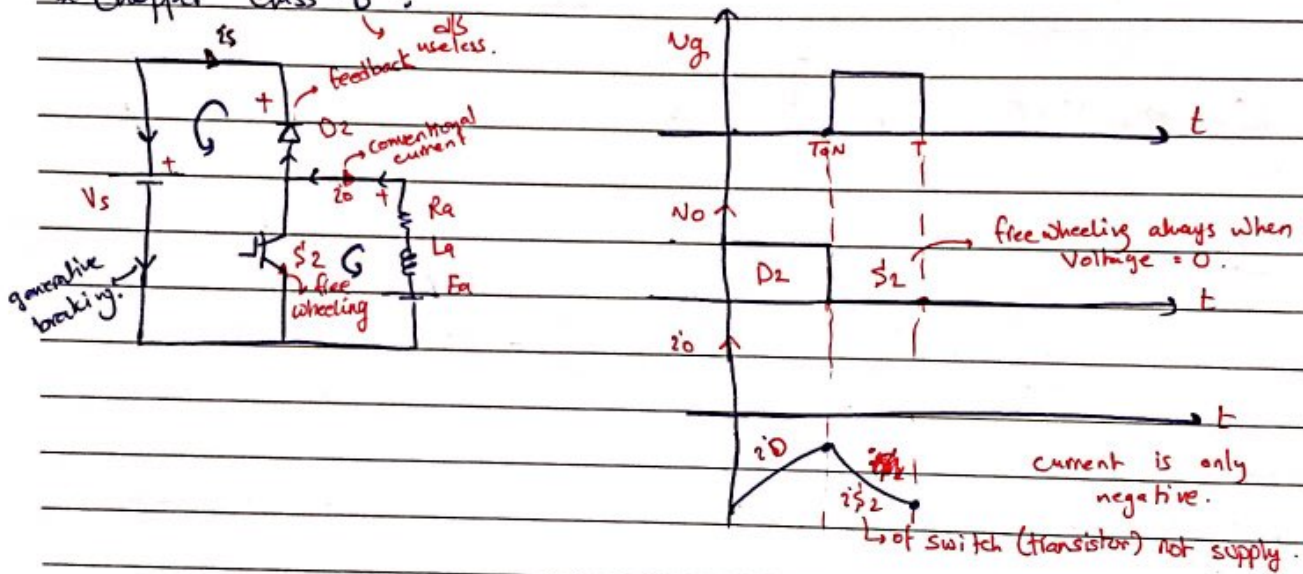

* chopper (B) can be used alone if E is coming from a DC Generator or from a PV system & in this case $E > V_s$.

* clipping if we ever get +ve current with chopper (B).



Tuesday 17/12/2019

* Analysis of chopper (B):

same equations for I_1, I_2 as Chopper (A) same analysis.

$0 < t < T_{ON}$ (D_2 is conducting) \rightarrow feedback.

$$V_s = i_D R + L \frac{di_D}{dt} + E$$

$T_{ON} < t < T$ (S_2 is conducting) \rightarrow free wheeling.

$$0 = i_{S_2} R + L \frac{di_{S_2}}{dt} + E$$

$$I_1 = I_s \left[\frac{1 - e^{-\frac{T_{ON}}{\tau}}}{1 - e^{-\frac{T}{\tau}}} \right] = I E \quad (*)$$


$$I_2 = I_s \left[\frac{1 - e^{-\frac{T_{ON}}{\tau}}}{1 - e^{-\frac{T}{\tau}}} \right] = I E \quad (*)$$

$V_o(av) = \delta V_s$, $\delta = \frac{T_{ON}}{T}$


$T_o(av) = \frac{\delta V_s - E}{R_a}$

always negative.

* chopper class 'c':

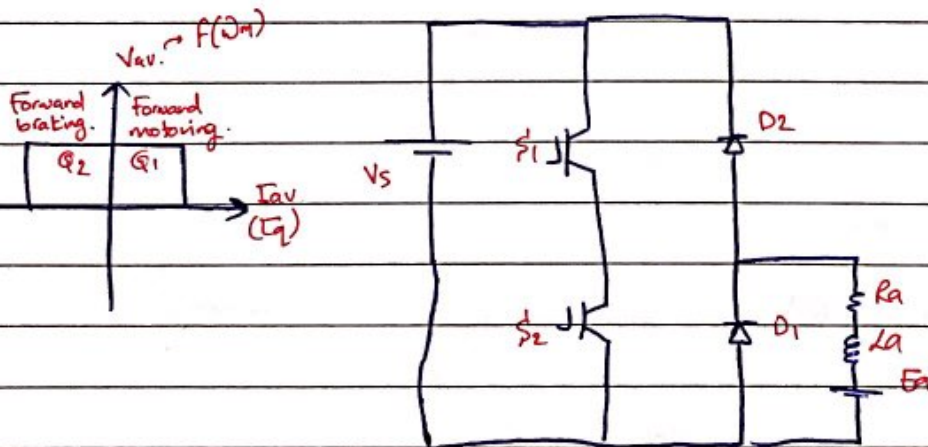

only CCM for chopper CC) NO DCM.

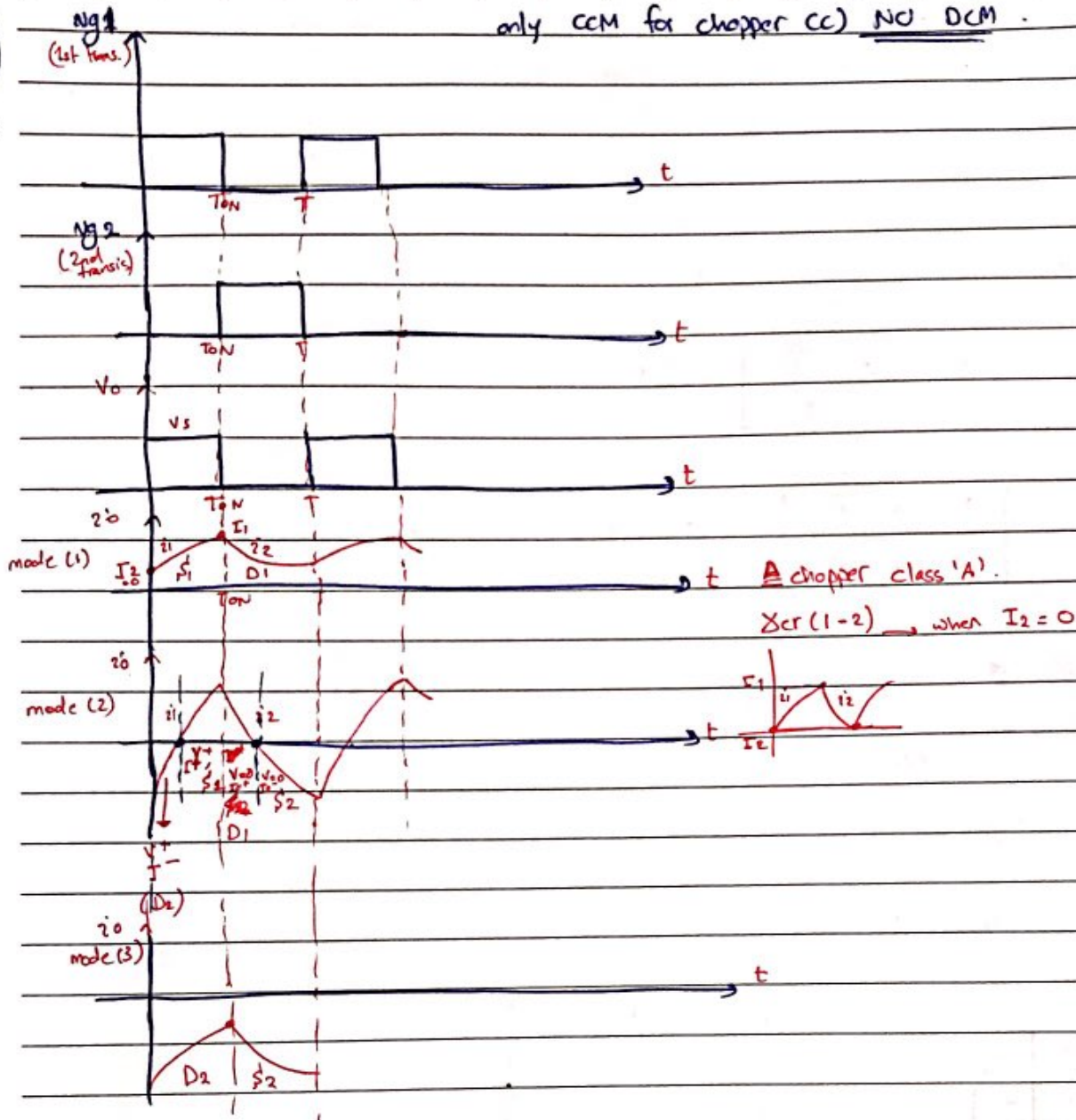

A chopper class 'A'.
 $\Delta \text{or } (1-2) \rightarrow \text{when } I_2 = 0$

$$I_{av} = \begin{cases} + \text{ always (mode 1)} \\ + \text{ or } - \text{ in mode 2} \\ - \text{ always (mode 3)} \end{cases}$$

$$I_{av} = \frac{V_o(\text{av}) - E}{R_a} ; I_{av} (+ve) \rightarrow \text{Motoring. [mode 1 and part of mode 2]}$$





$$V_o(\text{av}) = \delta V_s ; E(\text{av})$$

$\delta V_s > E \rightarrow I_o(\text{av}) +ve$, $\delta V_s = E \rightarrow I_o(\text{av}) \text{ zero}$
 \rightarrow No Tq & motor will start braking.

Thursday 19/12/2019

DRIVE

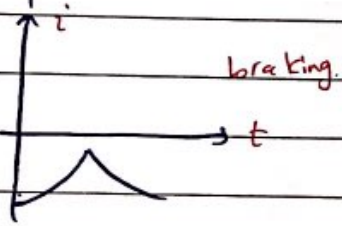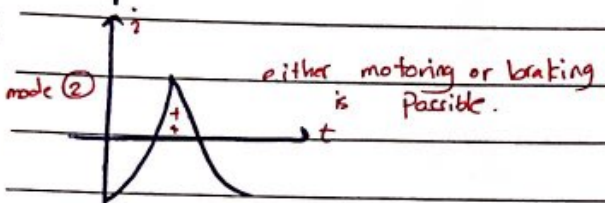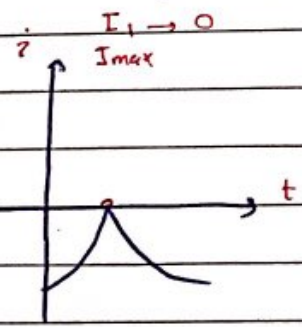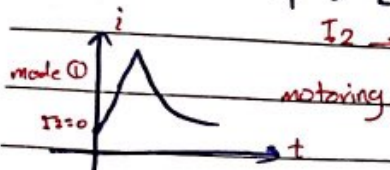* $\Delta_{cr(1 \rightarrow 2)} = \frac{E}{V_s} \ln \left[1 - \frac{E}{V_s} (1 - e^{\frac{E}{V_s}}) \right]$, $\Delta_{cr(2 \rightarrow 3)} = -\frac{E}{V_s} \ln \left[1 - \frac{E}{V_s} (1 - e^{-\frac{E}{V_s}}) \right]$



Thursday 26/12/2019

* frequency control of IM. (Major method)

• DC motor.
↓
limitations
(vibration, commutation sparks & mech. limitations)

$$\omega_s = \frac{60}{P} f \quad ; \quad 0 \leq f \leq \underline{\underline{3f_r}}$$

↳ Mechanical, limitation design.

$$V_{ph} = 4.44 N_{ph} \cdot f \cdot \phi_m$$

$$V_{ph} = k' \cdot f \cdot \phi \uparrow$$

↳ constant.

• case (A) $f < f_r$ while keeping V_{ph} constant.

The machine will experience bad saturation.

[NEVER ACCEPTED]

Solution: to vary V_{ph} by the same ratio as f ; such that $\frac{V}{f} = \text{constant}$.

• This type of control is known as: \rightarrow VVVF (variable voltage, variable freq. control).
 \rightarrow or constant flux control. (field).

• case (B) $V_{ph} = k' \cdot f \uparrow \cdot \phi \downarrow$

If, $f > f_r$; $\omega_m > \omega_m(r)$.


(V_{ph}) V_t will never be able to be increased above rated value. (ratio).

$$\frac{V_t}{f} = \frac{V_{rated}}{f_r} \quad ; \quad \frac{V}{f} = \text{constant decreasing} \downarrow$$

$$\phi = \frac{V_t}{k \cdot f} = k' \cdot \frac{V}{f} \quad ; \quad \phi \text{ reduced while } f \text{ increased.}$$


• This type of control is referred to field weakening control.

* Speed control Block:

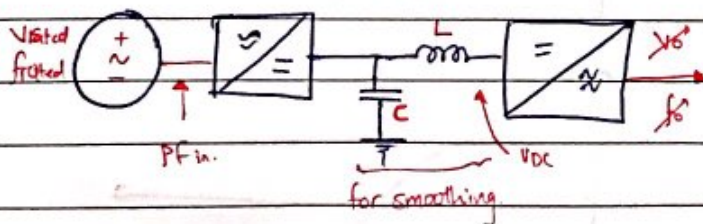

• $f_o \rightarrow$ only controlled by inverters, switching.

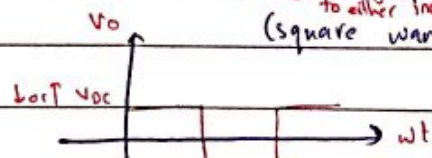• $V_o \rightarrow$ a) by using controlled rectifier to either increase or decrease V_{DC} . (square wave inverter).




side note: $PF = DPF \cdot DTF$
 both are functions of α

higher $\alpha \rightarrow$ lower PF.

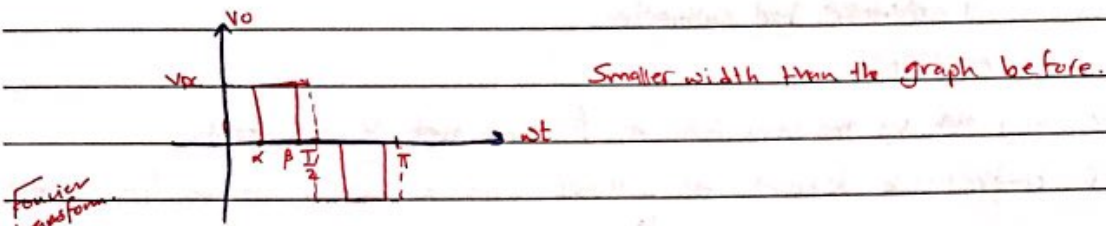b) by using uncontrolled rectifier. $\alpha=0$ leading to highest power factor.

V_o can be controlled by the inverter.

\rightarrow Pulse width modulation is to be applied.





Fourier transform

lots of harmonics so we use multi-pulse PWM.

1. Uniform PWM.
2. Sinusoidal PWM.

T_{ch} : chopping
 T_m : modeling.

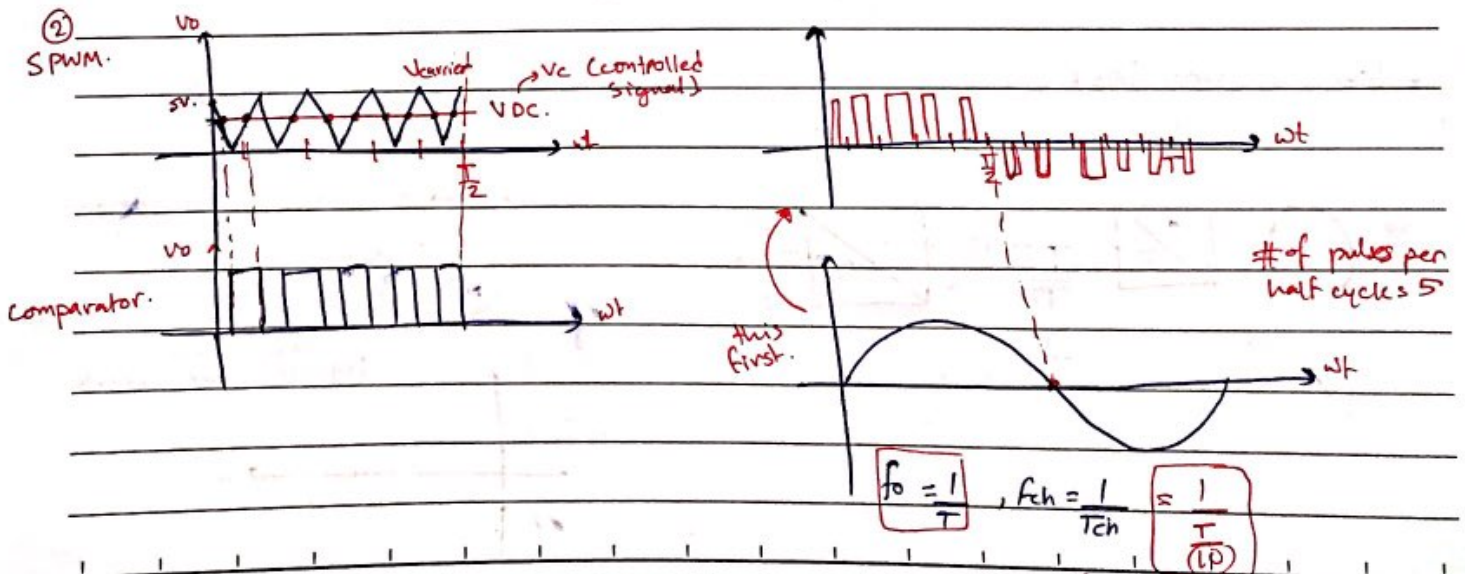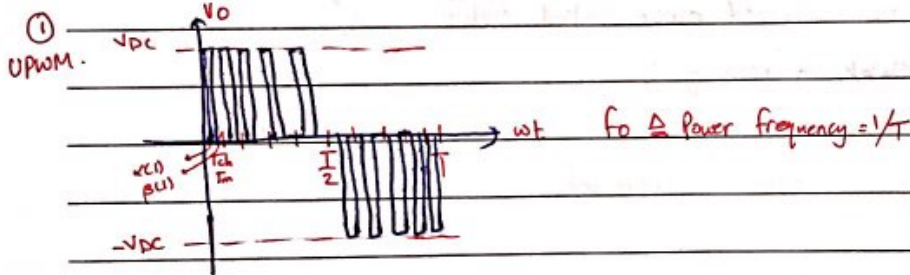

$\frac{f_{ch}}{f_o} = \frac{1/\frac{T}{5}}{1/T} = 5$; $f_{ch} = 5 f_o$

of pulses of full cycle.

* Frequency Control of I.M:


$N_s = \frac{60}{P} f$ → Synchronous speed
 $V \approx k \cdot f \cdot \phi$

Criteria: $\phi \leq \phi_{\text{rec.}} (= \phi_{\text{rated}})$

$\phi = k' \left(\frac{V}{f}\right)$

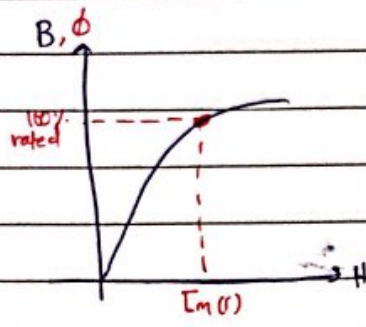(a) $f < f_r$

V should be reduced such that $\frac{V}{f} = \text{const.} \rightarrow \text{VVVF control.}$



$\phi \approx \text{constant at rated value.}$

(b) $f > f_r$

$\frac{V}{f}$ can't be increased to keep $\phi = \text{constant}$


$\phi \downarrow \rightarrow$ (field weakening).

$N_m(r) \leq N_m \leq (2-3)N_m(r) \rightarrow$ limitation is mechanical.

X Not used.

* $I_r = \frac{V_r}{\dots}$

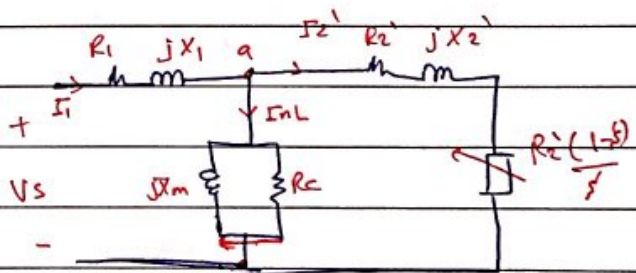$\frac{V}{\sqrt{(R_1+R_2')^2 + (X_1+X_2')^2}}$ (not accurate unless you neglect R_c & X_m)



$P_g \text{ (air-gap power)} = 3 I_2'^2 \frac{R_2'}{s}$

$T_g = \frac{P_g}{\omega_s} = 3 I_2'^2 \frac{R_2'}{s \omega_s}$

$P_{\text{conv.}} = 3 - I_2'^2 R_2' (1-s') = (1-s') P_g$

at no load $\rightarrow s' = 0 \rightarrow (1-0) = 1$

\therefore magnetization current = I_{mL}

$\eta \approx (1-s')$ → slip shouldn't be a large value.

$$\frac{P_{conv.}}{\omega_m} \Rightarrow T_{conv.} = \frac{P_g (1-s)}{\omega_s (1-s)} = \frac{P_g}{\omega_s} = T_g$$

• $s = \frac{\omega_s - \omega_m}{\omega_s}$
 • $\omega_m = (1-s)\omega_s$


• $T_{out} = T_g - T_{rot. loss}$

$I_{nl} \rightarrow$ Excitation (magnetization) branch current.

$I_{nl} \approx 20 - 50\% I_{rated}$

$X_m \ll R_c$; $L_m = \frac{N^2}{R_m}$ (Reluctance).
 ↳ core losses.

Very small because of air gap.

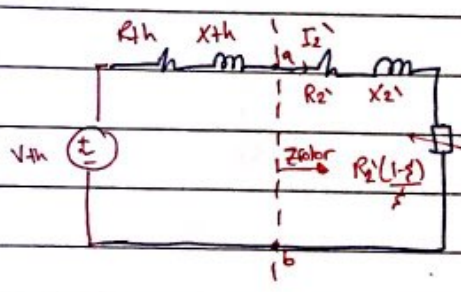

• $R_{th} \approx R_1 \left(\frac{X_m}{X_m + X_1} \right)^2$

• $I_1 = V_{th}$

$$\frac{V_{th}}{s} = \sqrt{(R_{th} + R_2')^2 + (X_{th} + X_2')^2}$$


• $X_{th} \approx X_1$

• $V_{th} = \left(\frac{X_m}{X_m + X_1} \right) V_s$

• $I_{st} = \frac{V_{th}}{s}$

$$\frac{V_{th}}{s} = \sqrt{(R_{th} + R_2')^2 + (X_{th} + X_2')^2}$$

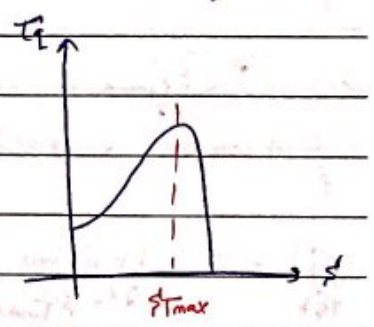• $s_{Tmax} = \frac{R_2'}{\sqrt{R_{th}^2 + (X_{th} + X_2')^2}}$



special case:

$Z_{th} \ll Z_{rotor}$

$Z_{th} \rightarrow 0$ ($R_{th} \rightarrow 0, X_{th} \rightarrow 0$)

• $s_{Tmax} = \frac{R_2'}{X_2'} = \frac{R_2'}{2\pi f_{rot} L_2'} = \frac{R_2'}{2\pi (Af_r) L_2'} = \frac{R_2'}{Af_r X_2'(r)}$

• $A_v = V$; $0 < A_v < 1$
 Vrated

• $A_f = \frac{f}{f_{rated}}$; $0 < A_f < (2-3) f_{rated}$

• $I_{st} = A_v V_r$

if f variable, v variable :

$$\frac{V_r}{s} = \sqrt{\left(\frac{R_2'}{A_f} \right)^2 + (X_2'(r) A_f)^2}$$

$\therefore I_{st}' = V_r A_v$

$$\frac{V_r}{s} = \sqrt{(R_2')^2 + (X_2'(r) A_f)^2}$$

• $I_{st} = A_v V_r$

$$\sqrt{R_2'^2 + X_2'(r)^2}$$

$$\frac{I_{st}(V, f)}{I_{st}(V_r, f_r)} = A_v \sqrt{\frac{R_2'^2 + X_2'^2}{(R_2')^2 + 4f^2 X_2'^2}}$$

$$= A_v \frac{R_2'}{\sqrt{(R_2')^2 + 4f^2 X_2'^2}}$$

$$= A_v \frac{R_2'}{R_2'} \sqrt{1 + \frac{(X_2'(f))^2}{R_2'^2}}$$

$$= A_v \sqrt{1 + \frac{4f^2 (X_2')^2}{R_2'^2}}$$

$$= A_v \sqrt{1 + \frac{1}{s_{Tmax}^2}}$$

$$= A_v \sqrt{1 + 4f^2 \frac{1}{s_{Tmax}^2}}$$

$$\frac{I_{st}}{I_{st}} = A_v \sqrt{\frac{1 + s_{Tmax}^2}{4f^2 + s_{Tmax}^2}}$$

ex: $f < f_r \rightarrow V < V_r$

$V \Delta \text{ constant} ; A_v = 2f = 2A < 1$

$$\frac{I_{st}}{I_{st}} = A \sqrt{\frac{1 + s_{Tmax}^2}{2^2 + s_{Tmax}^2}}$$

usually (12% - 20%)

$A = 0.5 ; A < 1 ; s_{Tmax} = 0.15$

try $A > 1 !!$

$$\frac{I_{st}}{I_{st}} = 0.5 \sqrt{\frac{1 + 0.0225}{0.25 + 0.0225}} = 0.97$$


$A = 0.8$

$$\frac{I_{st}}{I_{st}} = 0.8 \sqrt{\frac{1 + 0.0225}{0.64 + 0.0225}} = 1.5 \quad (\text{starting current will increase})$$

τ_{max}

$$\tau_{max} = \frac{3V_{th}^2}{2\omega_s [R_{th} + \sqrt{R_{th}^2 + (X_{eq})^2}]}$$
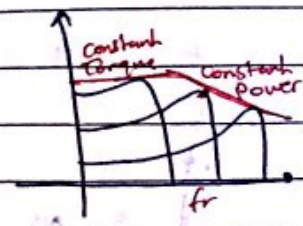
$$\tau_{max} = \frac{3V_{th}^2}{2\omega_s} \cdot \frac{1}{X_{eq}(f)}$$



$\omega_s = 60 f_r$
 $\omega_s(f) = \frac{P}{P} = 60(f) \rightarrow \tau f$

$\tau_{max}' = \frac{3 \tau_v^2 V_{th}}{2 \tau_f \tau_f X_{eq}(f)} = \frac{A_v^2}{\tau_f^2}$; $A_v = \tau f \rightarrow \frac{V}{f} = \text{constant}$

$\frac{\tau_{max}'}{\tau_{max}} = \left(\frac{\tau_v}{\tau_f}\right)^2$; τ_{max} will never be affected.

(b) $f > f_r, \tau_v = 1, \tau_f \gg 1$

$\frac{\tau_{max}'}{\tau_{max}} = \frac{1}{\tau_f^2}$

$\tau_{st} = \frac{3V_{th}^2 R_2'}{\omega_s [R_2'^2 + X_2'^2]}$

$\frac{\tau_{st}'}{\tau_{st}} = \frac{A_v^2}{R_2'^2 [1 + \frac{\tau_f^2}{\tau_{max}^2}]}$

$= \left(\frac{\tau_v^2}{\tau_f^2} \right) \left(\frac{A_v^2}{R_2'^2} \right) \left(\frac{\tau_{max}^2}{\tau_f^2} \right)$

$\tau_{st}' = \frac{3 A_v^2 V_{th}^2 R_2'}{\tau_f \omega_s [R_2'^2 + \tau_f^2 X_2'^2]}$

$R_2'^2 [1 + \frac{1}{\tau_{max}^2}]$

$\frac{\tau_{st}'}{\tau_{st}} = \frac{(\tau_{max}^2 + 1) A_v^2}{(\tau_{max}^2 + \tau_f^2) \tau_f}$


(a) $\frac{V}{f} = \text{constant} \rightarrow A_v = \tau f$

$\frac{\tau_{st}'}{\tau_{st}} = \frac{(\tau_{max}^2 + 1)}{(\tau_{max}^2 + \tau_f^2)}$

ex: $\tau_{max} = 0.15, \tau_f = 0.5$; Sol: $\frac{\tau_{st}'}{\tau_{st}} = 0.5 \left(\frac{0.0225 + 1}{0.0225 + 0.25} \right) = 1.87$

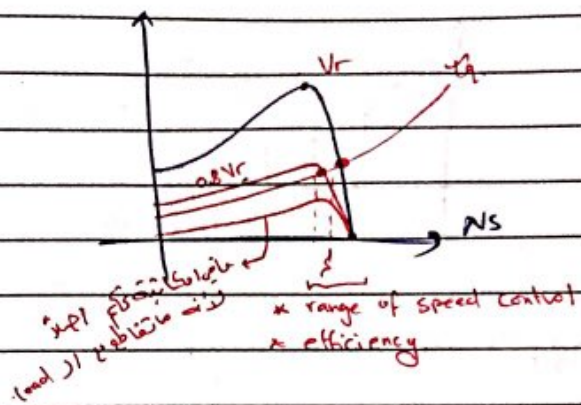(b) $f > f_r ; \tau_v = 1, \tau_f = 2$
 \rightarrow can't be larger than 1 if $f > f_r$.

$\frac{\tau_{st}'}{\tau_{st}} = \frac{1^2}{2} \left(\frac{0.0225 + 1}{0.0225 + 4} \right) = 0.127$



advantages freq. control:

↳ can be used for soft starting.

Speed control


- Increased starting Torque below rated frequency.
- Increased maximum Torque.

last example:

DCM. 230 V, 750 RPM, 56A, 0.28 Ω = Ra, Ia = 2.81 A, 15 hp.

driven by chopper class C [A → B]

Vs = 250 V DC, fch = 400 Hz.

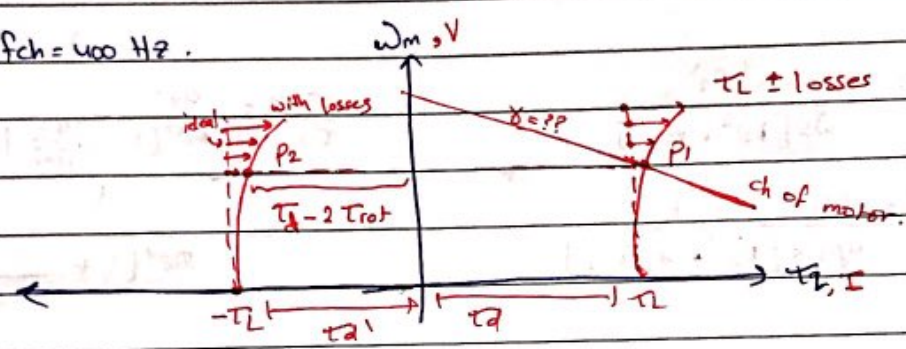

$$Ta' = Ta - 2 Trot.$$

Rated conditions:

$$P_{out} = 15 \times 746 = 11190 \text{ W}$$

$$P_{in} = 56 \times 230 \text{ V} = 12880 \text{ W}$$

$$P_{cu} = 56^2 \times 0.28 = 878 \text{ W}$$

$$P_{\text{tot}} = 12880 - 11190 - 878 = 812 \text{ W}$$

$$T_{rot} = \frac{812}{\omega_m(r)} = 4.43 \text{ N.m.}$$

$$E_a(r) = 230 - 0.28 \times 56 = 214.3 \text{ V}$$

$$k_a \phi = \frac{E_a(r)}{\omega_m(r)} = 1.169$$

$$T = \frac{2.81 \times 10^{-3}}{0.28} = 10.04 \text{ msec.}$$


$$\gamma = \frac{230}{250}$$

$$T_0 = \frac{1}{f_c n} = \frac{1}{400} = 2.5 \text{ msec}, \quad T_{ON} = \delta T = 2.3 \text{ msec}$$

$$I_1 = 63.81 \text{ A}$$

$$I_2 = 50.3 \text{ A}$$

both are positive
~1.69

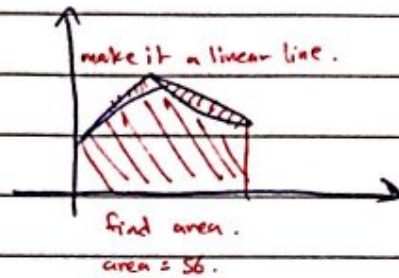

∴ Class A (motoring action).

$$T_d = K_a \cdot \phi \cdot I_a$$


$$T_d = 1.169 \cdot 56 = 65.46 \text{ N.m.}$$

$$T_L = 65.46 - 4.43$$

$$T_L = 61.03 \text{ N.m.}$$

$$I_a(av) = \frac{61.03}{1.169} = 52.2 \text{ A}$$

braking action:

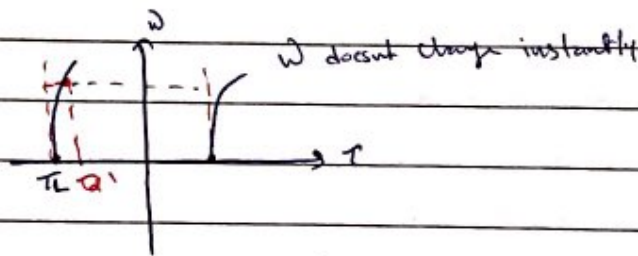

$$T_d = -(61.03 - 4.43)$$

$$T_d = -56.6 \text{ N.m}$$

$$I_a(av) = \frac{-56.6}{1.169} = -48.42 \text{ A}$$

~~both are positive~~

$$E_a' = K_a \cdot \phi \cdot \omega_m = E_a(r) = 214.3 \text{ V}$$

$$V_t' = 214.3 + (-48.42 \times 0.28) = 200.7 \text{ V}$$

$$\frac{V_t'}{V} = \frac{200.7}{250} = 0.8 \quad \therefore T_{ON} = 0.8 \times T = 2.007 \text{ msec}$$

$$I_1 = -31.35 \text{ A}$$

$$I_2 = -66.48 \text{ A}$$

both currents are +ve so avg current is +ve
So we are in braking condition.