

POWERUNIT

اللجنة الأكاديمية

في قسمي هندسة الكهرباء والحاسوب

4.7

LAB REPORT FOR EXPERIMENT 1

Name: _____

Date: 7/11/2019

Registration No: _____

Registration No: _____

Physics Section: _____

Instructor's Name: _____

PHYSICS LAB EXPERIMENT 1: ELECTRIC FIELD MAPPING

I. PURPOSE

To compute & find the electric field while plotting on couple of graphs between voltage & distance, and while finding the lines of the E.F using the pointer and two // plates.

II. DATA AND DATA ANALYSIS

A. Mapping The Equipotential Lines

1- Enter your data in Table 1.1 below:

Table (1.1 a)

For one type of electrodes:

Location of P (position of equipotential point)				
P ₁	P ₂	P ₃	P ₄	P ₅

For another type of electrodes:

Table (1.1 b)

Location of P (position of equipotential point)				
P ₁	P ₂	P ₃	P ₄	P ₅

2- Use your data of Table (1.1a) and Table (1.1 b) to plot the equipotential points on two sheets of graph paper.

3- Connect the **eight points** corresponding to each location P_i with a line which is an **equipotential line**.

4- On the same graph, draw the lines of force. These are everywhere **perpendicular** to the equipotential lines, explain why.

$$W = q \cdot \Delta V = \text{zero}$$

$$W = F \cdot d = Fd \cos \theta = 0$$

$$= qE d \cos \theta = 0$$

non-zero quantities

must equal zero

$$\Rightarrow \cos \theta = 90^\circ$$

B. Measurement of The Electric Field

The data in Table (1.2) below are V in volts and d in centimeters.

Table 1.2

V(volt)	d(cm)
0	0
1	5
2	11
3	16
4	18
5	19
6	20

1. Plot V (as dependent variable) versus d .
Find the slope of your graph.

$$\text{Slope} = \frac{\Delta V}{\Delta d} = \frac{5.1 - 4.5}{24 - 20} = 0.225 \text{ Volt/cm}$$


$$= 0.225 \text{ V/cm}$$


2. How is the slope related to the electric field?


The slope is equal to $\frac{\Delta V}{\Delta d}$ which is equal to E , \therefore slope = Electric field and it is constant between two plates.

3. What conclusion can you draw about the electric field in the region between the electrodes near the center?

That it is uniform electric field.

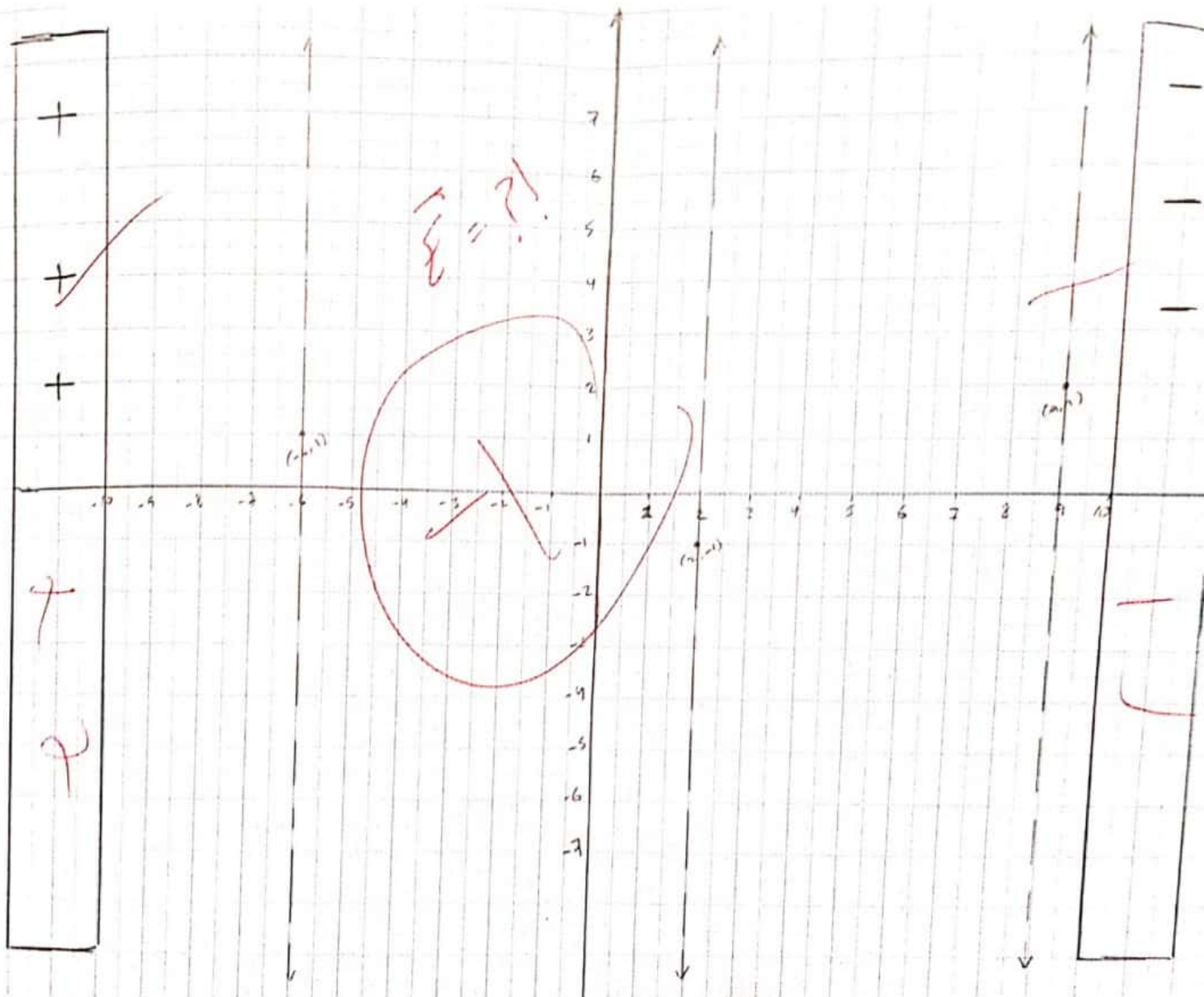

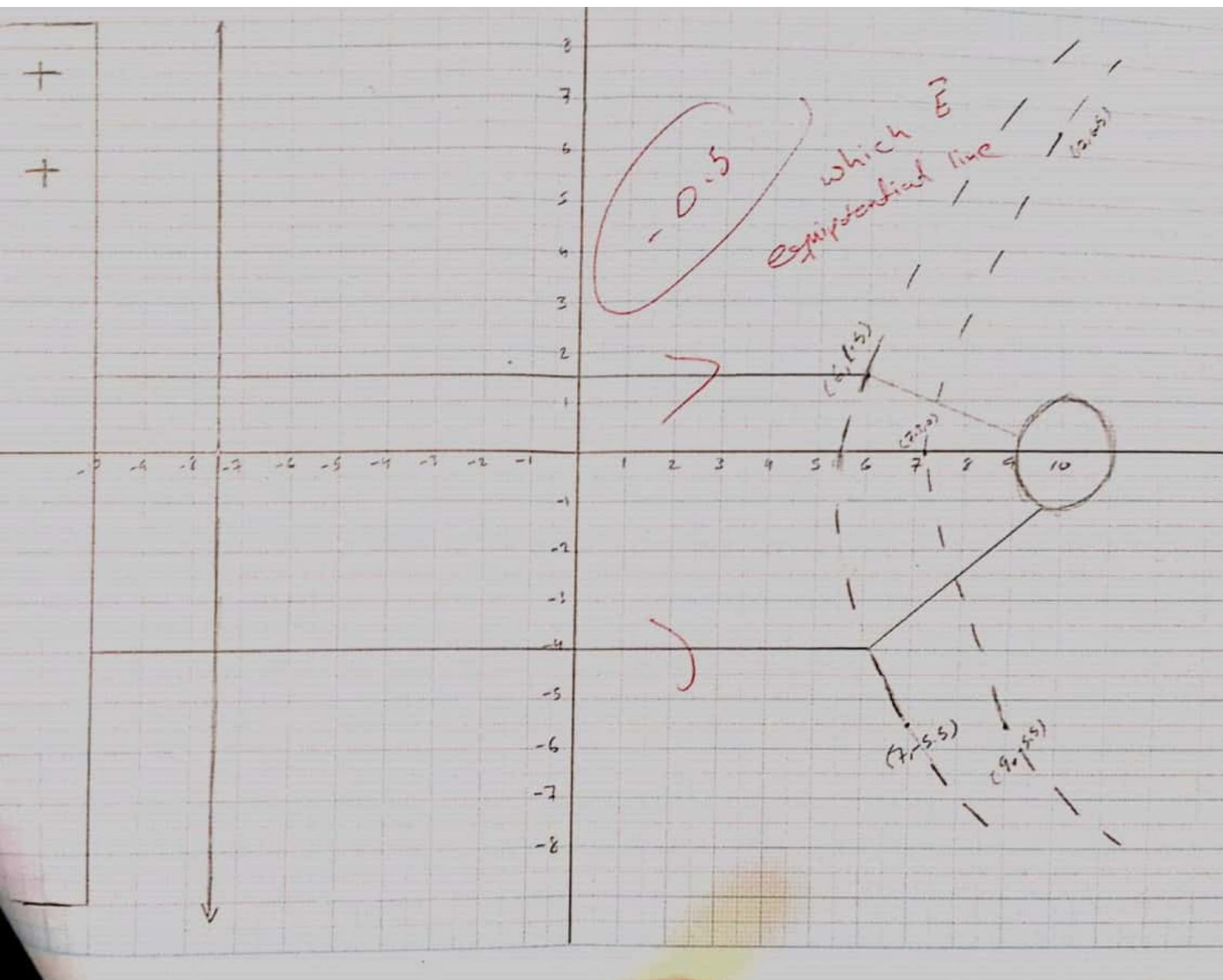

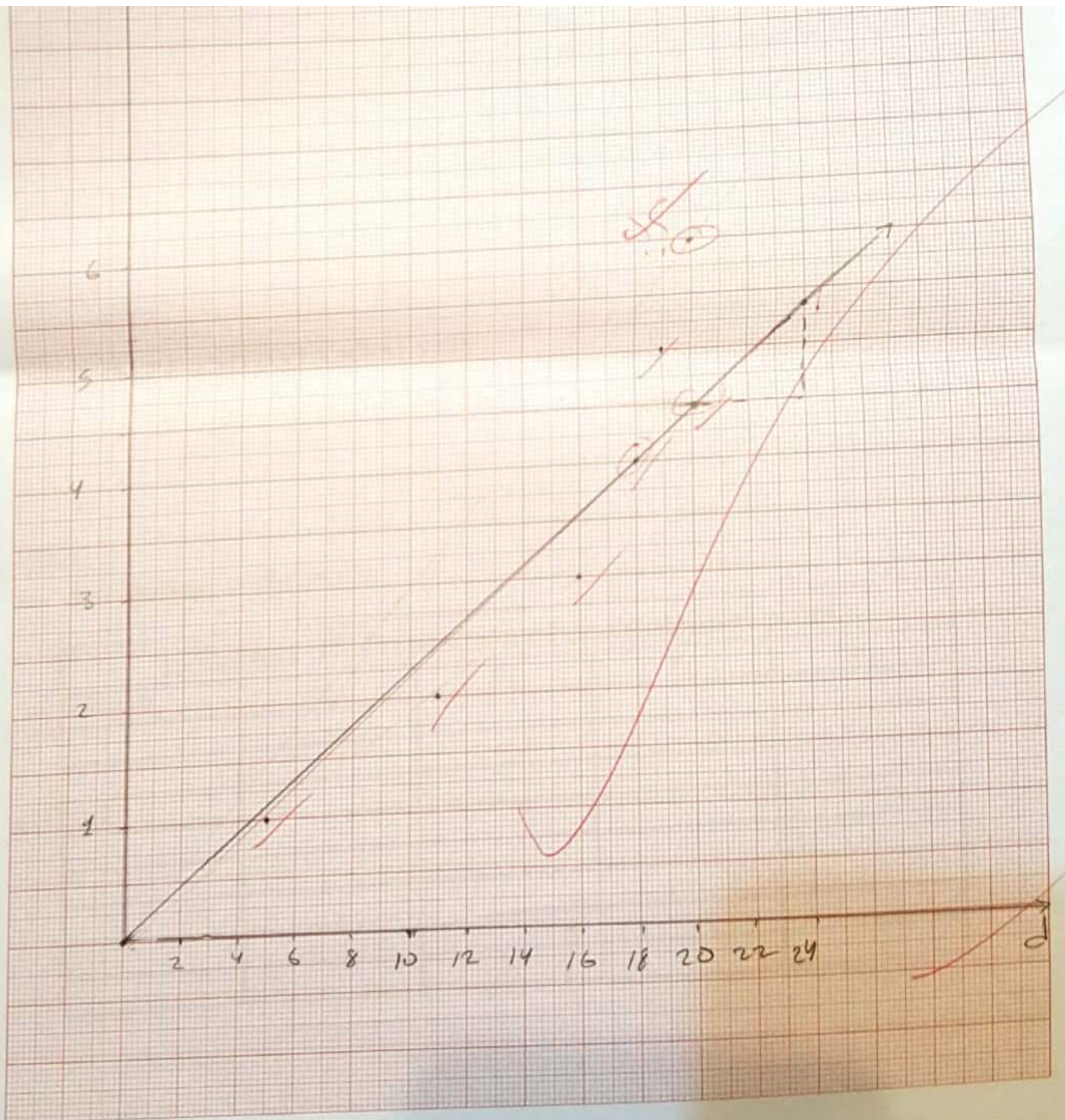

LAB REPORT FOR EXPERIMENT 2

Date: 30/9/2019

Name: _____

Partner's Name: _____

Registration No: _____

Registration No: _____

Physics Section: _____

Instructor's Name: _____

PHYSICS LAB EXPERIMENT 2: SPECIFIC CHARGE OF COPPER IONS

I. PURPOSE

To calculate the specific charge k , and
to calculate the charge of an electron.

AS

II. DATA AND DATA ANALYSIS

- Enter your data of the masses, m_1 and m_2 in kg as related to the current, I , in Ampere and time, t , in minutes in Table 2.1 below:

Table(2.1)

Current(I) (A)	Time (t) (min)	Amount of charge (It) (Coulomb)	m_1 (Kg)	m_2 (Kg)	Deposited mass $M_{Cu} = (m_2 - m_1)$ (Kg)
0.6A 0.8	10 ²⁰	480	28.14	28.35	0.21
0.3A 0.4	10 ²⁰	240	28.35	28.45	0.10
0.3A 0.4	5 ¹⁰	120	28.45	28.49	0.04

- Use the data in Table (2.1) to plot the amount of charge (It) versus the mass of the deposited copper M_{Cu} .

3. What type of relationship do you see between M_{Cu} and I_t ?

Direct and linear relationship.

4. From your graph find the specific charge, K , of copper ions by calculating the slope.

$$K = \text{slope} = \frac{380 - 280}{0.16 - 0.12} \times 10^3 = 2500 \times 10^3$$

$$= 25 \times 10^5 \text{ coul/kg}$$

5. What are the units of K ?

coul/kg

~~6.~~ Estimate the error, ΔK , in your value and write the result as $K \pm \Delta K$.

7. Calculate the charge carried by each copper ion in the solution.

$$Q = Km = K(\text{Atomic mass} \times \text{Atomic mass unit})$$

$$= K(63.6 \times 1.66 \times 10^{-27})$$


$$= K(105.576 \times 10^{-27})$$

$$= (25 \times 10^5)(105.576 \times 10^{-27})$$

$$= 2.6394 \times 10^{-19} \text{ coul}$$

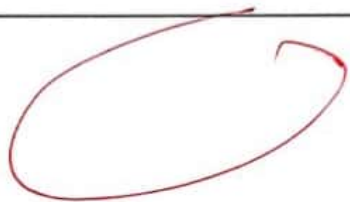8. Use the result above to calculate the **charge of the electron e**. How does it compare with the **standard value**?

$$e = \frac{Q}{2} = \frac{2.6394 \times 10^{-19}}{2} = 1.3197 \times 10^{-19} \text{ Coul.}$$




Q vs Δm

Q ↑

$$\text{slope} = \frac{380 - 280}{0.16 - 0.12}$$

$$= 2500 \times 10^3$$

$$= 25 \times 10^5$$

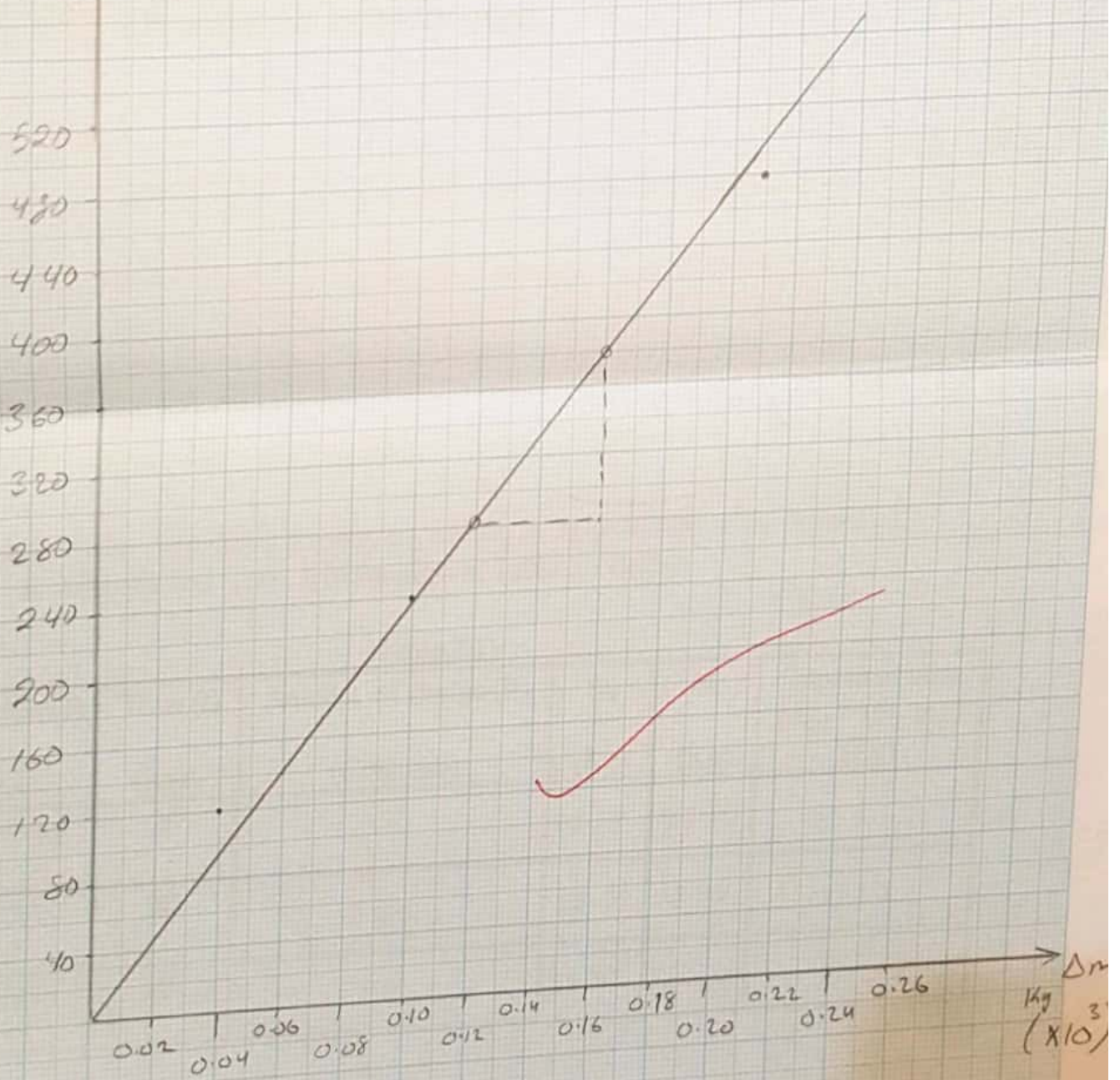

LAB REPORT FOR EXPERIMENT 3

Date: _____

Name _____

Partner's Name: _____

Registration No: _____

Registration No: _____

Physics Section: _____

Instructor's Name: _____

PHYSICS LAB EXPERIMENT 3: OHM'S LAW

1. PURPOSE

To improve ohm's law which states that
if a conductor is kept in a constant temperature
the current flowing through it would equal $\frac{\text{Potential difference}}{\text{Resistance}}$

II. DATA AND DATA ANALYSIS

1- Enter your data in Table 3.1

Table 3.1

R ₁ Wire resistance		R ₂ Carbon resistance		R ₁ and R ₂ in Series		R ₁ and R ₂ in Parallel	
V(Volt)	I(Amp.)	V(Volt)	I(Amp.)	V(Volt)	I(Amp.)	V(Volt)	I(Amp.)
1.6	2.2	2.2	4	3	2.2	1	3.8
3.8	2.8	3	5.3	3.8	2.6	1.5	4.8
5.2	3.6	3.6	8.8	4.8	3.1	2	6.2
6.2	4.6	4.5	8.2	5.3	3.5	2.6	8.2
7	5	5	8.6	5.6	4.1	3	9.2

- 2- Plot graphs of voltage V as a dependent variable versus current I .
- 3- Determine the values of R for each **unknown resistance** as well as for the series and parallel combinations by calculating the slopes of your graphs.

$$R_1 = \frac{\text{slope}}{\dots} = 2 \Omega$$

$$R_2 = \frac{\text{slope}}{\dots} = 0.667 \Omega$$

$$R \text{ equivalent of } R_1 \text{ and } R_2 \text{ in series} = 3 \Omega$$

$$R \text{ equivalent of } R_1 \text{ and } R_2 \text{ in parallel} = 0.4 \Omega$$

~~4~~ From the graph of V versus I for R_1 , estimate the error ΔR_1 .

_____ 0.37×10^{-3}

- 5- Using the value of R_1 obtained in (3) and the length and diameter of the wire used for R_1 , calculate the resistivity of the wire ρ .

$$R = \frac{\rho L}{A} \Rightarrow \rho = \frac{RA}{L}$$

$$= \frac{2 \times 1.07 \times 10^{-7}}{2}$$

$$= 2.14 \times 10^{-7} \Omega \cdot m$$

$$A = \pi \left(\frac{D}{2}\right)^2$$

$$= 3.14 \times \left(\frac{0.37}{2}\right)^2$$

$$= 1.07 \times 10^{-7}$$

- 6- Compare the calculated values with the experimental values you obtained for:

Combination of resistances in series:

- experimental value: 3Ω

- calculated value: $R_1 + R_2 = 2 + 0.667 = 2.667 \Omega$

Combination of resistances in parallel:

- experimental value: 0.4Ω


- calculated value: $\left(\frac{1}{2} + \frac{1}{0.667}\right)^{-1} = 0.5 \Omega$

$$\text{Slope of } R_{\text{series}} = \frac{7.5 - 6}{4 - 3.5} = 3$$

$$\text{Slope of } R_1 = \frac{6 - 5}{4.5 - 4} = 2$$

$$\text{Slope of } R_2 = \frac{4 - 3.5}{7.25 - 6.5} = 0.667$$
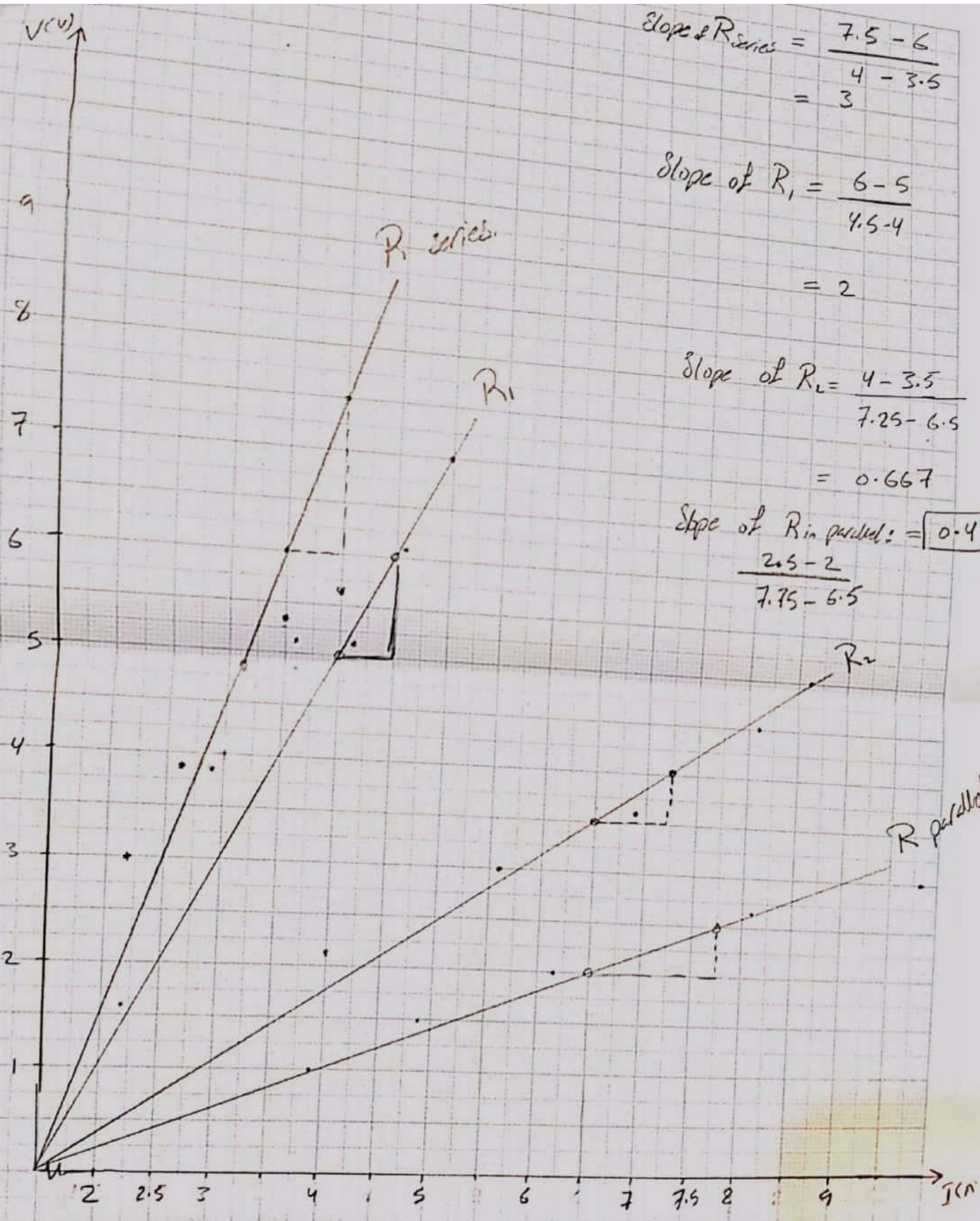
$$\text{Slope of } R_{\text{in parallel}} = \boxed{0.4} = \frac{2.5 - 2}{7.75 - 6.5}$$



LAB REPORT FOR EXPERIMENT 4

Date: _____

Name: _____

Partner's Name: _____

Registration No: _____

Registration No: _____

Physics Section: _____

Instructor's Name: _____

PHYSICS LAB EXPERIMENT 4: POWER TRANSFER

I. PURPOSE

To calculate R_s and to compare it to R_L and to find the relation between the power dissipated and the resistance.

II. DATA AND DATA ANALYSIS:

1. Use the equation $P = VI$ to calculate P_L the power dissipated by the load resistor R_L and enter the calculated values in Table (4.1) below:

Table 4.1

$R_s = 100 \Omega$				
Reading	$R_L (\Omega)$	I_L (mA)	V_L (V)	P_L (mW)
1	20	48 mA	1	48
2	40	40	1.8	72
3	60	35	2.2	77
4	80	32	2.6	83.2
5	100	29	3	87
6	200	19	4	76
7	400	12	4.8	57.6
8	600	8	5.2	41.6
9	800	6	5.4	31.8

$$I = \frac{V_s}{R_s + R_L}$$

2. Plot on a graph paper the power P_L as dependent variable versus the load resistor R_L . Find the value of the load resistor for which the power dissipated is maximum. How is this value related to the series resistance R_s .

The maximum power dissipated happens when the value of the resistance equals R_s .

$$P_{max} = 87 \text{ mWatt}, R_s = 100 \Omega$$

3. For what value of the load resistance R_L was:

1) The load current a maximum? ~~$20 \Omega, I = 48 \text{ mA}$~~

2) The load voltage a maximum? ~~$800 \Omega, V = 5.4 \text{ V}$~~

4. Using the expression for P_L power dissipated in the load resistance as a function of the load resistance R_L , determine the condition for the maximum power (differentiate P_L with respect to R_L and set $\frac{dP_L}{dR_L} = 0$)

$P = IV$	$\frac{dP}{dI} = 0 \Rightarrow P = (R_s + R_L)^2 V_s^2 - V_s^2 R_L (2R_s + 2R_L)$
$P_L = I^2 R_L$	$(R_s + R_L)^2 - 2R_L(R_s + R_L) = 0$
$P_L = \frac{V_s^2}{(R_s + R_L)^2} \cdot R_L$	$R_s + R_L - 2R_L = 0$
$P = \frac{V_s^2 R_L}{R_s^2 + 2R_s R_L + R_L^2}$	$R_s - R_L = 0 \Rightarrow \boxed{R_s = R_L}$
$\frac{dP}{dR_L} = \frac{(R_s^2 + 2R_s R_L + R_L^2) V_s^2 - V_s^2 R_L (2R_s + 2R_L)}{(R_s^2 + 2R_s R_L + R_L^2)^2}$	

- 5- Compare the value of R_L at maximum power found in (2) with that found in (4) above.

$$R_s = R_L \Rightarrow R_L (P_{max}) = 100 \Omega, R_s = 100 \Omega \Rightarrow 100 = 100 \therefore R_s = R_L \checkmark$$

- 6- If the internal resistance, R_s , is larger than the load resistance R_L , which resistance will dissipate more power?

~~R_s because $P = I^2 R$ and the current is equal therefore $P \propto R$.~~

$$P = I^2 R$$



LAB REPORT FOR EXPERIMENT 5

Date: 28/10/2019

Name:—

Partner's Name

Registration No:-----

Registration No:-----

Physics Section:-----

Instructor's Name:-----

PHYSICS LAB EXPERIMENT 5: THE WHEATSTONE BRIDGE

I. PURPOSE

Determining an unknown resistance
by using wheatstone bridge.

10

II. DATA AND DATA ANALYSIS :

1. Show that $\frac{R_s}{R_x} = \frac{L_1}{L_2}$

$$V_{ab} = V_{bc} \quad V_{bd} = V_{cd}$$

$$I_1 R_s = I_2 R_1 \quad I_1 R_x = I_2 R_2$$

$$\frac{I_1}{I_2} = \frac{R_1}{R_s} \quad \frac{I_1}{I_2} = \frac{R_2}{R_x}$$

$$\Rightarrow \frac{R_1}{R_s} = \frac{R_2}{R_x}$$

$$\frac{\frac{\rho L_1}{A}}{R_s} = \frac{\frac{\rho L_2}{A}}{R_x} \Rightarrow \frac{L_1}{R_s} = \frac{L_2}{R_x} \Rightarrow R_x = \frac{L_2}{L_1} R_s.$$

2. Record your data in Table (5.1) below:

Table 5.1

Reading	R_s (Ω)	L_1 (cm)	L_2 (cm)	R_x (Ω)	$\Delta R_x / R_x$ "Error"
1	1	11.5	88.5	7.696	4.38×10^{-2}
2	2	23.5	76.5	6.5	2.22×10^{-2}
3	3	32.1	67.9	6.345	1.72×10^{-2}
4	4	39.7	60.3	6.076	1.51×10^{-2}
5	5	45	55	6.111	1.44×10^{-2}
6	6	49.8	50.2	6.048	1.41×10^{-2}
7	7	54	46	5.963	1.43×10^{-2}
8	8	57.3	42.7	5.962	1.46×10^{-2}
9	9	60.2	39.8	5.950	1.5×10^{-2}
10	10	62.8	37.2	5.924	1.56×10^{-2}
$\bar{R}_x = 6.2568 \Omega$					

3. Using the equation derived in (1), calculate the value of the unknown resistance R_x . Repeat for the different values of R_1 and enter your calculation in table 5.1 above.

Example for one calculation:

$$R_x = \frac{L_2}{L_1} R_s = \frac{88.5}{11.5} (1) = 7.696 \Omega$$

4. Calculate the relative error $\Delta R_x / R_x$ for the different values of R_1 using the equation:

$$\frac{\Delta R_x}{R_x} = \left[\left(\frac{\Delta L_1}{L_1} \right)^2 + \left(\frac{\Delta L_2}{L_2} \right)^2 \right]^{\frac{1}{2}}$$

Example for one calculation:

$$\frac{\Delta R_x}{R_x} = \left[\left(\frac{0.05}{23.5} \right)^2 + \left(\frac{0.05}{76.5} \right)^2 \right]^{\frac{1}{2}} = 2.22 \times 10^{-2}$$

5. Is it essential that the battery supplies a constant current to the wire?
Explain your answer.

No, because the resistance depends on
the length " L_2 & L_1 " and on the
resistance source.

6. From the table, determine the values of L_1 and L_2 for which the error $\Delta R_x / R_x$ is a **minimum**.

$$L_1 = \underline{49.8 \text{ cm}}$$

$$L_2 = \underline{50.2 \text{ cm}}$$

2- Plot a graph of V_x versus L_x . State your conclusion.

The relation between V_x and L_x is
a direct linear relationship.

3- If the wire is uniform derive a simple relation between the voltmeter reading V_x at any point on the wire and the corresponding distance L_x .

$$V = IR$$

$$= \frac{I \rho L}{A}$$

$$V = \left(\frac{I \rho}{A} \right) \cdot L_x$$

$\left(\frac{I \rho}{A} \right)$ is slope

B. Measurement of an Unknown EMF

1- Calculate and record \bar{L}_x , the average value of L_x .

Trial	L_x (cm)
1	55
2	54.5
3	55.1
$\bar{L}_x = 54.87$ cm	

2- Use your graph of part A to find the value of E_x corresponding to \bar{L}_x .

$$E_x = \text{slope} \cdot \bar{L}_x = 0.025 \times 54.87$$

$$= 1.37 \approx 1.4 \text{ V}$$

- 3- What is the current flowing through E_x when pointer touches the potentiometer wire at the balance point?

The current at the balance point = zero.

- 4- What happens to the balance point when a small resistor is connected in series between E_x and the galvanometer? Explain the result you observe.

The balance point will not change because the current that passes through the wire is zero "No current is passing".

$$V = \frac{IP}{A} \cdot L$$

$\underbrace{\hspace{1cm}}_{\text{slope}} \Rightarrow \Omega \cdot N$

4.5

4

3.5

3

2.5

2

1.5

1

0.5

10

20

30

40

50

60

70

80

90

100



110

L_x

(cm)

$$\text{slope} = \frac{\Delta V}{\Delta L_x} = \frac{2.75 - 2.25}{110 - 90}$$

$$= 0.025 \Omega \cdot N$$

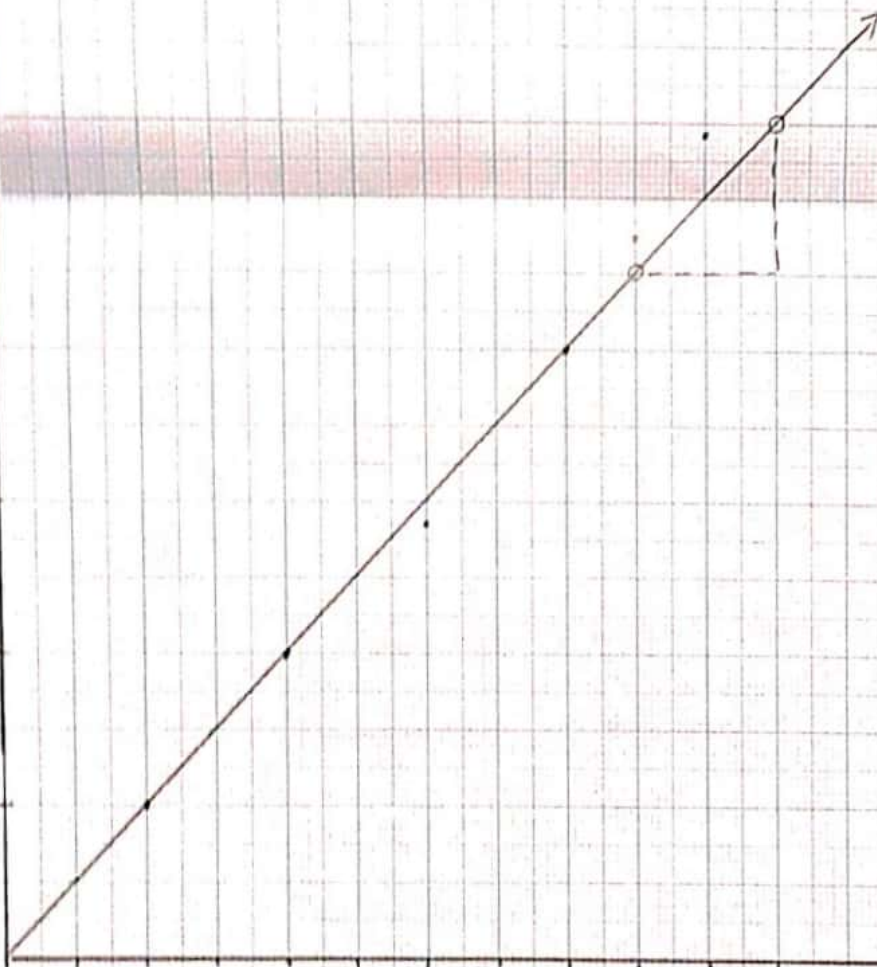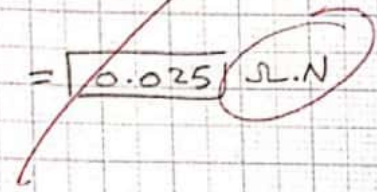

LAB REPORT FOR EXPERIMENT 7

10

Date: 18/11/2019

Name

Partner's

Registration No:-----

Registration No:-----

Physics Section:-----

Instructor's Name:-----

PHYSICS LAB EXPERIMENT 7 : THE RC TIME CONSTANT

I. PURPOSE

To learn how to calculate the RC time constant.

IV. DATA AND DATA ANALYSIS:

- 1- Enter your data of the **charging current**, the corresponding **time** and the measured voltage source V_0 in Table 7.1 below:

Plot the **charging current** as dependent variable versus **time** as independent variable for case 1. Is the plot linear? What can you say about the shape of your graph?

No, The shape of the graph is

exponential.

3- From the data of charging current versus time, determine the value of the initial charging current I_0 . This is the value of the current at $t = 0$. Record the value in table 7.1 .

4- Plot $\ln(I/I_0)$ as the dependent variable versus time. Here, I is the charging current and I_0 , the initial current determined in step (3) above. Is the plot linear?

Yes

5- Draw the straight line that best fits the data and determine the slope of the line. Record the value of the slope in table 7.1 .

6- Repeat steps 3,4 and 5 above for the second case.

7- Determine the time constant for each case from the equation:

$$\tau = \frac{-1}{\text{slope}}$$

and record it in table 7.1.

τ_1 (experimentally) = 11.11 s

τ_2 (experimentally) = 20 s

From the known values of C and R for each case, calculate $\tau_1 = RC_1$ and $\tau_2 = RC_2$ and compare these values with those obtained in step (6).


$$\tau_1 \text{ (Calculated)} = \frac{200 \times 10^{-6} \times 60 \times 10^3}{1} = \boxed{12} \text{ s}$$


$$\tau_2 \text{ (Calculated)} = \boxed{30} \text{ s}$$

- 9- From the known values of V_o and R, , calculate $I_o = \frac{V_o}{R}$ which is the same for both cases. Compare this value with the one obtained in step (3) above.

$$I_o \text{ (calculated)} = \underline{0.0001 \text{ A}}$$
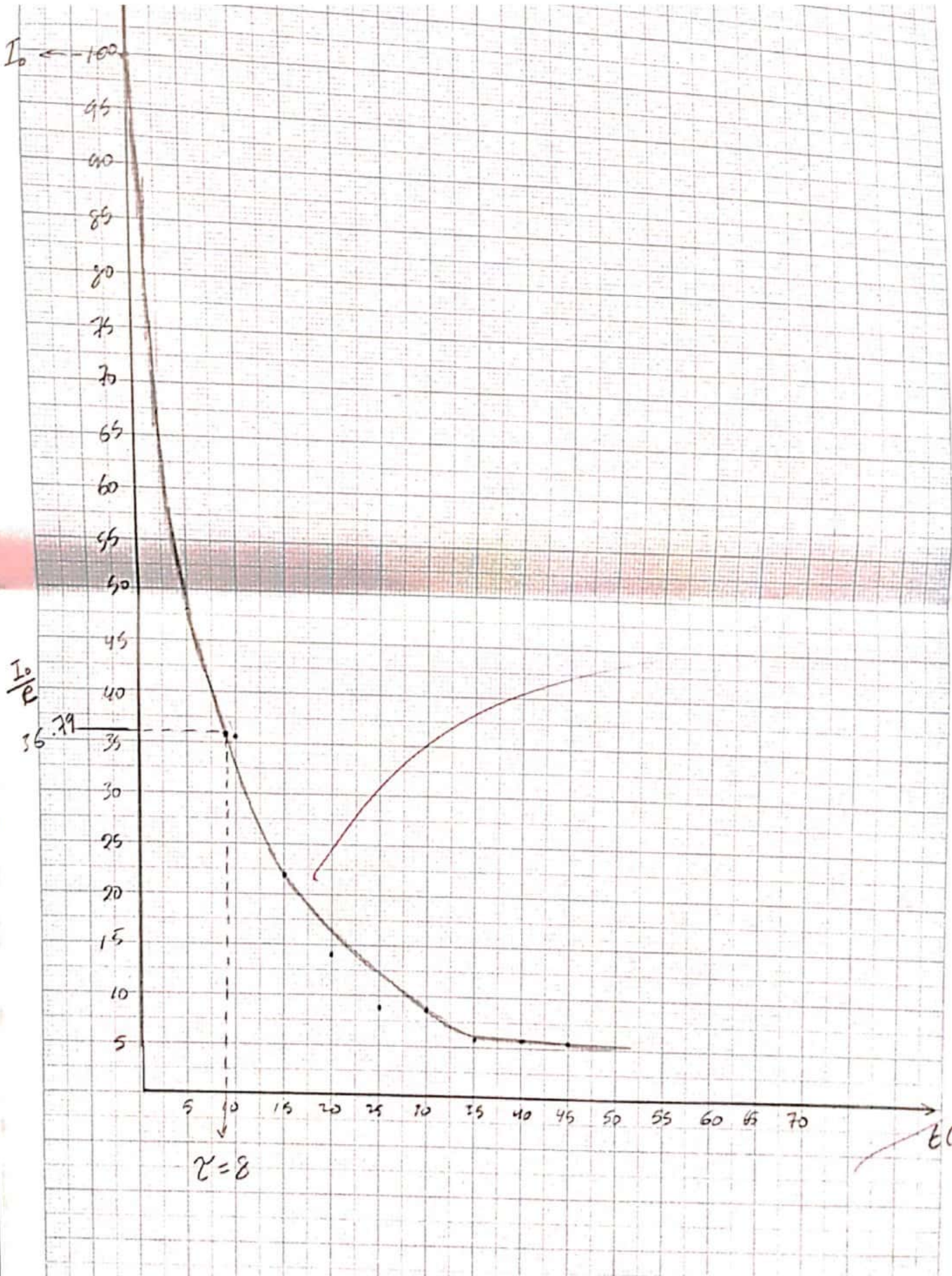
$$I_o = \frac{6}{60 \times 10^3} = \boxed{0.0001 \text{ A}}$$



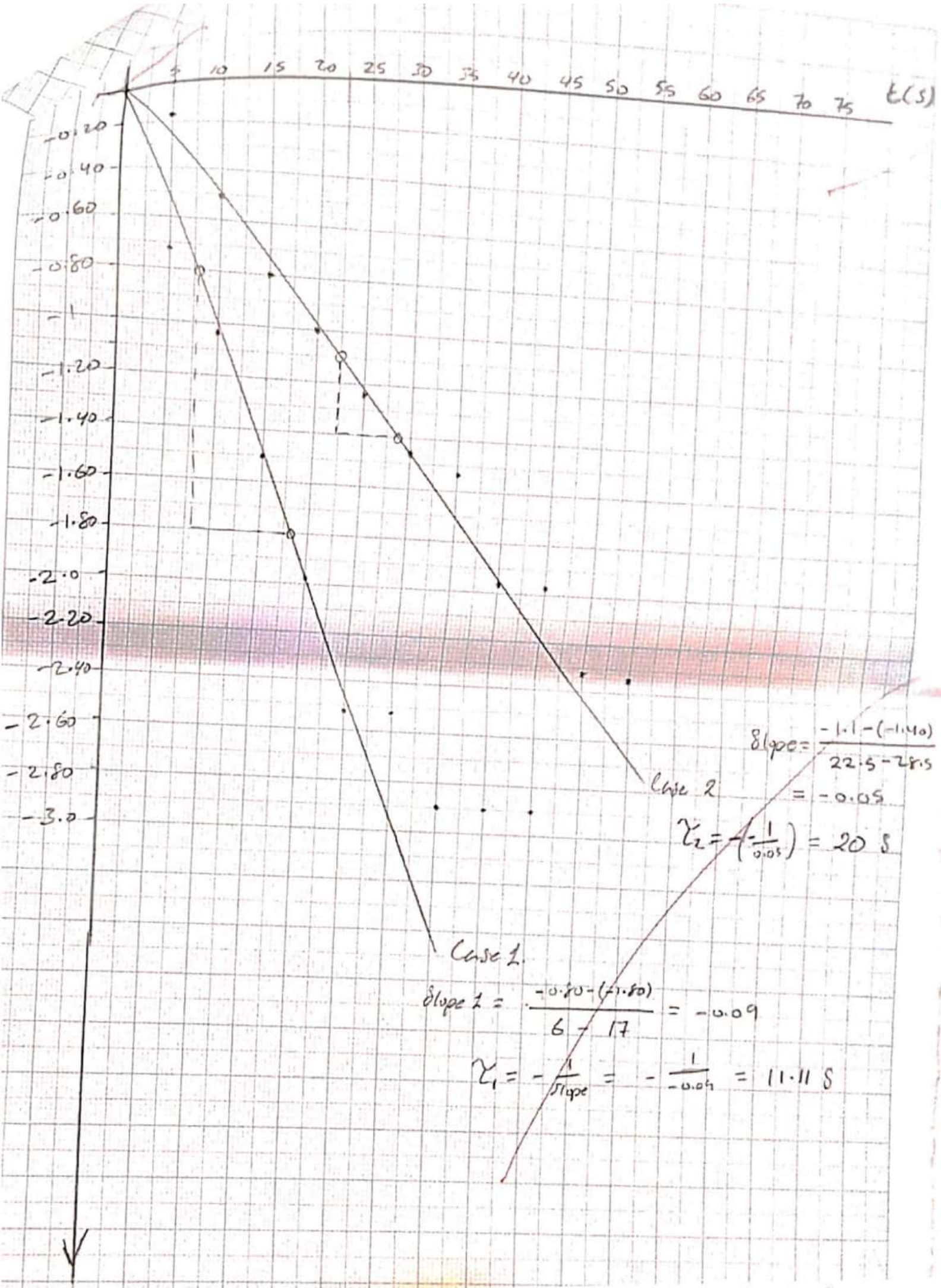

LAB REPORT FOR EXPERIMENT 8

Date: -----

Name.

Partner's Name.

Registration No:-----

Registration No:-----

Physics Section:-----

Instructor's Name:-----

PHYSICS LAB EXPERIMENT 8: THE MAGNETIC FIELD OF A CURRENT

10

I. PURPOSE

To find the magnetic field of a current
reduction factor manually using the tangent
galvanometer.

II. DATA AND DATA ANALYSIS:

1. Enter your data in Table 8.1 below:

Table 8.1

Reading	I(mA)	θ_1	θ_2	θ_3	θ_4	$\bar{\theta}$	$\tan \bar{\theta}$
1	30	26	26	35	37	31	0.6
2	40	34	34°	35	33	34	0.67
3	50	37	37°	31	41	38.5	0.79
4	60	42	43	44	40	42.5	0.91
5	70	45	46	57	54	50.5	1.21
6							
7							
8							
radius of the coil = 7.25 cm				N=50 turns			

- Using Table 8.1 plot a graph between the values of **I** as a dependent variable against the corresponding values of $\tan \bar{\theta}$ as the independent variable.
- Use your graph to find the value of the reduction factor **K** and the error ΔK .

$$K = \text{slope} = \frac{(60 - 55) \times 10^{-3}}{1.04 - 0.95} = \boxed{0.056}$$

K \pm ΔK =

Using the above value of $K \pm \Delta K$, find the value of $H_E \pm \Delta H_E$.

~~$$\tan \theta \quad H_E = \frac{2 \pi N I}{10 a}$$~~

~~$$H_C = \frac{2 \pi N I}{10 a}$$~~

~~$$K = \frac{10 H_E a}{2 \pi N}$$~~


~~$$0.056 = \frac{10 H_E (7.25)}{2 \pi \times 50}$$~~

 ~~\Rightarrow~~

~~$$H_E = 0.24 \text{ Gauss}$$~~

$$H_E \pm \Delta H_E = \quad \text{Gauss}$$
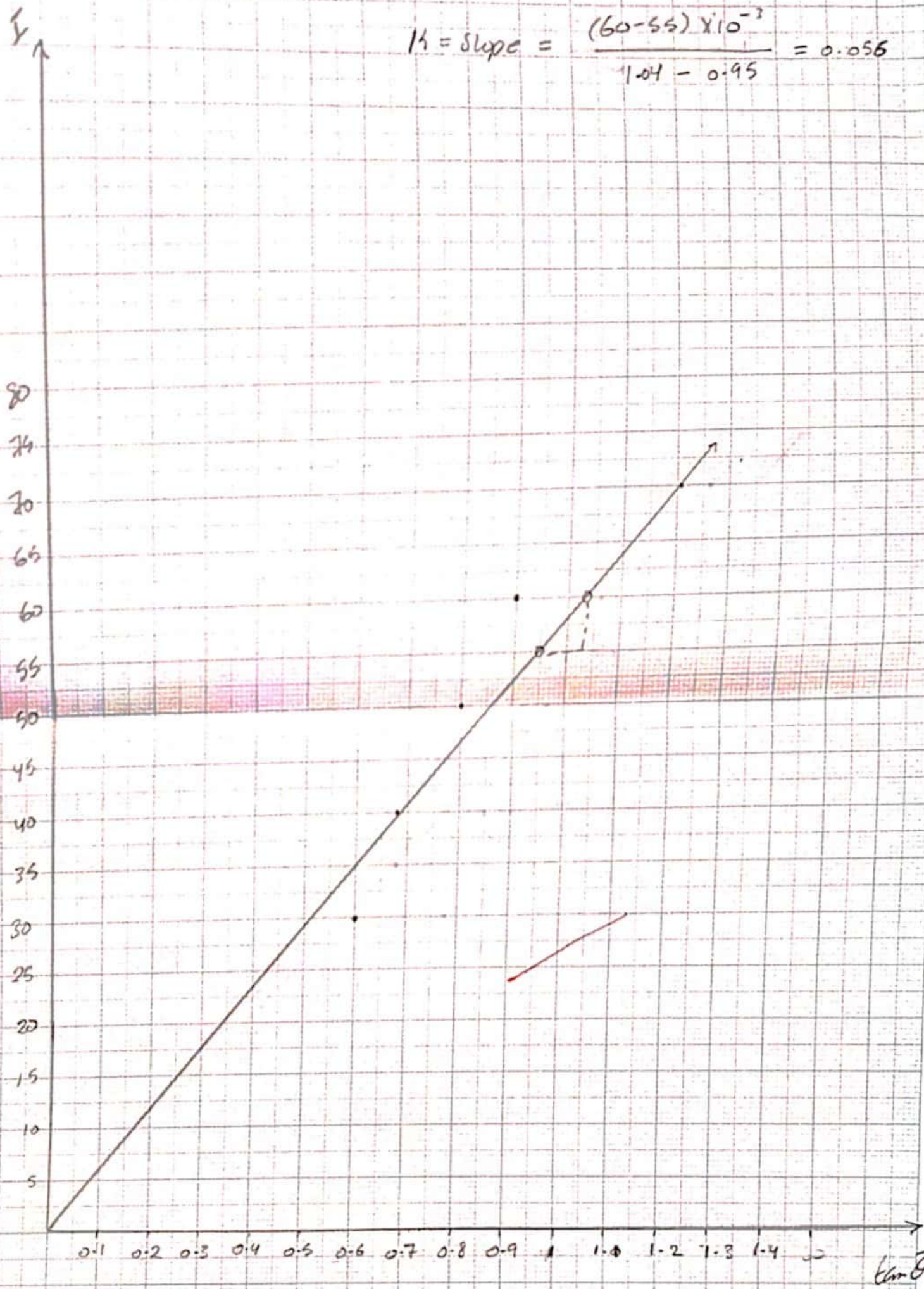
$$k = \text{slope} = \frac{(60-55) \times 10^{-3}}{1.04 - 0.95} = 0.056$$



**LAB REPORT FOR EXPERIMENT 9
KIRCHHOFF'S LAWS**

Date: 11/11/2019

Name:-- _____

Partner's Name: _____

Registration No:-----

Registration No:-----

Physics Section:-----

Instructor's Name:-----

PHYSICS LAB EXPERIMENT 9 : KIRCHHOFF'S LAWS

1. PURPOSE :

To apply KVL & KCL effectively.

AS

II. DATA AND DATA ANALYSIS:

A. DATA:

1. Record the measured values of V_1 , V_2 , V_{R_1} , V_{R_2} and V_{R_3} and their polarities on diagram 1 shown below.
2. Record the measured values of I_1 , I_2 , and I_3 and their direction of flow on diagram 1.


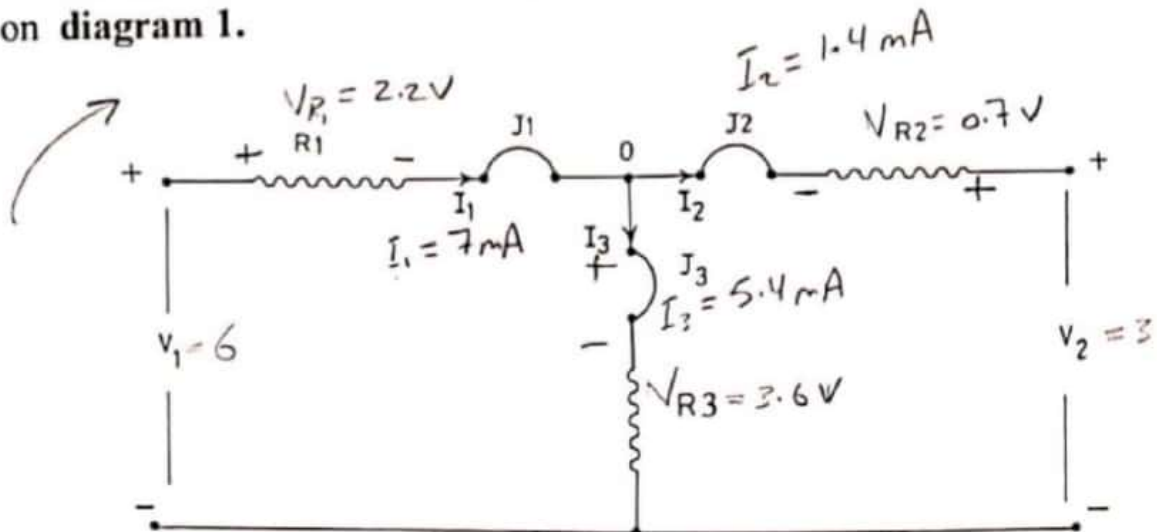


diagram 1

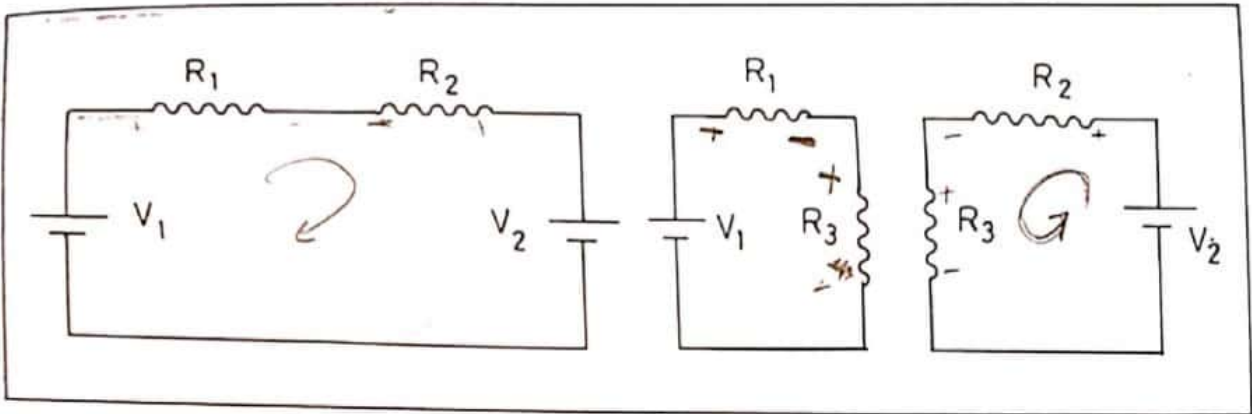B. Using the values obtained in part A, calculate the sum of voltage drops around the three loops shown below:



$$V_1 + V_{R_1} + V_{R_3} = \underline{-6 + 2.2 + 3.6 = 0.2} \text{ volt}$$

$$V_2 + V_{R_2} + V_{R_3} = \underline{-3 + 0.7 + 3.6 = 1.3} \text{ volt}$$

$$V_1 + V_{R_1} + V_{R_2} - V_2 = \underline{-6 + 2.2 - 0.7 + 3 = -1.5} \text{ volt}$$

Are the sums shown above equal to zero?

Yes they are close to zero.

C. Using the values of currents obtained in part A, calculate the total sum of currents at the junction O

$$I_1 + I_2 + I_3 = \underline{+7 \text{ mA} - 5.4 \text{ mA} - 1.4 \text{ mA} = 0.2}$$

Is the sum equal to zero?

Yes, $0.2 \approx 0$

D. Using the values of V_1 and V_2 and the values of R_1 , R_2 , and R_3 , set up the loop and branch equations, and solve them to determine the values of I_1 , I_2 and I_3 and compare with the values obtained experimentally in part A.

Loop equations:

$$\begin{aligned} \text{Outer Loop } -V_1 + I_1 R_1 - I_2 R_2 + V_2 &= 0 \\ -6 + 330 I_1 - 470 I_2 + 3 &= 0 \\ 330 I_1 - 470 I_2 &= 3 \text{ V} \quad \text{--- (2)} \end{aligned}$$

Branch equations:

$$\begin{aligned} -V_1 + I_1 R_1 + I_2 R_2 &= 0 & I_2 R_2 + V_2 - I_3 R_3 &= 0 \\ 330 I_1 + 0 I_2 + 680 I_3 &= 6 \text{ V} \quad \text{--- (1)} & 680 I_3 - 470 I_2 + 0 I_1 &= 3 \text{ V} \quad \text{--- (3)} \end{aligned}$$

$$\begin{bmatrix} 330 & 0 & 680 \\ 0 & -470 & 680 \\ -330 & -470 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 6 \\ 3 \\ 3 \end{bmatrix}$$

$$I_1 = I_2 + I_3$$

$$I_1 - I_2 - I_3 = 0$$

$$1 - 1 - 1 = 0 \rightarrow \text{(5)}$$

Calculated values:

$$I_1 = \underline{6.95 \times 10^{-3}} \text{ Ampere}$$

$$I_2 = \underline{1.5 \times 10^{-2}} \text{ Ampere}$$

$$I_3 = \underline{5.45 \times 10^{-2}} \text{ Ampere}$$

Experimental values:

$$I_1 = \underline{7 \times 10^{-3}} \text{ Ampere}$$

$$I_2 = \underline{1.4 \times 10^{-2}} \text{ Ampere}$$

$$I_3 = \underline{5.4 \times 10^{-2}} \text{ Ampere}$$

$$\begin{aligned} 90 \quad R_1 &= 33 \times 10^1 \\ R_2 &= 47 \times 10^1 \\ R_3 &= 68 \times 10^1 \end{aligned}$$

LAB REPORT FOR EXPERIMENT 10

Date: 2/12/2019

Name: _____

Partner's Name: _____

Registration No: _____

Registration No: _____

Physics Section: _____

Instructor's Name: _____

PHYSICS LAB EXPERIMENT 10: ELECTROMAGNETIC INDUCTION

I. PURPOSE:

To investigate the conditions required to
produce an induced current.

II. DATA AND DATA ANALYSIS:

Enter, in Table 10.1 below your observations and deductions on the investigated cases of induced current production.

Table 10.1

Action	Direction of Current		Size of deflection and comments
	Primary	Secondary	
(a)	clockwise	Counterclockwise	Small deflection
(b)	clockwise	clockwise	Small deflection
(c)	clockwise	Counterclockwise	Small deflection
(d)	counterclockwise	clockwise	Small deflection
(e)	clockwise	clockwise	Small deflection
(f)	clockwise	Counterclockwise	Small deflection
(g)	clockwise	Counterclockwise	Small deflection but greater than the past ones. → greater
(h)	clockwise	Counterclockwise	Small deflection
(i)		Counterclockwise	moderate deflection
(j)		clockwise	moderate deflection
(k)		clockwise	moderate deflection
(L)		Counterclockwise	moderate deflection

- 1- From the directions of the secondary current in case a and b determine whether Lenz's law is obeyed. Explain.

Case a:

Lenz's law is obeyed, because the secondary current direction flows in the other direction (counterclockwise), to oppose the change that produce it.

primary current is on "clockwise" \Rightarrow secondary current is produced in the opposite direction

Case b:

Lenz's law is obeyed, since:
Primary current is off \Rightarrow Secondary current is
"Clockwise" produced clockwise to
opposite the change in
the current.

2- Explain the reason for the **difference in deflection** of the galvanometer in case g when a soft iron rod is inserted in the winding.

The difference in deflection is larger in case g because the iron is a high magnetic material so the current is larger.

3- Explain what happens to the **size of deflection** of the galvanometer when a brass rod is inserted in the windings.

The size of deflection stays small (does not change) because the brass rod is less of a magnetic material than the iron so the current is small.