

CIRCUITS II

DR.SIREEN ALTHAHER



BY:MOHAMMED ZIAD

 **POWERUNIT** 

* Source \rightarrow Load

D.C \rightarrow Direct current


A.C \rightarrow Alternating current

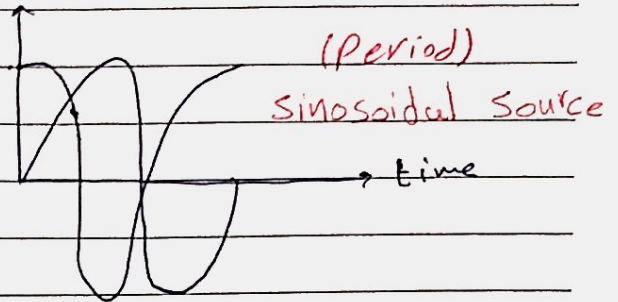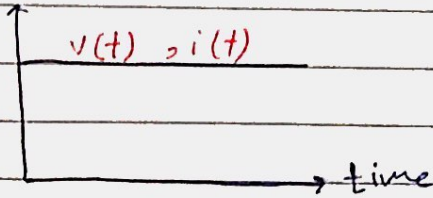

* Sinusoidal generation :-

1) Period $\Rightarrow T$ (Sec)

2) Frequency

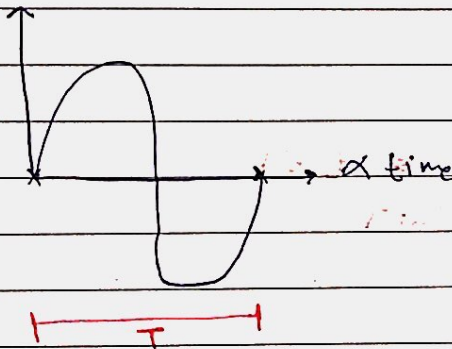

of periods $\Rightarrow 1$ sec

1 period $\Rightarrow T$ sec


$$f = \frac{1}{T} \text{ (sec)}^{-1} \text{ (Hz)}$$

3) Max \rightarrow ref = 0

(Peak)

Amplitude \rightarrow ref = avg \rightarrow max

$$y(t) = A \sin t$$

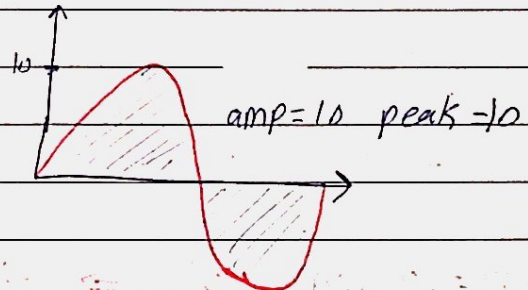

$$y_{\text{avg}} = \frac{1}{T} \int_0^T y(t) dt$$

(period)

$$= \frac{1}{T} \int_0^T A \sin t dt = -\frac{A}{T} \cos t \Big|_0^T = -\frac{A}{T} [1 - 1] = \text{Zero}$$

Ex: $V(t) = 5 + 3 \cos t$

① avg $= \frac{1}{T} \int_0^T 5 + 3 \cos t$
 $= 5 = 0c$

② peak $= 5 + 3 = 8$


③ Amp $= 8 - 5 = 3$

④ peak-peak min $\Rightarrow 5 + 3 * -1 = 2$
 min \rightarrow max $\Rightarrow 8 - 2 = 6$

angular speed $\Rightarrow \omega = \frac{\alpha}{t}$ \rightarrow angle

$\alpha = \omega t$

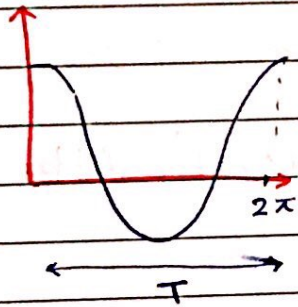$5 \cos x = 5 \cos \alpha = 5 \cos \omega t$



at $\alpha = 2\pi \Rightarrow t = T$

$\alpha = \omega t = \omega T$

$\omega = \frac{2\pi}{T} \Rightarrow \omega = 2\pi f$

$\omega \Rightarrow (\text{rad/sec})$

Assume a sinusoidal current

Amp = 10 A

period = 0.12 sec = T


Determine the times at which $i = 5A$

$i(t) = 10 \sin(\omega t) \Rightarrow \omega = \frac{2\pi}{t} = \frac{2\pi}{0.12} = 52.36 \text{ rad/sec}$

$5 = 10 \sin(52.36)t \Rightarrow 0.5 = \sin(52.36t) \Rightarrow$

$$\frac{\pi}{6} = 30^\circ \Rightarrow t_i = 10 \text{ m sec}$$

$$\frac{5\pi}{6}$$

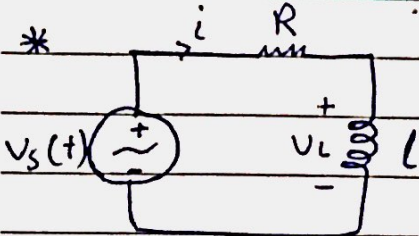

$$V_R = IR$$

$$V_L = L \frac{di}{dt}$$

$$V_s(t) = V_m \cos \omega t$$

$$i_c = C \frac{dv}{dt}$$

⇒ KVL

$$-V_m \cos \omega t + Ri(t) + L \frac{di}{dt} = 0$$

$$Li' + Ri = V_m \cos \omega t$$


Numerical ✓

diff → x

* Introduction (phasor) :-

Vector → space

(Phasor diagram)

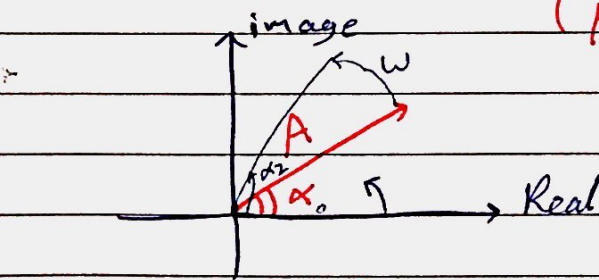

① at t=0

② rotate angular speed

$A \angle \alpha \Rightarrow$ Polar

$$\omega = \frac{\alpha}{t} \Rightarrow \alpha = \omega t + \alpha_0$$

③ Projection x-axis


$$t=0 \Rightarrow A \cos \alpha_0$$

$$t=1 \Rightarrow A \cos \alpha_2 \Rightarrow A \cos(\omega t + \alpha_0)$$

$A \angle \alpha_0$

Phasor domain

* Polar form

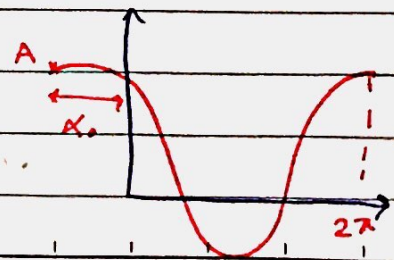

polar form $\Rightarrow A \angle \text{phase-shift} = \alpha_0$

$$\Rightarrow v(t) = 5 \sin(\omega t + 30^\circ)$$

phasor domain

$$v(t) = 5 \cos(\omega t + 30^\circ)$$

$$\sin x = \cos(x - 90^\circ) \quad +90^\circ$$

$$5 \angle -60$$

*

$$A \angle \theta_1$$


$$B \angle \theta_2$$

$$*(A \angle \theta_1) (B \angle \theta_2)$$

$$AB \angle \theta_1 + \theta_2$$

$$* \frac{A \angle \theta_1}{B \angle \theta_2} = \frac{A}{B} \angle \theta_1 - \theta_2$$

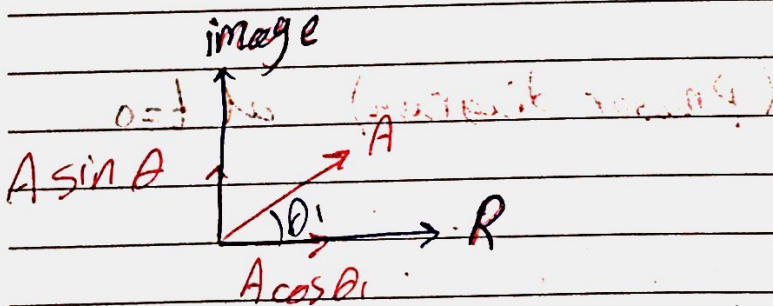polar $A \angle \theta \rightarrow$ rec form $j = \sqrt{-1}$



$$A \cos \theta + j A \sin \theta$$

$$A = \sqrt{R^2 + \text{imag}^2}$$


$$\theta = \tan^{-1} \frac{\text{imag}}{\text{real}}$$

time domain.

$$V(t) = V_m \cos(\omega t + \theta)$$

↳ phasor domain (polar form)

$$V_m \angle \theta$$

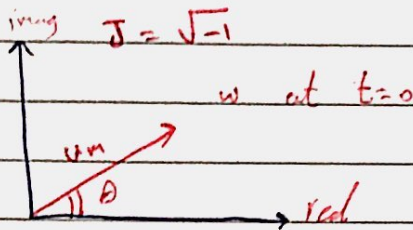


Ex $V(t) = -10 \sin(\omega t + 30) + 20 \cos(\omega t - 45)$ same ω *

$V_1 \Rightarrow -10 \cos(\omega t + 30 - 90)$ V_2

$V_1 = 10 \cos(\omega t + 120)$

$V_2 = 20 \angle -45^\circ$

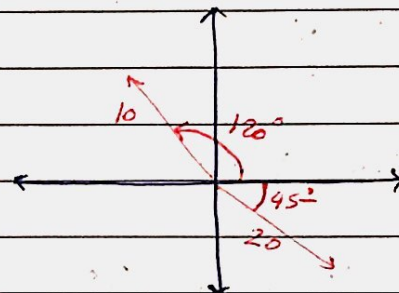* $\sin x = \cos(x - 90^\circ)$
 made \Rightarrow complex




$10 \angle 120^\circ + 20 \angle -45^\circ = 10.66 \angle -30.95 = 10.66 \cos(\omega t - 30.95)$


↳ work graphically ←


Source \Rightarrow phasor load $\Rightarrow R, L, C$

$V_m \cos(\omega t + \theta)$
 I_m

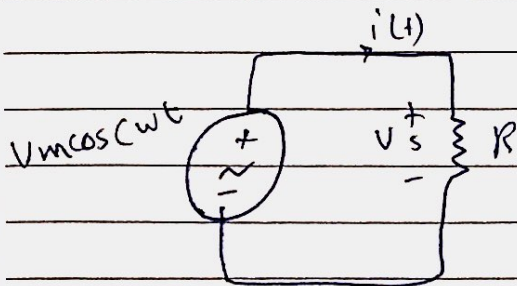

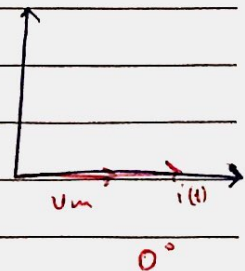$V = IR$
 $V_m \angle \theta = IR$
 $I = \frac{V_m \angle \theta}{R}$



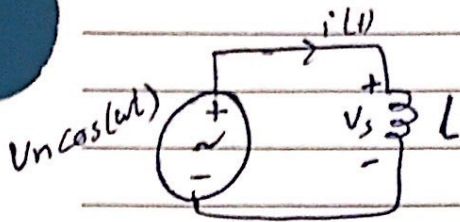


$$V_L = L \frac{di}{dt} \Rightarrow i = \frac{1}{L} \int_0^t V_L(t) dt$$

$$i(t) = \frac{1}{L} \int_0^t V_m \cos(\omega t - 90^\circ) dt$$

$$V_L = V_m \cos(\omega t)$$
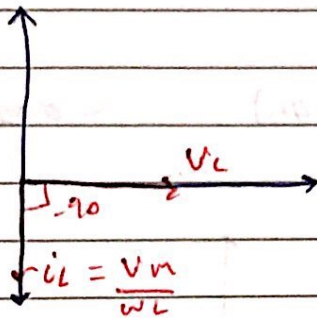
$$i(t) = \frac{V_m}{\omega L} \sin \omega t \Rightarrow \frac{V_m}{\omega L} \angle -90^\circ$$



Phase shift 90°

V_L leads i_L by 90°

i_L lags V_L by 90°

$$V_L = V_m \angle 0^\circ$$

$$I_L = \frac{V_m}{\omega L} \angle -90^\circ$$


$$V_L = \frac{V_m \angle 0^\circ}{\omega L} = \omega L \angle 90^\circ$$

$$I_L = \frac{V_m \angle -90^\circ}{\omega L}$$

$$\text{Impedance} = \frac{V_L}{I_L} = j\omega L \ (\Omega)$$

$L \geq \text{complex}$

$$Z_L = j\omega L \ (\Omega)$$

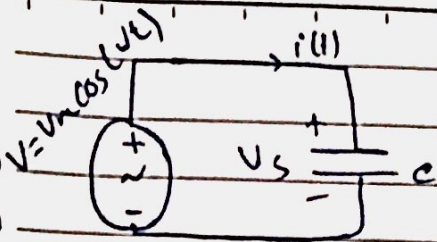


$$i_c = C \frac{dv}{dt}$$

$$i_c = -C (V_m(\omega) \sin \omega t)$$

$$i_c = V_m(\omega C) \cos(\omega t - 90^\circ + 180^\circ)$$

$$i_c = V_m(\omega C) \angle +90^\circ$$

$$V_c = V_m \angle 0$$

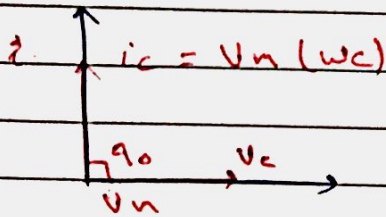

i_c leads V_c by 90°

$$Z_c = \frac{V_c}{I_c} = \frac{V_m \angle 0}{V_m \omega C \angle 90^\circ}$$

$$Z_c = \frac{1}{\omega C} \angle -90^\circ$$

$$Z_c = -j \Omega \quad V_c = I_c Z_c$$

*in summary :-

$$R \longrightarrow R \text{ } (\Omega)$$

$$i \longrightarrow j\omega L \text{ } (\Omega)$$

$$c \longrightarrow \frac{-j}{\omega} \text{ } (\Omega)$$

(Z_1, Z_2)


Series

$$Z_{eq} = Z_1 + Z_2$$

parallel

$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}}$$

Exo-

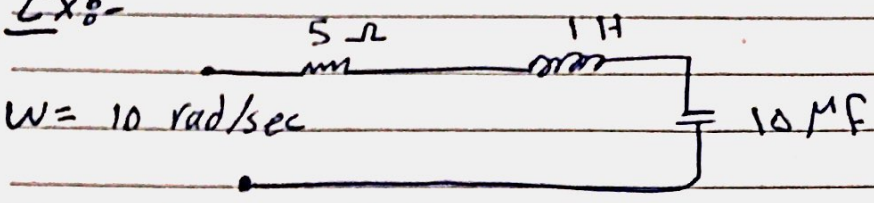

$$Z_C = \frac{-j}{10^{-4}} = -j10^4$$

$$Z_L = j10$$

$$Z_{eq} = 5 + j10 - j10^4 \Rightarrow 5 - j9990$$

in general :-

$$Z = \text{Real} + jx$$

$$Z = R + jx$$

\swarrow \searrow
 +ve resist part \hookrightarrow reactive +ve


image +ve \Rightarrow inductive impedance

I_z lags V_z by θ_z


image part -ve \Rightarrow capacitive impedance

i_z lead V_z by θ_z

$$Z = \frac{V_z}{I_z} = \frac{V_m}{I_m} \angle \theta_v - \theta_i \quad (\theta_z = \theta_v - \theta_i) \text{ phase shift}$$

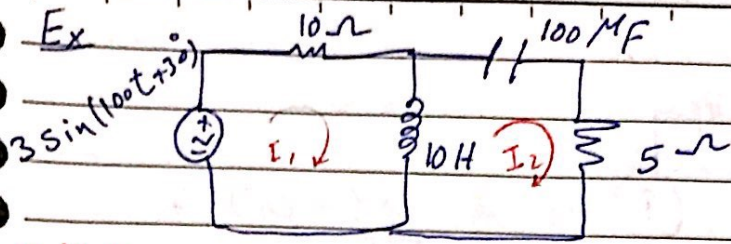

Method 1

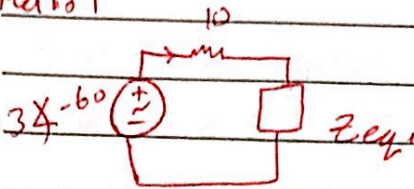

$$Z_{eq} = \frac{5 - j100 \times j1000}{5 + j900}$$

$$I_1 = \frac{3 \angle -60}{10 + Z_{eq}}$$

$$I_2 = I_1 \left(\frac{Z_{eq}}{5 - j100} \right)$$


Method 2 loops

$$3 \angle -60^\circ = +(10 + j1000) I_1 - I_2 (j1000)$$


$$0 = (-j1000) I_1 + I_2 (5 + j1000 - j100)$$

$$I_1 = I_2 \frac{5 + j900}{j1000}$$

Ex

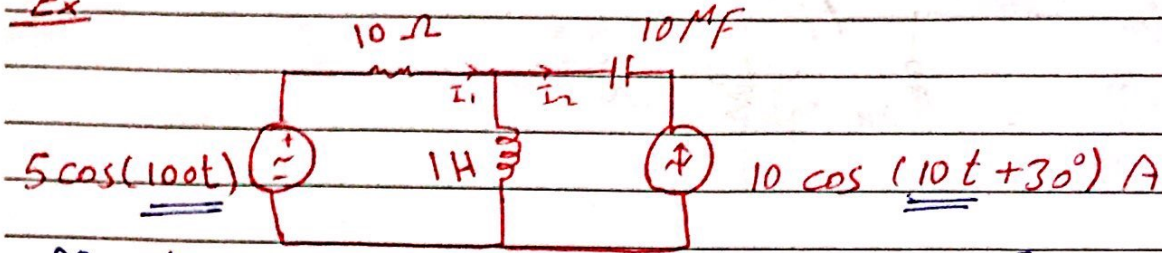

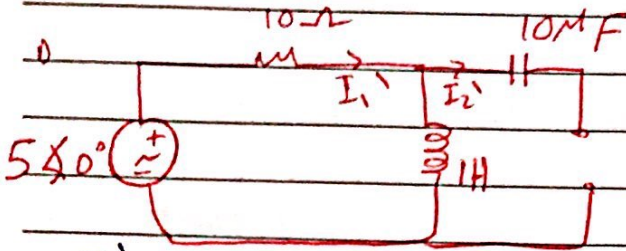different frequency \Rightarrow superposition \Rightarrow Killing $\left\{ \begin{array}{l} V.S \rightarrow S.C \\ C.S \rightarrow O.C \end{array} \right.$




$I_2' = 0$ $\omega = 100 \text{ rad/sec}$

$Z_{1H} = j100 \Omega$

$Z_{10mF} = \frac{-j}{100 + 10mF} = -j1000 \Omega$

$I_1' = \frac{5}{10 + j100}$

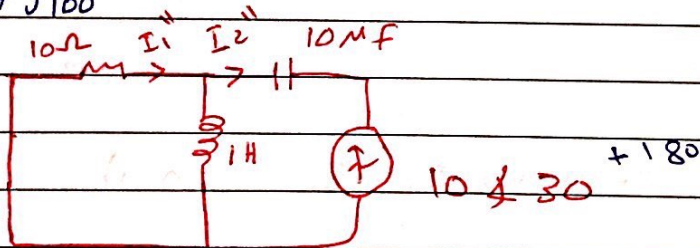

$\omega_2 = 10 \text{ rad/sec}$


$Z_{1H} = j10 \Omega$ $Z_{10mF} = \frac{-j}{(10mF)(10)} = -j10^4 \Omega$

$I_2'' = 10 \angle 30^\circ + 180^\circ$

$10 I_1'' + j10 (I_1'' + 10 \angle 30^\circ) = 0 \Rightarrow I_1'' = \frac{100 \angle -60^\circ}{10 + j10} = A_1 \angle \theta_1''$

$I_1 = A_1' \cos(100t + \theta_1') + A_1'' \cos(10t + \theta_1'')$ $\left\{ \begin{array}{l} \omega = 100 \\ \omega = 10 \end{array} \right.$

Ex 2

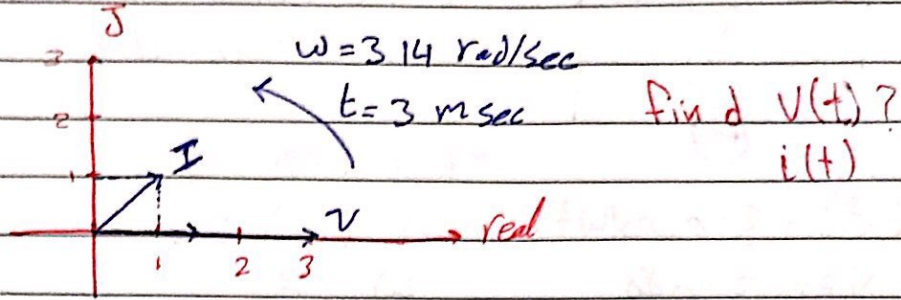

$$V(t) = V_m \cos(314t + \theta_v)$$

$$i(t) = i_m \cos(314t + \theta_i)$$

$$V_m = 3 \text{ V} \quad I_m = \sqrt{2} \text{ A}$$


$$0 = 314 * 3 \text{ m} + \theta_v$$

$$\theta_v = -314 * 3 * 10^{-3} = -942 * 10^{-3} \text{ rad} \quad \frac{*180}{\pi} = -53.97^\circ$$

$$V(t) = 3 \cos(314t - 53.97^\circ)$$

$$i(t) = \sqrt{2} \cos(314t + -53.97^\circ + 45^\circ) \quad \underline{\underline{I \text{ leads } V \text{ by } 45^\circ}}$$


ex:

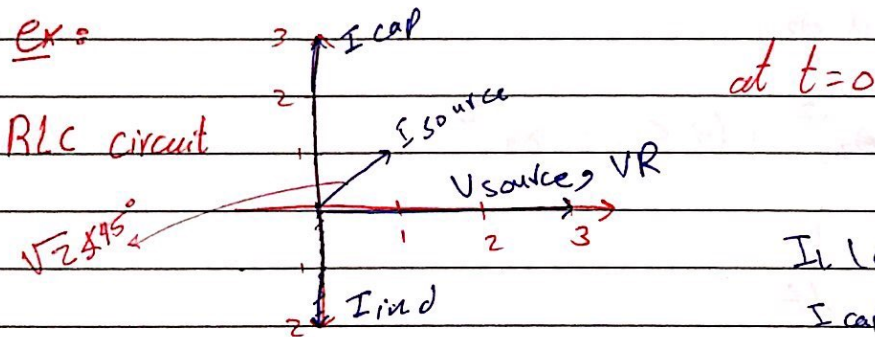

Draw the current ponding circuit, show all Z in Ω :-

$$V_s = 3 \cos(\omega t)$$
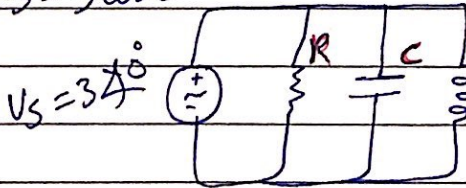
$$Z_L = \frac{V_L}{I_L} = \frac{3 \angle 0^\circ}{2 \angle -90^\circ} = 1.5 j \Omega$$




$$Z_C = \frac{3 \angle 0^\circ}{3 \angle 90^\circ} = -j \Omega$$

$$R = 3 \angle 0^\circ / I_R$$

$$I_R = \sqrt{2} \angle 45^\circ - (3 \angle 90^\circ + 2 \angle -90^\circ)$$

$$\begin{aligned} I_R &= \sqrt{2} \angle 45^\circ - j \\ &= 1 \end{aligned}$$

$$\therefore R = 3 \Omega$$

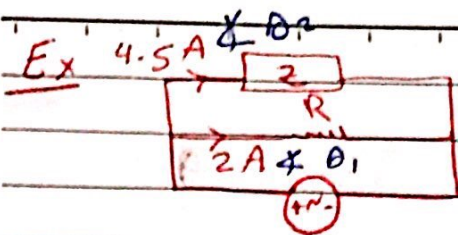

if the current in the impedance Z lags voltage at Z


* I_Z lags V_Z

$$V(t) = 300 \cos(\omega t)$$

$$V_Z = 300 \angle 0$$

a) Find $I_Z(t)$

b) Z

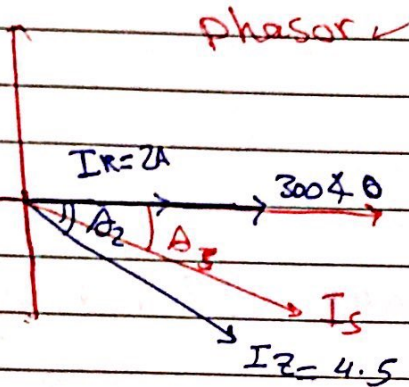

$$I_S \cos \theta_5 = 2 + 4.5 \cos \theta_2$$

$$I_S \sin \theta_5 = 4.5 \sin \theta_2$$

$$I_S^2 = (2 + 4.5 \cos \theta_2)^2 + (4.5 \sin \theta_2)^2$$


$$\theta_2 = \#$$

* Ac power

power = sign $V I$

- ⊕ absorbed
- ⊖ deliver


$p(t) = \text{sign } I(t) V(t)$

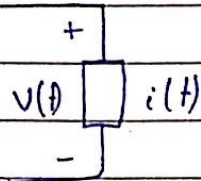

Ac circuit

$v(t) = V_m \cos(\omega t + \theta_v)$
 $i(t) = I_m \cos(\omega t + \theta_i)$
 $p(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$

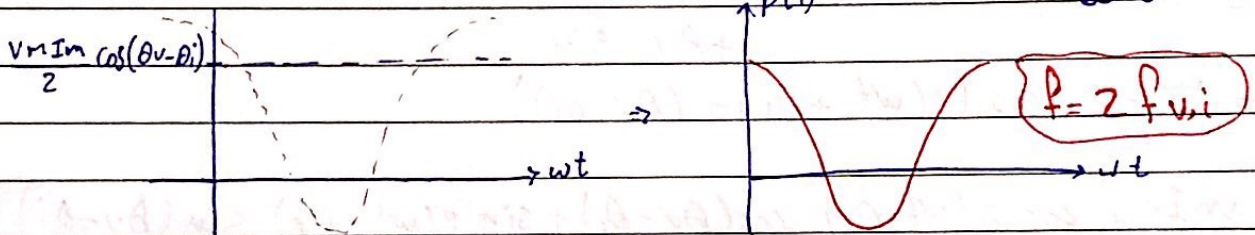$= \frac{V_m I_m}{2} [\cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i)]$
 constant



$\frac{V_m I_m \cos(\theta_v - \theta_i)}{2} = \text{Power avg}$

by $P_{avg} = \frac{1}{T} \int_0^T p(t) \cdot dt$

$P_{avg} = \frac{1}{T} \int_0^T \frac{V_m I_m}{2} [\cos(2\omega t + \theta_v + \theta_i) \cos(\theta_v - \theta_i)]$

$P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$
 ↳ phase shift

if $\theta_v - \theta_i = 0 \Rightarrow$ in phase

$$P = \frac{V_m I_m}{2}$$

if $\theta_v - \theta_i = \pm 90$

$P_{avg} = \text{zero}$

$$P = 0$$

$$P(t) = \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)}_{P_2(t)} + \underbrace{\frac{V_m I_m}{2} (\theta_v - \theta_i)}_{P_{avg}}$$

$$P_2(t) = \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)$$

$$= \frac{V_m I_m}{2} \cos(2(\omega t + \theta_v) - (\theta_v - \theta_i))$$

$$= \frac{V_m I_m}{2} [\cos 2(\omega t + \theta_v) \cos(\theta_v - \theta_i) + \sin 2(\omega t + \theta_v) \sin(\theta_v - \theta_i)]$$

$$P(t) = P_{avg} + P_2(t)$$

$$= \left[\frac{V_m I_m}{2} \cos(\theta_v - \theta_i) [1 + \cos(2(\omega t + \theta_v))] \right] \rightarrow \text{Real power}$$

$$+ \left[\frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2(\omega t + \theta_v) \right] \rightarrow \text{reactive power}$$

$$\underline{\underline{\text{Amp real (active) power}}} = P(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$\underline{\underline{\text{Amp reactive power}}} = Q(t) = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$\text{Complex power} = \underbrace{\frac{V_m I_m}{2} \cos(\theta_v - \theta_i)}_{\text{Real}} + j \underbrace{\frac{V_m I_m}{2} \sin(\theta_v - \theta_i)}_{Q}$$

$$S = P_{\text{avg}} + jQ$$

* S unit \rightarrow V.A

$$VI^* = \frac{V_m I_m}{2} \angle \theta_v + \theta_i \Rightarrow S = \frac{1}{2} \vec{V} \vec{I}^* \quad \text{cong}$$

$$S = P_{\text{avg}} + jQ \Rightarrow |S| \angle \theta_s = |S| \angle \theta_v - \theta_i$$

$-90^\circ < \theta_v - \theta_i < +90^\circ$

$$P_{\text{avg}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \geq 0$$

$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$

$$\theta_v - \theta_i > 0 \Rightarrow Q > 0$$

$$\theta_v - \theta_i < 0 \Rightarrow Q < 0$$

$$\theta_v - \theta_i = 0 \Rightarrow Q = 0$$



V leads i (inductor)

i lead V (capasitor)


pure resistance

$$|S| = \sqrt{P^2 + Q^2}$$
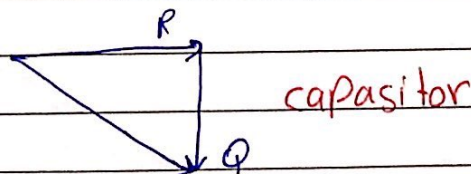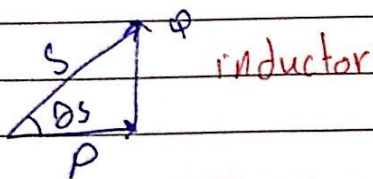
$$\theta_s = \theta_v - \theta_i = \tan^{-1} \frac{Q}{P}$$



Ex:

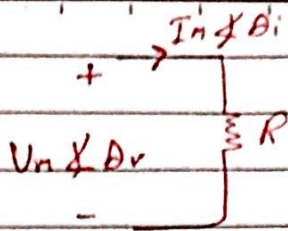

plot instantaneous power $P(t)$
show all max, min, zero crossing

$$P(t) = \frac{1}{2} v_m I_m \cos(\Delta v - \Delta i) + \frac{1}{2} v_m I_m \cos(2\omega t + \Delta v + \Delta i)$$

V_R and I_R are in phase $\rightarrow (\Delta v = \Delta i)$

$$P(t) = \frac{1}{2} v_m I_m [1 + \cos(2\omega t + 2\theta)]$$

at $\omega t = 0$

$$P(0) = \frac{1}{2} v_m I_m [1 + \cos(2\theta)]$$


$$P(t) \geq 0$$

$$P_{\max} \rightarrow \text{at } 2\omega t + 2\theta = 0 \quad (\omega t = -\theta)$$

$$P_{\max} = \frac{1}{2} v_m I_m (1+1) = v_m I_m$$

$$P_{\min} = \text{zero} \rightarrow 2\omega t + 2\theta = 180^\circ = \pi \Rightarrow \omega t = \frac{\pi - 2\theta}{2}$$

if $\theta = 0$

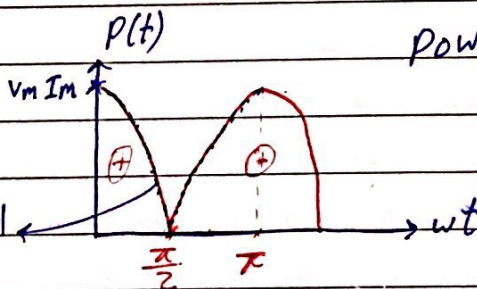

power always +ve in R (absorbed)

$$\omega_p = 2\omega_{v,i}$$

Peak-peak $\Rightarrow P - p = v_m I_m$
(max \rightarrow min)

$$P_{\text{avg}} = \frac{v_m I_m}{2}$$


$$P(t) = \frac{1}{2} v_m I_m [\cos(2\omega t) + 1]$$

$$\cos(2\omega t) = 0 \Rightarrow P(t) = P_{\text{avg}}$$

$$2\omega t = \frac{\pi}{2}$$

$$\omega t = \frac{\pi}{4} \rightarrow P_{\text{avg}}$$

Ex: $I_m \angle \theta_i$

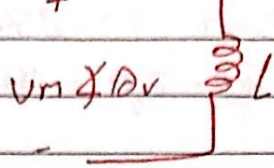

plot

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$

$$\theta_v - \theta_i =$$

ind \Rightarrow i leads

\Rightarrow if $\theta_v = 0 \Rightarrow \theta_i = -90^\circ$

$$p(t) = \frac{1}{2} V_m I_m \cos(2\omega t - 90^\circ)$$

$$* p(\omega t = 0) = 0$$

$$p(\omega t = ?) = p_{\max}$$

$$\text{at } 2\omega t - 90^\circ = 0 \Rightarrow \omega t = \frac{90^\circ}{2} = 45^\circ = \frac{\pi}{4}$$

$$p(0) = 0 \Rightarrow 2\omega t - 90^\circ = 90^\circ$$

$$\omega t = \frac{180^\circ}{2} = 90^\circ$$


$$p_{\min} \Rightarrow 2\omega t - 90^\circ = 180^\circ$$

$$\omega t = \frac{270^\circ}{2} = 135^\circ \Rightarrow \frac{3\pi}{4}$$

$$p_{\max} \Rightarrow \frac{1}{2} V_m I_m$$


$$p_{\min} \Rightarrow -\frac{1}{2} V_m I_m$$

\Rightarrow

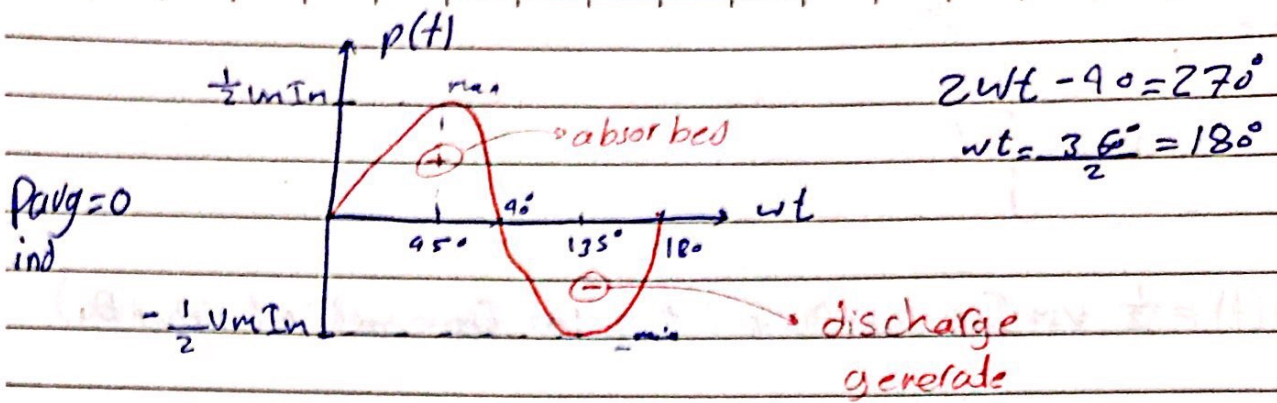

$P = P = V_m I_m = 2 \text{ W}$

Ex capacitor

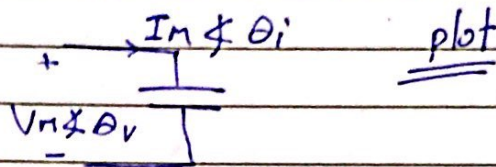

i leads v by 90°

$\theta_v - \theta_i = -90$

if $\theta_v = 0 \Rightarrow \theta_i = 90^\circ$


$p(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$

$\theta_v - \theta_i = -90^\circ$

$\frac{1}{2} V_m I_m \cos(2\omega t + 90^\circ)$

$\frac{1}{2} V_m I_m [\cos 2\omega t \cos 90 - \sin \omega t \sin 90]$

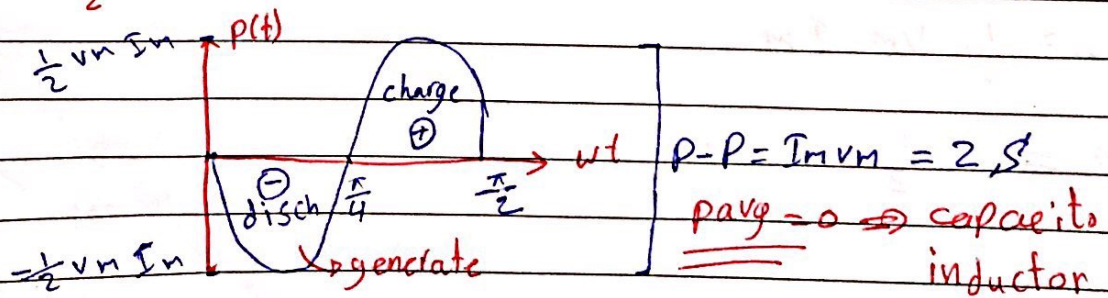$p(t) = -\frac{1}{2} V_m I_m \sin 2\omega t$



Ex $V(t) = 100\sqrt{2} \cos(\omega t)$


$I(t) = \sqrt{2} \cos(\omega t - \theta)$

finda - P- P inst power (P(t)) } a) $\theta = 0$
 Avg power } b) $\theta = 60^\circ$
 Reactive power } c) $\theta = 80^\circ$

$P(t) = \frac{1}{2} (100)(\sqrt{2})(\sqrt{2}) \cos(-\theta i) + \frac{1}{2} (100\sqrt{2})(\sqrt{2}) \cos(2\omega t + \theta i)$

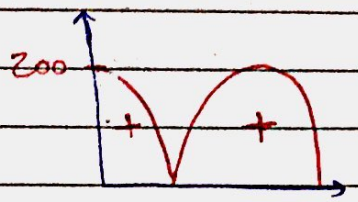a) $\theta = 0 \Rightarrow P(t) = 100 + 100 \cos(2\omega t) = 100(1 + \cos 2\omega t)$

$\therefore \theta v = \theta i = 0$
 \hookrightarrow in phase \Rightarrow resistance



$P-P = 200 \Rightarrow V_m I_m = 100\sqrt{2} \sqrt{2} = 200$
 $P_{avg} = 100 \text{ watt}$
 Reactive = 0

$|S| = \text{constant} = \frac{V_m I_m}{2} = \frac{P-P}{2} = \sqrt{P_{avg}^2 + Q^2}$

b) $\theta = 60^\circ \Rightarrow 100 \cos(-60^\circ) + 100 \cos(2\omega t + 60^\circ)$


$= 50 + 100 \cos(2\omega t + 60^\circ) \rightarrow P(t)$

$P_{avg} = 50, P_{max} = 150$

$P-P = 200 \Rightarrow P_{min} = 50 - 100 = -50$

$Q = \frac{1}{2} V_m I_m \sin(\theta - 60) \sin(2\omega t) = 100 \sin(-60) \sin 2\omega t$

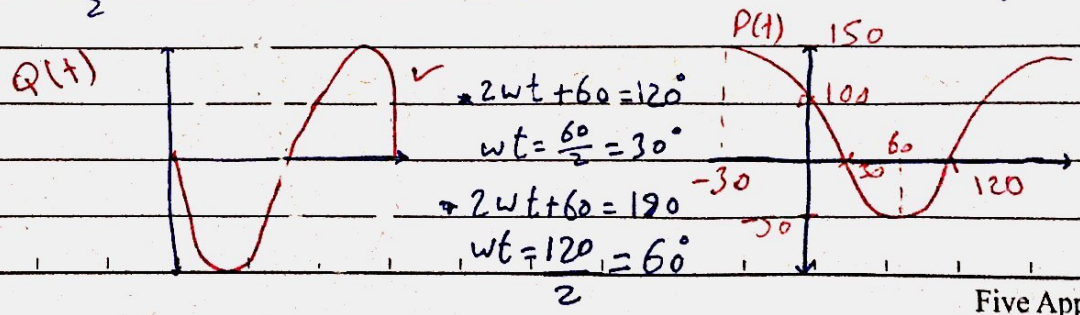$Q = -100 \frac{\sqrt{3}}{2} = -50\sqrt{3} \Rightarrow \text{capacitive } Q(t) = -50\sqrt{3}(\sin 2\omega t)$




AC power

$$S = P_{avg} + jQ$$

power factor = PF = pf

$$PF = \frac{P_{avg}}{|S|} = \frac{P_{avg}}{\sqrt{P_{avg}^2 + Q^2}} \leq 1$$

$$|S| = \sqrt{P^2 + Q^2}$$

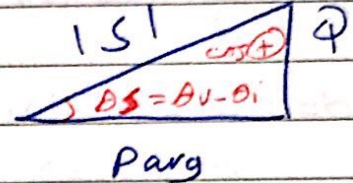

$$\cos \theta_S = \frac{P_{avg}}{|S|} = pf$$

$$\cos(\theta_V - \theta_I)$$

$$0 \leq pf = \cos(\theta_V - \theta_I) \leq 1$$

$Q \geq 0 \Rightarrow$ inductive


$$pf = \cos(\theta_V - \theta_I)$$

$$\theta_V - \theta_I \geq 0$$

$Q = 0 \Rightarrow pf = 1 \Rightarrow$ unity

Resistive $\Rightarrow P_{avg}$

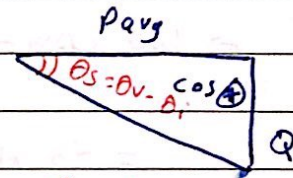$pf = 0.8 \rightarrow$ i lags v
 \rightarrow i leads v



load capacitive

$$pf = \cos(\theta_V - \theta_I)$$

$$\theta_V - \theta_I \leq 0$$

$$\cos \ominus$$


$pf \Rightarrow$ lag $\Rightarrow i$ lags v

\sim inductive $\Rightarrow Q \geq 0$

$pf \Rightarrow$ leads $\Rightarrow i$ leads v

\sim load capacitive $\Rightarrow Q \leq 0$

Ex

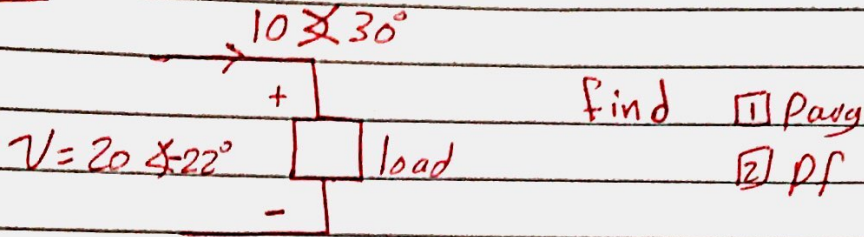

$$1) P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_V - \theta_i)$$

$$= \frac{1}{2} (20)(10) \cos(-22 - 30) = 927 \text{ watt}$$

$$2) pf = \frac{927}{S}, |S| = \sqrt{P_{avg}^2 + Q^2}$$


$$Q = \frac{1}{2} V_m I_m \sin(\theta_V - \theta_i)$$

$$= \frac{1}{2} (20)(10) \sin(-22 - 30)$$

= < 0

$$pf = \cos(\theta_V - \theta_i)$$
$$= \cos(-30 + 22) = \cos(-8) \text{ lead}$$

Ex

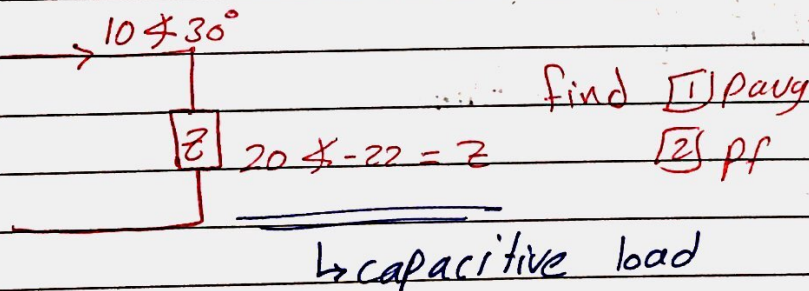

$$1) P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_V - \theta_i)$$

$$V_Z = I_Z = (10 \angle 30^\circ)(20 \angle -22^\circ) = 200 \angle 8^\circ$$

$$P_{avg} = \frac{1}{2} \times 200 \times 10 \cos(8 - 30^\circ) =$$

$$\theta_Z = \theta_V - \theta_i = \theta_S$$

OR

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$V = (I_m \angle \theta_i) \times |Z| \angle \theta_v - \theta_i$$

$$V = \underbrace{I_m |Z|}_{V_m} \angle \theta_v$$

$$P_{avg} = \frac{1}{2} (I_m) |Z| I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} I_m^2 \underbrace{|Z| \cos(\theta_v - \theta_i)}_{R} \Rightarrow R$$

$$P_{avg} = \frac{1}{2} I_m^2 R$$

$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$


$$= \frac{1}{2} I_m^2 |Z| \sin(\theta_z)$$

$$Q = \pm \frac{1}{2} I_m^2 X \xrightarrow{\text{reactance}}$$

$$|S| = \sqrt{P_{avg}^2 + Q^2}$$

$$\theta_s = \theta_v - \theta_i = \theta_z$$

Ex

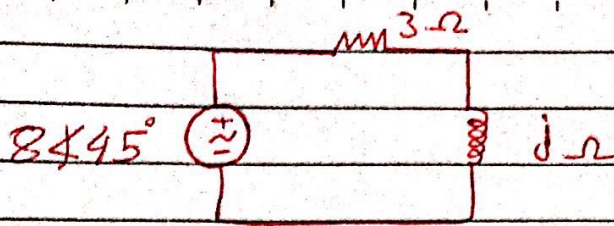

find

- 1) P_{avg} absorbed by R and L.
- 2) P_{avg} supply by the source.
- 3) Q supply / consume by the source.

$$P_{avg} = \frac{1}{2} I_m^2 R$$

$$I = \frac{8\angle 45^\circ}{3+j} = 2.53\angle 26.58^\circ$$

$$P_{avg,R} = \frac{1}{2} (2.53)^2 \cdot 3 = 9.6 \text{ watt consume.}$$

$$P_{avg,L} = \frac{1}{2} V_m I_m \cos(\theta_V - \theta_I)$$

$$= \frac{1}{2} (8)(2.53) \cos(45 - 26.56) = -9.6 \text{ watt supply}$$

$$Q_{source} = \frac{-1}{2} \times 8 \times 2.53 \sin(45 - 26.58) \geq 0$$

$$Q < 0 \Rightarrow \text{supply}$$

$$L \Rightarrow \text{consume } Q \geq 0$$

$$Q_{load} = +\frac{1}{2} I_m^2 X_L$$

$$20\angle -22 = Z$$


capacitive \Rightarrow i leads v

$$P_{avg} = \frac{1}{2} (200)(10) \cos(8 - 30) =$$

$$Q_Z = Q_S = Q_V - \theta_i$$

$$V_Z = I Z = (10\angle 50)(20\angle -22) = 200\angle 28^\circ$$

Ex

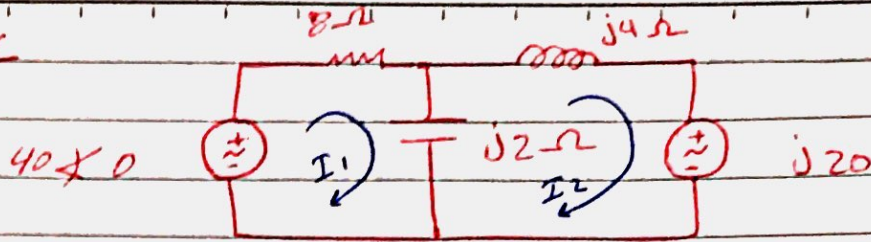

- power in each element
- find pf for the voltage sources

$$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_V - \theta_I) \quad , \quad P_{avg} = \frac{1}{2} I_m^2 R = \frac{1}{2} \frac{V_m^2}{R}$$

mesh $40\angle 0 = (8 - j2) I_1 - I_2(-j2) \quad \dots \text{--- [1]}$

$$-j20 = -I_1(-j2) + I_2(j4 - j2) \quad \dots \text{--- [2]}$$

Cramers

$$\begin{array}{c}
 40\angle 0 \\
 20\angle -90
 \end{array}
 = \begin{bmatrix}
 8 - j2 & j2 \\
 j2 & j2
 \end{bmatrix}
 \begin{array}{c}
 I_1 \\
 I_2
 \end{array}$$

$$B = AX \implies X = A^{-1} B$$

$$I_1 = 5 \angle 53.14^\circ \quad I_2 = 13.6 \angle -17.11$$

sings (+, -)

$$P_{avg} = -\frac{1}{2} (40)(5) \cos(0 - 53.14)$$

40∠0

$$= -100 \cos(-53.14) = -60 \text{ watt (generate power)}$$

(deliver)

$$P_{avg} = +\frac{1}{2} (20)(13.6) \cos(90 - (-17.6)) = -40 \text{ watt generate}$$

j2

$$Q = \frac{1}{2} (40)(5) \sin(0 - 53)$$

40∠0

$$Q_{40\angle 0} > 0 \quad \# \text{ consume}$$

$$P_{j20} = + \frac{1}{2} (20) (13.6) \sin(90 - 17.11)$$

$P_{j20} > 0$ # consume


$$P_{j4} = + \frac{1}{2} I^2 * X = + \frac{1}{2} * (13.6)^2 * 4$$

$$P_{-j2} = - \frac{1}{2} (|I_1 - I_2|)^2 * 2 \quad \text{generate}$$

$$pf = \cos(\theta_v - \theta_i)$$

$$P_{fs1} = 40 = \cos(0 - 53) \text{ lead}$$
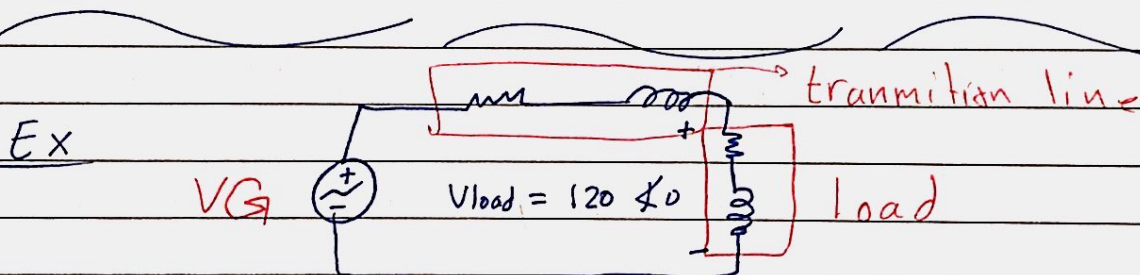
$$P_{fs2} = 120 = \cos(90 - (-17.11)) = \dots \text{ lag}$$



$$Z_{TL} = 1 + j2 \Omega \quad Z_{load} = 8 + j6 \Omega$$

find real and reactive power supplies by the generator?

$$P_{avg, source} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$$


$$I = \frac{V_{load}}{Z_{load}} = \frac{120 \angle 0^\circ}{8 + j6} = 12 \angle -36.9^\circ \text{ A}$$

KVL

$$V_G = (12 \angle -36.9^\circ) (1 + j2) + 120 \angle 0^\circ = 144.8 \angle 4.8^\circ \text{ V}$$

$$P_{avg} = -\frac{1}{2} (144.5) (12) \cos(4.8 - 36.9) = 1295 \text{ watt}$$
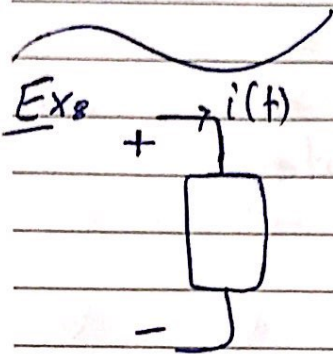
$$Q = -\frac{1}{2} (144.5) (12) \sin(4.8 + 36.9) = 1154 \text{ VAR}$$



$$v(t) = 110 \cos(\omega t + 60^\circ)$$

$$i(t) = 15 \sin(\omega t - 20^\circ)$$

$$\hookrightarrow \cos(\omega t - 110^\circ)$$

$$a) p(t) = \frac{1}{2} (110)(15) \cos(170^\circ) + \frac{1}{2} (110)(15) \cos(2\omega t - 50^\circ)$$


$$b) P_{avg} = -821.9 \text{ W (generate)}$$

$$c) Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) = 825 \sin(170^\circ) = \underline{143.26 \text{ VAR}}$$

consume

$$p.f. = \cos(170^\circ) = -0.984 \text{ (lagging (ind + Resistive))}$$

Exe

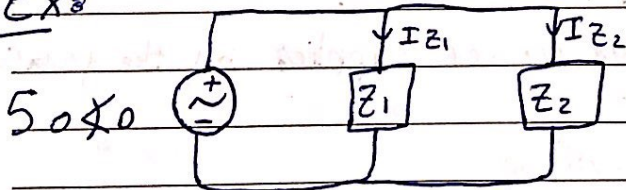

$$Z_1 = 50 \angle 45^\circ, \quad Z_2 = 25 \angle 30^\circ$$

$$a) I_{Z_1}, I_{Z_2}$$

$$c) I_{tot}$$

$$b) S_{absorbed}$$

$$d) S_{source}$$

Soll: $I_{z1} = 1 \angle -45^\circ \text{ A}$ $I_{z2} = 2 \angle -30^\circ \text{ A}$
 $I = 3 \angle -35^\circ$

$$S_{z1} = \frac{1}{2} (50 \angle 0)(1 \angle 45) \Rightarrow \frac{1}{2} \vec{I} \vec{U} \text{ vectors}$$

$$= 25 \angle 45^\circ \text{ ind}$$

$$S_{z2} = 50 \angle 30^\circ$$

$$S_{\text{source}} = -(S_1 + S_2) = -29.86 \angle 42.5^\circ$$

Ex different source with diff frequencies in the circuit

$$P_{\text{avg}} = \frac{1}{2} \left[\underset{1, \omega_1}{I^2} + \underset{2, \omega_2}{I^2} \right] R \Rightarrow \frac{7 \text{ mW}}{I_{\text{tot}}}$$

Ex $i(t) = 2 \cos 10t - 3 \cos 10t$, $R = 4 \Omega$

$$P_{\text{avg}} = \frac{1}{2} [2^2 + 3^2] 4 = 26 \text{ watt}$$

$$i(t) = 2 \cos(10t) - 3 \cos(10t)$$

$$P_{\text{avg}} = \frac{1}{2} (i)^2 \times 4 = 2 \text{ watt}$$

$$i(t) = 2 \cos(10t) - 3 \sin(10t)$$

$$\hookrightarrow i(t) = 2 \cos(10t) + 3 \cos(10t - 90 + 180)$$

$$\Rightarrow 2 \angle 0 + 3 \angle 90 = \sqrt{13} \angle 56.3$$

$$P_{\text{avg}} = \frac{1}{2} (\sqrt{13})^2 \times 4 = 26 \text{ watt}$$

$$\text{Ex: } V(t) = 8 \sin(200t) - 6 \cos(200t - 45^\circ) - 5 \sin(100t) + 4$$

$$\Rightarrow \underbrace{8 \cos(200t - 90^\circ)}_{\text{same } f} + \underbrace{6 \cos(200t - 45 + 180)}_{\text{same } f} - 5 \sin(100t) + 4$$

$$8 \angle -90^\circ + 6 \angle 135^\circ = 5.67 \angle -48^\circ$$

$V(t)$ has three components:

1) $5.67 \angle -48^\circ$ ($\omega = 100$)

2) $5 \angle -90^\circ$ ($\omega = 200$)

3) 4 (DC)



$$P_{\text{avg}} = \left(\frac{1}{2} [5.67^2 + 5^2] + 4^2 \right) \times \frac{1}{4}$$

$$\Downarrow \frac{1}{2} \frac{V_{AC}^2}{R} + \frac{V_{DC}^2}{R}$$

* Effective value of voltage / current (RMS)

$Ac \Rightarrow V(t)$

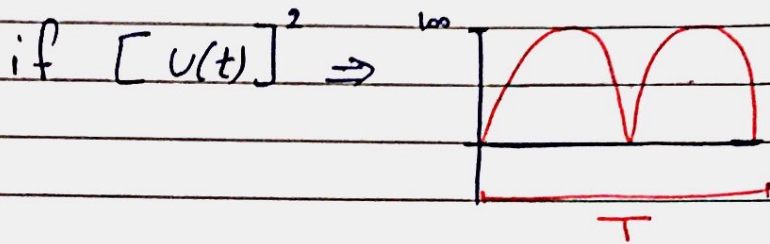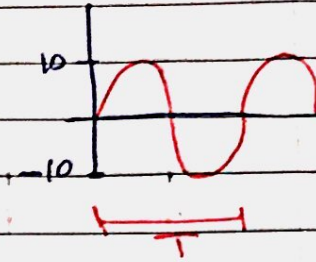$V_{avg} = \frac{1}{T} \int_0^T V(t) dt = 0$




$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$ root mean square
(also applicable for current)

$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T (V_m \cos(\omega t))^2 dt} \Rightarrow V_{RMS} = \frac{V_m}{\sqrt{2}}$ only sinusoidal source


$P_{avg} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{RMS} I_{RMS} \cos(\theta_v - \theta_i)$

$\vec{S} = \frac{1}{2} \vec{V} \vec{I}^* \Rightarrow |S| = V_{RMS} I_{RMS}$

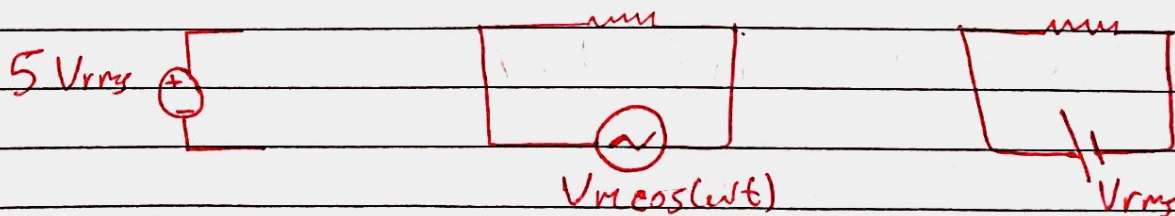

$P_{avg} = \left(\frac{V_m}{\sqrt{2}}\right)^2 / R$ * if we want to replace AC source with DC giving same power.

Ex if $V(t)$:- Find V_{rms}

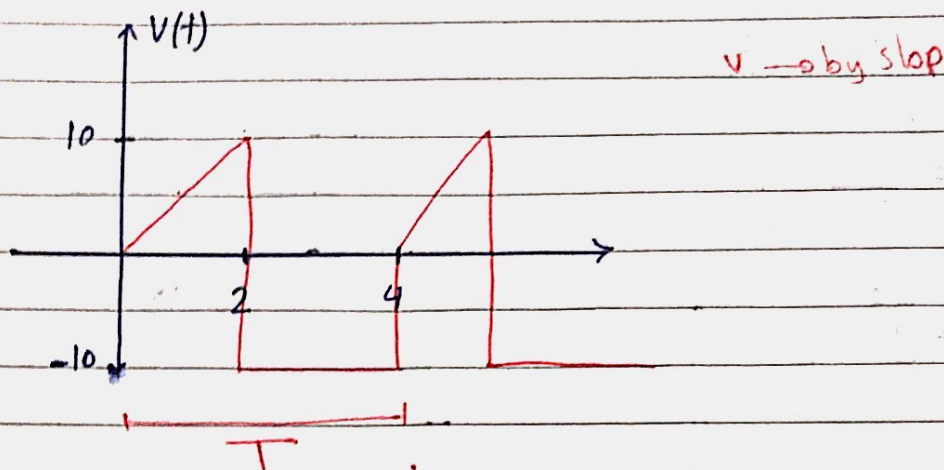

$$V_{rms} = \sqrt{\frac{1}{4} \left[\int_0^2 (5t)^2 dt + \int_2^4 (-10)^2 dt \right]} = \sqrt{\frac{1}{4} \left[\frac{25t^3}{3} \Big|_0^2 + 100t \Big|_2^4 \right]}$$

$$= \sqrt{\frac{1}{4} \left[25 \times \frac{8}{3} + 200 \right]} = 8.165 \text{ V}_{rms}$$

* different sources $\omega_1 \neq \omega_2$

if V, I are sinusoidal (cos, sin) $\Rightarrow V_{rms} DC = V_{DC}$

$$V_{rms} = \sqrt{V_{rms1}^2 + V_{rms2}^2 + \dots}, \quad I_{rms} = \sqrt{I_{rms1}^2 + I_{rms2}^2 + \dots}$$

Ex: $V(t) = 6 \cos(25t) + 5 \sin(30t) + 4$


$$V_{rms} = \sqrt{\left(\frac{6}{\sqrt{2}}\right)^2 + \left(\frac{5}{\sqrt{2}}\right)^2 + 4^2} = 6.82 \text{ V}_{rms}$$

$$V(t) = 6 \cos(25t) + 4 \sin(25t + 30^\circ)$$


$$\Rightarrow V_{rms} = 6.16 \text{ V}_{rms}$$

بدرجته مع وتبديل $\frac{V_1}{\sqrt{2}}$

* max power transfere

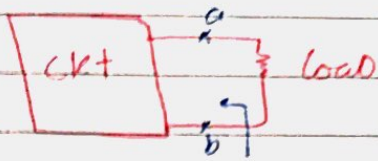

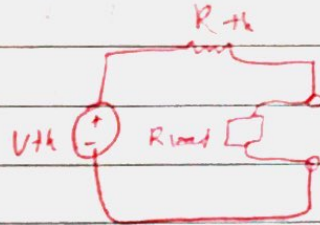$R = ?$ $P_{load} \Rightarrow \text{Max} \Rightarrow \text{min losses}$




$P = I^2 R_{load}$


$= \left(\frac{V_{th}}{R_{th} + R_{load}} \right)^2 \times R_{load}$

$P_{max DC} = \frac{V_{th}^2}{4 R_{th}}$

$\rightarrow R_{th} = R_{load}$

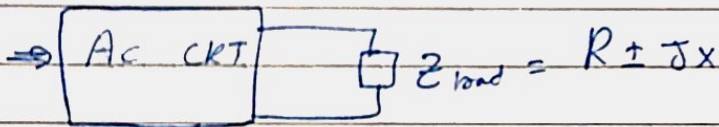


$P = \frac{1}{2} I^2 R_{load}$

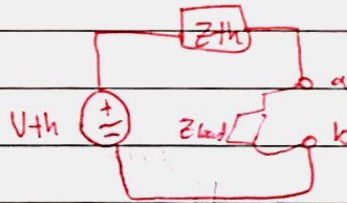

$I = \left| \frac{V_{th} \angle \theta}{Z_{th} + Z_{load}} \right|$


$Z_{load} = Z_{th}^*$

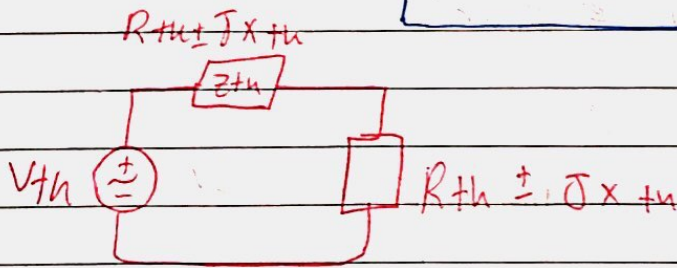

$P_{Rth} = \frac{1}{2} I^2 R_{th}$



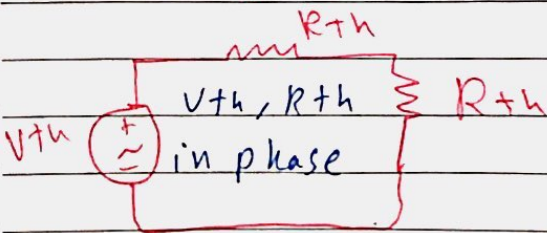$P = \frac{1}{2} \left(\frac{V_{th}^*}{2 R_{th}} \right)^2 R_{th}$



$= \frac{V_{th}^2}{8 R_{th}} = P_{max}$

under max condition

$$\eta = \frac{P_{out}}{P_{in}}$$


$$P_{out} = P_{load} = \frac{|V_{th}|^2}{8R_{th}}$$

$$P_{source} = P_{in} = \frac{1}{2} V_{th} I \cos(\theta V - \theta i)$$

$$I = \frac{V_{th}}{2R_{th}}$$

$$P_{in} = \frac{1}{2} V_{th} \left(\frac{V_{th}}{2R_{th}} \right) = \frac{V_{th}^2}{4R_{th}}$$

$$\frac{P_{out}}{P_{in}} = 0.5 = 50\%$$

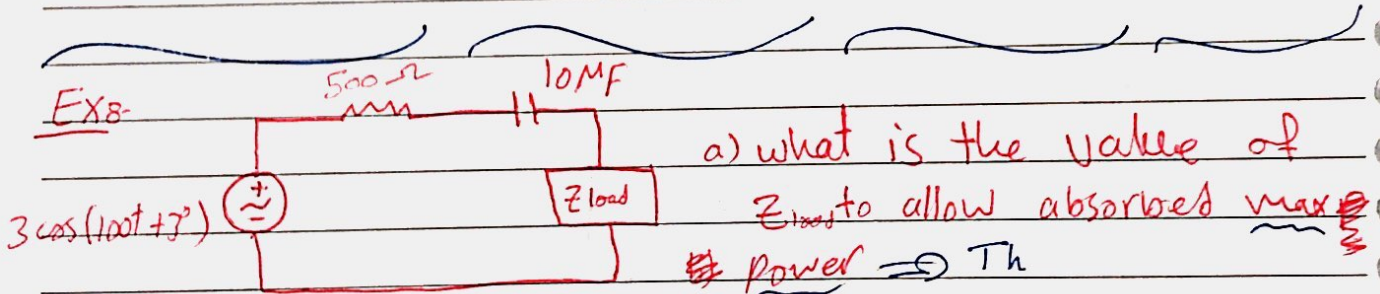

a) $10^6 \Rightarrow -j = -j1000 \Omega$
 $10^6 \times 100$

b) " " " " " "
inductive component . . .

$$Z_{th} = 500 - j1000$$

$$Z_{load} = 500 + j1000$$


$$P_{max \text{ load}} = \frac{V_{th}^2}{8R_{th}} = \frac{3^2}{8 \times 500}$$

b) $X = \omega L$

$$\frac{1000}{100} = 10 \text{ H} = L$$

Case II


load \Rightarrow Pure Resistive

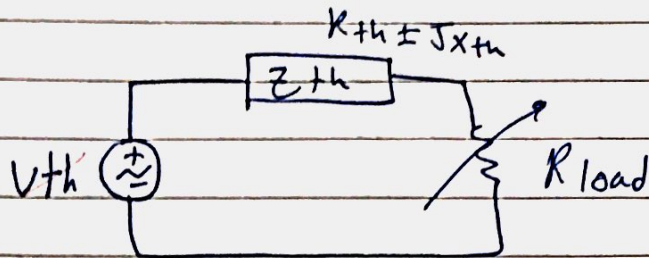

$$* R_{load} = |Z_{th}|$$

$$P_{max} = \frac{1}{2} |I|^2 R_{load}$$

$$I = \frac{V_{th}}{Z_{th} + R_{load}} = |I| \angle 0$$

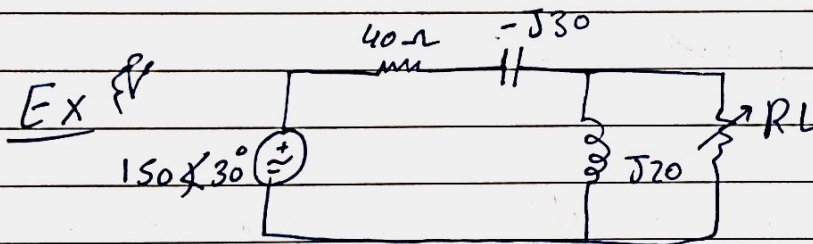

- 1) find R_L that will absorbed max power from ckt
- 2) P_{max} load


1) $R_L = |Z_{th}|$

$$Z_{th} = \frac{(40 - j30) (j20)}{40 - j10}$$

$$= 9.412 + j22.35$$

$$|Z_{th}| = 24.25 \Omega = R_{load}$$


2)

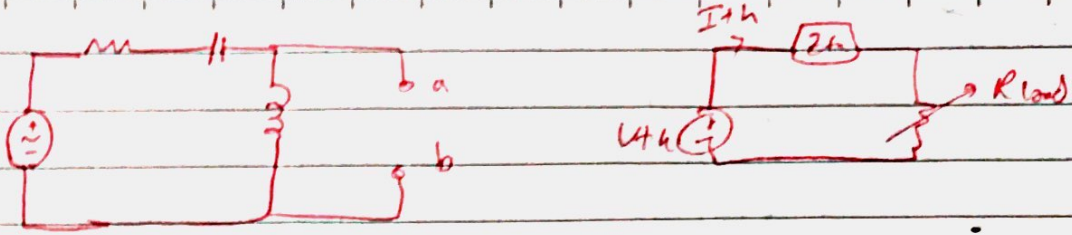

$$V_{o.c} = \left(\frac{150 \angle 30^\circ}{40 - j30 + j20} \right) \times j20 = 72.76 \angle 134^\circ$$

$$I_{th} = \frac{72.76 \angle 134^\circ}{9.412 + j22.35 + 24.25} = 1.8 \angle 100.42^\circ$$
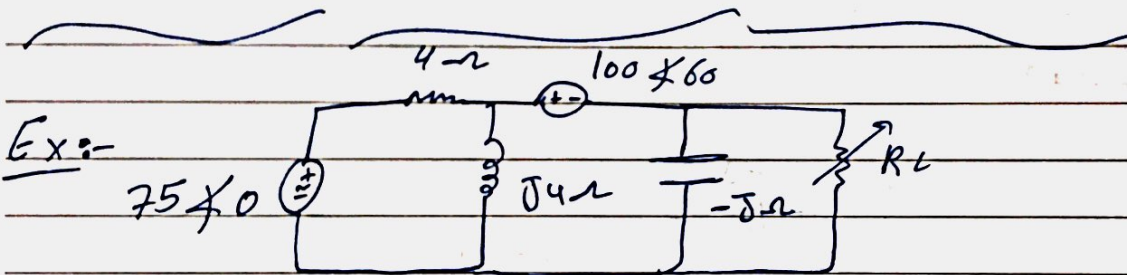
$$P_{max} = \frac{1}{2} (1.8)^2 \times 24.25 = 39.29 \text{ watt}$$



- find R_L which would result in max power transfer.
- power_{max, load}.


a) V.S \rightarrow short ckt $R_L \rightarrow$ o.c

$$4 \parallel j4 \parallel -j$$

$$\left(\frac{4(j4)}{4 + j4} \right) \parallel -j$$

$$Z_{th} = 1.26 \angle -71.6^\circ \quad R_{load} = 1.26 \Omega$$

b) $R_{load} \rightarrow V_{o.c}$

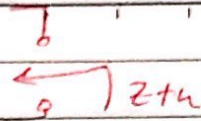

by mesh

$$75 \angle 0 = (4 + j4) I_1 - j4 I_2$$

$$-100 \angle 60 = -j4 I_1 + (j4 - j) I_2$$

;

$$V_{o.c} = I_2 (-j) \Rightarrow P_{max} - -$$

