

$V_{s1} = 5V$      $V_{s2} = -12.5V$     find  $I_1$  using mesh analysis.

Supermesh  $\rightarrow 5 + I_x + 2I_1 = 12.5$

$$I_x + 2I_1 = 7.5 \quad \text{--- (1)}$$

inside supermesh  $\rightarrow I_x - I_1 = 3I_x$

$$I_1 = -2I_x \quad \text{--- (2)}$$


(2) in (1)  $\rightarrow I_x + 2(-2I_x) = 7.5$

$$I_x - 4I_x = 7.5$$


$$-3I_x = 7.5$$

$$I_x = -2.5$$

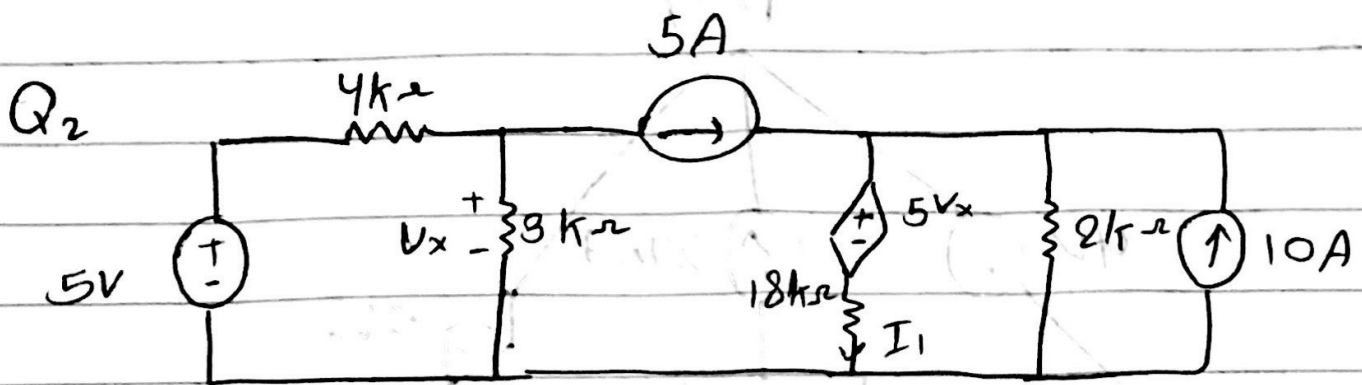from (2)  $\rightarrow I_1 = -2(-2.5) = 5\text{mA} \#$



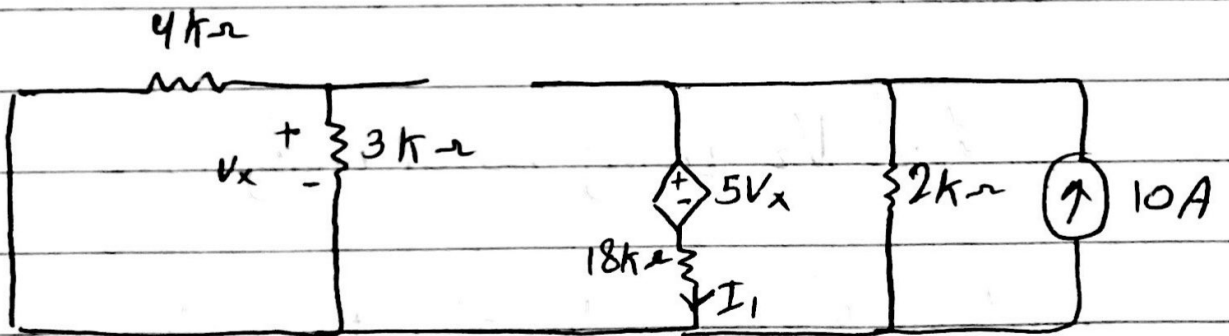find the contribution of (10A) only in the value of  $I_1$




\* Kill 5A and 5V sources.

Current division  $\rightarrow$


$$10 \cdot \frac{2}{18+2} = \frac{20}{20} = \boxed{1A}$$

Q3

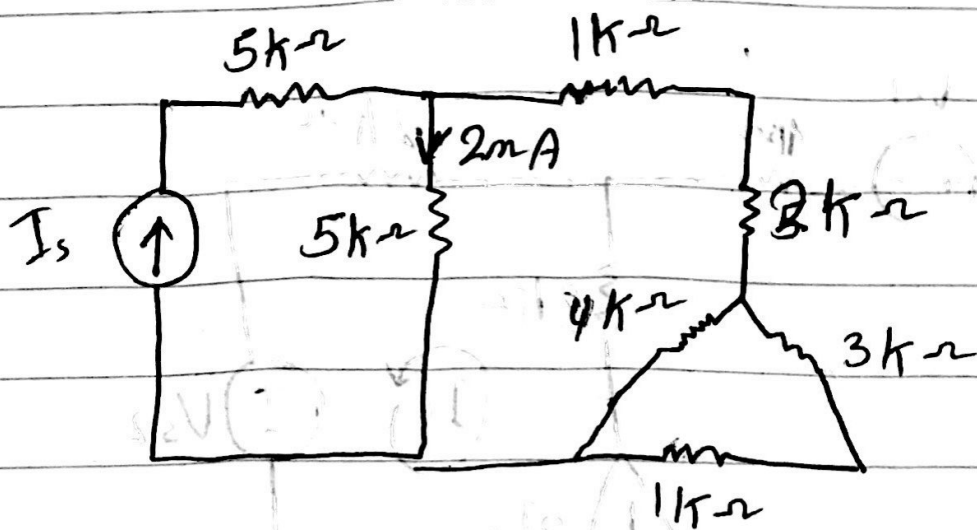

- find the absorbed power by  $5k\Omega$ .

$$3 + 1 = 4 // 4 = 2 + 2 + 1 = 5$$

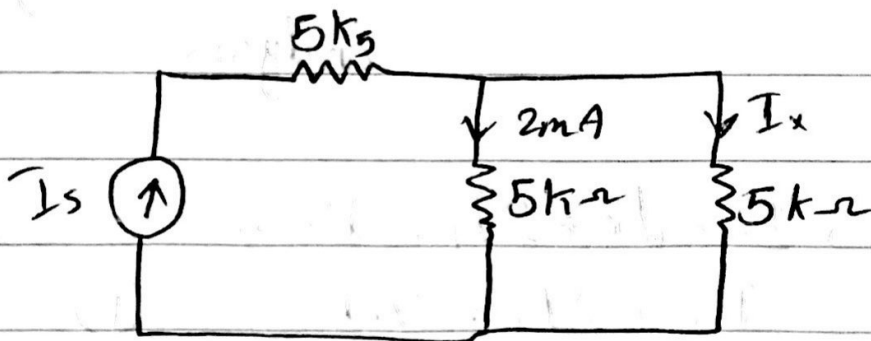

$$5 // 5 \rightarrow \text{voltage across } 5k\Omega = 10V$$


$$I_x = \frac{10V}{5} = 2$$

$$I_s = 2 + 2 = 4A$$

$$P = I^2 R$$

$$= 16 \times 5 = 80mW$$

Q4

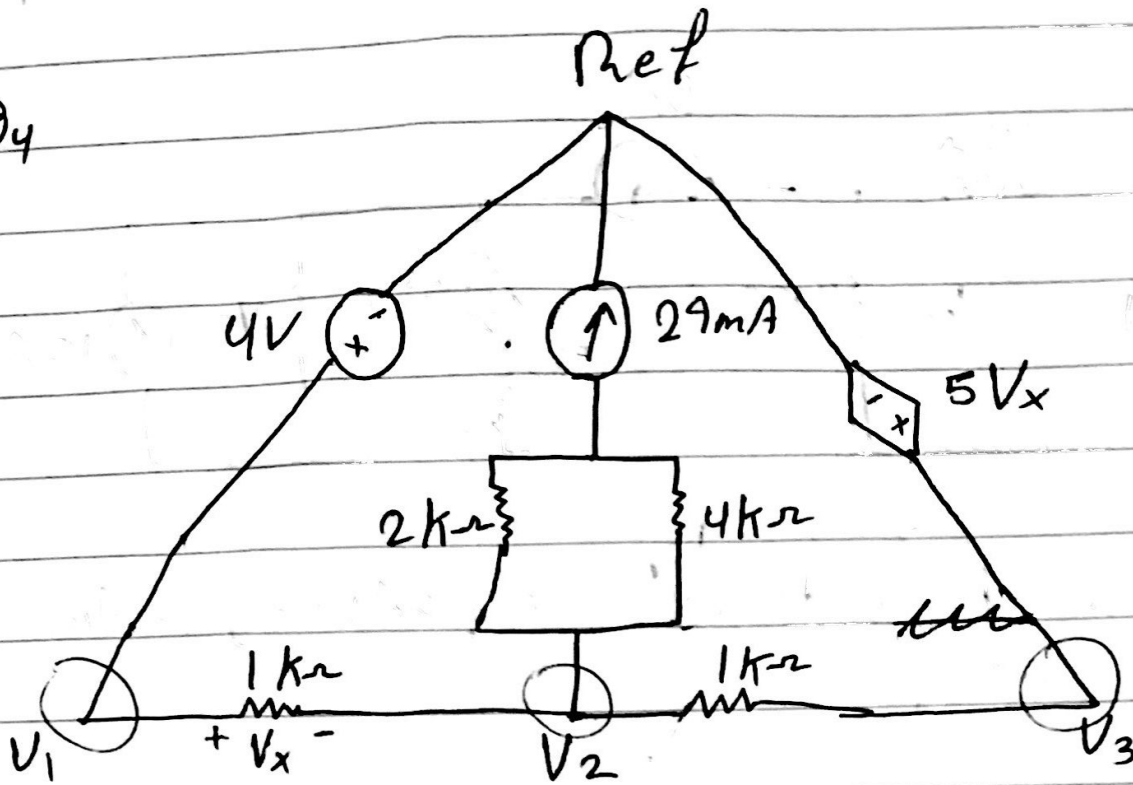

- Find  $V_2$  using nodal analysis.

$$\begin{aligned} \text{KCL at } V_2 \rightarrow V_2 - V_1 + V_2 - V_3 + 29 &= 0 \\ 2V_2 - V_3 - 4 + 29 &= 0 \\ 2V_2 - V_3 &= -25 \quad \dots (1) \end{aligned}$$

$$\begin{aligned} \text{KCL at } V_3 \rightarrow V_3 - 5V_x &= 0 \\ V_3 - 5(4 - V_2) &= 0 \quad \boxed{V_x = V_1 - V_2} \\ V_3 - 20 + 5V_2 &= 0 \\ V_3 + 5V_2 &= 20 \quad \dots (2) \end{aligned}$$

$$\begin{aligned} 2V_2 - V_3 &= -25 \\ V_3 + 5V_2 &= 20 \\ 7V_2 &= -5 \end{aligned}$$

$$\boxed{V_2 = \frac{-5}{7}}$$