

SUBJECT:

First exam Fall 2018

problem 1. solve the following short problems

[A] If $(212)_z = (38)_{10}$ then $z = \dots \Rightarrow$ لوحة
لوحة اليسار decimal

$$2z^0 + 1z^1 + 2z^2 = 38 \quad \text{اليسار} \quad \text{اليمين}$$

$$2z^2 + z + 2 = 38 \quad \text{اليسار} \quad \text{اليمين}$$

$$2z^2 + z - 36 = 0 \quad \text{اليسار} \quad \text{اليمين}$$

$$z = 4 \quad \text{or} \quad \left(\frac{-9}{2}\right) \rightarrow \text{this is ignored.}$$

answer is $z = 4$

SUBJECT:

[B] $(7706)_8$ is equal to $(3F18)_{16}$



00111111 - 00011000

↓ 3 F 1 8

[C] $(73)_{10}$ is equal to $(1243)_5$

$\frac{73}{5} \quad 3$



$\frac{14}{5} \quad 4$

$\frac{2}{5} \quad 2$

0

D (1293) is equal to (00100101010011)_{BCD}

0001 0010 1001 0011

E dual expression for function.

$$F(A, B, C, D) = (\bar{A} + A(\bar{C} + D)) \cdot A$$

$$\text{dual } F = (\bar{A} \cdot (A + (\bar{C} \cdot D))) + A$$

F simplified complement expression for

$$F(A, B, C) = \bar{A} \cdot \bar{C} + \bar{A} \cdot C$$

$$\text{dual } F = \bar{A} \cdot C : (\bar{A} + C)$$

$$\bar{F} = A \cdot C \cdot (A + \bar{C})$$

then : simplify

but for better answer

$$F(A, B, C) = \bar{A} \bar{C} + \bar{A} C \rightarrow \text{first simplify } (\bar{F})$$

$$= \bar{A} (\bar{C} + C)$$

$$= \bar{A} \rightarrow \text{then } \bar{F} = A$$

SUBJECT:

$$F(A, B, C) = \bar{A} + \bar{C} + \bar{A} \cdot \bar{C} = \bar{A} \cdot \bar{C} + \bar{A} \cdot C$$

Upcoming topics

K-means

[G1] Assume N is a 3-digit number

represented in octal, minimum number
of digits needed when N in decimal is (?)?

octal (base 8) \rightarrow 3 digits.

$8^3 = 512$ combinations to reach the
maximum possible combination

of 3 digits ($N=777$)₈

$$\text{so } \log_{10} 512 = 2.7$$

so you need 3 digits

SUBJECT:

/ /

E) The even parity bit for the following:


$(1100110011110111)_2$ code word

is: 1

E) The gate input cost with inverters
counted of

$$F(A, B, C, D) = (\bar{A} + A(\bar{C} + D)) \cdot A$$

GN: (10)

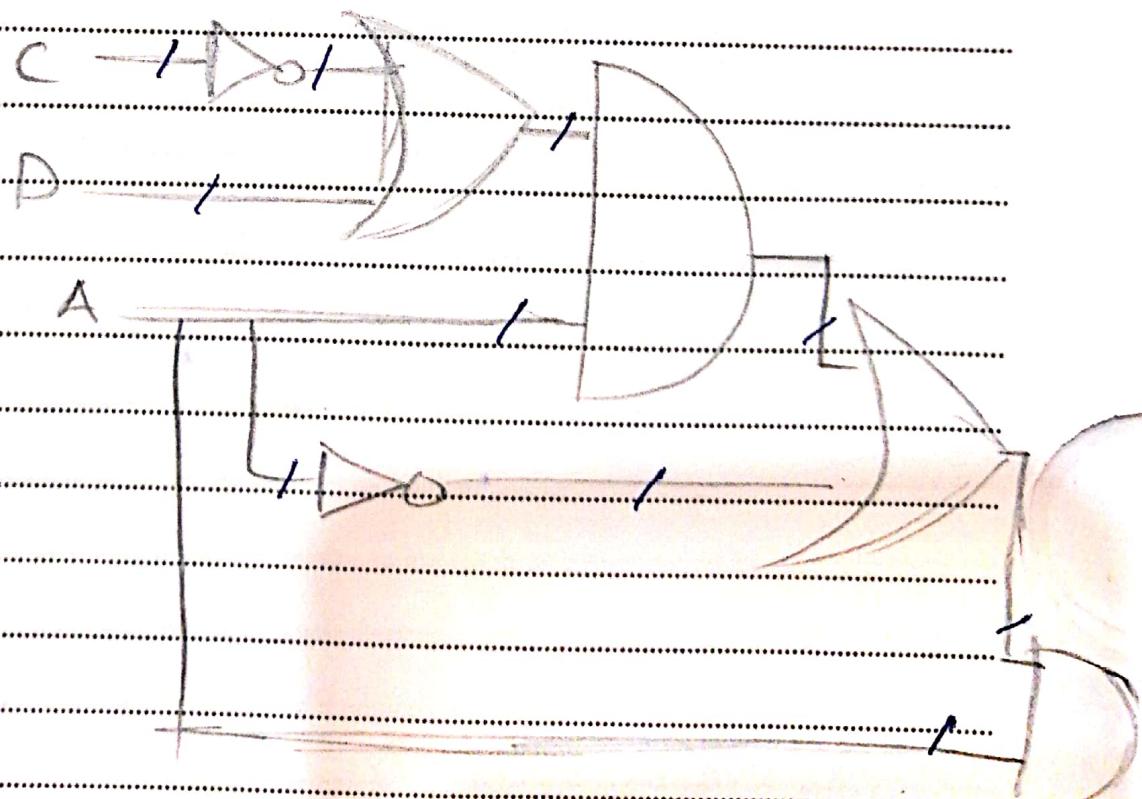

S T A R S N O T E B O O K

SUBJECT:

1 / 1

Given $F(A, B, C) = \Sigma_m(1, 4, 5) + \Sigma_d(0, 6)$

Then $\bar{F}(A, B, C)$?

0, 1, 2, 3, 4, 5, 6, 7

$$\bar{F}(A, B, C) = \Sigma_M(1, 4, 5) + \Sigma_d(0, 6)$$

↓


م تابع لذاته
وطابع ROM جدول المخرج

بس تكون عاونه مخرج (0)

SUBJECT: _____ / /

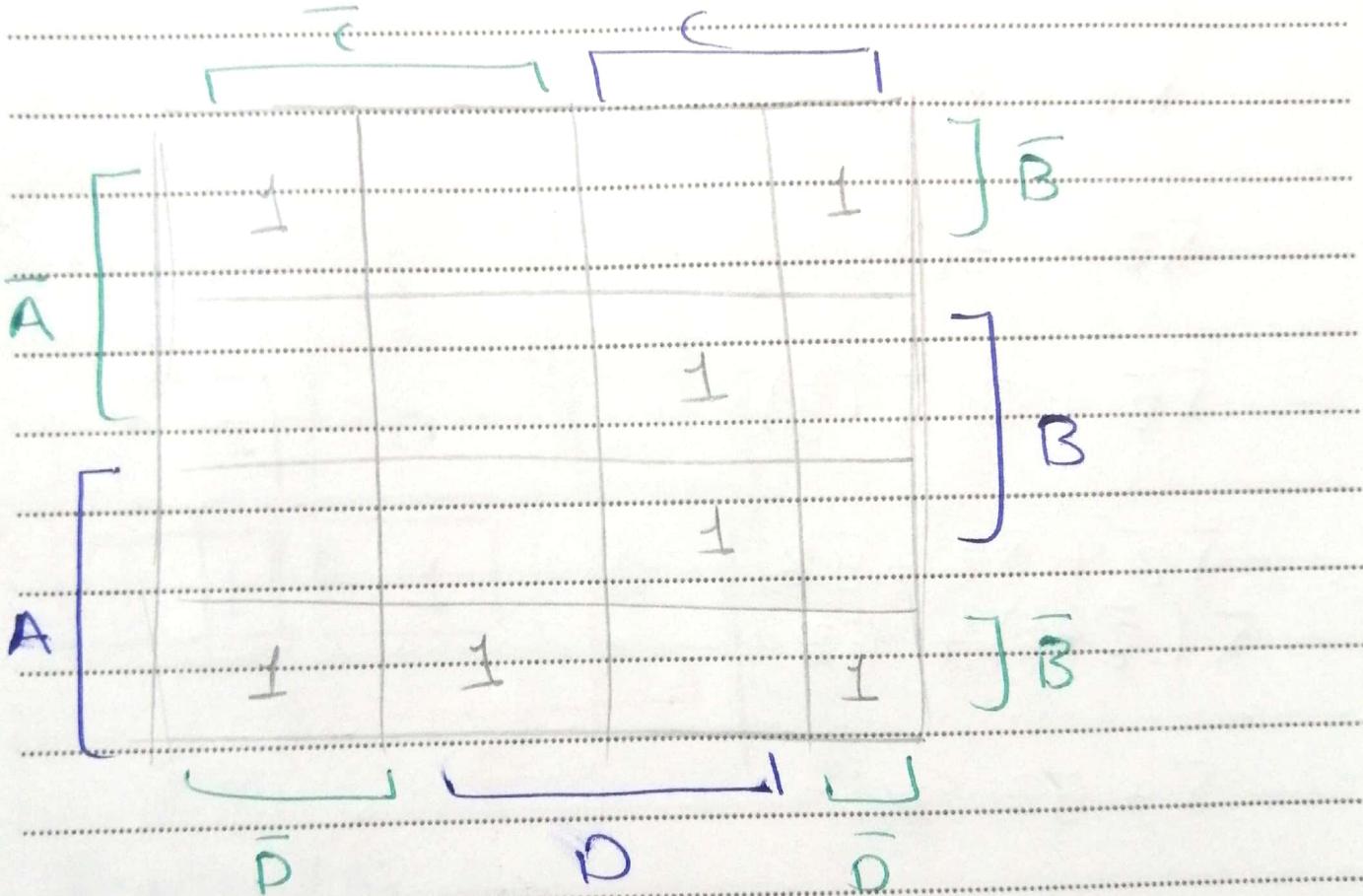Problem 2:

Fill-in the following k-map for function
 $F(A, B, C, D) = (\bar{B}\bar{D} + \bar{B}CD + A\bar{B}\bar{C}D)$



SUBJECT.....

Problem 3 use Boolean algebra only, prove that:

$$\overline{x+z} + \overline{x}yz + \overline{y}z = \overline{x} + \overline{y}z$$

$$\overline{x}\overline{z} + \overline{x}yz + \overline{y}z =$$

$$\overline{x}\overline{z} + z(\overline{x}y + \overline{y}) =$$

$$\overline{x}\overline{z} + z(\overline{x} + \overline{y}) =$$

$$\overline{x}\overline{z} + \overline{x}z + \overline{y}z$$

$$\overline{x}(\overline{z} + z) + \overline{y}z$$

$$\overline{x} + \overline{y}z$$

Problem 4: consider the following function
for the function $F(A, B, C, D)$ identifying
its prime implicants and determine which

are essential.

	\bar{B}		B	
	0	1	0	1
A	1	0	0	1
C	0	1	1	1
D	1	1	0	0

Implicants:

$\bar{B}C \rightarrow$ essential

$\bar{A}\bar{D} \rightarrow$ essential


$A\bar{B}C \rightarrow$ essential

$A\bar{B}C$

$B\bar{C}D$

$\bar{A}BD \rightarrow$ essential

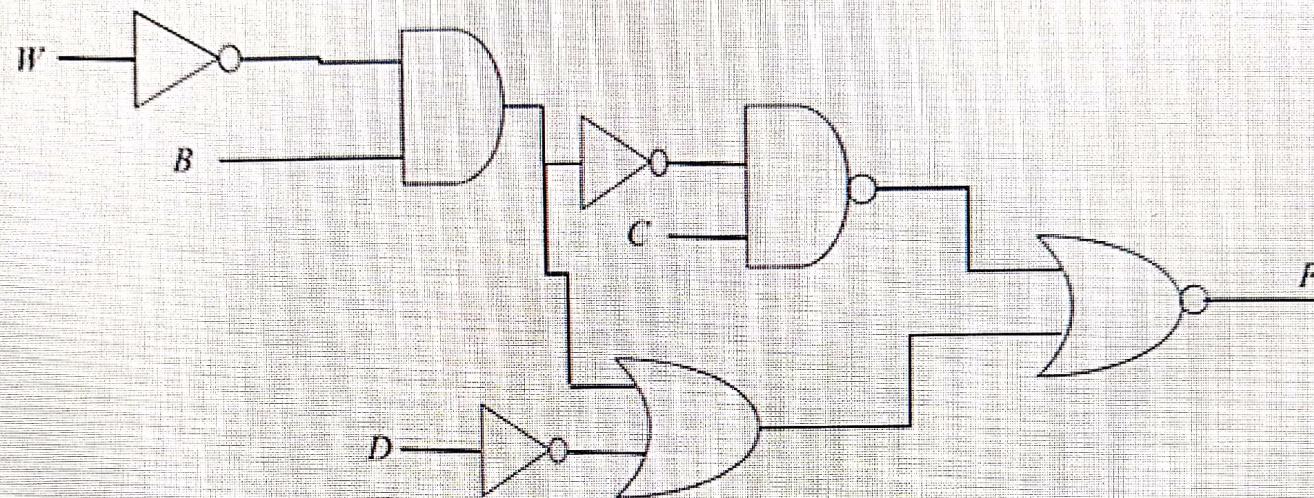
Problem 5: In the space give below redesign the following function using NOR gates and inverters only. (2 Points)



SUBJECT:

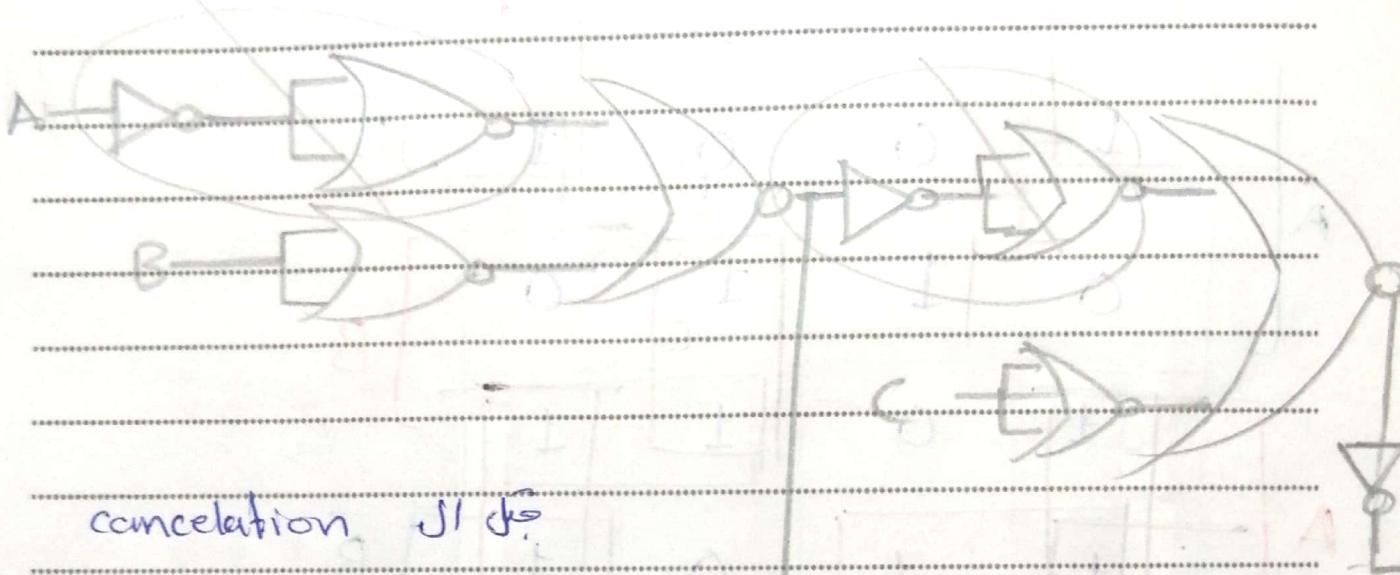
Problem 5

redesign the following function using
NOR gates and inverters only.




cancellation J1 J2

(part) 4 all inverters J

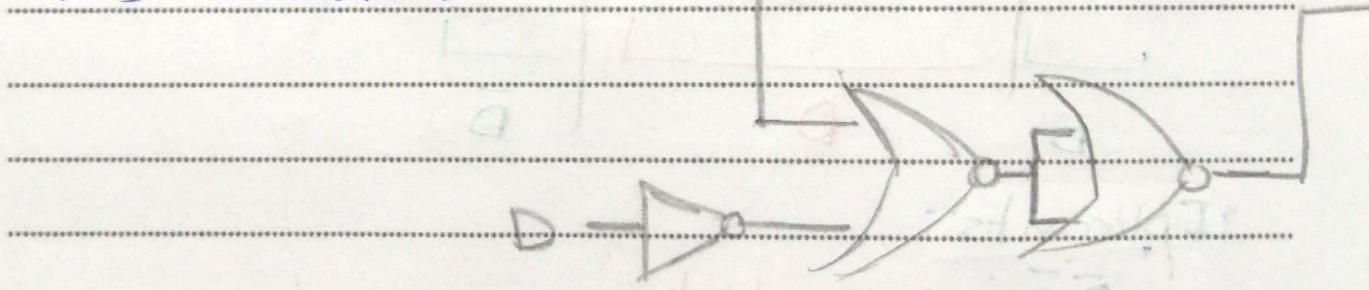

cancellation J1 J2

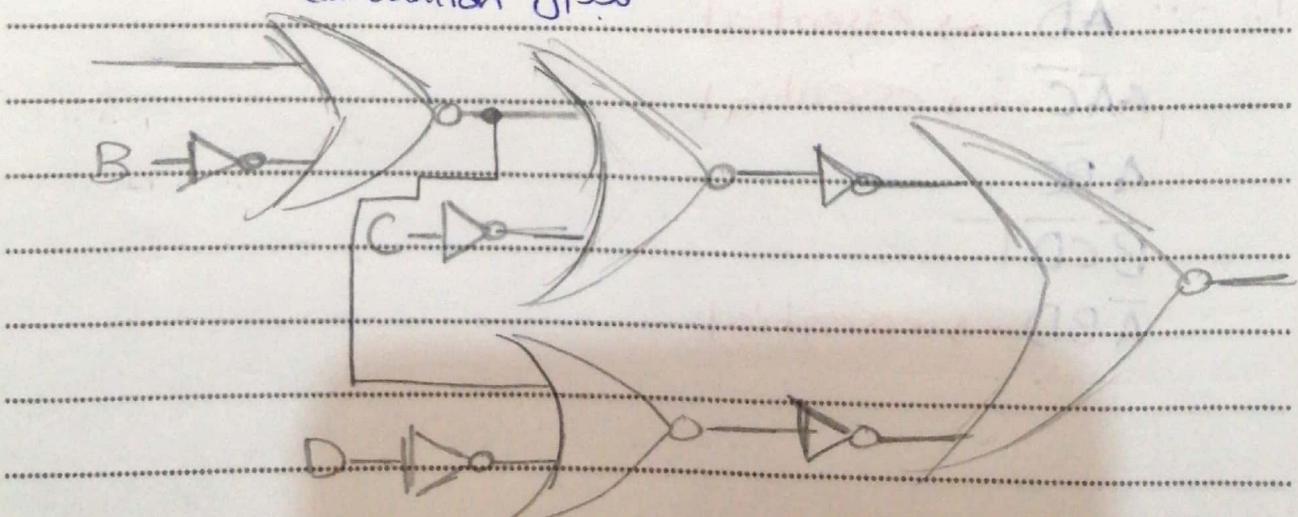

S T A R S N O T E B O O K


SUBJECT:

/ /

Problem 6

the truth table for $F(A, B, C)$, draw
the implementation of the function using
tri-state buffers and invertors only.

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

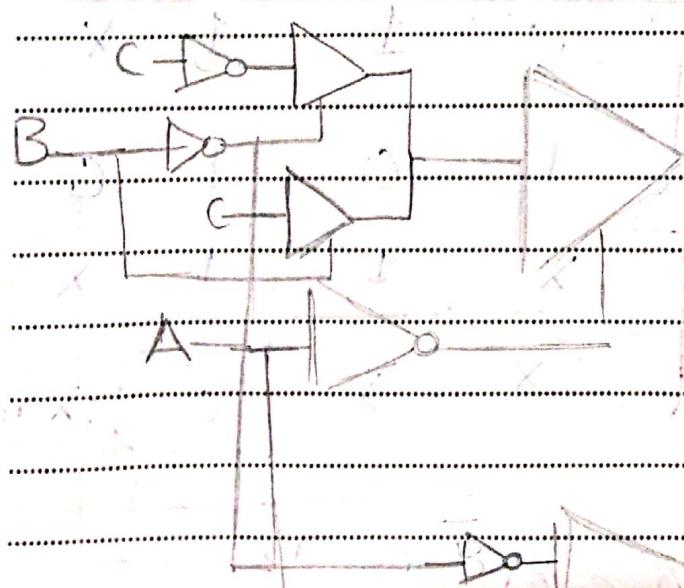

buffers


invertors

3

S T A R S H O T E B O O K

I

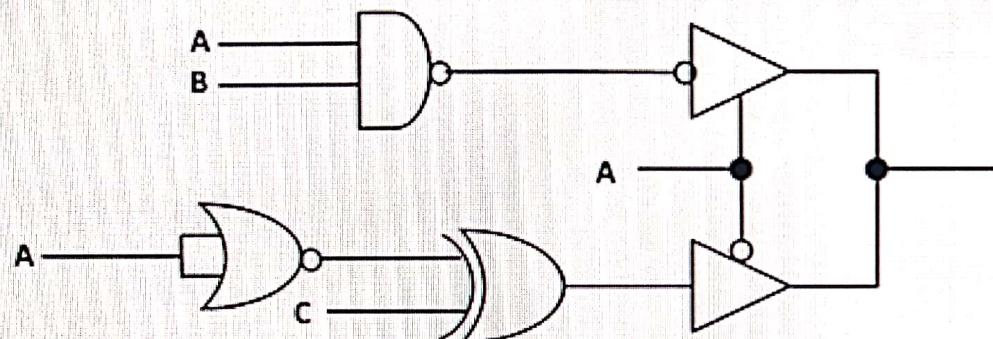Problem 7. Given the logic diagram of function F Fill in the table on the right for the given combinations
(2 Points)



A	B	C	F
1	0	0	
1	1	1	
0	1	0	
0	1	1	

Problem 8: Given the Kmap for function F write the Boolean expression of F as a POS. **(2 Points)**

C

Problem 8: Given the Kmap for function F write the Boolean expression of F as a POS. **(2 Points)**

I				
	A	C		
			B	
				D

0	1	1	X
1	0	1	0
X	1	1	X
X	X	0	X

$$F(A, B, C, D) =$$

SUBJECT:

/ /

Problem 7

Given the logic diagram of function F

Fill in the table the given combinations:

A	B	C	F
1	0	0	0
1	1	1	0
0	1	0	1
0	1	1	0

Problem 8

Given k-map for function F, write

boolean expression of F as a POS

$$\bar{F} = C\bar{D} + A\bar{B} + \bar{B}\bar{D} +$$

$\bar{A}B\bar{C}D$

dual $F =$

$$(C+\bar{D}) \cdot (A+\bar{B}) \cdot (\bar{B}+\bar{D})$$

$$+ \cdot (\bar{A} + B + \bar{C} + D)$$

$$F \text{ as POS} = (\bar{C}+D) \cdot (\bar{A}+B)$$

$$\cdot (B+D) \cdot (A+\bar{B}+C+\bar{D})$$

S	T	A	R	S	N	O	T	E	B	O	O	K
---	---	---	---	---	---	---	---	---	---	---	---	---

SUBJECT: / / / / / / / / / /

Problem 9

Box 1

Y

Box 2

0 or 10

Box 3

Y

Box 4

1 or x or y

Problem 10 write the truth table for a combinational logic circuit that takes as an input a 2 bit binary number A and produces as an output the multiplication of A by 2.

$A \times 2$	$A_1 A_0$	$0_2 0_1 0_0$			
0 \leftarrow 0 0	0 0	0 0 0	A_0 —		$2A$
2 \leftarrow 0 1	0 1	0 1 0	A_1 —		
4 \leftarrow 1 0	1 0	1 0 0			
6 \leftarrow 1 1	1 1	1 1 0			

2 bits \leftarrow cat JF POSITIVE

output JF bits JF negative out JF and put

S T A R S H O T E B O O I K