

\* The source free **RC** Circuits

$\tau$

$$\tau = RC$$

$$V(t) = V(0)e^{-t/\tau}$$

$$i(t) = i(0)e^{-t/\tau}$$

\* it takes  $5\tau$  for the circuit to reach its final state or steady state.

- life time of the circuit =  $5\tau$

\* if the value of  $\tau$  is  $\uparrow$  then  $\rightarrow$  more lifetime

\*  $\tau \uparrow \rightarrow$  more energy stored in capacitor.

\*  $\tau \uparrow \rightarrow$  less power absorbed or generated by R.

$$* V_c = V(t) = V(0)$$

\* 3 steps solution

$\Rightarrow$  step 1 at  $t = \infty$  " determine the type of the circuit and find  $\tau$  and write the solution form.

Step 2  $\rightarrow$  at  $t=0^-$  "switching ~~أعلى~~ ~~التي~~ ~~التي~~"

$\hookrightarrow$  draw the circuit at  $t=0^-$

$\hookrightarrow$  find  $i(0^-)$ ,  $V(0^-)$ ,  $V_C(0^-)$

step 3  $\rightarrow$  at  $t=0^+ = 0$  "switching ~~أعلى~~ ~~التي~~ ~~التي~~"

$\hookrightarrow$  Draw the circuit at  $t=0^+$

$\hookrightarrow$  Replace each capacitor by a voltage source.

$\hookrightarrow$  find  $i(0^+)$ ,  $V(0^+) = i(0)$ ,  $V(0)$

to use them in the solution

$$* V_C(0^-) = V_C(0^+) = V_C(0)$$

\* source free RL circuits.

$$T = \frac{L_{eq}}{R_{eq}}$$

$$i(t) = I(0^+) e^{-t/T}$$

$$V(t) = V(0^+) e^{-\frac{t}{\tau}}$$

$\rightarrow$  step 1:- at  $t=\infty \rightarrow$  find the type of the circuit then find  $T$ , and write the solution form.

$\rightarrow$  step 2:- at  $t=0^-$ :- Draw the circuit

$\hookrightarrow$  find  $i(0^-)$ ,  $V(0^-)$ ,  $i_C(0^-)$

→ step 3 → at  $t = 0^+$  :- Draw the circuit  
& replace each inductor by  
a current source  $i_L(0^-)$

$$* i_L(0^-) = i_L(0^+) = i_L(0)$$

find  $i(0^+)$ ,  $V(0^+)$  to use them in the  
solution.

$$* i_L(t) = i(t) = i(0) e^{-t/\tau}$$

Remember:- in DC circuits we replace inductor  
with short circuit, and capacitors with open circuits.

$$\frac{1}{s} \equiv \int \quad \int \equiv \frac{1}{s}$$

\* Driven RC and RL Circuits

$$V(t) = V(\infty) + (V(0) - V(\infty)) e^{-t/\tau} \text{ for } t > 0$$

$$V(t) = V(0) \text{ for } t < 0$$

$$i(t) = i(\infty) + (i(0) - i(\infty)) e^{-t/\tau}, t > 0$$

$$i(t) = i(0), t < 0$$

⇒ Step 1: determine the type at  $t = \infty$  and find  $\tau$  and find  $i(\infty)$  or  $V(\infty)$  or both. then write the solution form.

⇒ Step 2: at  $t = 0^-$  find  $i_L(0^-)$ ,  $i(s)$ ,  $V_C(0^-)$

⇒ Step 3: at  $t = 0^+$

$$\frac{1}{\tau} \equiv \downarrow V_C(0^+) = V_C(0^-)$$

$$\downarrow i_L(0^+) = i_L(0^-)$$

\* Source free RLC Circuit

\* series

$$\alpha = \frac{R}{2L}$$

parallel

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Characteristic roots

$$\begin{cases} s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{cases}$$

Solution :-

\* if  $\alpha > \omega_0 \Rightarrow$  over damped response

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

\* if  $\alpha = \omega_0 \Rightarrow$  Critically damped response

$$i(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$$

\* if  $\alpha < \omega_0 \Rightarrow$  underdamped response

$$i(t) = e^{-\alpha t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)]$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

\* Same solutions for  $V(t)$ .

## \* Driven RLC Circuits

$$i(t) = i(\infty) + \text{solution in source-free.}$$

$$V(t) = V(\infty) + \text{solution in source-free}$$

Note:-  $s_1 = s_2 \rightarrow$  Critical damped  
 $s_1, s_2$  (real numbers)  $\rightarrow$  overdamped.  
 $s_1, s_2$  (complex numbers)  $\rightarrow$  underdamped