

• Current

• Types :-

1. DC current (Direct constant) current :-

e.g. $I = 3A \rightarrow$ Amber, $I = -5A$, $I = 3.11A$, $I = 2.5A$.

↳ Doesn't change with time

"const. with time"

"Doesn't have to be integer"

Value, ~~it can~~

"negative current means that this current is moving in the opposite of real direction".

5A ← *in this direction*

$$I_x = \overrightarrow{-5A}$$


in this direction

2. AC current (Alternating current)

Simusaidly changes with time


e.g. $i(t) = 3\sin(\omega t)$, $i(t) = 4\cos(\omega t)$

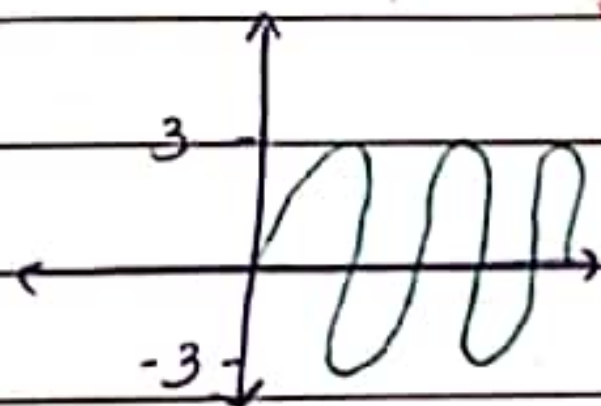"we write it as a funct. of sin and cos."




3. other types :-

e.g. exponential current

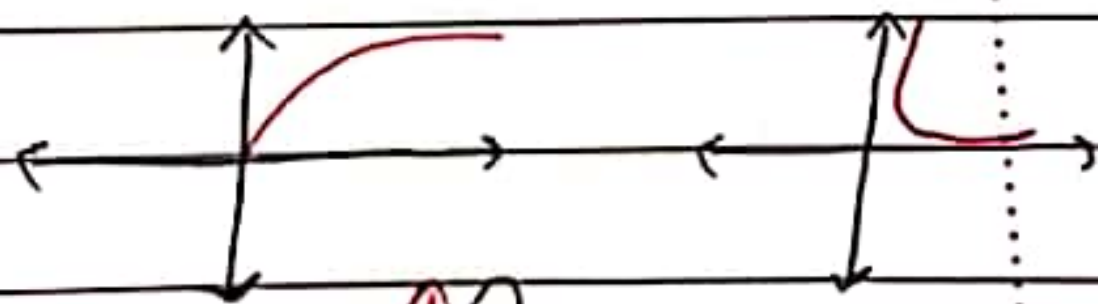


- damped sinusoidal current

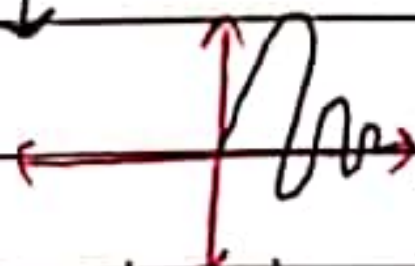

* Voltage

→ DC Voltage $V = 3V$, $V = -10.4V$!

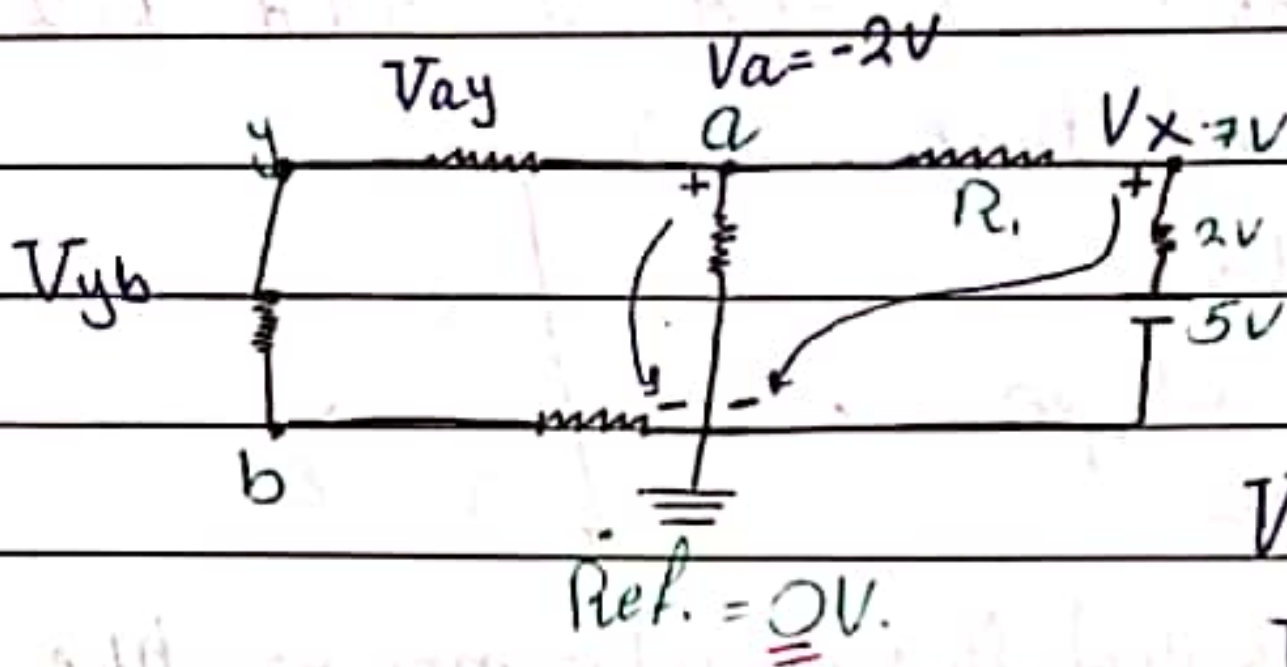

$V_{in Ref} > V_a$ by 2
 $V_a > V_{in Ref}$ by -2

V_{ab} - (a) positive, (b) negative

$$V_{ax} = V_a - V_x$$

$$V_a > V_x \text{ By } -9$$

→ AC voltage


$$V(t) = -9.1 \cos(\omega t), \quad V(t) = 4.2 \sin(\omega t) \text{ volt.}$$

* Power

$$P = I * V \text{ (W = watt)} \leftarrow \text{DC}$$




$$P(t) = i(t) * v(t) \text{ W} \leftarrow \text{AC}$$

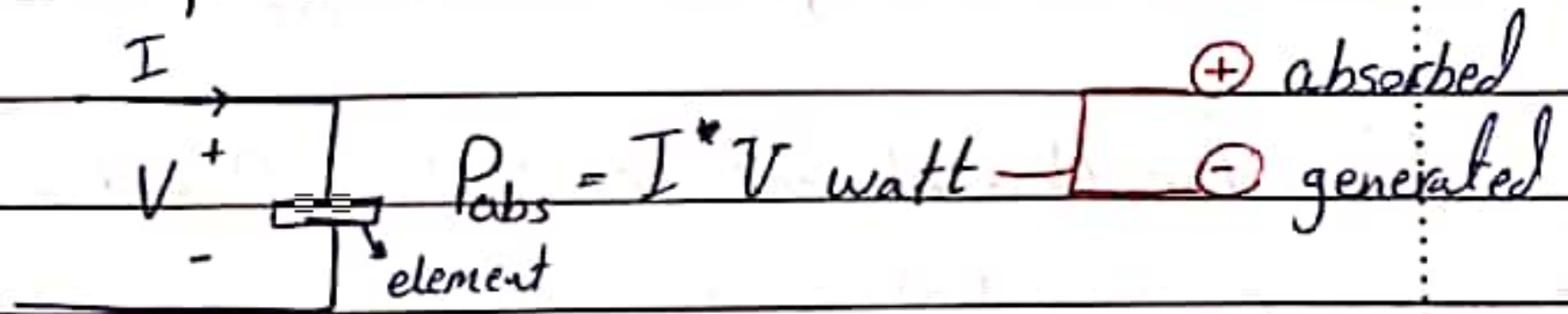Power could be absorbed (dissipated) or generated by the element and this depends on the element.



$$P_{\text{abs}} = -P_{\text{gen}}$$

Ex:- find the P_{abs} .

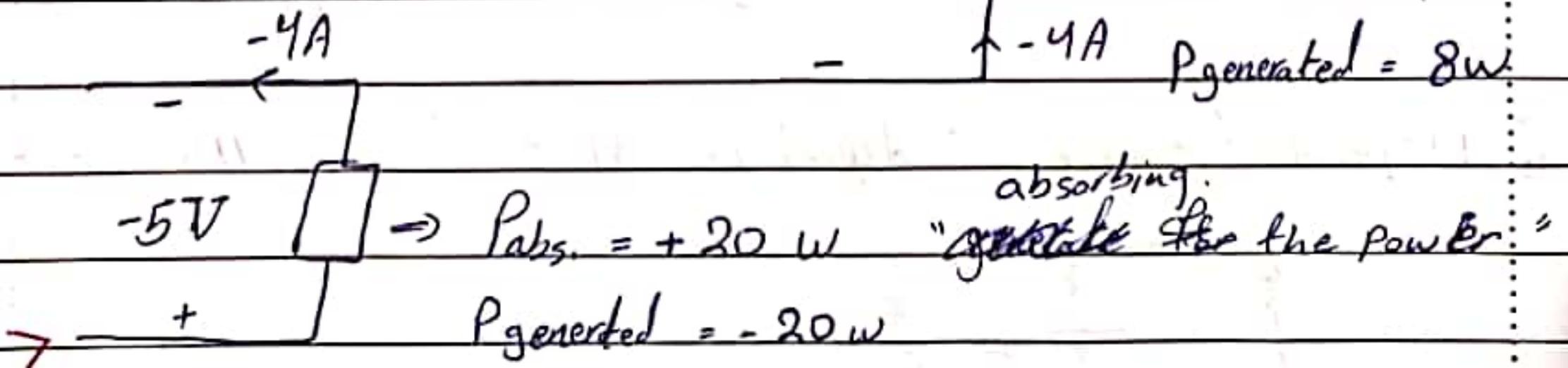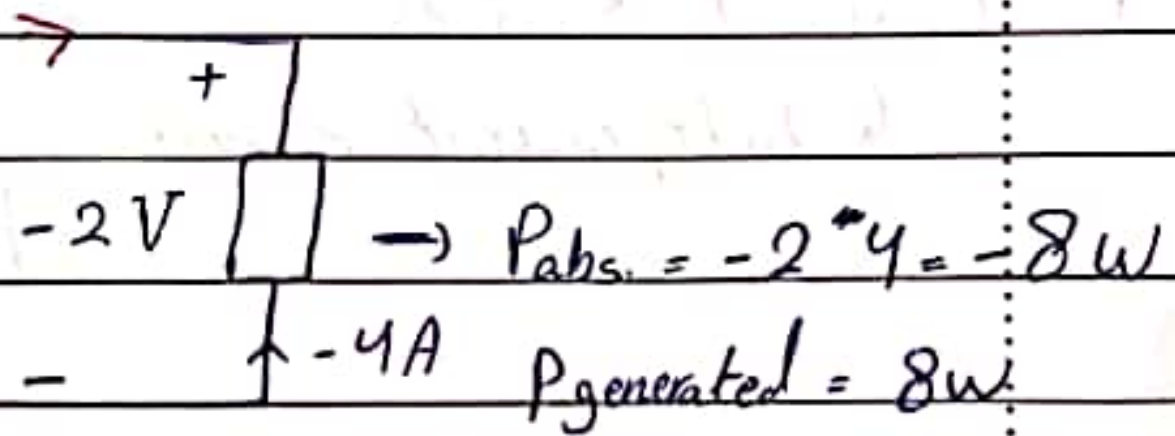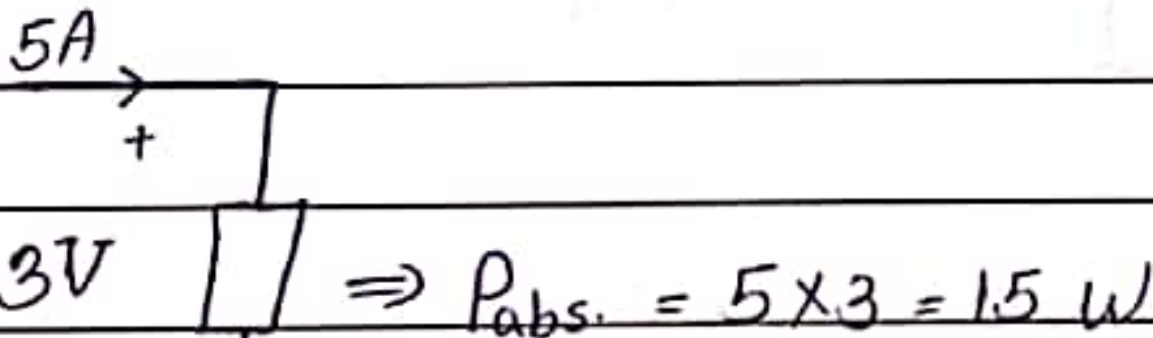


* Resistance always absorb the power.

→ Passive elements = it doesn't give power by itself. "conductor, Capacitor, Resistance".

→ Active elements = it gives.

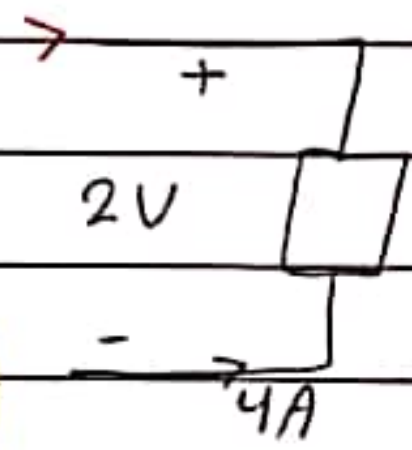Ex: for this element, could be a Resistor



$$P = 2 \times 4 = -8 \rightarrow P_g = 8 \text{ W}$$

it actually generates Power ... so it could never be a resistor.


* Sources

↳ Current sources

- ↳ Independent sources → AC
- | , DC

"doesn't depend on any value on the circuit"

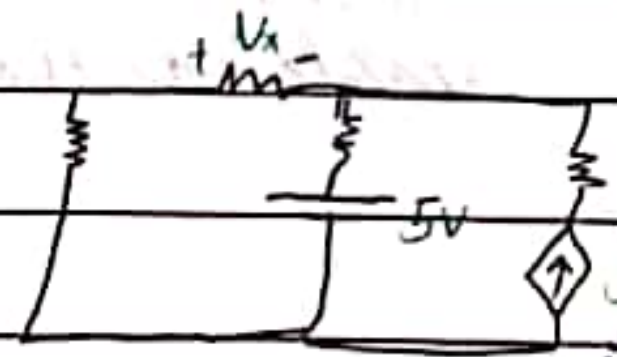↳ Dependent sources "depend on other values on the circuit"



→ final result in Amber

2. Voltage source

↳ Independent → AC

$V_s(t) = 7 \sin(\omega t) V$

↳ DC


$V_s = 5V$

$V_s = 3V$

↳ Dependent

$3V_x$

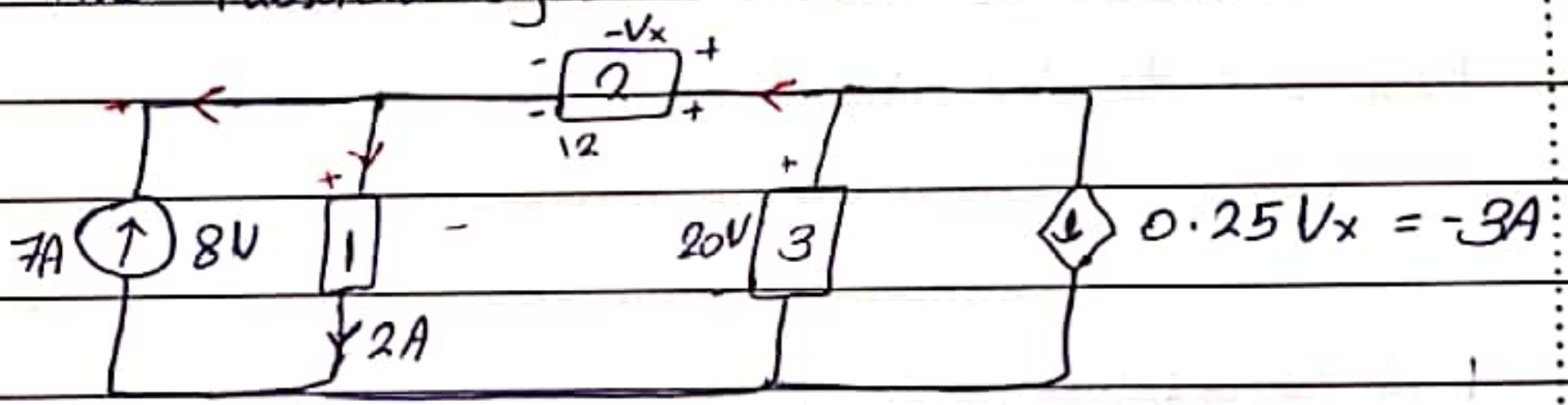Ex: Find $P_{absorbed}$ by each element in this circuit



$7A \rightarrow P_{abs.} = -7 \times 8 = -56 W$

$2 \rightarrow P_{abs.} = 12 \times -5 = -60 W$

$1 \rightarrow P_{abs.} = 2 \times 8 = 16 W$


$3 \rightarrow P_{ab} = 20 \times 8 = 160 W$

$\Sigma P_{abs} = Zero$

$\Sigma P_g = \Sigma P_{abs.}$

• Network :- two or more elements connected together. (2)

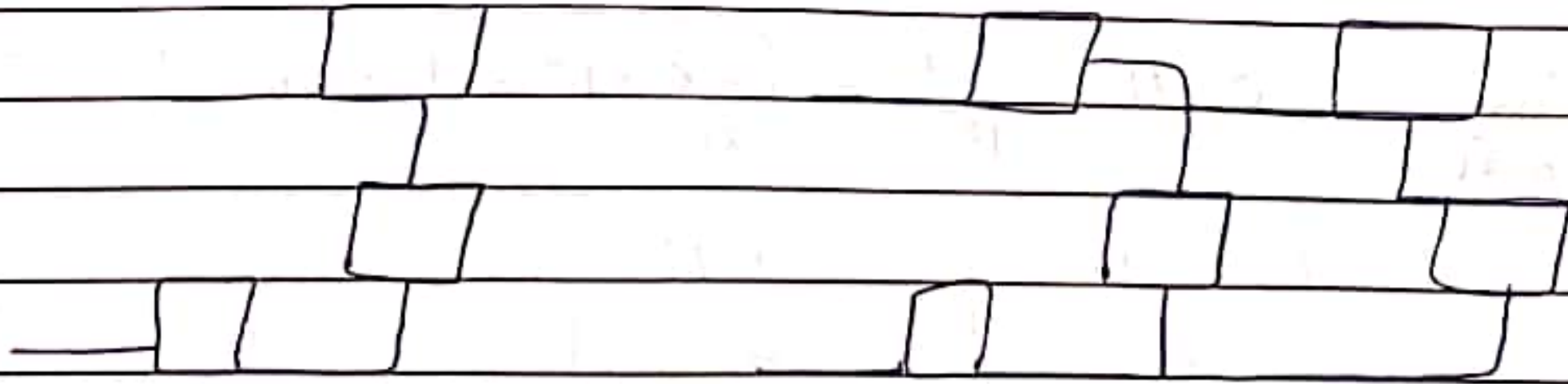• Circuit :- a network contains at least one closed path.



Network


Circuit

* every circuit is a network but not every network is a circuit.

* Ohm's law :-

$$V = RI$$

Voltage Resistor current.

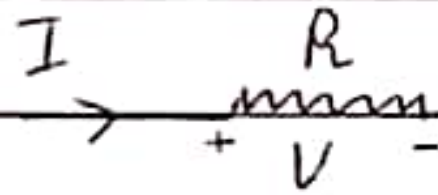


(+) where the current enter.


$$G = \frac{1}{R}$$

Conductance R mho or S siemens

Ex :- find R

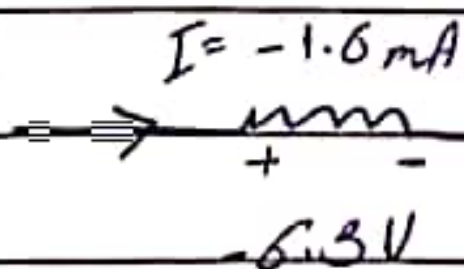
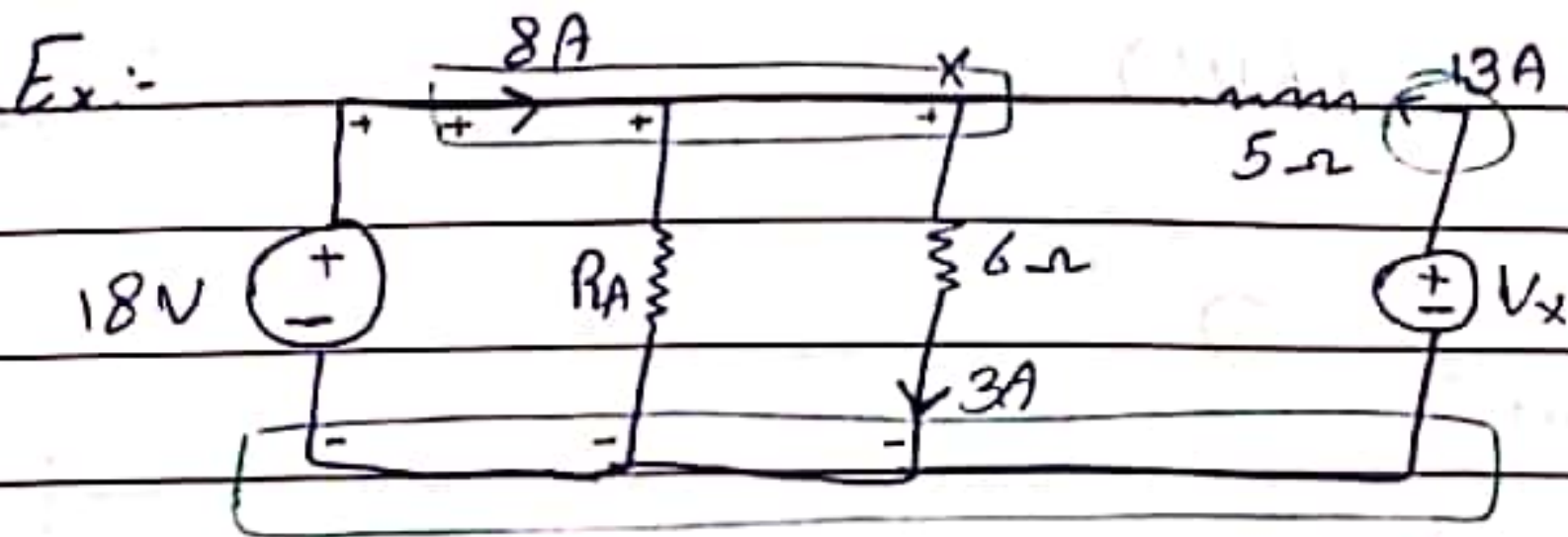
$$R = \frac{V}{I} = 3.94 \text{ k}\Omega$$



- Find the no. of branches $\rightarrow 5$ branches = elements.
- Find the no. of nodes $\rightarrow 3$
- Find the no. of elements $\rightarrow 5$
- Find R_A .

$$V_{RA} = 18V, \text{ KCL at node X}$$

$$8 + 13 - 3 - I_A$$

$$I = 18A$$

$$R_A = \frac{V_{RA}}{I_{RA}} = \frac{18}{18} = 1 \Omega$$


$$e) P_{\text{generated}} (18V) = 8 \times 18 = +144W$$

$$\hookrightarrow P_{\text{abs}} = 18 \times -8 = -144W$$

$$f) P_{\text{absorbed}} (6\Omega) = I^2 \times R = 9 \times 6 = 54W$$

Kirchhoff's voltage law (KVL)


$$\sum_{\text{enclosed path}} V = 0$$

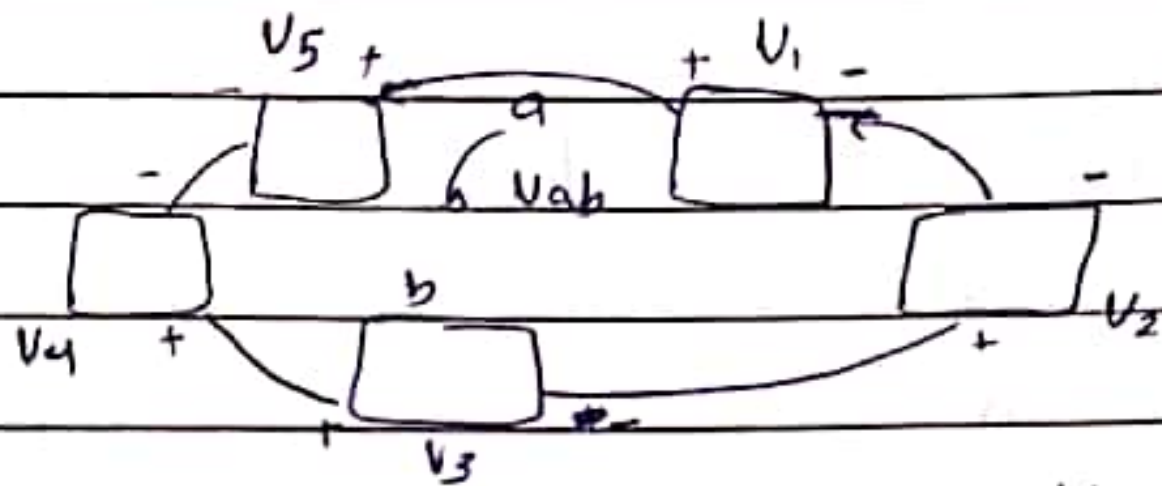

$$V_1 - V_2 - V_3 + V_4 - V_5 = 0$$

$$V_1 - V_2 - V_3 - V_{ab} = 0$$

$$V_5 - V_4 - V_{ab} = 0$$

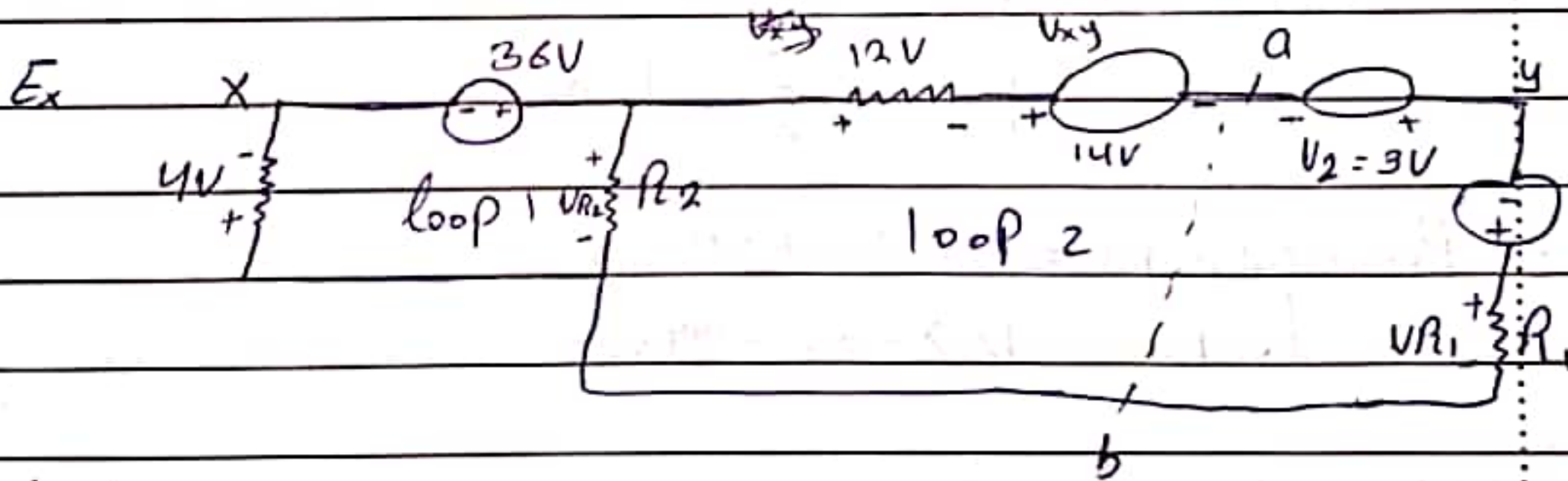

Find V_{R_2} , V_{ab} , V_{xy}

$$\text{KVL at loop 1} :- 4 - 36 + V_{R_2} = 0$$


$$V_{R_2} = 32V$$

$$\text{KVL at loop 2} :- 4 - 36 + 12 + 14 + V_{ab} = 0 \rightarrow V_{ab} = 6V$$

$$\text{KVL at loop 3} :- V_{xy} + 3 - 14 - 12 + 36 = 0$$

$$V_{xy} = -13V$$


1. Find I_y

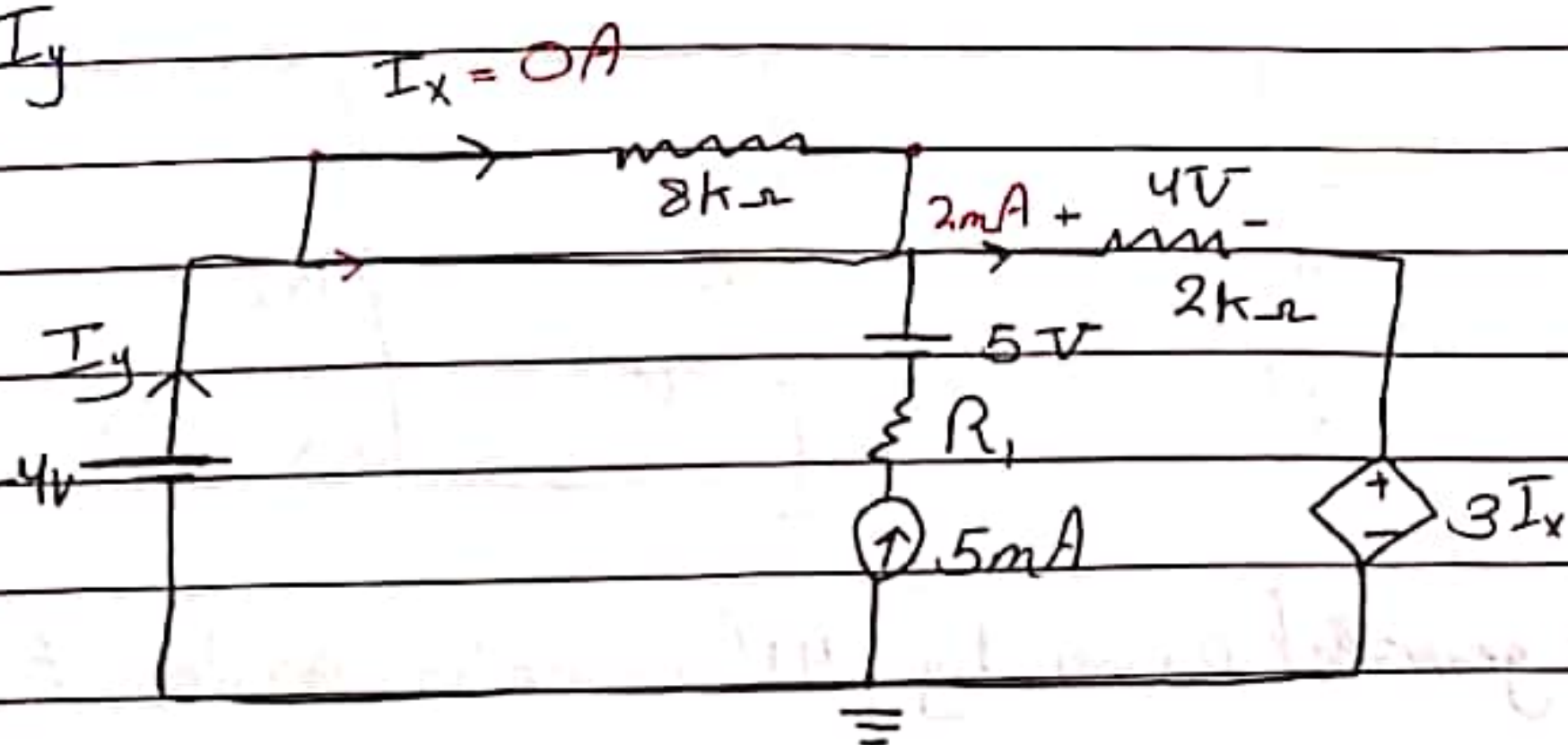

$$5 + I_y + 0 = 2$$

$$I_y = -3mA$$

2. Find V_x

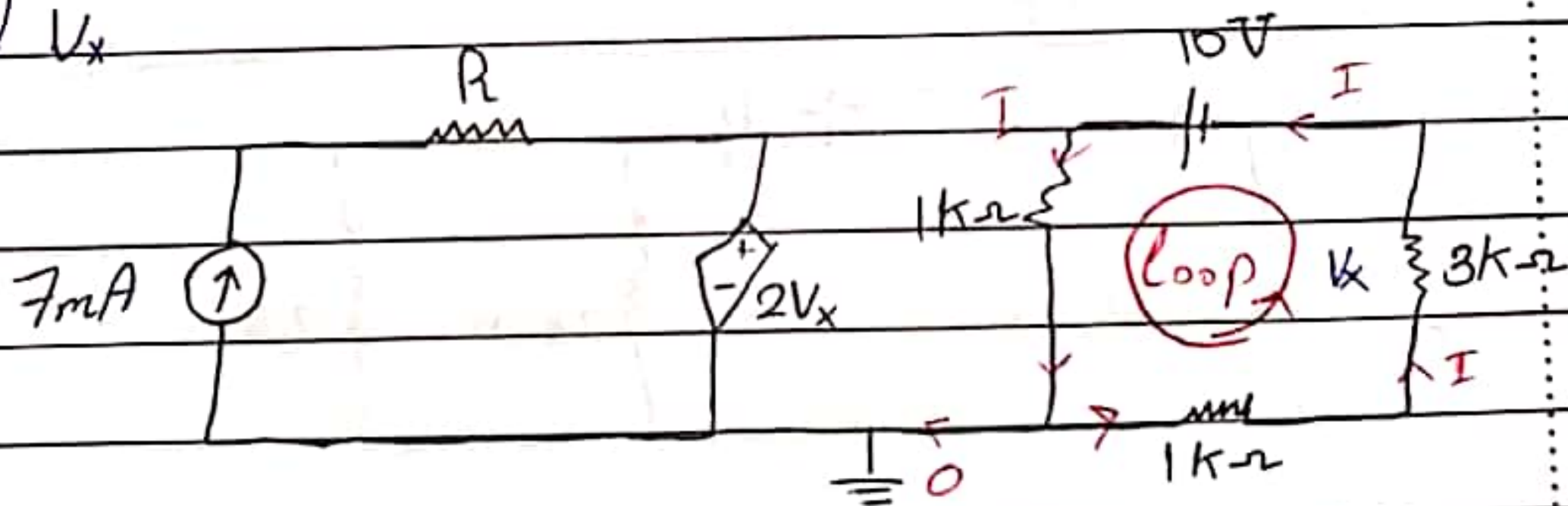


$$-10 + 1(I) + 3(I) + 1(I) = 0$$

$$I = 2mA$$

$$V_x = 6V$$

3.

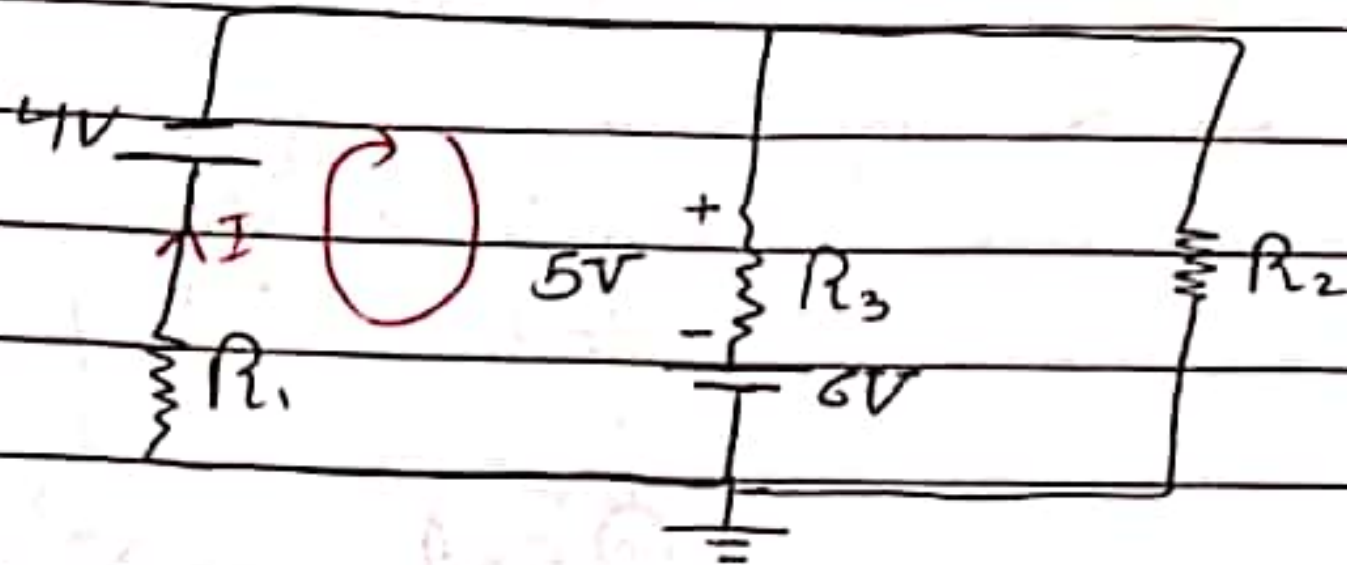

If the generated power by 4V source is 20mW find R_1

$$P_{abs} = I \cdot V$$


$$-20 = 4I$$

$$I = -5 \text{ mA}$$

$$IR_1 + 4 + 5 + 6 = 0$$

$$R_1 = 3 \text{ k}\Omega$$

4.

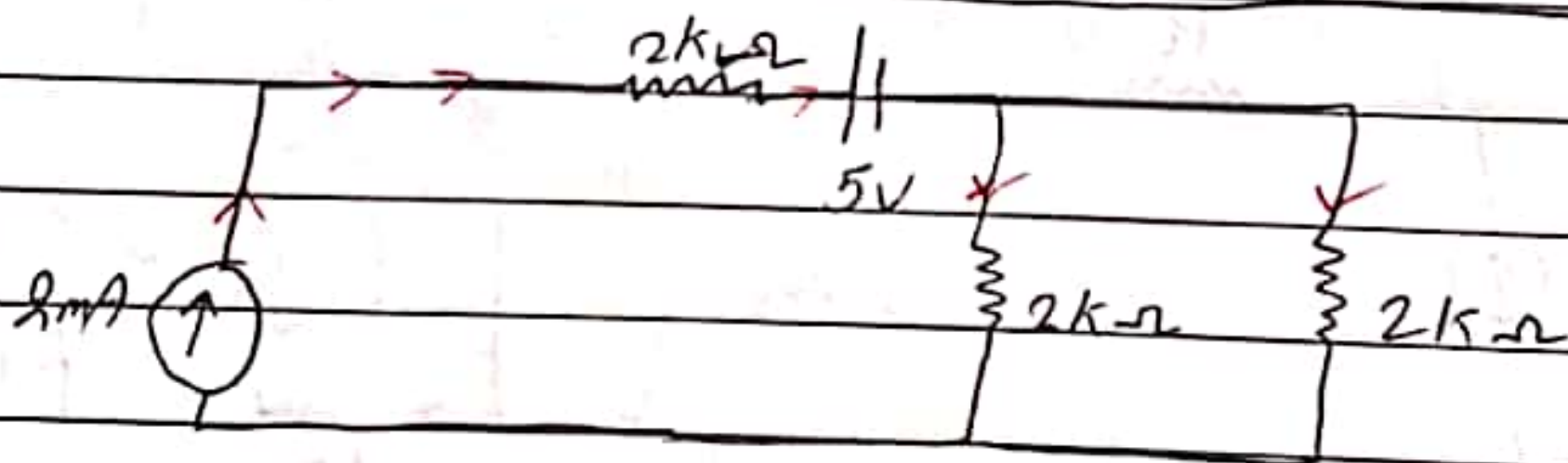


Find the generated power by 5V source

$$P_{abs} = I \cdot V$$

$$2 \times 5 = 10 \text{ mW}$$

$$P_g = -10 \text{ mW}$$

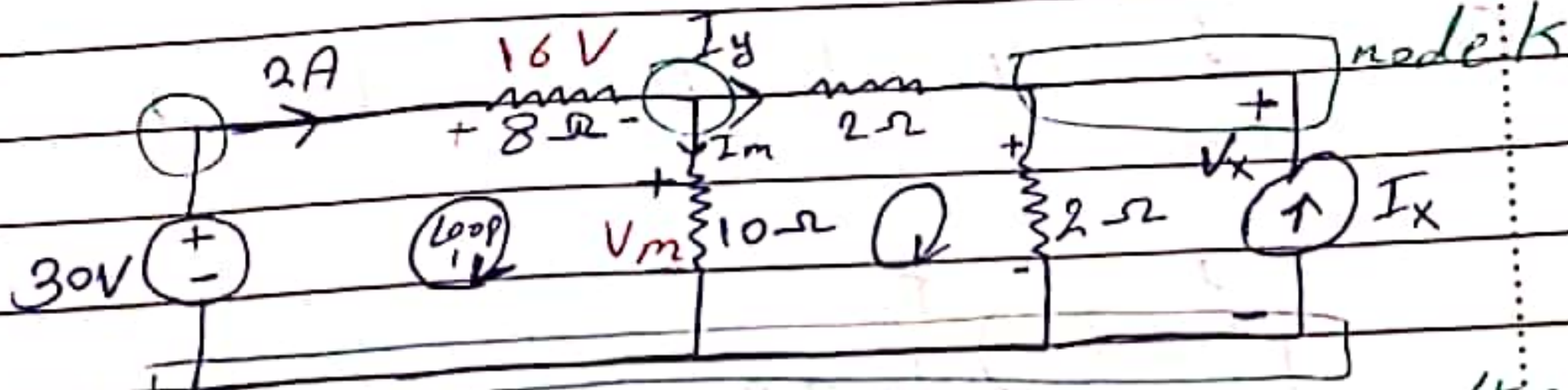

Find V_x and I_x

4 nodes

KCL at node k, $I_x + I_y - \frac{V_x}{2} = 0$

$I_x = 5.8 A$

KVL loop 1 :- $-30 + 2 \cdot 8 + V_m = 0$


$V_m = 14 V$

$I_m = \frac{14}{10} = 1.4 A$, $I_y = 2 - 1.4 = 0.6 A$

KVL loop 2, :- $-V_m + 2I_y + V_x = 0$

$V_x = 12.8 V$

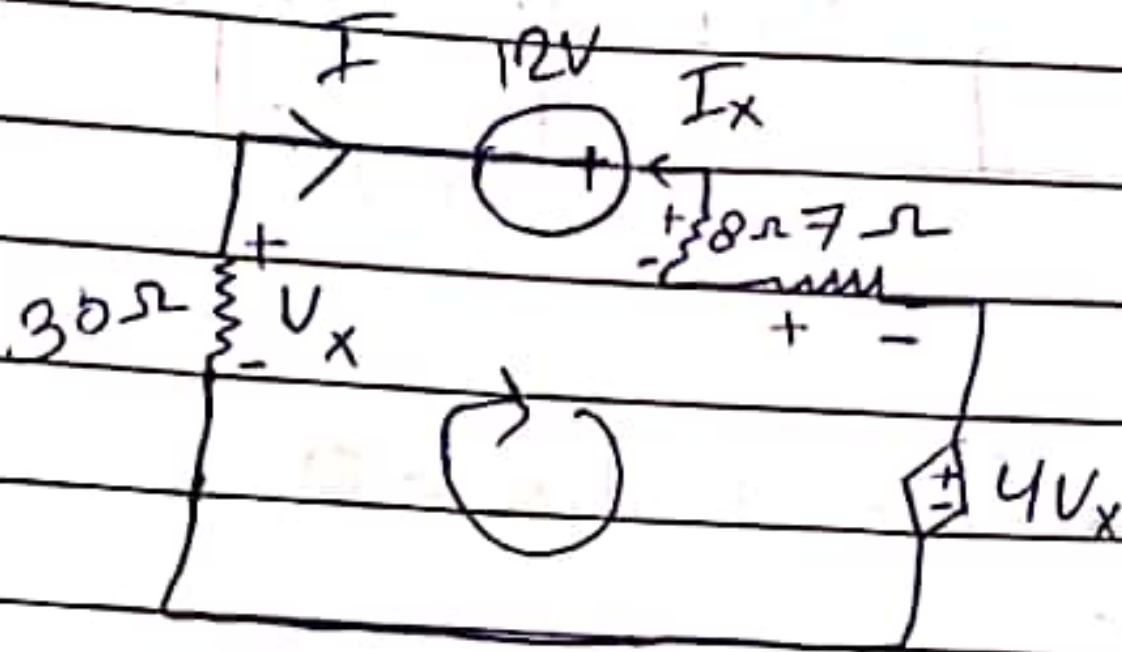Ex: Find the absorbed power by each element :-



KVL $\rightarrow -12 + 8I + 7I + 4V_x - V_x = 0$

$$-12 + 8I + 7I + 3(-30I) = 0$$

$$I = -160 \text{ mA}$$

$$\ast P_{\text{abs}}(30\Omega) = I^2 R = (-0.16)^2 \times 30 = 0.768 \text{ W}$$


$$\ast P_{\text{abs}}(12\text{V}) = I V = 0.16 \times 12 = 1.92 \text{ W}$$

$$\ast 8\Omega = P_{\text{abs}} = I^2 R = (0.16)^2 \times 8 = 0.2048 \text{ W}$$



$$\ast 7\Omega = P_{\text{abs}} = I^2 R = (0.16)^2 \times 7 = 0.1792 \text{ W}$$

$$\ast 4V_x \rightarrow P_{\text{abs}} = I V = (-0.16)(4 - 30I) = -3.072 \text{ W}$$

Ex

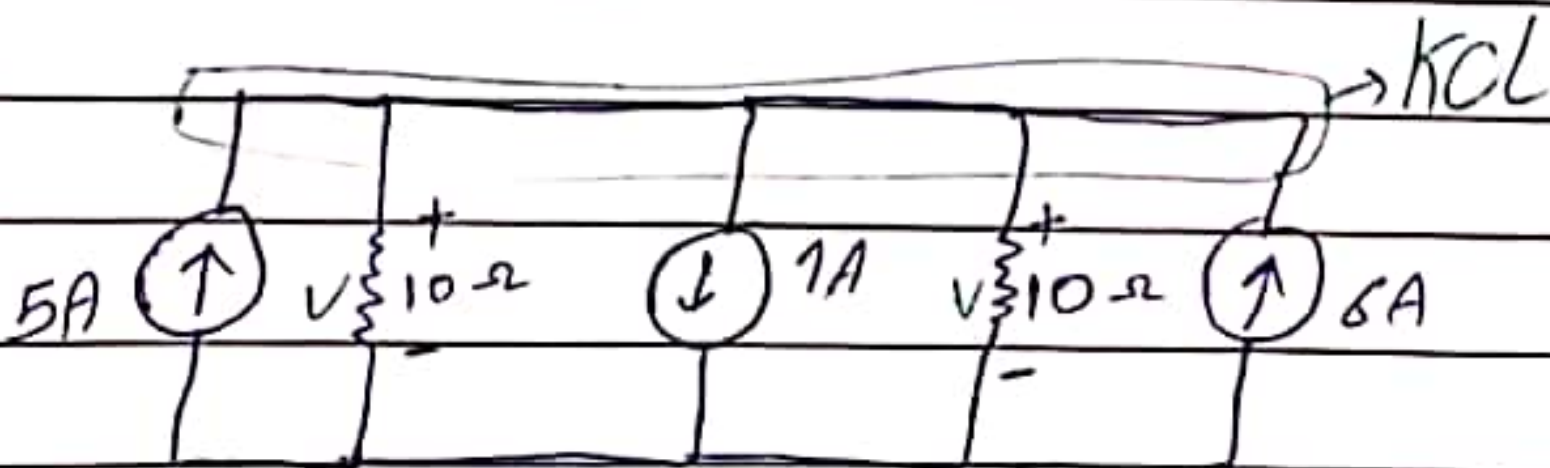
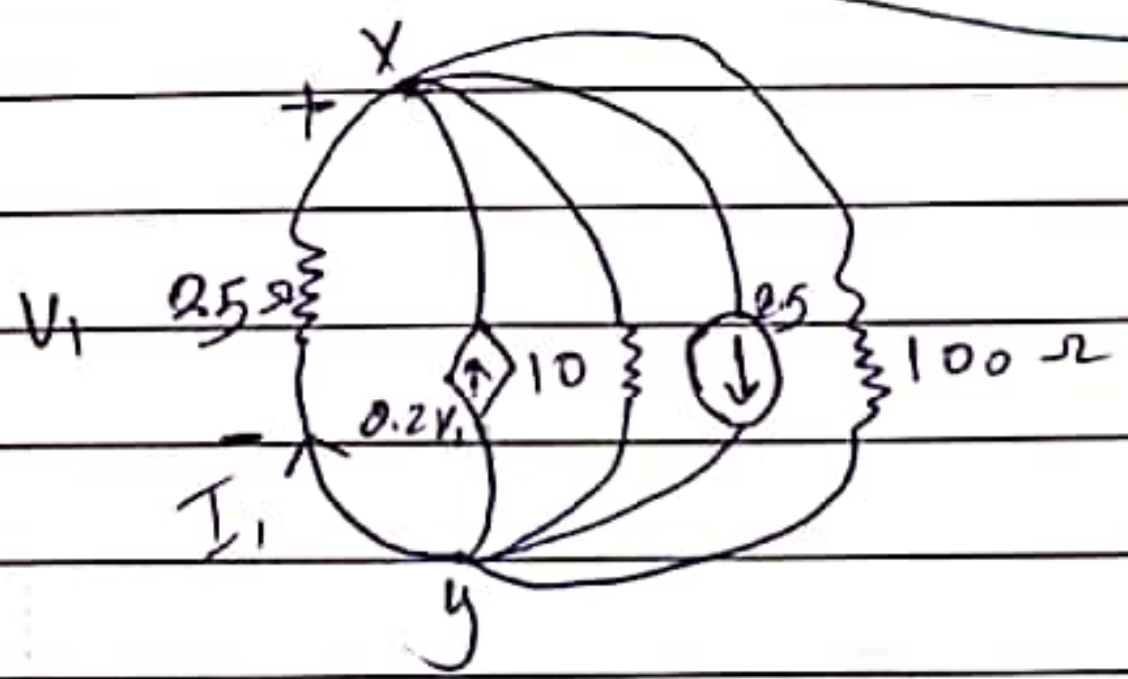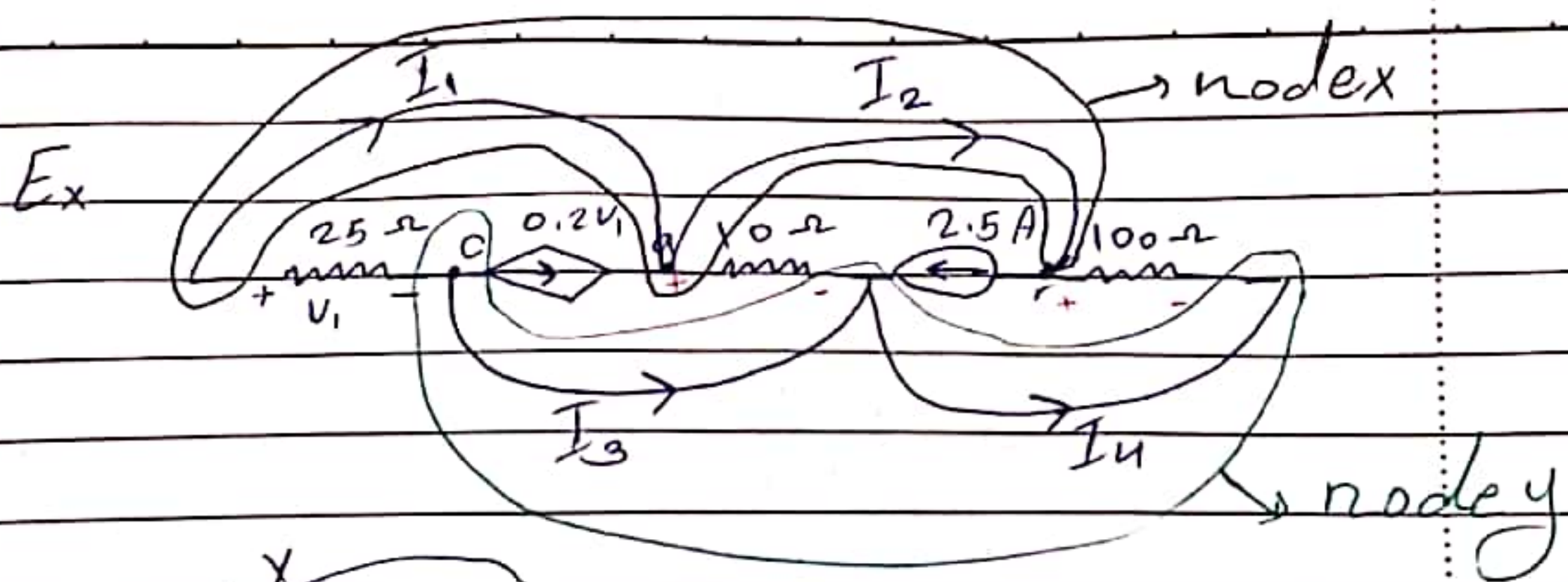
$$P_{5A} = -50 \text{ W} \quad / \quad P_{10\Omega} = 250 \text{ W} \quad / \quad P_{1A} = 50 \text{ W} \quad / \quad P_{6A} = -30 \text{ W}$$



KCL at node x = $\frac{V_1}{25} - 0.2V_1 + \frac{V_1}{10} + 2.5 + \frac{V_1}{100} = 0$

$V_1 = 50V$

$I_1 = \frac{-50}{25} = -2A$




KCL at node ^a → $I_1 + 0.2V_1 = \frac{V_1}{10} + I_2 \rightarrow I_2 = 3A$

KCL at c → $I_1 + 0.2V_1 + I_3 = 0 \rightarrow I_3 = -8A$


KCL at b → $I_2 + I_4 = 2.5 \rightarrow I_4 = -0.5A$

* Series and Parallel connections for sources.

* Voltage sources

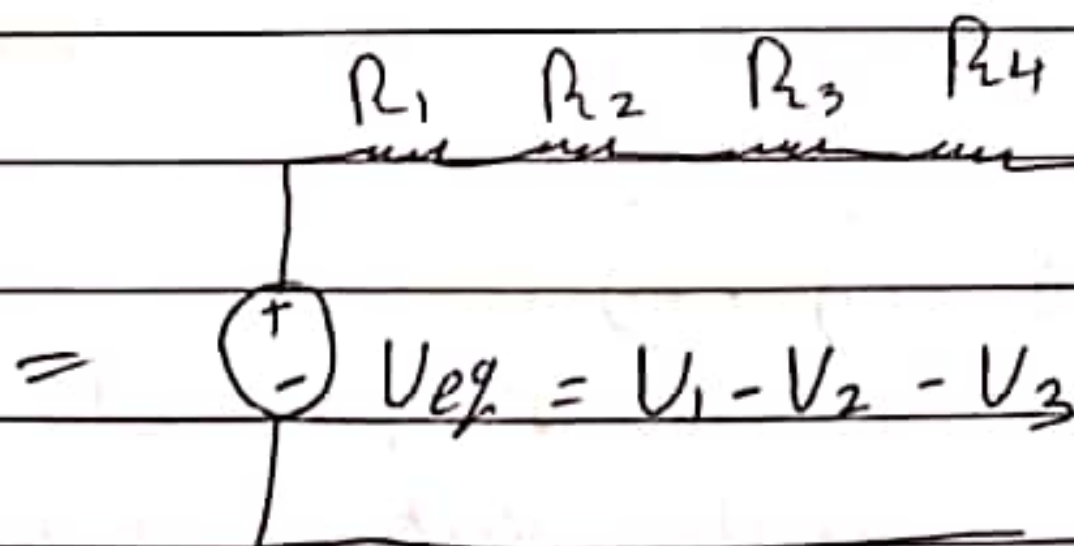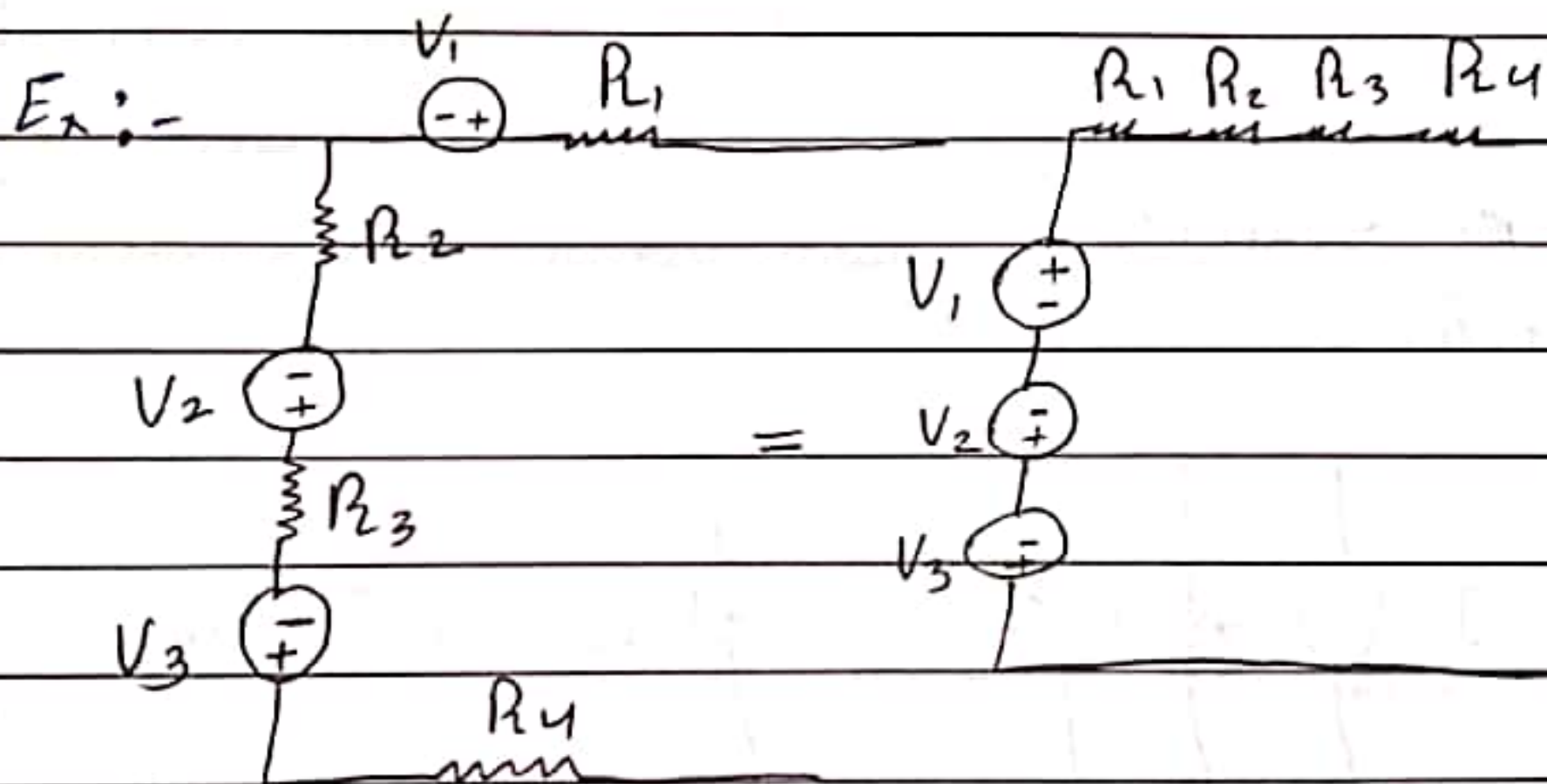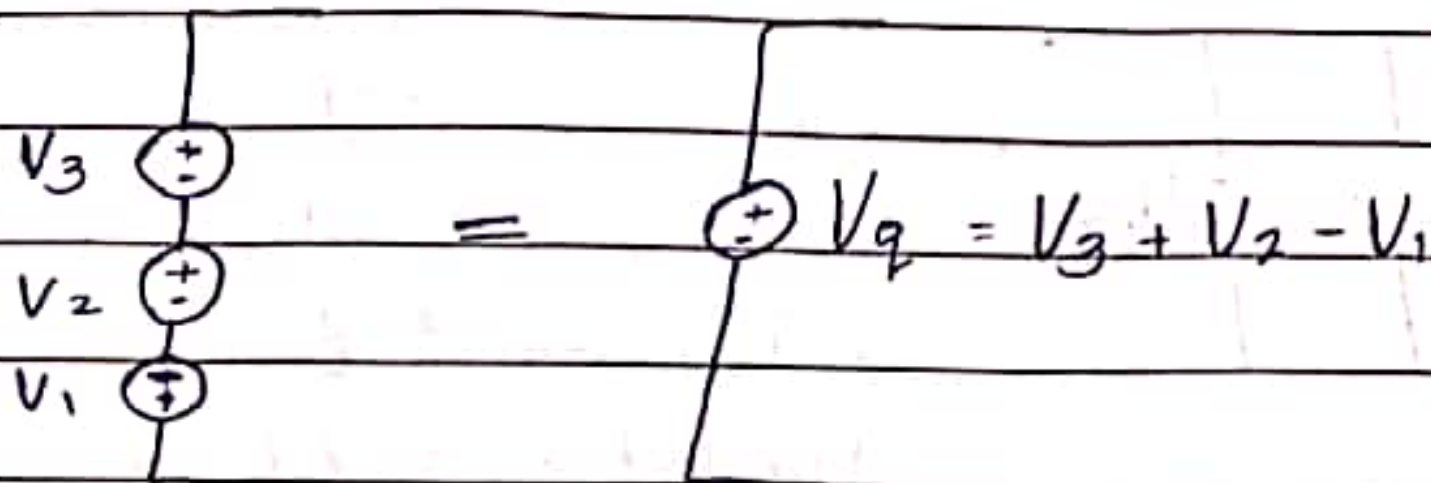

* Parallel

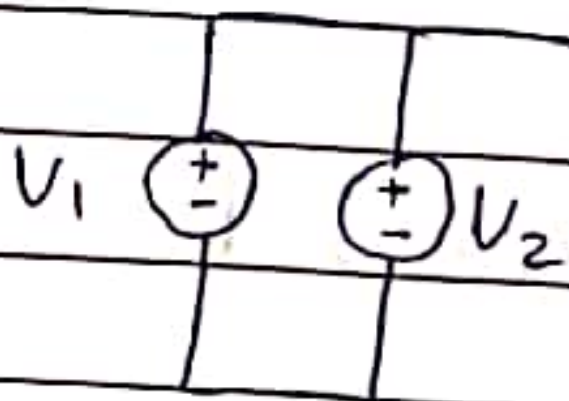

→ impossible!!


* it's correct only if $V_1 = V_2$.

* To connect two voltage sources
Parallel doesn't have advantage


"Not practical"

* Current sources

* Parallel

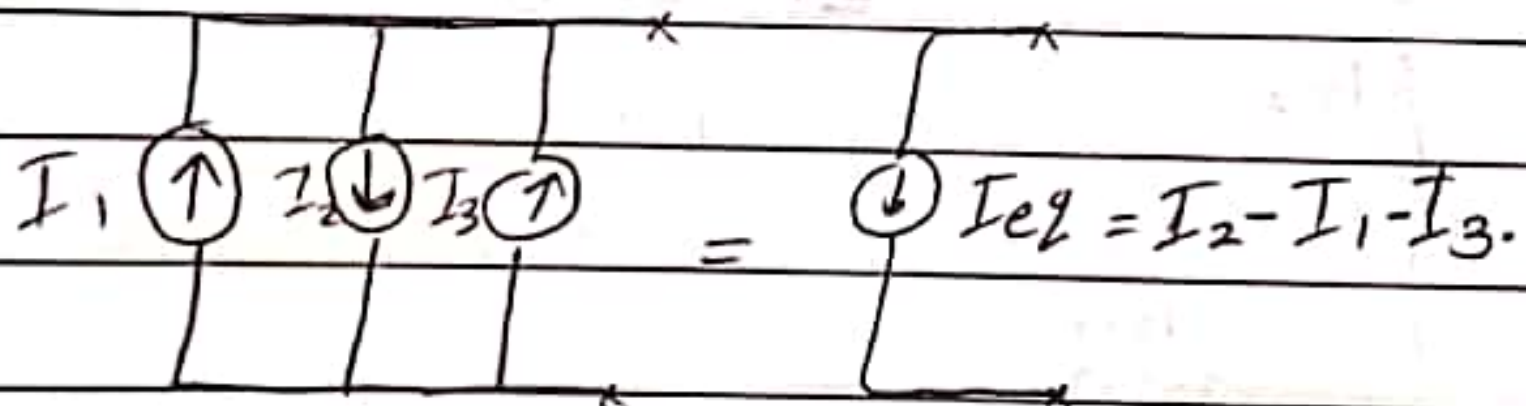

* series

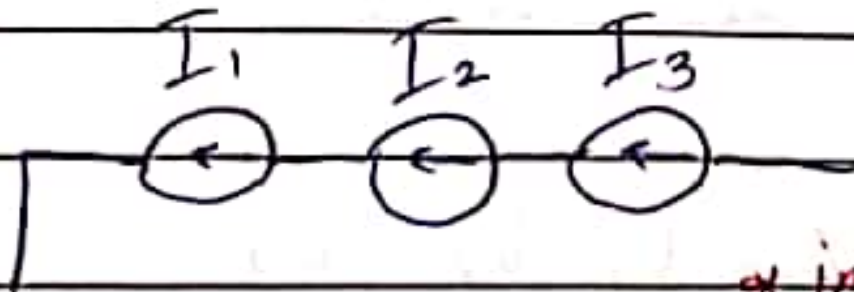

* impossible!!

* it's correct only if $I_1 = I_2 = I_3$:-!

* not practical connection.

* Series and parallel connections for resistors

* Series

$$R_1 \quad R_2 \quad R_3 = R_{eq} = R_1 + R_2 + R_3$$


* Parallel

same V


$$R_1 \quad R_2 \quad R_3 = R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$$

Note:- For 2 resistors in parallel

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

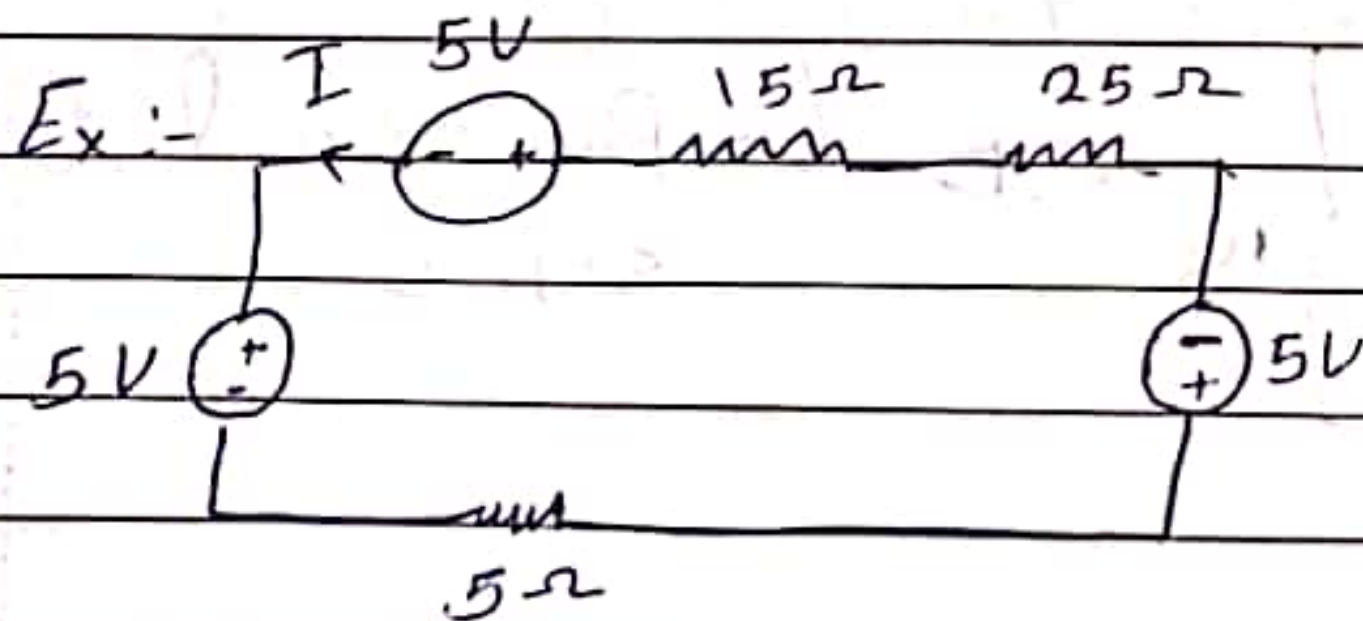


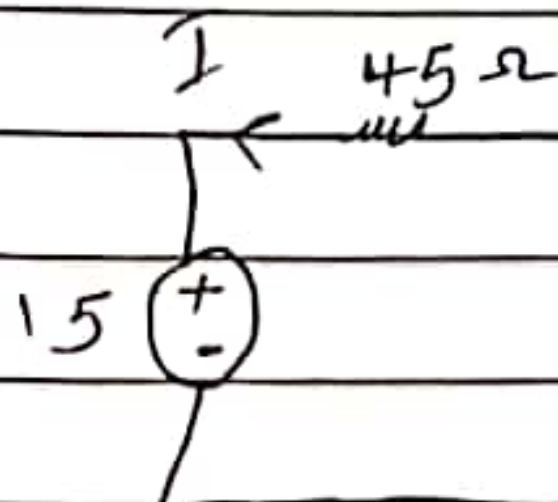simplify this circuit to one source and one resistor and find I




$$I = \frac{V}{R} = \frac{-15}{45} \text{ A}$$

Ex

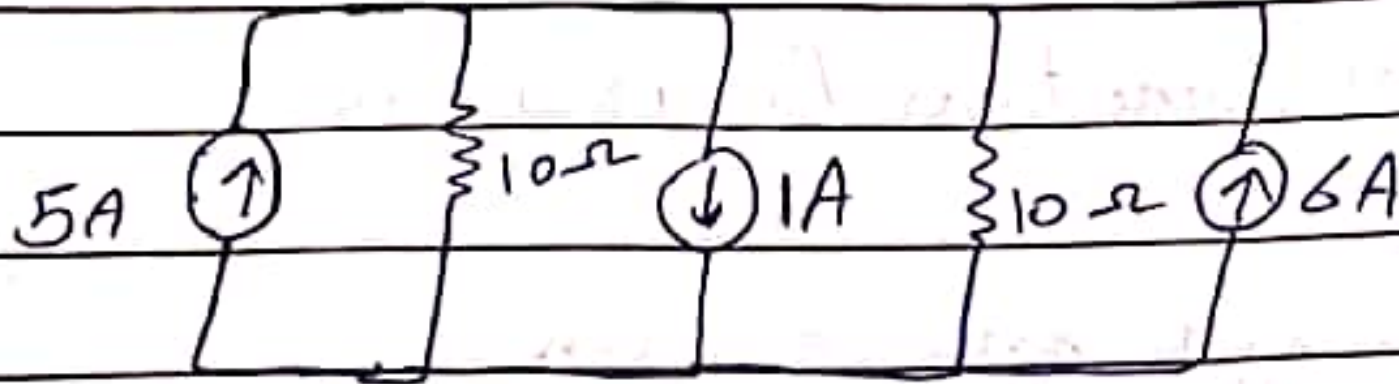


Sol: $I = 10A$ $R = 5\Omega$

Ex


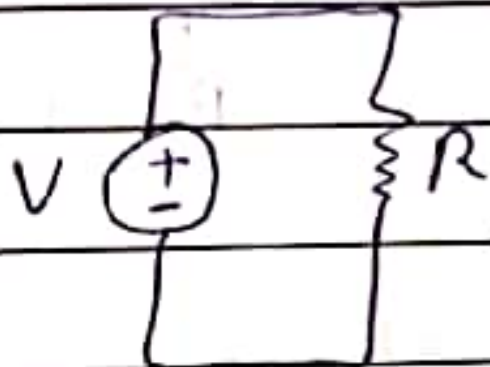


Parallel and series at the same time.

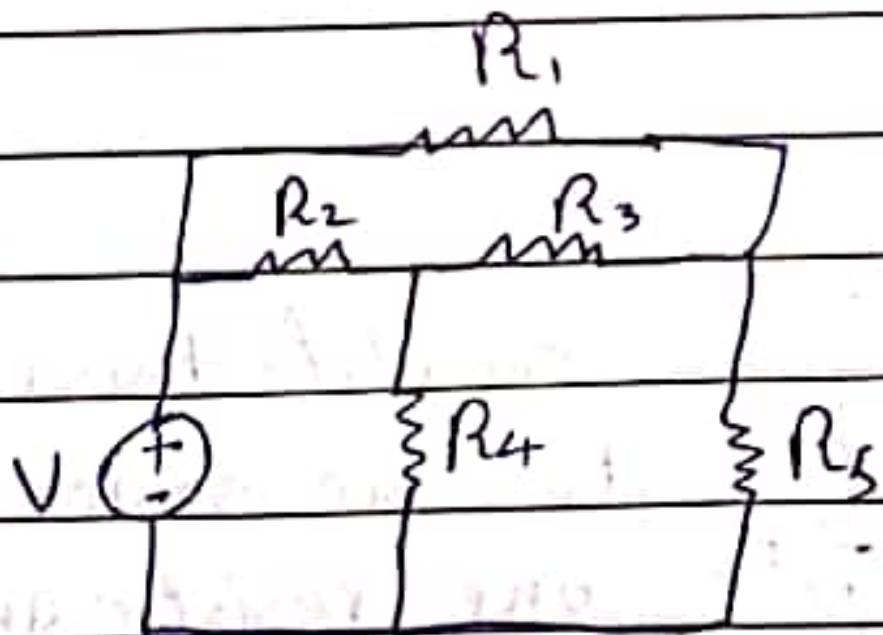


No Parallel and No series.

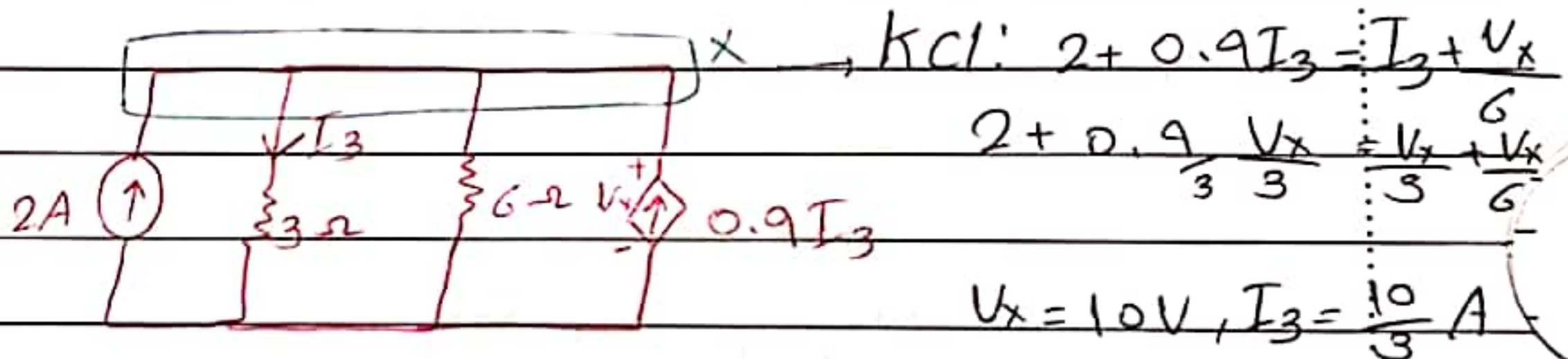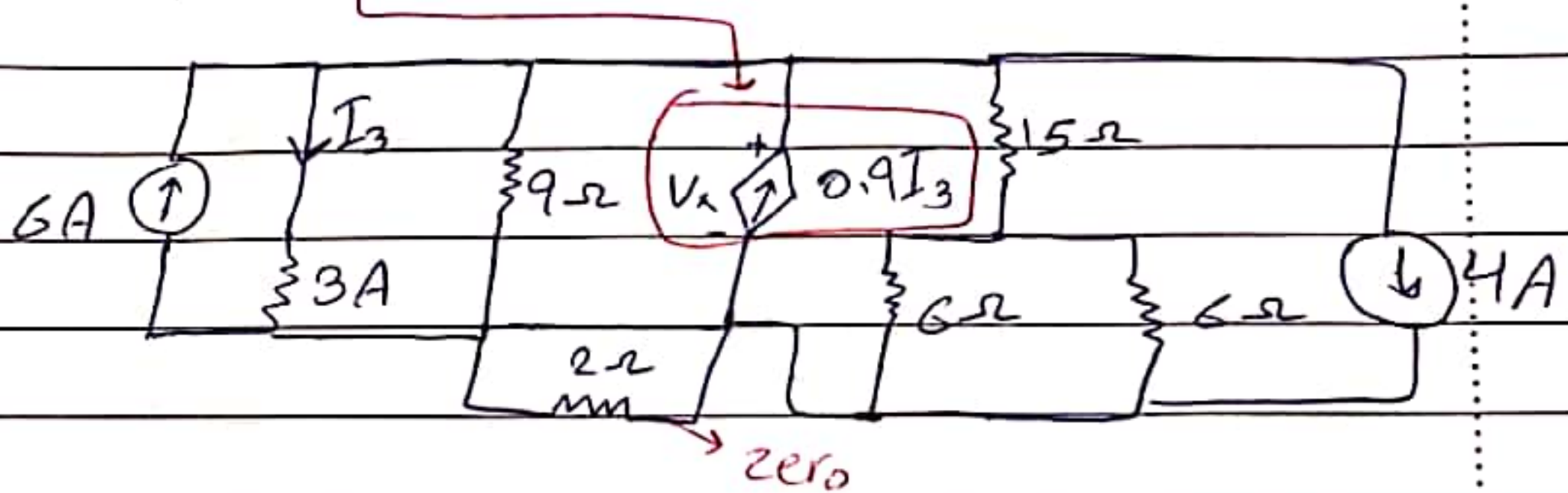Ex Find the power and voltage of the dependent source.




$$P_{abs} = 10 \times (-0.9I_3) = -30W.$$

Ex :- Find Req

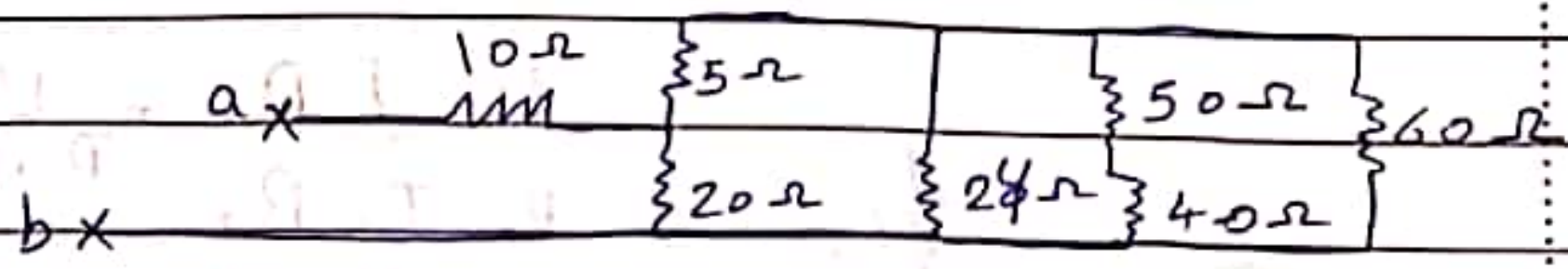

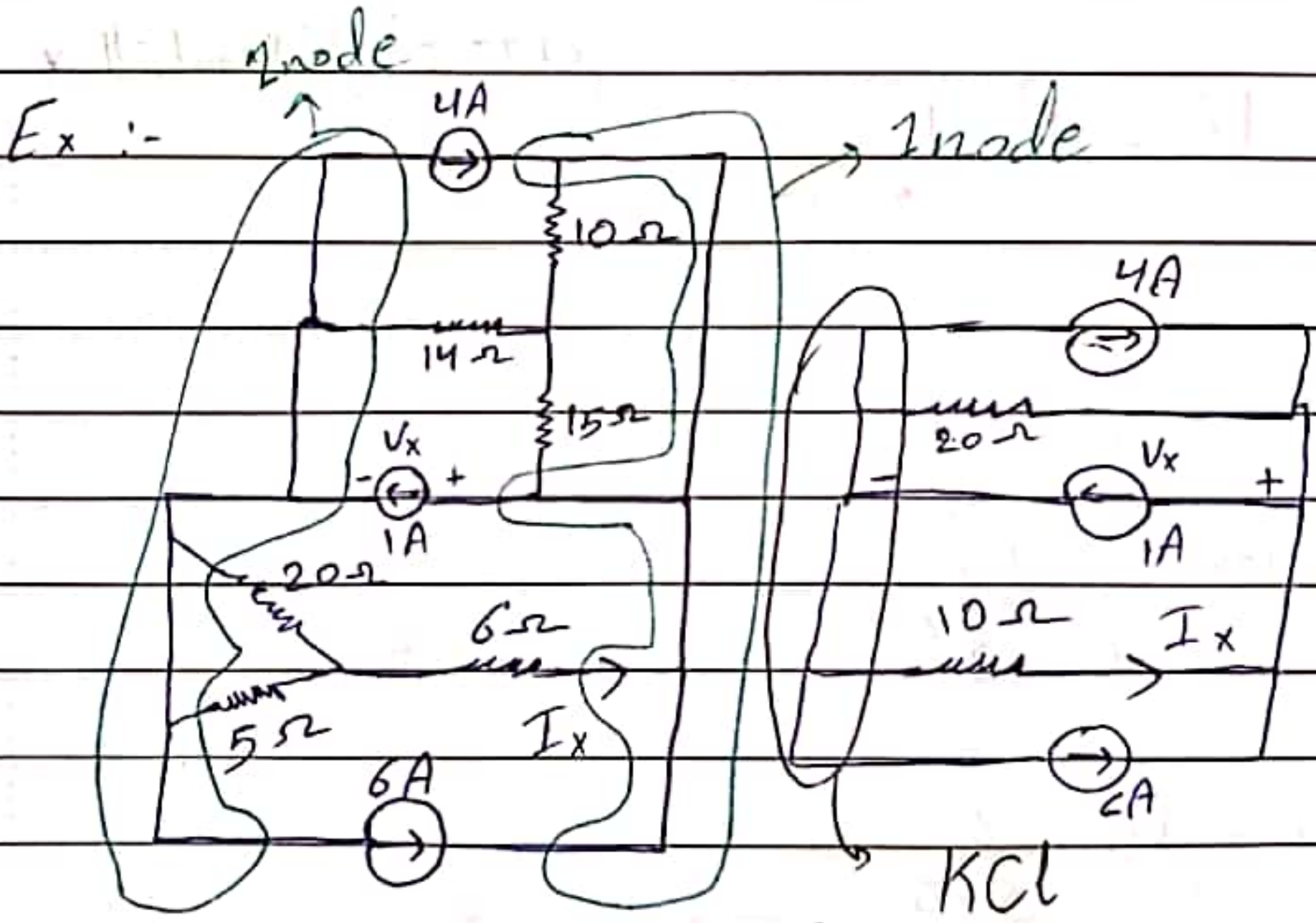
$$R_{eq} = ((50 + 40) \parallel 60 \parallel 24) + 5 \parallel 20 + 10 = 19.85 \Omega$$



$$V_x = 60 \text{ Volt}$$

$$I_x = \frac{-60}{10} = -6 \text{ A}$$

Voltage Division Rule :-

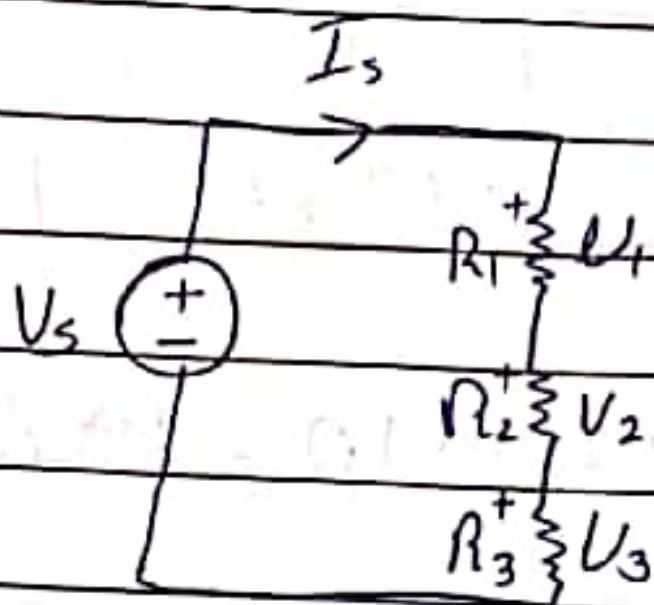

$$V_1 = I_s R_1 = \frac{V_s}{R_1 + R_2 + R_3} R_1$$


$$V_2 = I_s R_2$$

$$V_3 = I_s R_3$$

* القسمة الجبرية على \$V\$

$$V_x = V_s \frac{R_x}{R_1 + R_2 + R_3 \dots}$$


Ex :-

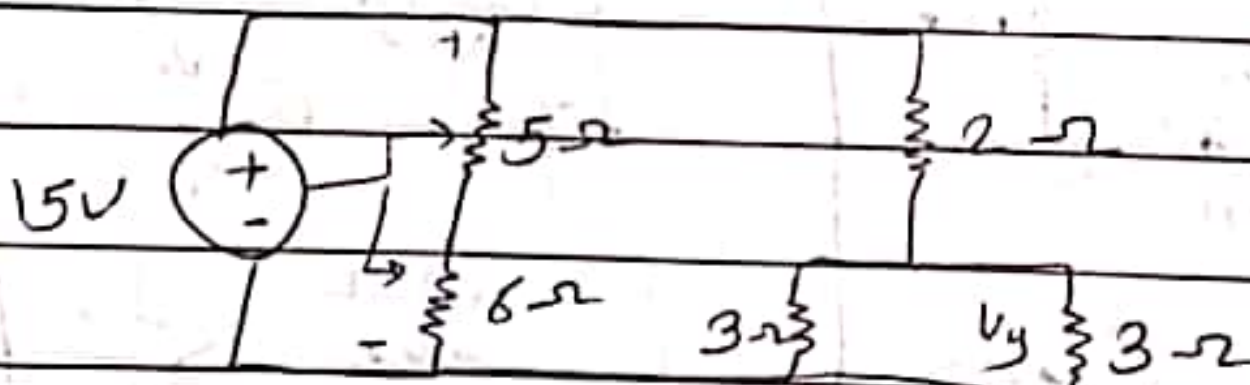

$$V_x = 15 \cdot \frac{6}{5+6} \text{ V}$$

$$V_y = 15 \cdot \frac{1.5}{1.5+2} \text{ V}$$


Parallel (3Ω, 3Ω)

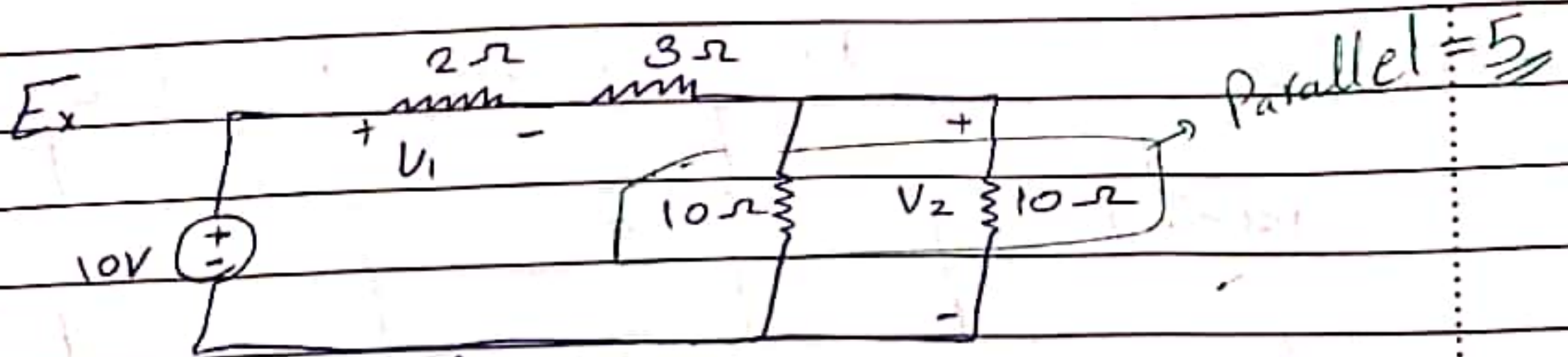

find V_1 and V_2 using voltage division rule

$$V_1 = 2V, \quad V_2 = 5V$$


→ Current division Rule

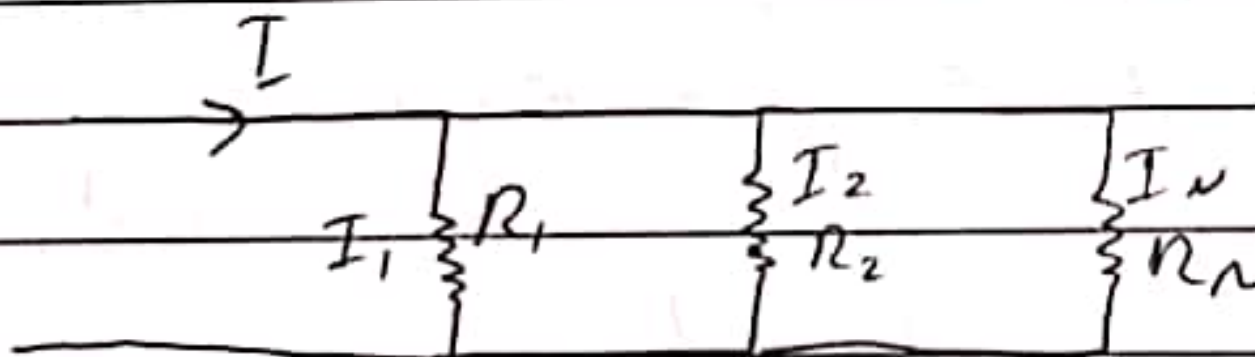

$$I_K = \frac{\frac{1}{R_K}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$

for two resistors
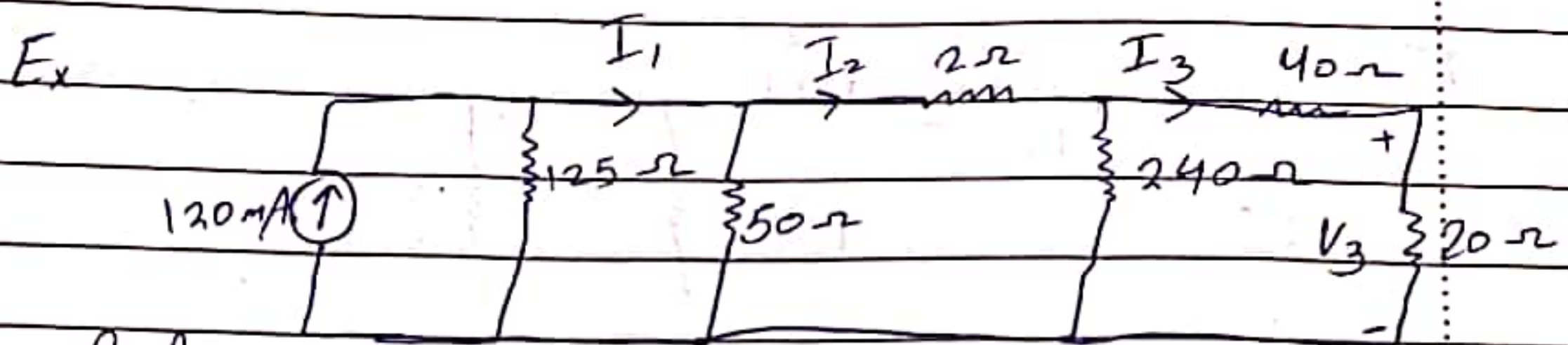
$$I_1 = I \frac{R_2}{R_1 + R_2}, \quad I_2 = I \frac{R_1}{R_1 + R_2}$$



Find I_1 , I_2 , V_3

$$R_{eq} = [(20 + 40) \parallel 240] + 2 \parallel 50 = 25 \Omega$$

$$I = 120 \times \frac{125}{125 + 25} = 100 \text{ mA}$$


$$R_{eq} = ((20 + 40) \parallel 240) + 2 = 50 \Omega$$

$$I_2 = I_1 \frac{50}{50 + 50} = 50 \text{ mA}$$

$$I_3 = I_2 \frac{240}{240 + 60} = 40 \text{ mA}$$

$$V_3 = 40 \times 10^{-3} \times 20 = 0.8 \text{ V}$$

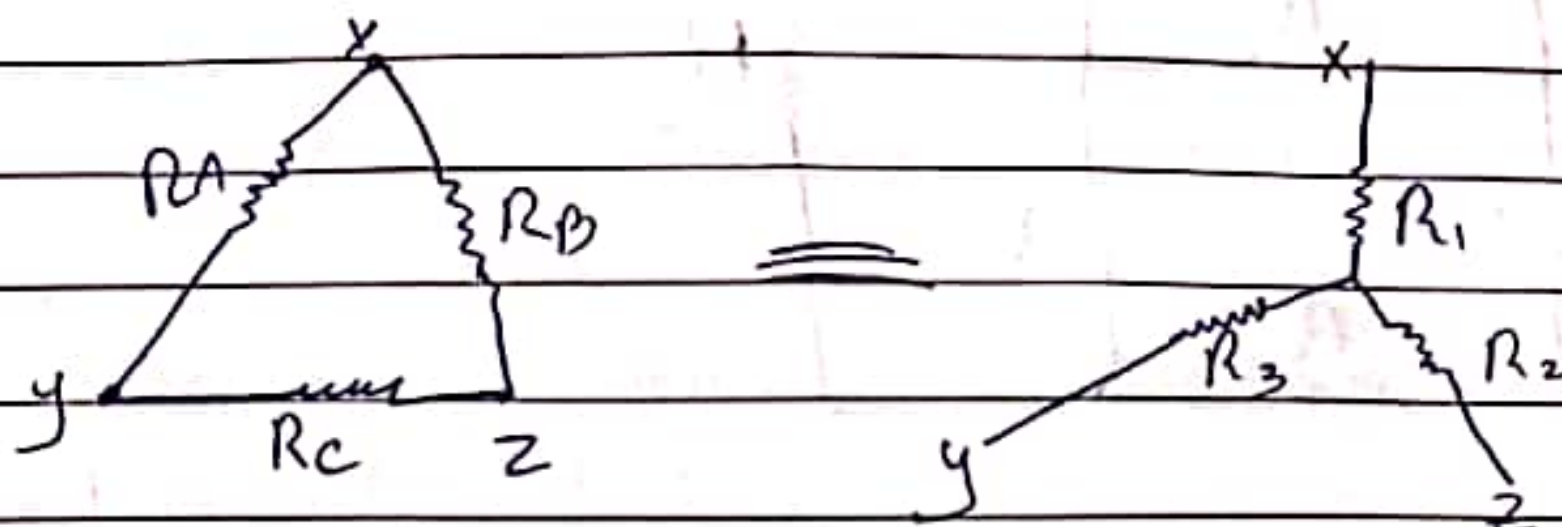• $\Delta \rightarrow Y$ Conversion "no series, no parallel"




$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}, \quad R_2 = \frac{R_B R_C}{R_A + R_B + R_C}, \quad R_3 = \frac{R_A R_C}{R_A + R_B + R_C}$$

• $Y \rightarrow \Delta$ Conversion

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}, \quad R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

Ex :-

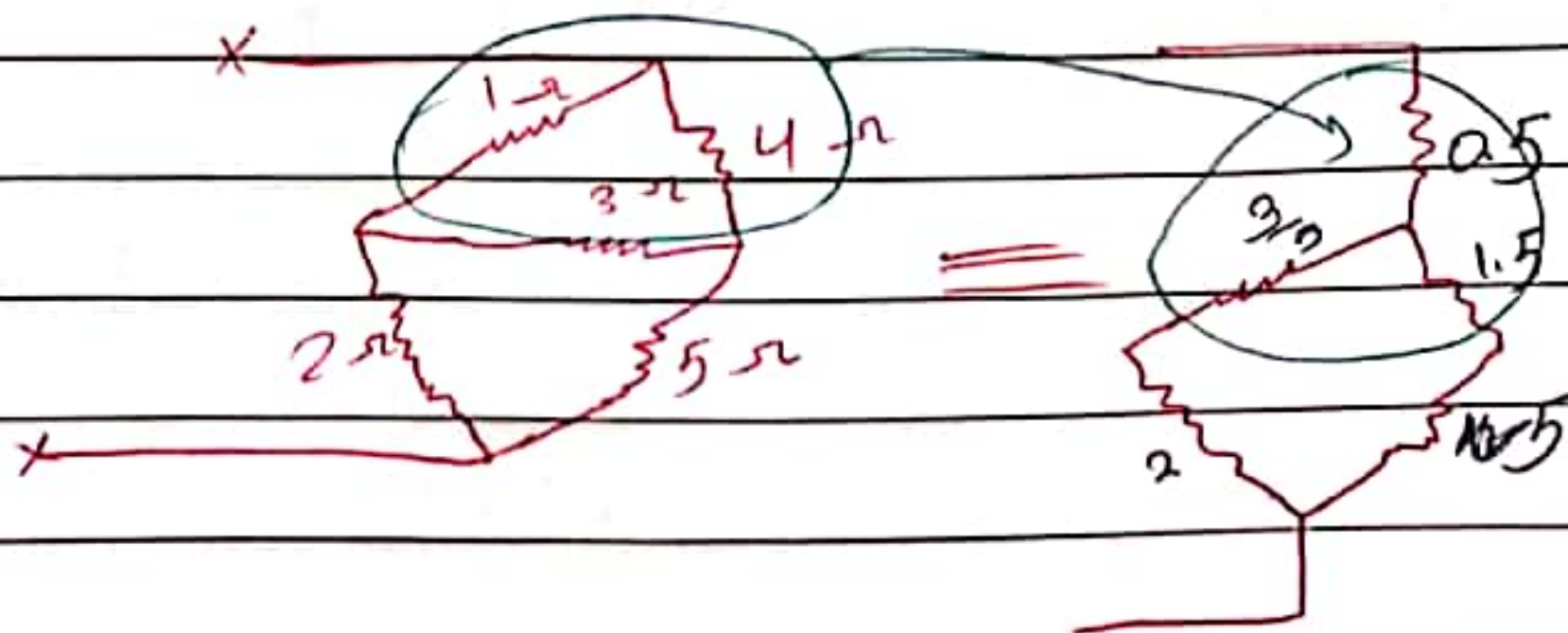


* Advanced Techniques

• Nodal Analysis - based on KCL

* Steps of Analysis

- 1- Determine the nodes in the circuit
- 2- select the node that has the higher number of connections as a Reference node.
- 3- Apply KCL at the rest of nodes
- 4- solve the equations $\rightarrow \left\{ \begin{array}{l} \text{no. of eqn.} = \text{no. of} \\ \text{nodes} - 1 \end{array} \right\}$

$$\sum I \text{ out of node} = 0$$

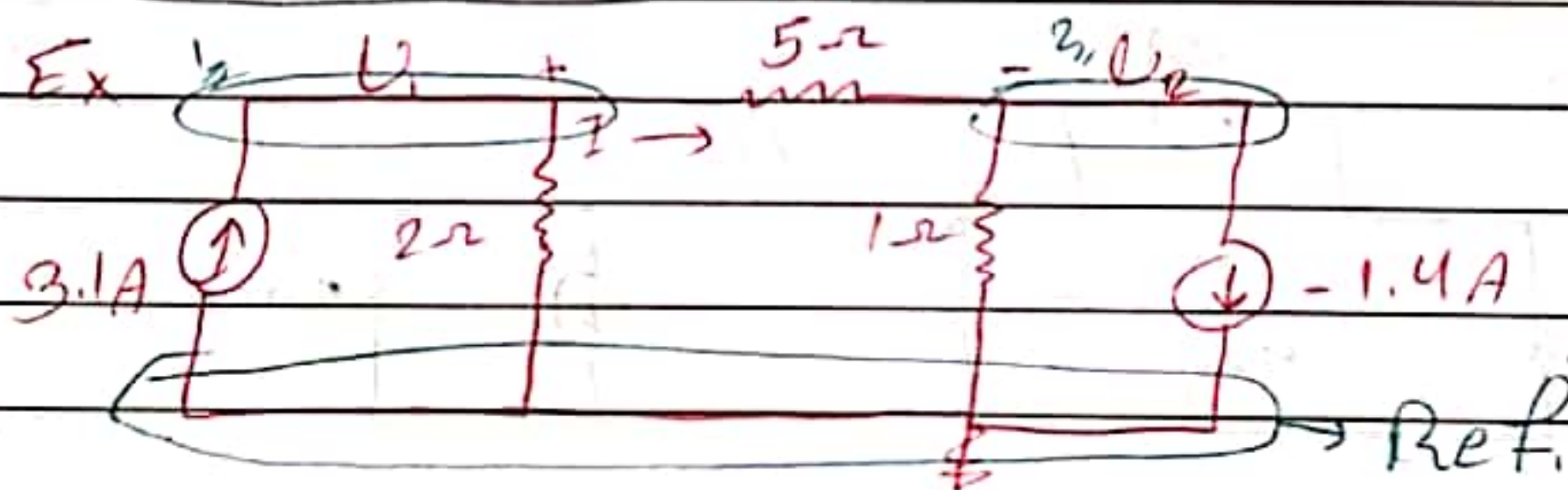


$$\text{KCL at node (1)} \Rightarrow \sum I \text{ out} = 0 \Rightarrow -3.1 + \frac{U_1 - 0}{2} + \frac{U_1 - U_2}{5} = 0$$

$$\text{KCL at node 2,} \Rightarrow -1.4 + \frac{U_2}{1} + \frac{U_2 - U_1}{5} = 0 \dots \text{eq (2)}$$

$$\text{solve 1, and 2, } U_1 = 5V$$

$$U_2 = 2V$$
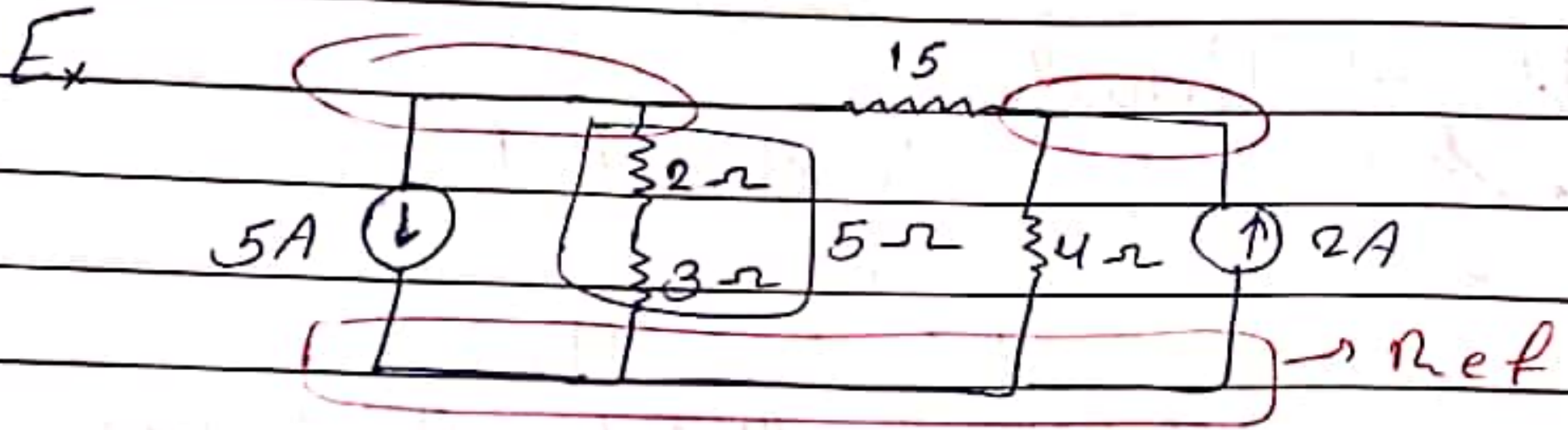
$$I = \frac{U_1 - U_2}{5} = \frac{5 - 2}{5} = \frac{3}{5} A$$





KCL at node 1 = $5 + \frac{V_1}{5} + \frac{V_1 - V_x}{15} = 0 \dots 1$

KCL at node 2 = $-2 + \frac{V_x}{4} + \frac{V_x - V_1}{15} = 0 \dots 2$

∴ nodes 1 & 2 are connected as a single node


Example :-

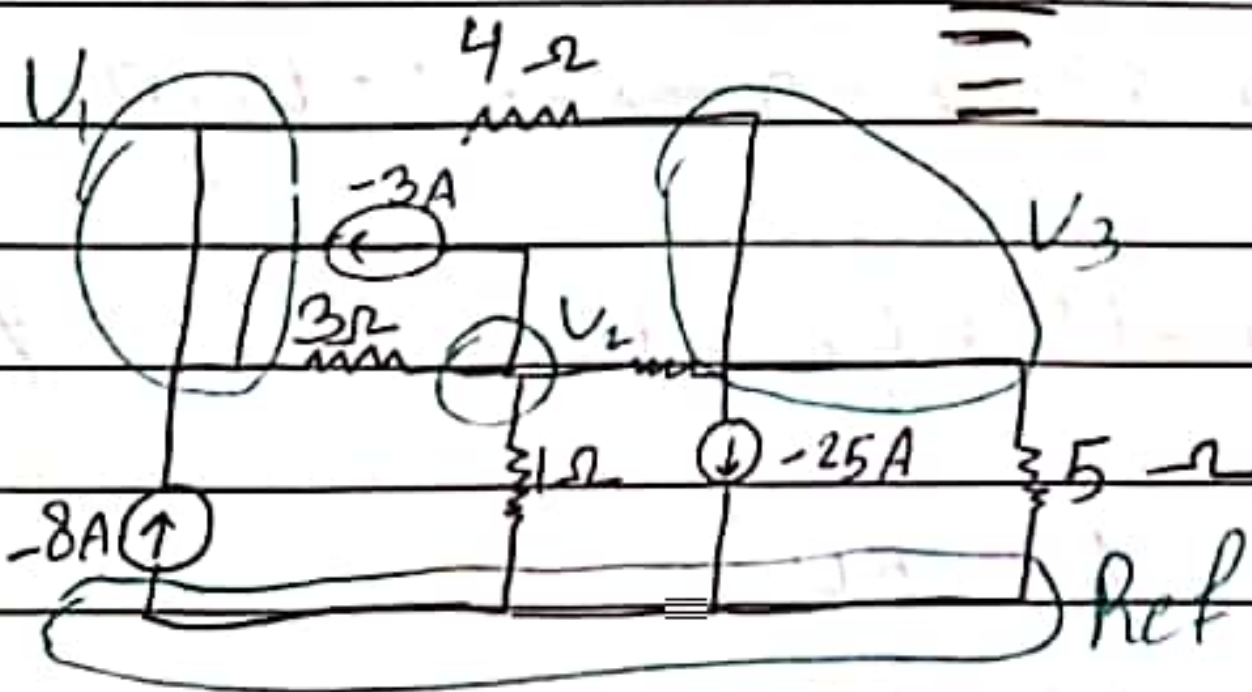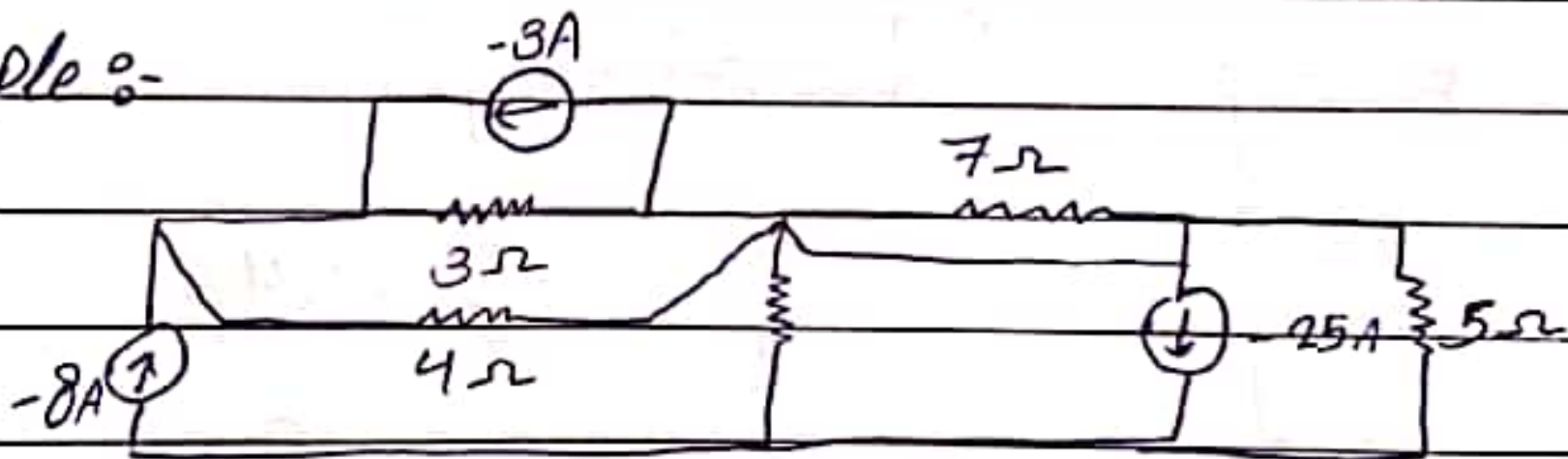

→ KCL at node 1: $8 + 3 + \frac{V - V_3}{3} + \frac{V - V_3}{4} = 0 \dots (1)$
 KCL at node 2: $-3 + \frac{V_2}{3} + \frac{V_2 - V_1}{3} + \frac{V_2 - V_3}{7} = 0 \dots (2)$
 KCL at node 3: $-25 + \frac{V_3}{5} + \frac{V_2 - V_3}{7} + \frac{V_3 - V_1}{4} = 0 \dots (3)$


• لا يكون 8 و 3 و 25 و 5 و 3 و 7 و 4

Example :-

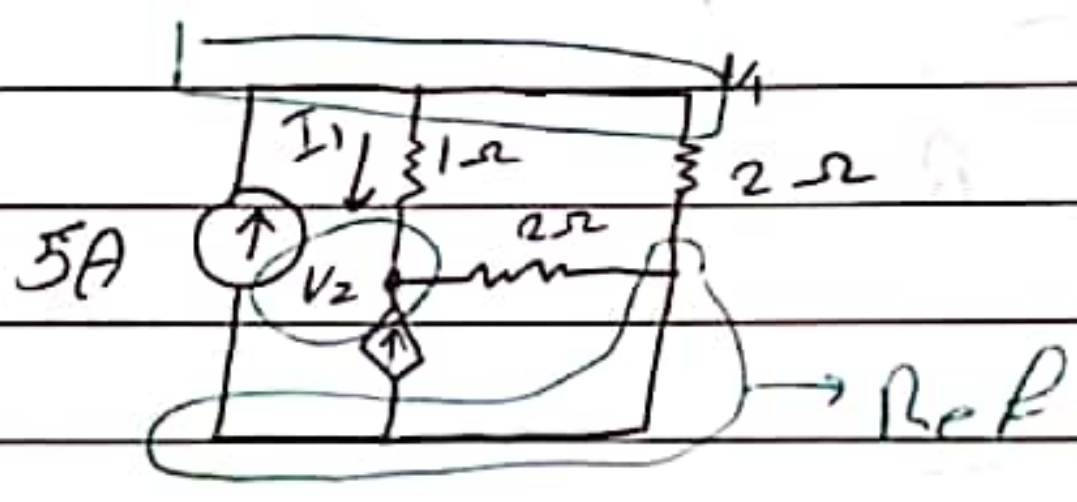

KCL node 1: $\frac{V_1}{2} + \frac{V_1 - V_2}{1} - 5 = 0 \dots (1)$
 KCL node 2: $-27 + \frac{V_2}{2} + \frac{V_2 - V_1}{1} = 0 \dots (2)$
 $V_1 - V_2$

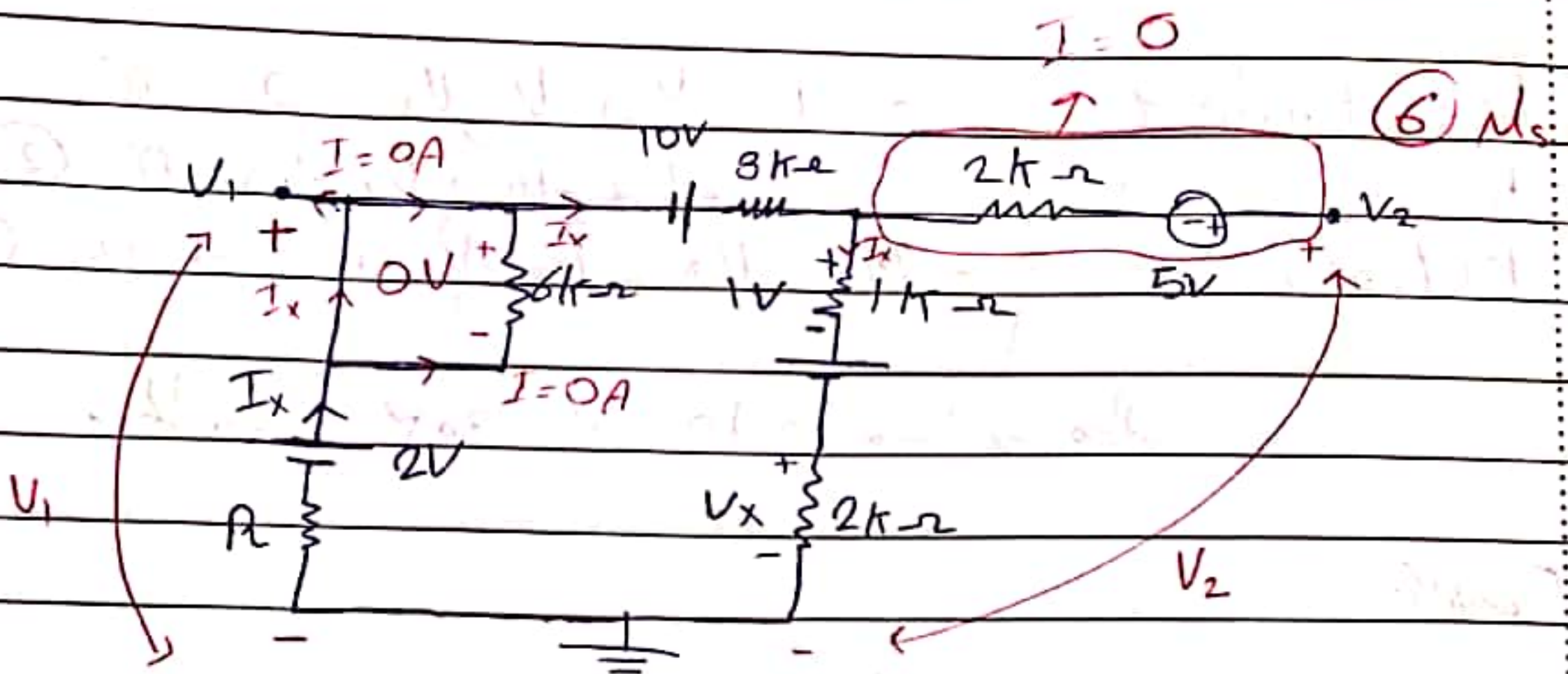$V_1 = \frac{70}{9} \text{ V} \quad \vee \quad V_2 = \frac{20}{3} \text{ V}$



a) find V_1, V_2, I_x, V_x, R

$$I_x = \frac{1V}{1k\Omega} = \boxed{1mA}$$

$$V_x = 2 \times 1 = \boxed{2V}$$

loop \wedge

$$-V_1 - 10 + 3 + 1 + 3 + 2 = 0$$

$$V_1 = \boxed{-1V}$$

loop \wedge

$$V_2 - V_x - 3 - 1 - 5 = 0$$

$$V_2 = \boxed{11V}$$

$$RI_x - 2 - 10 + 3 + 1 + 3 + 2 = 0$$


$$R = \boxed{3k\Omega}$$

b) Find P_{abs} by 10V and $P_{generated}$ by 3V source

$$P_{abs} = -1 \times 10 = -10 \text{ mW}$$


$$P_{generated} = -P_{abs} = -(1 \times 3) = -3 \text{ mW}$$

Q:- Find I_x using current division rule

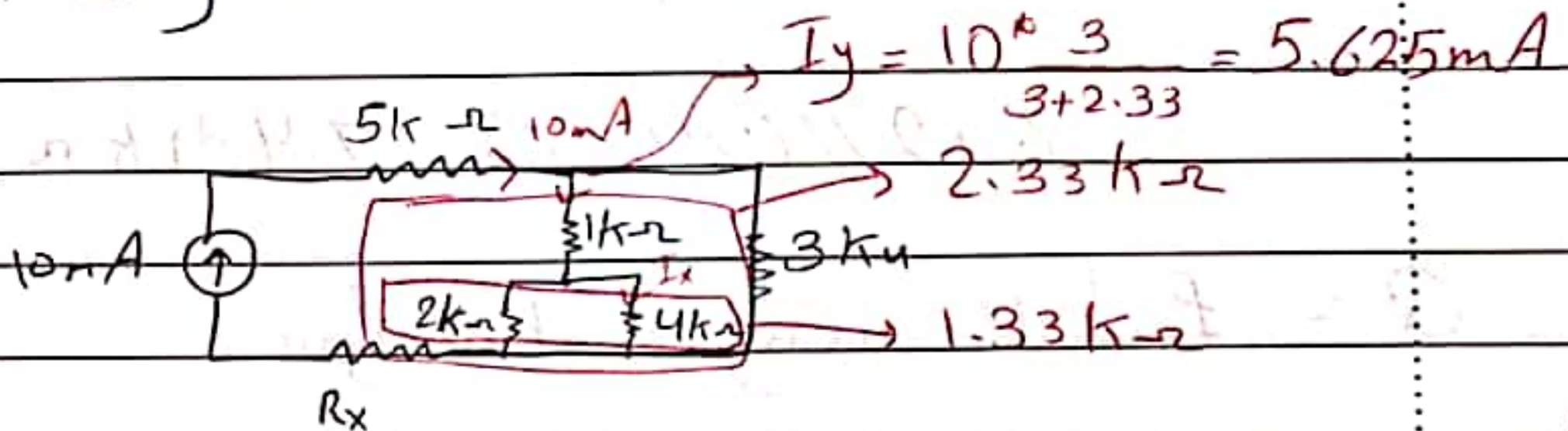


$$I_x = I_y \frac{2}{2 + 4} = 1.875 \text{ mA}$$

Q:- Find V_x using voltage division rule

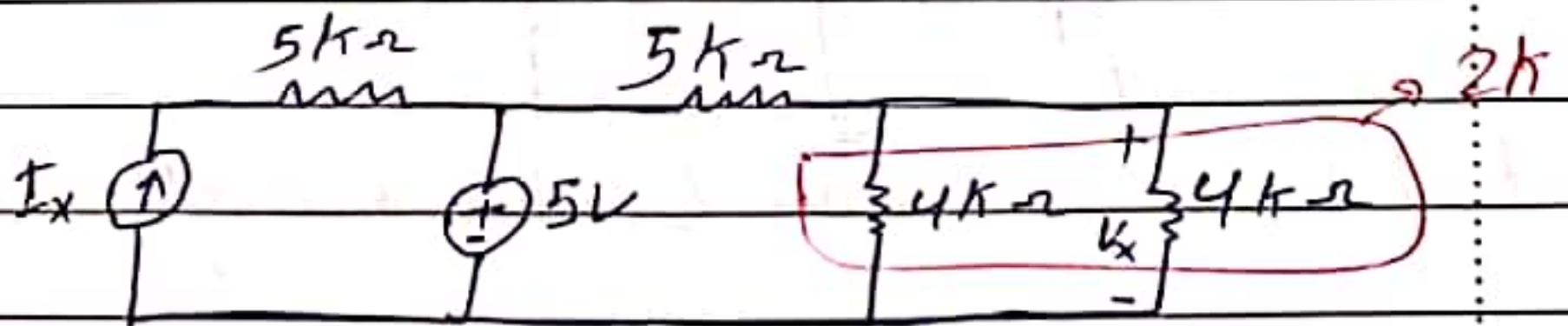

$$V_x = 5 \times \frac{2}{2 + 3} = 2 \text{ V}$$


Q:- Find Req.

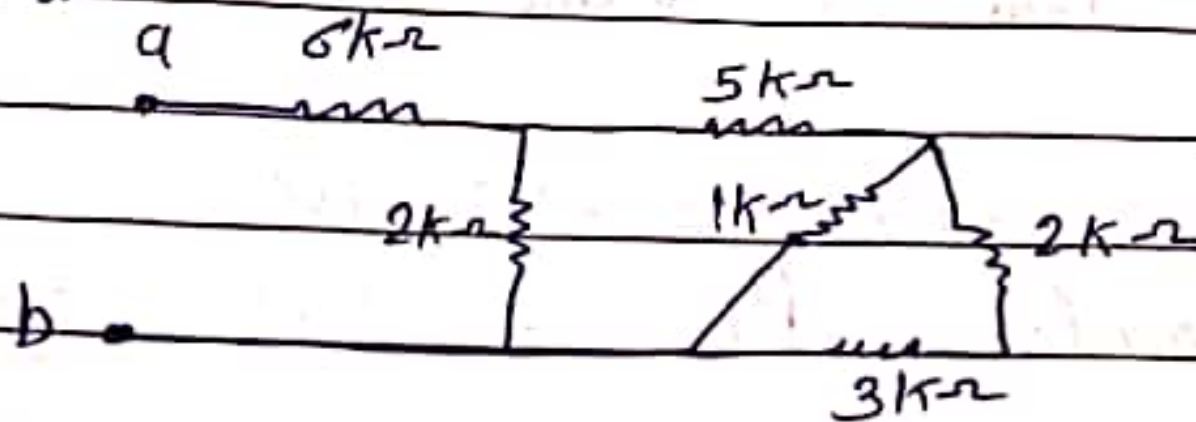

$$\rightarrow 2, 3 \rightarrow 5k\Omega // 1 + 3$$

$$6 + 2 // (1 // 5 + 3) = 7.489k\Omega$$

Q:- Find V_1 using nodal analysis

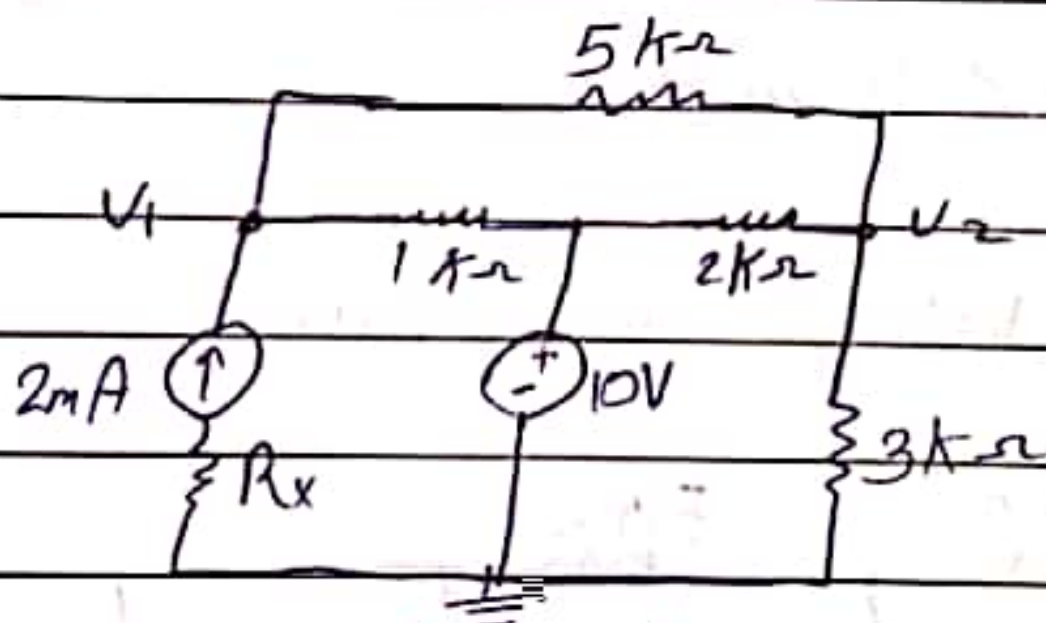


$$\text{Kcl } V_1: -2 + \frac{V_1 - 10}{1} + \frac{V_1 - V_2}{5} = 0 \dots (1)$$

$$\text{Kcl } V_2: \frac{V_2 - 0}{3} + \frac{V_2 + 10}{2} + \frac{V_2 - V_1}{5} = 0 \dots (2)$$

$$V_1 = 11.163V$$

$$V_2 = 6.978V$$

Supernode لئلا نجا لئلا node 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 21, 22, 23, 24, 25, 26, 27, 28, 29, 30, 31, 32, 33, 34, 35, 36, 37, 38, 39, 40, 41, 42, 43, 44, 45, 46, 47, 48, 49, 50, 51, 52, 53, 54, 55, 56, 57, 58, 59, 60, 61, 62, 63, 64, 65, 66, 67, 68, 69, 70, 71, 72, 73, 74, 75, 76, 77, 78, 79, 80, 81, 82, 83, 84, 85, 86, 87, 88, 89, 90, 91, 92, 93, 94, 95, 96, 97, 98, 99, 100

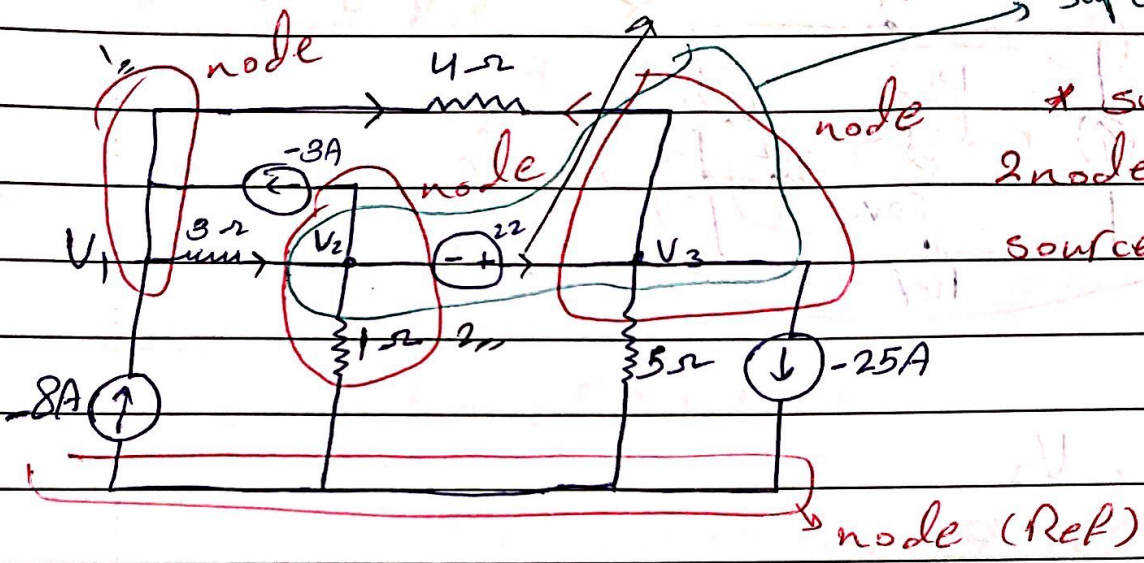

KCL node 1 :- $8 + 3 + \frac{V_1 - V_3}{4} + \frac{V_1 + V_2}{3} = 0 \dots \textcircled{1}$


KCL node 2 :- $-3 + \frac{V_2}{1} + \frac{V_2 - V_1}{3} = 0 \dots \textcircled{2}$

Supernode :- $-5 + \frac{V_3}{5} + \frac{V_2}{1} + \frac{V_2 - V_1}{3} - 3 + \frac{V_3 - V_1}{4} = 0 \dots \textcircled{3}$

Inside supernode :- $V_3 - V_2 = 22 \dots \textcircled{3}$

$V_1 = 1.071V, V_2 = 10.5V, V_3 = 32.5V$

Example :-

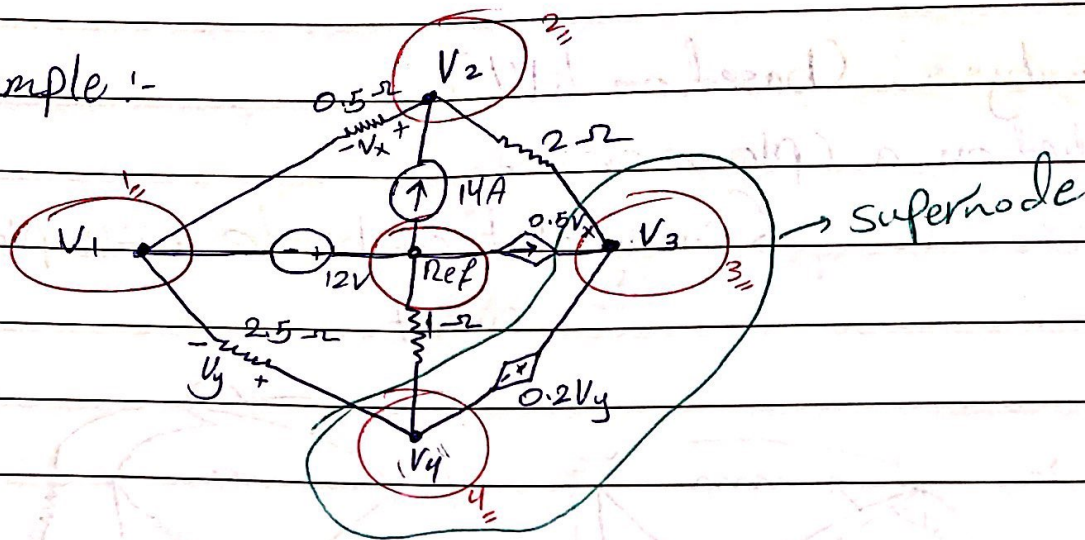

another:

* when the voltage source is between the Ref. and node the another node = zero - voltage source

$$0 - 12 = -12V = V_1$$

$$\text{KCL } V_2 = -14 + \frac{V_2 - V_1}{0.5} + \frac{V_2 - V_3}{2} \dots \textcircled{1}$$

KCL ~~V3~~ supernode \rightarrow "inside equation" = $V_3 - V_4 = 0.5V_y$

where $V_y = V_4 - V_1 = V_4 + 12$

~~sa~~ supernode $\rightarrow V_3 - V_2 = 0.2V_x$ "where $V_x = V_2 + 12$ "

$$\frac{V_4 - 0}{1} - \frac{V_4 - V_1}{2.5} = 0 \dots \textcircled{3}$$

$$V_1 = -12V, \quad V_2 = -4V, \quad V_3 = 1 \times 10^{-14} \approx 0$$


$$V_4 = -2V$$

• Mesh Analysis: (based on KVL)


* It's applied on a (planer circuit)

↳ circuit that can be drawn in a plane circuit.

Example:-

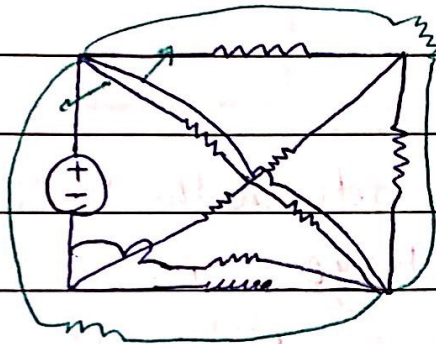

Planer

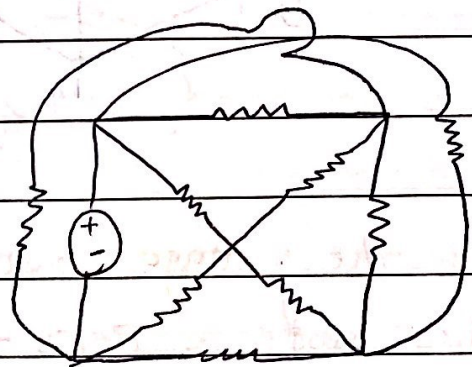

not Planer

"there will be an overlap if we reconnect it"

• Steps of mesh Analysis

1- Locate all the meshes in the circuit. (mesh \equiv window)
"closed loop"


2- Locate one current to each mesh.

3- Write the KVL equation for each mesh.

4- Solve the mesh equations.

Example:-

حل المسألة باستخدام الحلقات

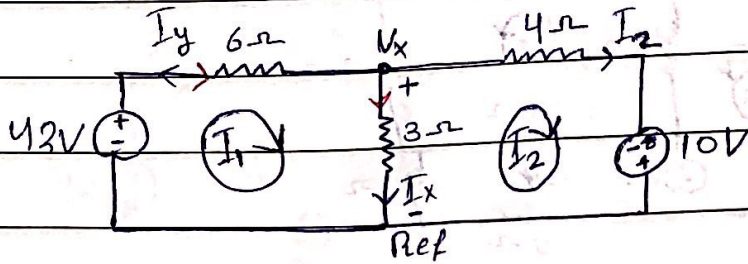

Find all the currents

$$\text{KVL at mesh 1: } -42 + 6I_1 + 3(I_1 - I_2) = 0 \dots \textcircled{1}$$

$$\text{KVL at mesh 2: } -10 + 3(I_2 - I_1) + 4I_2 = 0 \dots \textcircled{2}$$


$$\text{Solve 1 and 2} \rightarrow I_1 = 6A, I_2 = 4A$$

find I_x, I_y, I_2, V_x

$$I_y = -I_1 = -6A, I_2 = I_2 = 4A$$

$$I_x = I_1 - I_2 = 2A, V_x = 3I_x = 6V$$

Example:-

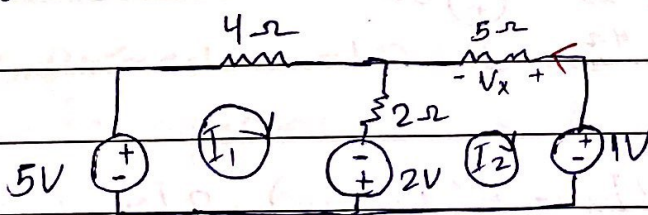

using mesh analysis find

1. Pabs by 4-Ω

2. V_x

$$\text{KVL at mesh 1: } -5 + 4I_1 + 2(I_1 - I_2) - 2 = 0 \dots \textcircled{1} \quad \times P_{abs} = I^2 R$$


$$\text{KVL at mesh 2: } 1 + 2 + 2(I_2 - I_1) + 5I_2 = 0 \dots \textcircled{2}$$

$$I_1 = \frac{43}{38} A, I_2 = \frac{2}{19} A$$

$$1) P_{abs} = \left(\frac{43}{38} \right)^2 4 W$$

$$2) V_x = -I_2 \times 5 = -\frac{2}{19} \times 5 V$$

Example:-

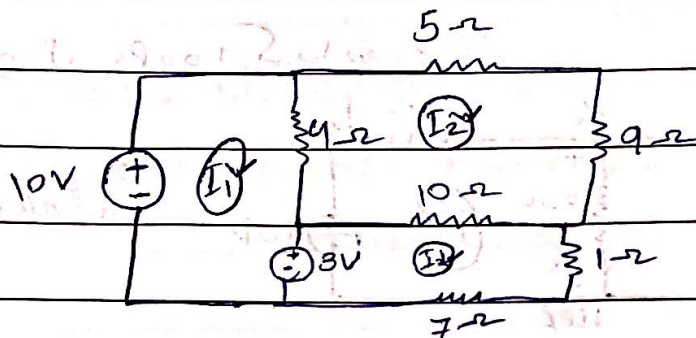

Find the current in each mesh:-


$$\text{KVL mesh 1: } -10 + 4(I_1 - I_2) + 3 = 0 \dots \text{①}$$

$$\text{KVL mesh 2: } 5I_2 + 9I_2 + 10(I_2 - I_3) + 4(I_2 - I_1) = 0 \dots \text{②}$$

$$\text{KVL mesh 3: } -3 + 10(I_3 - I_2) + I_3 + 7I_3 = 0 \dots \text{③}$$

$$I_1 = 2.22 \text{ A}, \quad I_2 = 470 \text{ mA}, \quad I_3 = 427.7 \text{ mA}$$

Example:-

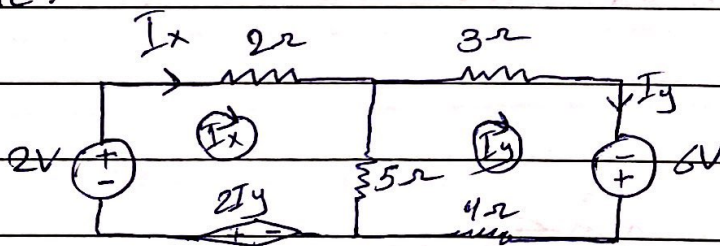


$$\text{KVL mesh 1: } -2 + 2I_x + 5(I_x - I_y) - 2I_y = 0 \dots \text{①}$$

$$\text{KVL mesh 2: } -6 + 3I_y + 4I_y + 5(I_y - I_x) = 0 \dots \text{②}$$

$$I_x = \frac{66}{49}, \quad I_y = \frac{52}{49}$$

Example:-

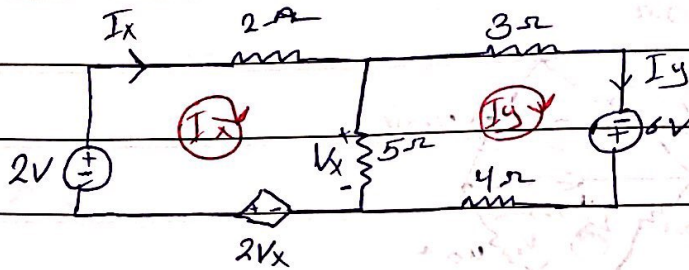


$$5(I_x - I_y)$$

KVL mesh 1:- $-2 + 2I_x + 5(I_x - I_y) - 2V_x = 0 \dots \textcircled{1}$

KVL mesh 2:- $-6 + 4I_y + 5(I_y - I_x) + 3I_y = 0 \dots \textcircled{2}$

$$I_x = \frac{6}{11} \text{ A}, \quad I_y = \frac{8}{11} \text{ A}$$

Example:-

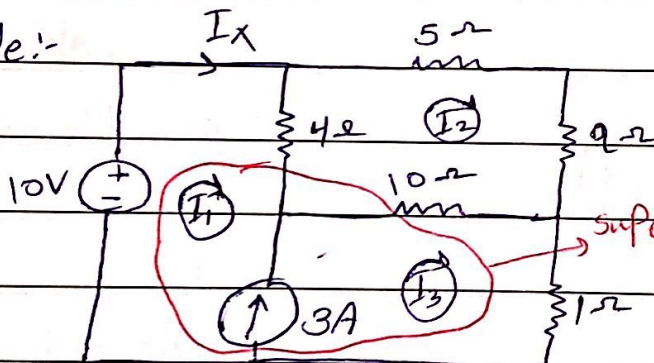

* Supermesh:- two meshes and current source between them.

Supermesh:- $-10 + 4(I_1 - I_2) + 10(I_3 - I_2) + 1(I_3) = 0 \dots \textcircled{1}$


inside supermesh = $I_3 - I_1 = 3 \dots \textcircled{2}$

mesh 2:- $5I_2 + 9I_2 + 4(I_2 - I_1) + 10(I_2 - I_3) = 0 \dots \textcircled{3}$

$$I_1 = \frac{29}{15} \text{ A}, \quad I_2 = \frac{11}{105} \text{ A}, \quad I_3 = \frac{16}{15} \text{ A}$$

$I_1 = I_x$, current in $10 \Omega = I_3 - I_2$

Example 1-

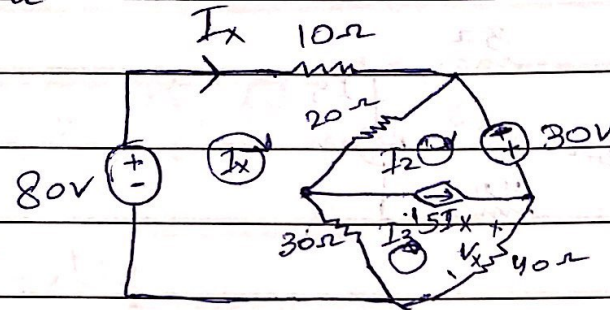

$$\text{mesh 1 :- } -80 + 10 I_x + 20 (I_x - I_2) + 30 (I_x - I_3) = 0$$


$$\text{supermesh :- } -30 + 4 I_3 + 30 (I_3 - I_x) + 20 (I_2 - I_x) = 0 \rightarrow \textcircled{2}$$

$$\text{inside supermesh :- } I_3 - I_2 = 15 I_x$$


$$I_1 = \frac{87}{149} \text{ A}, I_2 = \frac{-91.7}{149}, I_3 = \frac{388}{149} \text{ A}, V_x = 40 I_3$$

• Super Position

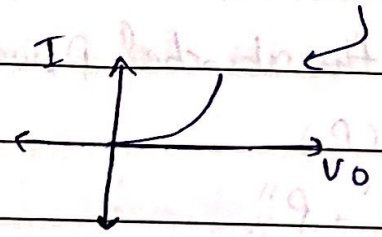- it's applied on linear circuits
- Linear circuit :- all its elements are linear (V or I is linear)
- e.g., R, C, L → linear elements
- Diode, transistor → not linear elements




* Example :-

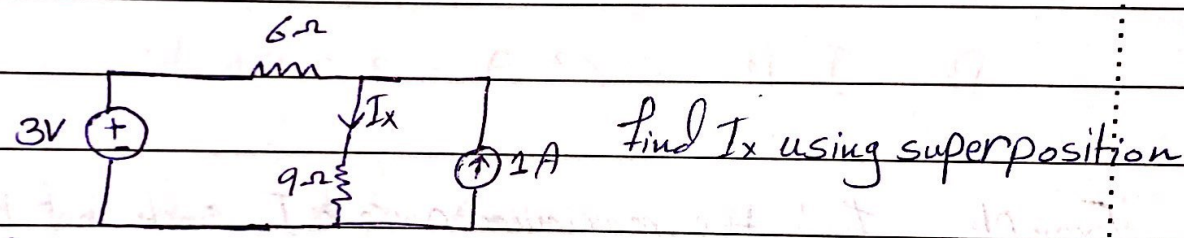

• we will find the contribution of each element in the value of I_x
 I_x' due to 3V only. (contribution of 3V in I_x)


→ Kill 1A source

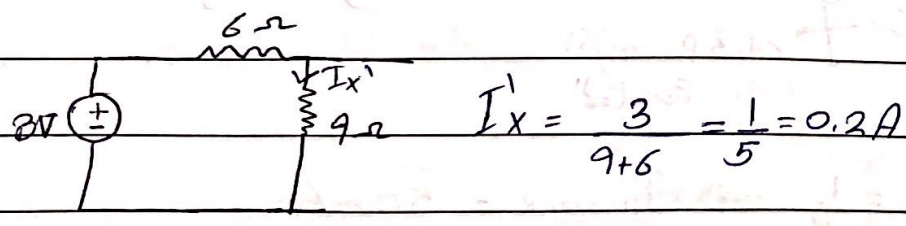

* killing current source :-
 - open circuit.
 * killing Voltage source :-
 short circuit.

I_x'' due to 1A only (contribution of ~~3V~~ 1A in I_x)

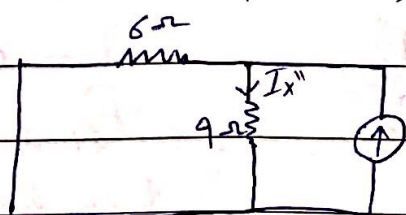
$$I_x'' = 1 \cdot \frac{6}{9+6} = \frac{6}{15}$$



$$I_x = I_x' + I_x'' = \frac{3}{5} = 0.6A$$

* Note:- we can use superposition to find the current or the voltage but not the power.

Example:-

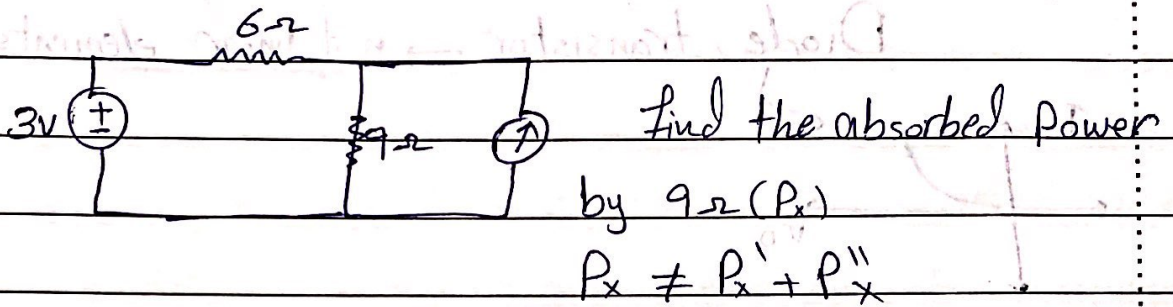


Sol:- find I_x then find P_x

$$\rightarrow I_x' = 0.2A \quad \rightarrow I_x'' = 0.4A \quad \rightarrow I_x = 0.2 + 0.4 = 0.6A$$

$$P_x = I_x^2 R = 0.6^2 \cdot 9 = 3.2W$$

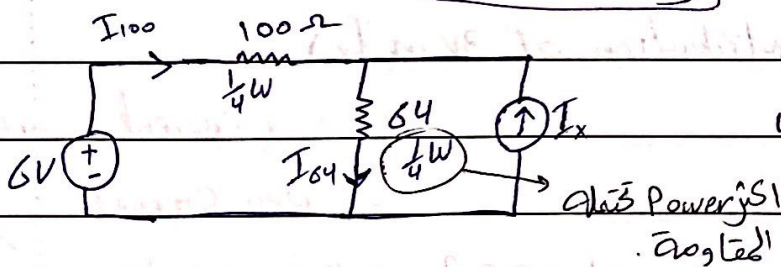Example:- find the maximum current I_x such that the resistors do not exceed their power rating \rightarrow maximum power that can be dissipated by the element without any damage



$$P_{rating} = I_{100}^2 \times 100 = \frac{1}{4} \Rightarrow I_{100max} = 50mA$$

$$= I_{64}^2 \times 64 = \frac{1}{4} \Rightarrow I_{64max} = 62.5mA$$

$$I_{100} \text{ due to } 6V \text{ only} \rightarrow I_{100}' = \frac{6}{164} = 36.59mA$$

$$I_{100} \text{ due to } I_x \text{ only} \rightarrow I_{100}'' = I_x \cdot \frac{64}{164}$$

$$I_{64} \text{ due to } 6V \text{ only} \rightarrow I_{64}' = \frac{6}{164} = 36.59mA$$

$$I_{64} \text{ due to } I_x \text{ only} \rightarrow I_{64}'' = I_x \cdot \frac{100}{164}$$

$$I_{100} = I_{100}' + I_{100}''$$

$$I_{64} = I_{64}' + I_{64}''$$

~~$$I_{64} = I_{64}' + I_{64}''$$~~


$$I_{64} < I_{64max} \rightarrow 36.59 + I_x \frac{100}{184} < 62.5 \rightarrow I_x < 42.49 \text{ mA}$$

$$I_{100} < I_{100max} \rightarrow 36.59 - I_x \frac{64}{184} < 50 \rightarrow I_x > -34.36 \text{ mA}$$


Range $\left\{ \begin{array}{c} \leftarrow \text{التيار الاقصى} \\ -34.36 \quad \quad \quad 42.49 \quad \rightarrow \text{التيار الاقصى} \end{array} \right\}$

* Note:- We don't Kill dependent sources in superposition.

Example:-

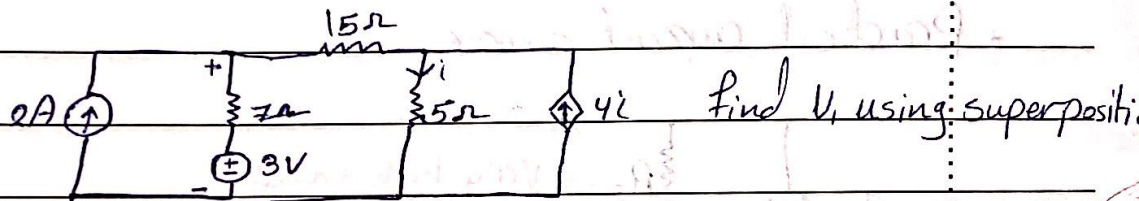


→ V_1' due to 2A only

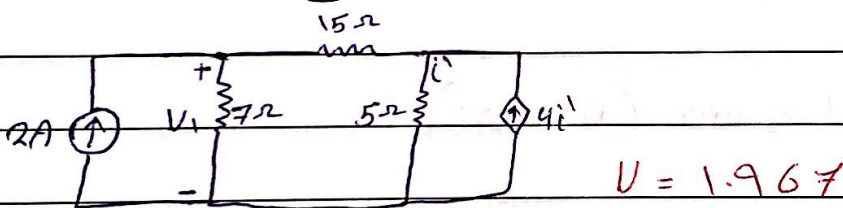

~~$V_1 = 9.18 + 1.967 = 11.147 \text{ V}$~~


→ V_1'' due to 3V only

Solve using nodal or mesh

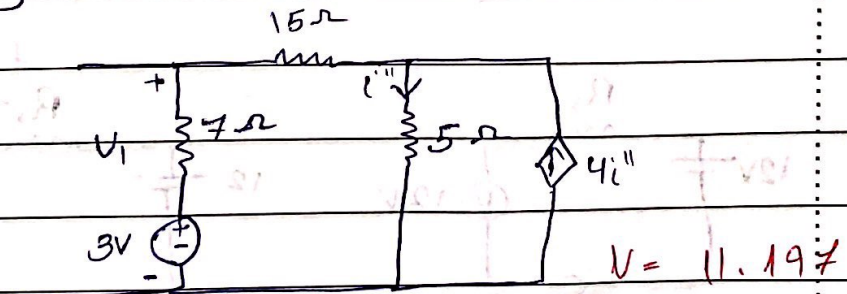


$$V_1 = 1.967 + 9.18 = 11.147 \text{ V}$$



Practical Voltage source

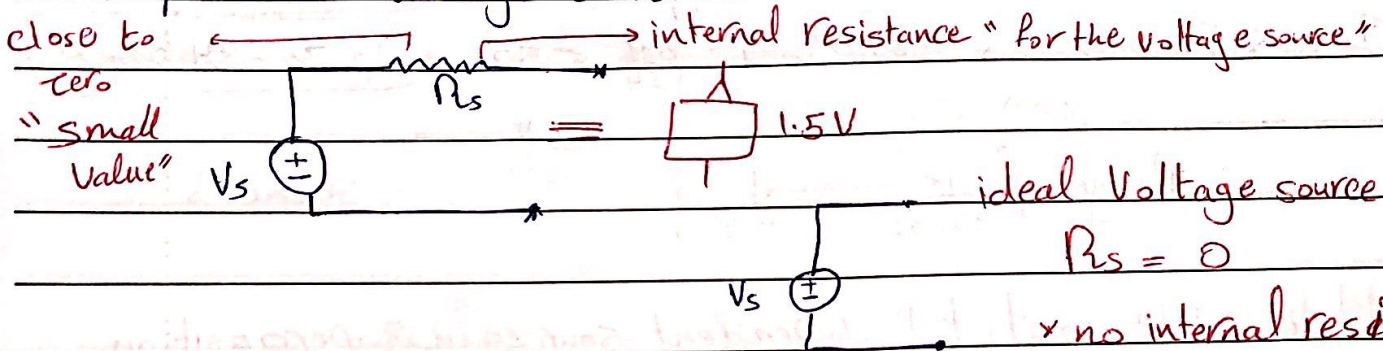


Practical current source

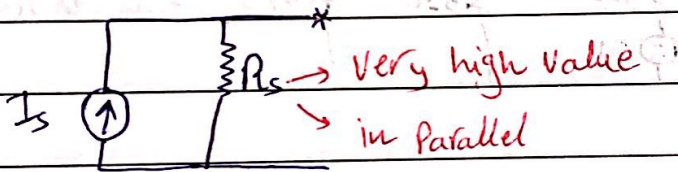

* ideal current source ($R_s = \infty$)

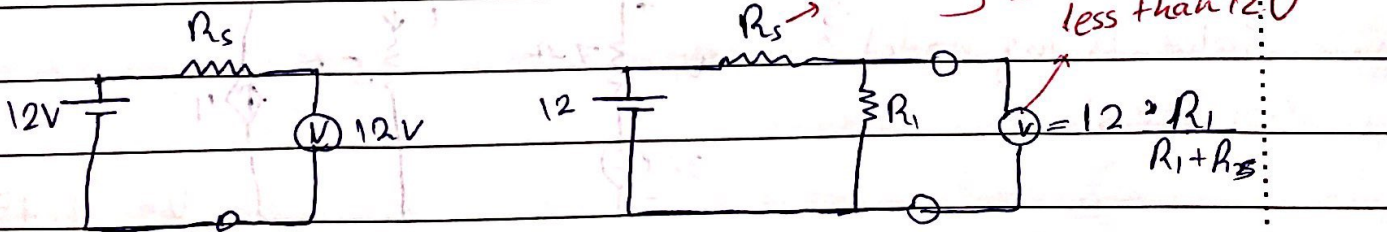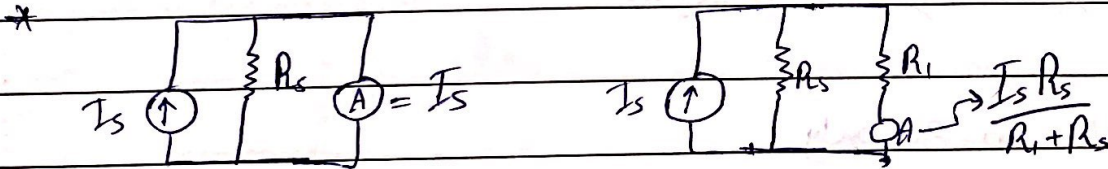

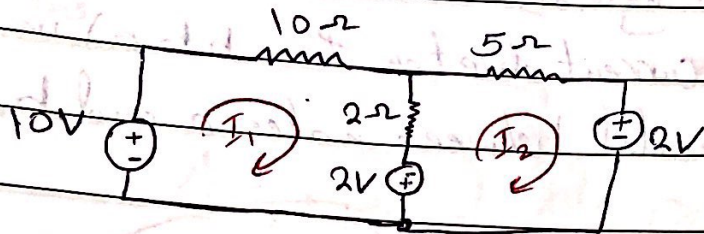Q₁ Find the mesh current equations for the circuit shown. 9 Ms




$$\text{mesh 1} \rightarrow -10 + 10I_1 + 2(I_1 - I_2) - 2 = 0 \dots \textcircled{1}$$

$$\text{mesh 2} \rightarrow 2 + 2 + 2(I_2 - I_1) + 5I_2 = 0 \dots \textcircled{2}$$


$$\text{Ans: } 12I_1 - 2I_2 = -12$$

$$-2I_1 + 7I_2 = -4$$

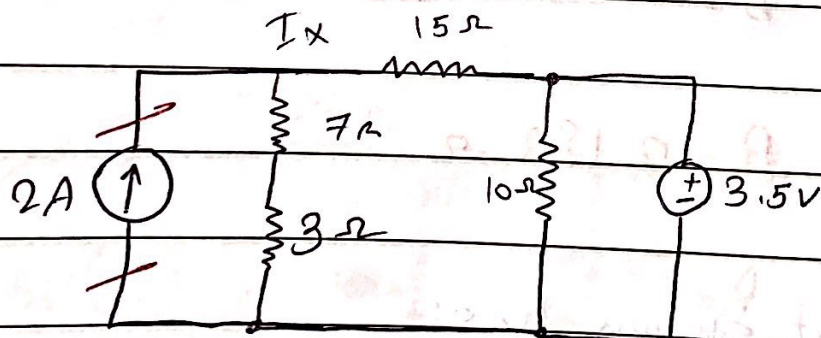Q₂ For the circuit shown, and based on the superposition principle, the portion of I_x under the effect of the 3.5 Voltage source acting alone is :-





$$I_x = 2 \times \frac{10}{10+15}$$

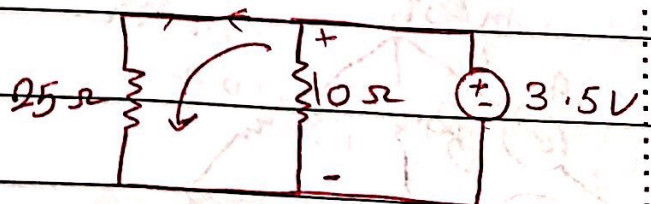


$$I_x = \frac{-3.5}{25} = -0.14A$$

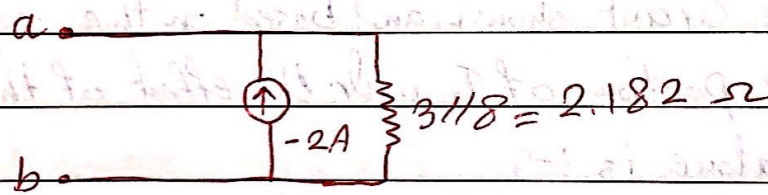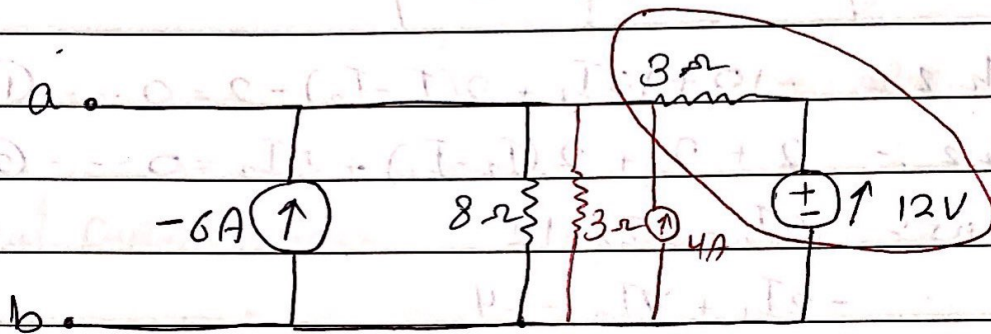Q₃ Using the principle of source transformation, convert the given circuit into a single node circuit with current source i (with current direction from b to a) in parallel with resistor R and connected between nodes a and b , find i and R .




$I = -2A, R = 2.182 \Omega$

Q₄: The circuit shown has:-

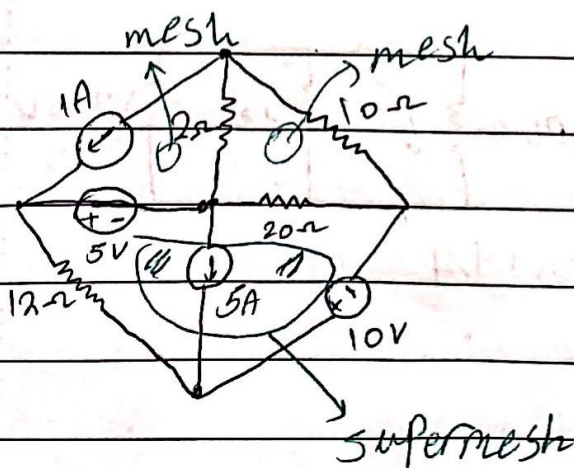


2 meshes and 1 supermesh.

• Source Transformation.

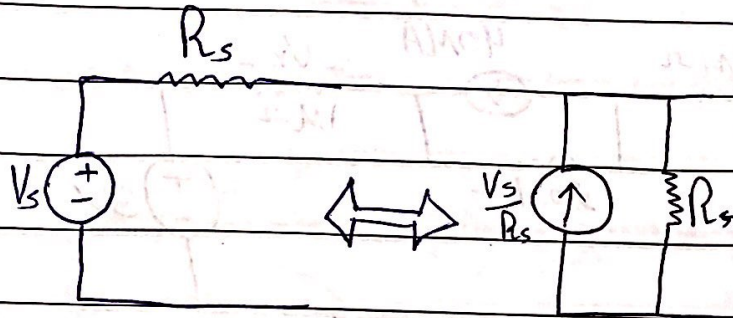


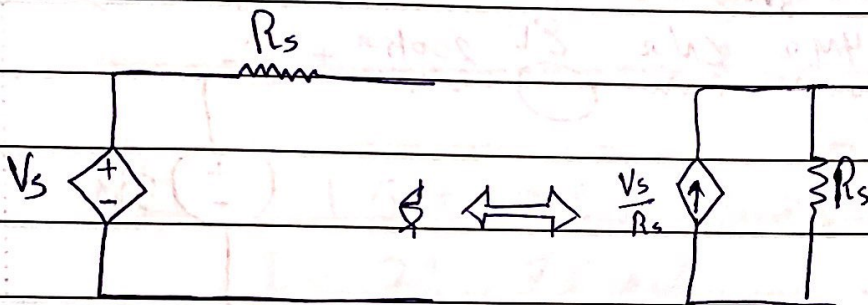* Voltage source with resistor in series can be converted to current source = $\frac{V_s}{R_s}$




* useful in analysis.

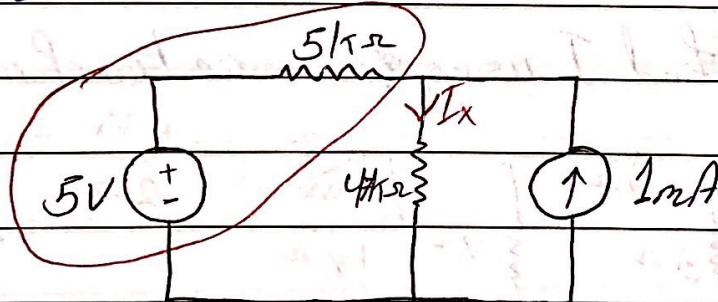Example :- Simplify the circuit then find I_x using source transformation





Sol :-

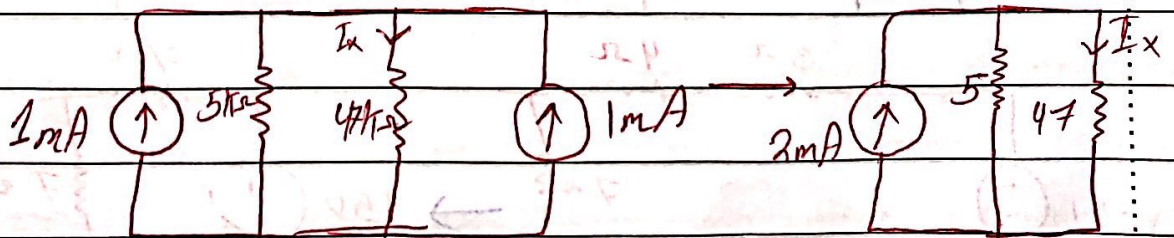

$$I_x = 2 \times \frac{5}{5+4} = 196 \mu\text{A}$$

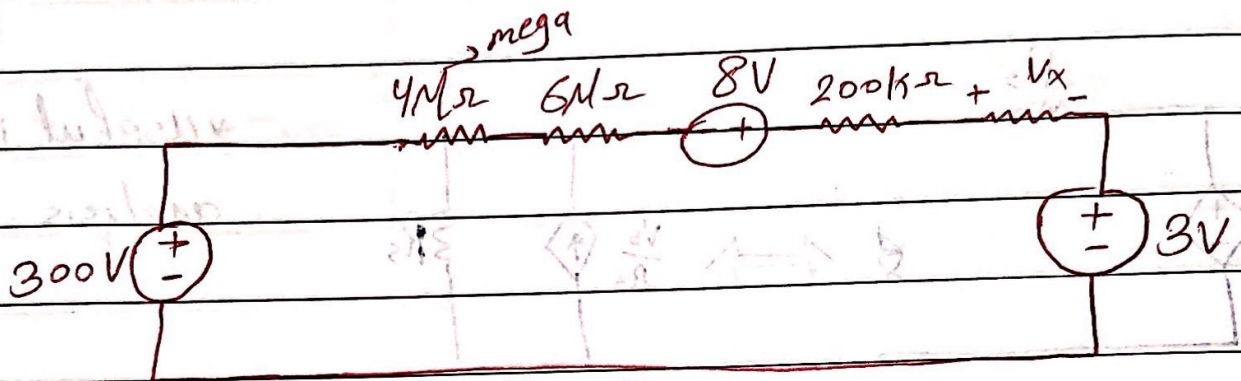
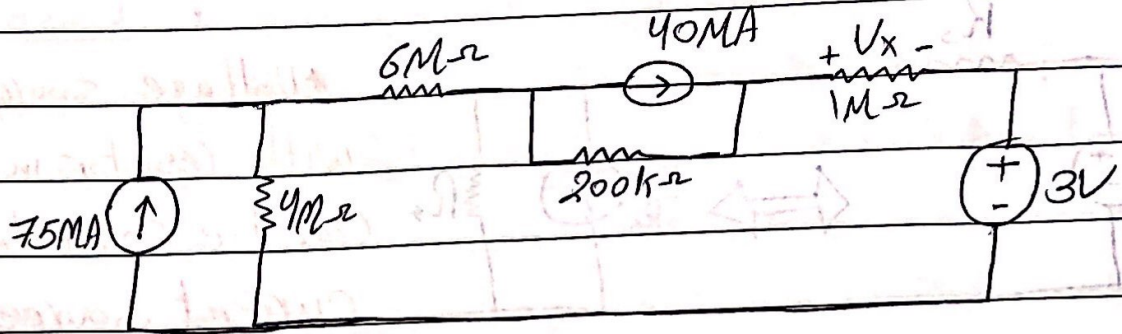
Example:- Simplify this circuit and find V_x .



$308 - 3 = 305$

$$V_x = \frac{305 \times 1}{10.2 + 1} = 27.23 \text{ V.}$$

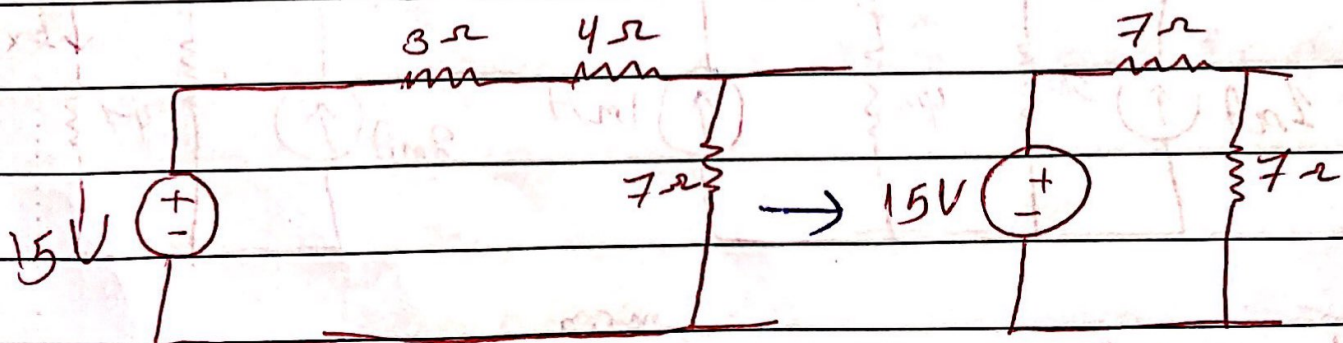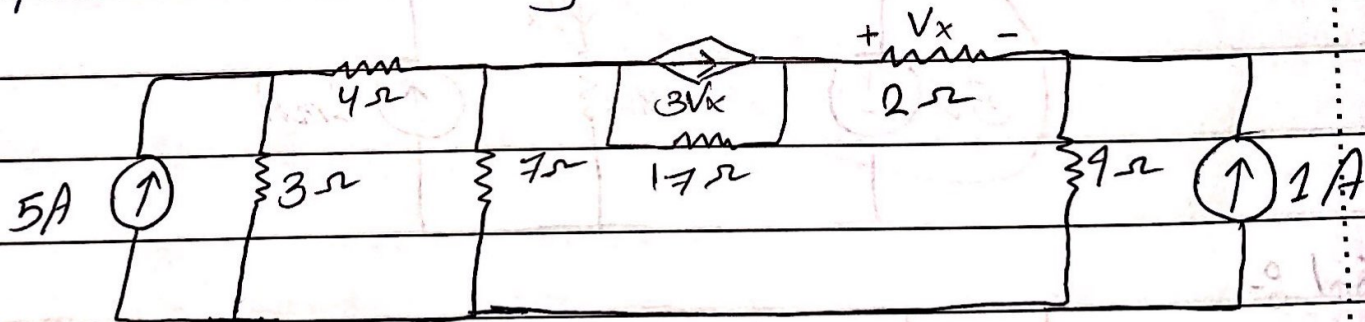Example:- Find I using source transformation





subject

Date

Date



No.

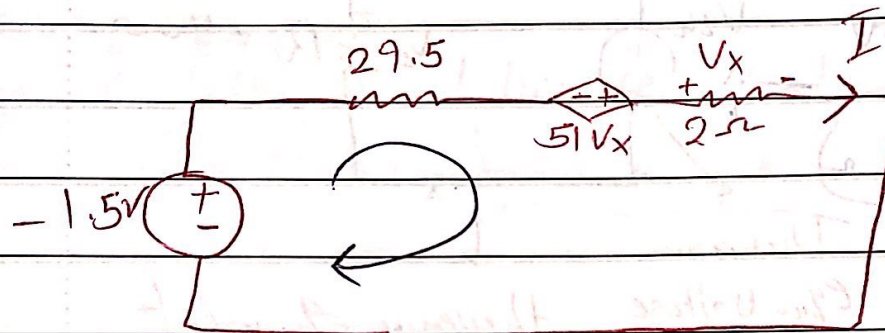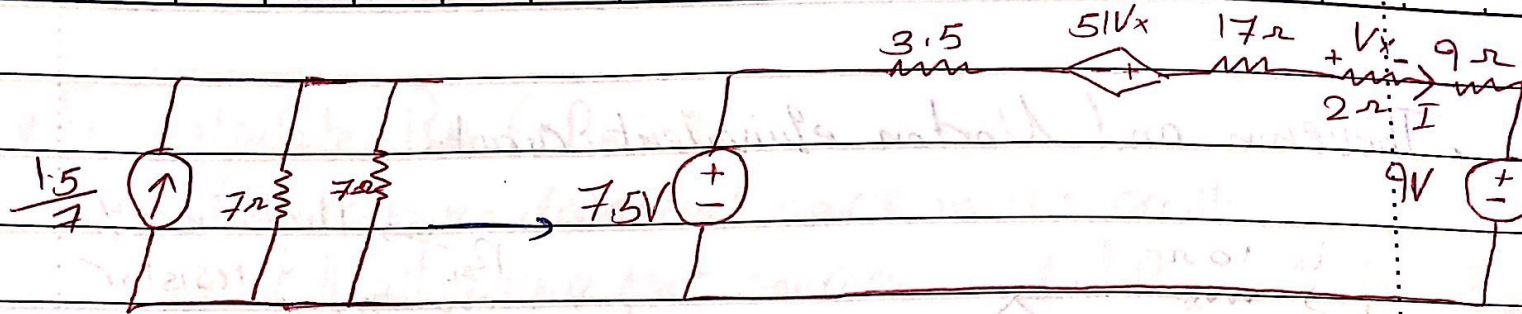

$$KVL = 1.5 + 29.5I - 5V_x + 2I = 0$$


$$I = 21.276 \text{ mA}$$

Thevenin and Norton equivalent circuits.

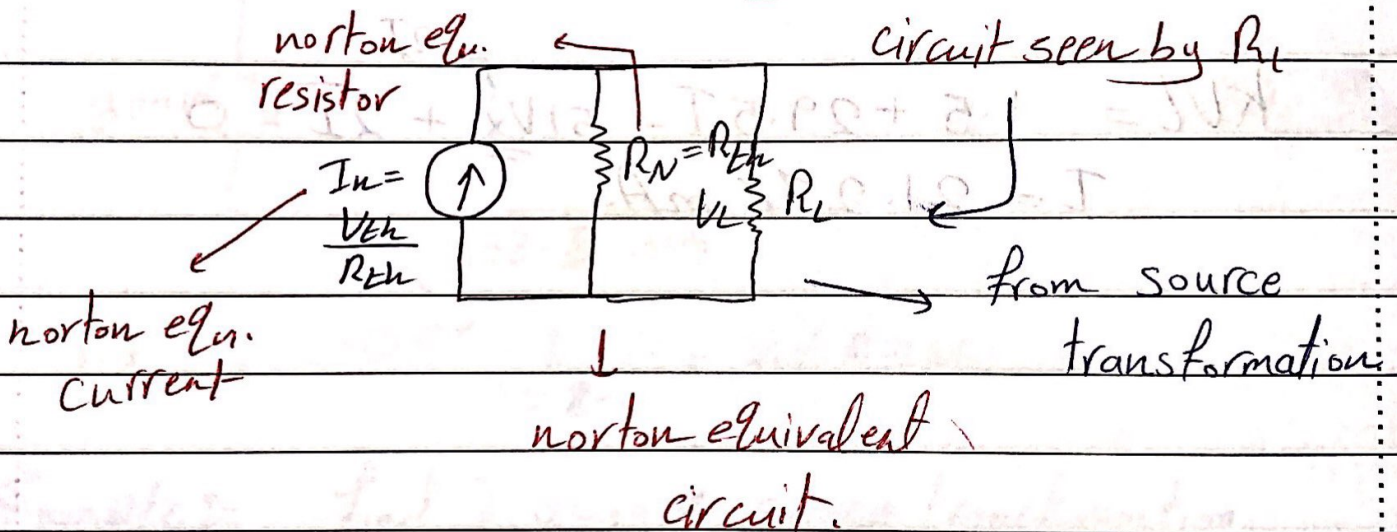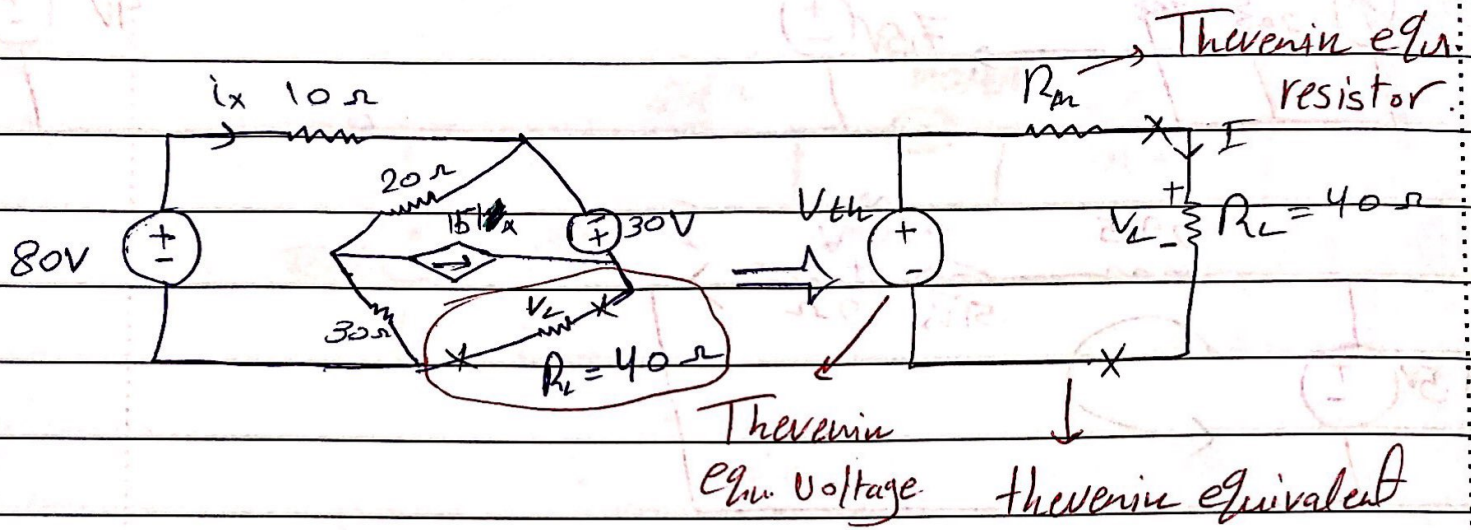

* To find V_{th} in any circuit $\rightarrow V_{th} = V_{o.c}$ (open circuit)

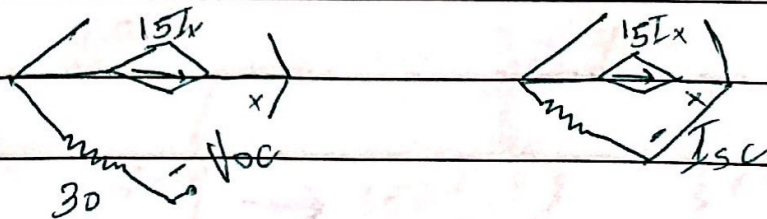* To find I_n in any circuit $\rightarrow I_n = I_{s.c}$ (short circuit)



* To calculate $R_{th} (= R_n)$:-

1. If there is no dependent source in the circuit


↳ Kill all independent sources → find R_{eq} ... $R_{eq} = R_{th}$

2. If the circuit has dependent and independent sources:


$$R_{th} = \frac{V_{oc} \rightarrow V_{th}}{I_{sc} \rightarrow I_N}$$

* R_{th} could be (-ve) cause it means the ratio $\frac{V_{th}}{I_N}$ - it's not a real value

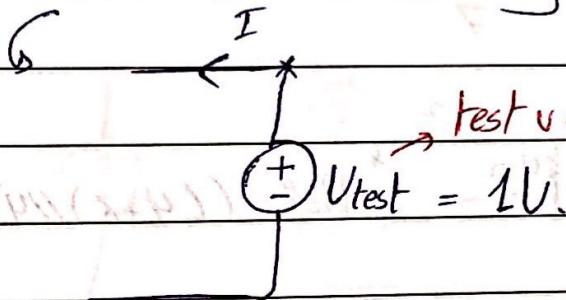3. If the circuit has only dependent source



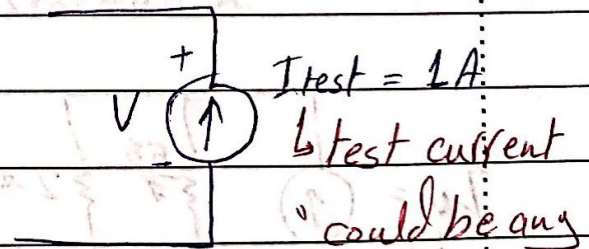
$$R_{th} = \frac{V_{test}}{I} = \frac{1}{I} \Omega$$



$$R_{th} = \frac{V}{I} = V \Omega \text{ value}$$


Note:- The method in type 3 can be used to solve type 1 and type 2.. but, we have to kill all independent sources.

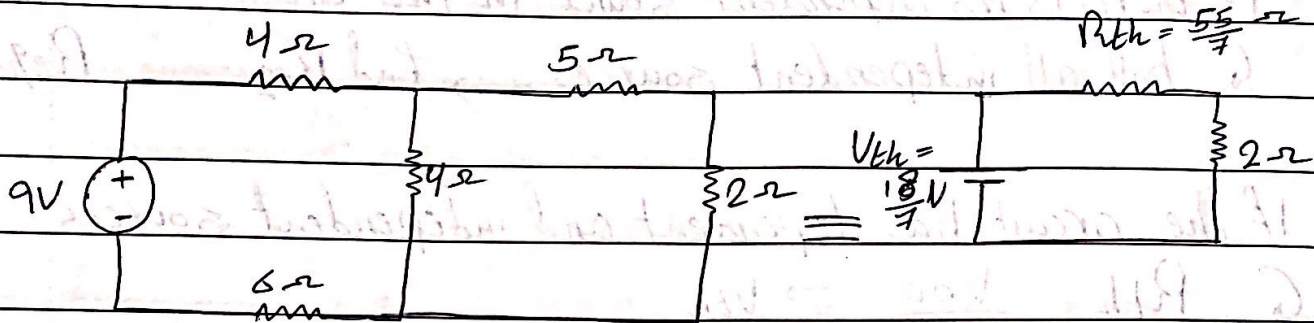Example :- Find Thevenin eq. circuit seen by $2\ \Omega$



$R_{th} = \frac{55}{7}\ \Omega$


$V_{th} = \frac{18}{7}\ V$

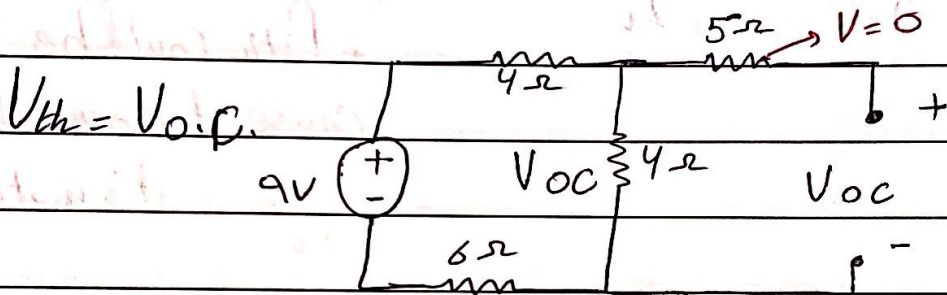


$V_{th} = V_{o.c.}$

$V_{th} = V_{oc} = \frac{9 \times 4}{4 + 4 + 6} = \frac{36}{14} = \frac{18}{7}\ V.$


R_{th} Type 1

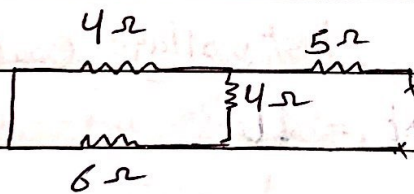

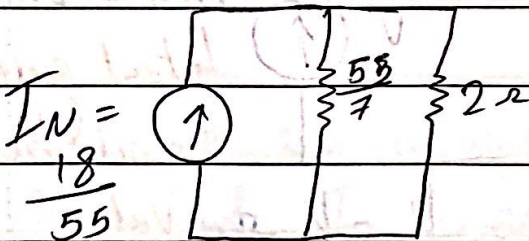$R_{th} = (4 + 6) // 4 + 5 = \frac{55}{7}$



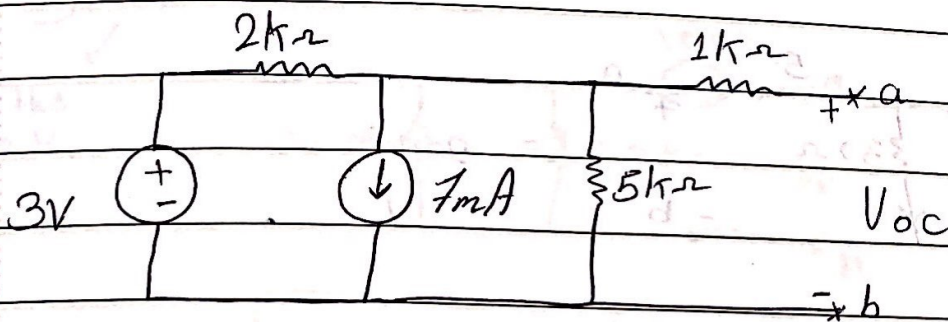Example:- Find thevenin eq. circuit seen between a & b




* We can use source transformation.

$$V_{th} = V_{oc} \rightarrow \frac{V_{oc} - 3}{2} + 7 + \frac{V_{oc}}{5} \rightarrow V_{oc} \left(\frac{1}{2} + \frac{1}{5} \right) = \frac{3}{2}$$


$$V_{oc} = \frac{-55}{V}$$

$$R_{th} = R_{eq} = 2 || 5 + 1 = \frac{17}{7} k\Omega$$

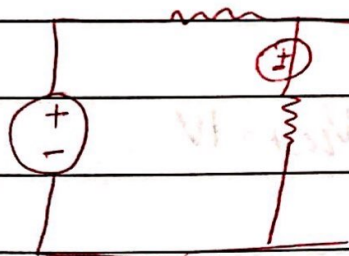

→ source transformation.

Example:-

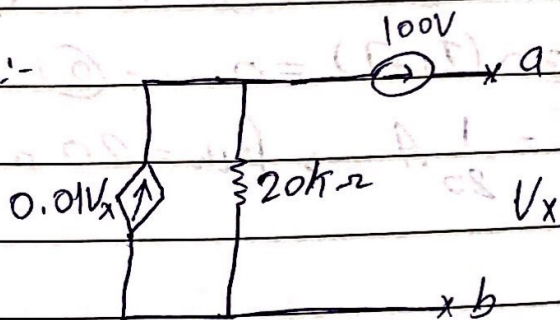

$$R_{th} = \frac{-502.5}{5} = -100.5$$


$$V_{th} = V_x$$

$$V_{20k\Omega} = 0.01V_x * 20 = 200V_x$$

$$V_x - V_{20k\Omega} - 100 = 0 \rightarrow V_x = 200V_x - 100 = 0$$

$$V_x = \frac{-100}{199} = -502.5 mV$$

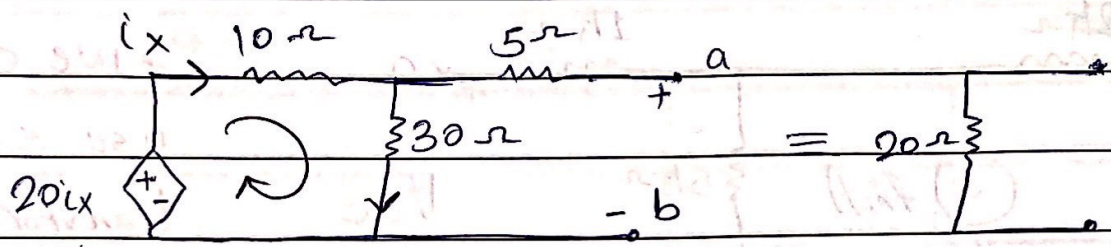Example :- Find V_{th} and R_{th} seen between a & b




KVL : $-20i_x + 10i_x + 30i_x \rightarrow i_x = 0A$

$\Rightarrow V_{oc} = 0V \rightarrow V_{th} = 0V \rightarrow I_x = 0A$

\Rightarrow Dead circuit !!

* I_{sc} in this circuit = zero

R_{th} .. type 3

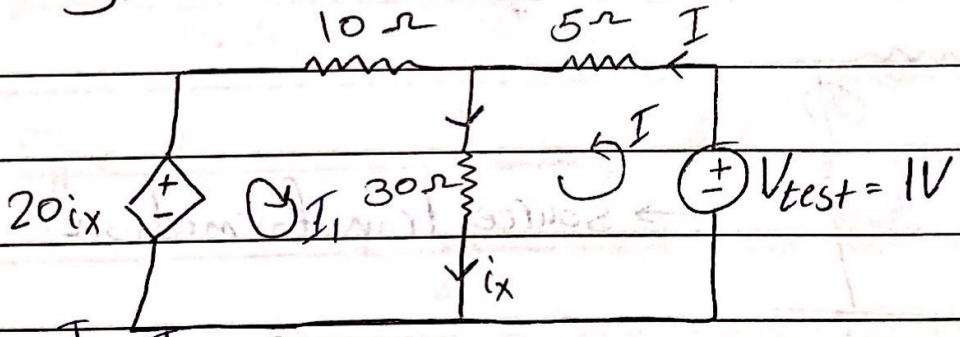



mesh 1 :- $-20i_x + 10I + 30(I_1 + I) = 0 \dots (1)$

mesh 2 :- $-1 + 5I + 30(I_1 + I) = 0 \dots (2)$

$I_1 = \frac{-1}{40} A, I = \frac{1}{20} A \rightarrow R_{th} = 20 \Omega$

Example:- Find V_{th} , R_{th} seen between a and b using type 3

kill the 100V

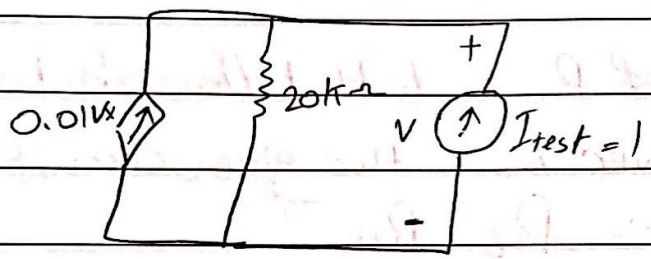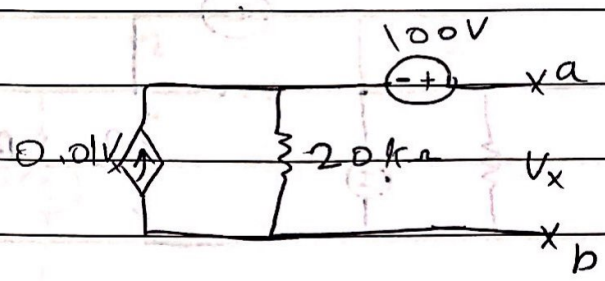


$$= 0.01V_x - 1 + \frac{V}{20} = 0$$

$$V = -100.5V$$

$$R_{th} = -100.5 \Omega$$


* Maximum Power transfer.

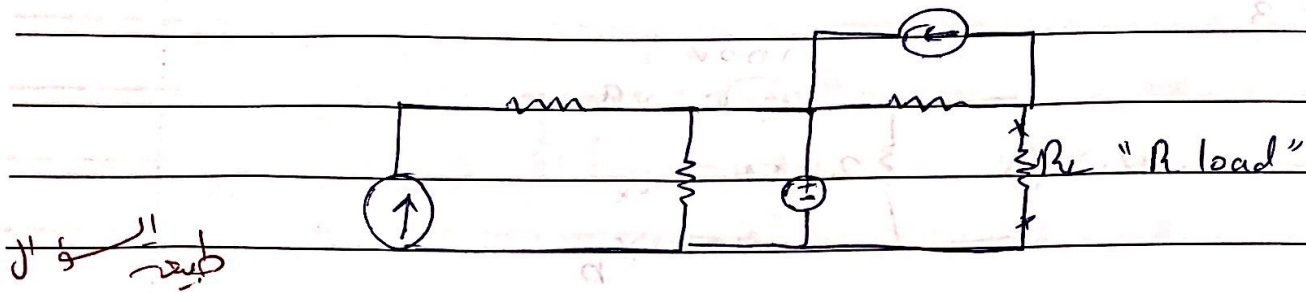

Q:- what is the value of R_L such that this resistor will absorb maximum power from the given circuit

answer:- $R_L = R_{th}$

why?

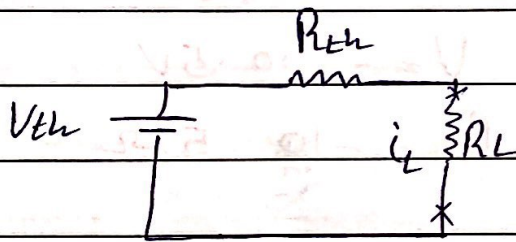

$$P_{R_L} = I_L^2 R_L = \left(\frac{V_{th}}{R_L + R_{th}} \right)^2 R_L$$


$$\frac{dP_{R_L}}{dR_L} = 0 \rightarrow \frac{V_{th}^2 (R_L + R_{th})^2 - 2(R_L + R_{th}) V_{th}^2 R_L}{(R_L + R_{th})^4}$$

$$\Rightarrow V_{th}^2 (R_L + R_{th})^2 = 2(R_L + R_{th}) V_{th}^2 R_L$$

$$R_L + R_{th} = 2R_L \therefore R_L = R_{th}$$

$$\boxed{P_{max} = \frac{V_{th}^2}{4R_{th}} \text{ W}} \quad \text{or} \quad \boxed{P_{max} = \frac{I_{sc}^2 R_{th}}{4} \text{ W}}$$

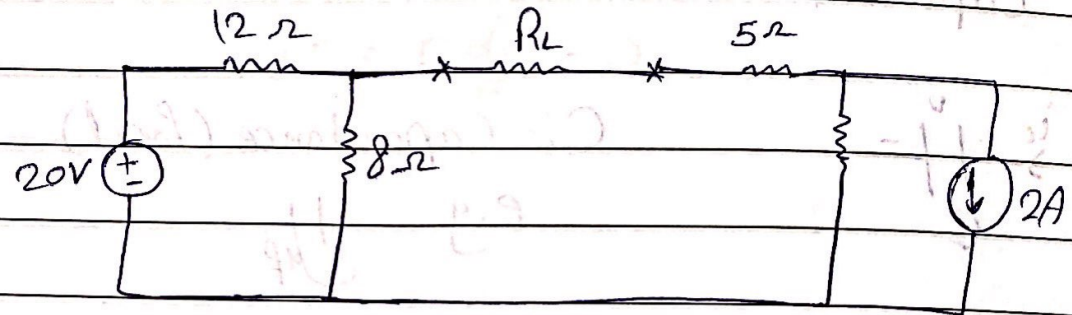Ex:- Find R_L that will absorb maximum power from the circuit.



Sol:- $R_L = R_{th} = R_{eq} = ((12/8) + 5) + 6 = 15.8 \Omega$

$P_{max} = \frac{V_{th}^2}{4R_{th}}$


$V_{th} = V_{oc} = V_a - V_b$

voltage division

$V_a = 20 \times \frac{8}{12+5} = 11.54$

$20 \times \frac{8}{12+5} = (-12)$

$= 20V$

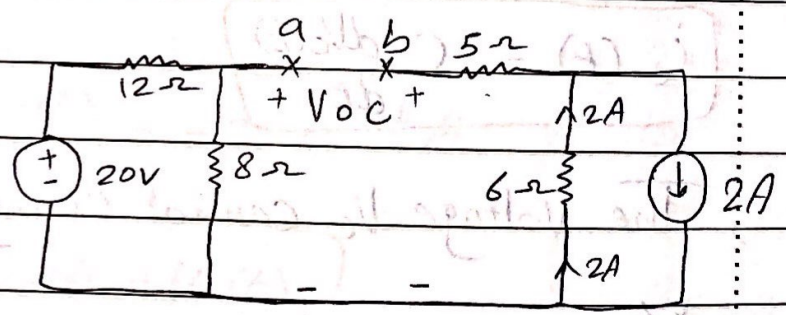

$P_{max} = \frac{(20)^2}{4 \times 15.8} = 6.329 W.$ / or source transformation

DC Circuit and analysis

Capacitors and Inductors

Capacitors

$$i_c + \frac{v}{e} =$$

C:- Capacitance (Farad)

e.g $\frac{1}{3 \mu F}$

→ Linear element (I vs Vc linear)

Micro = 10^{-6}

→ Passive element [P generated < 0]

Nano = 10^{-9}


over infinite time interval

pico = 10^{-12}

(Pav = 0)

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

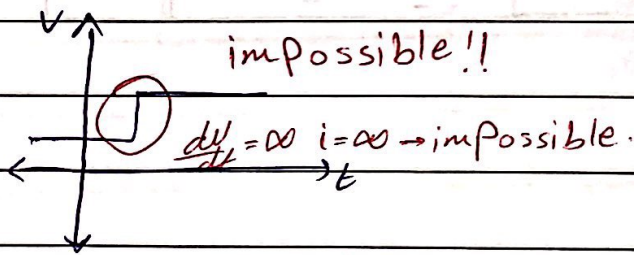→ The voltage Vc cannot change in zero time (suddenly)




→ The capacitor in DC circuits can be replaced by open circuit

↳ Because $\frac{dv_c}{dt} = 0$


so $i_c = 0$

⇒ C is open circuit.

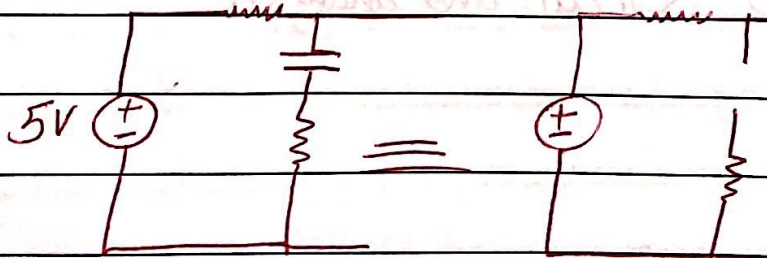

Ex: find $i_c(t)$, $C = 2F$

1) $V_c(t) = 5V$

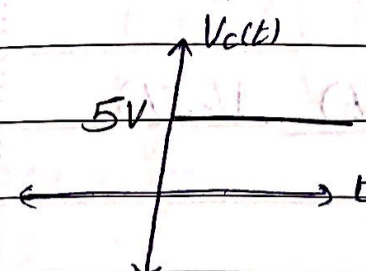

$$i_c = C \frac{dv}{dt} = 0$$

2) $V_c = 5 \sin(\pi t) V$

$$i_c = 2 [5\pi \cos \pi t]$$


$$= 10\pi \cos \pi t A$$

3) $V_c(t) = 2e^{-5t}$

$$i_c(t) = 2(-10e^{-5t}) = -20e^{-5t} A$$

$$V_c(t) = \frac{1}{C} \int_{t_0}^t i_c(t) dt + V_c(t_0)$$

Ex: find and draw $V_c(t)$, $C = 5mF$

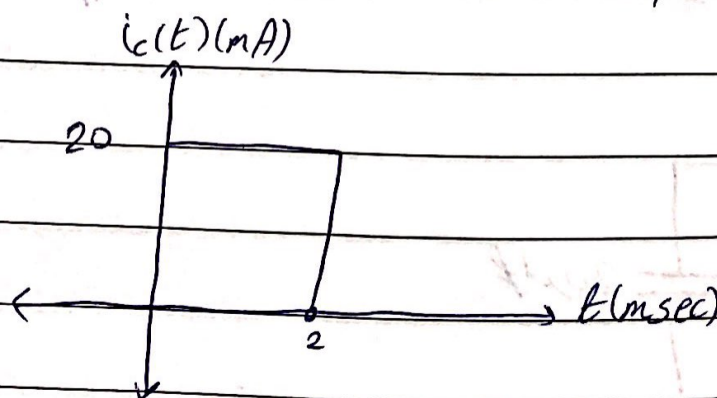

* For $-\infty < t < 0 msec$


$$V(t) = 0V$$

* For $0 < t < 2 msec$


$$V(t) = 4000t$$

* For $2 < t < \infty$

$$V_c(t) = 8V$$

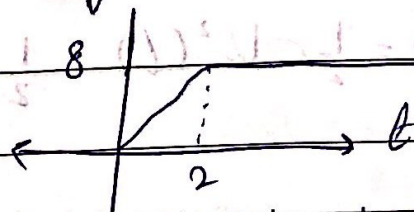

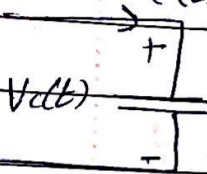* Stored energy in capacitor: $W_C(t)$ → Joule (J)



$$P(t) = i_c(t) V_c(t) = C \frac{dV_c(t)}{dt} \cdot V_c(t)$$

$$P(t) = \frac{dW_C(t)}{dt}$$

$$W_C(t) = \int_{t_0}^t P(\tau) d\tau = C \int_{t_0}^t V_c(\tau) \frac{dV_c(\tau)}{d\tau} d\tau$$


$$W_C(t) - W_C(t_0) = \frac{1}{2} C (V_c^2(t) - V_c^2(t_0))$$

$$W_C(t) = \frac{1}{2} C [V_c^2(t) - V_c^2(t_0)] + W_C(t_0)$$

if $W_C(t_0) = 0 \rightarrow V_c(t_0) = 0$ * initial value = 0

$$\therefore W_C(t) = \frac{1}{2} C V_c^2(t)$$

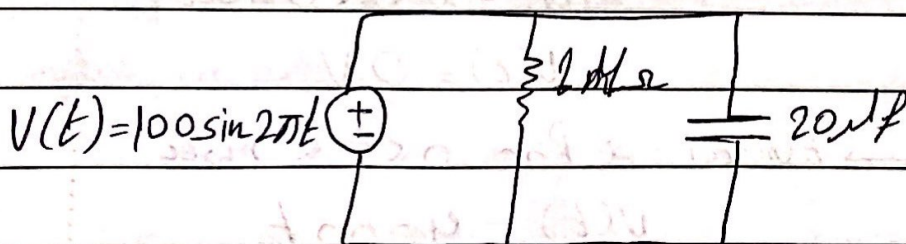Example:- find the maximum energy stored in the capacitor over the interval $0 < t < 0.5$ sec, also find the dissipated energy in the resistor




$$\text{Sol: } W_C(t) = \frac{1}{2} C V_c^2(t) = \frac{1}{2} \times 20 \times 10^{-6} \times 10^4 \sin^2(2\pi t) = 0.1 \sin^2(2\pi t)$$

Subject

Date

No.

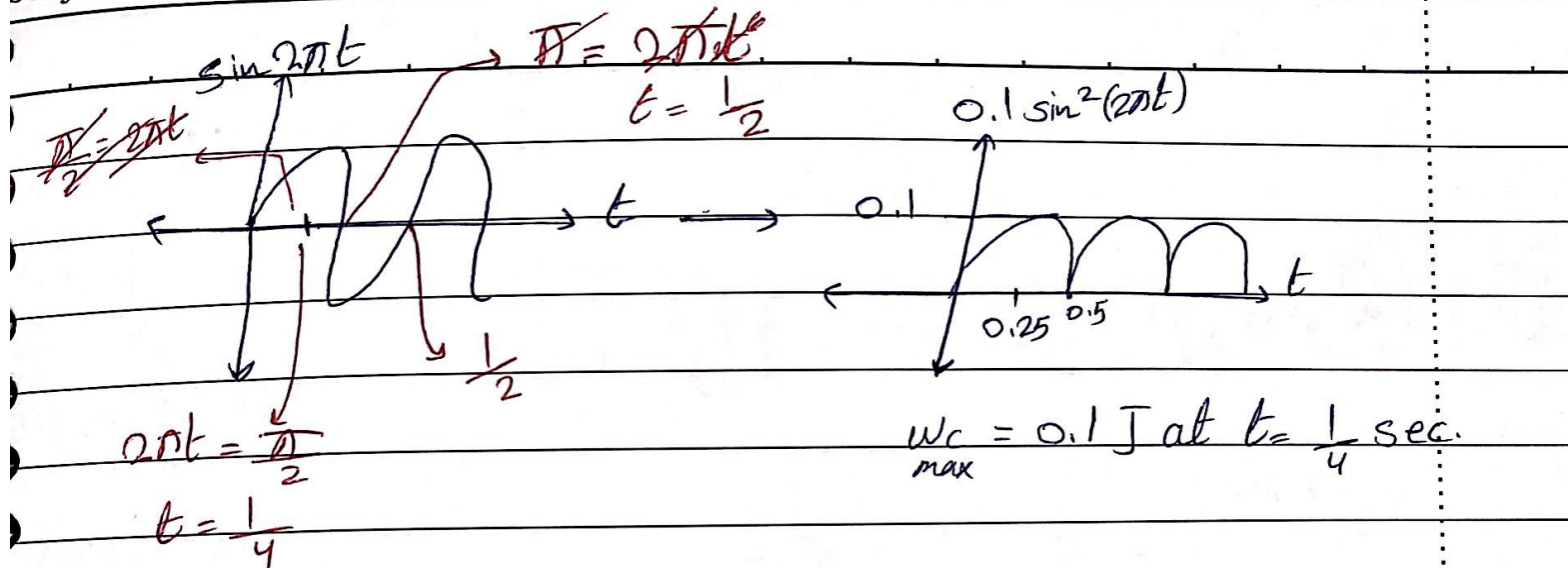


$$P_{\text{ave}} = (R(t) V_R(t)) = \frac{V_R^2(t)}{R} = \frac{(100)^2 \sin^2(2\pi t)}{1 \times 10^8} = 10^{-2} \sin^2(2\pi t)$$

$$W_{\text{ave}} = \int_0^{0.5} P(t) dt = \int_0^{0.5} 10^{-2} \sin^2(2\pi t) dt = \int_0^{0.5} 10^{-2} \times \frac{1}{2} (1 - \cos 4\pi t) dt = 2.5 \text{ mJ}$$


Inductor

→ Linear element

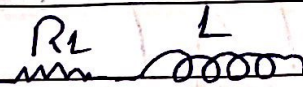

Practical

→ Passive element

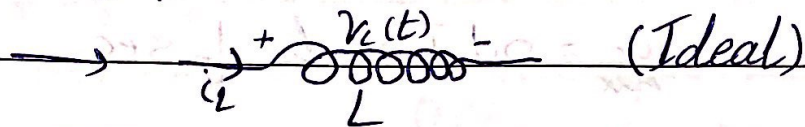


L :- Inductance
(H) Henry

$$* v_L(t) = L \frac{di_L(t)}{dt} \dots \textcircled{1}$$

$$* i_L(t) = \left(\int_{t_0}^t v_L(\tau) d\tau \right) \frac{1}{L} + i_L(t_0) \dots \textcircled{2}$$

→ From ①, the inductor in DC circuits can be replaced by short circuit, since $v_L(t) = L \frac{di_L(t)}{dt} \rightarrow DC = 0$

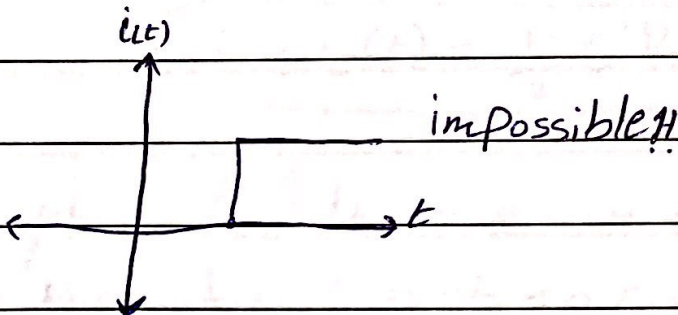
→ The current in the inductor cannot change in 0 time!




→ In AC inductor is a short circuit

→ In AC capacitor is an open circuit.



Example :- If $L = 3H$, find $V_L(t)$

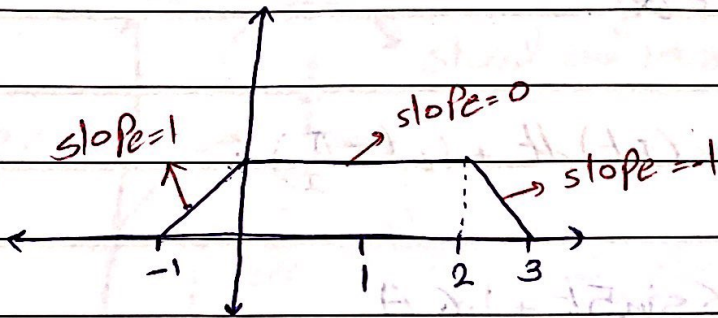
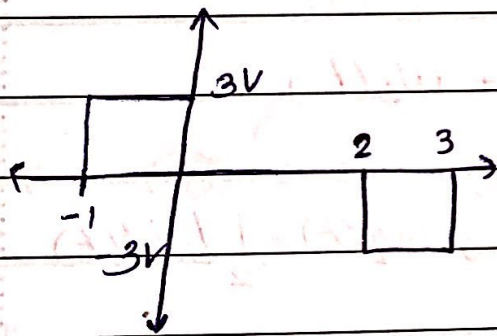
$$V_L(t) = L \times \text{slope} = \{3, -3\}$$



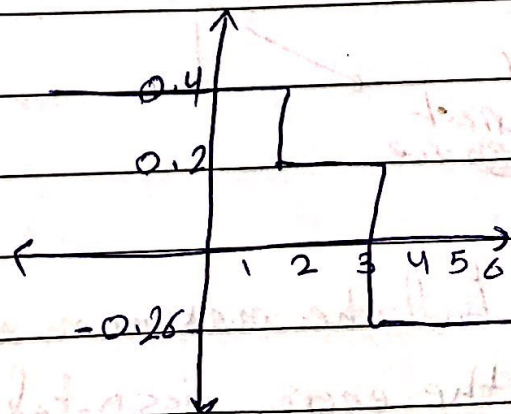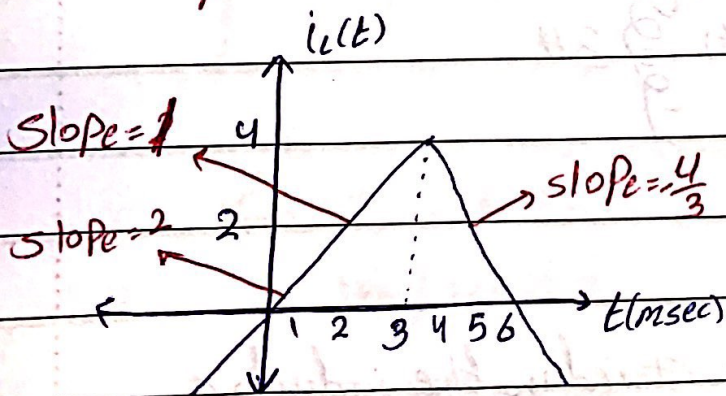Example :- $L = 200mH$... find $V_L(t)$ where $i_L(t)$:-



Example:- if $V_L(t) = 6 \cos(5t) \text{ V}$, $L = 2 \text{ H}$, $i_L(t = -\frac{\pi}{2}) = 1 \text{ A}$
 find $i_L(t)$ from $-\frac{\pi}{2} \leq t < \infty$.

$$i_L(t) = \frac{1}{L} \int_{-\frac{\pi}{2}}^t 6 \cos(5t) dt + i_L(-\frac{\pi}{2})$$


$$i_L(t) = 0.6 \sin 5t + 1.6 \text{ A}$$

* The stored energy in Inductor

$$W_L(t) = \frac{1}{2} L [i_L^2(t) - i_L^2(t_0)] + W_L(t_0)$$


$$\text{if } W_L(t_0) = 0 \rightarrow i_L(t_0) = 0 \rightarrow W_L(t) = \frac{1}{2} L i_L^2(t)$$

Example:-

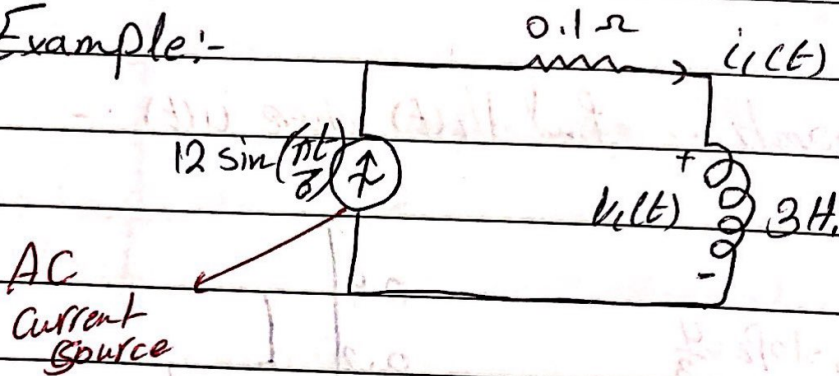



- Find the maximum energy stored in the inductor, and the energy dissipated in the resistor in the time during which the energy is being stored and then recovered from the inductor. given that $W_L(-\infty) = 0$.

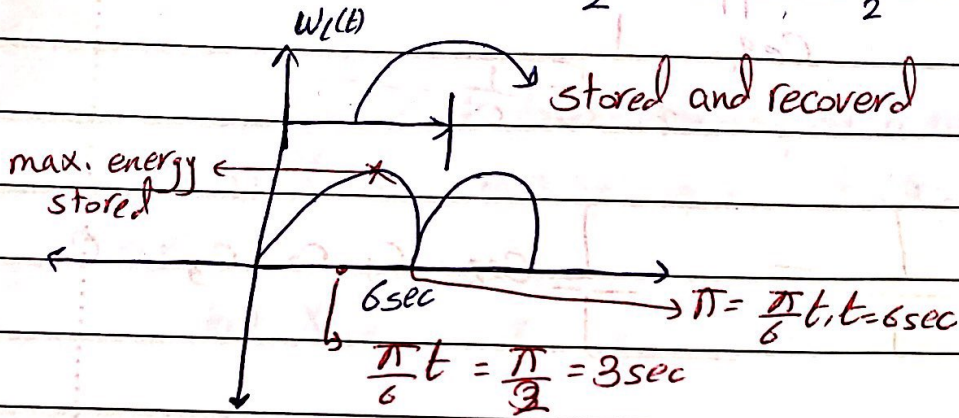Sol:- $W_L(t) = \frac{1}{2} L i_L^2(t) = \frac{1}{2} \times 3 \times (144 \sin^2(\frac{\pi}{6}t)) \text{ J}$





$W_L = 216 \text{ J}$

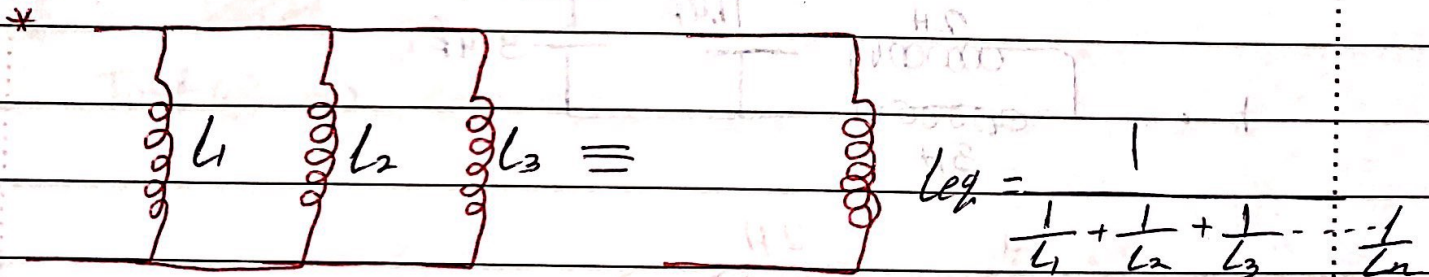
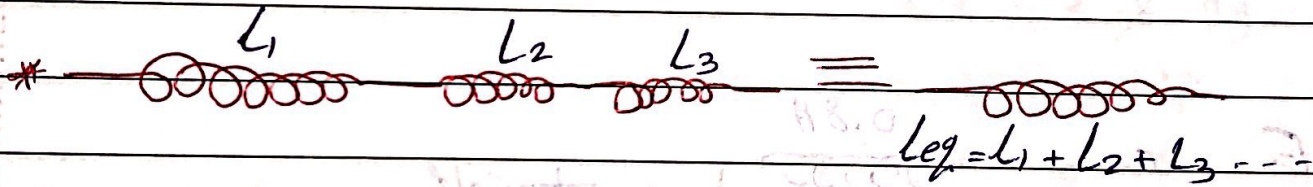
$W_R(t) = \int_0^6 P_R(t) dt = \int_0^6 0.1 (144 \sin^2(\frac{\pi}{6}t)) dt = 43.2 \text{ J}$



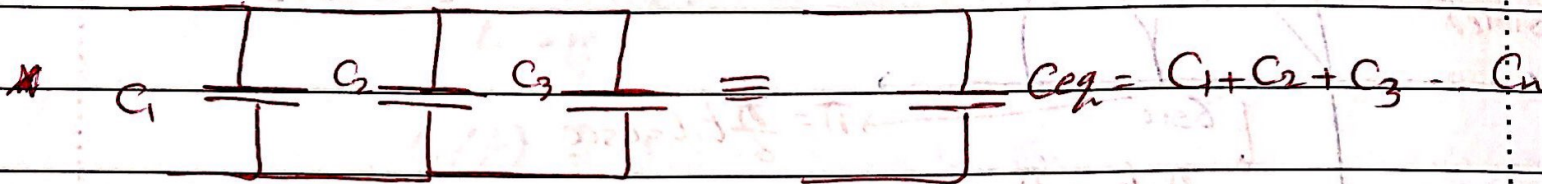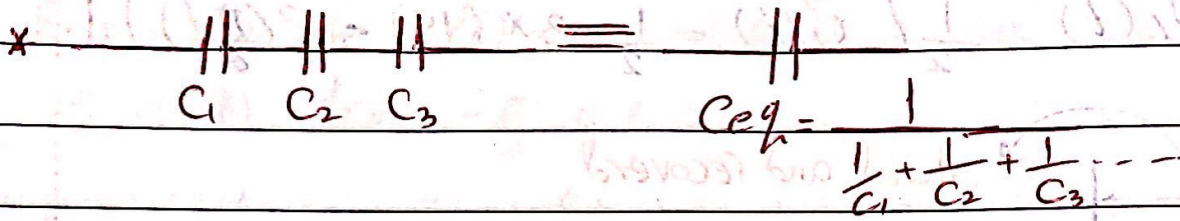For 2 inductors, L_1, L_2
in parallel $L_1 + L_2$



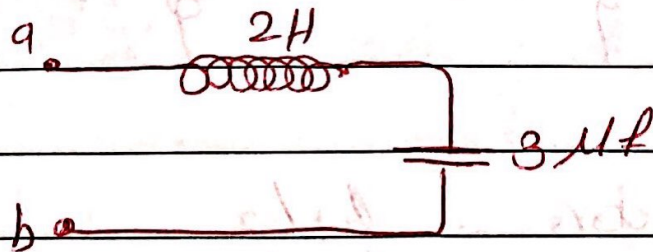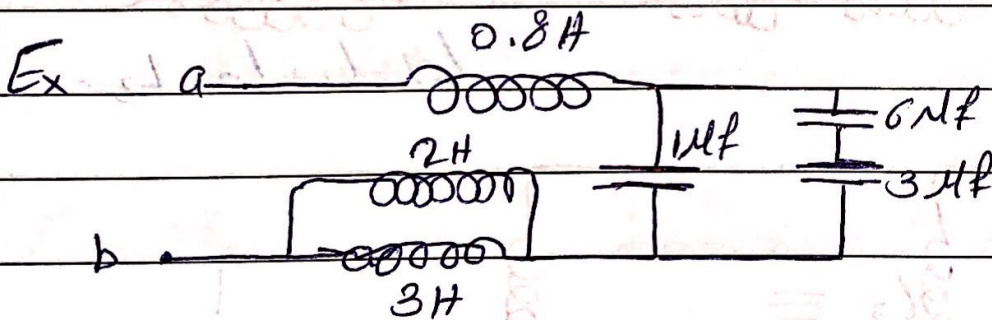For 2 capacitors in ~~parallel~~ series $C_{eq} = \frac{C_1 \times C_2}{C_1 + C_2}$



* Linearity in Capacitors and Inductors

To test the linearity of a relationship:- $y(x)$

a) $X_{new} = k_1 X \Rightarrow y_{new} = k_2 X_{new}$

or

b) $X_{new} = X_1 + X_2 \Rightarrow y_{new} = y_1 + y_2$

Ex:- $y = X + 3$

Test (a) $\Rightarrow X_{new} = CX \Rightarrow y_{new} = X_{new} + 3$ const.
 $CX + 3 \neq Ky$
 * not linear relationship

Ex:- ~~$y = X + 3$~~ $y = 5X$ const.

Test (a) $\Rightarrow X_{new} = CX \rightarrow y_{new} = 5X_{new}$
 $= 5(CX)$ const.
 $= C(5X)$ const.
 * linear relationship

Ex:- $V_L(t) = L \frac{di(t)}{dt}$

Test (a) $\Rightarrow i_{new} = K i(t) \Rightarrow V_{new} = L \frac{di_{new}}{dt}$

$= L \frac{d(Ki(t))}{dt}$

Linear


$= K \left(L \frac{di(t)}{dt} \right)$ ✓

Ex :- $y = 5x^2$

Best b) $\rightarrow 5(x_1^2 + x_2^2 + 2x_1x_2)$

* not linear.

\rightarrow In DC circuit \rightarrow  open circuit

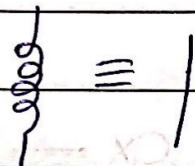 short circuit

\rightarrow In AC circuits

\hookrightarrow Direct approach:-

in solving AC circuits that have capacitors and inductors will result in integrodifferential equations

\rightarrow difficult to be solved.

Note:- All techniques studied before can be used to solve AC circuits that have capacitors and inductors.


"if the circuit has an AC source then it's AC circuit."

"if it has both AC and DC then it's AC circuit."

"if it hasn't any AC or DC sources then it's DC circuit."

Types of analysis for circuits

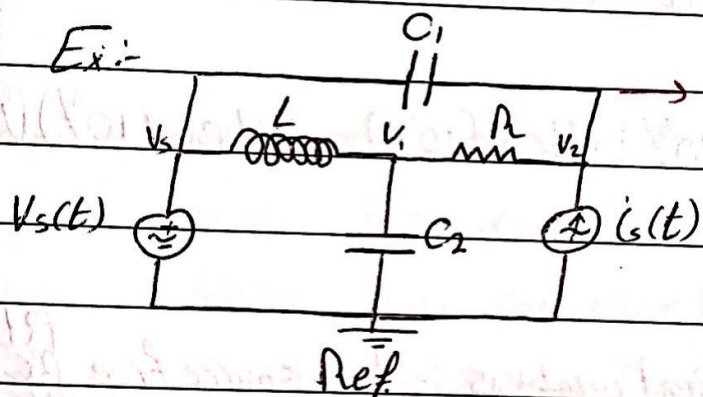- 1) DC analysis → for DC circuits "NO switching"
- 2) Transient analysis → for DC circuits with switching process. 3 steps solution
- 3) Steady state analysis → for AC circuits "NO switching"
 - ↳ direct approach → (integrodifferential equations) → hard to solve
 - ↳ indirect approach.




AC circuit → steady state analysis.
↳ direct approach.

node 1:
$$\frac{v_1 - v_2}{R} + C_2 \frac{dv_1(t)}{dt} + \frac{1}{L} \int_{t_0}^t (v_1 - v_s) dt + i_L(t_0) = 0 \dots \textcircled{1}$$

node 2:
$$-i_s(t) + \frac{v_2 - v_1}{R} + C_1 \frac{d(v_2(t) - v_s(t))}{dt} = 0 \dots \textcircled{2}$$

These are integrodifferential equations → difficult to be solved.

(direct approach) في كتابه الجاهل باله

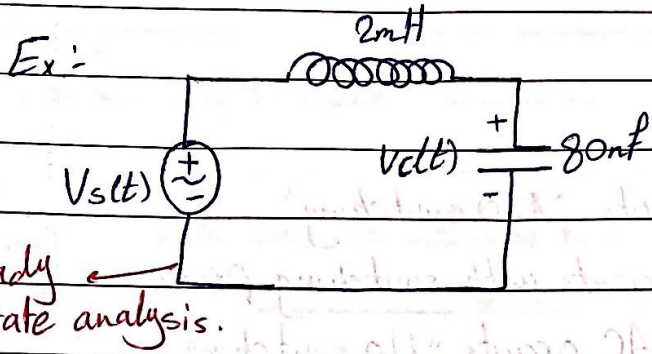

given $V_c(t) = 4 \cos 10^5 t$ V

Find $V_s(t)$

$$i_c(t) = C \frac{dV}{dt} = 80 \times 10^{-9} (-4 \times 10^5 \sin 10^5 t) = -32 \times 10^{-3} \sin(10^5 t) \text{ A}$$

$$\text{KVL} = -V_s(t) + L \frac{di(t)}{dt} + V_c(t) = 0$$

$$V_s(t) = -6.4 \cos(10^5 t) + 4 \cos(10^5 t) = -2.4 \cos(10^5 t) \text{ V}$$

* Transient Analysis

* Types of circuits in transient analysis :-

- 1- source free $\begin{matrix} RL \\ RC \\ RLC \end{matrix}$ circuits
- 2- Driven $\begin{matrix} RL \\ RC \\ RLC \end{matrix}$ circuits

* Solution \rightarrow 3 steps solution

step 1 :- at $t = \infty \rightarrow$ find they type of the circuit.

Find τ \rightarrow $\tau = R_{eq} C_{eq} \text{ sec} / \tau = \frac{L_{eq}}{R_{eq}} \text{ sec}$

time constant

\rightarrow Resistor and Capacitors

\rightarrow solution * source free $\begin{matrix} RC \\ RL \end{matrix} \rightarrow i(t) = i(0^+) e^{-\frac{t}{\tau}}$

no source after switching

\rightarrow R and inductors $V(t) = V(0^+) e^{-\frac{t}{\tau}}$

Final result.

$0^+ \rightarrow$ from step 3

natural response

* Driven $\left. \begin{matrix} RC \\ RL \end{matrix} \right\} i(t) = i(\infty) + \underbrace{(i(0^+) - i(\infty)) e^{-\frac{t}{\tau}}}_{\text{natural response}}$

forced response

$$V(t) = V(\infty) + (V(0^+) - V(\infty)) e^{-\frac{t}{\tau}}$$

→ step 2: at $t=0^-$ switching $\left. \begin{matrix} \text{الخطوة قبل} \\ \text{التبديل} \end{matrix} \right\}$

↳ Draw the circuit at $t=0^-$

↳ Find $i(0^-), V(0^-), V_C(0^-), i_L(0^-)$

capacitor $\left. \begin{matrix} \text{في حالة} \\ \text{التبديل} \end{matrix} \right\}$

inductor $\left. \begin{matrix} \text{في حالة} \\ \text{التبديل} \end{matrix} \right\}$

→ step 3: at $t=0^+ = 0$ switching $\left. \begin{matrix} \text{الخطوة بعد} \\ \text{التبديل} \end{matrix} \right\}$

↳ Draw the circuit at $t=0^+$

↳ Replace each capacitor by a voltage source of $V_C(0^-)$

↳ Replace each inductor by a current source of $i_L(0^-)$

Because $V_C(0^-) = V_C(0^+) = V_C(0)$

Because $i_L(0^-) = i_L(0^+) = i_L(0)$


↳ Find $i(0^+), V(0^+)$

Q₁ Find the maximum power absorbed by R_x

M_s

$$R_x = R_{th} = 20 \parallel 50 = 14.29 \Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

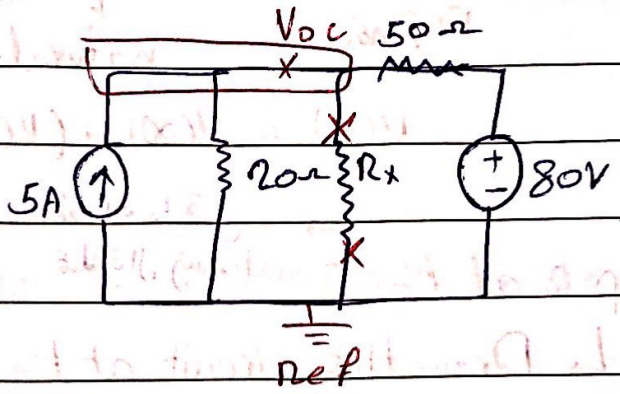


$$-5 + \frac{V_{oc}}{20} + \frac{V_{oc}}{50} - 80 = 0$$

$$V_{oc} = 94.29V = V_{th}$$

$$P_{max} = 155.54W$$

Q₂ Find R_{th} between points a and b
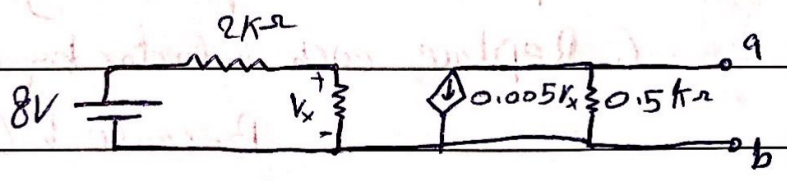
$$R_{th} = \frac{V_{oc}}{I_{sc}} = 0.5k\Omega$$



$$V_{oc} = -0.005V_x \times 0.5$$

$V_x = 4V \rightarrow$ voltage division.

$$V_{oc} = -10V$$

$$I_{sc} = -0.005V_x$$


$$= -20mA$$

find I_x

Q₃

$$I_x = 2 \times \frac{2}{2+3} \rightarrow \text{Current division}$$

$$= 0.8 \text{ mA}$$

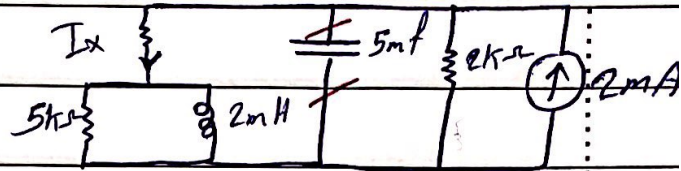

Q₄ find the stored energy in a capacitor at $t=2$ seconds given that the initial voltage on the capacitor is 0V, $C=5 \mu\text{F}$, and the applied voltage on the capacitor is $V_c(t) = 2 \cos(3\pi t) \text{ V}$.


$$W_c(t) = \frac{1}{2} C [V_c^2(t) - V_c^2(t_0)]$$

$$= \frac{1}{2} \times 5 \times (4 \cos^2(3\pi t)) \mu\text{J}$$

$$W_c(t) = 10 \mu\text{J}$$

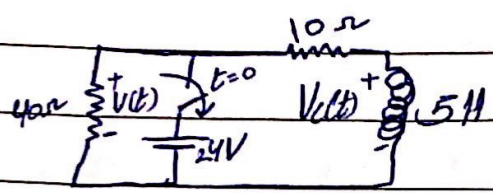
Example:- Find $V(t)$ and $V_L(t)$ for $-\infty < t < \infty$.. (14)
 then find $V(t=200 \text{ msec})$

* في حال طلب السؤال $V(t=200)$
 يجب ان نحل voltage او current
 في وقت معين بالوقت المطلوب



* Switching \rightarrow \therefore Transient analysis. \rightarrow 3 steps solution.

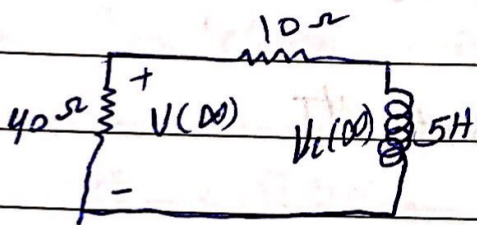- step 1: at $t = \infty \rightarrow$ switch (open)




1. Type :- source free RL
2. solution:- $V(t) = V(0) e^{-\frac{t}{\tau}}$
 $V_L(t) = V_L(0) e^{-\frac{t}{\tau}}$

τ هو RL في RL $\tau = \frac{L}{R}$

$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{5}{50} = 0.1 \text{ sec}$$

step 2:- at $t = 0^-$ switch (close)

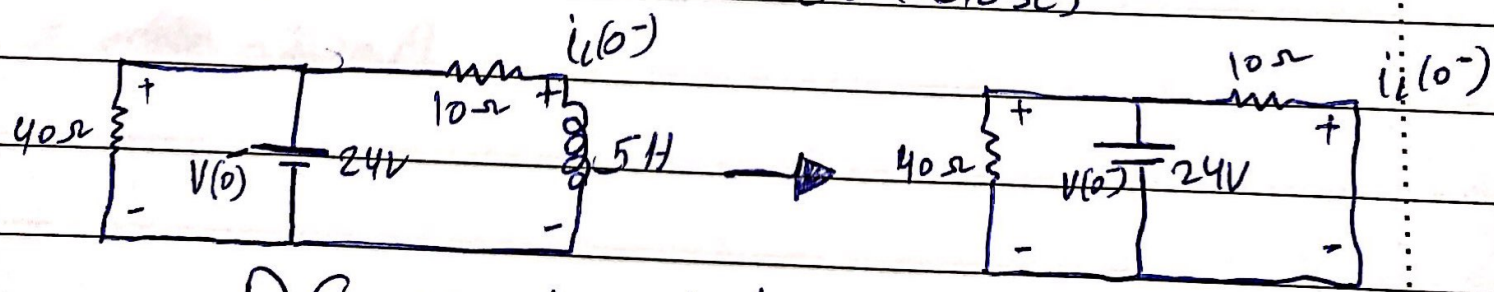


DC circuit \rightarrow $L = 1$
 short circuit.

$$V_L(0^-) = 0, V(0^-) = 24V$$

$$i_L(0^-) = \frac{24}{10} = 2.4A$$

- step 3 at $t=0^+$ switch (open)

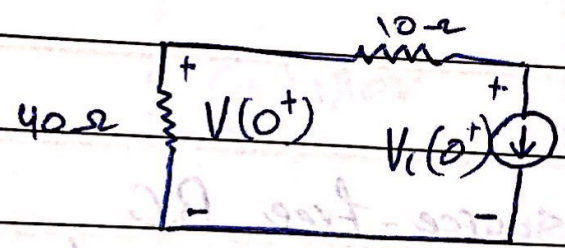

$$i_L(0^+) = i_L(0^-) = 2.4A$$

$$V(0^+) = -2.4 * 40 = -96V$$

$$V_L(0^+) \Rightarrow -(-96) + 10 * 2.4 + V_L(0^+) = 0$$

$$V_L(0^+) = -120V$$

$$V(t) = \begin{cases} 24, & t < 0 \\ -96e^{-\frac{t}{0.1}}, & t \geq 0 \end{cases}$$

Annotations: $V(0^-)$ points to 24; $V(0^+), V(0)$ points to -96.

$$V_L(t) = \begin{cases} 0, & t < 0 \\ -120e^{-\frac{t}{0.1}}, & t \geq 0 \end{cases}$$



$$i_L(t) = \begin{cases} 2.4, & t < 0 \\ 2.4e^{-\frac{t}{0.1}}, & t \geq 0 \end{cases}$$

Annotation: 'لو طلب مني احسبه' (if asked to calculate it) with an arrow pointing to the expression.

$V(t=200\text{msec}) \rightarrow V(t) \text{ at } t=0.2$


$$= -96e^{-\frac{200}{0.1}}$$

Example:-

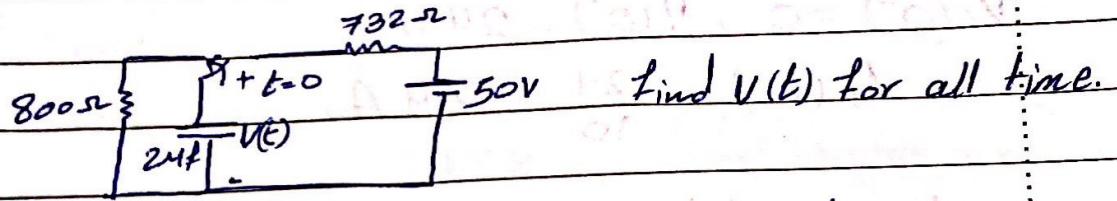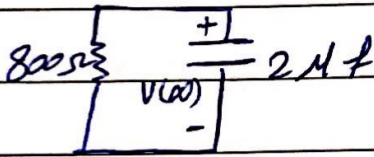switching \rightarrow transient analysis \rightarrow 3 steps solution.step 1 at $t = \infty$ Type \rightarrow source-free R.Csolution $\rightarrow V_c(t) = V_c(0) e^{-t/\tau}$ * $V_c(0^+) = V_c(0^-) = V_c(0)$ in capacitor

* so we don't have to use step 3.


$$\tau = RC = 800 \times 2 \times 10^{-6} = 1.6 \text{ msec.}$$

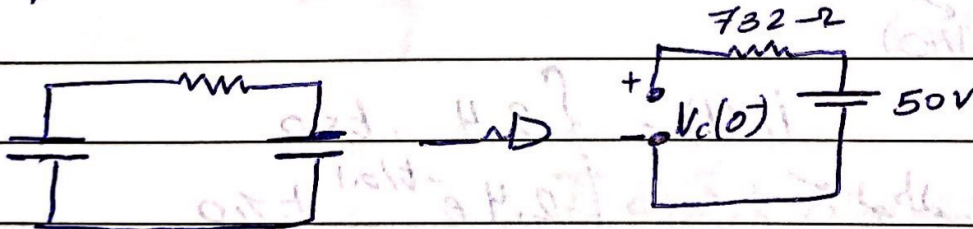step 2 at $t = 0^-$ DC circuit \rightarrow capacitor (open circuit)

$$\therefore V_c(0^-) = 50 \text{ V.}$$

$$\therefore V_c(t) = \begin{cases} 50 \text{ V} & t < 0 \\ 50 e^{-\frac{t}{1.6 \times 10^{-6}}} & t \geq 0 \end{cases}$$

Example:- find $i_1(t)$ and $i_2(t)$

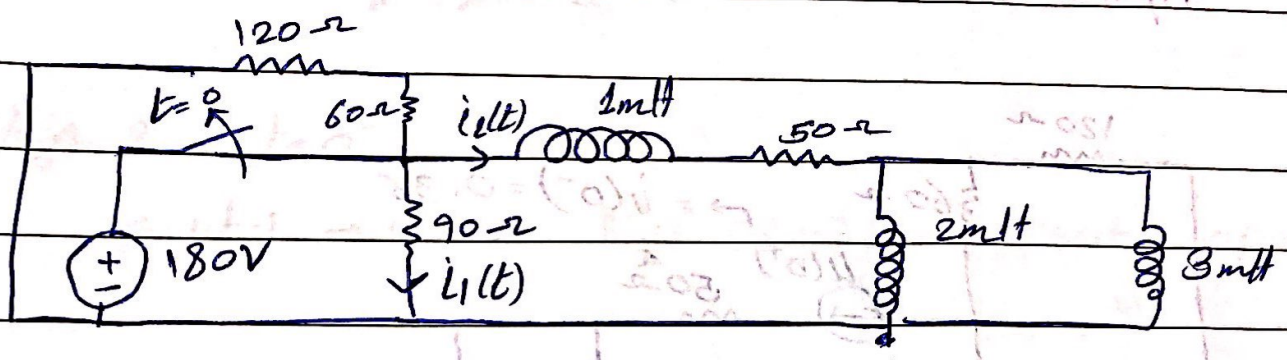

switch \rightarrow 3 steps solution

step 1 : $t = \infty$ type \rightarrow source free RL circuit

switch (open) - solution: $i_1(t) = i_1(0) e^{-\frac{t}{\tau}}$


$i_2(t) = i_2(0) e^{-\frac{t}{\tau}}$

$i_L(0) = i_L(0^+) = i_L(0^-)$ for inductor.

$$\Rightarrow \tau = \frac{L_{eq}}{R_{eq}} = \frac{2.2\text{mH}}{50\Omega \parallel (60+120)} = 20\mu\text{sec.}$$

step 2: at $t = 0^-$

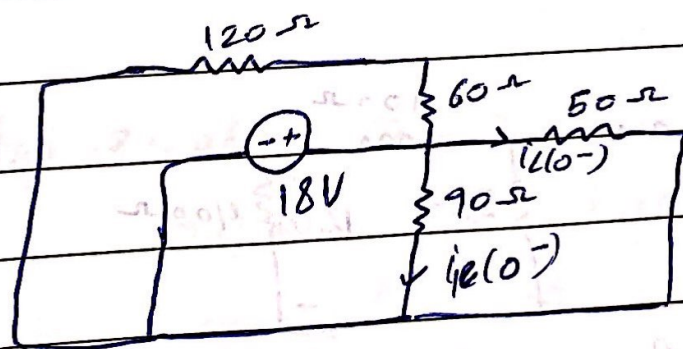switch (closed), inductors \rightarrow short circuits "DC"




$$i_1(0^-) = \frac{18}{90} = 0.2$$

$$i_2(0^-) = \frac{18}{50} = 0.36$$

step 3 :- $t = 0^+ = 0$

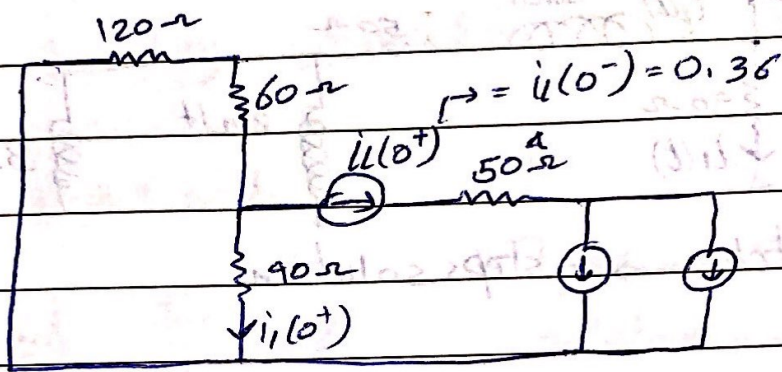replace every inductor \rightarrow current source $i_L(0^+)$




$$i_1(0^+) = \frac{-0.36 \times 180}{180 + 90} = -0.24 \text{ A} \quad \text{"current division"}$$

$$i_1(t) = \begin{cases} 0.2 & t < 0 \\ -0.24 e^{-\frac{t}{\tau}} & t \geq 0 \end{cases}$$

$$i_L(t) = \begin{cases} 0.36 & t < 0 \\ 0.36 e^{-\frac{t}{\tau}} & t \geq 0 \end{cases}$$

Ex: Find $V_c(t)$ and $V_o(t)$

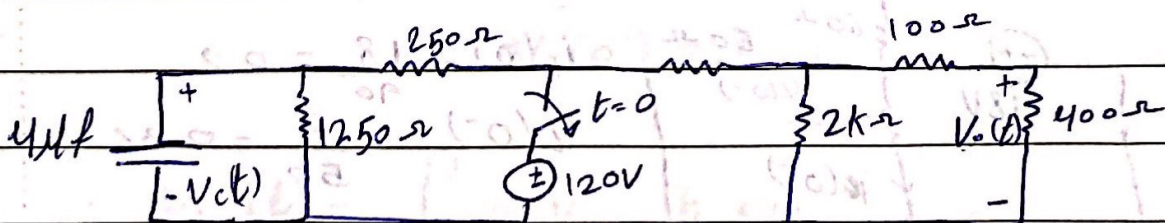

step 1: $t = \infty$ source free \rightarrow RC circuit

$$\text{solution :- } V_c(t) = V_c(0) e^{-\frac{t}{\tau}}, \quad t \geq 0$$


$$V_o(t) = V_o(0) e^{-\frac{t}{\tau}}, \quad t \geq 0$$

$$R_{eq} = ((100 + 400) \parallel 2k + 600) + 250 \parallel 1250 = 625 \Omega$$

$$\tau = R_{eq} C_{eq} = 625 \times 4 = 2.5 \text{ ms}$$

- Step 2 :- $t = 0^-$

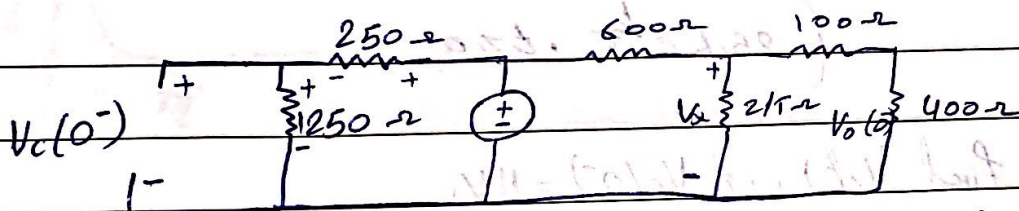switch \rightarrow closed (DC circuit) \rightarrow Capacitor (open circuit)



$$* R_{eq} = 400 \Omega$$


$$V_C(0^-) = 120 \times \frac{1250}{1250 + 250} = 100 \rightarrow \text{Voltage division}$$

$$V_x(0^-) = 120 \times \frac{400}{400 + 600} = 48V$$

$$V_0(0^-) = 48 \times \frac{400}{400 + 100} = 38.4$$

Step 3 :- at $t = 0^+ = 0$

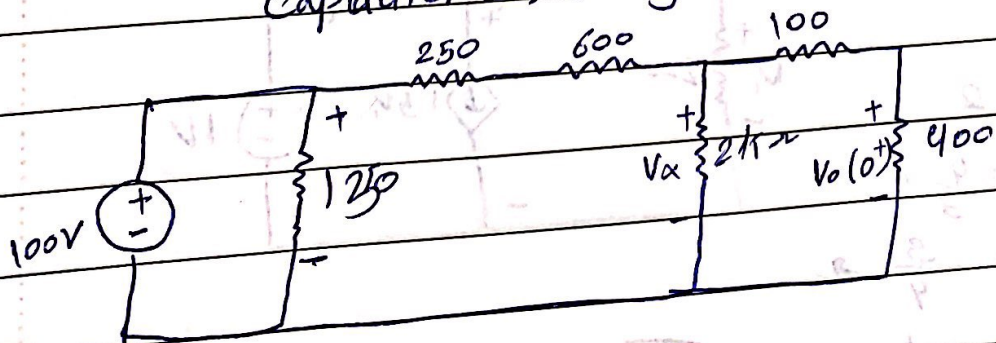capacitor \rightarrow voltage source ($V_C(0^-)$)




$$V_x(0^+) = \frac{100 \times 400}{400 + 250 + 600} = \frac{40000}{1250} = 32V$$

$$V_o(0^+) = \frac{32 \times 400}{400+100} = 25.6V$$

$$V_c(t) = \begin{cases} 100, & t < 0 \\ 100e^{-\frac{t}{\tau}}, & t \geq 0 \end{cases}$$

$$V_o(t) = \begin{cases} 38.4, & t < 0 \\ 25.6e^{-\frac{t}{\tau}}, & t \geq 0 \end{cases}$$

Ex: Find $V_c(t)$, if $V_c(0^+) = 11V$.

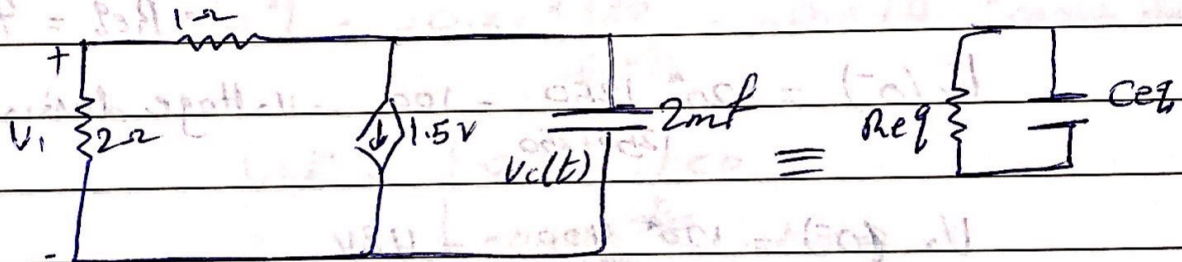


switching \rightarrow $t = \infty$ \rightarrow source free RC circuit

Step 1: $t = \infty$ type: source free RC circuit.

solution $V_c(t) = V_c(0^+) e^{-\frac{t}{\tau}}$

Rth seen by C \rightarrow $V_c(t) = 11 e^{-\frac{t}{\tau}}$

$$\tau = R_{eq} C_{eq}$$

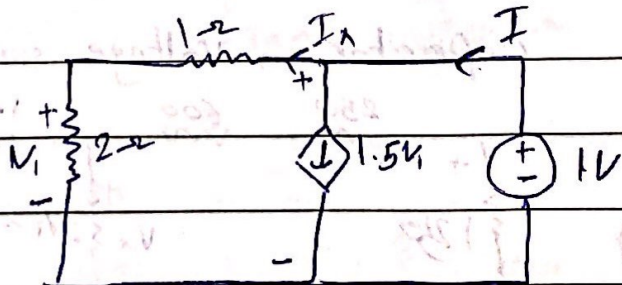

$$V_1 = 1 \times \frac{2}{3} = \frac{2}{3}$$

$$I = I_1 + 1.5V_1 = \frac{4}{3} A$$

$$R_{eq} = \frac{1}{I} = \frac{3}{4} \Omega$$


$$\tau = \frac{3}{4} \times 2 = 1.5 ms$$

$$V_c(t) = 11 e^{-\frac{t}{15 \times 10^{-3}}}$$

* Time constant (τ)

- for RL circuits $\tau = \frac{L}{R}$ -- why?

$$i(t) = I_0 e^{-\frac{R}{L}t}$$

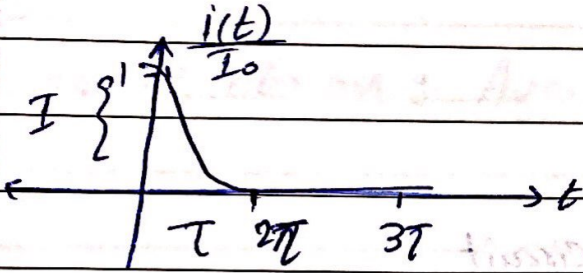

τ :- time required for the current to drop to zero if it continues to drop at its initial rate,

$$\text{slope } \left. \frac{d(i(t))}{dt} \right|_{t=0}$$

$$\bullet \frac{d(i(t)/I_0)}{dt} \Big|_{t=0} = \frac{-R}{L} e^{-\frac{R}{L}t} \Big|_{t=0} = \frac{-R}{L} = \text{initial rate of decaying}$$

$$\frac{-R}{L} = \frac{t-0}{0-\tau} \quad \therefore \tau = \frac{L}{R}$$

$$i(t=T) = I_0 e^{-\frac{T}{\tau}} = I_0 e^{-1} = 0.3679 I_0$$

$$1\tau \rightarrow 36\% I_0$$

$$2\tau \rightarrow 13.5\% I_0$$

$$3\tau \rightarrow 4.9\% I_0$$

$$4\tau \rightarrow 0.832\% I_0$$

$$5\tau \rightarrow 0.6738\% I_0 \approx 0$$

↳ life time of the circuit

في الساعات τ is lifetime of the circuit

$$RC \text{ circuit} \Rightarrow \tau = RC$$

في الساعات $\tau \uparrow = \text{more lifetime}$

$$\tau \uparrow \Rightarrow R \uparrow \text{ or } C \uparrow$$


$$P_{avg} = \frac{V_0^2}{R \uparrow}$$

more energy stored


16

* The unit step function

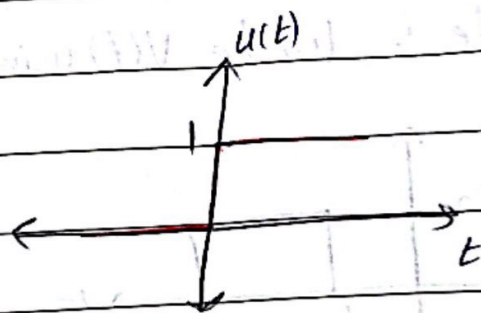
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \\ \text{undefined} & t = 0 \end{cases}$$




* $5u(t)$

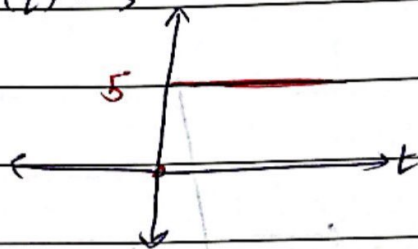

* $u(t-3)$

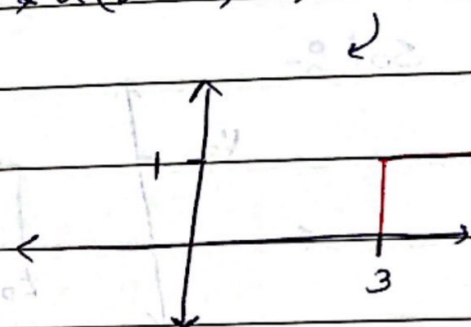

* $5u(4-t)$

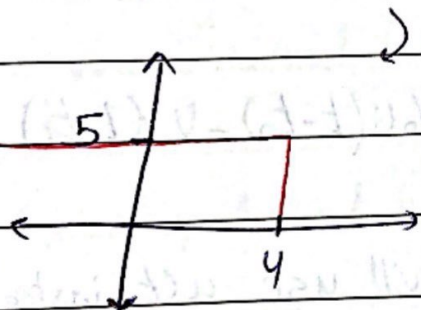

$$\begin{aligned} u(-ve) &= 0 \\ u(+ve) &= 1 \end{aligned}$$

* نعوض قيمة أقل من

٣ إذا كانت سالبة


فالتقيمة صفر وإذا

كانت موجبة فالتقيمة (١)


ولا يكون اتجاه الحركة باتجاه الذي

ظاهرت فيه القيمة (١)


* $-2u(-t)$

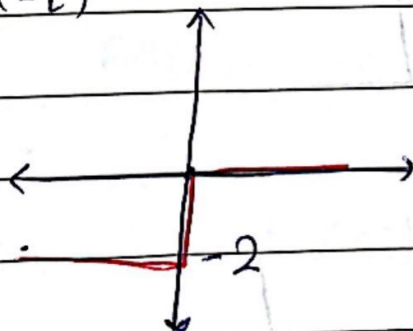

Example :- Write $V(t)$ using $u(t)$

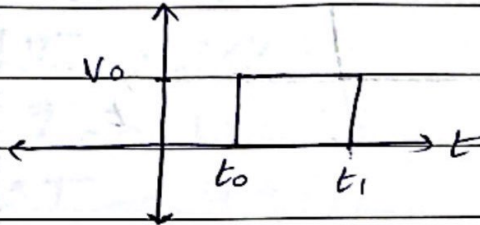

Sol :-

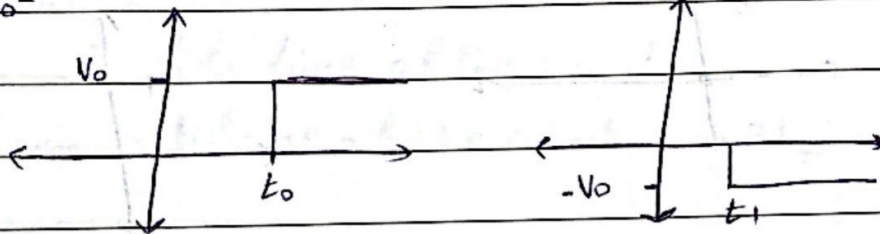


$V_0 u(t - t_0)$


$-V_0 u(t - t_1)$

$V(t) = V_0 u(t - t_0) - V_0 u(t - t_1)$


Ex :-

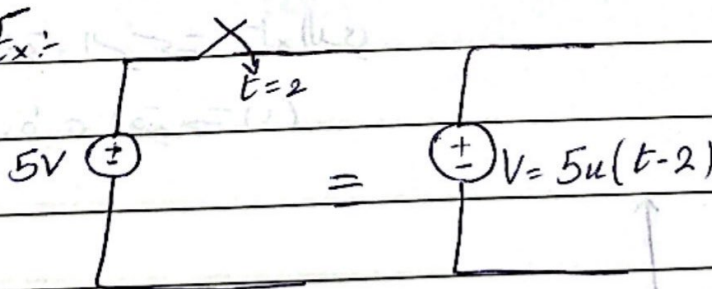

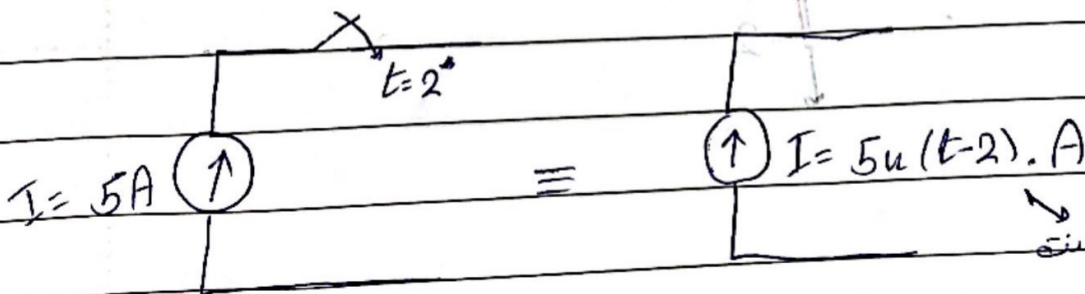
* we will use $u(t)$ instead of switch in some circuits.



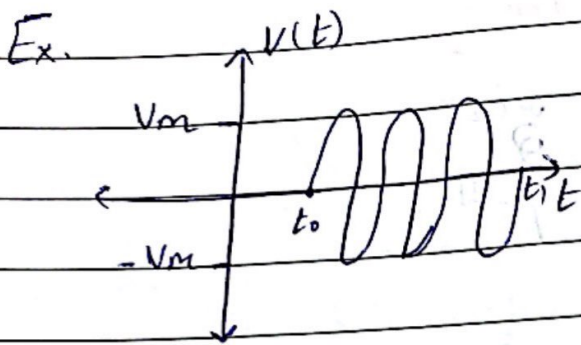Open circuit, Zero = Current
 (Note: The handwritten text 'الس 2' is also present near the current source.)


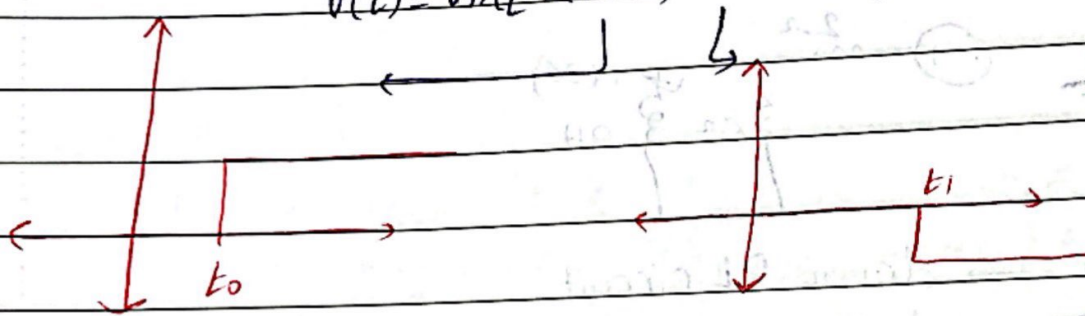
$$v(t) = V_m [u(t-t_0) - u(t-t_1)] \sin \omega t$$



* Driven RL and RC circuits "there is independent source when we apply step 1"

→ step 1: at $t = \infty$

type: \sim (C) \sim (L)

$$\text{solution: } i(t) = \underbrace{i(\infty)}_{\text{forced response}} + \underbrace{(i(0^+) - i(\infty)) e^{-\frac{t}{\tau}}}_{\text{natural response}}$$


→ step 2: $t = 0^-$

$$i(0^-), i(s), V_C(0^-)$$


→ step 3: $t = 0^+$

$$\frac{1}{s} \equiv \int_0^\infty e^{-st} dt \quad V_C(0^-) = V_C(0^+), \quad \frac{1}{s} \equiv \int_0^\infty e^{-st} dt \quad i_L(0^-) = i_L(0^+) = i_L(0^+)$$

* Example:- Find $i(t)$ → Switching

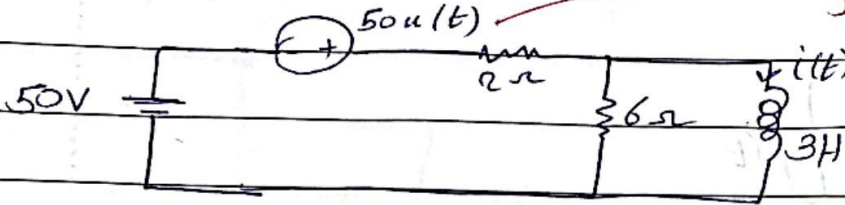

→ step 1 :- $t = \infty$

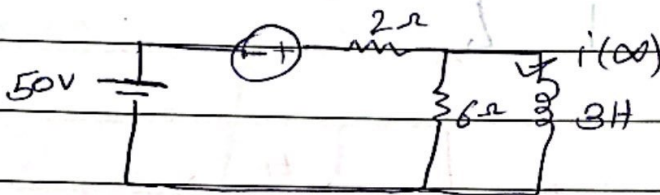

- type → driven RL circuit

$$- \tau = \frac{L e^{\%}}{R_{eq}} = \frac{3}{2/6} = 2 \text{ sec}$$

$$i(\infty) = \frac{100V}{2\Omega} = 50A \rightarrow \text{"inductor} = \text{short circuit"}$$


"current through $6\Omega = \text{zero}$ "

$$\text{Solution:- } i(t) = i(\infty) + (i(0) - i(\infty))e^{-\frac{t}{\tau}}, t \geq 0$$

$$= i_L(0^-) \leftarrow \text{inductor current}$$

$$= i_L(0^+)$$

→ step 2 at $t = (0^-)$

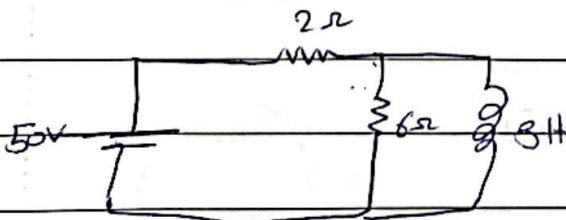


$$i_L(0^-) = \frac{50}{2} = 25A$$

$$i_L(0^+) = i_L(0^-)$$

$$i_L(t) = \begin{cases} 25A, & t < 0 \\ 50 + (25 - 50)e^{-\frac{t}{2}}, & t \geq 0 \end{cases}$$

(17)

Ex: Find $i(t)$ and $V_c(t)$

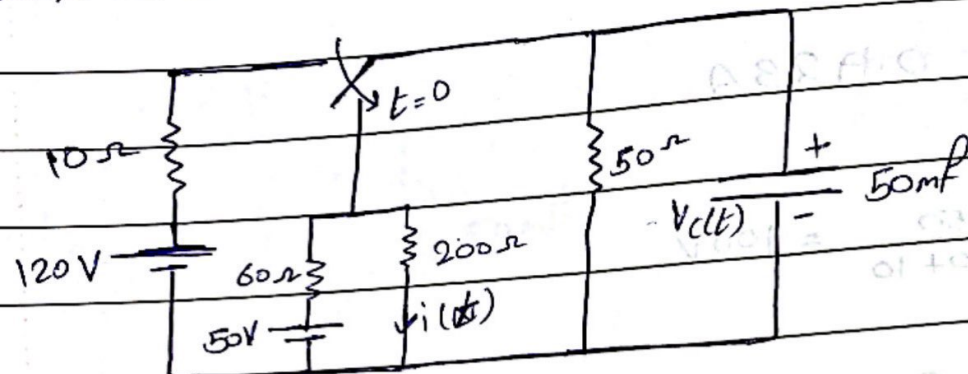


step 1 - $t = \infty$

type: driven RC circuit.

→ $\tau = R_{eq} C_{eq} = (60 \parallel 200 \parallel 50) \times 50mF$

$$\tau = 1.2 \text{ sec}$$

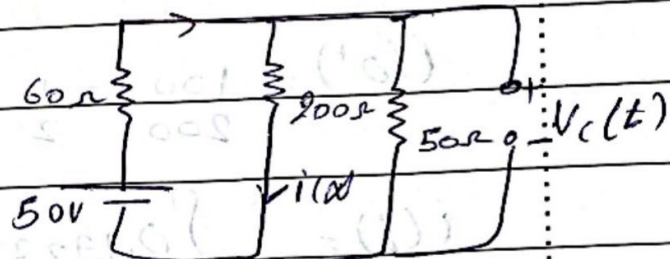
$$i(\infty) = \frac{50}{60} \times \frac{200}{\frac{1}{200} + \frac{1}{60} + \frac{1}{50}}$$



$$V_c(\infty) = 0.1 \times 200 = 20 \text{ V}$$

$$\rightarrow i(t) = 0.1 + (i(0) - 0.1) e^{-\frac{t}{1.2}}, t \geq 0$$
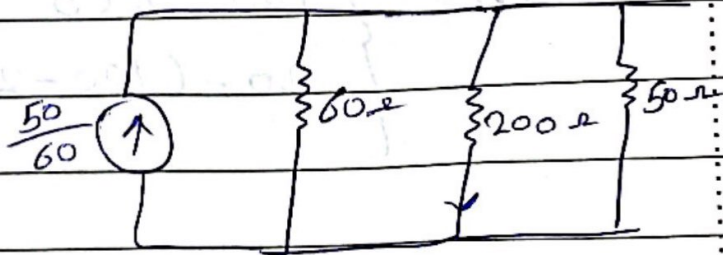
$$V_c(t) = 20 + (V_c(0) - 20) e^{-\frac{t}{1.2}}, t \geq 0$$




→ Step 2: $t = 0^-$

$$i(0^-) = \frac{50}{260} = 0.1923 \text{ A}$$

$$V_c(0^-) = 120 \times \frac{50}{50+10} = 100 \text{ V}$$

→ step 3 $t = 0^+ = 0$

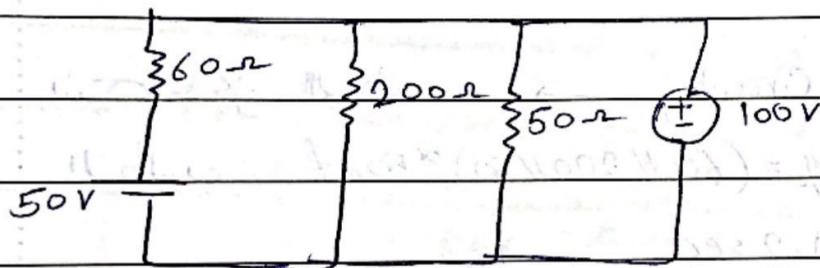

$$i(0^+) = \frac{100}{200} = \frac{1}{2} \text{ A}$$


$$i(t) = \begin{cases} 0.1923 \text{ A}, & t < 0 \\ 0.1 + (\frac{1}{2} - 0.1)e^{-\frac{t}{1.2}}, & t \geq 0 \end{cases}$$

$$V_c(t) = \begin{cases} 100, & t < 0 \\ 20 + (100 - 20)e^{-\frac{t}{1.2}}, & t \geq 0 \end{cases}$$

$$i(t=5) = 0.1 + 0.4 e^{-\frac{5}{1.2}}$$


$$i(t=0) = 0.1 + 0.4 = 0.5 \text{ A}$$

Example - find $i(t)$

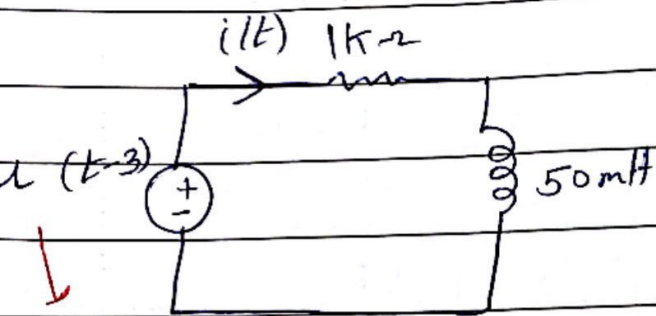

switching = $12u(t')$

→ step 1: $t' = \infty$

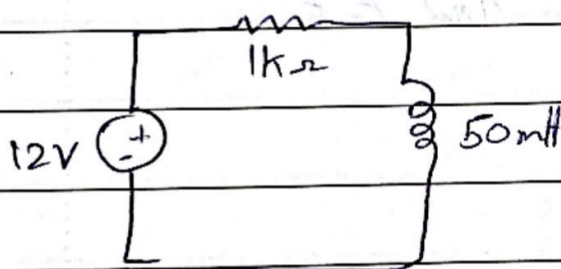

type: driven RL circuit.


$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{50 \times 10^{-3}}{1000} = 50 \mu\text{sec}$$

$$i(\infty) = \frac{12}{1000} = 12 \text{ mA}$$

$$i(t') = 12 + (i(0) - 12) e^{-\frac{t'}{50 \times 10^{-6}}}$$

→ step 2: at $t' = 0$



$$i(0^-) = i(0^+) = 0 \text{ A}$$

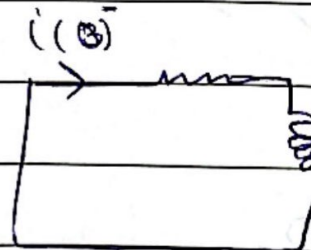


$$i(t) = \begin{cases} 0, & t < 0 \\ 12 - 12 e^{-\frac{t}{50 \times 10^{-6}}}, & t \geq 0 \end{cases}$$

$$i(t) = \begin{cases} 0, & t < 0 \\ 12 - 12e^{-\frac{(t-5)}{50 \times 10^{-6}}} & t > 0 \end{cases}$$

Example:-

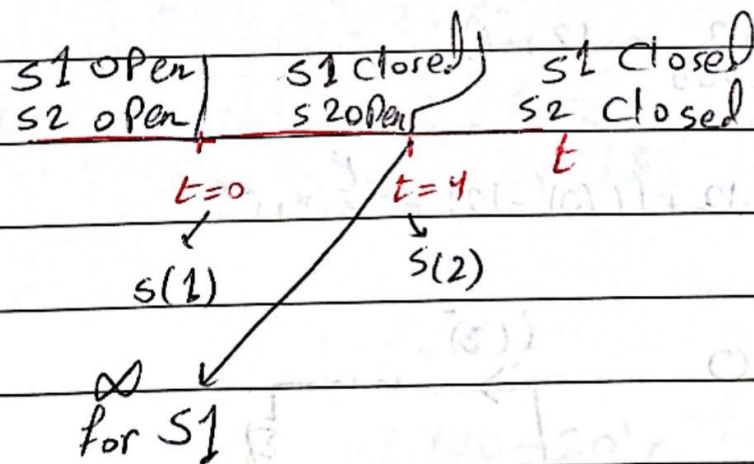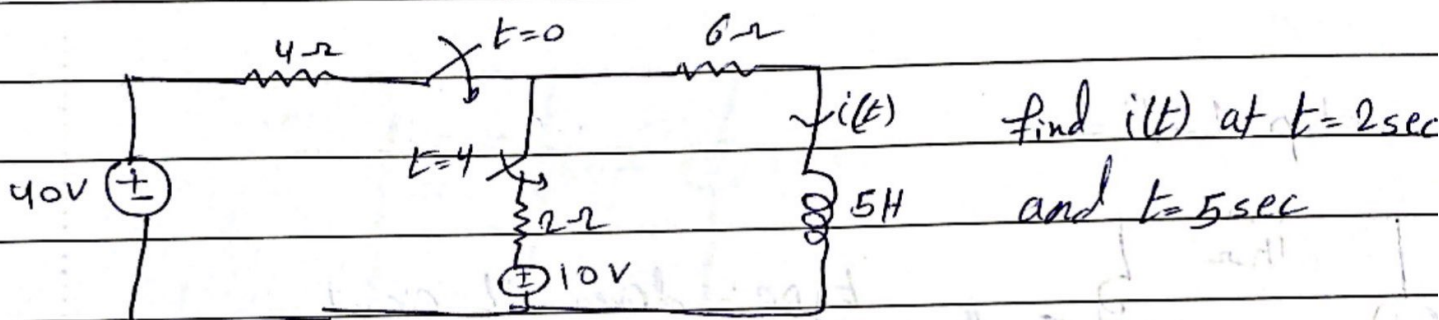

for s_1 at $t=0$

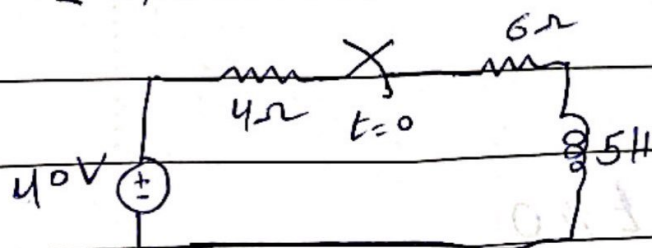

→ step 1 :- at $t = \infty$ ($t < 4 \text{ sec}$)

Type → Driven RL circuit.

Solution $i(t) = i(\infty) + (i(0) - i(\infty)) e^{-\frac{t}{T}}$


$$T = \frac{5}{10} = 0.5 \text{ sec}$$

$$i(\infty) = \frac{40}{10} = 4 \text{ A}$$

→ step 2 at $t = 0^-$

$$i(0^-) = 0 \text{ A}$$
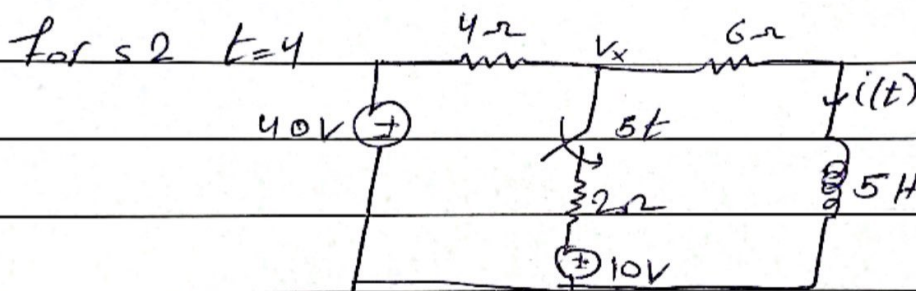
$$i(t) = \begin{cases} 0, & t < 0 \\ 4 + (0 - 4)e^{-\frac{t}{0.5}}, & 0 \leq t < 4 \end{cases}$$



→ step 1 $t = \infty$ ($t > 4$)

Type = Driven RL circuit

Solution → $i(t) = i(\infty) + (i(0) - i(\infty)) e^{-\frac{t}{T}}$

$$T = \frac{5}{2 + \frac{4 \cdot 6}{6}} = \frac{15}{25} \text{ sec}$$

nodal analysis → $i(\infty) \rightarrow \frac{V_x - 40}{4} + \frac{V_x - 10}{2} + \frac{V_x - 0}{6} = 0 \rightarrow V_x = 10 + 5$

$$V_x = \frac{108}{11} \text{ V}$$

$$i(\infty) = \frac{V_x}{6} = 2.72 \text{ A}$$

is switch open
 الفجوة مفتوحة
 switch is open
 الفجوة مفتوحة

Step 2 $t' = 0^-$

$$i(0^-) = \frac{40}{10} = 4A$$

$$i(t') = 2.72 + (4 - 2.72)e^{-\frac{t'}{0.5}}, t' \geq 0$$

$$i(t) = 2.72 + (4 - 2.72)e^{-\frac{t-4}{0.5}}, t-4 \geq 0 = t \geq 4$$

$$i(t) = \left\{ \begin{array}{l} 0A, t < 0 \\ 4 - 4e^{-\frac{t}{0.5}}, 0 \leq t < 4 \\ 2.72 + 1.273e^{-\frac{t-4}{0.5}}, t \geq 4 \end{array} \right\} \text{ s1}$$

* RLC circuit.

18

* Step 1 :- at $t = \infty$

Type :- ① source free RLC circuit

↳ Parallel

↳ series

② Driven RLC circuit

↳ Parallel

↳ series

$$\Rightarrow \text{Find } \omega_0 = \frac{1}{\sqrt{LC}} \text{ (resonant frequency) (rad/sec)}$$

Naper frequency ②
exponential damping coefficient $\rightarrow \alpha = \frac{1}{2RC}$ (in parallel) , $\frac{R}{2L}$ (in series)

$$(3) s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$(4) s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

\Rightarrow solution (for driven RLC circuit)

$$i(t) = i(\infty) + \text{solutions in source free.}$$

\Rightarrow solution (for source free)

* if $\alpha > \omega_0 \Rightarrow$ over damp response

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


* if $\alpha = \omega_0 \Rightarrow$ critical damp response.

$$i(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$$


* if $\alpha < \omega_0 \rightarrow$ underdamped response

$$i(t) = e^{-\alpha t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)]$$
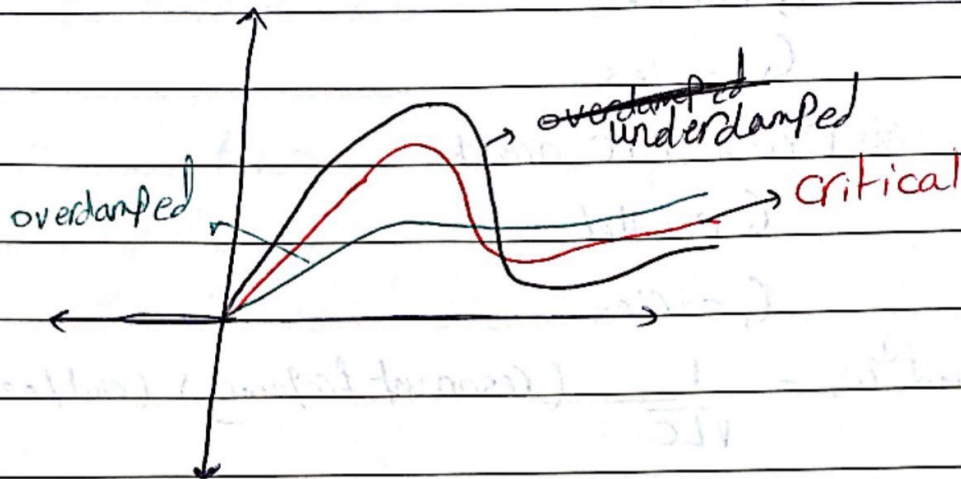
$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \text{ (natural resonant frequency)}$$




Example:- find $V_L(t)$ and $i_R(t)$

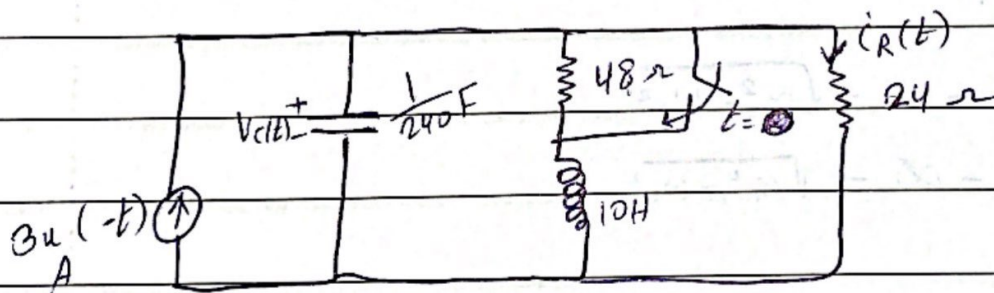

Step 1: $t = \infty$

Type:- source-free parallel RLC circuit

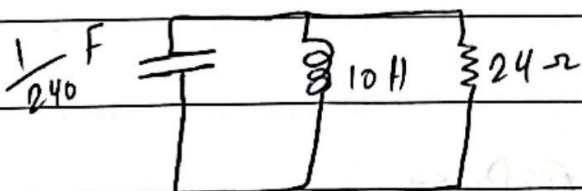

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 24 \times \frac{1}{240}} = 5 \text{ sec}^{-1} (\text{Hz})$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{24} \text{ rad/sec}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -4 \text{ sec}^{-1}$$


$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -6 \text{ sec}^{-1}$$

Because $\alpha > \omega_0 \Rightarrow$ overdamped

$$V_c(t) = A_1 e^{-4t} + A_2 e^{-6t}$$

$$i_R(t) = B_1 e^{-4t} + B_2 e^{-6t}$$

\Rightarrow step 2 :- $t = 0^-$

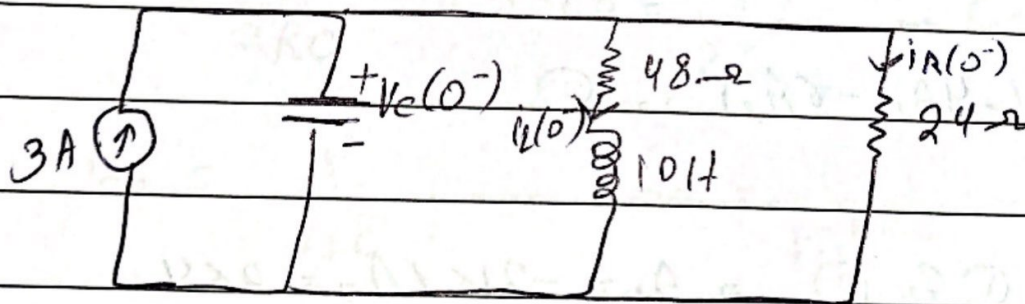


$$V_c(0^-) = 3(24 \parallel 48) = 48 \text{ V}$$

$$i_R(0^-) = \frac{48}{24} = 2 \text{ A}$$

$$i_L(0^-) = \frac{48}{48} = 1 \text{ A}$$

⇒ step 3: ($t=0^+$)

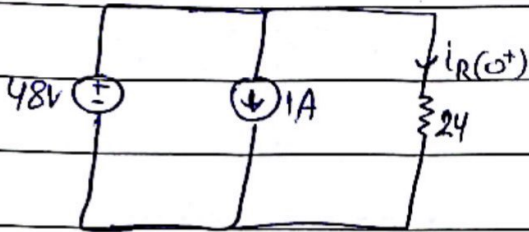

$$V_C(0^+) = V_C(0^-) = 48V = V_C(0)$$

$$i_R(0^+) = i_R(0) = \frac{48}{24} = 2A$$

* To find A_1 and A_2

$$V_C(0) = 48 = A_1 + A_2 \dots \textcircled{1}$$

$$i_C(t) = C \frac{dV(t)}{dt} = \frac{1}{240} \times (-4A_1 e^{-4t} - 6A_2 e^{-6t})$$

$$i_C(0) = \frac{1}{240} = (-4A_1 - 6A_2) \dots \textcircled{2}$$

Solve $\textcircled{1}$ & $\textcircled{2} \rightarrow A_1 = -216 / A_2 = 264$

$$\therefore V_C(t) = \begin{cases} 48V, & t < 0 \\ -216e^{-4t} + 264e^{-6t}, & t \geq 0 \end{cases}$$

$$i_R(t) = \frac{V_C(t)}{24} = \begin{cases} 2A, & t < 0 \\ \frac{216}{24}e^{-4t} + \frac{264}{24}e^{-6t}, & t \geq 0 \end{cases}$$

Example:- A parallel RLC circuit, $L = 10 \text{ mH}$, $C = 100 \text{ nF}$. Find R that will lead to :- 1) overdamped response, 2) Underdamped response
3) critical damped response.

\Rightarrow overdamped :- $\alpha > \omega_0$

$$\frac{1}{2RC} > \frac{1}{\sqrt{LC}} \rightarrow \frac{1}{2R \times 100 \times 10^{-6}} > \frac{1}{100}$$

$$R < 5 \Omega$$

1. $R < 5$ 2. $R > 5$ 3. $R = 5$

Ex:- Parallel RLC circuit, $R = 100 \Omega$, $\alpha = 1000 \text{ sec}^{-1}$, $\omega_0 = 800 \text{ rad/sec}$.
Find L, C, S_1, S_2 .

$$\alpha = \frac{1}{2RC} \rightarrow 1000 = \frac{1}{2 \times 100 C} \rightarrow C = 5 \mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow 800 = \frac{1}{\sqrt{100 \times 5 \times 10^{-6}}} \rightarrow L = 312.5 \text{ mH}$$

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -400 \text{ sec}^{-1}$$


$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -1600 \text{ sec}^{-1}$$

* $S_1 = S_2 \rightarrow$ Critical damped

* S_1 and $S_2 \rightarrow$ real numbers \rightarrow over damped

* S_1 and $S_2 \rightarrow$ Complex, underdamped.

19

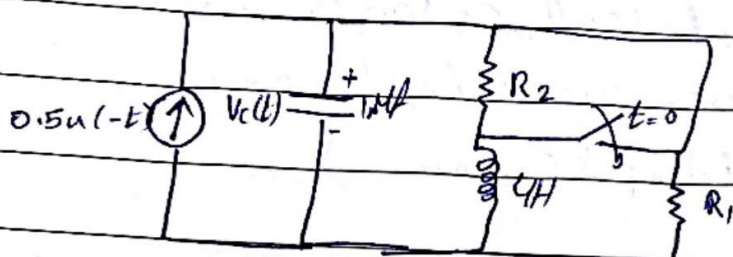

a) select R_1 so that the response after $t=0$ will be critically damped.

b) Select R_2 to obtain $V_c(0) = 100V$

c) find $V_c(t)$ at $t=1$ msec.

Solⁿ: step 1: at $t = \infty$

↳ source-free parallel RLC circuit.

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

for critical damping $\rightarrow \alpha = \omega_0$


$$\frac{1}{R_1 C} = \frac{1}{\sqrt{LC}} \Rightarrow \frac{1}{2R_1 \times 10^{-6}} = \frac{1}{\sqrt{4 \times 10^{-6}}}$$

$$\therefore R_1 = 1k \Omega \quad \alpha = 500 \text{ sec}^{-1}$$

$$V_c(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$$

$$= A_1 t e^{-500t} + A_2 e^{-500t}$$

⇒ step 2: $t = 0^-$

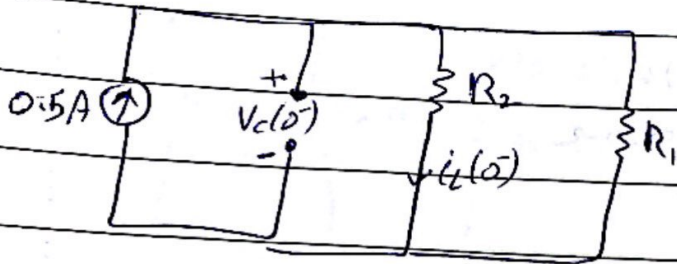


$$V_c(0^-) = 100 = 0.5 R_1 \parallel R_2$$

$$R_2 = 250 \Omega$$

$$i(0^-) = 0.5 \frac{R_1}{R_1 + R_2} = 0.4 \text{ A}$$

⇒ step 3: at $t = 0^+ = 0$

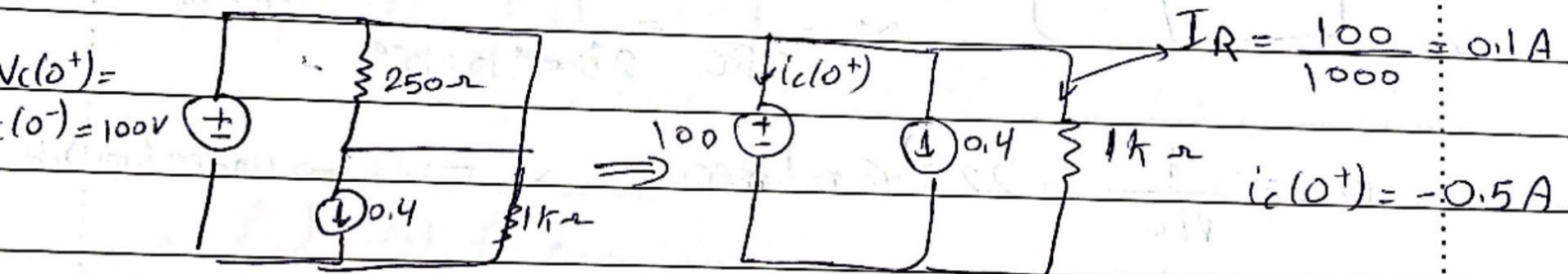

$$I_R = \frac{100}{1000} = 0.1 \text{ A}$$

$$i_c(0^+) = -0.5 \text{ A}$$

$$V_c(0) = A_2 \dots \textcircled{1} \rightarrow A_2 = 100$$

$$i(0^+) = C \frac{dV_c(t)}{dt} \Big|_{t=0} \dots \textcircled{2}$$


$$-0.5 = 1 \times 10^{-6} [A_1 e^{-500t} - 500 A_1 t e^{-500t} - 500 A_2 e^{-500t}]$$

$$A_1 = -45 \times 10^4$$


$$\therefore V_c(t) = \begin{cases} -45 \times 10^4 t e^{-500t} + 100 e^{-500t}, & t > 0 \\ 100, & t < 0 \end{cases}$$

$$V_c(t = 1 \text{ ms}) = -212 \text{ V}$$

Example:- Find $V_c(t)$ for all t .

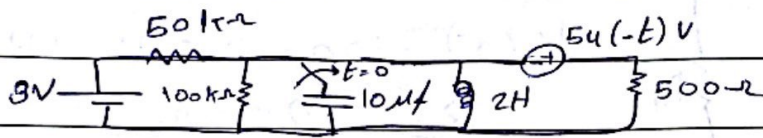

⇒ step 1: $t = \infty$

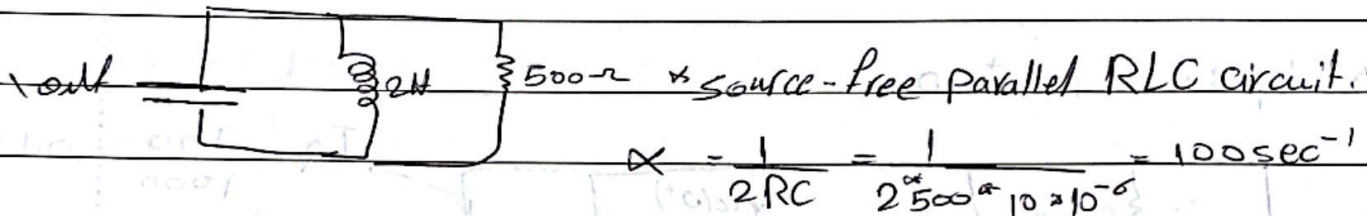

$$\omega_0 = \frac{1}{\sqrt{LC}} = 223.6 \text{ rad/sec.} \quad \alpha < \omega_0 \Rightarrow \text{underdamped}$$

$$V_c(t) = [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)] e^{-\alpha t}$$


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 200 \text{ rad/sec.}$$

$$V_c(t) = [A_1 \cos(200t) + A_2 \sin(200t)] e^{-100t}$$

$$i_L(0) = C \frac{dV_c(t)}{dt}$$

⇒ step 2: $t = 0^-$

voltage division.

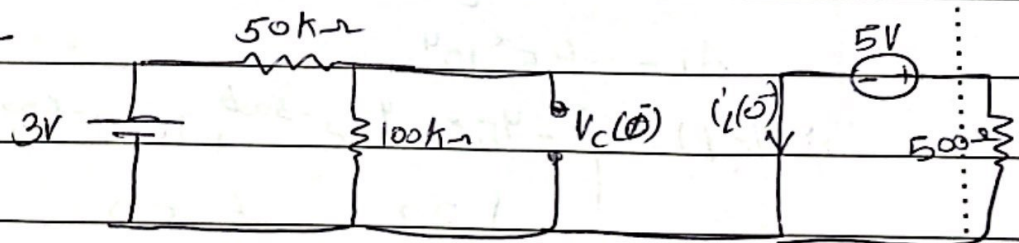


$$V_c(0^-) = 3 \times \frac{100}{100+500} = 2 \text{ Volt.}$$

$$i_L(0^-) = \frac{-5}{500} = -0.01 \text{ A.}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 9.968 \text{ rad/sec}$$

$$V_c(t) = [A_1 \cos(9.968t) + A_2 \sin(9.968t)] e^{-0.8t}$$

⇒ step 2 $t = 0^-$

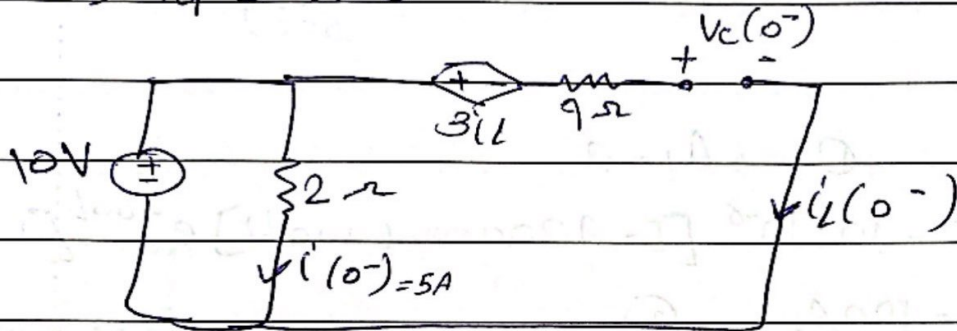


$$-V_c(0^-) = -3 \cdot 5 + 10 = 0$$

$$V_c(0^-) = -5V \quad \text{--- (1)}$$

$$i = \frac{10}{2} = 5$$

$$i_c(0^-) = 0A$$

⇒ step 3 $t = 0^+ = 0$

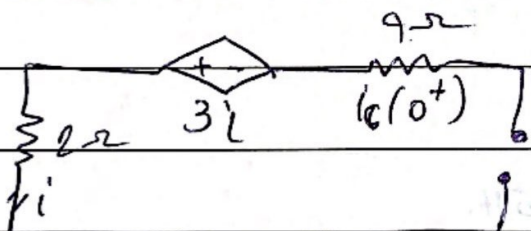

$$i_c(0^+) = 0 = \frac{dV_c(t)}{dt} \Big|_{t=0} \quad \text{--- (2)}$$


$$i_c(0^+) = 0A$$

$$A_1 = -5, A_2 = -0.4013$$

$$V_c(t) = \begin{cases} -5, & t \leq 0 \\ [-5 \cos(9.968t) - 0.4013 \sin(9.968t)] e^{-0.8t}, & t > 0 \end{cases}$$

Ex:- Find $V_c(t)$ for all time

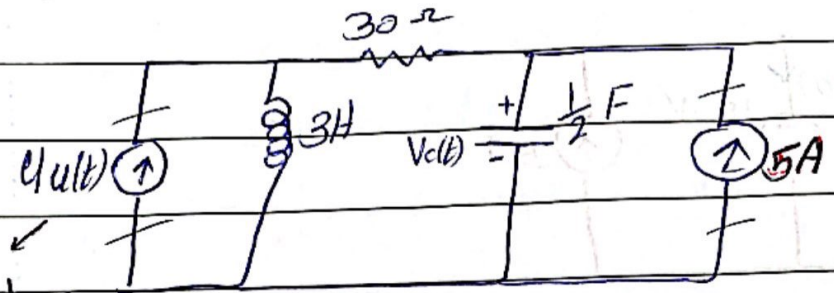* to determine whether the RLC driven circuit is parallel or series Kill all the independent sources.



switching process.

⇒ step 1 :- at $t = \infty$

type :- Driven series RLC

solution :- $V_c(t) = V_{cf} + V_{cn}$

V_{cf} :- force response

V_{cn} :- natural response

$$= V_c(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$V_c(\infty) = 5 * 30 = 150V$$

according to type of damping.

$$\alpha = \frac{R}{2L} = 5 \text{ sec}^{-1}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = 3 \text{ rad/sec}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1 \text{ sec}^{-1}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -9 \text{ sec}^{-1}$$

∵ $\alpha > \omega_0 \Rightarrow$ overdamping.

⇒ step 2 :- at $t = 0^-$

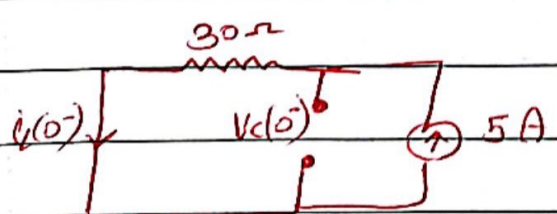


$$V_c(0^-) = 5 * 30 = 150V$$

$$i_L(0^-) = 5A$$

Remember - if there is an inductor we have to find $i_L(0^-)$, and if there is a capacitor we have to find $V_c(0^-)$

⇒ step 3 :- at $t = 0^+ = 0$

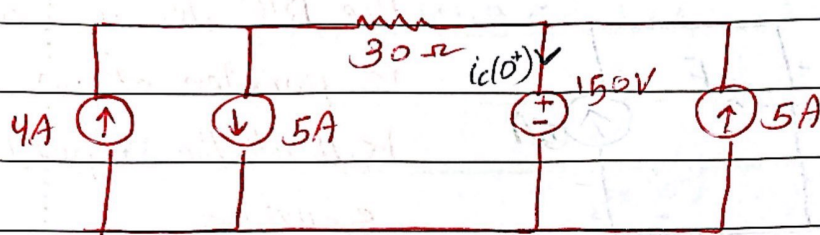

$$i_c(0^+) = i_c(0) = 4A$$

- to find A_1 and A_2

تحويل في الحالة الأولية

$$V_c(0) = 150 = 150 + A_1 + A_2 \dots \dots \textcircled{1}$$

$$i_c(0) = C \frac{dV_c(t)}{dt} \Big|_{t=0} \Rightarrow 4 = \frac{1}{27} [-A_1 - 9A_2] \dots \dots \textcircled{2}$$

$$A_1 = 13.5, A_2 = -13.5 \left\{ \therefore V_c(t) = \begin{cases} 150, & t < 0 \\ 150 + 13.5e^{-t} - 13.5e^{-9t} & t > 0 \end{cases}$$

Note: Lossless LC circuit

↳ parallel RLC \Rightarrow if $R = \infty$, then lossless LC circuit

↳ series RLC \Rightarrow if $R = 0$ " " " " "


$$\alpha = \frac{1}{2RC} = 0 \Rightarrow \alpha < \omega_0$$

$$\alpha = \frac{R}{2L} = 0 \Rightarrow \alpha < \omega_0$$

} underdamping

$$V(t) = e^{-\alpha t} [A_1 \cos(\omega_0 t) + A_2 \sin(\omega_0 t)]$$

$$\Rightarrow V(t) = A_1 \cos(\omega_0 t) + A_2 \sin(\omega_0 t)$$

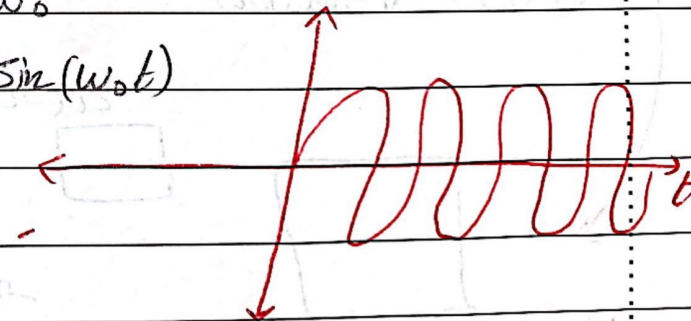

Quiz 2


→ AC circuit without switching.

* Sinusoidal steady-state Analysis


21

* Solution → Sources as a function of time

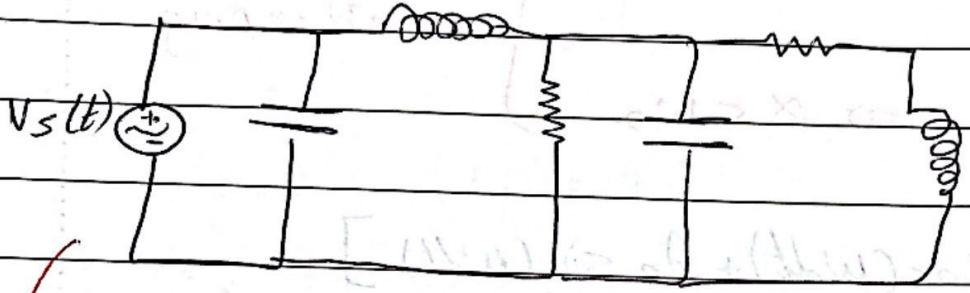time domain \leftrightarrow Frequency-domain (or phaser-domain)



$$V_s(t) = V \sin(\omega t)$$

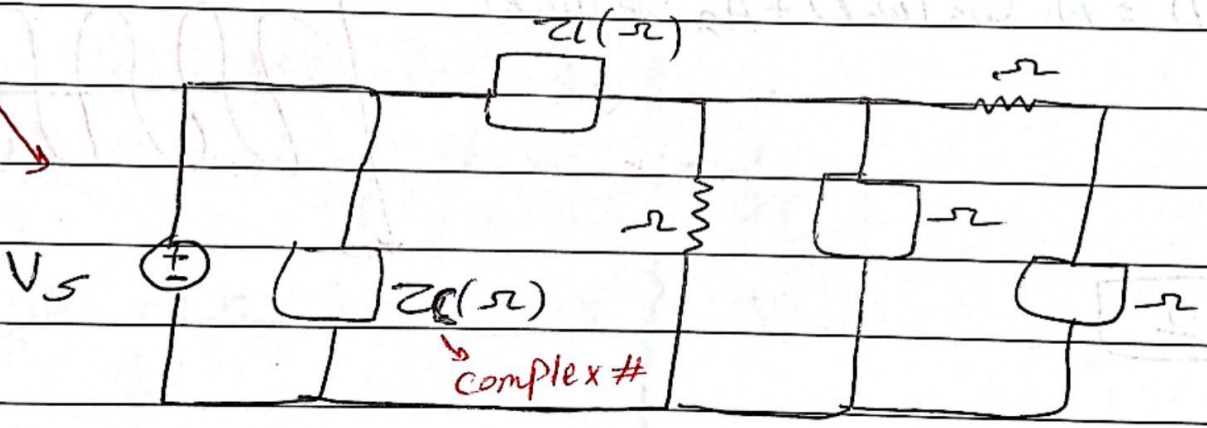

in phaser domain we represent (capacitors and inductors) as a blocks $Z_L(\omega)$ " ω " and $Z_C(\omega)$ " ω "

↑ inductors
 ↑ capacitors

* Complex numbers :- Real number + imaginary number.

ex:- $\bar{X} = 5 + j(3)$

↳ -jx-imaginary part

$\Rightarrow j = \sqrt{-1}$

-imaginary

$j^2 = -1$ $j^3 = -j$ $1/j = -j$

↳ operator


$j^4 = 1$

How to represent complex number

1. Rectangular form

$$\text{Ex: } \bar{X} = 3 + j4$$

$$\bar{Y} = -1.3 - j3.4$$

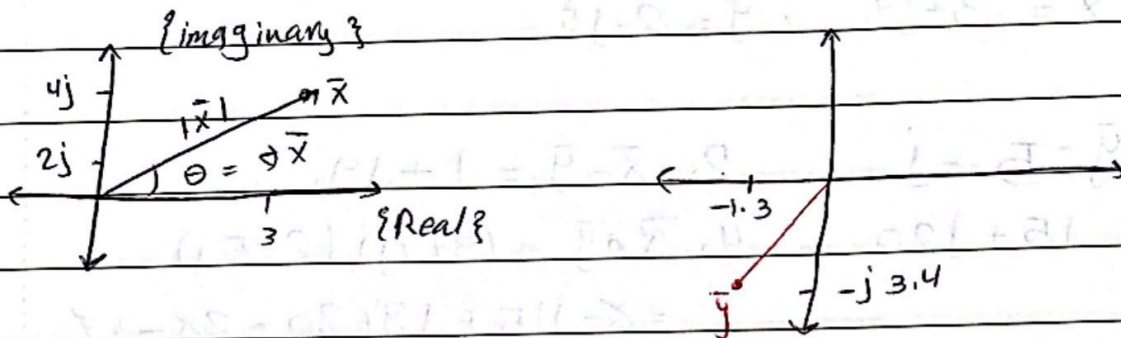

2. Polar form (exponential form)

$$\bar{X} = |\bar{X}| \angle \theta$$

$$= |\bar{X}| e^{j\theta}$$

* if $\bar{X} = a + jb$

$$\hookrightarrow |\bar{X}| = \sqrt{a^2 + b^2}, \theta = \tan^{-1} \frac{b}{a}$$

$$a = |\bar{X}| \cos \theta, b = |\bar{X}| \sin \theta$$

Ex: ① if $\bar{A} = 4 + j2$ write A in

Polar form.

$$|\bar{A}| = \sqrt{16 + 4} = \sqrt{20} = 4.47$$

$$\theta = \tan^{-1} \frac{2}{4} = 26.6^\circ \quad \bar{A} = 4.47 \angle 26.6^\circ$$

② if $\bar{X} = 5 \angle -36.9^\circ$ write X in the rectangular form.

$$\bar{X} = 5 \cos(-36.9) + j 5 \sin(-36.9) = 4 - j3$$

$$\text{Ex: } \vec{X} = e^{j90^\circ} \rightarrow \bar{X} = j.$$

$$\text{Ex: } \vec{X} = e^{-j90^\circ} \rightarrow \bar{X} = -j$$

* Mathematical operations for Complex numbers.

$$\text{ex: if } \vec{X} = 3 + j4, \vec{Y} = 2 - j5$$

$$1. \vec{X} + \vec{Y} = 5 - j$$

$$2. \vec{X} - \vec{Y} = 1 + j9.$$

$$3. 5\vec{X} = 15 + j20$$

$$4. \vec{X} \cdot \vec{Y} = (3 + j4)(2 - j5)$$

$$= 6 - j15 + j8 + 20 = 26 - j7$$

$$5. \text{Conjugate of } \vec{X} \Rightarrow \vec{X}^* = 3 - j4 \rightarrow \text{imaginary part}$$

$$\vec{Y} \Rightarrow \vec{Y}^* = 2 + j5.$$

$$\text{Ex: } \vec{X} + \vec{X}^* = 6, \vec{X} - \vec{X}^* = j8, \vec{X} \cdot \vec{X}^* = 3^2 + 4^2 = 25.$$

$$(\vec{X}^*)^* = \vec{X}.$$

$$6. \frac{\vec{X}}{\vec{Y}} = \frac{(3 + j4)(2 + j5)}{(2 - j5)(2 + j5)} = \frac{6 + 15j + 8j - 20}{4 + 25}$$

$$= \frac{-14 + 23j}{29} = \frac{-14}{29} + \frac{23}{29}j$$

Polar form.

$$\text{OR } \frac{\vec{X}}{\vec{Y}} = \frac{5 e^{j \tan^{-1}(\frac{4}{3})}}{\sqrt{29} e^{j \tan^{-1}(2.5)}} = \frac{5}{\sqrt{29}} e^{j(\tan^{-1}(\frac{4}{3}) - \tan^{-1}(2.5))}$$

* Integers

* If a and b are integers with $a \neq 0$, we say that a divides b if there is an integer c such that $b = ac$.
When a divides b we say that a is a factor of b and that b is a multiple of a .

- * the notation $a|b$ denotes that a divides b .
- * the notation $a \nmid b$ denotes that a does not divide b .

* Example: $3 \nmid 7$, $5 \nmid 12$, $4 \nmid 14$

2 0 6 8 | 2 1 8 , 3 1 1 2 , 5 1 1 5
لوقا لوقا
لوقا لوقا
لوقا لوقا

* Division

- let a, b , and c be integers. Then

* if $a|b$ and $a|c$, then $a|(b+c)$, $b+c = 6+9$

ex. $3|6$ and $3|9$, then $3|15$

* if $a|b$ and $b|c$, then $a|c$

$3|6$, and $6|24$ then $3|24$

* if $a|b$, then $a|bc$ for all integers c

$3|6$ then $3|12$, $3|18$, $3|24$.

* if a, b and c are integers such that $a|b$ and $a|c$, then $a|(mb+mc)$

316, and 319 then 3115, 3130, 3145

~~* let a be~~

↳ Division Algorithm

* let " a " be an integer and " d " a positive integer.

Then there are unique integers " q " and " r ", with $0 \leq r < d$ such that $a = dq + r$

* d is called the divisor, a is called the dividend, q is called the quotient, and r is called the remainder.

* $q = a \text{ div } d \rightarrow$ ناتج القسمة

* $r = a \text{ mod } d \rightarrow$ الباقي

Examples:-

* what are the quotient and remainder when 101 is divided by 11 $q = 9$ $r = 2$

$$?? a = dq + r$$

$$= 11 \times 9 + 2 = 101$$

* what are the quotient and remainder when -11 is divided by 3

$$q = -4 \quad r = 1$$

$$-11 = 3(-4) + 1 = -11$$

$$* 18 \text{ div } 4 = 4$$

$$* 18 \text{ mod } 4 = 2$$

$$* -14 \text{ div } 5 = -3$$

$$* -14 \text{ mod } 5 = 1$$

$$* 22 \text{ mod } 5 = 2 \quad \left. \vphantom{22} \right\} \text{ mod } \underline{5} \text{ is}$$

$$* 7 \text{ mod } 5 = 2$$

* $22 \equiv 7 \pmod{5}$ indicates that 22 is congruent to 7 modulo 5

* Modular Arithmetic

* $a \equiv b \pmod{m}$ indicates that a is congruent to b modulo m .

* $a \equiv b \pmod{m}$ iff $a \text{ mod } m = b \text{ mod } m$

* $a \equiv b \pmod{m}$ if m divides $a - b$

Examples:-

* Determine whether 17 is congruent to 5 module 6

$$17 \equiv 5 \pmod{6}$$

$$17 \pmod{6} = 5$$

$$5 \pmod{6} = 5$$

* Determine whether 24 is congruent to 14 module 6

$$24 \equiv 14 \pmod{6}$$

$$24 - 14 = 10$$

$$6 \nmid 10 \rightarrow \neq$$

$$24 \pmod{6} = 0$$

$$14 \pmod{6} = 2$$

* Determine whether $22 \equiv 13 \pmod{4}$

$$22 - 13 = 9$$

$$4 \nmid 9$$

$$22 \pmod{4} = 2$$

$$13 \pmod{4} = 1$$

* Determine whether $15 \equiv 7 \pmod{4}$

$$15 - 7 = 8$$

$$4 \mid 8 \checkmark$$

* Modular Arithmetic.

let m be a positive integer. If $a \equiv b \pmod{m}$ and $c \equiv d \pmod{m}$, then.

* $a + c \equiv b + d \pmod{m}$

* $ac \equiv bd \pmod{m}$

* Example:-

From $7 \equiv 2 \pmod{5}$ and $11 \equiv 1 \pmod{5}$, then:

$18 \equiv 3 \pmod{5}$

$77 \equiv 2 \pmod{5}$

* Arithmetic Modulo m

- let Z_m be the set of nonnegative integers less than m

- we define addition of these integers, denoted by $+_m$

as: $a +_m b = (a + b) \pmod{m}$.

- we define addition of these integers, denoted by \cdot_m as:

$a \cdot_m b = (a \cdot b) \pmod{m}$.

- Example :-

* $7 +_m 9 = (7 + 9) \pmod{11} = 16 \pmod{11} = 5$

* $7 \cdot_m 9 = 63 \pmod{11} = 8$

* Arithmetic Modulo property = "+_m and ._m"

1) Closure → "المغلق" الجوانب يبقى لنفس المجموعة

2) Associativity → ارتباط

3) Commutativity → ابدال

4) Identity elements → العنصر المحايد = 1، العنصر = 0

5) Additive inverse → العنصر العكسي

6) Distributivity → توزيع

Assume +11

$$(2)^{-1} = 9 \text{ why??} \rightarrow 2+9=11 \rightarrow 11 \bmod 11 = 0, (2+11 \cdot 9) = 0$$

$$(1)^{-1} = 10 \rightarrow 1+10=11 \rightarrow 11 \bmod 11 = 0$$

* Primes. → (أعداد أولية)

* A positive integer p is greater than 1 is called prime if the only positive ~~integer~~ factors of p are 1 and p .

A positive integer is greater than 1 and is not prime is called composite.

* 7 is a prime number while 9 is a composite number.

- The primes less than 100 are :-

2, 3, 5, 7, 11, 13, 17, 19, 23, 29, 31, 37, 41, 43, 47,
53, 59, 61, 67, 71, 73, 79, 83, 89, 97.

The Fundamental theorem of Arithmetic.

- every positive integer greater than 1 can be written uniquely as a prime or as the product of two or more primes where the prime factors are written in order of nondecreasing size.

"أي عدد طبيعي أكبر من 1 يمكن كتابته بشكل فريد إما كعدد أولي أو كحاصل ضرب عددين أوليين أو أكثر."

ex:- what are the prime factorizations of 100, 49 and 60.

$$100 = 2 \times 5 \times 2 \times 5 = 2^2 \times 5^2$$

$$49 = 7 \times 7 = 7^2$$

$$11 = 11$$

$$60 = 6 \times 10 = 3 \times 2 \times 2 \times 5 = 2^2 \times 3 \times 5$$

* greatest common divisors → أكبر عدد يقسم العدد a والعدد b

- let a and b be integers, not both zero. The largest integer d such that $d|a$ and $d|b$ is called the greatest common divisor of a and b. The greatest common divisor of a and b is denoted by $\gcd(a, b)$

ex:- what is the gcd of 24 and 36?

$$24 = 6 \times 4 = 2^3 \times 3$$

$$36 = 6 \times 6 = 2 \times 3 \times 2 \times 3 = 2^2 \times 3^2$$

أما هذا العدد المشترك والأكبر هو العدد المشترك.

$$\gcd = 2^2 \times 3 = 12$$

ex:- find gcd for 100 and 30

$$100 = 2 \times 5 \times 2 \times 5 = 2^2 \times 5^2$$

$$30 = 2 \times 5 \times 3$$

$$\text{gcd}(100, 30) = 2 \times 5 = 10$$

ex:- $\text{gcd}(17, 22)$

$$17 = 17$$

$$22 = 2 \times 11$$

$$\text{gcd} = 1$$

* The integers a and b are relatively prime if their greatest common divisor is 1.

ex:- $\text{gcd}(8, 9) = 1$

* Pairwise Relatively prime

The integers a_1, a_2, \dots, a_n are pairwise relatively prime if $\text{gcd}(a_i, a_j) = 1$ whenever $1 \leq i < j \leq n$

ex:- Determine whether the integers 10, 17 and 21 are pairwise relatively prime and whether the integers 10, 19, 24

$$\text{gcd}(10, 17) = 1, \text{gcd}(10, 21) = 1, \text{gcd}(17, 21) = 1$$

$$\text{gcd}(10, 19) = 1, \text{gcd}(10, 24) = 2 \quad \times$$

* Least Common Multiple:- a و b باقي الصغرة a و b ~~الاصغر~~
 - LCM of the positive integers a and b is the smallest positive integer that is divisible by both a and b . The least common multiple of a and b is denoted by $\text{lcm}(a, b)$

ex:- what is lcm of 24 and 36?

$$24 = 2 \times 4 \times 3 = 2 \times 2 \times 2 \times 3 = 2^3 \times 3$$

$$36 = 2^2 \times 3^2$$

نأخذ كل الأعداد ونأخذ الأس الأكبر من الأعداد المشتركة

$$\text{lcm} = 2^3 \times 3^2 = 72$$

ex:- $\text{lcm}(100, 30)$

$$100 = 2^2 \times 5^2$$

$$30 = 2 \times 3 \times 5$$

$$\text{lcm}(100, 30) = 2^2 \times 3 \times 5^2 = 300$$

* let a and b be positive integers. Then ~~ab~~

$$ab = \text{gcd}(a, b) \cdot \text{lcm}(a, b)$$

ex:- $a = 100$ $b = 30$

$$\text{lcm} = 300$$

$$\text{gcd} = 10$$

$$ab = 3000$$

$$\text{gcd} \cdot \text{lcm} = 3000$$

* Mathematical Induction.

* Mathematical Induction can be used to prove statements that assert that $P(n)$ is true for all positive integers n , where $P(n)$ is a propositional function.

* A proof by mathematical induction has two parts, a basis step, where we ~~have~~ show that $P(1)$ is true, and an inductive step, where we show that for all positive integers k , if $P(k)$ is true, then $P(k+1)$ is true.

$P(k) \rightarrow P(k+1)$

↳ using direct Proof

examples :-

show that if n is a positive integer, then

$1 + 2 + \dots + n = \frac{n(n+1)}{2}$

proof $\sum_{k=1}^n k = \frac{n(n+1)}{2}$

\Rightarrow step 1: $P(1) \rightarrow 1 \stackrel{?}{=} \frac{1(2)}{2}$ ✓

\Rightarrow step 2: $P(k) \rightarrow P(k+1)$

Assumption: $1 + 2 + \dots + k = \frac{k(k+1)}{2}$

PROVE: $P(k+1)$

$\frac{k(k+1)}{2} + (k+1) = \frac{k(k+1) + 2(k+1)}{2} = \frac{(k+1)(k+2)}{2}$

ex: Show that $1 + 2 + 2^2 + \dots + 2^n = 2^{n+1} - 1$ for all nonnegative integer n .

$n \geq 0$

$\underline{1} \quad P(0) \rightarrow 1 \stackrel{?}{=} 2^1 - 1 \quad \checkmark$

$\underline{2} \quad P(k) \rightarrow P(k+1)$

assumption $\rightarrow 1 + 2 + 2^2 + \dots + 2^k = 2^{k+1} - 1$

prove $\rightarrow P(k+1)$

L.H.S

R.H.S.

$1 + 2 + 2^2 + \dots + 2^k + 2^{k+1} = 2^{k+2} - 1$

$= 1 + 2 + 2^2 + \dots + 2^k + 2^{k+1}$

$= 2^{k+1} - 1 + 2^{k+1}$

$= 2 \cdot 2^{k+1} - 1$

$2^{k+2} - 1 \neq \text{R.H.S.}$

ex. $\sum_{k=1}^n k^2 = \frac{n(n+1)(2n+1)}{6}$ M₆

بشكل آخر

$$1+4+9 \dots n^2 = \frac{n(n+1)(2n+1)}{6}$$

$n=1$

$$\hookrightarrow P(1) \quad 1 \stackrel{?}{=} \frac{1(2)(3)}{6} = \frac{6}{6} = 1 \quad \checkmark$$

$\Rightarrow P(k) \rightarrow P(k+1) \rightarrow$ direct Proof

\Rightarrow assumption $P(k)$ is true

$$1+4+9 \dots + k^2 = \frac{k(k+1)(2k+1)}{6}$$

\Rightarrow Proof $\neq P(k+1)$

L.H.S

R.H.S.

$$1+4+9 \dots + k^2 + (k+1)^2 = \frac{(k+1)(k+2)(2(k+1)+1)}{6}$$

$$\frac{k(k+1)(2k+1)}{6} + (k+1)^2 \quad \text{R.H.S.}$$

$$\frac{k(k+1)(2k+1) + 6(k+1)^2}{6}$$

علاوة

$$\frac{(k+1) [k(2k+1) + 6(k+1)]}{6}$$

$$\frac{(k+1) [2k^2 + k + 6k + 6]}{6} = \frac{(k+1) (2k^2 + 7k + 6)}{6}$$

$$\text{R.H.S.} \Rightarrow \frac{(k+1)(k+2)(2k+3)}{6} = \frac{(k+1)(2k^2 + 7k + 6)}{6} \quad \neq$$

$$* -17 \text{ div } 3 = -6$$

$$* -17 \text{ mod } 3 = 1$$

* باقي القسمة 2/8

أكون عدد موجب

0 ≤ r < d

$$* 14 \text{ mod } 12 = 2 \text{ mod } 12$$

$$\downarrow \quad \quad \quad \downarrow$$

$$\text{So, } 14 \equiv 2 \pmod{12}$$

$$* 15 \equiv 4 \pmod{3} \quad X$$

$$\rightarrow 15 \text{ mod } 3 = 0$$

$$4 \text{ mod } 3 = 1$$

$$\text{other way, } 3 \nmid (15-4) = 3 \nmid (11) \quad X$$

$$* (a+b) \text{ mod } 9 = a +_9 b \quad \text{"نظرية الجمع للضرب"}$$

$$\text{ex: } 4 +_9 8 = 3$$

$$4 \cdot_9 8 = 7$$

* inverse العدد في الجمع هو عبارة عن عدد يجمع العدد الأصلي ويأخذنا mod

والنتيجة = "العنصر المحايد"

* inverse العدد في الضرب هو عبارة عن عدد يضرب بالعدد الأصلي ويأخذنا mod

والنتيجة = "1" "العنصر المحايد"

* Sine wave signals "we use it to convert time domain to frequency domain"

ex: ↙

$$V(t) = V_m \sin \omega t$$

Amplitude

"Peak value"

Argument "Angle"


ω :- radian frequency "angular frequency" [rad/sec]

$$\omega = 2\pi f = \frac{2\pi}{T} \text{ where } f = \frac{1}{T}$$

T → Period of the signal. (sec) → *المدة الزمنية*

f → Frequency of the signal. (Hz) *سعة الأمواج*

Ex :- $V(t) = 5 \sin(3\pi t)$

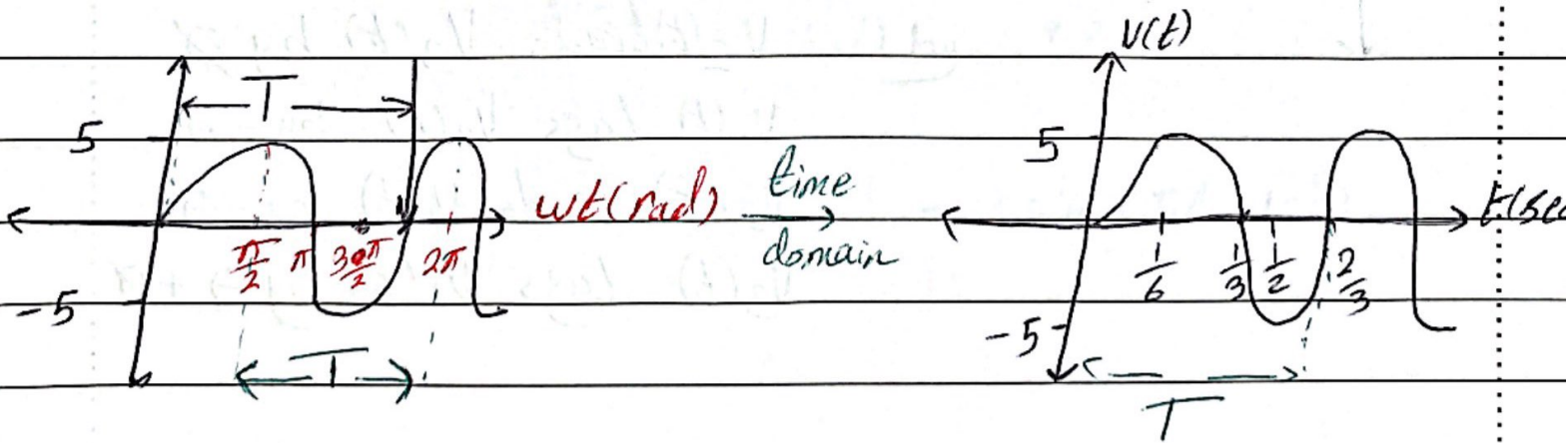

$$3\pi t = \frac{\pi}{2} \rightarrow t = \frac{1}{6}$$

$$3\pi t = \pi \rightarrow t = \frac{1}{3}$$

$$\omega = 2\pi f$$


$$3\pi = 2\pi f$$

$$f = 1.5 \text{ Hz}$$

$$T = \frac{2}{3}$$

* In general, $V(t) = V_m (\sin(\omega t + \theta))$ Phase angle shift to the left.

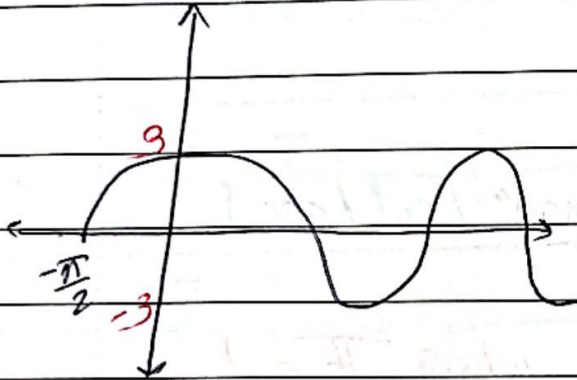ex:- $V(t) = 3 \sin(\underbrace{2\pi t}_{\omega_0} + 90^\circ)$




$$2\pi = 2\pi f$$

$$f = 1 \text{ Hz}$$

$$T = 1 \text{ sec.}$$

* "-" to shift to the right

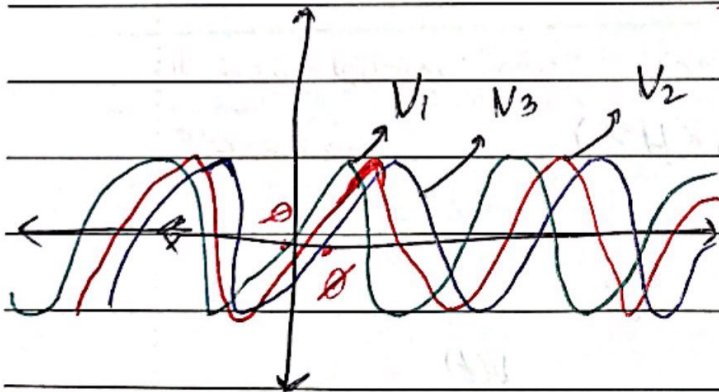المعنى $V_1(t)$ تسبق $V_2(t)$ الى مقدار θ X-axis



$V_1(t)$ leads $V_2(t)$ by θ

$V_2(t)$ lags $V_1(t)$ by θ

$V_2(t)$ leads $V_3(t)$ by θ

$V_1(t)$ lags $V_2(t)$ by $-\theta$

$V_2(t)$ leads $V_1(t)$ by $-\theta$

$V_3(t)$ lags $V_1(t)$ by $\theta + \theta$

* Let $V_1(t) = V_{m1} \sin(\omega t + \theta)$, $V_2(t) = V_{m2} \sin(\omega t + \phi)$

↳ if $\theta = \phi$, then $V_1(t)$ and $V_2(t)$ are in phase

if $\theta \neq \phi$ then $V_1(t)$ and $V_2(t)$ are out of phase

* To compute V_1 and V_2

1. Must be positive sine or cosine
2. Must be positive amplitude
3. Same frequency

~~ex~~ $+\sin(\omega t + 180) \equiv -\sin \omega t$

$+\cos(\omega t + 180) \equiv -\cos \omega t$

$\cos(\omega t + 90) \equiv -\sin \omega t$

$\sin(\omega t + 90) \equiv +\cos \omega t$


ex^o- if $V_1(t) = 3 \cos(5t + 10^\circ)$, $V_2(t) = 4 \sin(5t - 30^\circ)$

then $V_1(t)$ leads $V_2(t)$ by ??

$V_1(t) = 3 \sin(5t + 10^\circ + 90) = 3 \sin(5t + 100^\circ)$

$\omega t + 100 = 0 \rightarrow \omega t = 0 = V_1$

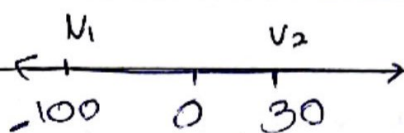$\omega t - 30 = 0 \rightarrow \omega t = 30 = V_2$



V_1 leads V_2 by 130°

V_2 lags V_1 by 130°


Ex: if $V_1(t) = -3 \cos(4t - 30^\circ)$, $V_2(t) = -2 \sin(4t + 40^\circ)$
 $V_2(t)$ lags $V_1(t)$ by ??

$$V_1(t) = 3 \cos(4t - 30^\circ + 180^\circ) = 3 \cos(4t + 150^\circ)$$

$$V_2(t) = 2 \cos(4t + 40^\circ + 90^\circ) = 2 \cos(4t + 130^\circ)$$

$$\omega t + 40 = 0 \rightarrow \omega t = -40 = V_1$$
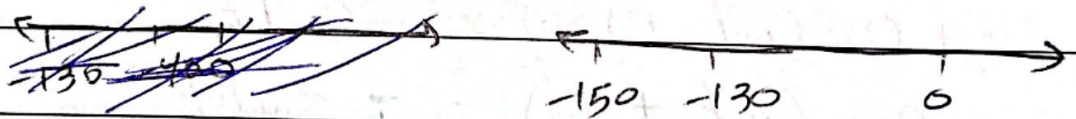
$$\omega t + 130 = 0 \rightarrow \omega t = -130 = V_2$$




V_2 lags V_1 by 20°

V_1 leads V_2 by 20°

V_2 leads V_1 by $-20^\circ \equiv 340^\circ$

* Sinusoidal steady-state Analysis

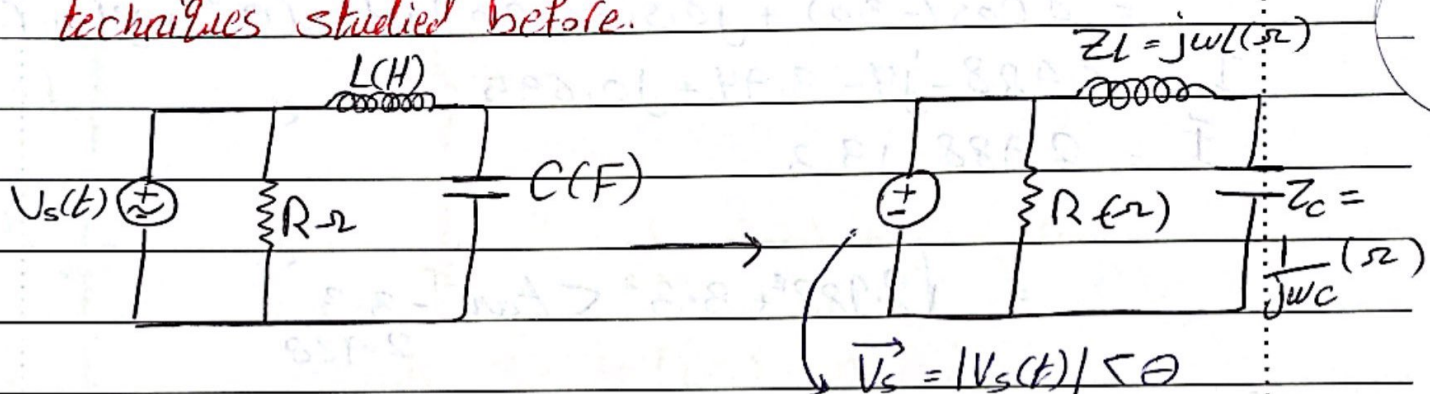- step 1 :- Time-domain → Frequency domain (phasor domain)
- step 2 :- Solve the circuit in phasor domain using all techniques studied before.



↳ phasor form of $V_s(t)$

* $\omega = 2\pi f$

* The phasor.

To write the phasor form of a given signal :-

1. Write the given signal using positive cosine function

↳ $V_s(t) = V_m \cos(\omega t + \theta)$

2. $\vec{V}_s = V_m \angle \theta$

ex:- if $V(t) = 100 \cos(400t - 30^\circ)$

$\vec{V} = 100 \angle -30$

ex:- $i(t) = -5 \sin(580t - 110^\circ)$

$= 5 \cos(580t - 110^\circ + 90^\circ) = 5 \cos(580t - 20^\circ)$

$\vec{I} = 5 \angle -20^\circ$

$$\begin{aligned} \text{ex:- } i(t) &= 8 \cos(4t - 30^\circ) + 4 \sin(4t - 120^\circ) \\ &= 8 \cos(4t - 30^\circ) + 4 \cos(4t - 120^\circ - 90^\circ) \\ &= 8 \cos(4t - 30^\circ) + 4 \cos(4t - 150^\circ) \end{aligned}$$

$$\vec{I} = 8 \angle -30^\circ + 4 \angle -150^\circ$$

$$= 8 \cos(-30^\circ) + j8 \sin(-30^\circ) + 4 \cos(150^\circ) + j4 \sin(150^\circ)$$

$$\vec{I} = 6.928 - j4 - 3.94 + j0.695$$

$$\vec{I} = 2.988 - j3.3$$

$$= \sqrt{2.988^2 + 3.3^2} \angle \tan^{-1} \frac{-3.3}{2.988}$$

$$\vec{I} = 4.45 \angle -47.8^\circ$$




$$\text{ex:- find } i(t) \text{ if } \vec{I} = 20 + j10 \text{ A. } \omega = 2000 \text{ rad/sec.}$$

$$\vec{I} = \sqrt{20^2 + 10^2} \angle \tan^{-1} \frac{10}{20}$$


$$= 22.36 \angle 26.56^\circ$$

$$i(t) = 22.36 \cos(2000t + 26.57^\circ) \text{ A.}$$

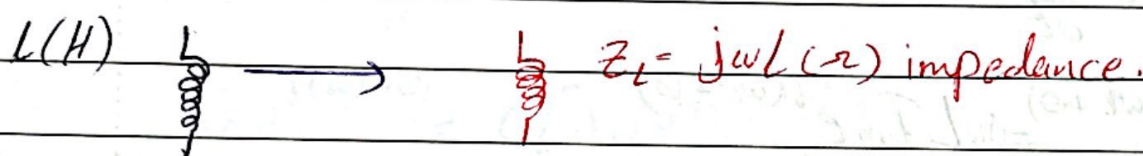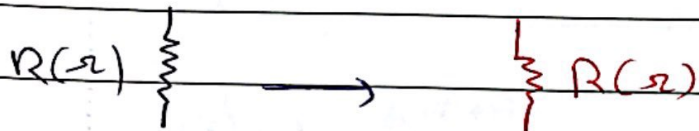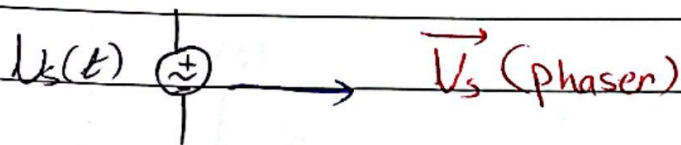* Time-domain \longrightarrow Frequency domain



* Resistor $R \rightarrow R$... why?

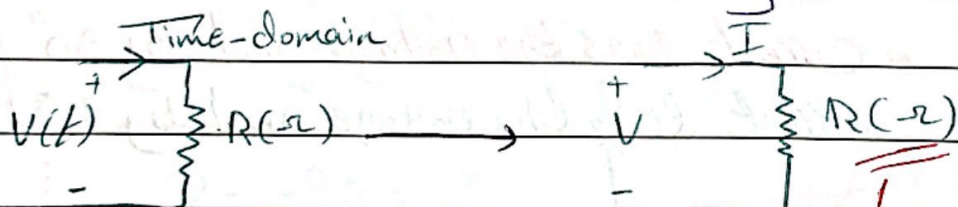

general form of $v(t)$

$$v(t) = V_m \cos(\omega t + \theta) + j V_m \sin(\omega t + \theta) = V_m e^{j(\omega t + \theta)}$$

let $v(t) = V_m e^{j(\omega t + \theta)}$

$i(t) = I_m e^{j(\omega t + \theta)}$


$v(t) = R i(t)$

$V_m e^{j(\omega t + \theta)} = R I_m e^{j(\omega t + \theta)}$

$V_m e^{j\theta} e^{j\omega t} = R I_m e^{j\theta} e^{j\omega t}$

$\vec{V} = R \vec{I}$

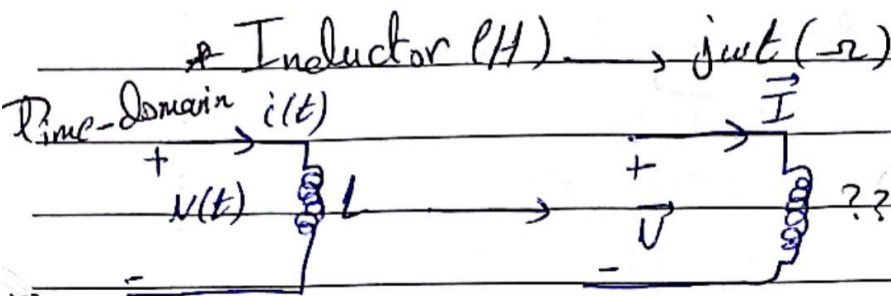$\phi = 0 \Rightarrow$ The current and voltage on R are in phase



$$\text{let } V(t) = V_m e^{j(\omega t + \theta)}$$

$$i(t) = I_m e^{j(\omega t + \phi)}$$

$$V(t) = L \frac{di}{dt}$$

$$V_m e^{j(\omega t + \theta)} = j\omega L I_m e^{j(\omega t + \phi)}$$


$$V_m e^{j\omega t} \cdot e^{j\theta} = j\omega L I_m e^{j\omega t} e^{j\phi}$$

$$\vec{V} = j\omega L \cdot \vec{I}$$


Rule:

$$\theta = 90^\circ + \phi$$

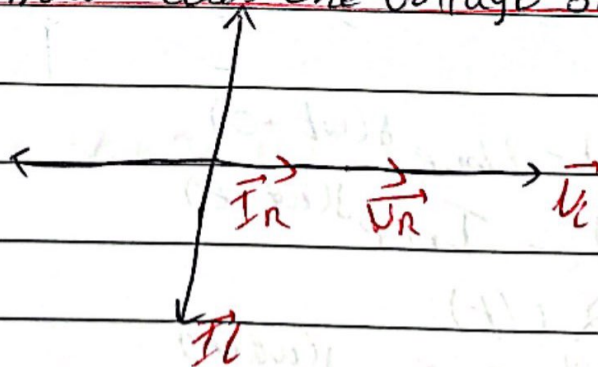* Current: lags the voltage on L by 90°
 current leads the voltage on L by 270°



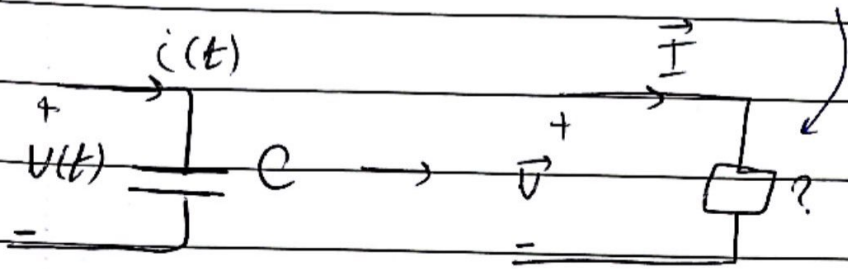* Capacitor. $C (F) \rightarrow Z_c = \frac{1}{j\omega C} (\Omega)$



$$v(t) = V_m e^{j(\omega t + \phi)}$$

$$i(t) = I_m e^{j(\omega t + \theta)}$$

$$i(t) = C \frac{dv}{dt}$$

$$I_m e^{j(\omega t + \theta)} = C [j\omega e^{j(\omega t + \phi)}]$$


$$I_m e^{j\theta} = C j\omega V_m e^{j\phi}$$

$$\vec{I} = j\omega C \vec{V}$$

$$\vec{V} = \frac{1}{j\omega C} \vec{I} (\Omega)$$

$$\theta = -90 + \phi$$

* current leads the voltage on C by 90°

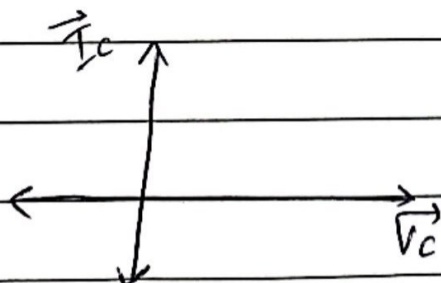

24

• Impedance \rightarrow Resistance "real part"

$$\vec{Z} = R + jX \rightarrow \text{Reactance } (-r) = |Z| \angle \theta$$

"imaginary part"

impedance (Ω) \downarrow

$$\vec{Z} = \frac{\vec{V}}{\vec{I}} = \frac{|V| \angle \theta}{I \angle \phi}$$

* if $\theta = 0 \Rightarrow$ Resistive load. (I and V are in phase)

* if $\theta = 90^\circ \Rightarrow$ purely inductive load. (I lags V by 90°)

* if $\theta = -90^\circ \Rightarrow$ purely capacitive load. (I leads V by 90°)

* if θ is positive \Rightarrow inductive load (not purely). (I lags V by θ)

* if θ is negative \Rightarrow capacitive load (I leads V by θ)

ex: $\vec{Z} = 5 \Omega$ \rightarrow Purely resistive load.

$\vec{Z} = j20 \Omega$ \rightarrow Purely inductive load.

$\vec{Z} = \frac{1}{j20} \Omega = -j \frac{1}{20}$ \rightarrow Purely capacitive load.

$\vec{Z} = 4 + j3 \rightarrow \tan^{-1} \frac{3}{4}$ \rightarrow inductive load.


$\vec{Z} = 2 - j2 \rightarrow \tan^{-1} -1$ \rightarrow capacitive load.

• Admittance: $\vec{Y} = \frac{1}{\vec{Z}} \left(\frac{S}{\Omega} \right)$


$\vec{Y} = G + jB \rightarrow$ susceptance

Admittance \downarrow


Series

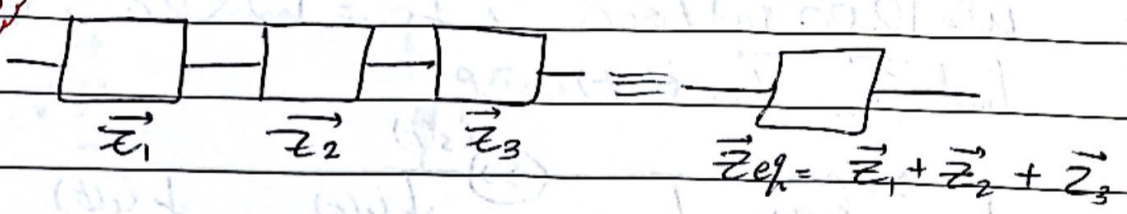

Parallel

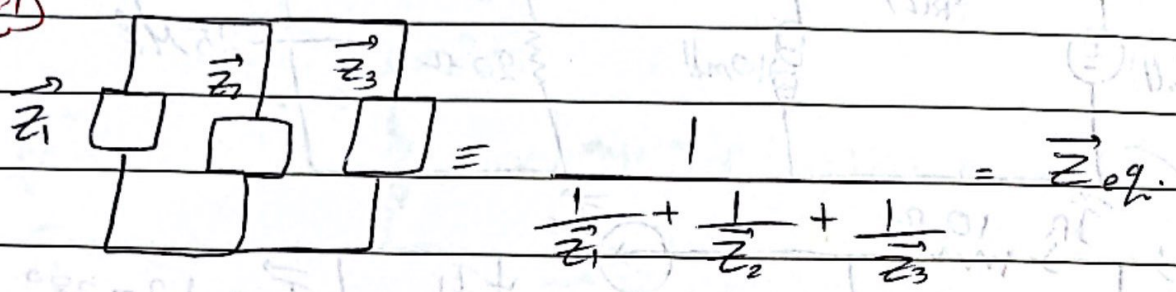


ex:- find \vec{Z}_{eq}

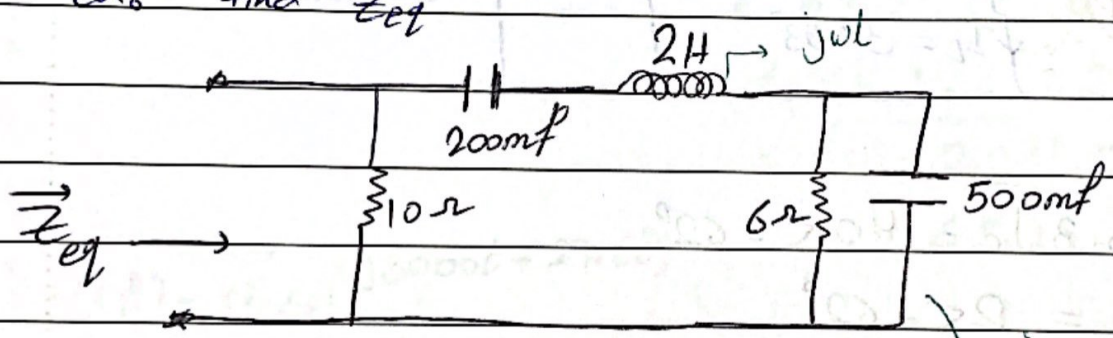

$\omega = 5\text{ rad/sec}$


frequency domain

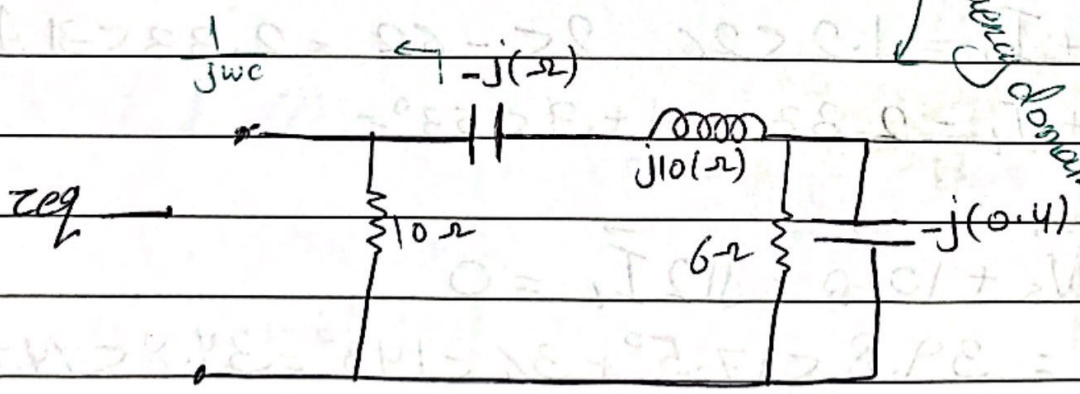

$$\vec{Z}_{eq} = \left[\frac{(-j0.4 // 6) + 10j - j}{10} \right] = \frac{(-j2.4 + 9j) // 10}{6 - j0.4}$$

$$= 4.256 + j4.929\ \Omega$$

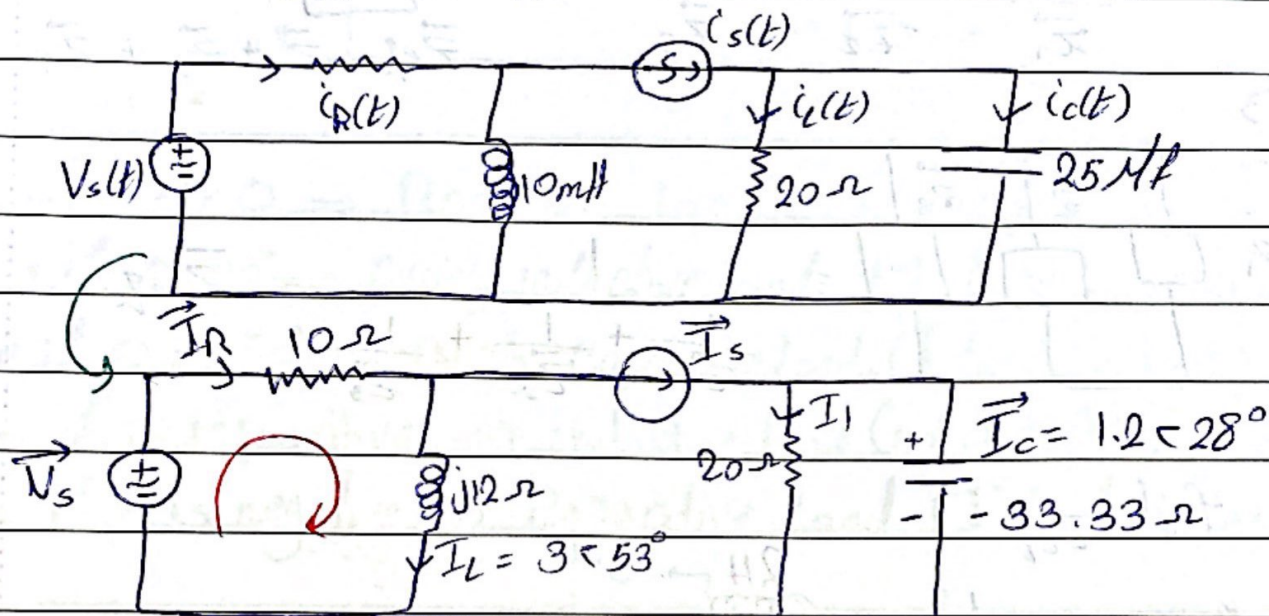ex:- $\omega = 1200 \text{ rad/sec}$, $\vec{I}_c = 1.2 \angle 28^\circ$, $\vec{I}_L = 3 \angle 53^\circ$
 Find \vec{I}_s , \vec{V}_s , $i_R(t)$



$$\vec{V}_c = -j33.3 \vec{I}_c = 40 \angle -62^\circ$$

$$\vec{I}_1 = \frac{V_c}{20} = 2 \angle -62^\circ$$



$$\vec{I}_s = \vec{I}_c + \vec{I}_1 = 1.2 \angle 28^\circ + 2 \angle -62^\circ = 2.33 \angle -31^\circ \text{ A}$$

$$\vec{I}_R = \vec{I}_s + \vec{I}_L = 2.33 \angle -31^\circ + 3 \angle 53^\circ =$$

$$\text{KVL :- } -\vec{V}_s + 10\vec{I}_R + j12\vec{I}_L = 0$$

$$\vec{V}_s = 39.8 \angle 17.5^\circ + 36 \angle 143^\circ = 34.8 \angle 74.7^\circ \text{ V}$$
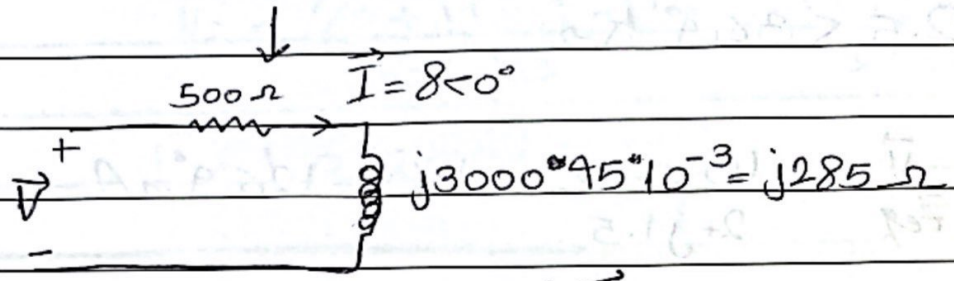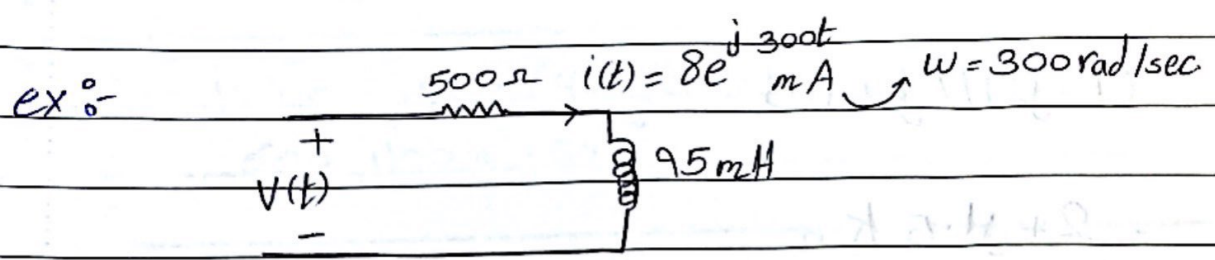
$$V_s(t) = 34.8 \cos(1200t + 74.7^\circ) \text{ V}$$



$$\vec{V} = \vec{I} (500 + j285)$$

$$= 8 \angle 20^\circ (500 + j285)$$

$$= 4 + j2.280 \text{ V}$$



$$= \sqrt{16 + 2.28^2} \angle \tan^{-1} \frac{2.28}{4}$$

$$= 4.6 \angle 29.68^\circ$$

$$V(t) = 4.6 e^{(j3000t + 29.68^\circ)}$$

$$= 4.6 \cos(3000t + 29.68^\circ) + j4.6 \sin(3000t + 29.68^\circ)$$

ex: Find $i(t)$

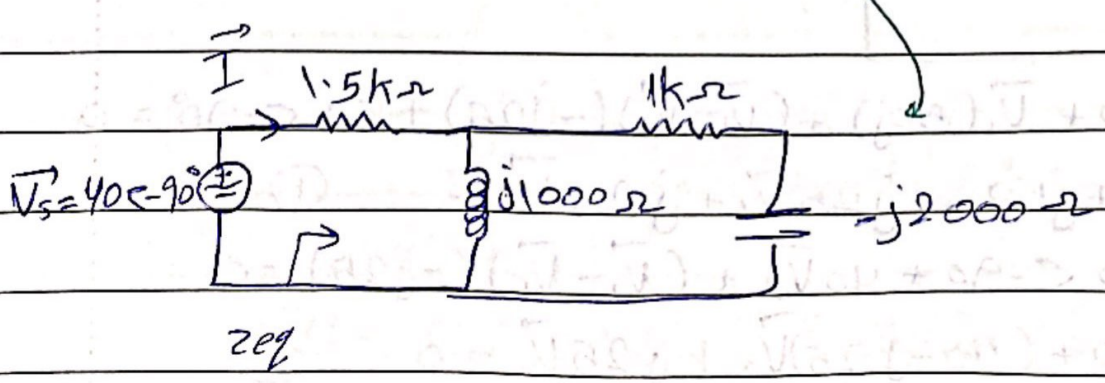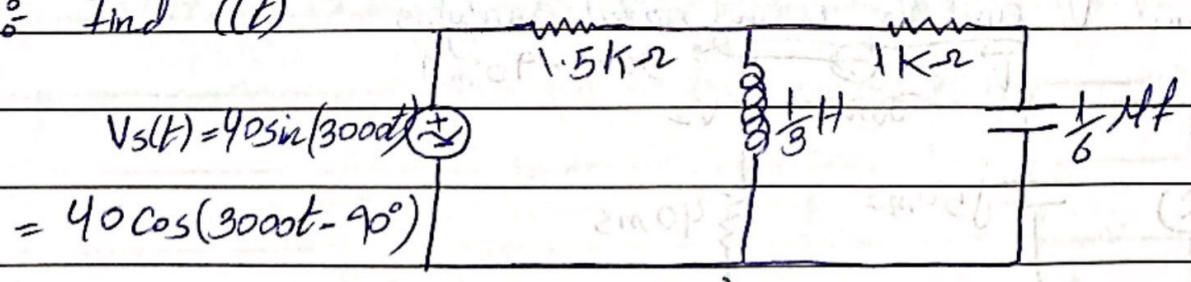

$$\vec{Z}_{eq} = (1-j2) // j+1.5$$


$$= 2 + j1.5 \text{ k}\Omega$$

$$= 2.5 \angle 36.9^\circ \text{ k}\Omega$$


$$\vec{I} = \frac{\vec{V}}{\vec{Z}_{eq}} = \frac{40 \angle -90^\circ}{2 + j1.5} = 16 \angle -126.9^\circ \text{ mA}$$

$$\vec{I}(t) = 16 \cos(3000t - 126.9^\circ) \text{ mA}$$

\vec{I} lags V by 36.9°

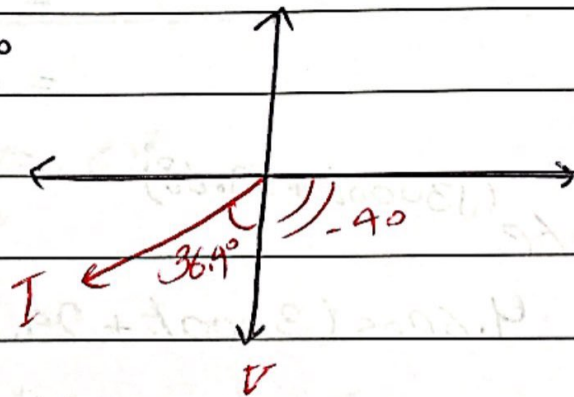

ex:- find \vec{V}_1 and \vec{V}_2 using nodal analysis

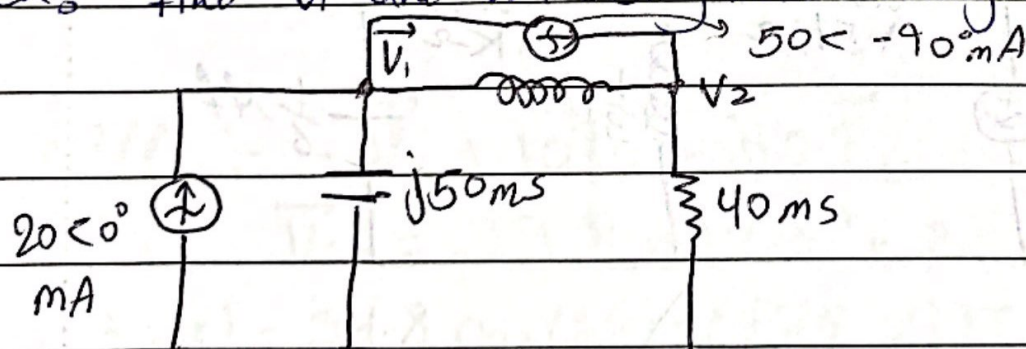

node 1 :- $-20 + \vec{V}_1(50j) + (\vec{V}_1 - \vec{V}_2)(-j25) + 50 \angle -90^\circ = 0$

$$20 + j50 = j25\vec{V}_1 + j25\vec{V}_2 \dots \textcircled{1}$$

node 2 :- $-50 \angle -90 + 40\vec{V}_2 + (\vec{V}_2 - \vec{V}_1)(-j25) = 0$

$$j50 + (40 - j25)\vec{V}_2 + j25\vec{V}_1 = 0 \dots \textcircled{2}$$

$$j25\vec{V}_1 = -j50 - (40 - j25)\vec{V}_2$$


$$20 + j50 = -j50 - (40 - j25)\vec{V}_2 + j25\vec{V}_2$$

$$60 + j100 = j50\vec{V}_2$$

$$\vec{V}_2 = \frac{(60 + j100) - j50}{j50 - j50} = \frac{j3000 + 5000}{2500} = 1.593 \angle -8^\circ$$

$$\vec{V}_1 = 1.062 \angle 23.3^\circ \text{ V}$$


ex 3:-

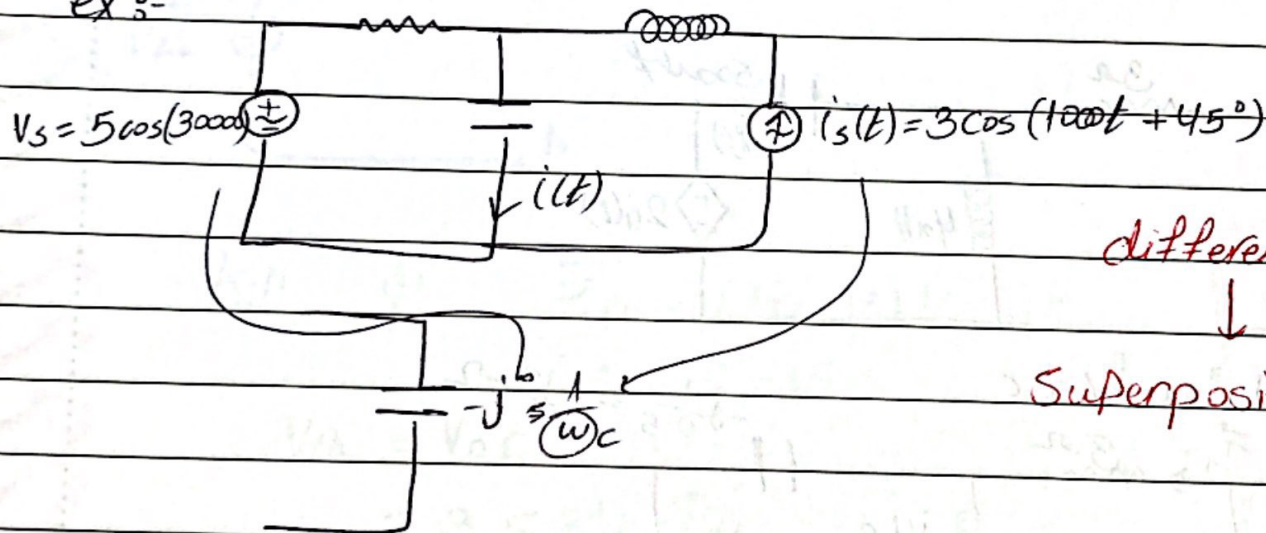

different frequency

Superposition!

So, solution is using superposition

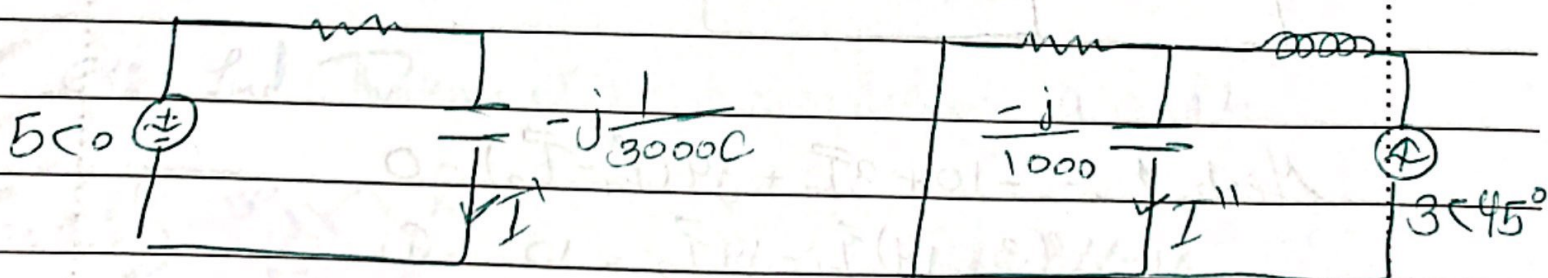

$I' \rightarrow i'(t)$ time-domain $j\omega \rightarrow s$

$I'' \rightarrow i''(t)$



$$i(t) = i'(t) + i''(t) = 5 \cos(3000t + 30^\circ) + 6 \cos(1000t + 20^\circ)$$

* 2 sources one of them is AC and the other DC
 \Rightarrow superposition.

* C in DC \rightarrow open circuit.

L in DC \rightarrow short circuit.

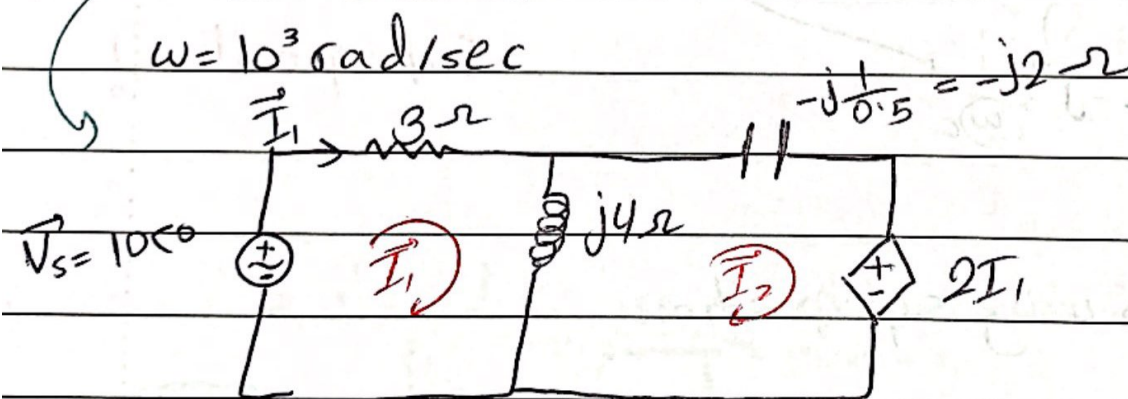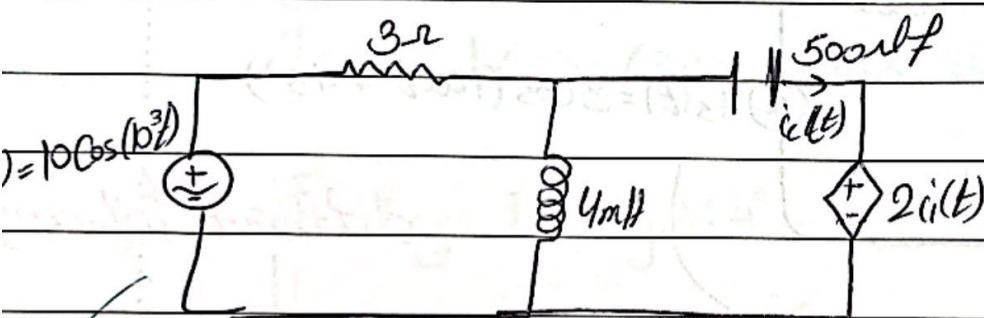ex: find $i_1(t)$ and $i_2(t)$ using mesh analysis



$$\text{Mesh 1 :- } -10 + 3\vec{I}_1 + j4(\vec{I}_1 - \vec{I}_2) = 0$$

$$(3 + j4)\vec{I}_1 - j4\vec{I}_2 = 10 \dots \text{--- (1)}$$



$$\text{Mesh 2 :- } -j2\vec{I}_2 + 2\vec{I}_1 + j4(\vec{I}_2 - \vec{I}_1) = 0$$

$$(2 - 4j)\vec{I}_1 + 2j\vec{I}_2 = 0 \dots \text{--- (2)}$$

$$\vec{I}_1 = 1.24 \angle 29.7^\circ \text{ A} \Rightarrow i_1(t) = 1.24 \cos(10^3 t + 29.7^\circ)$$

$$\vec{I}_2 = 2.77 \angle 56.3^\circ \text{ A} \Rightarrow i_2(t) = 2.77 \cos(10^3 t + 56.3^\circ) \text{ A}$$

ex: find Thevenin eq. circuit.

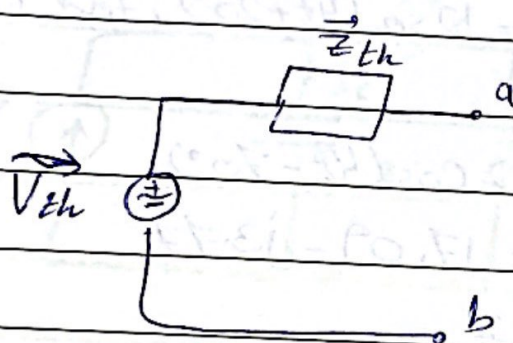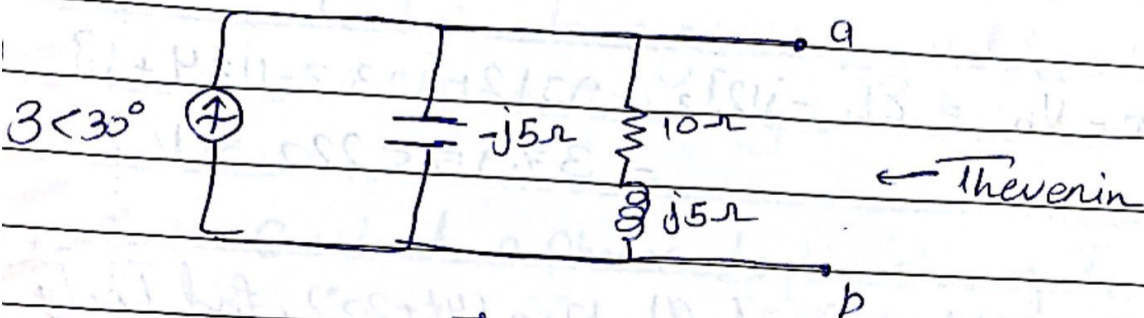


Kill \oplus $\vec{Z}_{th} = (10 + j5) \parallel -j5$
 $= 2.5 - j5 \Omega$

$$V_{th} = V_{oc}$$

$$= 3 \angle 30^\circ \times \vec{Z}_{th}$$

$$= 16.77 \angle -33.47^\circ$$

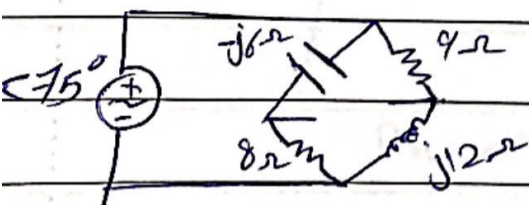ex: find Thevenin eq. circuit seen between a and b



$$\vec{Z}_{th} = 4 \parallel j12 + 8 \parallel -j6$$

$$= 6.48 - j2.64 \Omega$$

$$\vec{I}_1 = \frac{120 \angle 75^\circ}{8 - j6} = 11.64 + j2.913$$

$$\vec{I}_2 = \frac{120 \angle 75^\circ}{4 + j12} = 0.724 - j9.45$$

$$V_a = 8I_1, \quad \vec{V}_b = j12\vec{I}_2$$


$$V_{oc} = \vec{V}_a - \vec{V}_b = 8\vec{I}_1 - j12\vec{I}_2 = 93.12 + j23.3 - 113.4 + j8 \\ = 37.95 \angle 220.31^\circ \text{ V.}$$

ex:- $i_x(t) = 15 \cos(4t + 30^\circ)$, $i_y(t) = 12 \sin(4t + 20^\circ)$, find \vec{I}_x , \vec{I}_y

$$\dot{i}_y(t) = 12 \cos(4t + 20 - 90) = 12 \cos(4t - 70^\circ)$$

$$15 \angle 30^\circ + 12 \angle -70^\circ = 17.09 - j3.77 \\ = 17.5 \angle -12^\circ$$

$$17.5 \cos(4t - 12^\circ)$$

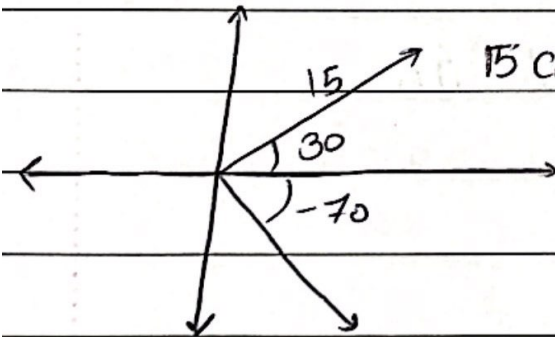


$$15 \cos 30^\circ + j15 \sin(30^\circ)$$

$$12 \cos(-70^\circ) + j12 \sin(-70^\circ)$$


* Phasor Diagram

↳ it provides a graphical method for solving certain problems which may be used to check more exact methods.

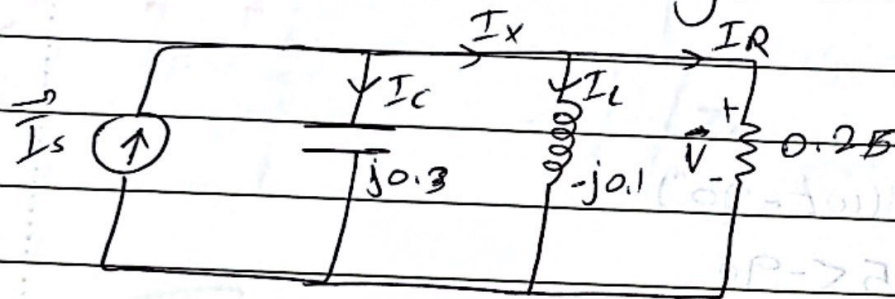ex: Construct a phasor diagram showing $\vec{I}_R, \vec{I}_L, \vec{I}_C, \vec{I}_s, \vec{I}_x, \vec{V}$




Let $\vec{V} = 1 \angle 0^\circ$

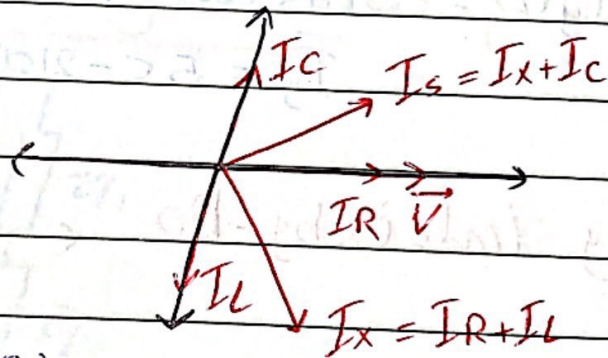


~~Go make sure :-~~

ex: $V_x = 3 \cos(\omega t + 45^\circ)$

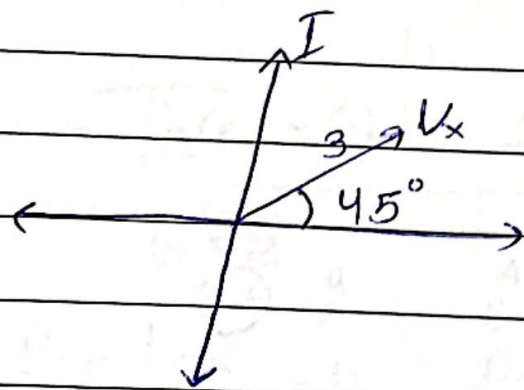


Phasor diagram.

time domain

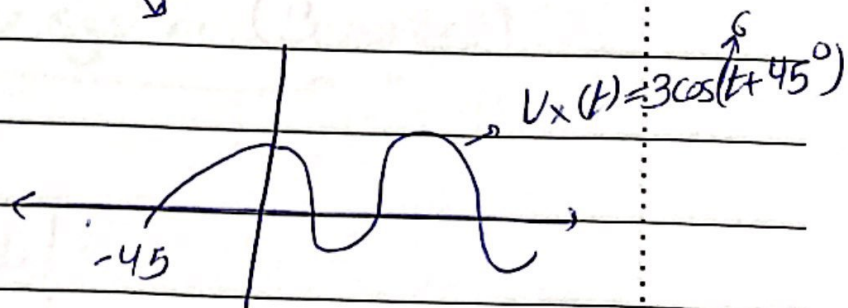

ex: Draw i_x in phasor diagram

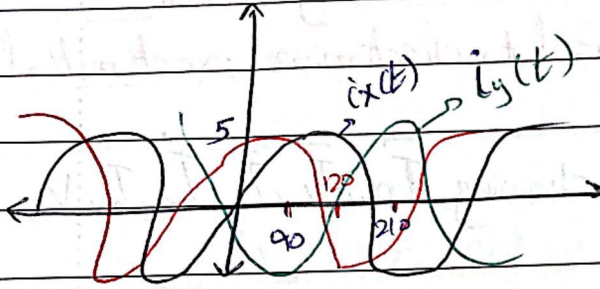


$$i_x(t) = 5 \cos(\omega t - 90^\circ)$$

$$\vec{I}_x = 5 \angle -90^\circ$$

$$i_y(t) = 5 \cos(\omega t - 210^\circ)$$

$$\vec{I}_y = 5 \angle -210^\circ$$

I_y leads i_x by -120

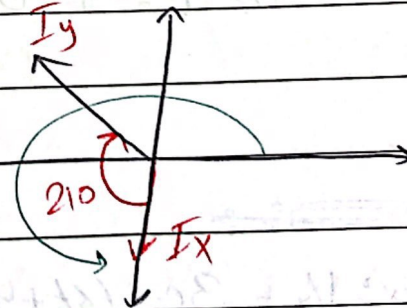


Three-phase Systems.


25

- Single phase system (1 angle)


- system
- 1) source
- 2) load
- 3) wire

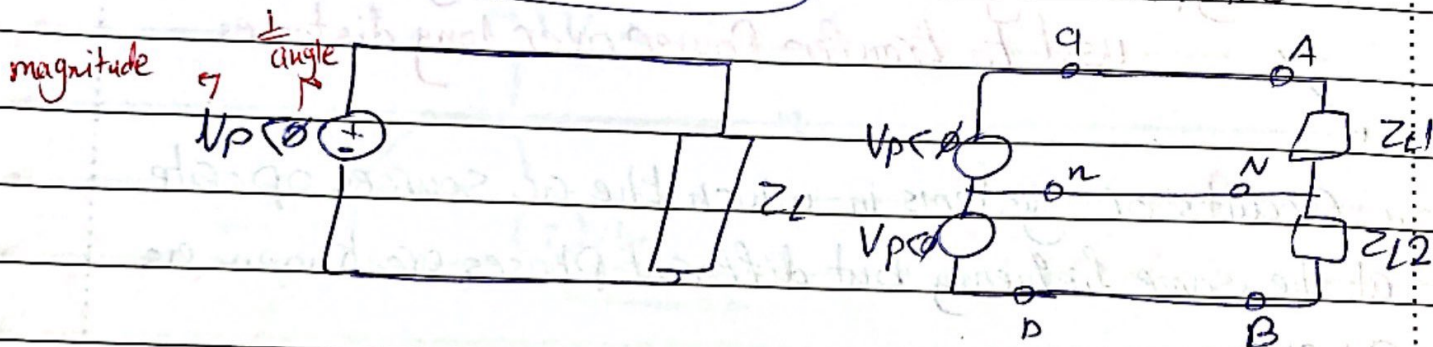

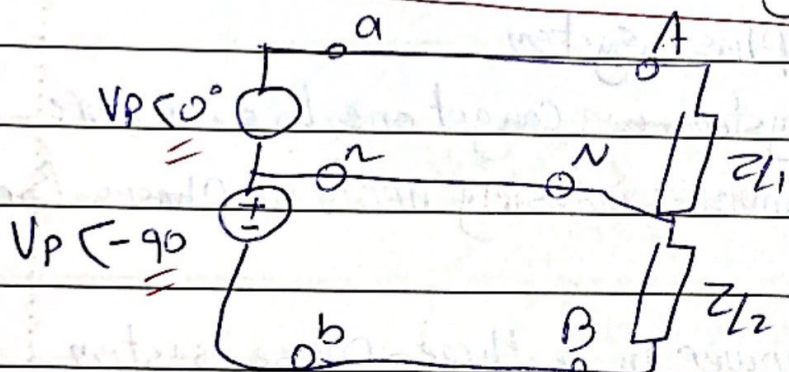- Two-phase Three-wire system (two angles)



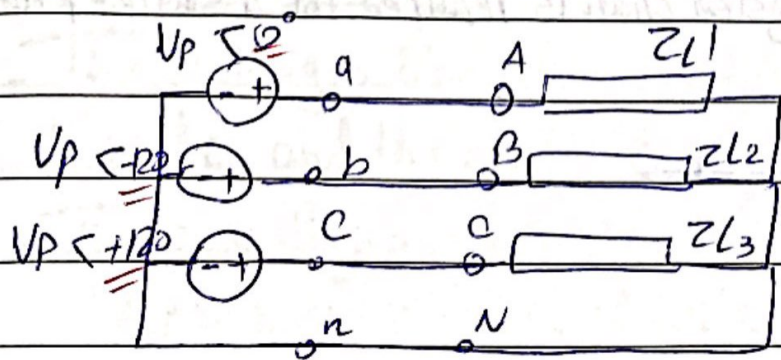- Three-phase four-wire system (3 angles)



* Single phase system \rightarrow 1 angle (used for light loads) like lighting and heating.

* Polyphase systems \rightarrow more than 1 angle.
used to transfer power over long distances.


* Circuits or systems in which the ac sources operate at the same frequency but different phases are known as Polyphase.

* Advantages of Three-phase system


- 1- From three-phase system, we can get one, two, or more than three phases (aluminum industry needs 48 phases for melting).
- 2- The instantaneous power in a three-phase system can be constant (not pulsating)
- 3- Less material is needed to deliver the same power with a three-phase system than is required for a single-phase system.

~~So we will study it in this~~


Three-Phase Voltages

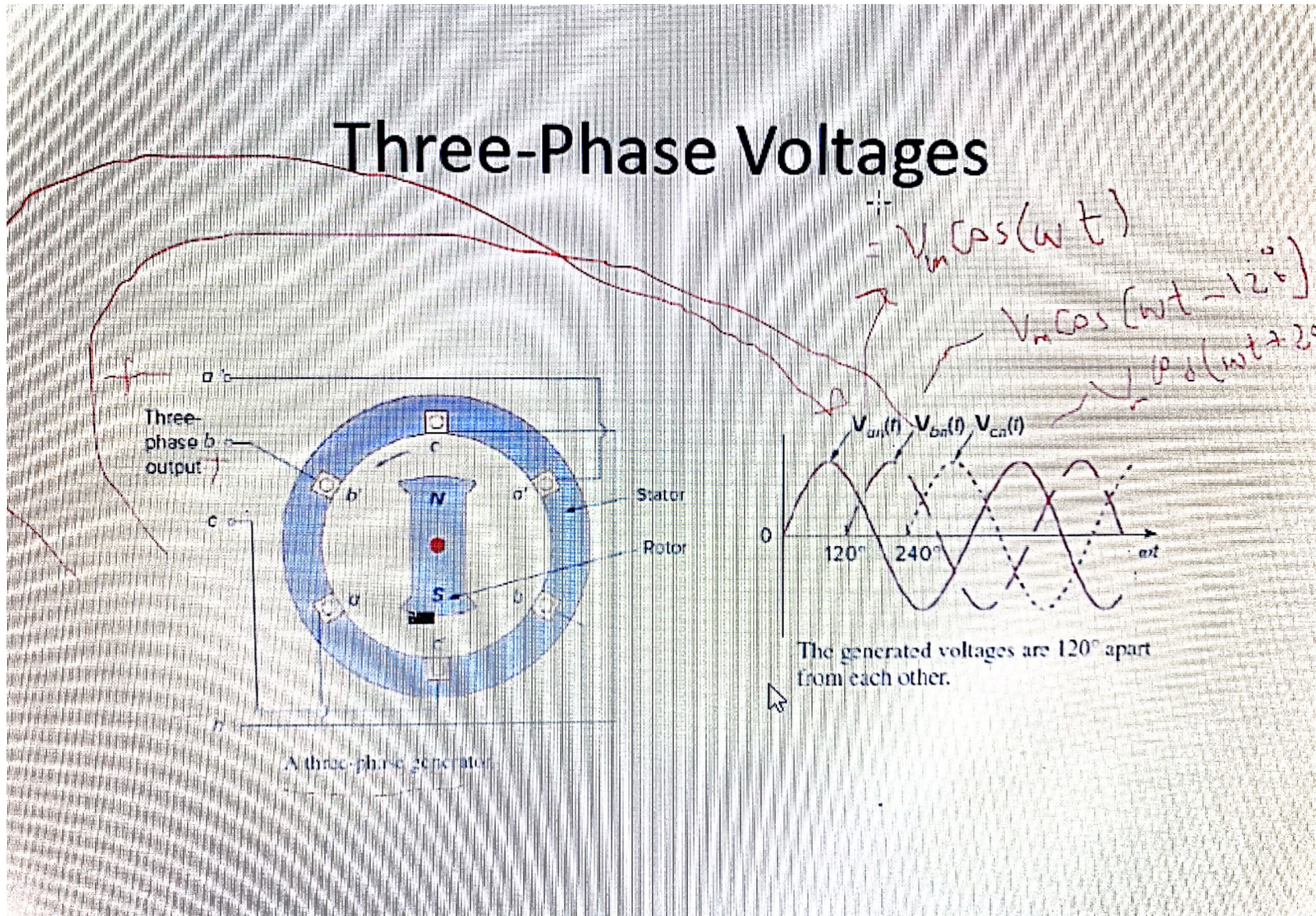

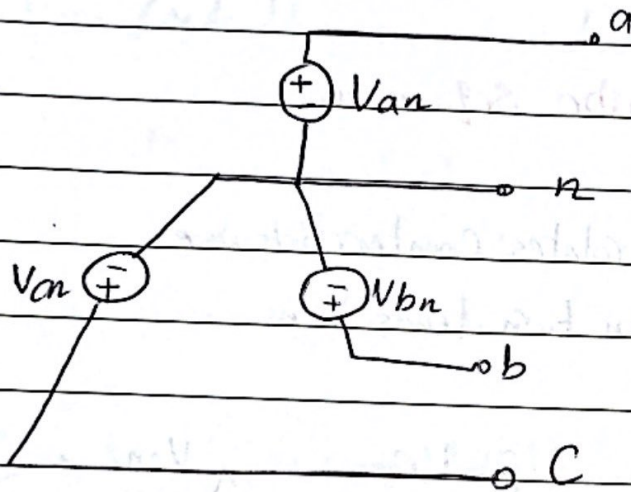* Three-phase system (generator) is equivalent to three single-phase circuits.



Y-connected.
4 wires

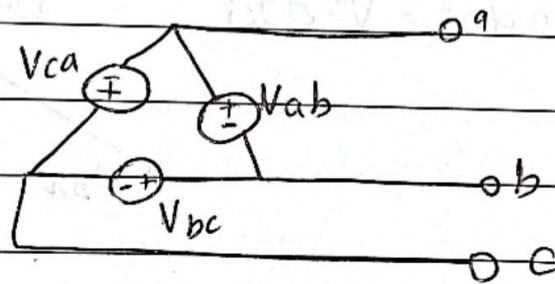

Δ-connected.
3 wires

* Balanced Three-phase Voltages.

- The voltages V_{an} , V_{bn} , V_{cn} are respectively between lines a, b and c, and the neutral line n.

- These voltages are called phase voltages.

- If the voltage source have the same amplitude and frequency ω and are out of phase with each other by 120° , the voltages are said to be balanced. (Balanced three-phase voltages.)

$$\begin{aligned}
 V_{an} + V_{bn} + V_{cn} &= V_p \angle 0^\circ + V_p \angle 120^\circ + V_p \angle 120^\circ \\
 &= V_p (1.0 - 0.5 - j0.866 - 0.5 + j0.866) \\
 &= 0
 \end{aligned}$$

- Positive sequence or abc sequences


- Produced when the rotor rotates counterclockwise
- V_{an} leads V_{bn} , which in turn leads V_{cn}

$$V_{an} = V_p \angle 0$$

$$V_p = V_{rms}$$

$$V_{bn} = V_p \angle -120$$

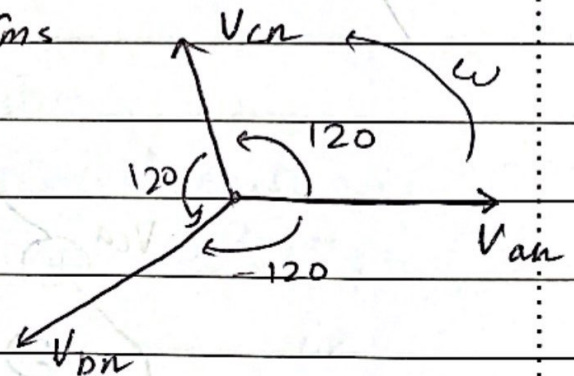
$$V_{cn} = V_p \angle -240^\circ = V_p \angle 120^\circ$$



- As the phasors rotate in the counterclockwise direction with frequency ω , they pass through the horizontal axis in a sequence abcabc... Thus, the sequence is abc or bca or cab.

* Negative sequence or acb sequence

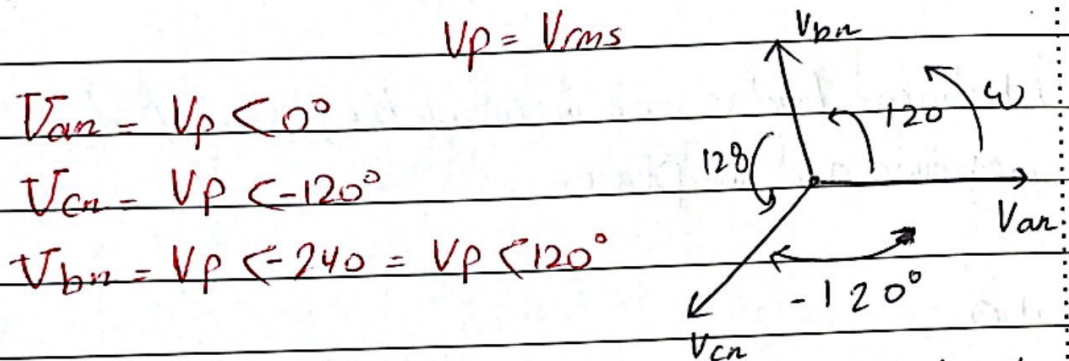- Produced when the rotor rotates clockwise
- V_{an} leads V_{cn} , which in turn leads V_{bn}



- For the phasors, as they rotate in the counter clockwise direction, they pass the horizontal axis in a sequence acb. --- This describes the acb sequence.

ex = Determine the phase sequence of the set of voltages.

$$V_{an} = 200 \cos(\omega t + 10^\circ)$$

$$V_{bn} = 200 \cos(\omega t - 230^\circ), \quad V_{cn} = 200 \cos(\omega t - 110^\circ)$$

Solution :- The voltages can be expressed in phasor form as:

$$V_{an} = 200 \angle 10^\circ \text{ V}, \quad V_{bn} = 200 \angle -230^\circ \text{ V}$$

$$V_{cn} = 200 \angle -110^\circ \text{ V}$$

We notice that V_{an} leads V_{cn} by 120° and V_{cn} in turn leads V_{bn} by 120° ,



So, we have an acb sequence.

b.

* Three-phase Balanced Load

- Three phase load can be either Y-connected or delta-connected depending on the end application.

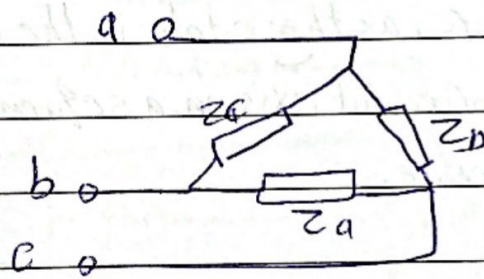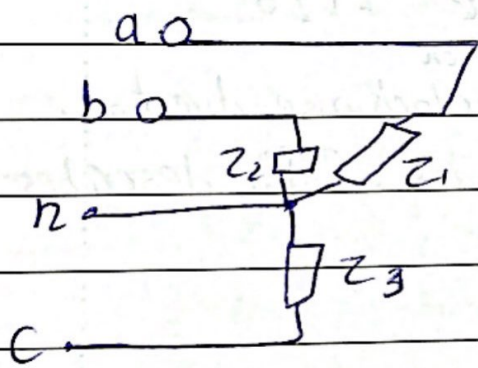- A balanced load is one in which the phase impedances are equal in magnitude and in phase.



$$Z_a = Z_b = Z_c = Z_\Delta$$

$$Z_1 = Z_2 = Z_3 = Z_Y$$


$$Z_Y = \frac{1}{3} Z_\Delta$$

* Possible connection between sources and loads.

- 1) Y-Y connection. ex :- (Y-connected source with a Y-connected load).
- 2) Y- Δ connection
- 3) Δ - Δ connection
- 4) Δ -Y connection.

Balanced Y-Y Connection

26

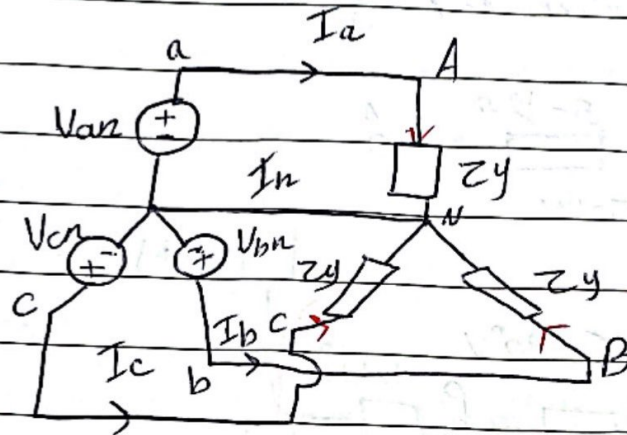

Currents :- line current
Phase current.

Line Current = Phase Current

$$Z_y = Z_s + Z_l + Z_r$$

* Assuming the positive sequence :-

Connection
Y-Y

Phase Voltage/Currents

Line V/I

$$V_{an} = V_p \angle 0^\circ \times \sqrt{3} + 3^\circ, \quad V_{ab} = \sqrt{3} V_p \angle 30^\circ$$

$$V_{bn} = V_p \angle -120^\circ, \quad V_{bc} = V_{ab} \angle -120^\circ$$

$$V_{cn} = V_p \angle +120^\circ, \quad V_{ca} = V_{ab} \angle +120^\circ$$

same as line

currents.

$$I_a = V_{an} / Z_y$$

$$I_b = I_a \angle -120^\circ$$

$$I_c = I_a \angle +120^\circ$$

if (-) sign

$$\frac{V_{bn}}{Z_y}$$

$$\frac{V_{cn}}{Z_y}$$


$$I_a + I_b + I_c = 0$$

$$I_n = -(I_a + I_b + I_c) = 0$$

$$V_{nN} = Z_n I_n = 0$$

The ~~neutral~~ neutral line can thus be removed without affecting the system.

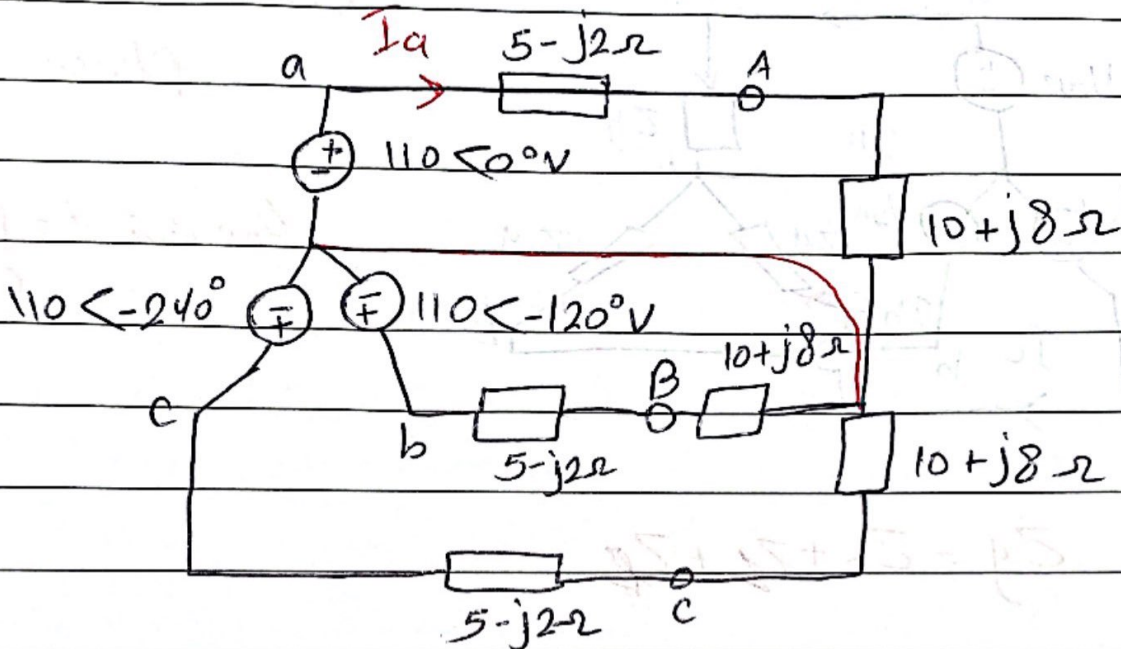Example :- Calculate the line currents in the three-wire Y-Y system.



$$Z_y = (5 - j2) + (10 + j8) = 15 + j6 = 16.155 \angle 21.8^\circ$$

$$I_a = \frac{110 \angle 0^\circ}{16.155 \angle 21.8^\circ} = 6.81 \angle -21.8^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 6.81 \angle -141.8^\circ \text{ A}$$

$$I_c = I_a \angle -240^\circ = 6.81 \angle -261.8^\circ \text{ A} = 6.81 \angle 98.2^\circ \text{ A}$$

↓
+120°

Parallel and Series Resonance

- Resonance occurs in any system that has a complex conjugate pair of poles; it is the cause of oscillations of stored energy from one to another.


- The concept of resonance applies in several areas of science and engineering.

- Resonance occurs in any circuit that has at least one inductor and one capacitor.

- Resonance is a condition in an RLC circuit in which the capacitive and inductive reactances are equal in magnitude, thereby in a purely resistive impedance.

- Resonant circuit (series or parallel) are useful for constructing filters as their transfer functions can be highly frequency selective. They are used in many applications such as selecting the desired stations in radio and TV receivers.

Series Resonant RLC circuit

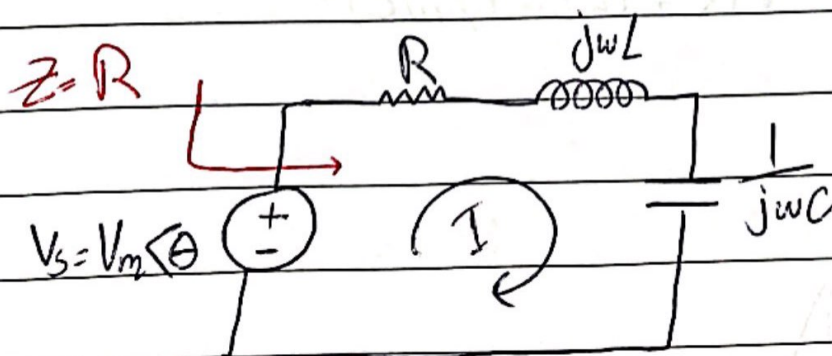

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

Resonance results when imaginary part of the transfer function is zero, or

$$\text{Im}(Z) = \omega L - \frac{1}{\omega C} = 0$$

The value of ω that satisfies this condition is called the resonant frequency ω_0 . Thus, the resonance condition is


$$\omega_0 L = \frac{1}{\omega_0 C} \quad \text{or} \quad \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

Since $\omega_0 = 2\pi f_0$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

The current amplitude versus frequency for the series RLC circuit

$$I = |I| = \frac{V_m}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

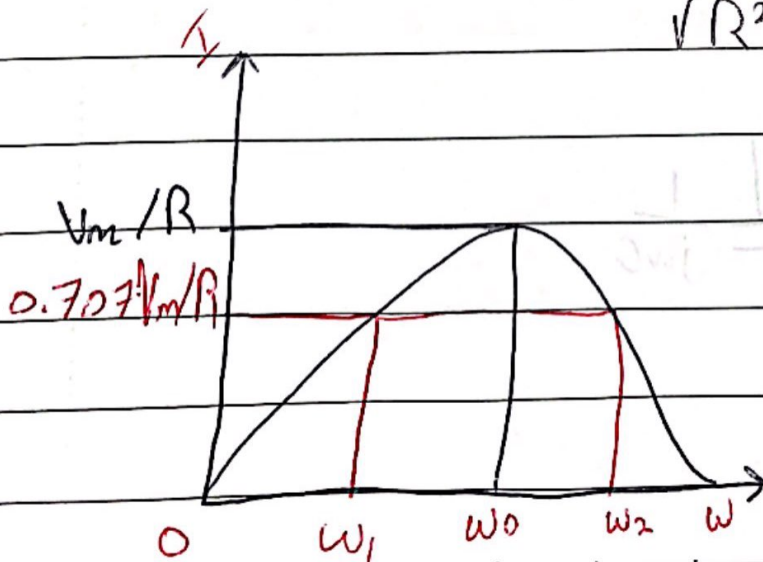

* The average power dissipated by the RLC circuit

$$P(\omega) = \frac{1}{2} I^2 R$$

* The highest power dissipated occurs at resonance, when $I = V_m/R$ so that

$$P(\omega_0) = \frac{1}{2} \frac{V_m^2}{R}$$

* At certain frequencies $\omega = \omega_1, \omega_2$, the dissipated power is half the maximum value; that is

$$P(\omega_1) = P(\omega_2) = \frac{(V_m/\sqrt{2})^2}{2R} = \frac{V_m^2}{4R}$$

Hence, ω_1 and ω_2 are called the half power frequencies.

$$\text{Bandwidth} = \omega_2 - \omega_1$$


* average power on inductor or capacitor = 0

$$\omega_1 = \frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

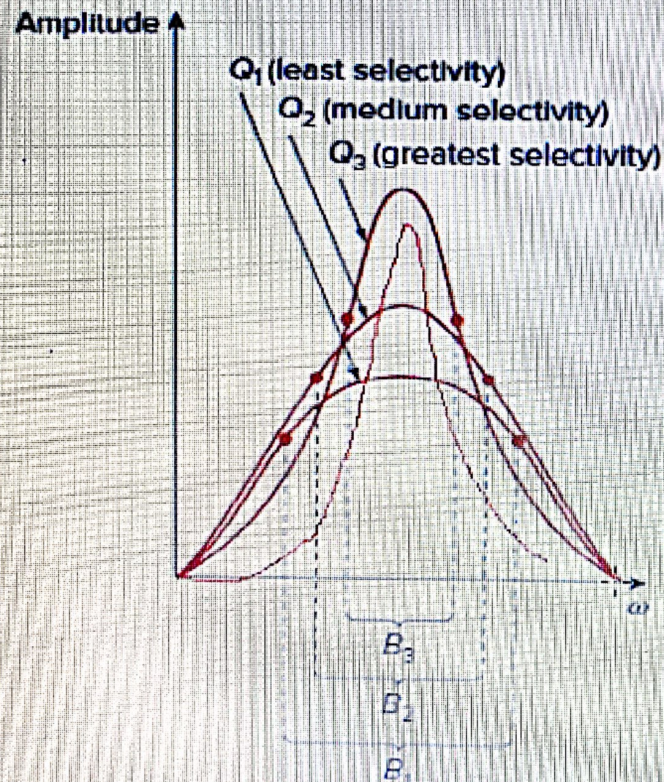- The “sharpness” or selectivity of the resonance in a resonant circuit is measured quantitatively by the quality factor Q



The higher the circuit Q , the smaller the bandwidth.

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$

$$B = \frac{R}{L} = \frac{\omega_0}{Q}$$

Quality factor Q

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR}$$


sharp response

$$B = \frac{R}{L} = \frac{\omega_0}{Q}$$

✓ The higher the circuit Q , the smaller the bandwidth.

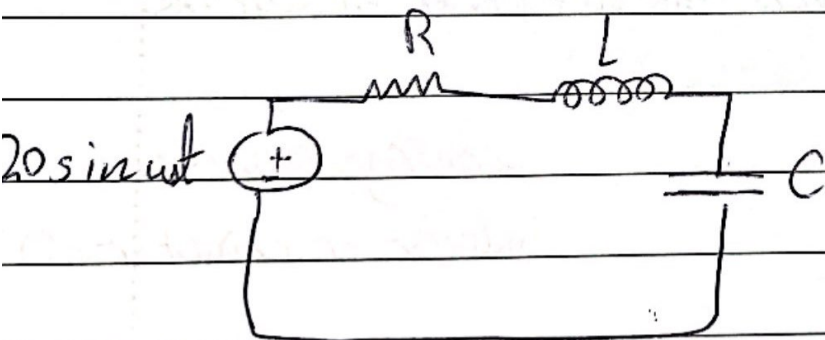Example 2: In the circuit $R = 2 \Omega$, $L = 1 \text{ mH}$, $C = 0.4 \mu\text{F}$

- Find the resonant frequency and half power frequencies.
- Calculate the quality factor and bandwidth.
- Determine the amplitude of the current at ω_0 , ω_1 , ω_2



$$a) \omega_0 = \frac{1}{\sqrt{LC}} = 50 \text{ krad/s}$$

Solution:

(a) The resonant frequency is

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 0.4 \times 10^{-6}}} = \underline{50 \text{ krad/s}}$$

■ **METHOD 1** The lower half-power frequency is

$$\begin{aligned} \rightarrow \omega_1 &= -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \\ &= -\frac{2}{2 \times 10^{-3}} + \sqrt{(10^3)^2 + (50 \times 10^3)^2} \\ &= -1 + \sqrt{1 + 2500} \text{ krad/s} = \underline{49 \text{ krad/s}} \end{aligned}$$

Similarly, the upper half-power frequency is

$$\omega_2 = 1 + \sqrt{1 + 2500} \text{ krad/s} = \underline{51 \text{ krad/s}}$$

(b) The bandwidth is

$$B = \omega_2 - \omega_1 = 2 \text{ krad/s}$$

or

$$B = \frac{R}{L} = \frac{2}{10^{-3}} = 2 \text{ krad/s}$$

The quality factor is

$$Q = \frac{\omega_0}{B} = \frac{50}{2} = 25$$

■ **METHOD 2** Alternatively, we could find

$$Q = \frac{\omega_0 L}{R} = \frac{50 \times 10^3 \times 10^{-3}}{2} = 25 \quad \checkmark$$

From Q , we find

$$B = \frac{\omega_0}{Q} = \frac{50 \times 10^3}{25} = 2 \text{ krad/s} \quad \checkmark$$

Since $Q > 10$, this is a high- Q circuit and we can obtain the half-power frequencies as

$$\omega_1 = \omega_0 - \frac{B}{2} = 50 - 1 = 49 \text{ krad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 50 + 1 = 51 \text{ krad/s}$$

as obtained earlier.


(c) At $\omega = \omega_0$,

$$I = \frac{V_m}{R} = \frac{20}{2} = 10 \text{ A}$$

At $\omega = \omega_1, \omega_2$,

$$I = \frac{V_m}{\sqrt{2} R} = \frac{10}{\sqrt{2}} = 7.071 \text{ A}$$

* Parallel Resonant RLC circuit

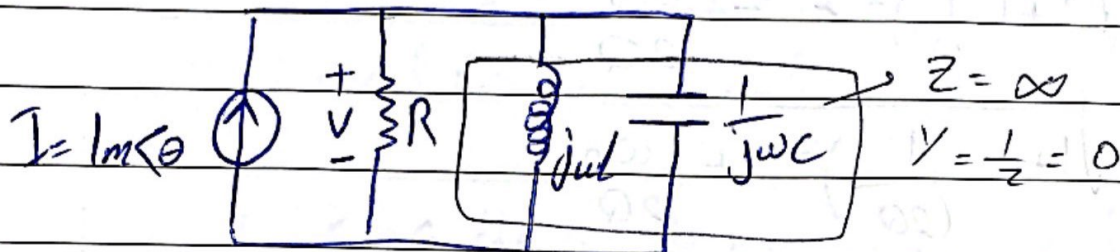


$$Y = \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$$

Resonance occurs when the imaginary part of

$$Y = \text{zero}$$

$$\omega C - \frac{1}{\omega L} = 0$$
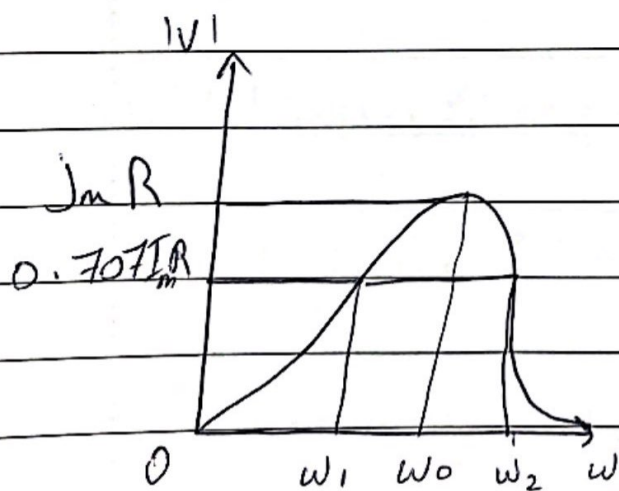
$$\text{or } \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$



$$\omega_1 = \frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$B = \omega_2 - \omega_1 = \frac{1}{RC}$$

Bandwidth

$$Q = \frac{\omega_0}{B} = \omega_0 RC = \frac{R}{\omega_0 L}$$

$$\omega_1 = \omega_0 \sqrt{1 + \left(\frac{1}{Q}\right)^2} - \frac{\omega_0}{2Q}$$

$$\omega_2 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} + \frac{\omega_0}{2Q}$$

Summary of the characteristics of resonant *RLC* circuits.

Characteristic	Series circuit	Parallel circuit
Resonant frequency, ω_0	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
Quality factor, Q	$\frac{\omega_0 L}{R}$ or $\frac{1}{\omega_0 RC}$	$\frac{R}{\omega_0 L}$ or $\omega_0 RC$
Bandwidth, B	$\frac{\omega_0}{Q}$	$\frac{\omega_0}{Q}$
Half-power frequencies, ω_1, ω_2	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$
For $Q \geq 10$, ω_1, ω_2	$\omega_0 \pm \frac{B}{2}$	$\omega_0 \pm \frac{B}{2}$

Filters

28

- A filter is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others.

- Filters are the circuits used in radio and TV receiver to allow us to select one desired signal out of multitude of broadcast signals in the environment.

- A filter is passive filter if it consists of only passive elements R, L, C . It is said to be an active filter if it consists of active elements (such as transistors and op amps) in addition to passive elements R, L, C .





- Types of passive filters:-

1- A low-pass filter passes low frequencies and stops high frequencies.

2. A high-pass filter passes high frequencies and rejects low frequencies.

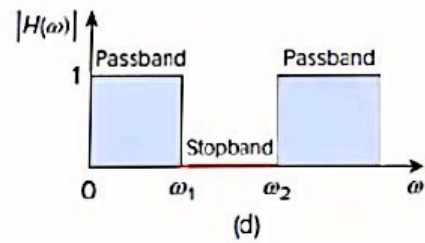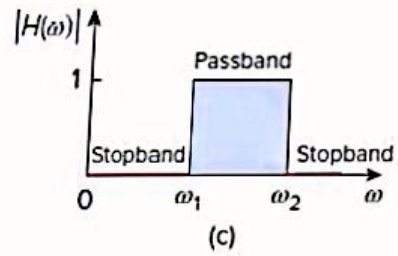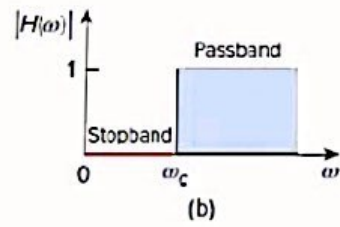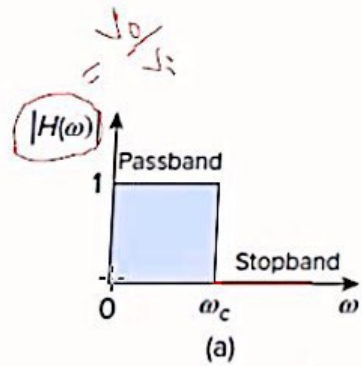3. A band-pass filter pass frequencies within a frequency band and blocks or attenuates frequencies outside the band.

4- A band-stop filter passes frequencies outside a frequency band and blocks or attenuates frequencies within the band.





Low-Pass Filter

$$\mathbf{H}(\omega) = \frac{V_o}{V_i} = \frac{1/j\omega C}{R + 1/j\omega C}$$
$$\mathbf{H}(\omega) = \frac{1}{1 + j\omega RC}$$

$$H(\omega_c) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{1}{RC}$$

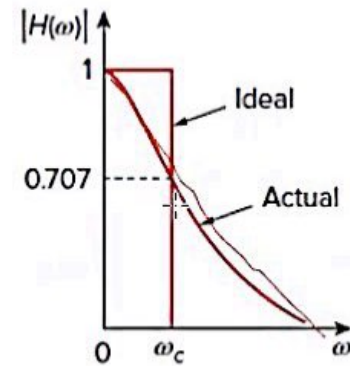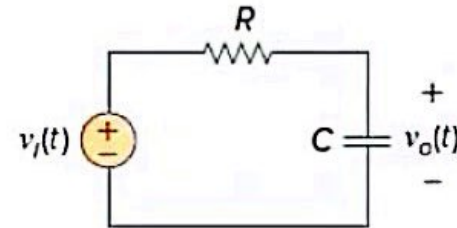ω_c : cutoff frequency or rolloff frequency





High-Pass Filter

$$\mathbf{H}(\omega) = \frac{V_o}{V_i} = \frac{R}{R + 1/j\omega C}$$

$$\mathbf{H}(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

$$\omega_c = \frac{1}{RC}$$

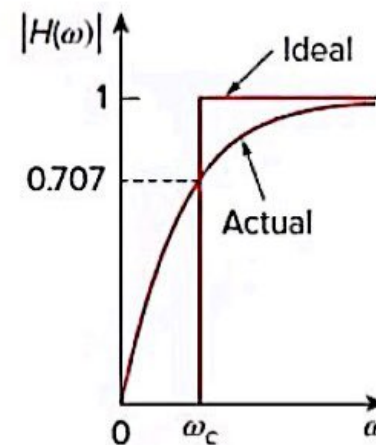
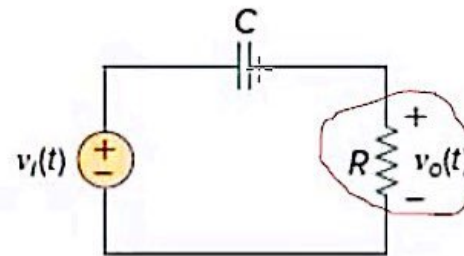


Band-Pass Filter

$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + j(\omega L - 1/\omega C)}$$

+

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

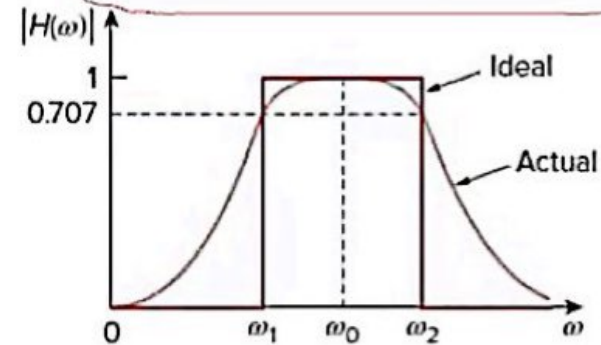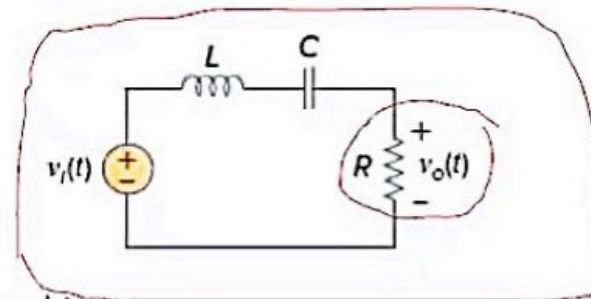

Band-Stop Filter

$$H(\omega) = \frac{V_o}{V_i} = \frac{j(\omega L - 1/\omega C)}{R + j(\omega L - 1/\omega C)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

