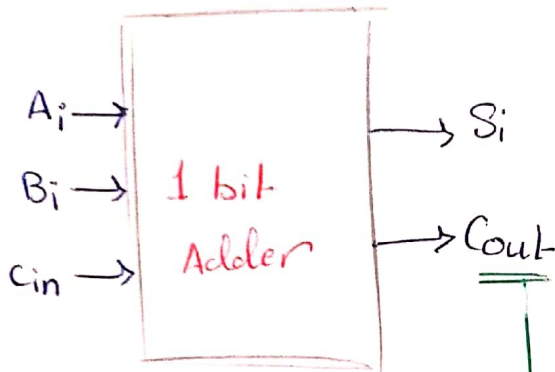


[ Adders are example for Iterative combinational circuits ]

[ 4 bits + 4 bits = 5 bits ]

ال carry لا خير راج يكون  
جزء من الجواب ✓




it will become  
the  $C_{in}$  (the carry)  
for the next adder  
if exists ✓

$A_i$	$B_i$	$C_{in}$	$S_i$	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

After doing the k-map, and performing equations we find a

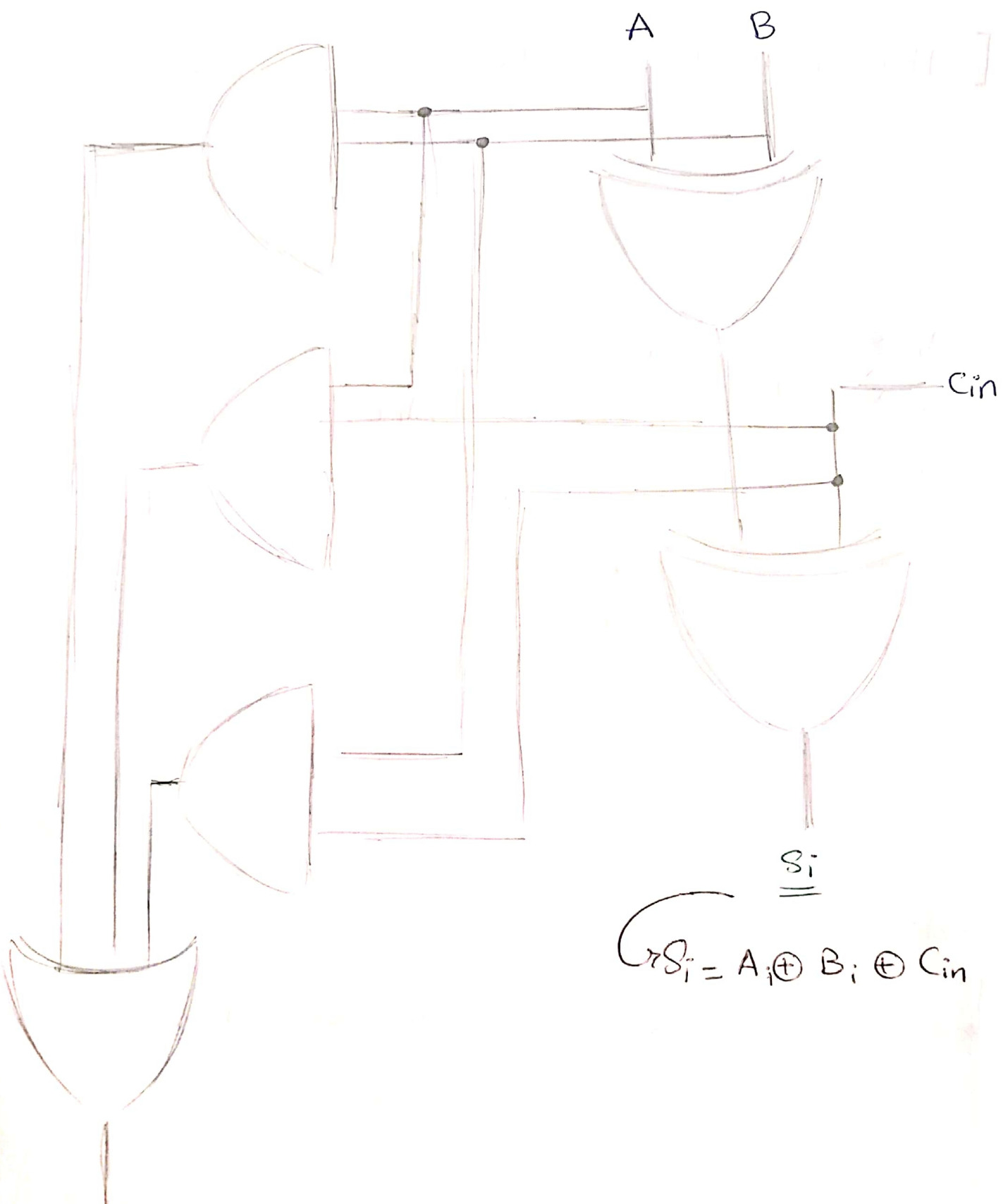↳  $S_i$  (sum equation) = XOR function / the odd function ✓  
 $= A_i \oplus B_i \oplus C_{in}$   
 $C_{in} = \text{And gates} \checkmark$



Cout  $\rightarrow A_i B_i + A_i C_{in} + B_i C_{in}$


Si  
 $S_i = A_i \oplus B_i \oplus C_{in}$

[ you do the single bit adder  
 then you design the vector

Single bit  $\rightarrow$  HALF ADDER 2 input-bit addition block  
 $\rightarrow$  FULL ADDER 3 input-bit addition block

[(HA) helps to design the (FA) circuit with less cost]


HAIF ADDER design:

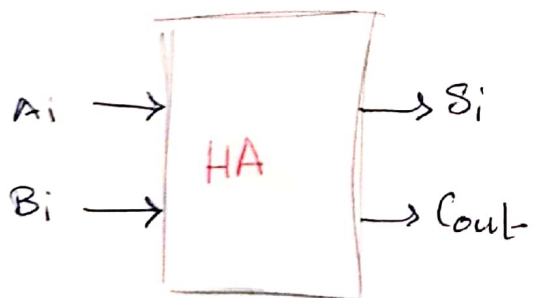

$A_i$	$B_i$	$S_i$	$C_{out}$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S_i = A_i \oplus B_i$$

$$C_{out} = A_i B_i \quad \checkmark$$

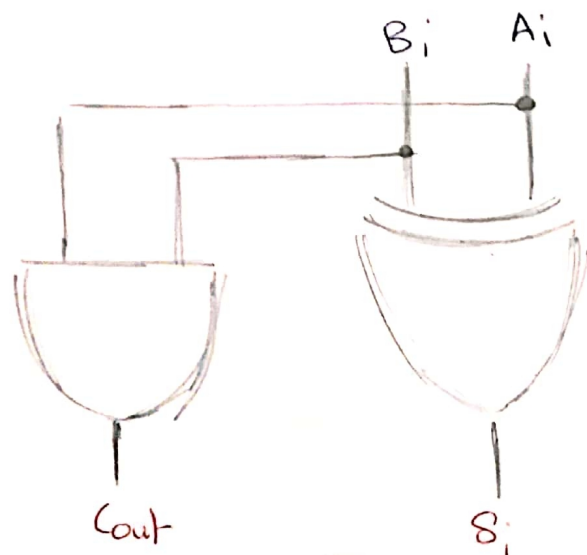


الطريقة بين ال FA وال HA ~~منه~~ من ثلاثه اى باحري

FA equations

$$S_i = A_i \oplus B_i \oplus C_{in}$$

$$C_{out} = A_i B_i + A_i C_{in} + B_i C_{in} = A_i B_i + C_{in} (A_i \oplus B_i)$$

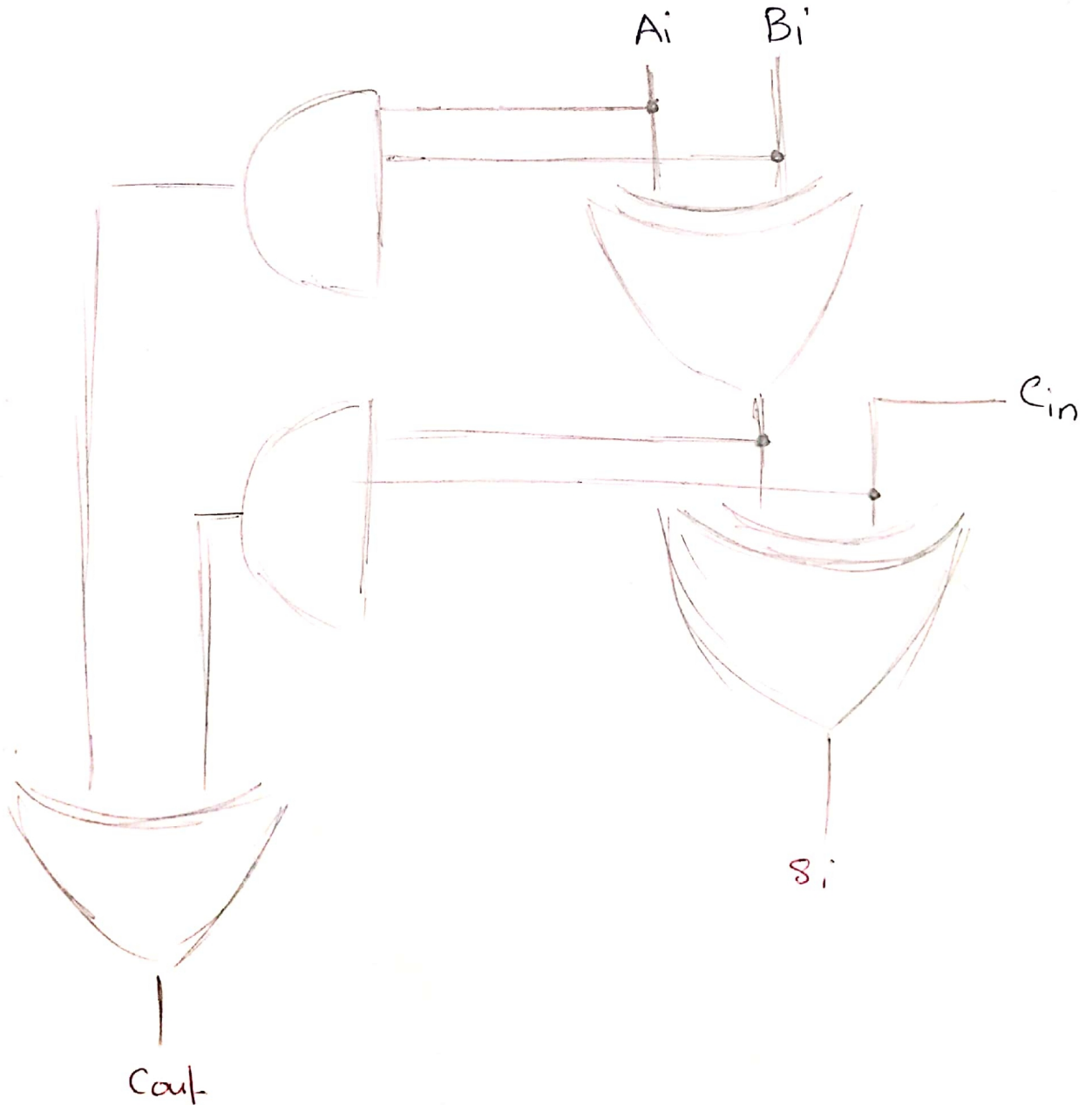
لصاى صاى ال HA الكيفية بال sum بنسختهها عسنة نقل عدال  
And Gates



[After Designing the internal adder block you design the vector (Ripple-carry Adder)]

✓ الـ Cout الى خارج block ، بصير الـ cin للبلوك اللي بعده

4-bit Ripple-Carry Adder :-

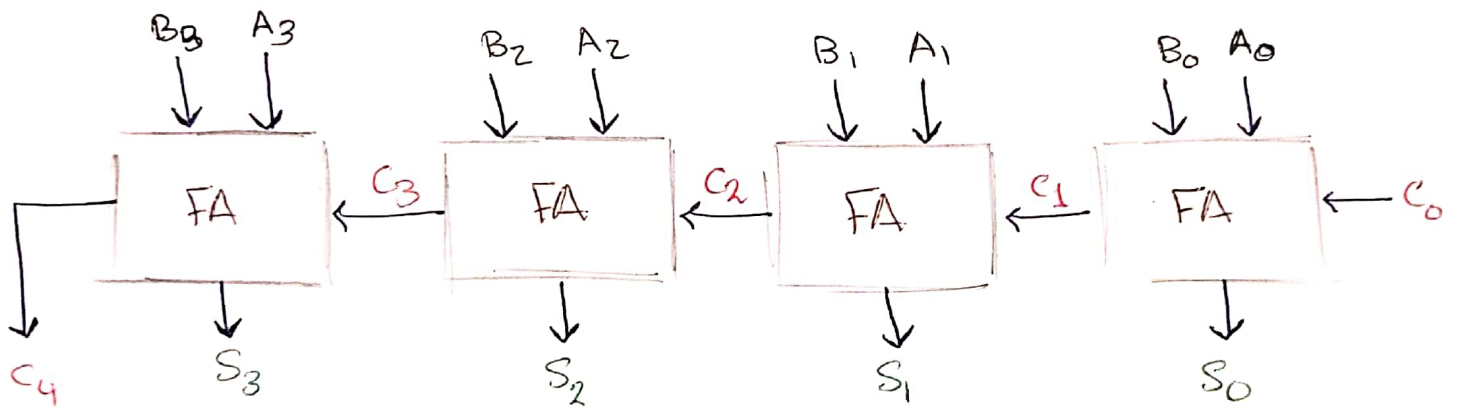

# [Subtraction]

$$\begin{array}{r} N - \\ \underline{M} \end{array}$$

↳ if  $N < M$  → do the subtraction and the dummy borrow

② do the correction.

## [To Summarize]

end borrow = 1

$$(N < M)$$

→ do the subtraction with dummy borrow

and will result →  $(N - M) + 2^n$

→ do the correction

$$2^n - (N - M) + 2^n$$

and will result the negative number ✓

end borrow = 0

$$(N \geq M)$$

→ do the subtraction normally, for a positive answer

## [The Complements]

↳ Diminished Radix Complement

→ you simply take the complement to the max number

also

$$(r-1)'s = r^n - 1 - N$$

↳ Radix complement.

→ find the  $(r-1)$ 's comp. then add 1

also

$$r's = r^n - N$$

## → Binary Complements

(r-1)'s → only flip the bits

① 1's complement can be found by NOT (inverter)

② 2's → 1's + 1

or use the fast method  $\left[ \begin{array}{l} \text{تسبب الأرقام بعد أول (1) تعبير} \\ \text{بقلب باقي ال (bits)} \end{array} \right]$

Subtraction

علاقة ال complement بال

لـ سحري حرقه حرقه للخرج

$$N - M = N + 2's \text{ of } M$$

needs correction

↳ find 2's M and add it to N

↳ the end carry will be 0

↳ the correction is done as follows:

find the 2's for the result and make it negative.

does not need correction

↳ find 2's M and add it to N

↳ the end carry will be 1 and won't be taken with the result.

↳ the result should be taken as is.