

## Gate Delay

the delay between an input change(s) and the resulting output change. ( $t_G$ )

it can be represented by timing diagram.

For truth table such that

A	B	C	D	F
---	---	---	---	---

D is the least digit

A is the most digit.  $\rightarrow$  truth tables are unique

The boolean expression

such  $\rightarrow x + \bar{y}z$

The boolean function

$$F = x + \bar{y}z$$

Precedence

$\rightarrow$  parentheses

$\rightarrow$  NOT

$\rightarrow$  AND

$\rightarrow$  OR

\* Truth tables are unique, expressions and logic diagrams are not.  
flexibility for implementation.

# Identities

## Basic

(+) و (.) جداول

$x+0 = x$	$x \cdot 1 = x$ $x \cdot 0 = 0$ $x \cdot x = x$ $x \cdot \bar{x} = 0$	$\bar{\bar{x}} = x$
$x+1 = 1$		
$x+x = x$		
$x+\bar{x} = 1$		

## Other important

$x+y = y+x$	$(x+y)+z = x+(y+z)$ $(x \cdot y) \cdot z = x \cdot (y \cdot z)$	$x \cdot (y+z) = (x \cdot y) + (x \cdot z)$ $x+(y \cdot z) = (x+y) \cdot (x+z)$
$x \cdot y = y \cdot x$		

## DeMorgan's ✓

$\overline{x+y} = \bar{x} \cdot \bar{y}$  ✓

$\overline{x \cdot y} = \bar{x} + \bar{y}$  ✓

## Theorems

### Minimization

$xy + \bar{x}y = y$  ← عادل مشترك

### Absorption

$x + xy = x$

مهمين للبراهين والتبسيط ✓

### Simplification

توزيع على الطرفين  $x + \bar{x}y = x+y$

### Consensus

(اجماع)

$xy + \bar{x}z + yz = xy + \bar{x}z$

## converting function to SOM or POM

→ use the truth table. → use boolean algebra.

### Sum of Product (SOP)

- logical sum of AND terms that are not necessarily represented as minterms.
- SOP often represent a simplified. expression of SOM.

Special case: (weird)

$$F(A, B, C, D) = \bar{A}\bar{B}CD = \Delta(\text{SOM})$$

چاڳا ڪنڊ عدد ڪم ۾ رکيل، وڃي ڄاڻ ۾ اڙيڻ  
متغيرن، بصري ڪم ۾ بغير تبديل  
ٿيڻ وڃي. (اصل ۾ SOM)

← ڪنڊ ڪم ۾ ڪم ۾، اڄ ڪم ۾ بصري  
لما ڪم ۾ (POM) و ڪم ۾ ڪم ۾ ڪم ۾.  
و ڪم ۾ بصري ڪم ۾ المتغيرن ٿيڻ وڃي.

### Product of Sum (POS)

Same Idea of (SOP)

Special case: (weird)

$$F(A, B, C) = (\bar{A} + B + C) \Rightarrow \text{(POM)}$$

COST  $\Rightarrow$  it can be found by L, G, GN

Karnaugh maps (K-Maps) → simplify  
→ optimize  
→ derive POS from SOP

5

↳ each square represent a minterm.

↳ Grey code

↳ prime implicants + essential prime implicants

Don't cares :-  $\Sigma d(-, -, -)$

① cases:

- input values for the minterm will never occur
- output value for the minterm is not used.

② it helps to lower the cost of logic circuit

\* it appears when using ~~BDD~~ BCD to design a logic circuit and such thing.

deriving POS

→ first find  $\bar{F}$  by evaluation zeros-rectangles

→ derive  $F$  as POS by doing duality the complementing it  
↳ when there is don't-cares they're combined with zeros in their rectangles

دقيق تشيزه  
 ويصحبني سؤال  
 items  
 الي بصنوه ✓

**\* Simple Approach :-**

- ① functional block ✓ k inverters
  - ② truth table
  - ③ functions نوعون عليها اسلاك  
نوع ان inputs  $2^k$  Ands
  - ④ diagram ✓  $GN = k + 2^k + k$
- inverters
And Gates

straight forward design.

**\* Expansion Approach :- less GN ✓**

عدد ال Ands هو عدد ال  $2^k$  ، بس نوعون عليها سلكين فقط ال غير ✓  
نوع

$\hookrightarrow$  even, take it as is  
 $\hookrightarrow$  odd, (ceiling, then floor)

how to calculate GN for expansion Approach.

$$\text{Ands} * 2 + k = \underline{\underline{GN}}$$

\* GN never differ between small decoders when designing them using straight forward design or expansion approach. ✓

it differs for the big decoders. ✓