

DIGITAL ELECTRONICS

 POWERUNIT  

Digital Electronics

CPE

Dr.Mohammad Abdel-Majeed

Assistant Professor

University of Jordan

Outline

- **Course Introduction**
 - **Course Information**
 - **Textbook**
 - **Grading**
 - **Course Outline**

Course Information

- Instructor: **Mohammad Abdel-Majeed**
- Email: m.abdel-majeed@ju.edu.jo
- Homepage: www.piazza.com
- Office: **CPE 421**
- Office Hours:
- Prerequisites:

Textbook

- *CMOS Digital Integrated Circuits Analysis and Design.* (Kang and Leblebici)
- *CMOS VLSI Design, A Circuits And Systems Perspective.* (Weste and Harris)


Grading Information

- **Grading**

- Midterm Exam 30%
- Assignments and Quizzes 20%
- Final Exam 50%

- **Policies**

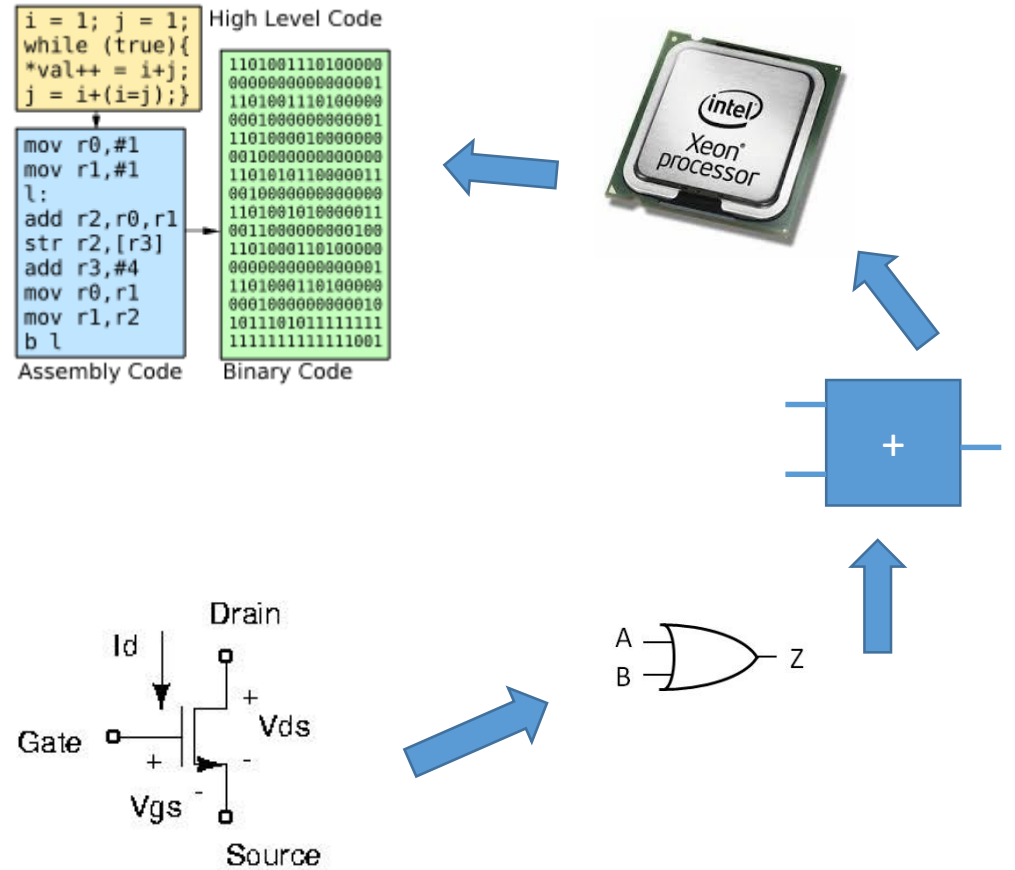- Attendance is required
- Cheating will not be tolerated
- No Makeup Exams



C/ C++	Apps
Assembly/ Machine code	Processor/Mem/ I/O
Processor/Mem/I/O	
Functional units	
Logic Gates	
Transistors	
Voltage/Current	

Objective and Organization

- Provide in-depth understanding of the intricate issues in digital circuit design like:
 - **Performance**
 - **Interconnect**
 - Reliability
 - Low-power design
- Sequence of topics
 - Design Flow
 - MOS transistor (Overview)
 - MOS Inverter
 - MOS Inverter switching characteristics
 - Combinational MOS circuits
 - Sequential MOS Circuits
 - MOS Fabrication, schematic and Layout.(LTSpice and Electric Tools)

Objective and Organization

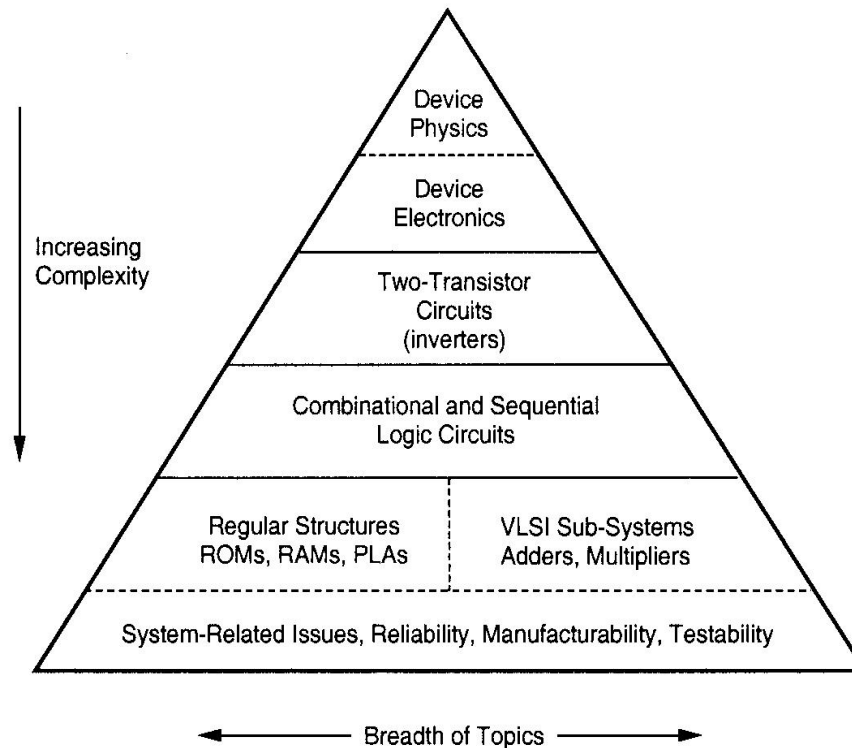


Figure 1.4 The ordering of topics covered in a typical digital integrated circuits course.

Lecture1

Design Flow

Dr.Mohammad Abdel-Majeed

Assistant Professor

University of Jordan

Coping with Complexity

- How to design System-on-Chip?
 - Many millions (even billions!) of transistors
 - Tens to hundreds of engineers
- Structured Design
- Design Partitioning






Structured Design

- _____: Divide and Conquer
 - Recursively system into modules
- _____:
 - Reuse modules wherever possible
 - Ex: Standard cell library
- _____: well-formed interfaces
 - Allows modules to be treated as black boxes
- _____:
 - Physical and temporal

Structural Decomposition of 4-b Adder

Structural Decomposition of 4-b Adder

- Easier to handle

    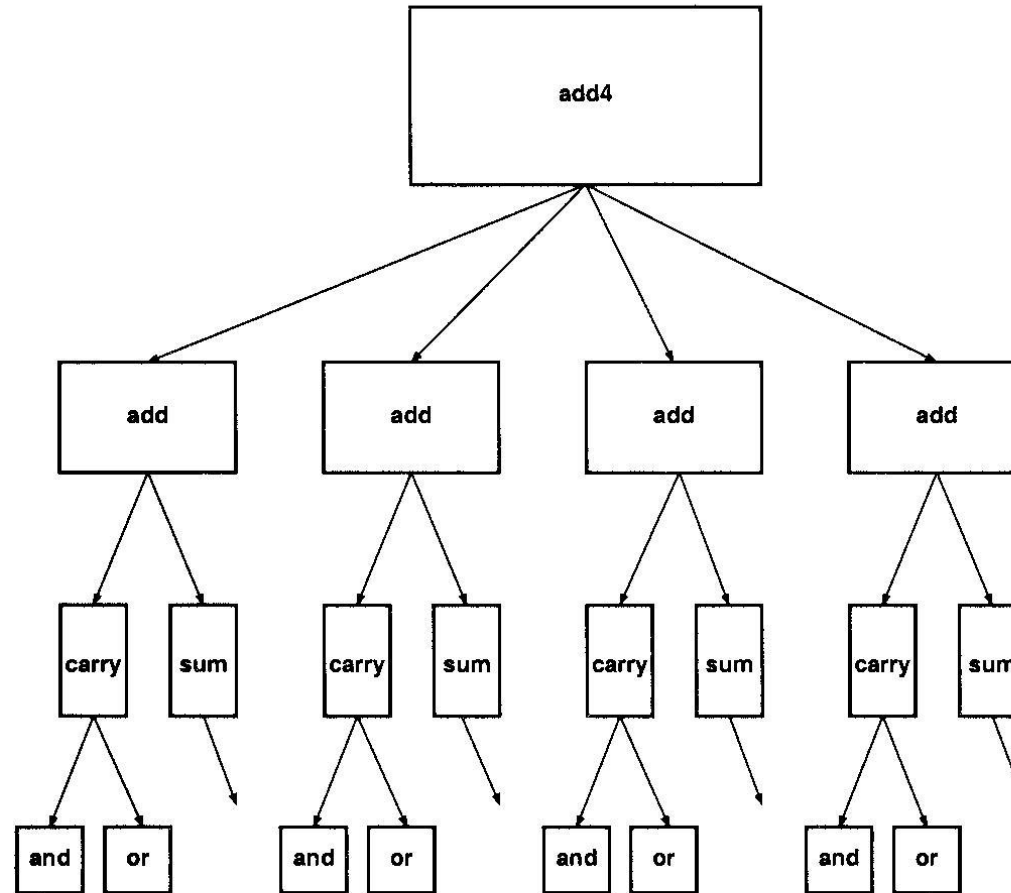

Structural Hierarchy of 16-b Adder

Structural Hierarchy of 16-b Adder

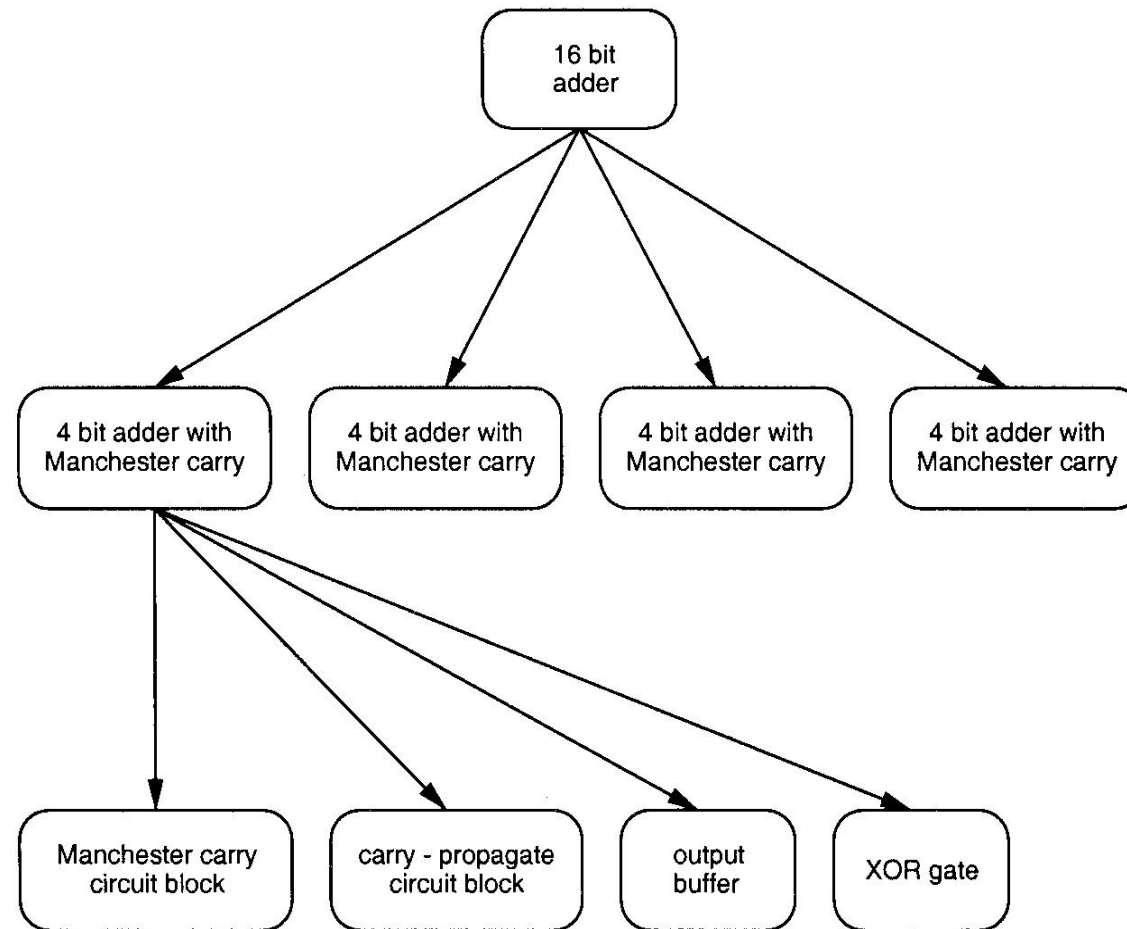


Figure 1.25 Structural hierarchy of the 16-bit adder circuit.

Concepts of Regularity

- Regularity
 - decomposition into similar blocks
 - Example: parallel multiplication array

 
 


Figure 1.26 Regular design of (a) 2-1 MUX and (b) DFF, using inverters and tri-state buffers as basic building blocks.


Concepts of Modularity and Locality

- Modularity
 - Functional blocks have well-defined functions and interfaces
 - Each block can be designed independently and combined easily
 - Design process parallelized
- Locality
 - Ensures connections are mostly between neighboring modules
 - Delay minimized by avoiding long interconnect

Design Partitioning

- **Architecture:** User's perspective, what does it do?
 - Instruction set, registers
 - MIPS, x86, Alpha, PIC, ARM, ...
- **Microarchitecture**
 - Single cycle, multicycle, pipelined, superscalar?
- **Logic:** how are functional blocks constructed
 - Ripple carry, carry lookahead, carry select adders
- **Circuit:** how are transistors used
 - Complementary CMOS, pass transistors, domino
- **Physical:** chip layout
 - Datapaths, memories, random logic

Flow of Circuit

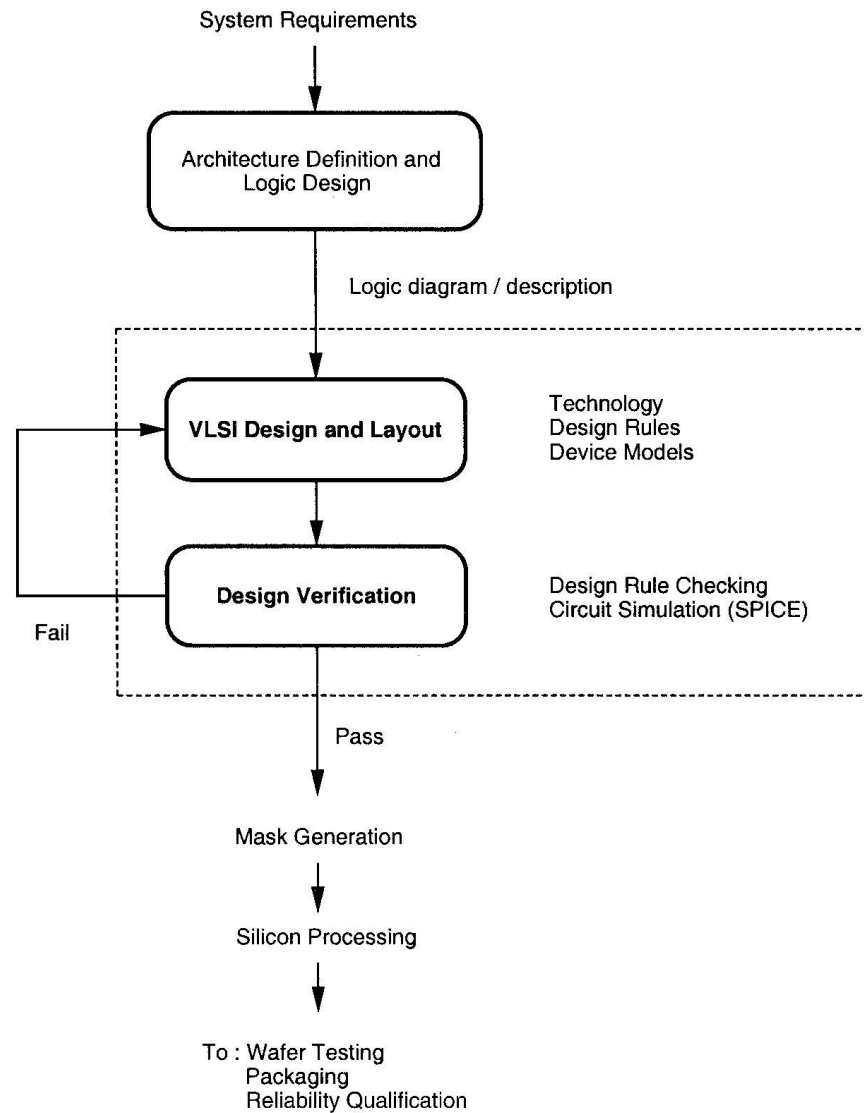

More Simplified VLSI Design Flow


- Simplified design flow
 - Verification plays an important role in every step
 - Top-down and bottom-up approaches combined in the design process

Behavioral Representation

Logic (Gate-level) Representation

Circuit Representation

Layout Representation

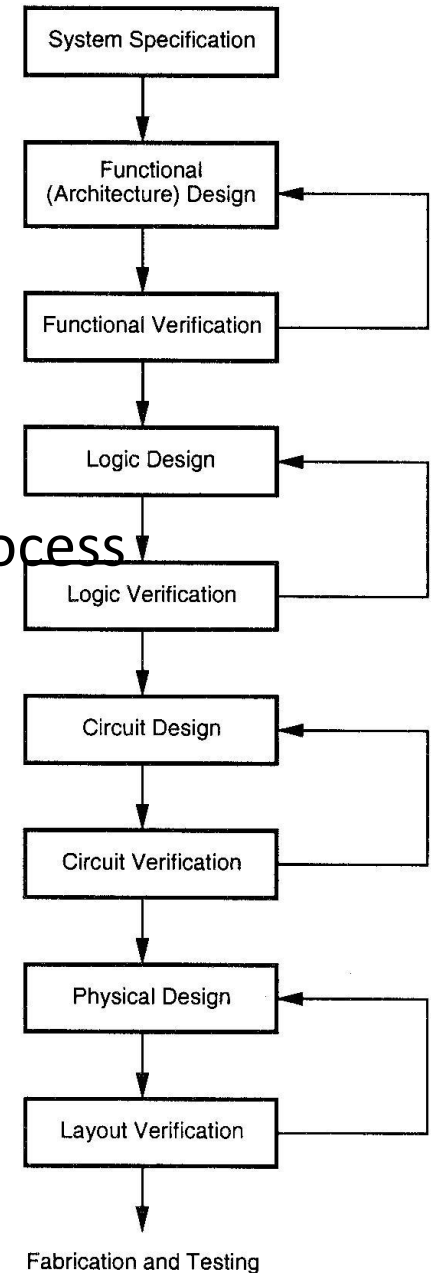

Example 1.1 (1)

- Problem: Design of 1-bit full-adder circuit using ___ nm, twin-well CMOS technology
 - Specifications:
 - Propagation delay of sum and carry_out < _____
 - Transition delay of sum and carry_out < _____
 - Circuit area < $10 \mu\text{m}^2$
 - Dynamic power dissipation (@ $V_{DD} = 1.1\text{V}$ and $f_{max} = 500\text{MHz}$) < $20 \mu\text{W}$

Example 1.1 (2)

- Boolean Description

- Boolean Functions:


- A , B = Two inputs
 - C = Carry in
 - $\text{sum_out} = ABC + AB'C' + A'B'C + A'C'B$
 - $\text{carry_out} = AB + AC + BC$
 - Alternatively, $\text{sum_out} = ABC + (A+B+C)(\text{carry_out})'$

Example 1.1 (2)

- Boolean Description

- Boolean Functions:

- A , B = Two inputs
 - C = Carry in
 - $sum_out = ABC + AB'C' + A'B'C + A'C'B$
 - $carry_out = AB + AC + BC$
 - Alternatively, $sum_out = ABC + (A+B+C)(carry_out)'$

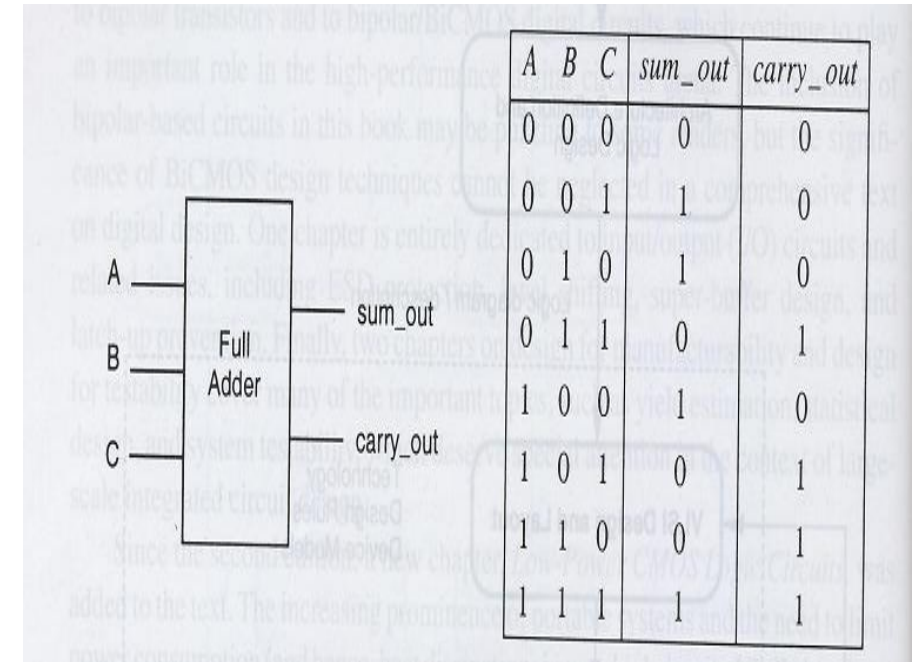

Example 1.1 (3)

- Logi

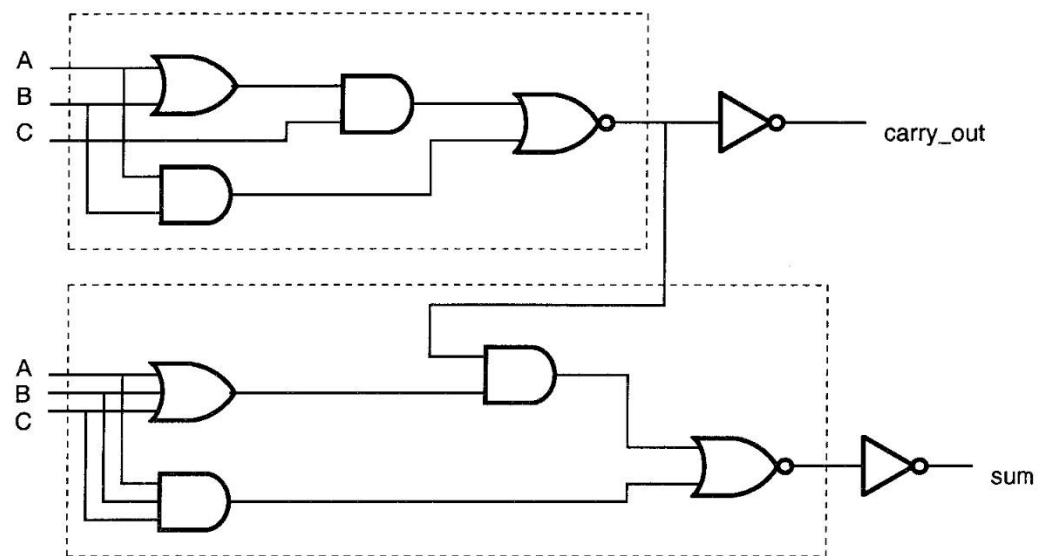


Figure 1.7 Gate-level schematic of the one-bit full-adder circuit.

Example 1.1 (4)

- Transistor-level circuit
 - AND = Series-connected nMOS
 - OR = Parallel- connected nMOS
 - pMOS network = dual of nMOS network

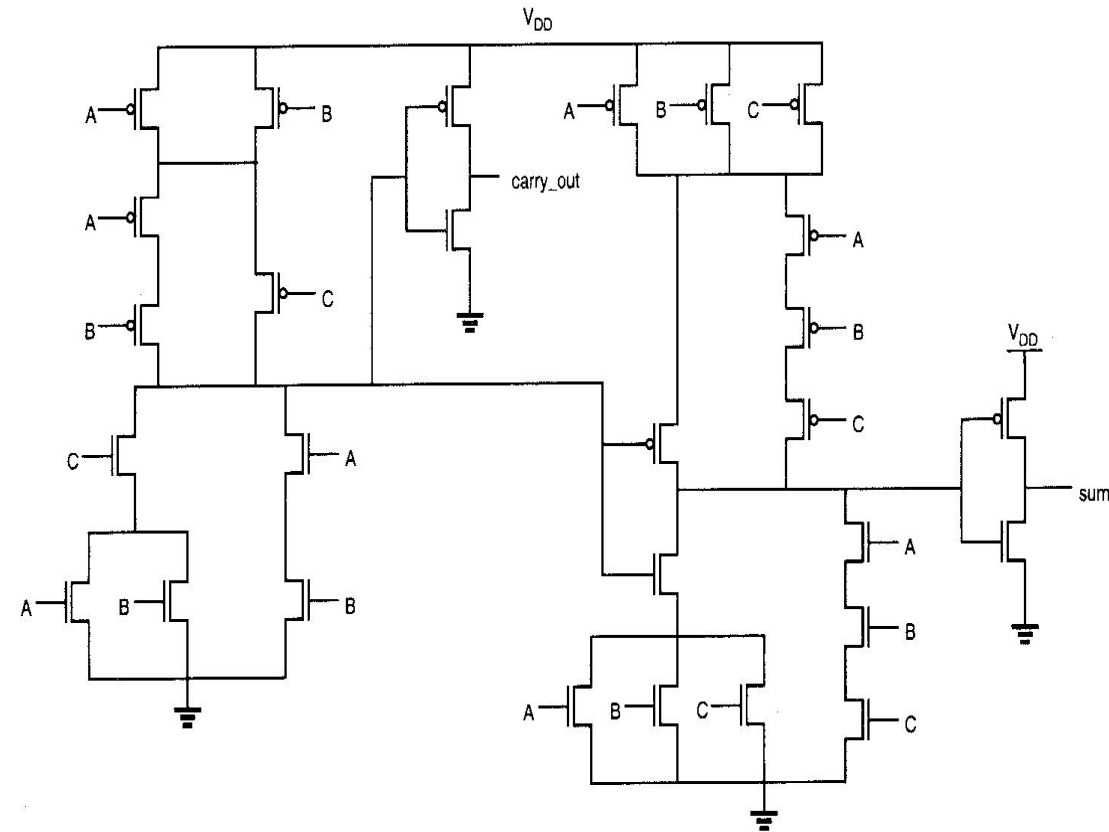


Figure 1.8 Transistor-level schematic of the one-bit full-adder circuit.

Example 1.1 (6)

- Initial sizes
 - nMOS, $(W/L) = 90\text{nm}/50\text{nm}$
 - pMOS, $(W/L) = 90\text{nm}/50\text{nm}$
 - May need to be changed depending on performance

 


Figure 1.10. Simulated input and output waveforms of the full-adder circuit.

Example 1.1 (7)

- Timing constraint violation
 - sum_out and carry_out violate timing constraints
 - Worst-case delay 250 ps (> 220 ps)
 - Modification necessary

 


Figure 1.11. Simulated output waveforms of the full adder circuit with minimum transistor dimensions, showing the signal propagation delay during one of the worst-case transitions.

Example 1.1 (8)

- Resizing transistors to improve design
 - is an iterative process
 - To meet timing specifications (W/L) of (n/p)MOS is increased

 


Figure 1.13. Simulated output waveforms of the full-adder circuit with optimized transistor dimensions, showing the signal propagation delay during the same worst-case transition.

Example 1.1 (8)

- Layout Design
 - Design rule checker (DRC) tool used to check violation of design rules
 - Parasitic capacitances and resistances extracted
- Design Verification
 - Extracted parasitics used to create SPICE input file
 - Simulation is run
- Simulation Results
 - Not all specifications met

Example 1.1 (9)

- New and compact layout for 1-bit full adder (optimized)
- Now, all the design specifications are satisfied
 - Propagation and transition (rise/fall) delay within 220 ps
 - Dynamic power dissipation = 4.9 μW ($<20\mu\text{W}$)
 - Area = $(2.04 \mu\text{m} \times 3.01 \mu\text{m}) = 6.14 \mu\text{m}^2$ ($<10 \mu\text{m}^2$)

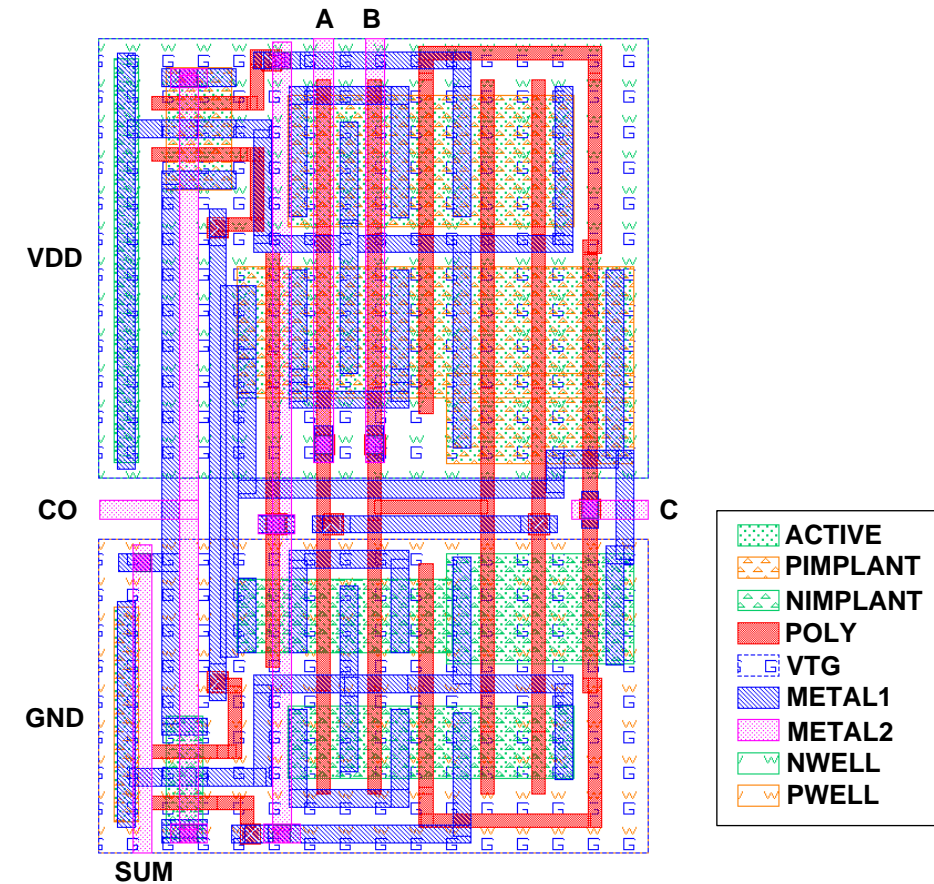


Figure 1.12. Layout of the full-adder circuit, with optimized transistor dimensions.

8-bit Binary Adder (1)

- Obtained by cascading 8 full adders – called “carry ripple adder”
 - Speed limited by the delay of carry bits



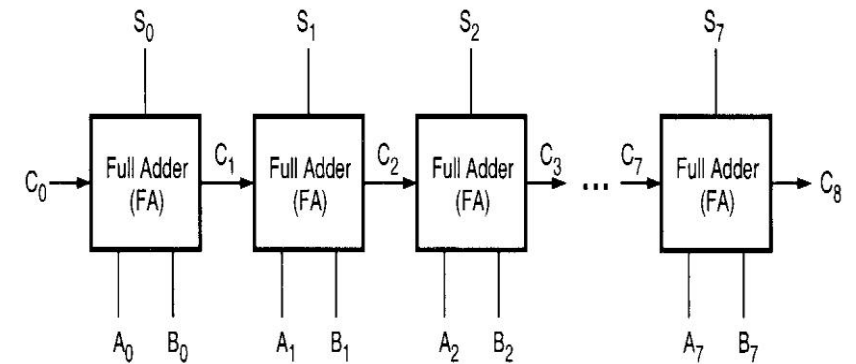


Figure 1.15 Block diagram of a carry ripple adder chain consisting of full adders.

 


8-bit Binary Adder (2)

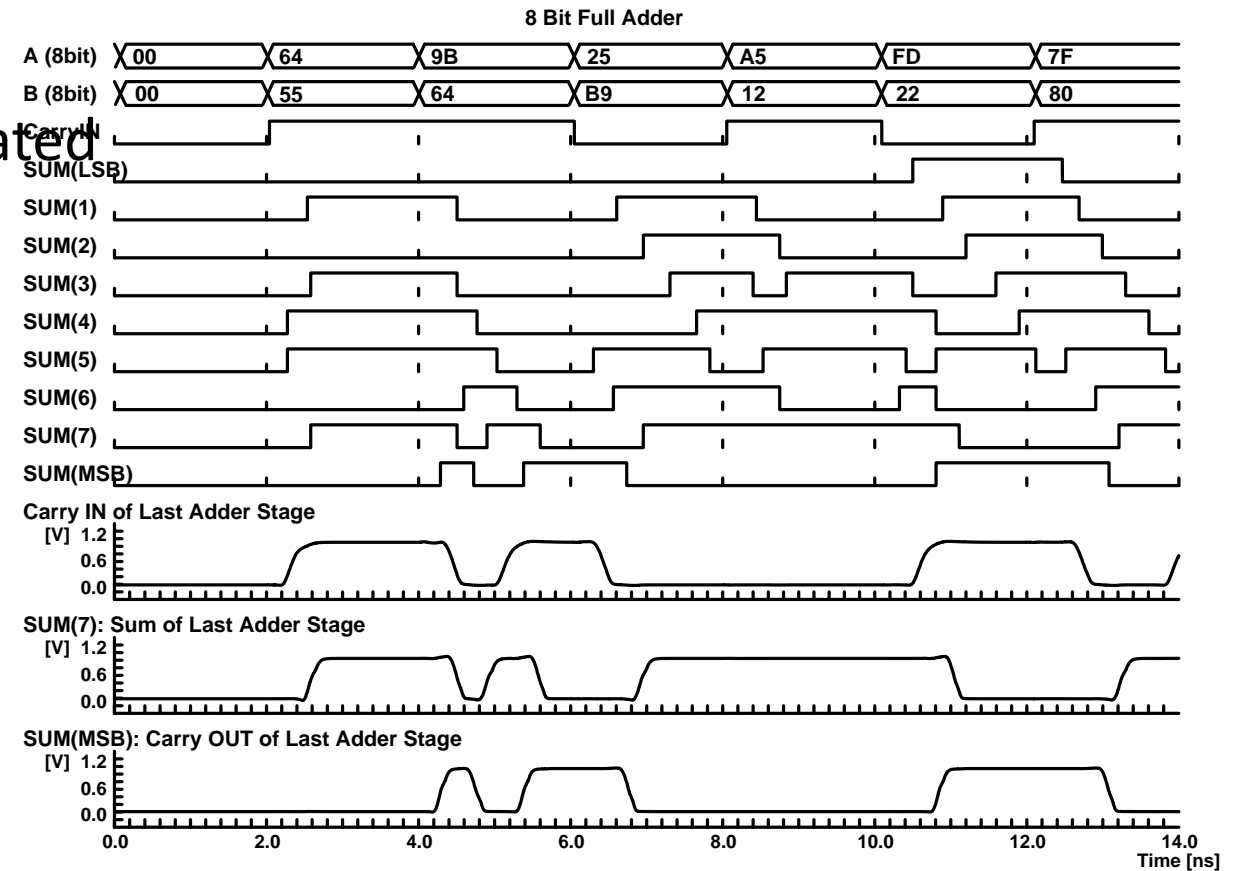- Simulation results
 - Sum bit of last adder stage is generated last
 - Overall delay as long as 0.7 ns



Y-Chart

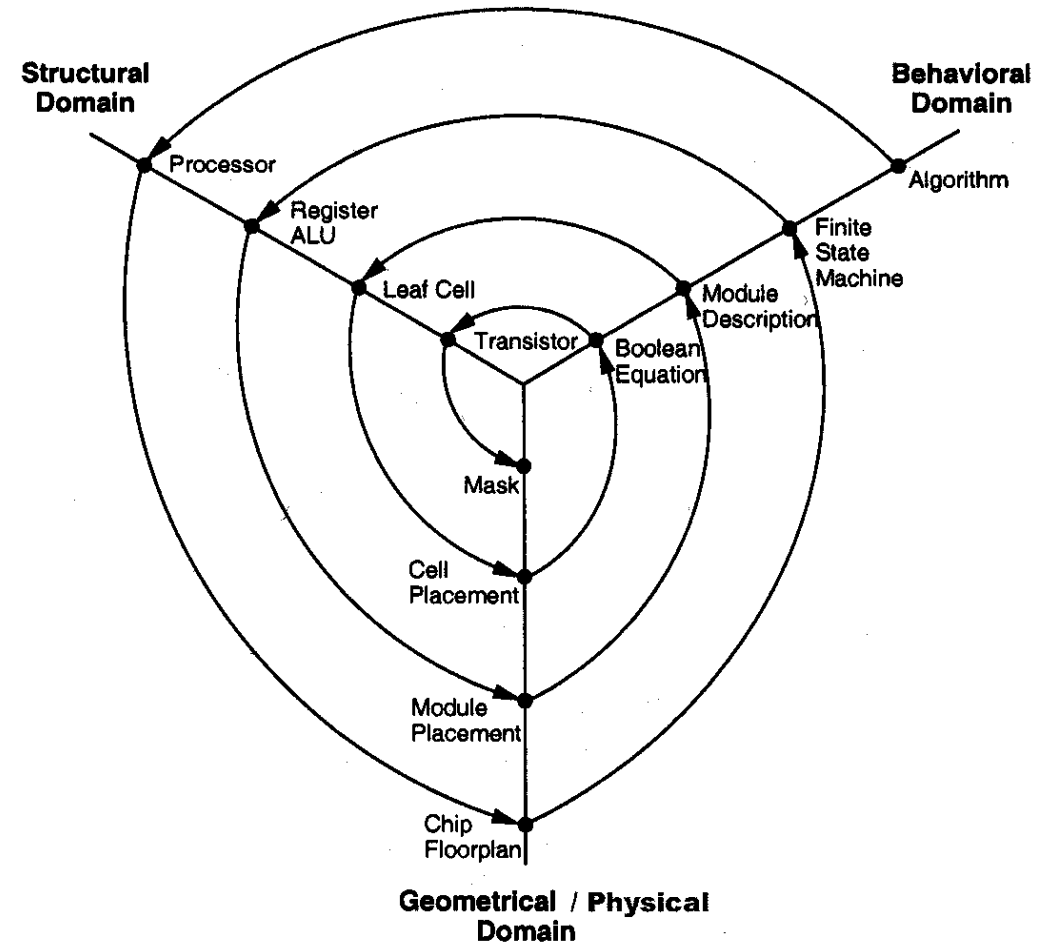

VLSI Design Styles

- Field Programmable Gate Array (FPGA)
 - Consists of
 - I/O buffers
 - Array of configurable logic blocks (CLBs)
 - Programmable interconnect structure
 - Contains thousands of logic gates
 - Routing between CLBs and I/O blocks done by setting the configurable switch matrices
- Proper choice of design style is essential to delivering the product in time with low cost
 - Full-custom
 - Semi-custom

Field Programmable Gate Array (1)

 


Figure 1.27 General architecture of Xilinx FPGAs.

<https://www.youtube.com/watch?v=gUsHwi4M4xE>

Verilog Example

```

module fulladder(input  a, b, c,
                  output s, cout);

```

```

    sum      s1(a, b, c, s);

```

```

    carry    c1(a, b, c, cout);

```

```

endmodule

```

```

module carry(input  a, b, c,
             output cout)

```

```


    assign cout = (a&b) | (a&c) | (b&c);

```

```

endmodule

```

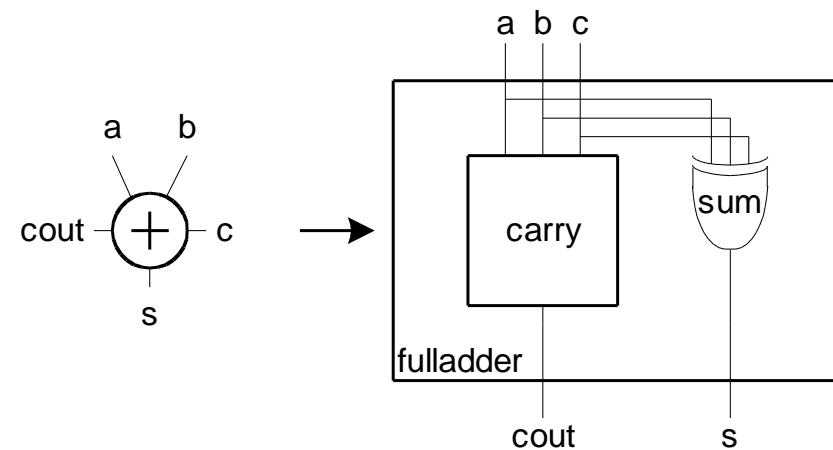

Gate-level Netlist(Synthesis)

```

module carry(input  a, b, c,
               output cout)

```

```

  wire    x, y, z;

```

```

  and g1(x, a, b);

```

```

  and g2(y, a, c);

```

```

  and g3(z, b, c);

```

```


  or  g4(cout, x, y, z);

```



```

endmodule

```

 

Place and route

  

Circuit Design

- How should logic be implemented?
 - NANDs and NORs vs. ANDs and ORs?
 - Fan-in and fan-out?
 - How wide should transistors be?
- These choices affect speed, area, power
- Logic synthesis makes these choices for you
 - Good enough for many applications
 - Hand-crafted circuits are still better

Standard-Cell Based Design (1)

- One of the most prevalent full custom design styles
 - Commonly used logic cells are optimized and developed
 - Several versions are stored in a standard library cell
- Each cell is characterized by
 - Delay time vs. load capacitance
 - Circuit simulation model
 - Timing simulation model
 - Fault simulation model
 - Cell data for place-and-route
 - Mask data

Standard-Cell Based Design (2)

- Each cell layout is designed with fixed height
 - Cells can be placed side-by-side
 - Routing of intercell connection is easy

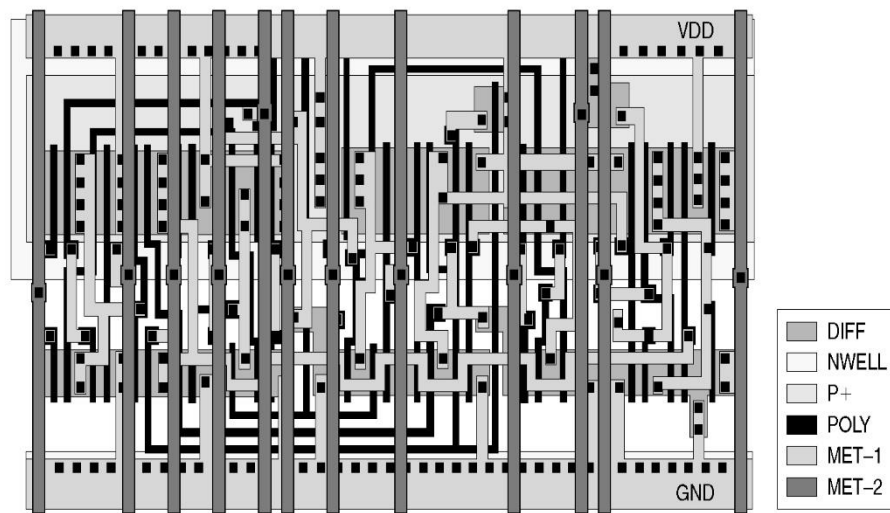


Figure 1.36 A standard cell layout example.

 


Figure 1.37 A simplified floorplan of standard-cells based design.

- ◆ Floorplan for a standard-cell based design contains
 - I/O frame, cell rows
 - Channels between rows
 - channels may be reduced or removed if over-the-cell routing is done

Standard-Cell Based Design (3)

- Common bus may be incorporated if cells must share same input and/or output signals

 


Figure 1.38 Simplified floorplan of a standard-cells based design, consisting of two separate blocks and a common signal bus.

Structured ASIC (_____)

FPGA Vs. Standard Cell ASIC

- Easy to Design
- Short Development Time
- Low NRE Costs
- Design Size Limited
- Design Complexity Limited
- Performance Limited
- High Power Consumption
- High Per-Unit Cost

- Difficult to Design
- Long Development Time
- High NRE Costs
- Support Large Designs
- Support Complex Designs
- High Performance
- Low Power Consumption
- Low Per-Unit Cost (at high volume)

Structured ASIC's Combine the Best of Both Worlds


- Generally speaking
 - 100:33:1 ratio between the number of gates in a given area for _____, _____, _____
 - ___:___:___ ratio for performance (based on clock frequency)
 - ___:___:___ ratio for power

Full Custom Design (1)

- Design is done from scratch
 - Geometry, orientation and placement of every transistor done by designer
 - Development cost and time very high
 - “Design Reuse” becoming popular to reduce cost and time
 - Example of a true full custom design – design of memory cell (static or dynamic)

Full Custom Design (2)

 - Full custom design rarely used due to high labor cost
 - Rather combination of different design styles are used to develop a chip



Design Quality

- Important metrics for measuring the quality of design
 - Testability
 - Yield and manufacturability
 - Reliability
 - Technology updateability

Testability

- Fabricated chips should be fully testable which requires
 - Generation of good test vectors
 - Availability of reliable test fixture at speed
 - Design of testable chip

Yield and Manufacturability

- Yield may be defined in two ways
 - (1) No. of good tested chips divided by the total no. of tested chips
 - (2) No. of good tested chips divided by the total no. of chip sites available at the start of wafer processing – strictest definition
- Chip yield can be further divided into
 - Functional yield – obtained by testing the functionality of the chip at a speed lower than required
 - Weeds out problems of short, open and leakage
 - Can detect logic and circuit design faults
 - Parametric yield – performed at the required speed on chips that passed functional test
 - Delay testing done in this phase

Reliability

- Reliability depends on design and process conditions
 - Major causes of chip reliability problem are
 - Electrostatic discharge (ESD) and electrical overstress (EOS) and electromigration
 - Latch-up in CMOS I/O internal circuits
 - Hot carrier induced aging
 - Oxide breakdown and single event upset
 - Power and ground bouncing
 - On-chip noise and crosstalk
- Measures taken to ensure reliability
 - Metal wire widened to avoid over-etching
 - Rise time of signals applied to nMOS gate reduced to avoid aging

Technology Updateability

- Process technology advancing at a high pace
 - Design styles should be chosen such that chips are technology updateable
 - “Silicon Compilation” – where physical layout is done automatically – is used

References

Backup

MIPS Architecture

- Example: subset of MIPS processor architecture
 - Drawn from Patterson & Hennessy
- MIPS is a 32-bit architecture with 32 registers
 - Consider 8-bit subset using 8-bit datapath
 - Only implement 8 registers (\$0 - \$7)
 - \$0 hardwired to 00000000
 - 8-bit program counter
- You'll build this processor in the labs
 - Illustrate the key concepts in VLSI design

Instruction Set

Table 1.7 MIPS instruction set (subset supported)				
Instruction	Function	Encoding	op	funct
add \$1, \$2, \$3	addition: \$1 → \$2 + \$3	R	000000	100000
sub \$1, \$2, \$3	subtraction: \$1 → \$2 - \$3	R	000000	100010
and \$1, \$2, \$3	bitwise and: \$1 → \$2 and \$3	R	000000	100100
or \$1, \$2, \$3	bitwise or: \$1 → \$2 or \$3	R	000000	100101
slt \$1, \$2, \$3	set less than: \$1 → 1 if \$2 < \$3 \$1 → 0 otherwise	R	000000	101010
addi \$1, \$2, imm	add immediate: \$1 → \$2 + imm	I	001000	n/a
beq \$1, \$2, imm	branch if equal: PC → PC + imm ^a	I	000100	n/a
j destination	jump: PC_destination ^a	J	000010	n/a
lb \$1, imm(\$2)	load byte: \$1 → mem[\$2 + imm]	I	100000	n/a
sb \$1, imm(\$2)	store byte: mem[\$2 + imm] → \$1	I	110000	n/a


Instruction Encoding

- 32-bit instruction encoding
 - Requires four cycles to fetch on 8-bit datapath


format	example	encoding					
R	add \$rd, \$ra, \$rb	6 0	5 ra	5 rb	5 rd	5 0	6 funct
I	beq \$ra, \$rb, imm	6 op	5 ra	5 rb	16 imm		
J	j dest	6 op	26 dest				

MIPS Microarchitecture

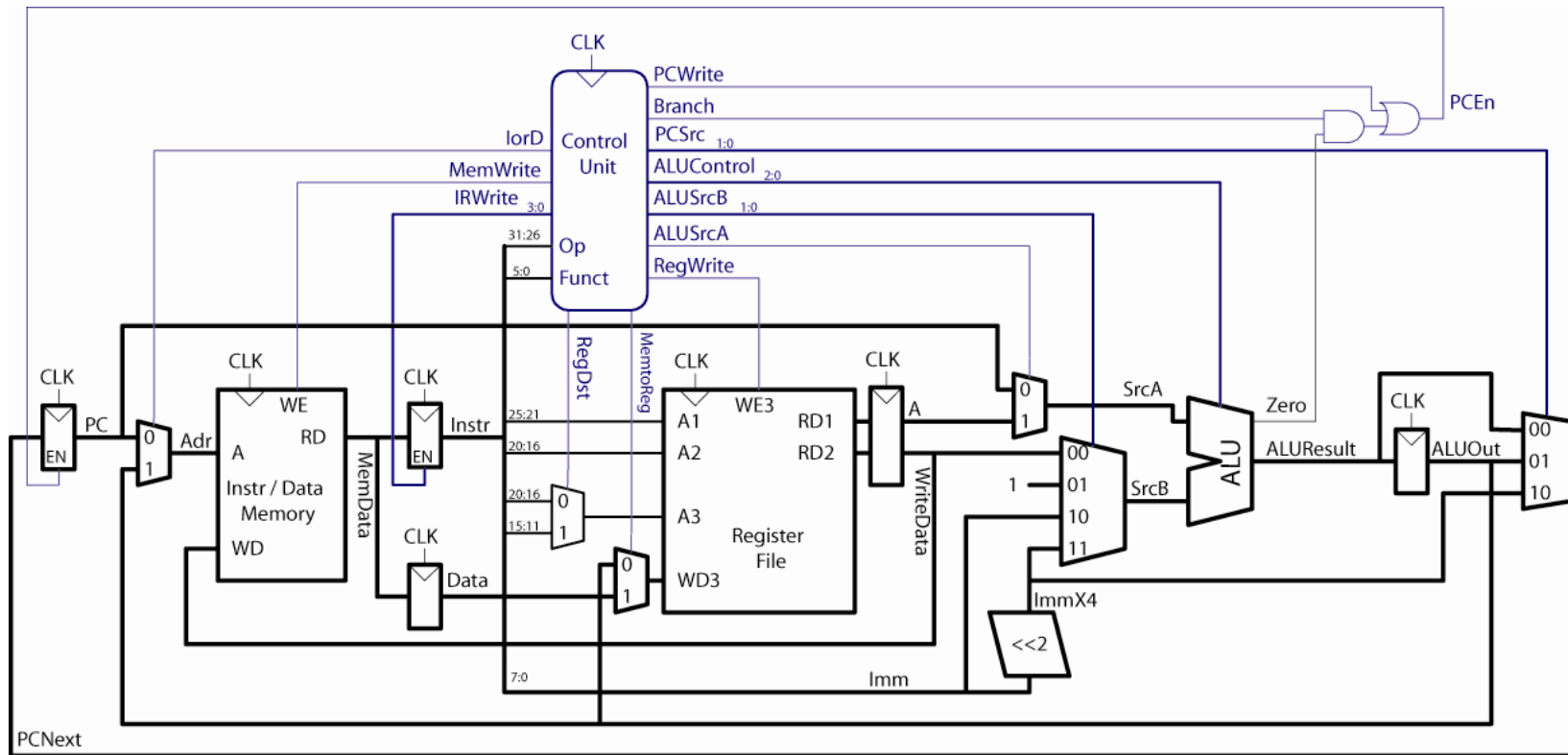- Multicycle μ architecture ([Paterson04], [Harris07])




Multicycle Controller

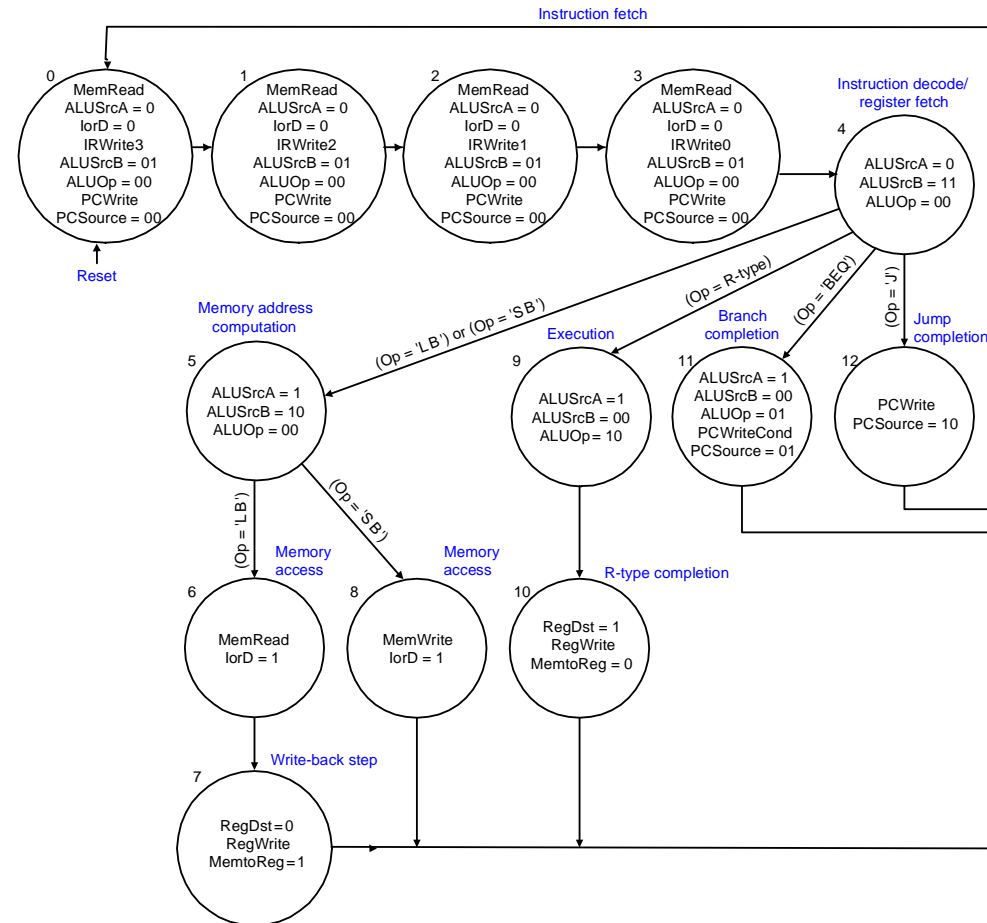


Logic Design

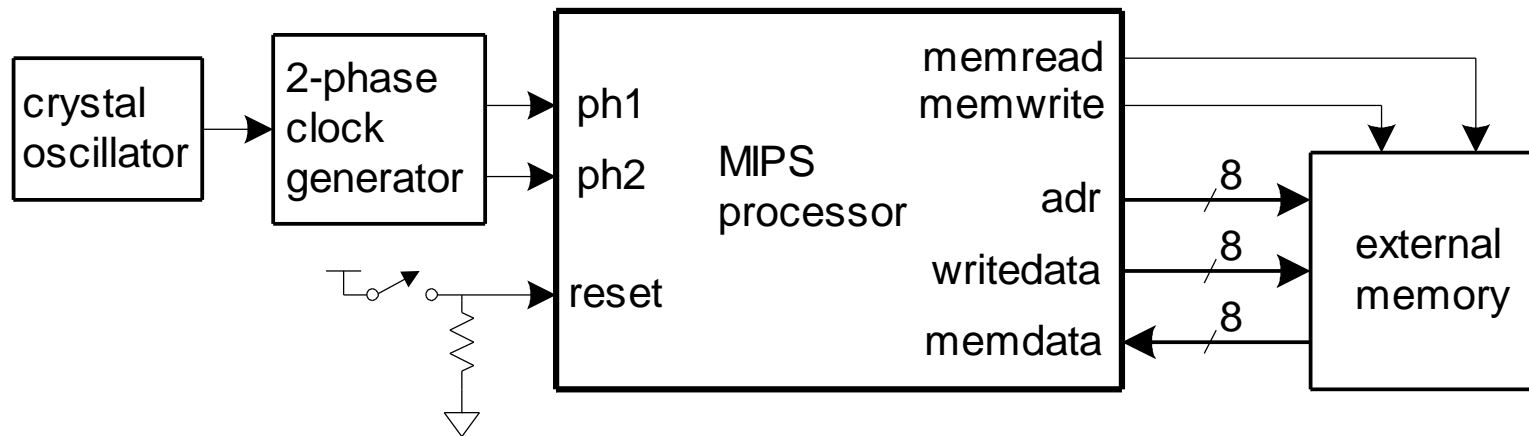
- Start at top level
 - Hierarchically decompose MIPS into units
- Top-level interface



Block Diagram

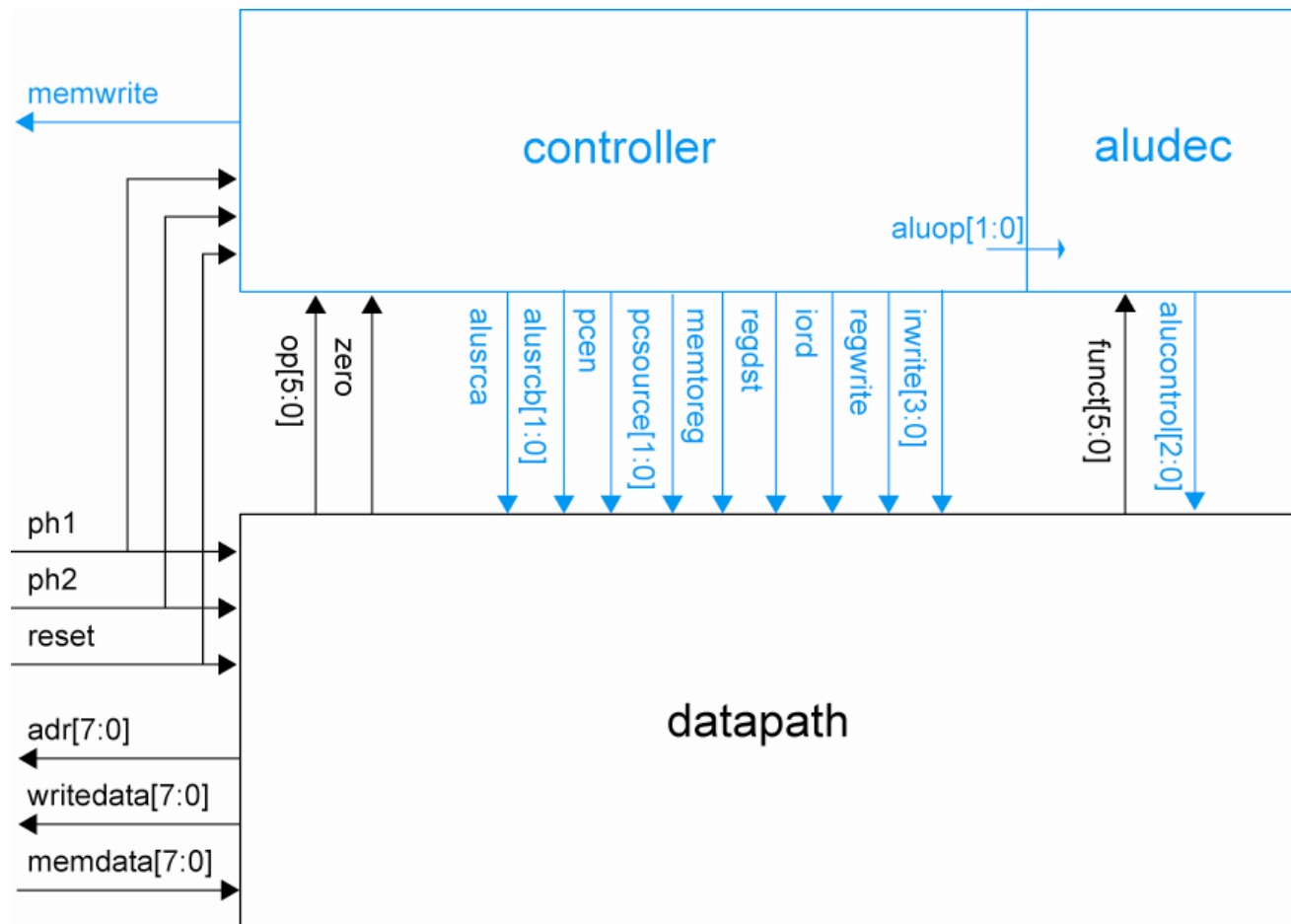

Hierarchical Design

 

CMOS Transistor

Dr.Mohammad Abdel-Majeed

Assistant Professor


University of Jordan

How Does a Transistor Work?

- <http://www.youtube.com/watch?v=lcrBqCFLHIY>

Terminal Voltages

 - Mode of operation depends on V_g , V_d , V_s
 - $V_{gs} = V_g - V_s$
 - $V_{gd} = V_g - V_d$
 - $V_{ds} = V_d - V_s = V_{gs} - V_{gd}$
- Source and drain are symmetric diffusion terminals
 - By convention, source is terminal at lower voltage
 - Hence $V_{ds} \geq 0$
- nMOS body is grounded. First assume source is 0 too.
- Three regions of operation
 - *Cutoff*
 - *Linear*
 - *Saturation*



NMOS cross section


Cutoff

Linear

Saturation


nMOS Cutoff

- No channel
- $I_{ds} \approx 0$

 


nMOS Linear

 - Channel forms
- Current flows from d to s
 - e^- from s to d
- I_{ds} increases with V_{ds}
- Similar to linear resistor



nMOS Saturation

 - Channel pinches off
- I_{ds} independent of V_{ds}
- We say current *saturates*
- Similar to current source





I-V Characteristics

- In Linear region, I_{ds} depends on
 - How much charge is in the channel?
 - How fast is the charge moving?

Channel Charge

  - MOS structure looks like parallel plate capacitor while operating in inversions
 - Gate – oxide – channel
- $Q_{\text{channel}} =$
- $C = C_g =$
- $V =$



Carrier velocity

- Charge is carried by e-
- Electrons are propelled by the lateral electric field between source and drain
 - $E =$
- Carrier velocity v proportional to lateral E-field
 - $v =$
- Time for carrier to cross channel:
 - $t =$

nMOS Linear I-V

- Now we know
 - How much charge Q_{channel} is in the channel
 - How much time t each carrier takes to cross

$$I_{ds} = \frac{Q_{\text{channel}}}{t}$$

$$= \mu C_{\text{ox}} \frac{W}{L} \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$= \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$\beta = \mu C_{\text{ox}} \frac{W}{L}$$

nMOS Saturation I-V

- If $V_{gd} < V_t$, channel pinches off near drain

When $V_{ds} > V_{dsat} = V_{gs} - V_t$

- Now drain voltage no longer increases current

$$I_{ds} = \beta \left(V_{gs} - V_t - \frac{V_{dsat}}{2} \right) V_{dsat}$$

$$= \frac{\beta}{2} (V_{gs} - V_t)^2$$

nMOS I-V Summary

- *Shockley* 1st order transistor models


$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

Example

- Plot I_{ds} vs. V_{ds} Given that
 - $t_{ox} = 100 \text{ \AA}$
 - $\mu = 350 \text{ cm}^2/\text{V}\cdot\text{s}$
 - $V_t = 0.7 \text{ V}$
 - $\xi_0 = 8.85 \cdot 10^{-12} \text{ F/m}$
 - $\xi_{ox} = 3.9$
 - $V_{gs} = 0, 1, 2, 3, 4, 5$
 - Use $W/L = 4/2 \lambda$


Example

$$\beta = \mu C_{ox} \frac{W}{L} = (350) \left(\frac{3.9 \times 8.85 \cdot 10^{-14}}{100 \cdot 10^{-8}} \right) \left(\frac{W}{L} \right) = 120 \frac{W}{L} \mu\text{A}/\text{V}^2$$

 

pMOS I-V

 - All dopings and voltages are inverted for pMOS
 - Source is the more positive terminal
- Mobility μ_p is determined by holes
 - Typically 2-3x lower than that of electrons μ_n
 - 120 cm²/V•s in AMI 0.6 μ m process
- Thus pMOS must be wider to provide same current
 - In this class, assume $\mu_n / \mu_p = 2$



Problem

- NMOS Transistor
- $V_{th}=.7$ $V_s=1V$ $V_G=2.5$ $V_d=4V$ $B=23\mu A/V^2$
- Find W/L

The Threshold Voltage (1)(Optional)

- Physical components of the threshold voltage of a MOS structure
 - The work function difference between the gate and the channel.
 - The gate component to change the surface potential.
 - The gate voltage component to offset the depletion region charge.
 - The voltage component to offset the fixed charges in the gate oxide and in the silicon-oxide interface.

The Threshold Voltage (2) (Optional)

- The work function difference Φ_{GC} between the gate and the channel determines the built-in potential of the MOS system.

- For metal gate

$$\Phi_{GC} = \phi_F(\textit{substrate}) - \phi_M$$

- For polysilicon gate

$$\Phi_{GC} = \phi_F(\textit{substrate}) - \phi_F(\textit{gate})$$

The Threshold Voltage (3) (Optional)

- Because of the fixed acceptor ions located in the depletion region near the surface, depletion charge exists.

- Depletion region charge

$$Q_{B0} = -\sqrt{2q \cdot N_A \cdot \epsilon_{Si} \cdot |-2\phi_F|}$$

- Consider the voltage bias of the body.

$$Q_B = -\sqrt{2q \cdot N_A \cdot \epsilon_{Si} \cdot |-2\phi_F + V_{SB}|}$$

- The component that offsets the depletion region charge is equal to:

$$-Q_B / C_{OX}$$

$$C_{OX} = \frac{\epsilon_{ox}}{t_{ox}}$$

The Threshold Voltage (4) (Optional)

- There always exists a fixed positive charge density Q_{ox} at the interface between the gate oxide and the silicon substrate.
- The gate voltage component that is necessary to offset this positive charge at the interface is .
 - For zero substrate bias

$$V_{T0} = \Phi_{GC} - 2\phi_F(\text{substrate}) - \frac{Q_{B0}}{C_{ox}}$$

The Threshold Voltage (optional)

- We can use the (3.23) for both n-channel device and p-channel device.
- However, some of the terms and coefficient in (3.23) have different polarities for the n-channel case and for the p-channel case.
 - The substrate Fermi potential ϕ_F is negative in nMOS, positive in pMOS.
 - The depletion region charge density Q_{B0} and Q_B are negative in nMOS, positive pMOS.
 - The substrate bias coefficient γ is positive in nMOS, negative in pMOS.
 - The substrate bias voltage V_{SB} is positive in nMOS, negative in pMOS.

Example 3.2 (1) (optional)

- Calculate the threshold voltage V_{T0} (@ $V_{SB}=0$).

- $N_A = 4 \times 10^{18} \text{ cm}^{-3}$
- $N_D = 2 \times 10^{20} \text{ cm}^{-3}$
- $t_{ox} = 26.3 \text{ \AA}$
- $N_i = 1.45 \times 10^{18}$

- Sol.

- Calculate the Fermi potentials

$$\phi_F(\text{substrate}) = \frac{kT}{q} \ln\left(\frac{n_i}{N_A}\right) = 0.026\text{V} \cdot \ln\left(\frac{1.45 \cdot 10^{10}}{4 \times 10^{18}}\right) = -0.51\text{V}$$

- Calculate the work function difference

$$\Phi_{GC} = \phi_F(\text{substrate}) - \phi_F(\text{gate}) = -0.51\text{V} - 0.55\text{V} = -1.06\text{V}$$

Example 3.2 (2) (optional)

- Sol.(Cont'd)

- The depletion region charge density at $V_{SB} = 0$

$$\begin{aligned}
 Q_{B0} &= -\sqrt{2 \cdot q \cdot N_A \cdot \epsilon_{Si} \cdot |-2\phi_F(\text{substrate})|} \\
 &= -\sqrt{2 \cdot 1.6 \cdot 10^{-19} \cdot (4 \times 10^{18}) \cdot 11.7 \cdot 8.85 \cdot 10^{-14} \cdot |-2 \cdot 0.51|} \\
 &= -1.16 \cdot 10^{-6} \text{ C/cm}^2
 \end{aligned}$$

- The gate oxide capacitance per unit area


$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.97 \cdot 8.85 \cdot 10^{-14} \text{ F/cm}}{1.6 \cdot 10^{-7} \text{ cm}} = 2.2 \cdot 10^{-6} \text{ F/cm}^2$$


- Combine all components

$$\begin{aligned}
 V_{T0} &= \Phi_{GC} - 2\phi_F(\text{substrate}) - \frac{Q_{B0}}{C_{ox}} \\
 &= -1.06 - (-1.02) - (-0.53)
 \end{aligned}$$

Body effect

$$V_T = V_{T0} + \gamma \left(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|} \right)$$

 

 

Lecture 4: Nonideal Transistor Theory

Outline

- ❑ Nonideal Transistor Behavior
 - High Field Effects
 - Mobility Degradation
 - Velocity Saturation
 - Channel Length Modulation
 - Threshold Voltage Effects
 - Body Effect
 - Drain-Induced Barrier Lowering
 - Short Channel Effect
 - Leakage
 - Subthreshold Leakage
 - Gate Leakage
 - Junction Leakage
- ❑ Process and Environmental Variations


Ideal Transistor I-V

- Shockley long-channel transistor models

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$


Ideal vs. Simulated nMOS I-V Plot

□ 65 nm IBM process, $V_{DD} = 1.0$ V

 


ON and OFF Current

 □ $I_{on} = I_{ds} @ V_{gs} = V_{ds} = V_{DD}$
– Saturation



 □ $I_{off} = I_{ds} @ V_{gs} = 0, V_{ds} = V_{DD}$
– Cutoff



Electric Fields Effects

- Vertical electric field: $E_{\text{vert}} = \underline{\hspace{2cm}}$
 - Attracts carriers into channel
 - Long channel: $Q_{\text{channel}} \propto E_{\text{vert}}$
- Lateral electric field: $E_{\text{lat}} = \underline{\hspace{2cm}}$
 - Accelerates carriers from drain to source
 - Long channel: $v = \mu E_{\text{lat}}$

Coffee Cart Analogy

- ❑ Tired student runs from VLSI lab to coffee cart
- ❑ Freshmen are pouring out of the physics lecture hall
- ❑ V_{ds} is how long you have been up
 - Your velocity = fatigue \times mobility
- ❑ V_{gs} is a wind blowing you against the glass (SiO_2) wall
- ❑ At high V_{gs} , you are buffeted against the wall
 - *Mobility degradation*
- ❑ At high V_{ds} , you scatter off freshmen, fall down, get up
 - *Velocity saturation*
 - Don't confuse this with the saturation region

Mobility Degradation

- High E_{vert} effectively reduces mobility
 - Collisions with oxide interface


$$\mu_{\text{eff}-n} = \frac{540 \frac{\text{cm}^2}{\text{V} \cdot \text{s}}}{1 + \left(\frac{V_{gs} + V_t}{0.54 \frac{\text{V}}{\text{nm}} t_{\text{ox}}} \right)^{1.85}}$$

$$\mu_{\text{eff}-p} = \frac{185 \frac{\text{cm}^2}{\text{V} \cdot \text{s}}}{1 + \frac{|V_{gs} + 1.5V_t|}{0.338 \frac{\text{V}}{\text{nm}} t_{\text{ox}}}}$$

Velocity Saturation

- At high E_{lat} , carrier velocity rolls off
 - Carriers scatter off atoms in silicon lattice
 - Velocity reaches v_{sat}
 - Electrons: 10^7 cm/s
 - Holes: 8×10^6 cm/s
 - Better model
 
$$v = \begin{cases} \frac{\mu_{eff} E}{1 + \frac{E}{E_c}} & E < E_c \\ v_{sat} & E \geq E_c \end{cases} \quad E_c = \frac{2v_{sat}}{\mu_{eff}}$$



Vel Sat I-V Effects

- ❑ Ideal transistor ON current increases with V_{DD}^2

$$I_{ds} = \mu C_{ox} \frac{W}{L} \frac{(V_{gs} - V_t)^2}{2} = \frac{\beta}{2} (V_{gs} - V_t)^2$$

- ❑ Velocity-saturated ON current increases with V_{DD}

$$I_{ds} = C_{ox} W (V_{gs} - V_t) v_{max}$$


- ❑ Real transistors are partially velocity saturated
 - Approximate with α -power law model
 - $I_{ds} \propto V_{DD}^\alpha$
 - $1 < \alpha < 2$ determined empirically (≈ 1.3 for 65 nm)

α -Power Model

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ I_{dsat} \frac{V_{ds}}{V_{dsat}} & V_{ds} < V_{dsat} & \text{linear} \\ I_{dsat} & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$


$$I_{dsat} = P_c \frac{\beta}{2} (V_{gs} - V_t)^\alpha$$
 
$$V_{dsat} = P_v (V_{gs} - V_t)^{\alpha/2}$$



Channel Length Modulation

 - ❑ Reverse-biased p-n junctions form a *depletion region*
 - Region between n and p with no carriers
 - Width of depletion L_d region grows with reverse bias
 - $L_{\text{eff}} = L - L_d$
- ❑ Shorter L_{eff} gives _____ current
 - I_{ds} _____ with V_{ds}
 - Even in saturation



Chan Length Mod I-V

$$I_{ds} = \frac{\beta}{2} (V_{gs} - V_t)^2 (1 + \lambda V_{ds})$$

- $\lambda =$ *channel length modulation coefficient*
 - not feature size
 - Empirically fit to I-V characteristics

Threshold Voltage Effects

- ❑ V_t is V_{gs} for which the channel starts to invert
- ❑ Ideal models assumed V_t is constant
- ❑ Really depends (weakly) on almost everything else:
 - Body voltage: *Body Effect*
 - Drain voltage: *Drain-Induced Barrier Lowering*
 - Channel length: *Short Channel Effect*

Body Effect

- ❑ Body is a fourth transistor terminal
- ❑ V_{sb} affects the charge required to invert the channel
 - Increasing V_s or decreasing V_b increases V_t

$$V_t = V_{t0} + \gamma \left(\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s} \right)$$

- ❑ $\phi_s =$ *surface potential at threshold*

$$\phi_s = 2v_T \ln \frac{N_A}{n_i}$$

- Depends on doping level N_A
- And intrinsic carrier concentration n_i

- ❑ $\gamma =$ *body effect coefficient*

$$\gamma = \frac{t_{ox}}{\epsilon_{ox}} \sqrt{2q\epsilon_{si}N_A} = \frac{\sqrt{2q\epsilon_{si}N_A}}{C_{ox}}$$

Body Effect Cont.

- For small source-to-body voltage, treat as linear

$$V_t = V_{t0} + k_\gamma V_{sb}$$


$$k_\gamma = \frac{\gamma}{2\sqrt{\phi_s}} = \frac{\sqrt{\frac{q\epsilon_{si}N_A}{v_T \ln \frac{N_A}{n_i}}}}{2C_{ox}}$$

DIBL

- ❑ Electric field from drain affects channel
- ❑ More pronounced in small transistors where the drain is closer to the channel
- ❑ Drain-Induced Barrier Lowering
 - Drain voltage also affect V_t

$$V_t' = V_t - \eta V_{ds}$$

 - ❑ High drain voltage causes current to _____




Short Channel Effect

- ❑ In small transistors, source/drain depletion regions extend into the channel
 - Impacts the amount of charge required to invert the channel
 - And thus makes V_t a function of channel length
- ❑ Short channel effect: V_t increases with L
 - Some processes exhibit a reverse short channel effect in which V_t decreases with L

Leakage

- ❑ What about current in cutoff?
- ❑ Simulated results
- ❑ What differs?

—

 

Leakage Sources

- ❑ Subthreshold conduction
 - Transistors can't abruptly turn ON or OFF
 - Dominant source in contemporary transistors
- ❑ Gate leakage
 - Tunneling through ultrathin gate dielectric
- ❑ Junction leakage
 - Reverse-biased PN junction diode current

Subthreshold Leakage

- Subthreshold leakage exponential with V_{gs}


$$I_{ds} = I_{ds0} e^{\frac{V_{gs} - V_{t0} + \eta V_{ds} - k_{\gamma} V_{sb}}{n v_T}} \left(1 - e^{-\frac{V_{ds}}{v_T}} \right)$$

- n is process dependent
 - typically 1.3-1.7
- Rewrite relative to I_{off} on log scale

$$I_{ds} = I_{off} 10^{\frac{V_{gs} + \eta(V_{ds} - V_{dd}) - k_{\gamma} V_{sb}}{S}} \left(1 - e^{-\frac{V_{ds}}{v_t}} \right)$$

$$S = \left[\frac{d(\log_{10} I_{ds})}{dV_{gs}} \right]^{-1} = n v_T \ln 10$$

 - $S \approx 100$ mV/decade @ room temperature




Gate Leakage

- ❑ Carriers tunnel through very thin gate oxides
- ❑ Exponentially sensitive to t_{ox} and V_{DD}

$$I_{\text{gate}} = WA \left(\frac{V_{\text{DD}}}{t_{\text{ox}}} \right)^2 e^{-B \frac{t_{\text{ox}}}{V_{\text{DD}}}}$$


- A and B are tech constants
- Greater for electrons
 - So nMOS gates leak more

 - ❑ Negligible for older processes ($t_{\text{ox}} > 20 \text{ \AA}$)
- ❑ Critically important at 65 nm and below ($t_{\text{ox}} \approx 10.5 \text{ \AA}$)



Junction Leakage

 - ❑ Reverse-biased p-n junctions have some leakage
 - Ordinary diode leakage
 - Band-to-band tunneling (BTBT)
 - Gate-induced drain leakage (GIDL)



Diode Leakage

- ❑ Reverse-biased p-n junctions have some leakage

$$I_D = I_S \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

- ❑ At any significant negative diode voltage, $I_D = -I_S$
- ❑ I_S depends on doping levels
 - And area and perimeter of diffusion regions
 - Typically $< 1 \text{ fA}/\mu\text{m}^2$ (negligible)

Band-to-Band Tunneling

- ❑ Tunneling across heavily doped p-n junctions
 - Especially sidewall between drain & channel when *halo doping* is used to increase V_t
- ❑ Increases junction leakage to significant levels


$$I_{BTBT} = WX_j A \frac{E_j}{E_g^{0.5}} V_{dd} e^{-B \frac{E_g^{1.5}}{E_j}}$$

$$E_j = \sqrt{\frac{2qN_{halo}N_{sd}}{\epsilon(N_{halo} + N_{sd})}} \left(V_{DD} + v_T \ln \frac{N_{halo}N_{sd}}{n_i^2} \right)$$

- X_j : sidewall junction depth
- E_g : bandgap voltage
- A, B: tech constants


Gate-Induced Drain Leakage

 - ❑ Occurs at overlap between gate and drain
 - Most pronounced when drain is at V_{DD} , gate is at a negative voltage
 - Thwarts efforts to reduce subthreshold leakage using a negative gate voltage



Temperature Sensitivity

 - ❑ Increasing temperature
 - Reduces mobility
 - Reduces V_t
- ❑ I_{ON} _____ with temperature
- ❑ I_{OFF} _____ with temperature




So What?

- ❑ So what if transistors are not ideal?
 - They still behave like switches.
- ❑ But these effects matter for...
 - Supply voltage choice
 - Logical effort
 - Quiescent power consumption
 - Pass transistors
 - Temperature of operation

Parameter Variation

 - ❑ Transistors have uncertainty in parameters
 - Process: L_{eff} , V_t , t_{ox} of nMOS and pMOS
 - Vary around typical (T) values
- ❑ Fast (F)
 - L_{eff} : _____
 - V_t : _____
 - t_{ox} : _____
- ❑ Slow (S): opposite
- ❑ Not all parameters are independent for nMOS and pMOS



Environmental Variation

- ❑ V_{DD} and T also vary in time and space
- ❑ Fast:
 - V_{DD} : _____
 - T : _____

Corner	Voltage	Temperature
F		
T	1.8	70 C
S		

Process Corners

- ❑ Process corners describe worst case variations
 - If a design works in all corners, it will probably work for any variation.
- ❑ Describe corner with four letters (T, F, S)
 - nMOS speed
 - pMOS speed
 - Voltage
 - Temperature

Important Corners

- ❑ Some critical simulation corners include

Purpose	nMOS	pMOS	V_{DD}	Temp
Cycle time				
Power				
Subthreshold leakage				

Inverter Static Characteristics

Dr.Mohammad Abdel-Majeed

Assistant Professor


University of Jordan

Combinational Logic

- A combinational logic cell, logic circuit or gate is generally a multiple input, single output system that performs a Boolean function
 - In the positive logic convention, logic 1 is shown by high voltage V_{DD} and logic 0 by low voltage of zero


Ideal Inverter and Inverter Threshold Voltage

- Logic symbol & truth table

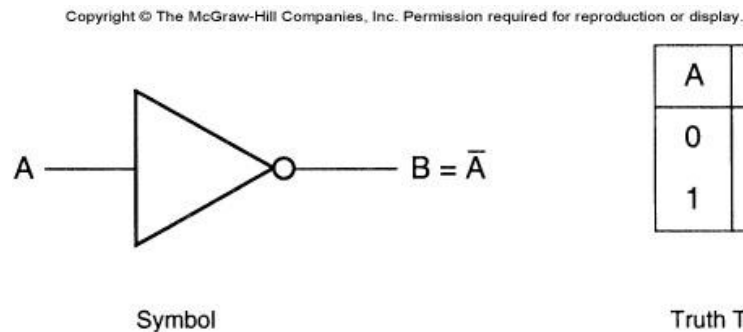


A	B
0	1
1	0

Truth Table

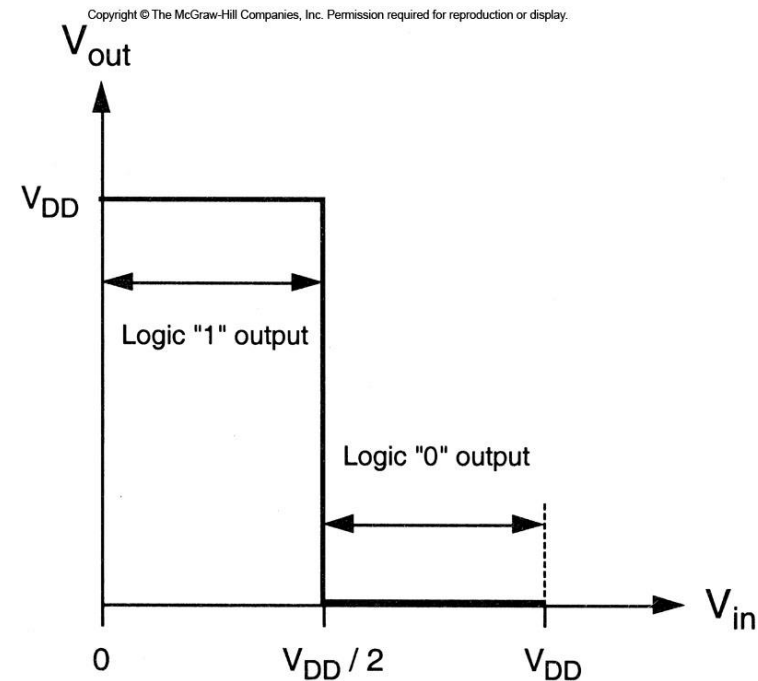


VTC of an NMOS inverter

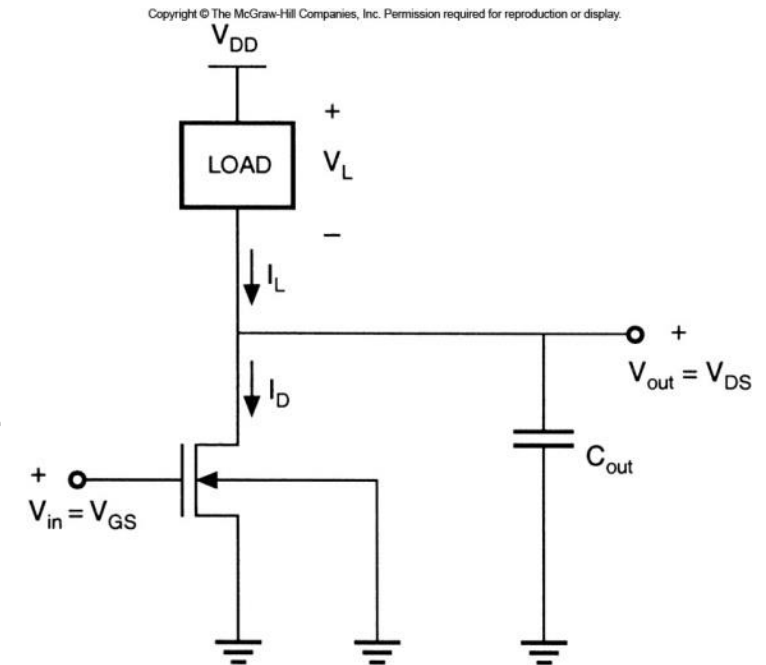- V_{in} is _____
- V_{out} is _____
- $V_{SB} =$ _____
- The circuit connected to the output node can be represented using the capacitance C_{out}
- $I_D = I_L$ (_____). By solving this equation we can derive the VTC




VTC

 

nMOS Inverter: Schematic & VTC

 - $V_{OH} : V_{OUT,MAX}$ when the output level is logic "1"
- $V_{OL} : V_{OUT,MIN}$ when the output level is logic "0"
- $V_{IL} : V_{IN,MAX}$ which can be *interpreted* as logic "0"
- $V_{IH} : V_{IN,MIN}$ which can be *interpreted* as logic "1"
- Inverter threshold Voltage V_M is defined as the point where $V_{in} = V_{out}$




- _____ $\leq V_{in} \leq$ _____
 - V_{in} is interpreted as “0”
 - This means that V_{IL} is low enough to ensure a logic 1 output
- _____ $\leq V_{in} \leq$ _____
 - V_{in} is interpreted as “1”
 - This means that V_{IH} is low enough to ensure a logic 0 output


Tolerance

- Ability to interpret range of values as logic 0 or logic 1 allows the circuits to operate with certain _____
- Noise sources
 - Unwanted capacitive coupling
 - Radiations
 - ...

Noise Margin

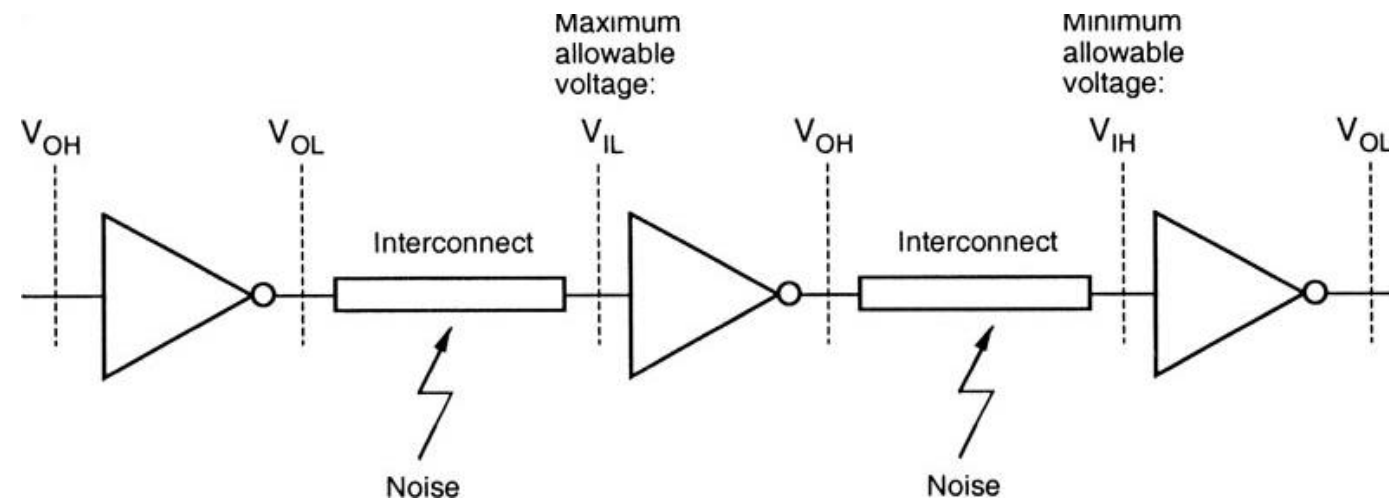


Input Noise Margin

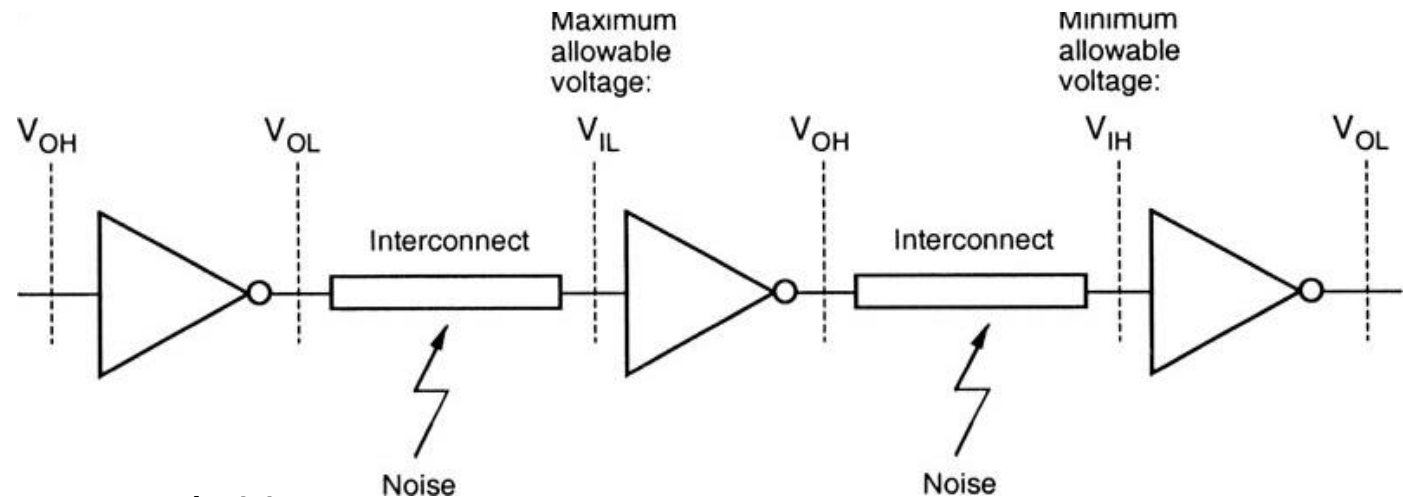


- By definition the output of the first inverter is V_{OL}
- The output signal of the 1st inverter will be perturbed during transmission because of on-chip interconnect
- If the input voltage of the 2nd inverter is smaller than V_{OL} , then this signal will be interpreted correctly as a logic "0" input by 2nd inverter
- But if the input voltage becomes larger than V_{IL} , then it may not be interpreted correctly by the inverter
- Thus, V_{IL} is the maximum allowable voltage at the input of the 2nd inverter

Output Noise Margin

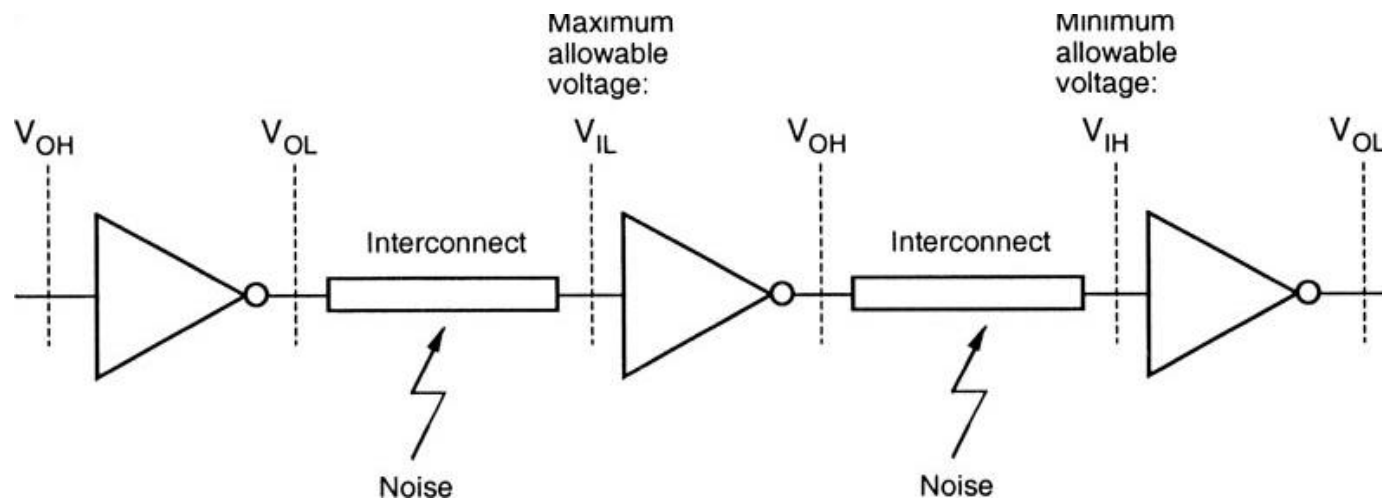


Input Noise Margin

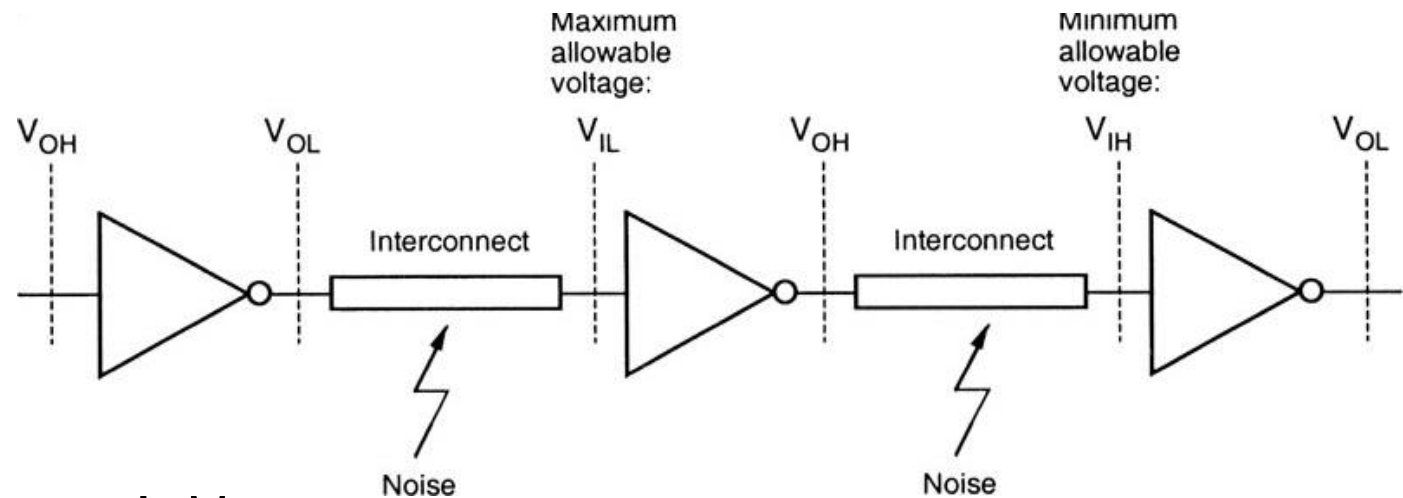

- Assume the output of the 2nd inverter is V_{OH}
- Input of the 3rd inverter will be different from V_{OH} due to noise interference
- If the input voltage of the 3rd inverter is larger than V_{OH} this signal is interpreted correctly as a logic "1"
- If the voltage level drops below V_{IH} , the input may not be interpreted as a logic "1"
- Therefore, V_{IH} is the minimum allowable voltage at the input of the 3rd inverter

Noise Margin

- $NM_L =$
- $NM_H =$

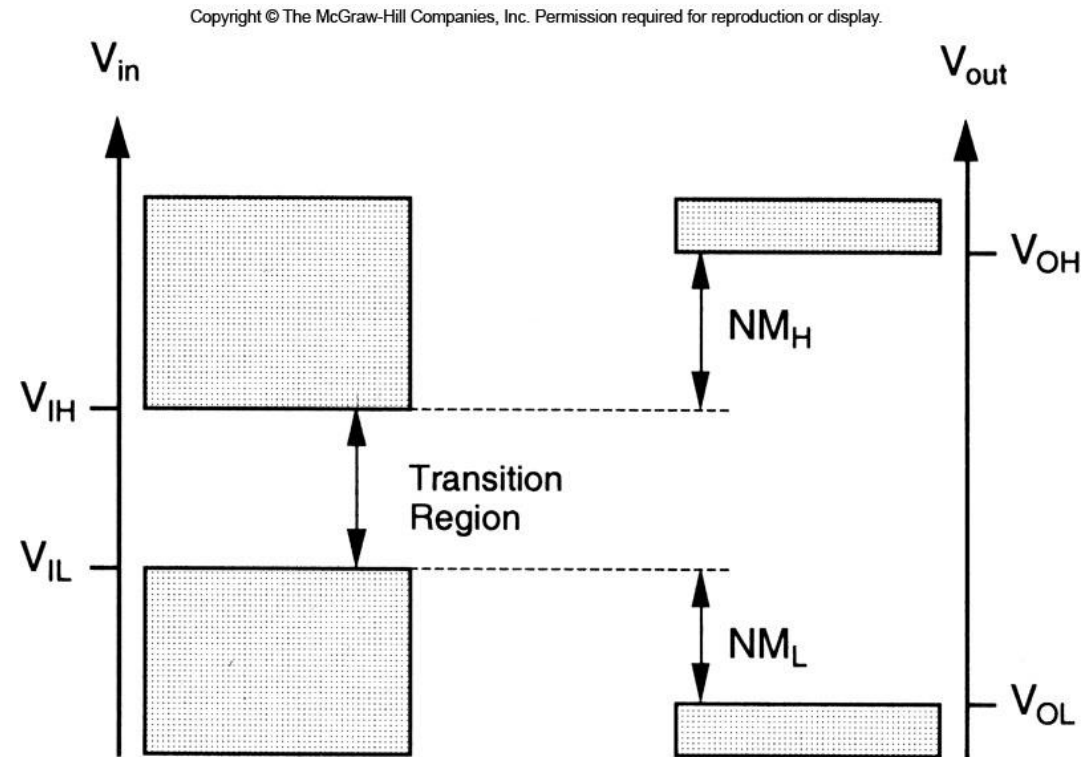

Power



- Lower consumption extends battery-based operation time for portable systems
- DC power dissipation: $P_{DC} = V_{DD} \cdot I_{DC}$
- DC power is input and output voltage dependent
- To calculate avg DC power assume 50% of the time input is at $V_{in} = \text{low}$ and 50% at $V_{in} = \text{high}$
 - $P_{DC} = 0.5 V_{DD} \{I_{DC} (V_{in} = \text{low}) + I_{DC} (V_{in} = \text{high})\}$
- Inverter type and its design affects the power dissipation significantly

Inverter

- Resistive Load Inverter
- NMOS depletion load inverter
- CMOS inverter


Resistive-Load Inverter

  - Resistive-load inverter circuit & its VTC





Resistive-Load Inverter

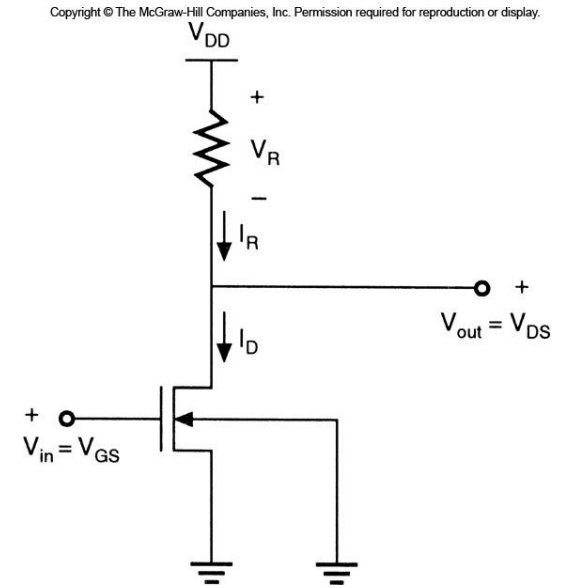- Resistive-load inverter circuit & its VTC
- $V_{in} < V_{T0}$, nMOS off
 - $I_D = \underline{\hspace{2cm}}$
 - $V_{out} = \underline{\hspace{2cm}}$
- $V_{in} > V_{T0}$, nMOS in sat.
 - $V_{ds} = \underline{\hspace{2cm}} > V_{in} - V_{T0}$
 - $I_R = \underline{\hspace{2cm}}$
- $V_{in} > V_{T0}$ & $V_{out} < V_{DSAT}$, nMOS in lin.
 - $I_R = \underline{\hspace{2cm}}$





Calculation of V_{OH}

  - $V_{out} = V_{dd} - R_L \cdot I_R$
- When $V_{in} < V_{T0}$
 - Transistor is in _____
 - $I_R = I_D = 0$
 - $V_{OH} =$ _____



Calculation of V_{OL}

  - V_{OL} is obtained when $V_{in} = V_{OH} = \underline{\hspace{2cm}}$
 - V_{in}
 - NMOS is in
 - Using KCL $I_R = I_D$





Calculation of V_{OL}

- V_{OL} is obtained when $V_{in} = V_{OH} = \underline{\hspace{2cm}}$
 - V_{in}
 - NMOS is in
 - Using KCL $I_R = I_D$
 - $(V_{DD} - V_{OL}) / R_L = B/2 \cdot (2 \cdot (V_{DD} - V_{T0}) \cdot V_{OL} - V_{DD}^2)$



$$V_{OL} = V_{DD} - V_{T0} + \frac{1}{k_n R_L} - \sqrt{\left(V_{DD} - V_{T0} + \frac{1}{k_n R_L}\right)^2 - \frac{2V_{DD}}{k_n R_L}}$$

  - Use the KCL and V_{OL} definition to find the value of V_{OL}





Calculation of V_{IL}

  - At $V_{in} = V_{IL}$ $dV_{out}/dV_{in} = -1$
- NMOS is in _____
 - Using KCL $I_R = I_D$





Calculation of V_{IL}

  - At $V_{in} = V_{IL}$ $dV_{out}/dV_{in} = -1$
- NMOS is in _____
 - Using KCL $I_R = I_D$
 - $(V_{DD} - V_{out})/R_L = B/2 (V_{in} - V_{T0})^2$ (eq1)
- Differentiate both side
 - $-1/R_L \cdot (dV_{out}/dV_{in}) = B(V_{IL} - V_{T0})$
- substitute $dV_{out}/dV_{in} = -1$
 - $-1/R_L \cdot (-1) = B(V_{IL} - V_{T0})$
 - $V_{IL} = V_{T0} + 1/(B \cdot R_L)$ (eq2)



Calculation of V_{IH}

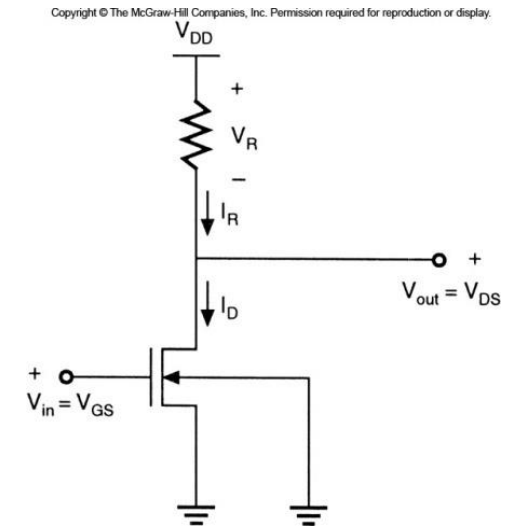 - At $V_{in} = V_{IH}$ $dV_{out}/dV_{in} = -1$
- V_{in} is slightly larger than V_{OL}
- NMOS is in _____



Calculation of V_{IH}

- At $V_{in} = V_{IH}$ $dV_{out}/dV_{in} = -1$
- V_{in} is slightly larger than V_{OL}
- NMOS is in _____

- Using KCL $I_R = I_D$



- $(V_{DD} - V_{out})/R_L = B/2 \cdot (2 \cdot (V_{in} - V_{T0}) \cdot V_{out} - V_{out}^2) \dots \text{eq}(1)$

- Differentiate both side

- $-1/R_L \cdot (dV_{out}/dV_{in}) = B/2 \cdot (2 \cdot (V_{in} - V_{T0}) \cdot dV_{out}/dV_{in} - 2V_{out} \cdot dV_{out}/dV_{in}) \dots \text{eq}(2)$

- Solve eq1 and eq2 and substitute $dV_{out}/dV_{in} = -1$ and V_{in} with V_{IH}
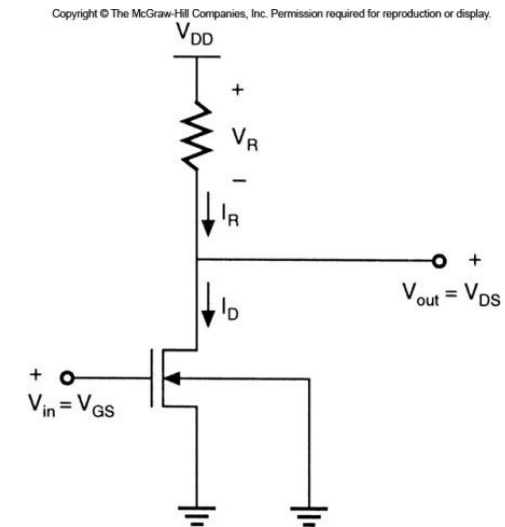 
$$V_{IH} = V_{T0} + \sqrt{\frac{8}{3} \cdot \frac{V_{DD}}{k_n R_L}} - \frac{1}{k_n R_L}$$




VTC, Power & Chip Area

- VTC of the resistive-load inverter for different $(k_n \cdot R_L)$

$$V_{IH} = V_{T0} + \sqrt{\frac{8}{3} \cdot \frac{V_{DD}}{k_n R_L} - \frac{1}{k_n R_L}}$$

$$V_{IL} = V_{T0} + \frac{1}{k_n R_L}$$

 

Power

- $V_{in} = V_{OH}$
 - NMOS is in Linear
 - $I_D = I_R = (V_{dd} - V_{OL})/R_L$
- $V_{in} = V_{OL}$
 - NMOS is cutoff
 - $I_D = 0$
- $P_{DC}(\text{Average}) = (V_{dd} / 2) \cdot (V_{dd} - V_{OL})/R_L$

Resistor

- Two possibilities for fabricating resistors:
 - Diffused resistor: an isolated n or p-type diffusion region.
 - 20-100 ohm/square: needs large area not practical for VLSI
 - Metal Resistor
 - Undoped polysilicon resistor:
 - mask off during poly doping to create about 10M ohm/square.


Example 5.1 - Inverter Design

- Resistive-load inverter circuit

- $V_{DD}=5V$, $\mu^*C_{ox}=30\mu A/V^2$, $V_{T0}=1V$
- $V_{OL}=200mV$

- Determine (W/L) ratio of the driver T_r . And R_L to obtain the required V_{OL}

 
- $V_{out} = \underline{\hspace{2cm}}$, $V_{in} = \underline{\hspace{2cm}}$. NMOS is in $\underline{\hspace{2cm}}$




(W/L)-Ratio	Load resistor (R_L [k Ω])	DC power consumption ($P_{DC,avg}$ [μ W])
1		
2		
3		
4		
5		
6		

Inverters with MOSFET Load

- Enhancement-Load Inverter

 


(a)

 

(b)

Inverters with MOSFET Load

- Enhancement-Load Inverter

 

(a)


Load NMOS operates in _____

$V_{OH} =$ _____

Power

Inverters with MOSFET Load

- Enhancement-Load Inverter

 

(b)


Load NMOS operates in _____

$V_{OH} =$ _____


Power

CMOS Inverter

 - Has NMOS and PMOS Transistors
- Cons
 - Complexity
- Pros
 - Power
 - VTC is sharp




(a)

 

Operation

 
- $V_{GS,n}$ _____
- $V_{GS,p}$ _____
- $V_{DS,n}$ _____
- $V_{DS,p}$ _____



(a)

Operation

 
- $V_{GS,n} < V_{th,n}$
- NMOS is OFF
- PMOS operates in _____



(a)

Operation

 
- $V_{GS,p} > V_{th,p}$
- PMOS is OFF
- NMOS operates in _____



(a)

Operation

 
- $V_{in} = V_{IL}$
- NMOS is in _____
- PMOS is in _____



(a)

Operation

 
- $V_{in} = V_M = V_{DD}/2$
- NMOS is in _____
- PMOS is in _____




(a)

Operation

 - $V_{in} = V_{IH}$
- NMOS is in _____
- PMOS is in _____



(a)

 

Region	V_{in} in the region	V_{out}	NMOS	PMOS
A	$< V_{th,n}$	V_{OH}	Cut-off	Linear
B	V_{IL}	$\sim V_{OH}$	Sat.	Linear
C	V_M	V_M	Sat.	Sat.
D	V_{IH}	$\sim V_{OL}$	Linear	Sat.
E	$> V_{tdd} + V_{th,p}$	V_{OL}	Linear	Cut-off

V_{OH} & V_{OL}

- $V_{OH} =$ _____

- $V_{OL} =$ _____

V_{IL}

- $V_{in} = V_{IL} \rightarrow dV_{out}/dV_{in} = -1$
- NMOS is in _____
- PMOS is in _____

V_{IL}

- $V_{in} = V_{IL} \rightarrow dV_{out}/dV_{in} = -1$
- NMOS is in _____
- PMOS is in _____
- $B_n/2(V_{GS,n} - V_{th,n})^2 = B_p/2 (2 \cdot (V_{GS,p} - V_{th,p}) \cdot V_{DS,p} - V_{DS,p}^2)$

$$V_{IL} = \frac{2V_{out} + V_{T0,p} - V_{DD} + k_R V_{T0,n}}{1 + k_R}$$

- $K_R = K_n/K_p$

V_{IH}

- $V_{in} = V_{IH} \rightarrow dV_{out}/dV_{in} = -1$
- NMOS is in _____
- PMOS is in _____

$$V_{IH}$$

- $V_{in} = V_{IH} \rightarrow dV_{out}/dV_{in} = -1$
- NMOS is in _____
- PMOS is in _____
- $B_p/2(V_{GS,p} - V_{th,p})^2 = B_n/2 (2 \cdot (V_{GS,n} - V_{th,n}) \cdot V_{DS,n} - V_{DS,n}^2)$

$$V_{IH} = \frac{V_{DD} + V_{T0,p} + k_R \cdot (2V_{out} + V_{T0,n})}{1 + k_R}$$

- $K_R = K_n/K_p$


Inverter threshold voltage

- $V_{in} = V_{out}$
- NMOS and PMOS are in Saturation


Inverter threshold voltage

- $V_{in} = V_{out}$
- NMOS and PMOS are in Saturation

$$V_{th} = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R}} \cdot (V_{DD} - |V_{T0,p}|)}{\left(1 + \sqrt{\frac{1}{k_R}}\right)}$$

 

Design of CMOS Inverter

 

Design of CMOS Inverters (2)

- If symmetric CMOS inverter with $V_{T0,n} = |V_{T0,p}|$ and $k_R = 1$,


$$V_{IL} = \frac{1}{8} \cdot (3V_{DD} + 2V_{T0,n})$$

$$V_{IH} = \frac{1}{8} \cdot (5V_{DD} - 2V_{T0,n})$$

→ $V_{IL} + V_{IH} = V_{DD}$
 in a symmetric inverter

→ $NM_L = V_{IL} - V_{OL} = V_{IL}$
 $NM_H = V_{OH} - V_{IH} = V_{DD} - V_{IH}$

→ $NM_L = NM_H = V_{IL}$

 

Inverter Transient Characteristics

Dr.Mohammad Abdel-Majeed


Assistant Professor


University of Jordan

Timing Analysis


- Delay models are required for _____ and the _____



Example

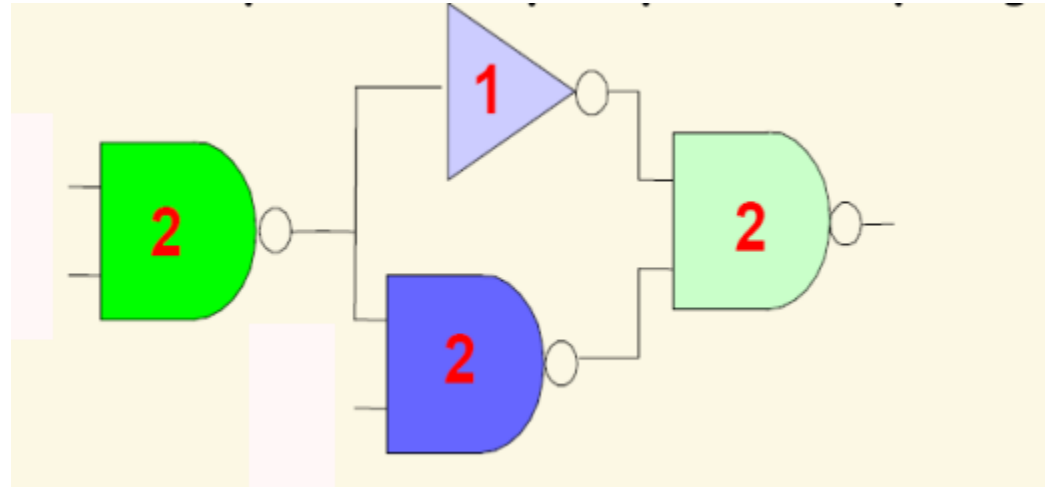


 


Inverter delay

 

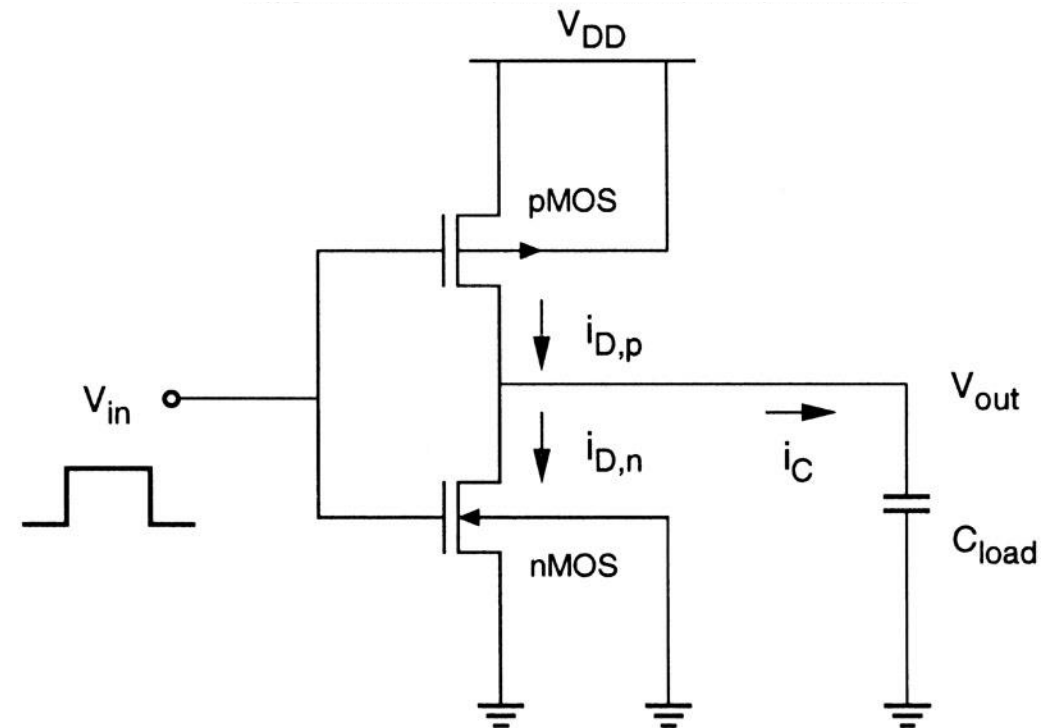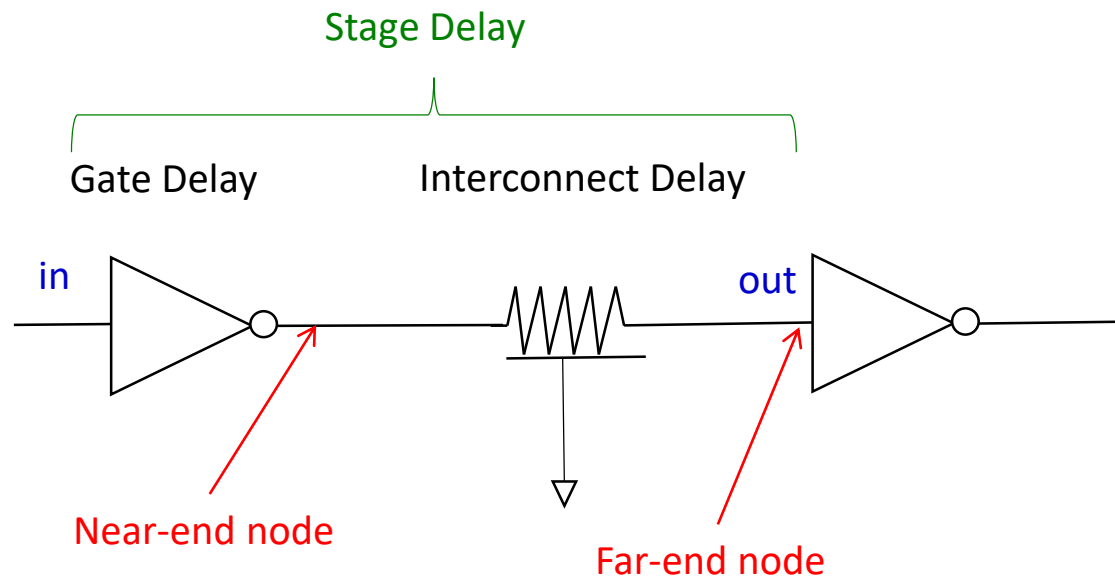


 


- Load = _____

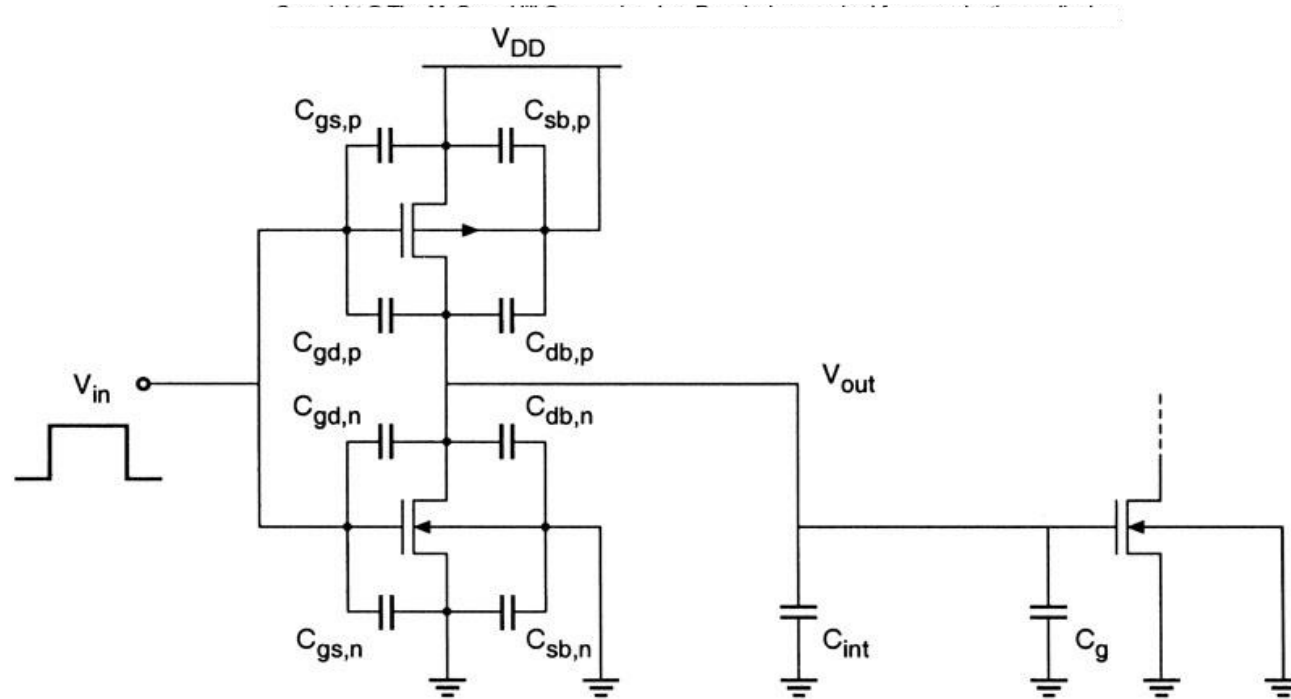


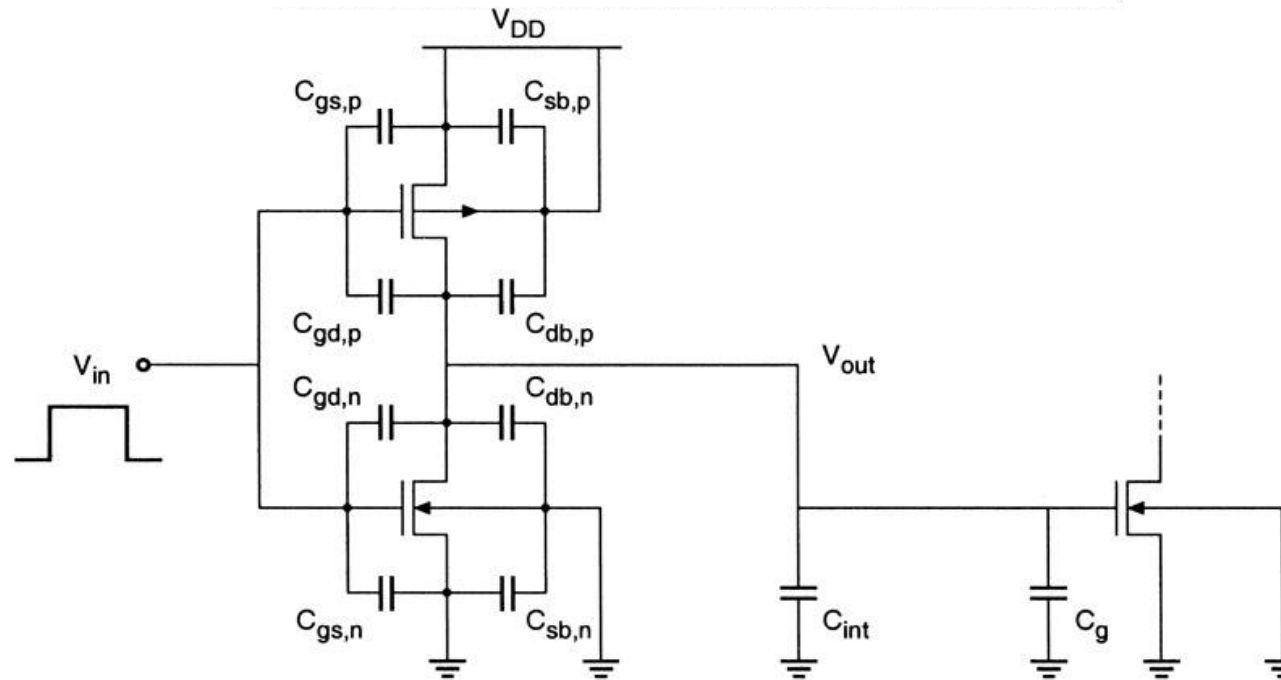- $C_{load} = C_{gd,n} + C_{gd,p} + C_{db,n} + C_{db,p} + C_{int} + C_g$



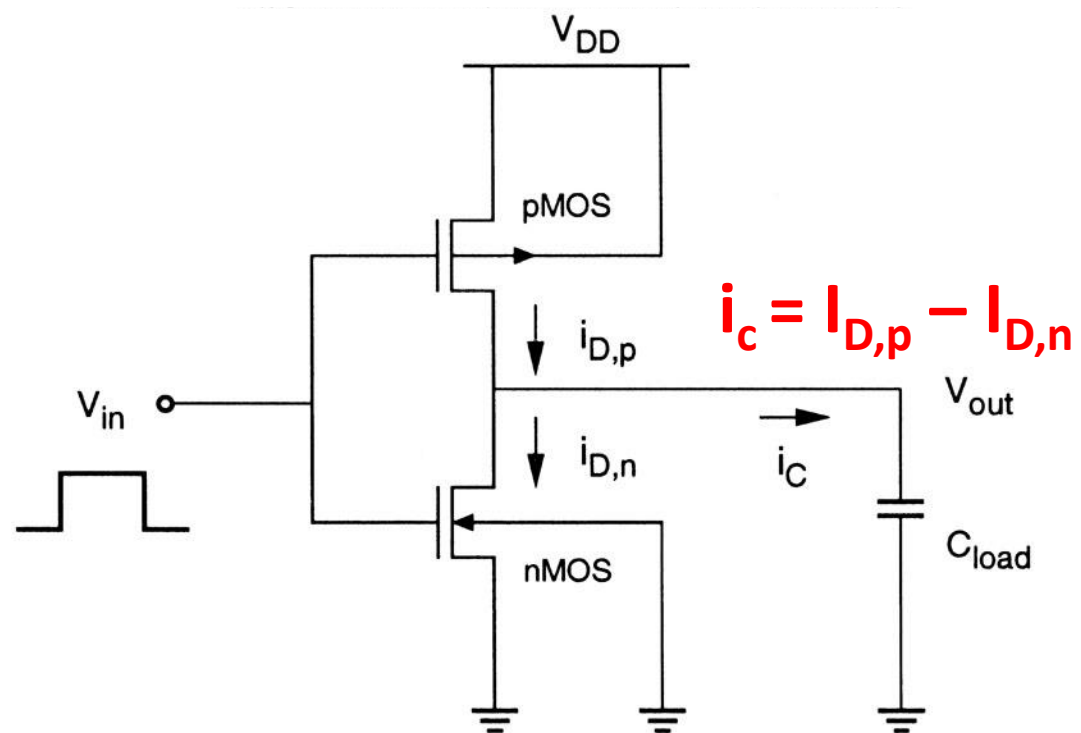


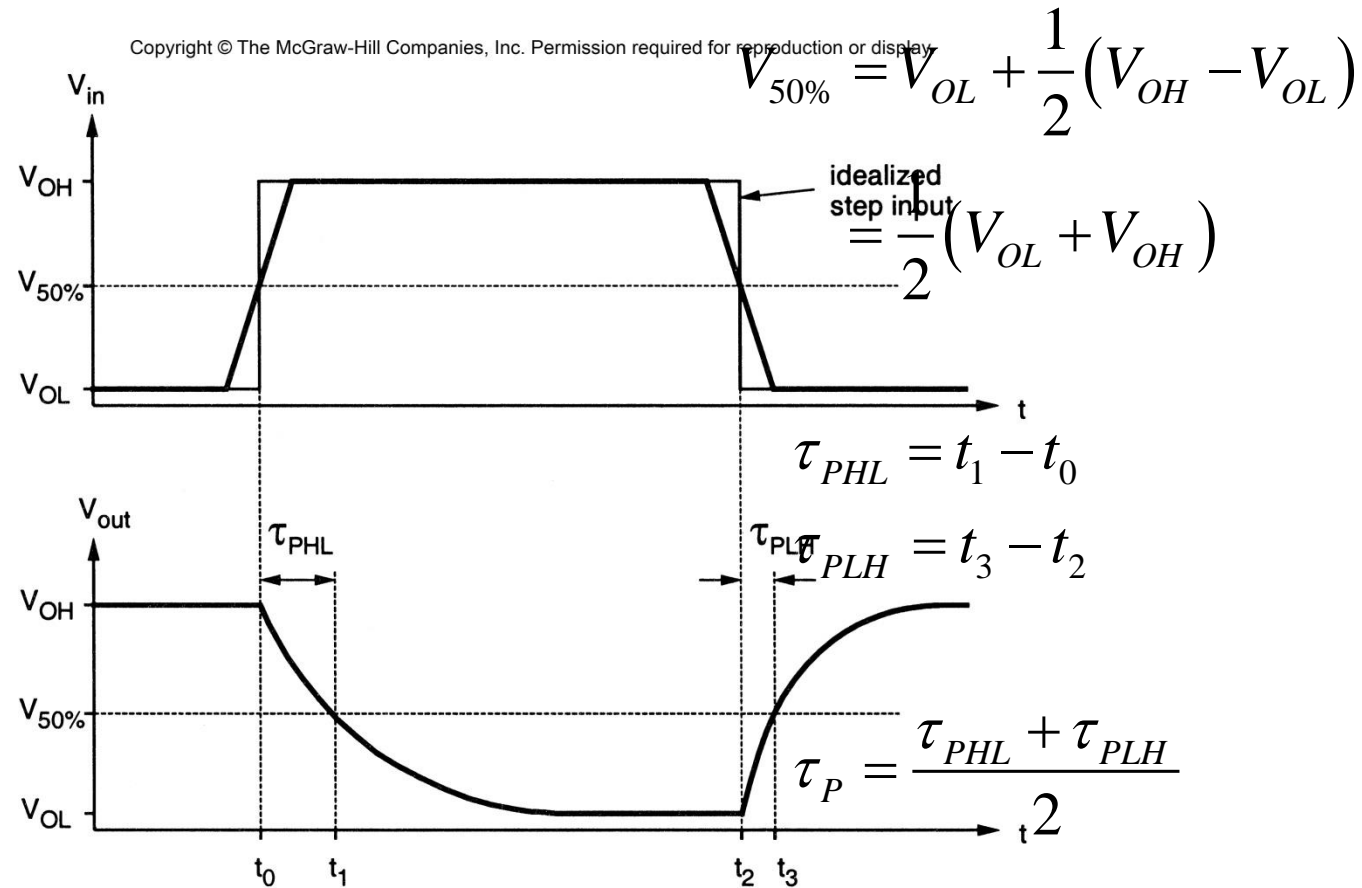Delay-Time Definitions: Propagation Delays



Delay-Time Definitions: Rise & Fall Times

 Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$V_{10\%} = V_{OL} + 0.1 \cdot (V_{OH} - V_{OL}) \quad \tau_{fall} = t_B - t_A$$

$$V_{90\%} = V_{OL} + 0.9 \cdot (V_{OH} - V_{OL}) \quad \tau_{rise} = t_D - t_C$$

Calculation of Propagation Delay (AVG current method)

- Simplest method : estimating the average capacitance current

Calculation of Propagation Delay (AVG current method)

- Simplest method : estimating the average capacitance current

$$\tau_{PHL} = \frac{C_{load} \cdot \Delta V_{HL}}{I_{avg,HL}} = \frac{C_{load} \cdot (V_{OH} - V_{50\%})}{I_{avg,HL}}$$
$$\tau_{PLH} = \frac{C_{load} \cdot \Delta V_{LH}}{I_{avg,LH}} = \frac{C_{load} \cdot (V_{50\%} - V_{OL})}{I_{avg,LH}}$$

Calculation of Propagation Delay (AVG current method)

- Simplest method : estimating the average capacitance current

$$\tau_{PHL} = \frac{C_{load} \cdot \Delta V_{HL}}{I_{avg,HL}} = \frac{C_{load} \cdot (V_{OH} - V_{50\%})}{I_{avg,HL}}$$

$$\tau_{PLH} = \frac{C_{load} \cdot \Delta V_{LH}}{I_{avg,LH}} = \frac{C_{load} \cdot (V_{50\%} - V_{OL})}{I_{avg,LH}}$$


- The average current

$$I_{avg,HL} = \frac{1}{2} \left[i_C (V_{in} = V_{OH}, V_{out} = V_{OH}) + i_C (V_{in} = V_{OH}, V_{out} = V_{50\%}) \right]$$

$$I_{avg,LH} = \frac{1}{2} \left[i_C (V_{in} = V_{OL}, V_{out} = V_{50\%}) + i_C (V_{in} = V_{OL}, V_{out} = V_{OL}) \right]$$

Calculation of Rise and fall time (AVG current method)

 - $T_{rise} = t_D - t_C = \frac{C_{load}(V_{90\%} - V_{10\%})}{I_{avg, rise}}$
- $I_{avg, rise} = \frac{I_C + I_D}{2}$
- $I_{avg, rise} = \frac{I_{sd,p}(V_{in}=VOL, V_{out}=V_{10\%}) + I_{sd,p}(V_{in}=VOL, V_{out}=V_{90\%})}{2}$




Example

- CMOS inverter with NMOS $\mu C_{ox} = 20\mu A/V^2$, $(W/L)_n = 10$, $V_{t,n} = 1V$,
 $C_{load} = 1pF$ and $V_{DD} = 5V$
 - Calculate output fall time


Example 6.4 (2)

- The falling-output propagation delay

 


Example 6.4 (3)

- The (Area x Delay) product

 

Ring oscillator

CMOS Ring Oscillator Circuit

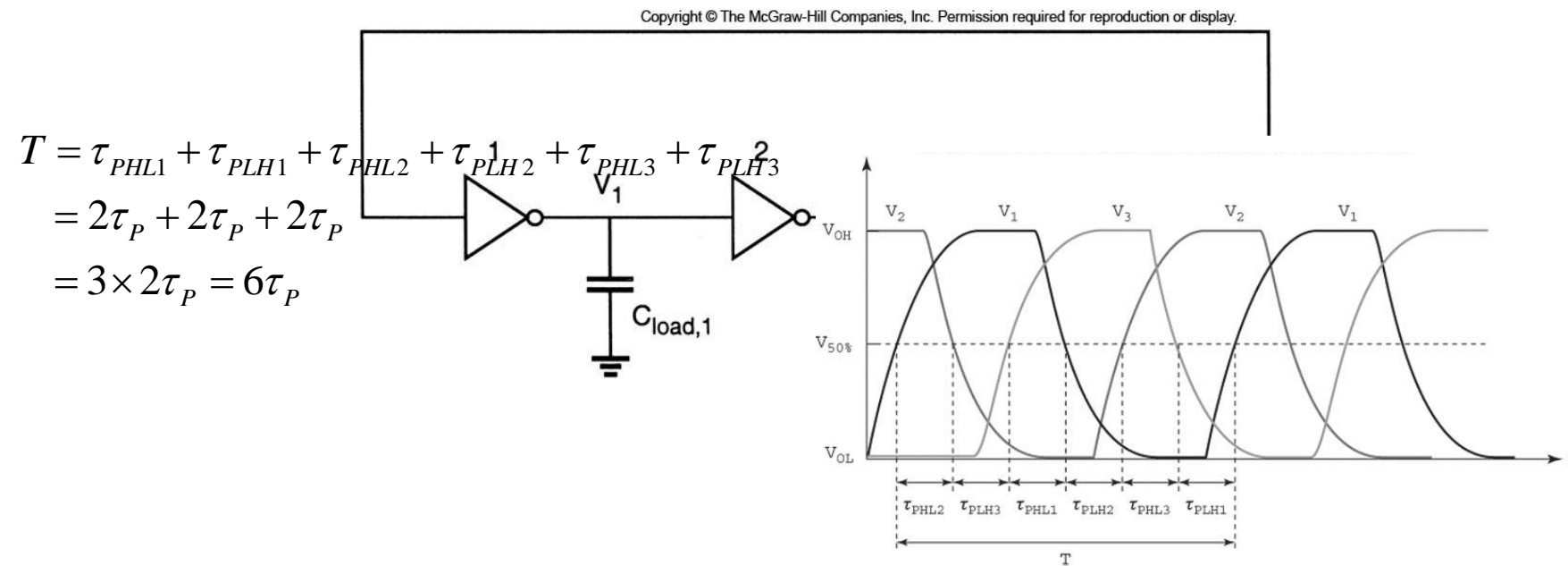


MOSFET Capacitor

- The on-chip capacitance found in MOS circuit are in general complicated functions of the layout geometries and the manufacturing processes.
- We will develop simple approximations for the on-chip MOSFET capacitances.

MOSFET Capacitor (2)

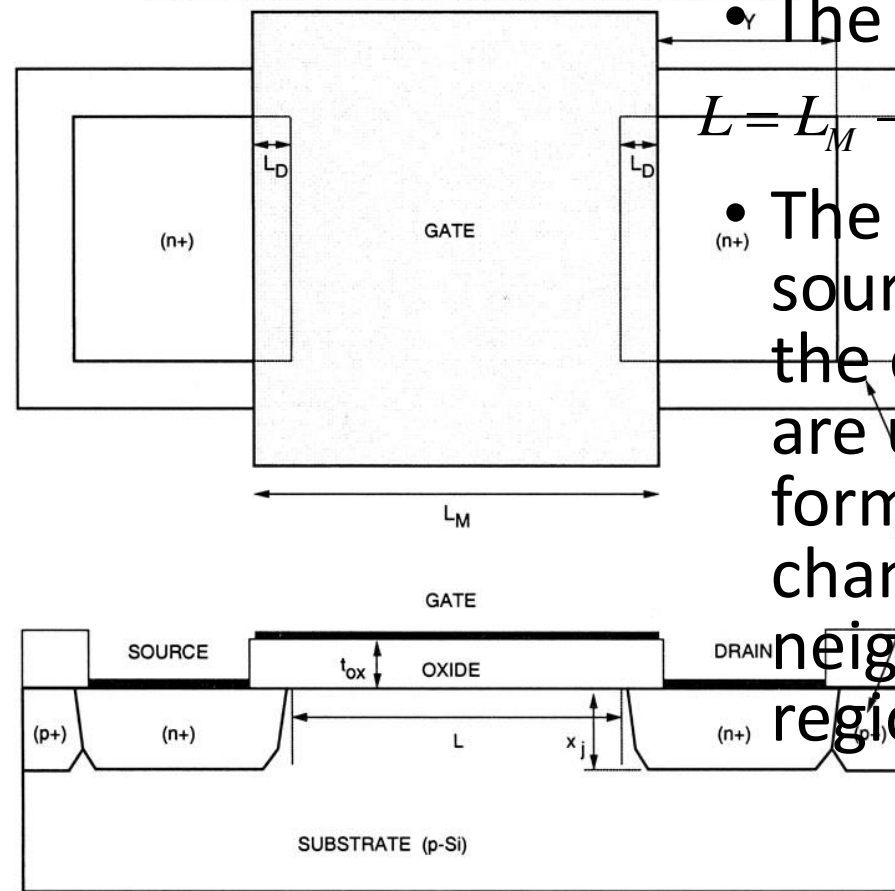Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




- The channel length is given by


$$L = L_M - 2 \cdot L_D \quad (3.117)$$

- The p+ regions around the source and drain, namely the channel-stop implants, are used to prevent the formation of any unwanted channels between two neighboring n+ diffusion regions

MOSFET Capacitor (3)

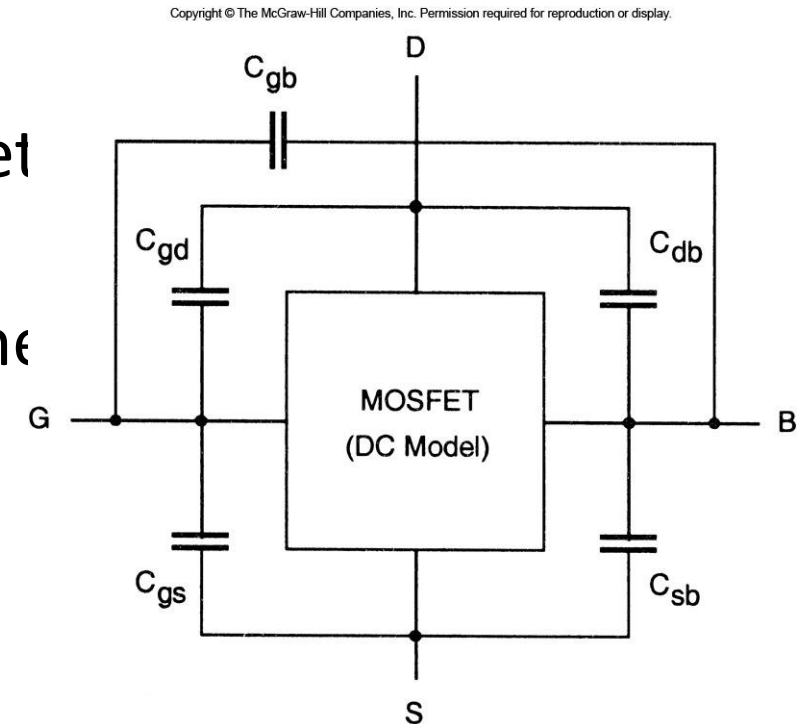- MOSFET parasitic capacitances are observed between terminals.
- Most of the capacitances are distributed and therefore complex.
- Capacitances can be modeled as
 - Lumped
 - distributed
- Parasitic device capacitances can be classified into two major groups
 - Oxide-related capacitance
 - Junction capacitance



 

Oxide-related Capacitances (1)

- The gate electrode overlaps both the source region and the drain region at the edges.
 - The two overlap capacitances that arise as a result of this structural arrangement.
 - $C_{GD}(\text{overlap})$
 - $C_{GS}(\text{overlap})$
 - The overlap capacitances can be found as

$$C_{GS}(\text{overlap}) = C_{ox} \cdot W \cdot L_D$$




$$C_{GD}(\text{overlap}) = C_{ox} \cdot W \cdot L_D$$

with $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$

Oxide-related Capacitances (2)

- Capacitances which result from the interaction between the gate voltage and the channel charge.
 - C_{gs} , C_{gd} , C_{gb}

   Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Oxide-related Capacitances (2)

- Cut-off mode

- The surface is not inverted.
- No conducting channel between source and drain


- $C_{gs} = C_{gd} = 0$

(3.120)

- The gate-to-substrate capacitance can be approximated by

$$C_{gb} = C_{ox} \cdot W \cdot L$$

 Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Oxide-related Capacitances (2)


- Linear mode

- The inverted channel extends across the MOSFET.
- Conducting inversion layer shields the substrate from the gate electric field :

$$C_{gb} = 0$$

- The distributed gate-to-channel capacitance (equal S,D)

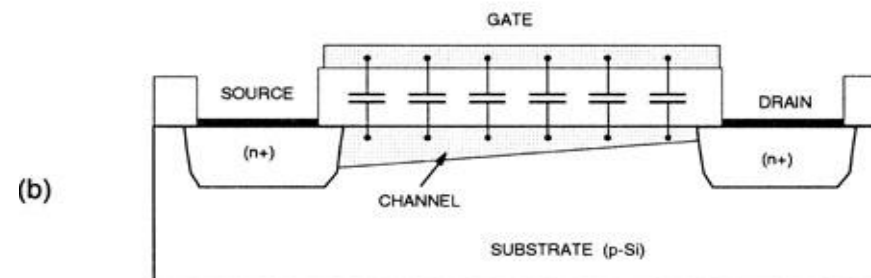
$$C_{gs} \approx C_{gd} \approx \frac{1}{2} \cdot C_{ox} \cdot W \cdot L$$



Oxide-related Capacitances (3)

- Saturation mode
 - The inversion region is pinched off.
 - The gate-to-drain capacitance component is equal to zero
 - $C_{gd} = 0$
 - Source still linked to the conducting channel.
 - Shielding effect still remain : $C_{gb} = 0$
 - The distributed gate-to-channel capacitance as seen between the gate and the source can be approximated by
 
$$C_{gs} \cong \frac{2}{3} \cdot C_{ox} \cdot W \cdot L$$




Oxide-related Capacitances (4)

Capacitance	Cut-off	Linear	Saturation
C_{gb} (total)	$C_{ox}WL$	0	0
C_{gd} (total)	$C_{ox}WL_D$	$1/2C_{ox}WL + C_{ox}WL_D$	$C_{ox}WL_D$
C_{gs} (total)	$C_{ox}WL_D$	$1/2C_{ox}WL + C_{ox}WL_D$	$2/3C_{ox}WL + C_{ox}WL_D$

- We have to combine the distributed C_{gs} and C_{gd} values found here with the relevant overlap capacitance values, in order to calculate the total capacitance between the external device terminals.


Oxide-related Capacitances (5)

 - Variation of the distributed (gate-to-channel) oxide capacitances as function of gate-to-source voltage.



Junction Capacitances (1)

 - Consider the voltage-dependent source-substrate and drain-substrate junction capacitances : C_{sb} , C_{db}




Junction	Area	Type
1	$W \cdot x_j$	n+/p
2	$Y \cdot x_j$	n+/p+
3	$W \cdot x_j$	n+/p+
4	$Y \cdot x_j$	n+/p+
5	$W \cdot Y$	n+/p

Junction Capacitances (2)


- C_{sb} and C_{db} are due to the depletion charge surrounding the respective source or drain diffusion regions embedded in the substrate.
 - both of these junctions are reverse-biased under normal operating conditions.
 - The amount of junction capacitance is a function of the applied terminal voltages.
 - Junction capacitances associated with sidewalls (2,3,4) will be different from the other junction capacitance.

Estimation of Interconnect Parasitics

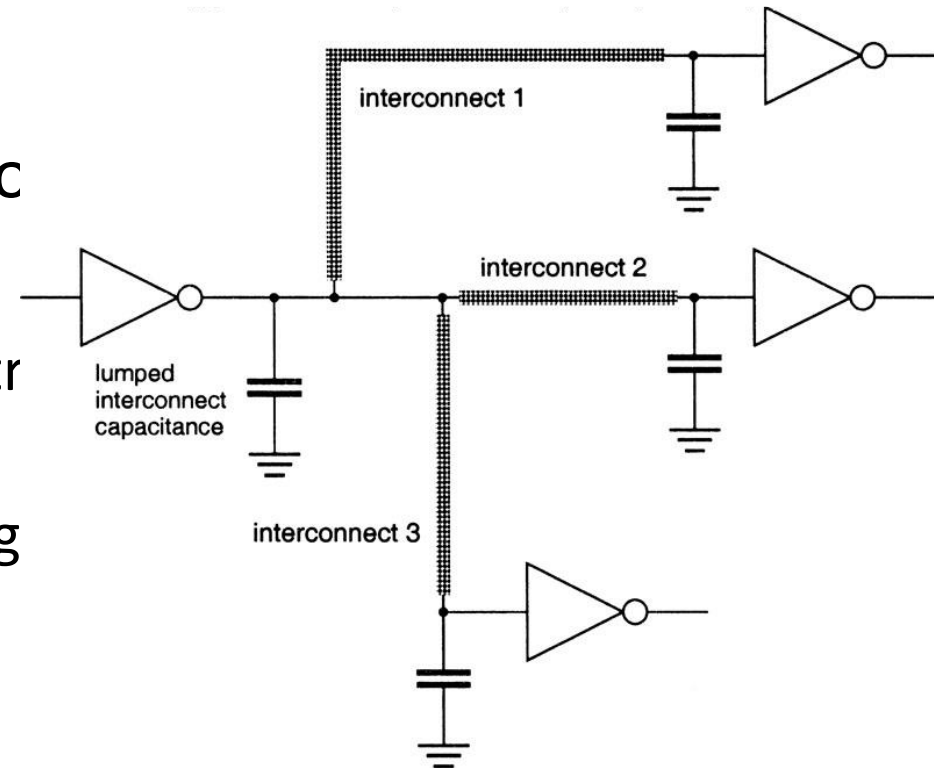- Main components of the output t_c
 - Internal parasitic capacitances of t_r
 - Interconnect capacitances
 - Input capacitances of the fan-out t_d




Interconnect Delay

 

- Dealing with the implications and optimizing a system for speed
 - Estimating the interconnect parasitics in a large chip
 - Simulating the transient effects.


Statistical distribution

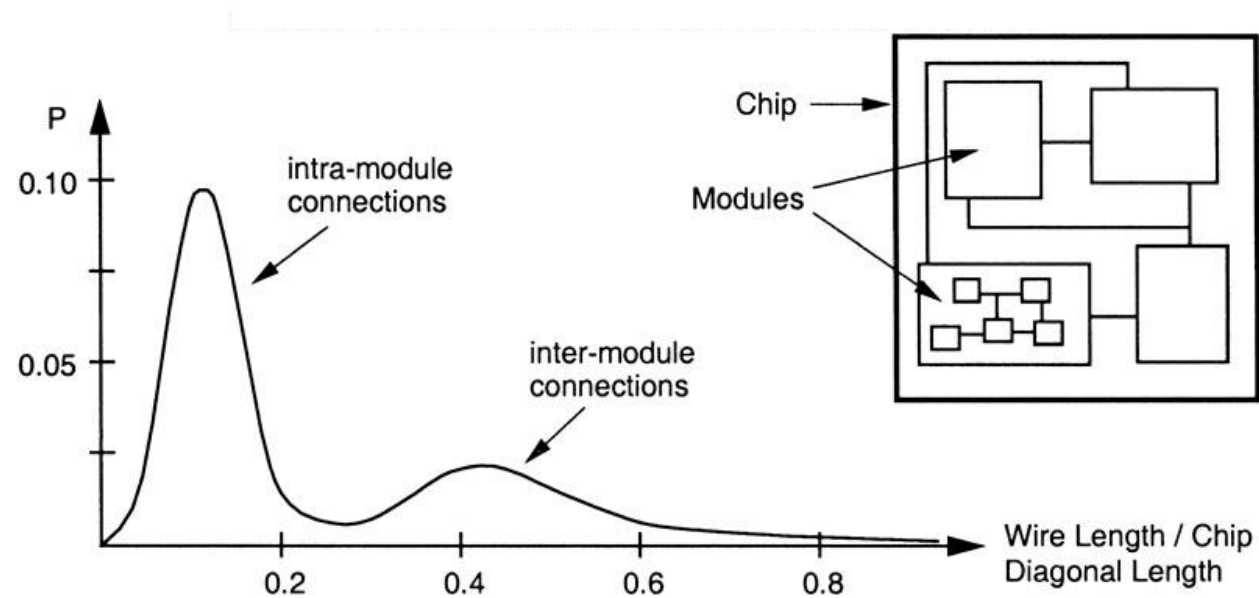- Statistical distribution of interconnection length on a typical chip




Interconnect Capacitance Estimation (1)

 - A simplified view of six interconnections on three different levels




Interconnect Capacitance Estimation (2)

- The section of a single interconnect

 

Interconnect Capacitance Estimation (3)

- The total parasitic capacitance

 

Thickness value of different layers

Field oxide thickness	3μm
Gate oxide thickness	2.6nm
Polysilicon thickness	1μm (minimum width 0.06μm)
Poly-metal oxide thickness	1.1μm
Metal 1 thickness	1.8μm (minimum width 0.09μm)
Metal 2~7 thickness	2.2μm (minimum width 0.1μm)
Metal 8~9 thickness	9μm (minimum width 0.4μm)
Via oxide thickness (PO-M1)	1.75μm
Via oxide thickness (M1-M6)	2.2μm
Via oxide thickness (M6-M9)	9μm
n⁺ junction depth	23nm
p⁺ junction depth	28nm
n-well junction depth	3μm

Interconnect Resistance Estimation

- Total resistance in indicated current direction


$$R_{wire} = \rho \cdot \frac{l}{w \cdot t} = R_{sheet} \left(\frac{l}{w} \right)$$

- The sheet resistivity of the line

$$R_{sheet} = \left(\frac{\rho}{t} \right)$$

RC Delay Models


- Simple lumped RC model & T-model

 


$$V_{out}(t) = V_{DD} \left(1 - \exp\left(-\frac{t}{RC}\right) \right)$$

$$V_{50\%} = V_{DD} \left(1 - \exp\left(-\frac{\tau_{PLH}}{RC}\right) \right)$$


$$\tau_{PLH} \approx 0.69RC$$

 


- Distributed RC ladder network model

 


Various RC Models

 


(a) lumped RC model

 


(b) T-model

 


(c) T2-model

 

(d) π -model

 


(e) π 2-model

 

(f) π 3-model

The Elmore Delay (1)

 

$$\tau_{Di} = \sum_{j=1}^N C_j \sum_{\substack{\text{for all} \\ k \in P_{ij}}} R_k$$

- The general topology of the RC tree network
 - Let P_i denote the unique path from the input node to node i , $i = 1, 2, 3, \dots, N$.
 - Let $P_{ij} = P_i \ll P_j$ denote the portion of the path between the input and the node i , which is *common* to the path between the input and node j .



The Elmore Delay (2)

$$\tau_{D7} = R_1 C_1 + R_1 C_2 + R_1 C_3 + R_1 C_4 + R_1 C_5 + (R_1 + R_6) C_6$$

$$+ (R_1 + R_6 + R_7) C_7 + (R_1 + R_6 + R_7) C_8$$

$$\tau_{D5} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2) C_3 + (R_1 + R_2 + R_4) C_4$$
  
$$+ (R_1 + R_2 + R_4 + R_5) C_5 + R_1 C_6 + R_1 C_7 + R_1 C_8$$



$$\tau_{DN} = \sum_{j=1}^N C_j \sum_{k=1}^j R_k \quad \tau_{DN} = \sum_{j=1}^N \left(\frac{C}{N} \right) \sum_{k=1}^j \left(\frac{R}{N} \right)$$

$$= \left(\frac{C}{N} \right) \left(\frac{R}{N} \right) \left(\frac{N(N+1)}{2} \right) = RC \left(\frac{N+1}{2N} \right)$$

$$\tau_{DN} = \frac{RC}{2} \quad \text{for } N \rightarrow \infty$$

Example 6.5 (optional)

- 1) Examine the propagation delay across a long polysilicon interconnect line (length=1000 μm , width=1 μm)
 - $R_{\text{sheet}} = 15 \Omega/\text{square}$

- 1) Sol.

$$\begin{aligned}
 R_{\text{lumped}} &= R_{\text{sheet}} \times (\# \text{ of squares}) \\
 &= 15(\Omega/\text{square}) \times \left(\frac{1000\mu\text{m}}{1\mu\text{m}} \right) = 15\text{k}\Omega
 \end{aligned}$$


$$\begin{aligned}
 C_{\text{parallel-plate}} &= (\text{unit area capacitance}) \times (\text{area}) \\
 &= 0.106\text{fF} / \mu\text{m}^2 \times (1000\mu\text{m} \times 1\mu\text{m}) = 106\text{fF}
 \end{aligned}$$

$$\begin{aligned}
 C_{\text{fringe}} &= (\text{unit length capacitance}) \times (\text{perimeter}) \\
 &= 0.043\text{fF} / \mu\text{m} \times (1000\mu\text{m} + 1000\mu\text{m} + 1\mu\text{m} + 1\mu\text{m}) = 86\text{fF}
 \end{aligned}$$


$$C_{\text{lumped-total}} = C_{\text{parallel-plate}} + C_{\text{fringe}} = 192\text{fF}$$

Example 6.5 (2)

- The simulated output voltage waveforms

 

Example 6.5 (4)

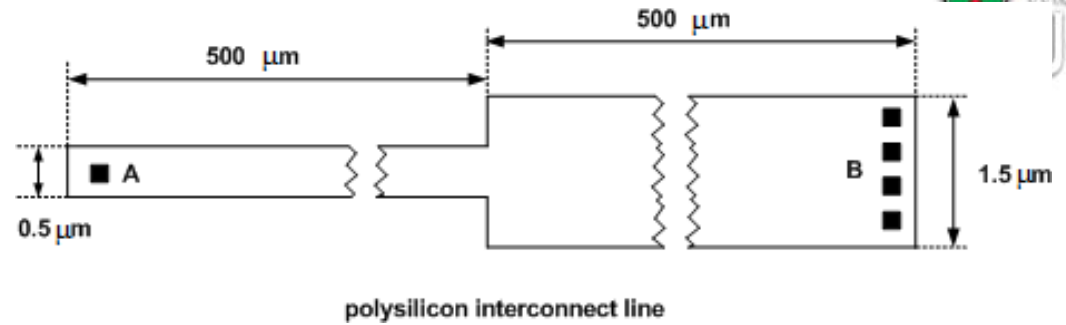

- 2) Consider a polysilicon line consisting of two segments ($W=1.5 \mu\text{m}$ & $W=0.5 \mu\text{m}$, each $500 \mu\text{m}$)

$$R_{lumped-1} = 15(\Omega/\text{square}) \times \left(\frac{500\mu\text{m}}{0.5\mu\text{m}} \right) = 15\text{k}\Omega, \quad R_{lumped-2} = 15(\Omega/\text{square}) \times \left(\frac{500\mu\text{m}}{1.5\mu\text{m}} \right) = 5\text{k}\Omega$$

$$R_{lumped-total} = R_{lumped-1} + R_{lumped-2} = 20\text{k}\Omega$$

- 2) Sol.

$$C_{parallel-plate-1} = 0.106\text{fF} / \mu\text{m}^2 \times (500\mu\text{m} \times 0.5\mu\text{m}) = 26.5\text{fF}$$

$$C_{parallel-plate-2} = 0.106\text{fF} / \mu\text{m}^2 \times (500\mu\text{m} \times 1.5\mu\text{m}) = 79.5\text{fF}$$

$$C_{fringe-1} \approx C_{fringe-2} = 46\text{fF}$$

$$C_{lumped-total} = C_{parallel-plate-1} + C_{parallel-plate-2} + C_{fringe-1} + C_{fringe-2} = 192\text{fF}$$

Layout, Fabrication, and Elementary Logic Design

Dr.Mohammad Abdel-Majeed

Assistant Professor


University of Jordan

Introduction

- Integrated circuits: many transistors on one chip.
 - *Very Large Scale Integration (VLSI)*: very many
- *Metal Oxide Semiconductor (MOS)* transistor
 - Fast, cheap, low-power transistors
 - Complementary: mixture of n- and p-type leads to less power
- Today: How to build your own simple CMOS chip
 - CMOS transistors
 - Building logic gates from transistors
 - Transistor layout and fabrication
- Rest of the course: How to build a good CMOS chip


Silicon Lattice

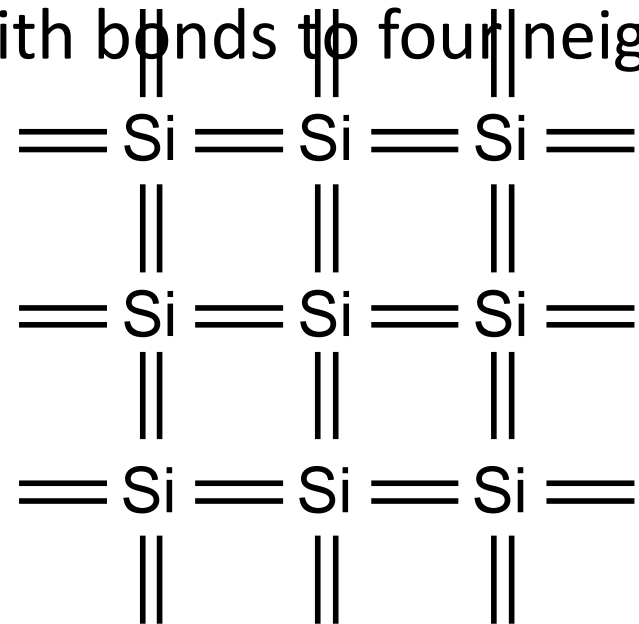- Transistors are built on a silicon substrate
- Silicon is a Group IV material
- Forms crystal lattice with bonds to four neighbors




Dopants

 - Silicon is a semiconductor
- Pure silicon has no free carriers and conducts poorly
- Adding dopants increases the conductivity
- Group V: extra electron (n-type)
- Group III: missing electron, called hole (p-type)




p-n Junctions

 - A junction between p-type and n-type semiconductor forms a diode.
- Current flows only in one direction




anode

cathode

 


nMOS Transistor

 - Four terminals: gate, source, drain, body
- Gate – oxide – body stack looks like a capacitor
 - Gate and body are conductors
 - SiO_2 (oxide) is a very good insulator
 - Called metal – oxide – semiconductor (MOS) capacitor
 - Even though gate is no longer made of metal




nMOS Operation

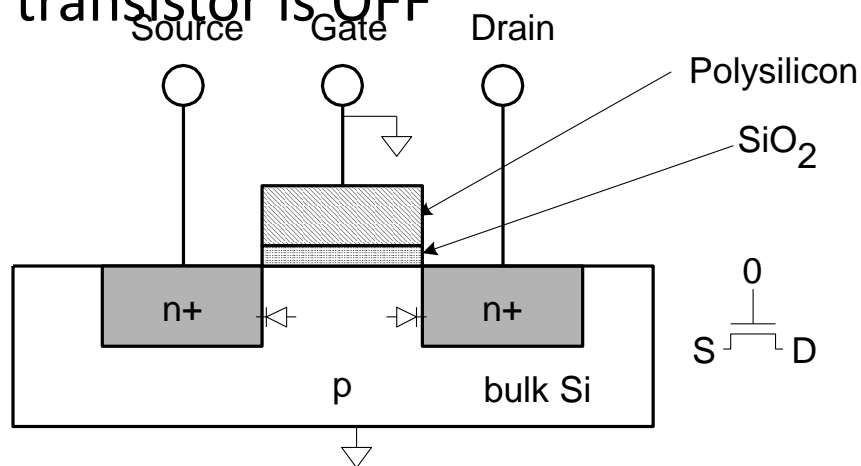- Body is commonly tied to ground (0 V)
- When the gate is at a low voltage:
 - P-type body is at low voltage
 - Source-body and drain-body diodes are OFF
 - No current flows, transistor is OFF




nMOS Operation

 - When the gate is at a high voltage:
 - Positive charge on gate of MOS capacitor
 - Negative charge attracted to body
 - Inverts a channel under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



pMOS Transistor

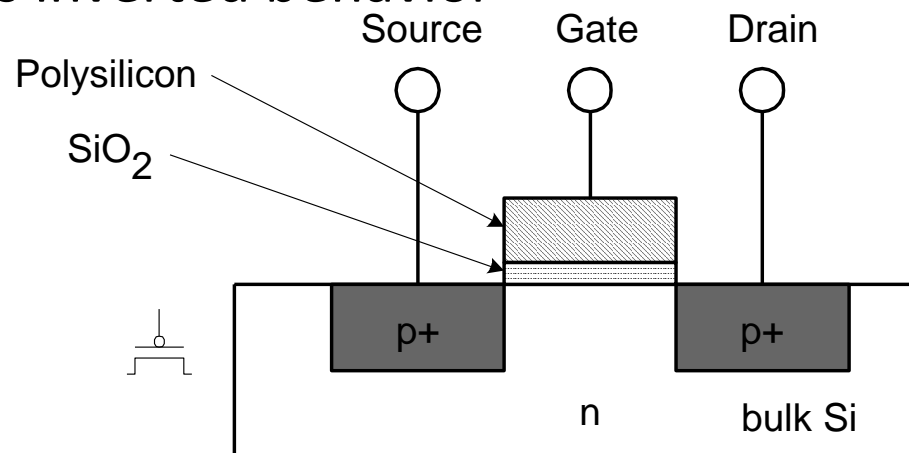- Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior



Power Supply Voltage


- $GND = 0\text{ V}$
- In 1980's, $V_{DD} = 5\text{V}$
- V_{DD} has decreased in modern processes
 - High V_{DD} would damage modern tiny transistors
 - Lower V_{DD} saves power
- $V_{DD} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, \dots$

CMOS Fabrication

- CMOS transistors are fabricated on silicon wafer
- Lithography process similar to printing press
- On each step, different materials are deposited or etched
- Easiest to understand by viewing both top and cross-section of wafer in a simplified manufacturing process


Inverter Cross-section

 - Typically use p-type substrate for nMOS transistor
 - Requires n-well for body of pMOS transistors
 - Several alternatives: SOI, twin-tub, etc.




Well and Substrate Taps

 - Substrate must be tied to GND and n-well to V_{DD}
- Metal to lightly-doped semiconductor forms poor connection called Shottky Diode
- Use heavily doped well and substrate contacts / taps




Inverter Mask Set

 - Transistors and wires are defined by *masks*
- Cross-section taken along dashed line



Detailed Mask Views

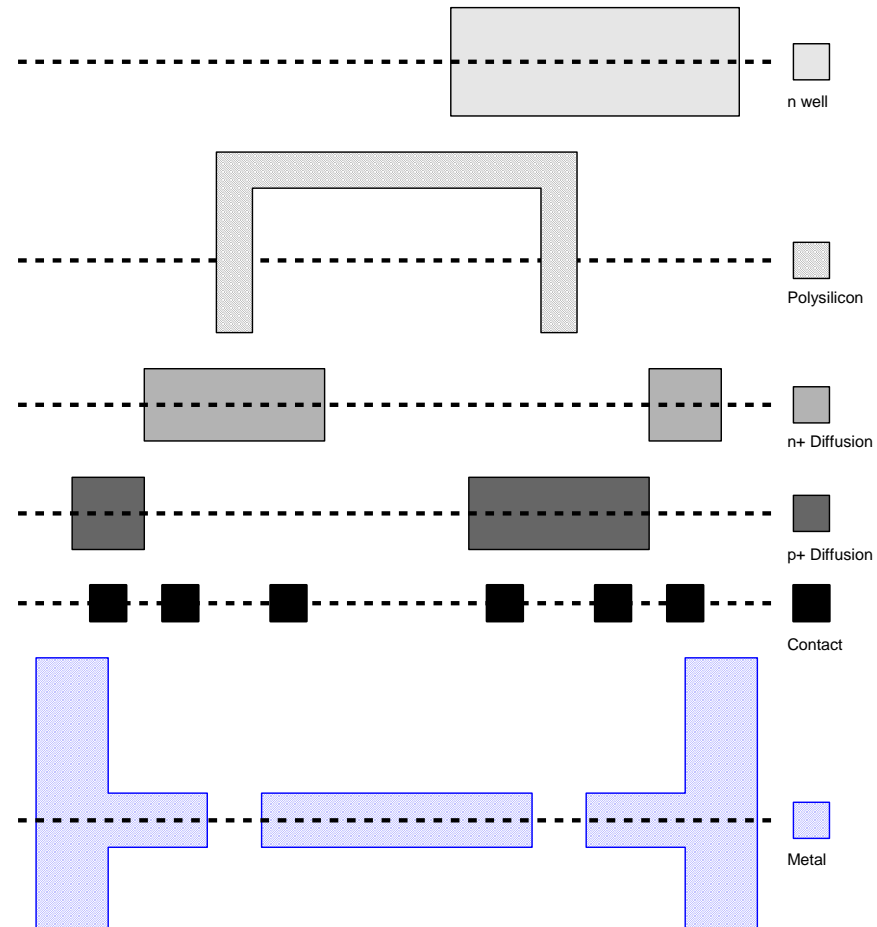- Six masks
 - n-well
 - Polysilicon
 - n+ diffusion
 - p+ diffusion
 - Contact
 - Metal




Fabrication Steps

- Start with blank wafer
- Build inverter from the bottom up
- First step will be to form the n-well
 - Cover wafer with protective layer of SiO_2 (oxide)
 - Remove layer where n-well should be built
 - Implant or diffuse n dopants into exposed wafer
 - Strip off SiO_2




Oxidation

 - Grow SiO_2 on top of Si wafer
 - 900 – 1200 C with H_2O or O_2 in oxidation furnace




Photoresist

 - Spin on photoresist
 - Photoresist is a light-sensitive organic polymer
 - Softens where exposed to light




Lithography

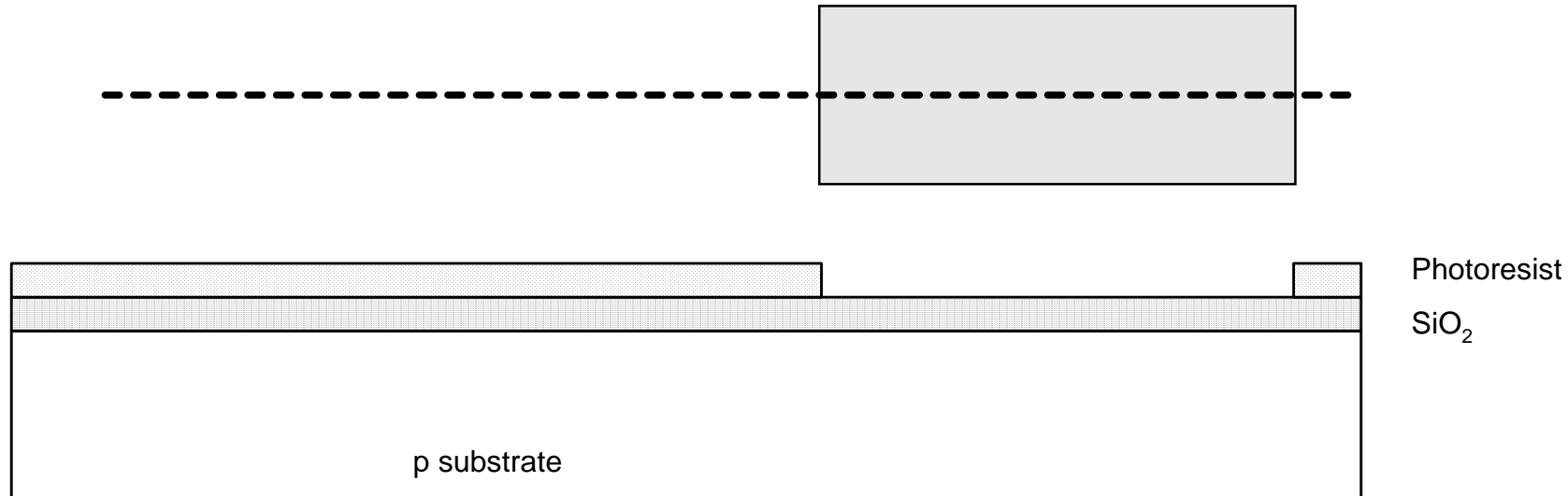- Expose photoresist through n-well mask
- Strip off exposed photoresist




Etch

 - Etch oxide with hydrofluoric acid (HF)
 - Seeps through skin and eats bone; nasty stuff!!!
- Only attacks oxide where resist has been exposed




Strip Photoresist

 - Strip off remaining photoresist
 - Use mixture of acids called piranha etch
- Necessary so resist doesn't melt in next step




n-well

 - n-well is formed with diffusion or ion implantation
- Diffusion
 - Place wafer in furnace with arsenic gas
 - Heat until As atoms diffuse into exposed Si
- Ion Implantation
 - Blast wafer with beam of As ions
 - Ions blocked by SiO_2 , only enter exposed Si




Strip Oxide

 - Strip off the remaining oxide using HF
- Back to bare wafer with n-well
- Subsequent steps involve similar series of steps




Polysilicon

 - Deposit very thin layer of gate oxide
 - $< 20 \text{ \AA}$ (6-7 atomic layers)
- Chemical Vapor Deposition (CVD) of silicon layer
 - Place wafer in furnace with Silane gas (SiH_4)
 - Forms many small crystals called polysilicon
 - Heavily doped to be good conductor




Polysilicon Patterning

 - Use same lithography process to pattern polysilicon




Self-Aligned Process

 - Use oxide and masking to expose where n+ dopants should be diffused or implanted
- N-diffusion forms nMOS source, drain, and n-well contact




N-diffusion

 - Pattern oxide and form n+ regions
- *Self-aligned process* where gate blocks diffusion
- Polysilicon is better than metal for self-aligned gates because it doesn't melt during subsequent processing




N-diffusion

 - Historically dopants were diffused
- Usually ion implantation today
- But regions are still called diffusion




N-diffusion

 - Strip off oxide to complete patterning step




P-Diffusion

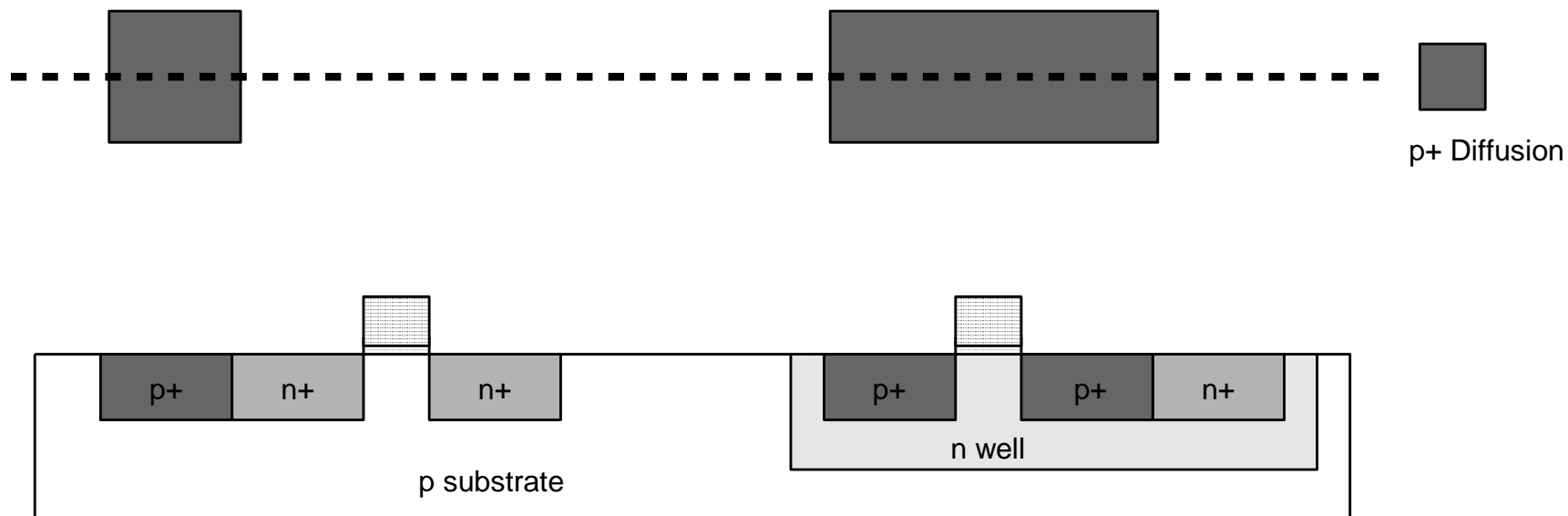- Similar set of steps form p+ diffusion regions for pMOS source and drain and substrate contact




Contacts

 - Now we need to wire together the devices
- Cover chip with thick field oxide
- Etch oxide where contact cuts are needed



Metallization

 - Sputter on aluminum over whole wafer
- Pattern and remove excess metal, leaving wires




Layout

- Chips are specified with set of masks
- Minimum dimensions of masks determine transistor size (and hence speed, cost, and power)
- Feature size f = distance between source and drain
 - Set by minimum width of polysilicon
- Feature size improves 30% every 3 years or so
- Normalize for feature size when describing design rules
- Express rules in terms of $\lambda = f/2$
 - E.g. $\lambda = 0.3 \mu\text{m}$ in $0.6 \mu\text{m}$ process




Simplified Design Rules

- Conserv

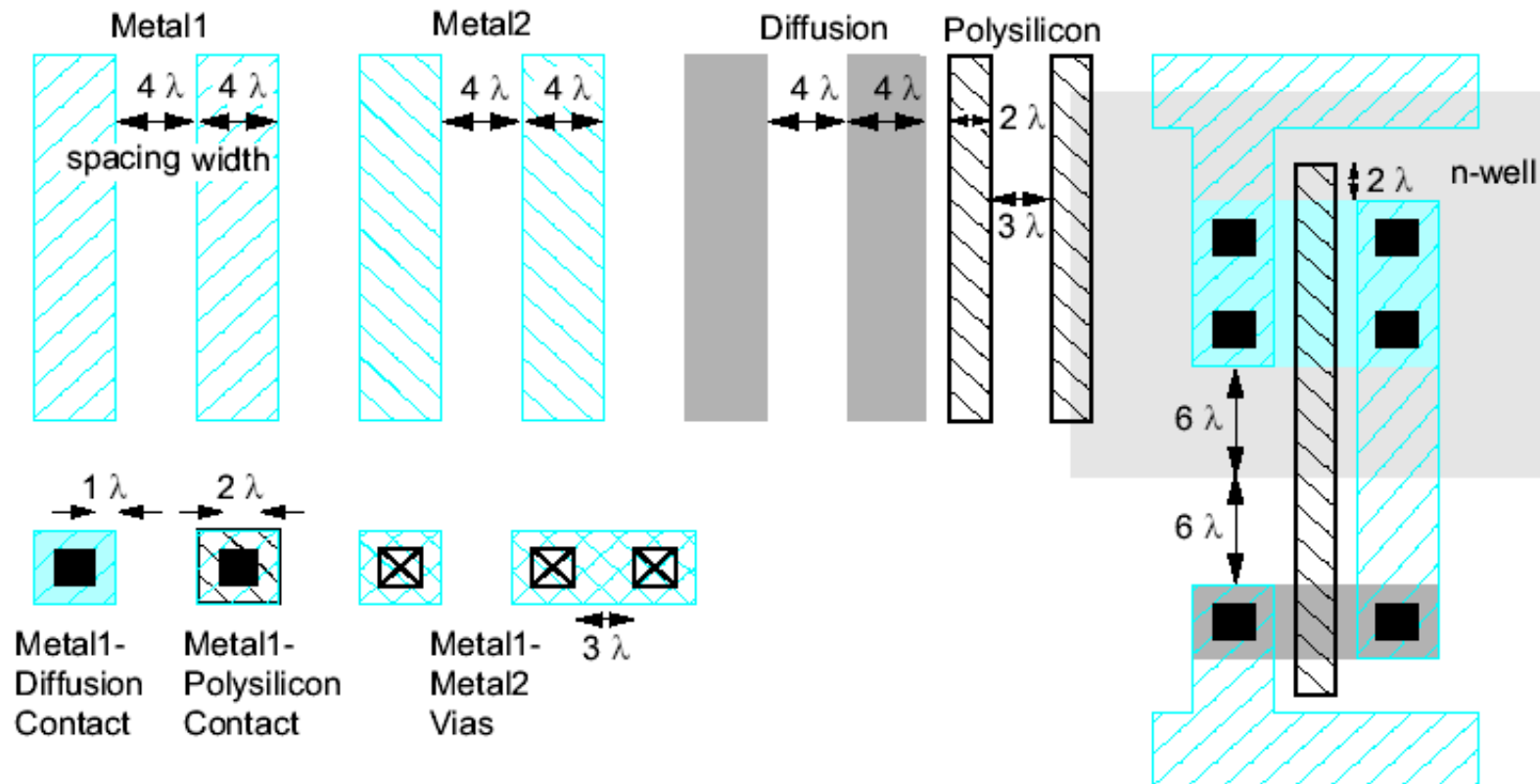

Inverter Layout

   - Transistor dimensions specified as Width / Length
 - Minimum size is $4\lambda / 2\lambda$, sometimes called 1 unit
 - For $0.6 \mu\text{m}$ technology, V_{DD} ; $W=1.2 \mu\text{m}$, $L=0.6 \mu\text{m}$



Summary

- MOS Transistors are stack of gate, oxide, silicon
- Can be viewed as electrically controlled switches
- Build logic gates out of switches
- Draw masks to specify layout of transistors

- Now you know everything necessary to start designing schematics and layout for a simple chip!

Combinational Logic


Dr.Mohammad Abdel-Majeed

Assistant Professor

University of Jordan


Transistors as Switches

 - We can view MOS transistors as electrically controlled switches
- Voltage at gate controls path from source to drain





CMOS Circuits

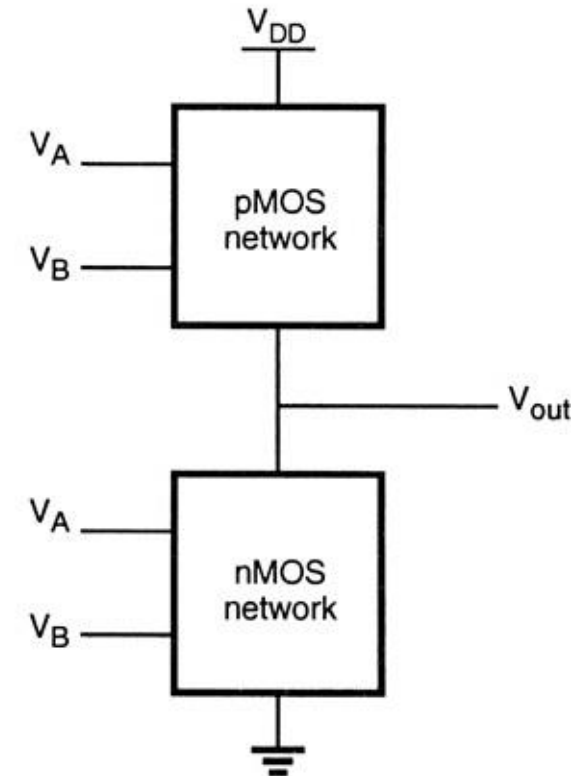- For the gate to output a '1'
 - Some path of PMOS transistors from VDD to output on
 - We call the PMOS transistors the Pull-Up Network
- For the gate to output a '0'
 - Some path of NMOS transistors from GND to output on
 - We call the NMOS transistors the Pull-Down Network





CMOS Inverter

A	Y
0	
1	

  



CMOS Inverter

A	Y
0	
1	0

  



CMOS Inverter

A	Y
0	1
1	0

  



CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	
1	0	
1	1	

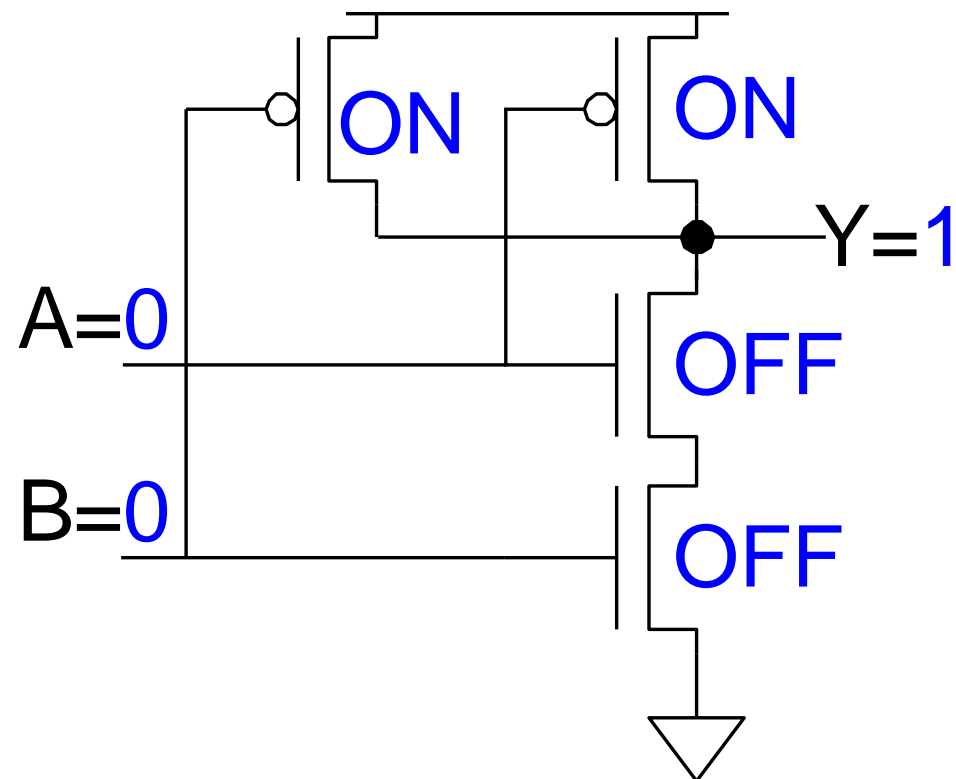 



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	
1	1	

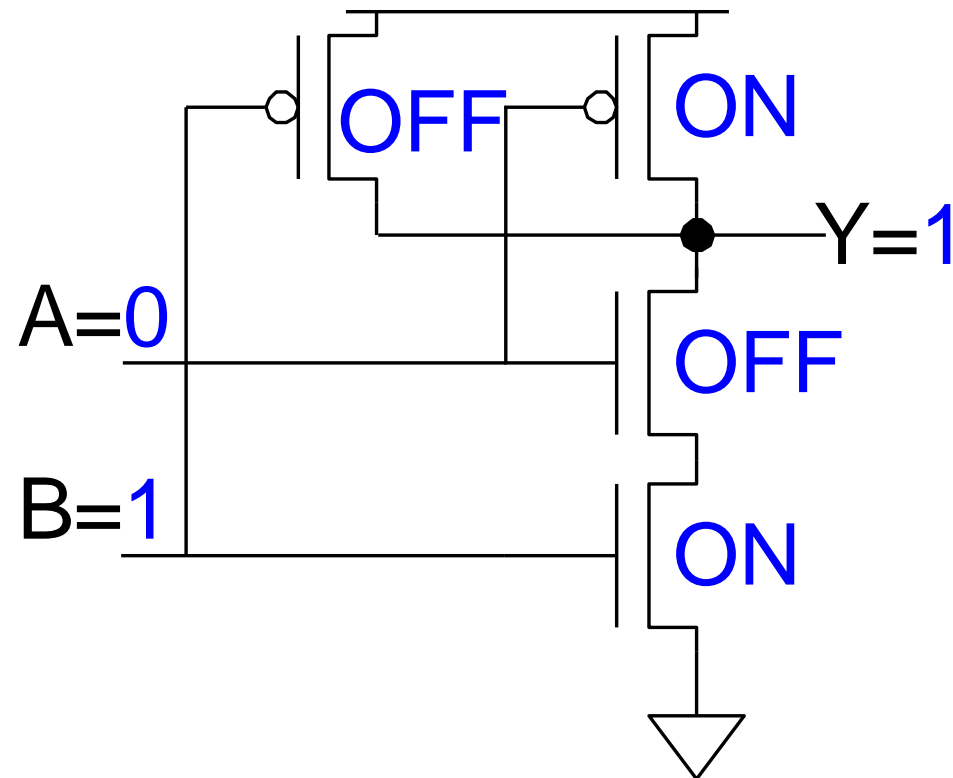 



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	

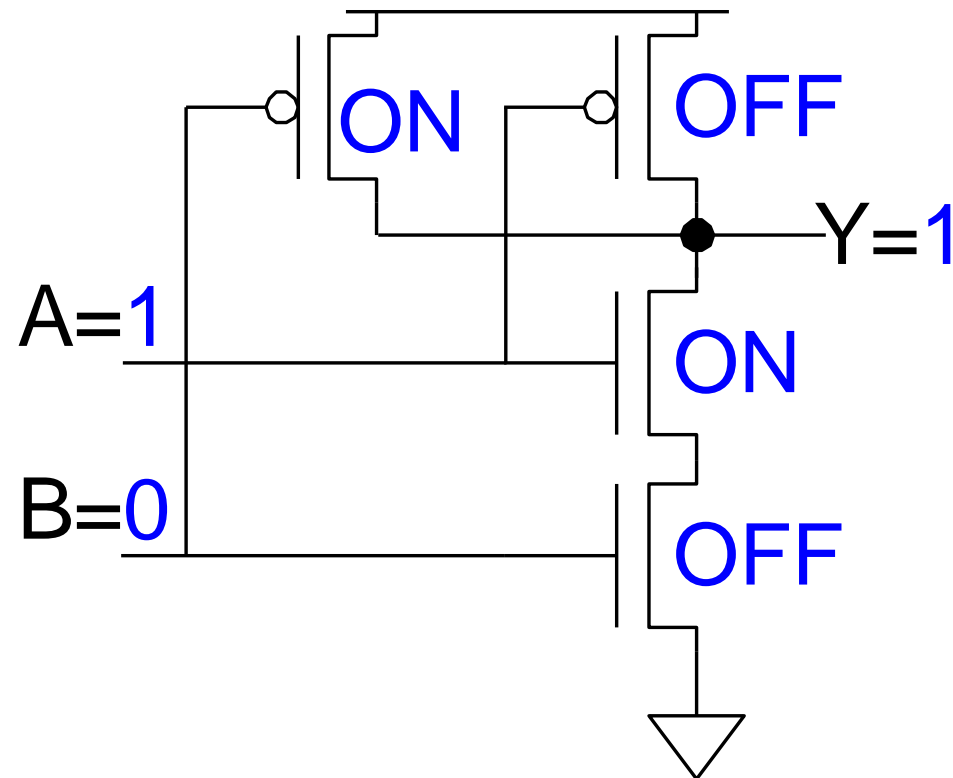 



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

  

CMOS NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

  


3-input NAND Gate



- Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0

3-input NAND Gate

 - Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0



Sizing

  


Sizing

- Delay is dependent on the pattern of inputs
- The ratio of the $\{W/L\}_{PUN} / \{W/L\}_{PDN}$ should be two (or higher) to make up for slow PMOS


Sizing

 - Delay is dependent on the pattern of inputs
- Low to high transition
 - both inputs go low
 - delay is $(R_p/2)*C_L$
- one input goes low
 - delay is $(R_p)*C_L$
 - Worst case: R_p*C_L
- High to Low transition
 - both inputs go high
 - delay is $(2*R_n)*C_L$




$$R_p = 2R_n \rightarrow W_p = W_n$$


NAND Sizing

 


Inverter Sizing

 

NOR Sizing

 

NAND capacitance

 

Complex Gates

- $A = \overline{D + A \cdot (B + C)}$

Complex Gates Sizing

- $A = \overline{D + A \cdot (B + C)}$

Stick Diagrams

- VLSI design aims to translate circuit concepts onto silicon.
- stick diagrams are a means of capturing topography and layer information using simple diagrams.
- Stick diagrams convey layer information through colour codes (or monochrome encoding).
- Acts as an interface between symbolic circuit and the actual layout.


Stick Diagrams

- Does show all components/vias.
- It shows relative placement of components.
- Goes one step closer to the layout
- Helps plan the layout and routing

Stick Diagrams


- Does ***not*** show
 - Exact placement of components
 - Transistor sizes
 - Wire lengths, wire widths, tub boundaries.
 - Any other low level details such as parasitics..

Stick Diagram

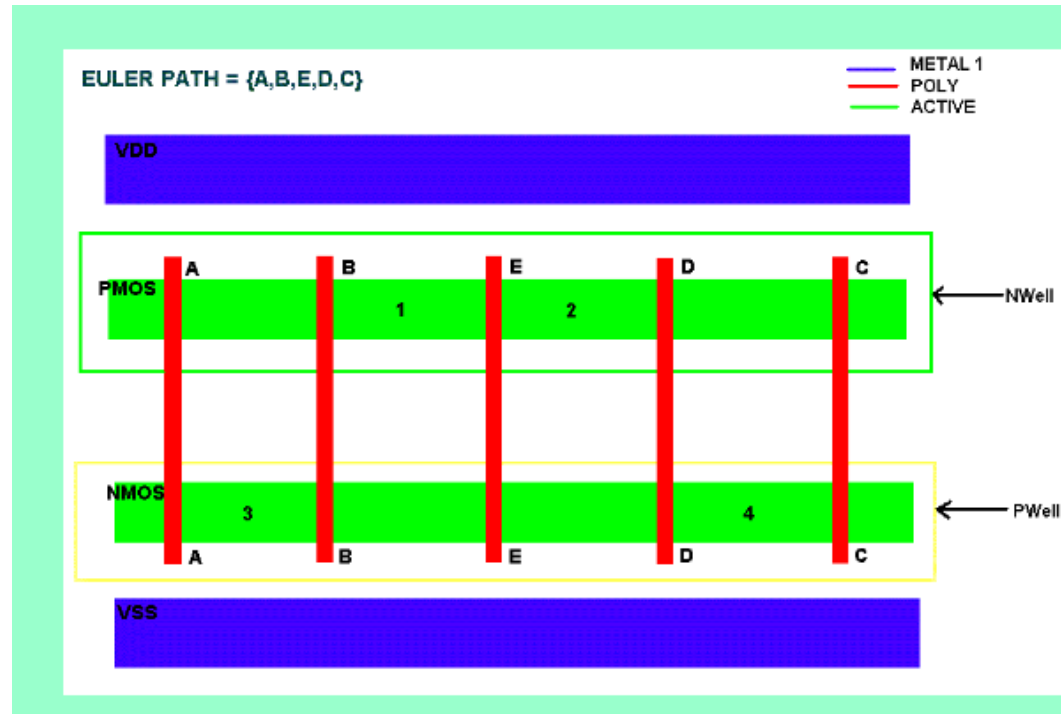


EULER PATH = {A,B,E,D,C}

— METAL 1
— POLY
— ACTIVE

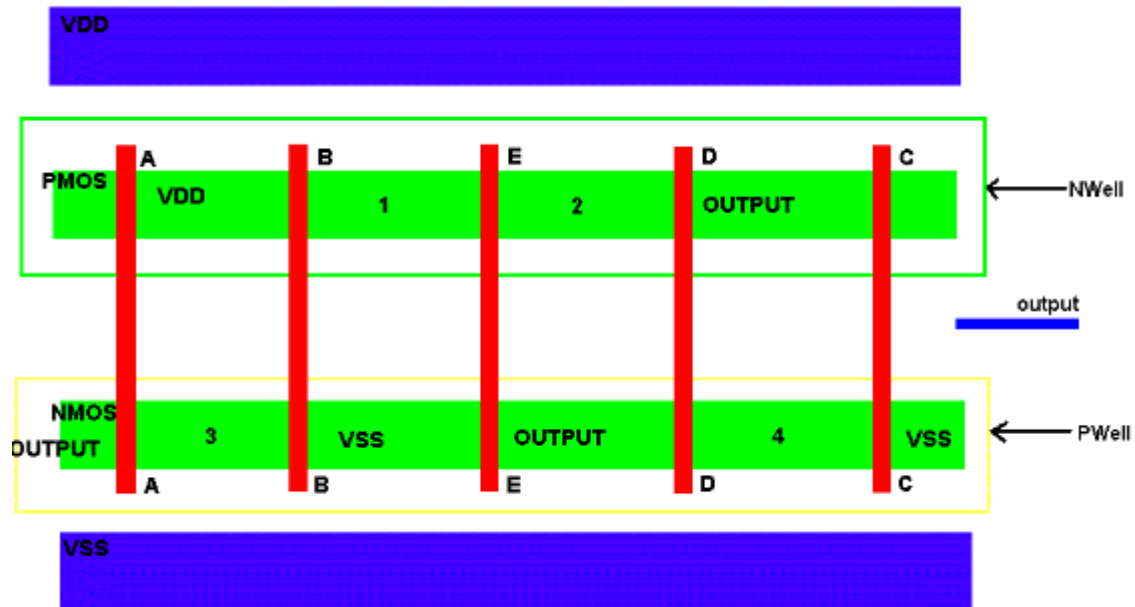

Stick Diagram

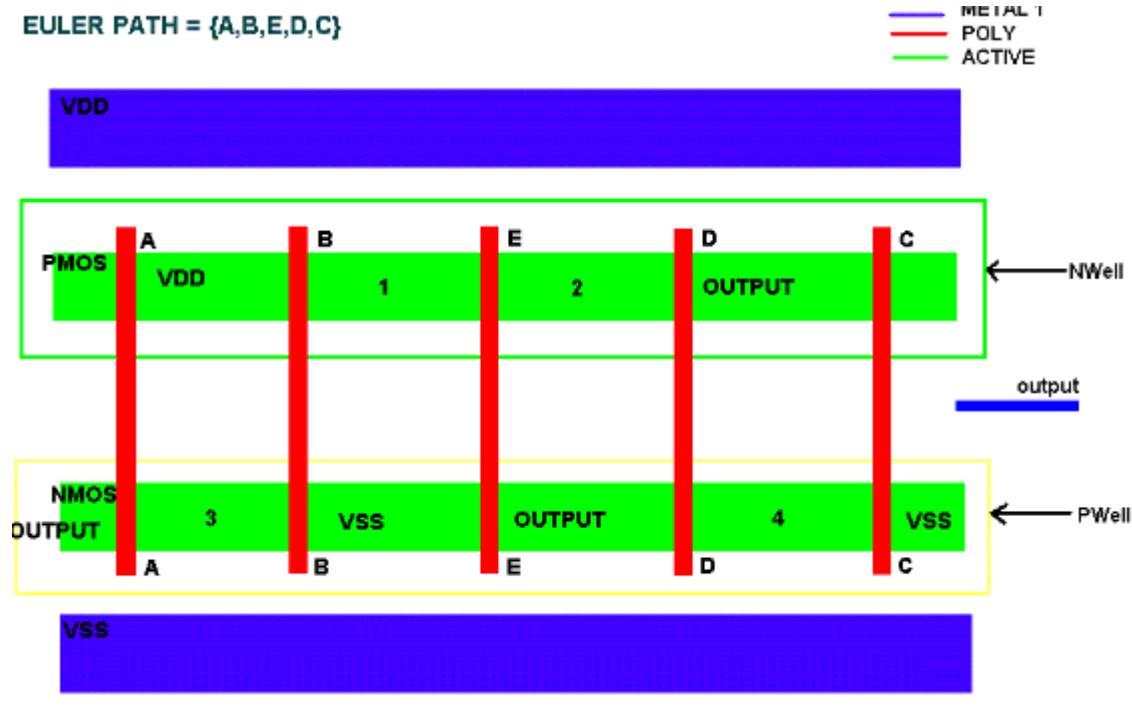

Example

- $F = \overline{A + B}$

Example


- $F = \overline{A \cdot B}$

Example

- $F = \overline{A + BC}$

Example

- $F = \overline{A(D + E) + BC}$

 


Euler Path

- The number of diffusion breaks can be minimized by changing the ordering of the polysilicon columns
- A simple method for finding the optimum gate ordering is the **Euler-path** approach
- Find a common Euler path for both pull-down and pull-up graphs
- The polysilicon columns can be arranged according to the sequence (in Euler-path)
- Diffusion will be unbroken if identically labeled Euler paths can be found for the p and n trees


Euler Path

- construct one Euler path for both the Pull up and Pull down network
 - Path the traverses each node in the path, such that each edge is visited only once.
 - If the path traverses transistor A then B then C. Then the path name is {A, B, C}
 - The Euler path of the Pull up network must be the same as the path of the Pull down network.
 - Euler paths are not necessarily unique.
 - It may be necessary to redefine the function to find a Euler path.

Euler Path

 


Common Euler path
:
E - D - A - B - C

 

pMOS network

 - The advantages of this new layout are more compact layout area, simple routing of signals, and consequently, lower parasitic capacitance



Euler Path

- $A = \overline{D + AB + CE}$

Example


- $A = \overline{D + AB + CE}$

Example

- $f = \overline{A(D + E) + BC}$



CMOS Transmission Gates (Pass Gates)

 - Representations of the CMOS transmission gate (TG)




- One nMOS + one pMOS
- Bidirectional switch
- If $C=V_{DD}$, TG is turned on (low-resistance path)
- If $C=GND$, TG is turned off (high-impedance state)

DC Analysis of Transmission Gate (1)

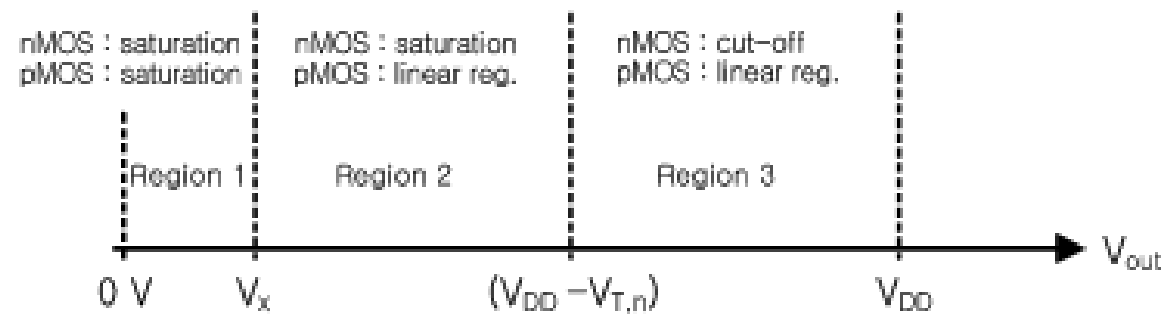 


CMOS TG Implementations (1)


- Two-input multiplexor

 

- 8-TRs XOR function

 


- 6-TRs XOR function

 

CMOS TG Implementations (2)

- Boolean function realization

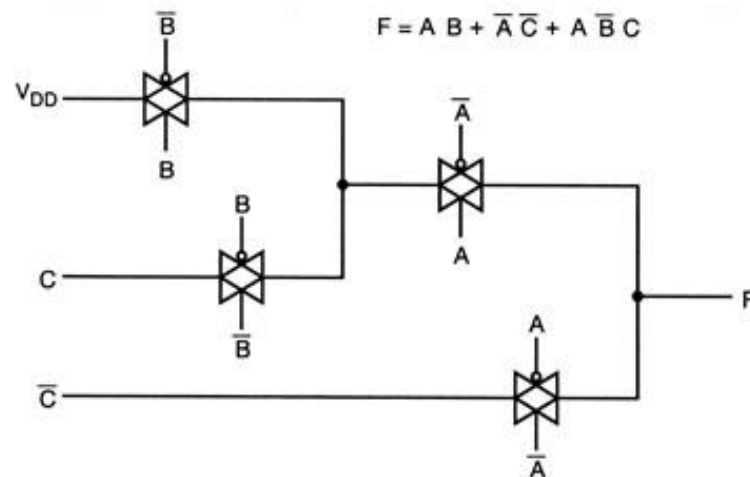


Transistors scaling

Outline

- Scaling
 - Transistors
 - Interconnect
 - Future Challenges


Moore's Law

 - Recall that Moore's Law has been driving CMOS



Moore's Law

 
- Recall that Moore's Law has been driving CMOS



Moore's Law today

Moore's Law

 - Recall that Moore's Law has been driving CMOS



Corollary: clock speeds have improved

Why?

- Why more transistors per IC?
 - Smaller transistors
 - Larger dice
- Why faster computers?
 - Smaller, faster transistors
 - Better microarchitecture (more IPC)
 - Fewer gate delays per cycle

Scaling

- The only constant in VLSI is constant change
- Feature size shrinks by 30% every 2-3 years
 - Transistors become cheaper
 - Transistors become faster and lower power
 - Wires do not improve
(and may get worse)
- Scale factor S
 - Typically
 - Technology nodes

$$S = \sqrt{2}$$

Dennard Scaling

- Proposed by Dennard in 1974
- Also known as *constant field* scaling
 - Electric fields remain the same as features scale
- Scaling assumptions
 - All dimensions ($x, y, z \Rightarrow W, L, t_{ox}$)
 - Voltage (V_{DD})
 - Doping levels

Device Scaling

Parameter	Sensitivity	Dennard Scaling
L: Length		1/S
W: Width		1/S
t_{ox} : gate oxide thickness		1/S
V_{DD} : supply voltage		1/S
V_t : threshold voltage		1/S
NA: substrate doping		S
β	$W/(Lt_{ox})$	S
I_{on} : ON current	$\beta(V_{DD}-V_t)^2$	1/S
R: effective resistance	V_{DD}/I_{on}	1
C: gate capacitance	WL/t_{ox}	1/S
τ : gate delay	RC	1/S
f: clock frequency	$1/\tau$	S
E: switching energy / gate	CV_{DD}^2	1/S ³
P: switching power / gate	Ef	1/S ²
A: area per gate	WL	1/S ²
Switching power density	P/A	1
Switching current density	I_{on}/A	S

Observations

- Gate capacitance per micron is nearly independent of process
- Gates get faster with scaling (good)
- Dynamic power goes down with scaling (good)
- Current density goes up with scaling (bad)

Real Scaling


- t_{ox} scaling has slowed since 65 nm
 - Limited by gate tunneling current
 - Gates are only about 4 atomic layers thick!
 - High-k dielectrics have helped continued scaling of effective oxide thickness
- V_{DD} scaling has slowed since 65 nm
 - SRAM cell stability at low voltage is challenging
- Dennard scaling predicts cost, speed, power all improve
 - Below 65 nm, some designers find they must choose just two of the three

Interconnect Scaling

Parameter	Sensitivity	Scale Factor
w: width		1/S
s: spacing		1/S
t: thickness		1/S
h: height		1/S
D_c : die size		D_c
R_w : wire resistance/unit length	1/wt	S^2
C_{wf} : fringing capacitance / unit length	t/s	1
C_{wp} : parallel plate capacitance / unit length	w/h	1
C_w : total wire capacitance / unit length	$C_{wf} + C_{wp}$	1
t_{wu} : unrepeated RC delay / unit length	$R_w C_w$	S^2
t_{wr} : repeated RC delay / unit length	$\text{sqrt}(RCR_w C_w)$	$\text{sqrt}(S)$
Crosstalk noise	w/h	1
E_w : energy per bit / unit length	$C_w V_{DD}^2$	1/S ²

Reachable Radius

 - We can't send a signal across a large fast chip in one cycle anymore
- But the microarchitect can plan around this
 - Just as off-chip memory latencies were tolerated



Observations

- Local wires are getting faster
 - Not quite tracking transistor improvement
 - But not a major problem
- Global wires are getting slower
 - No longer possible to cross chip in one cycle


ITRS

- Semiconductor Industry Association forecast
 - Intl. Technology Roadmap for Semiconductors

Year	2009	2012	2015	2018	2021
Feature size (nm)	34	24	17	12	8.4
L_{gate} (nm)	20	14	10	7	5
V_{DD} (V)	1.0	0.9	0.8	0.7	0.65
Billions of transistors/die	1.5	3.1	6.2	12.4	24.7
Wiring levels	12	12	13	14	15
Maximum power (W)	198	198	198	198	198
DRAM capacity (Gb)	2	4	8	16	32
Flash capacity (Gb)	16	32	64	128	256


Dynamic Power

 - Intel VP Patrick Gelsinger (ISSCC 2001)
 - If scaling continues at present pace, by 2005, high speed processors would have power density of nuclear reactor, by 2010, a rocket nozzle, and by 2015, surface of sun.
 - “Business as usual will not work in the future.”
- Attention to power is increasing



Static Power

 - V_{DD} decreases
 - Save dynamic power
 - Protect thin gate oxides and short channels
 - No point in high value because of velocity sat.
- V_t must decrease to maintain device performance
- But this causes exponential increase in OFF leakage
- Major future challenge



Productivity

- Transistor count is increasing faster than designer productivity (gates / week)
 - Bigger design teams
 - Up to 500 for a high-end microprocessor
 - More expensive design cost
 - Pressure to raise productivity
 - Rely on synthesis, IP blocks
 - Need for good engineering managers

Physical Limits

- Will Moore's Law run out of steam?
 - Can't build transistors smaller than an atom...
- Many reasons have been predicted for end of scaling
 - Dynamic power
 - Subthreshold leakage, tunneling
 - Short channel effects
 - Fabrication costs
 - Electromigration
 - Interconnect delay

Sequential Logic



Dr.Mohammad Abdel-Majeed

Assistant Professor

University of Jordan

Introduction


- Sequential Circuit

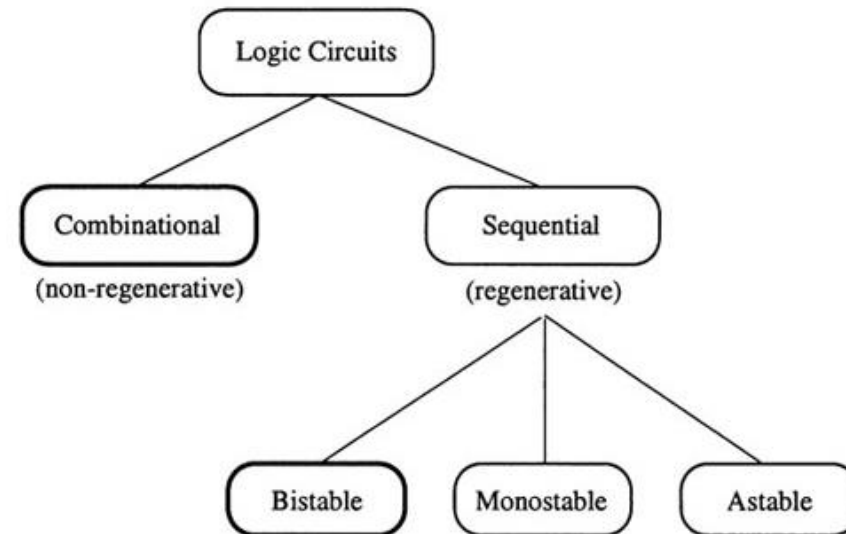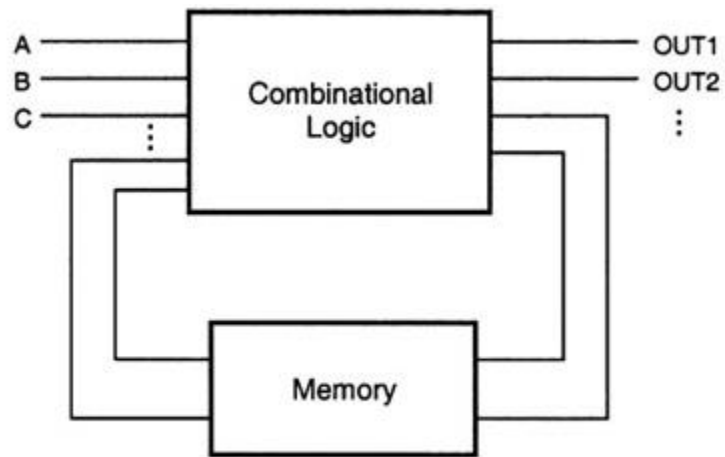


Combinational block
+memory block

SR Latch Circuit

- SR latch circuit based on NOR2 gates

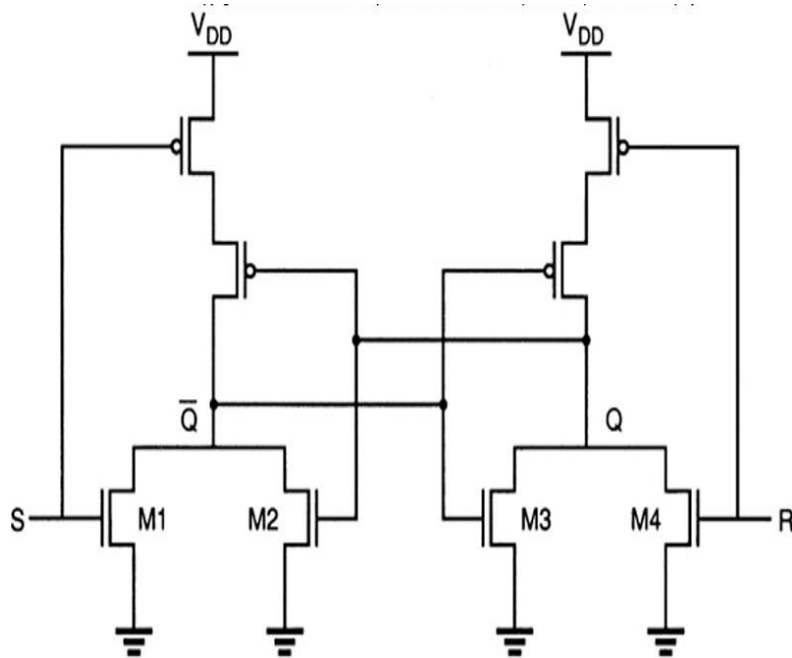

- Gate level schematic and block diagram

 

Truth Table and Operation Mode

- Truth table of the NOR based SR latch circuit


S	R	Q_{n+1}	$\overline{Q_{n+1}}$	Operation
0	0	Q_n	$\overline{Q_n}$	hold
1	0	1	0	set
0	1	0	1	reset
1	1	0	0	not allowed

- Operation mode of the NOR based SR latch circuit

S	R	Q_{n+1}	$\overline{Q_{n+1}}$	Operation
V_{OH}	V_{OL}	V_{OH}	V_{OL}	M1 and M2 on, M3 and M4 off
V_{OL}	V_{OH}	V_{OL}	V_{OH}	M1 and M2 off, M3 and M4 on
V_{OL}	V_{OL}	V_{OH}	V_{OL}	M1 and M4 off, M2 on, or
V_{OL}	V_{OL}	V_{OL}	V_{OH}	M1 and M4 off, M3 on

NAND Based SR Latch


- Gate level schematic & Block diagram

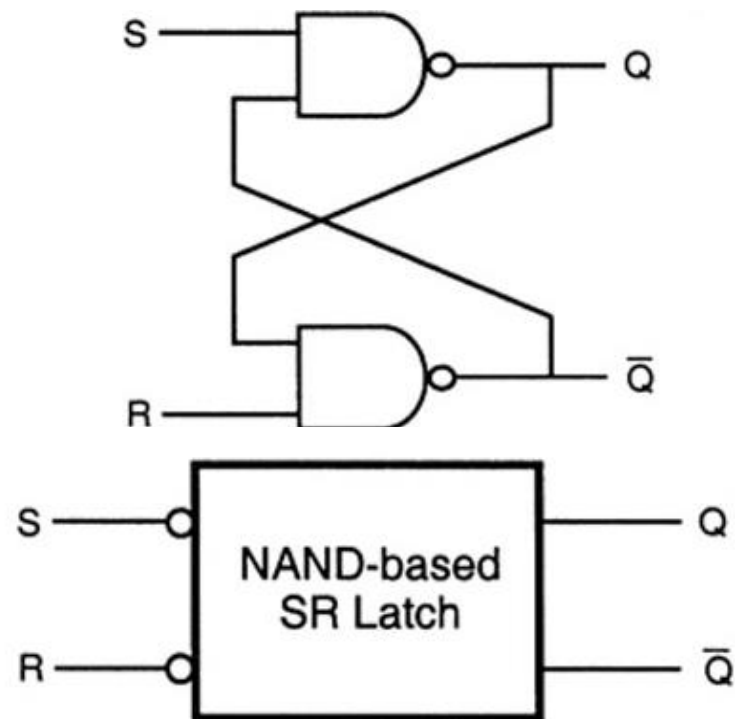

S	R	Q_{n+1}	\overline{Q}_{n+1}	Operation
0	0	1	1	not allowed
0	1	1	0	set
1	0	0	1	reset
1	1	Q_n	\overline{Q}_n	hold


CMOS SR Latch : Another Type

- SR latch based on NAND2 gates

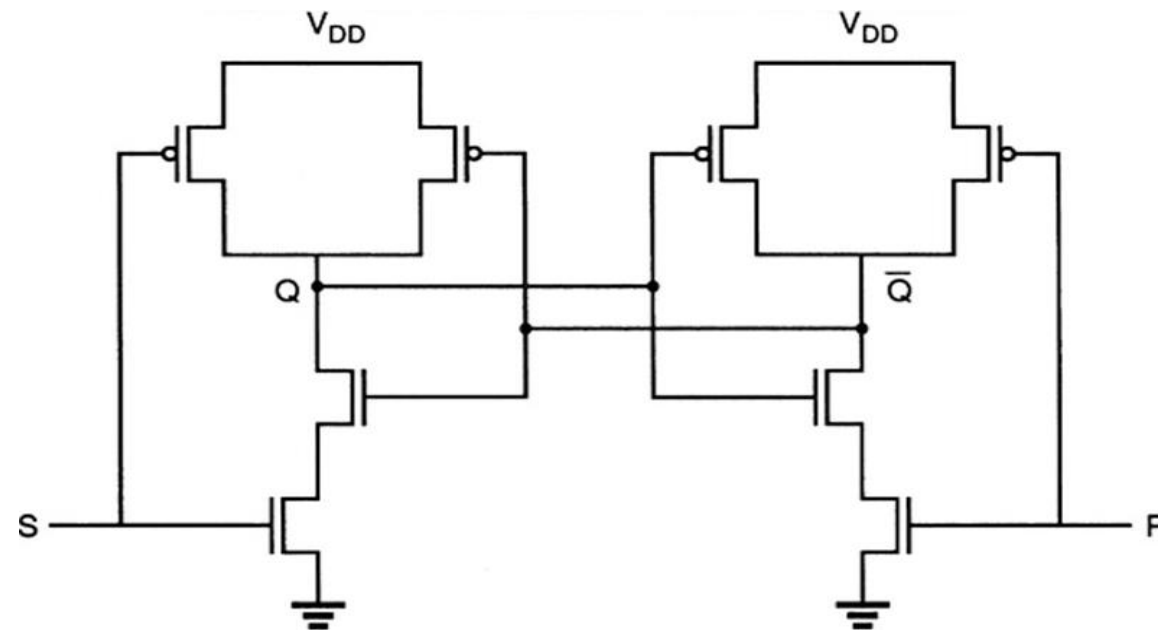


Clocked SR Latch

- Gate level schematic

 


- Input and output waveform

 

Level sensitive circuit



Clocked NOR Based SR Latch : AOI

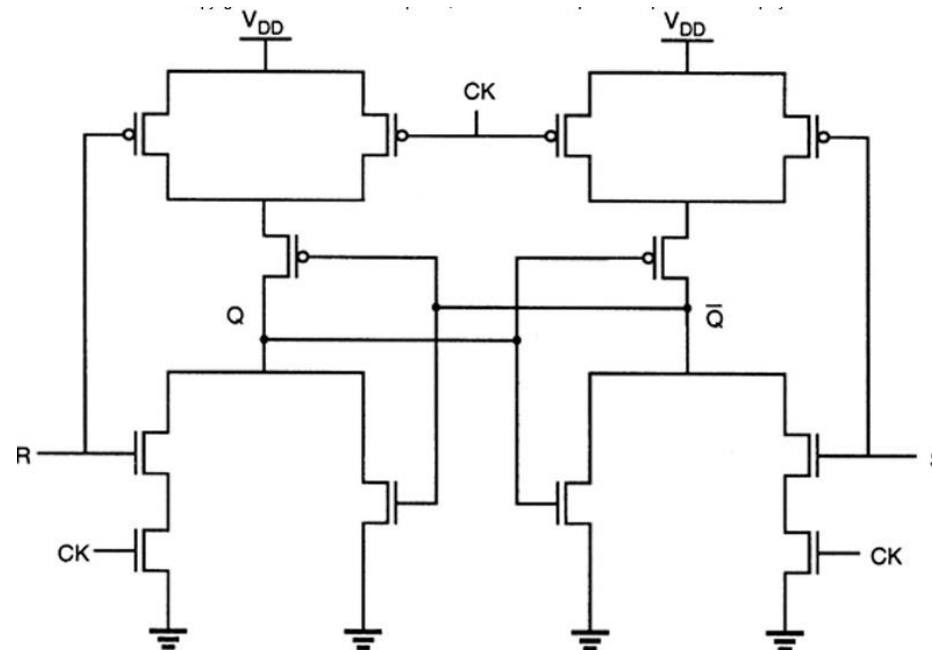- AOI-based implementation of the clocked NOR-based SR-latch Circuit





Clocked JK Latch

- Gate level schematic

 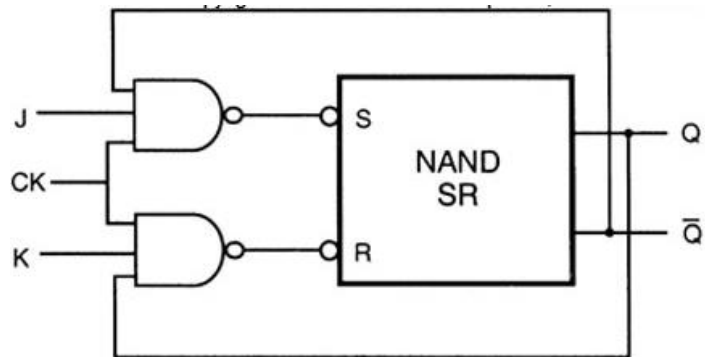

- SR-latch : indeterminate when both inputs S and R are activated
- JK latch : adding two feedback lines from the outputs to the inputs

Clocked NOR-based JK latch

  


Clocked JK Latch : Truth Table

J	K	Q_n	$\overline{Q_n}$	S	R	Q_{n+1}	$\overline{Q_{n+1}}$	Operation
0	0	0	1	1	1	0	1	hold
		1	0	1	1	1	0	
0	1	0	1	1	1	0	1	reset
		1	0	1	0	0	1	
1	0	0	1	0	1	1	0	set
		1	0	1	1	1	0	
1	1	0	1	0	1	1	0	toggle
		1	0	1	0	0	1	

Master-Slave Flip-Flop

- Master-Slave Flip-Flop


- Two ci

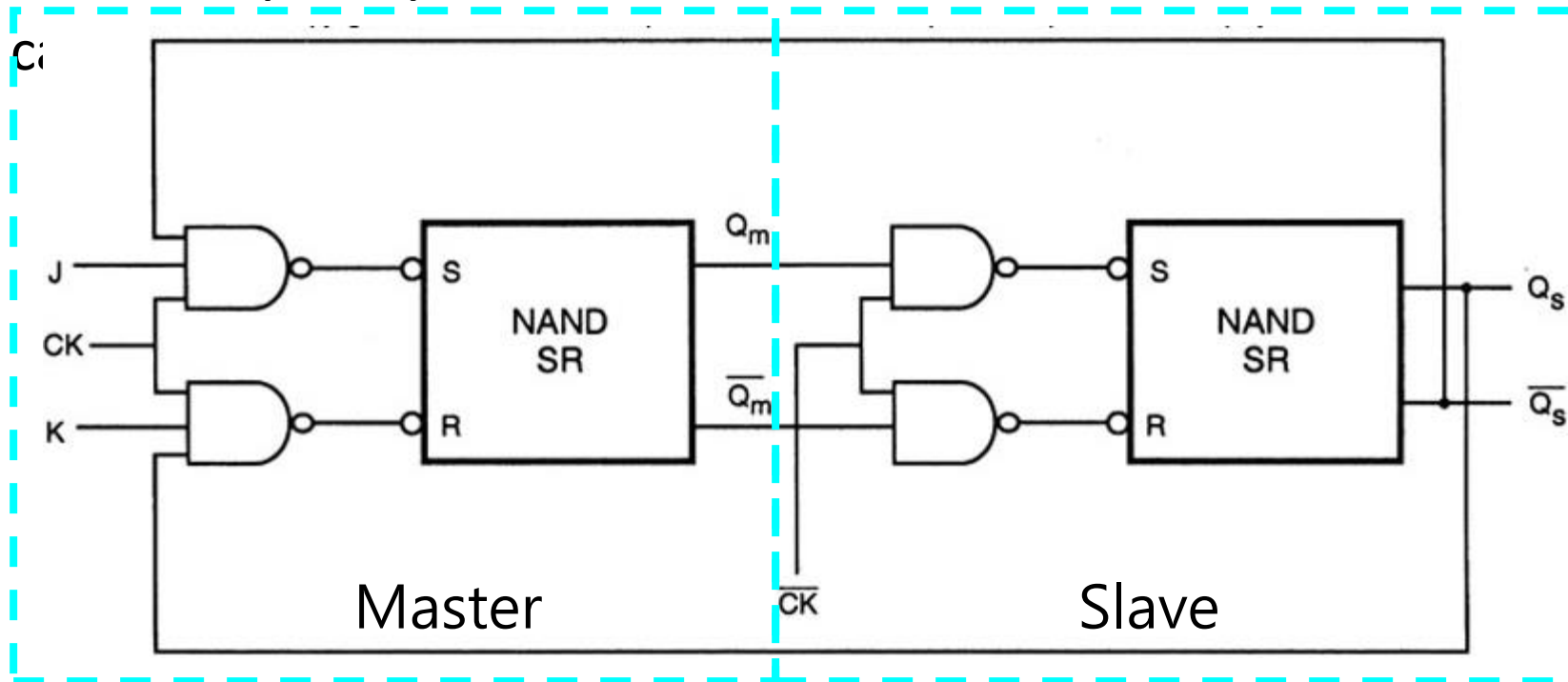

Master Slave FF



- The master latch is activated when $CK="1,"$ during this period, the primary inputs, J and K, allow data to be entered into the flip-flop, and the first stage outputs are set according to the primary inputs
- When $CK="0,"$ the master latch becomes inactive, and the slave latch becomes active
- Note that, the output levels of the flip-flop are determined during this phase ($CK="0,"$) based on the master-stage outputs set in the previous phase ($CK="1"$)

NOR based JK master slave FF

 

CMOS D-Latch


- Gate-level schematic

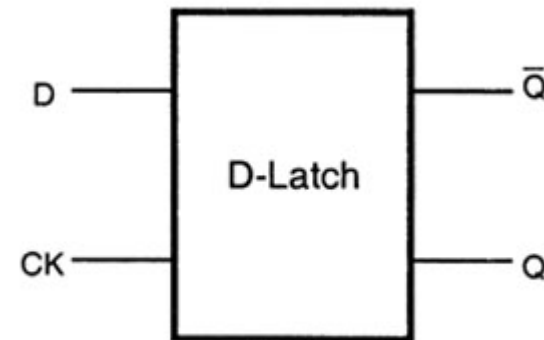 

- CK : 1 \rightarrow Q assumes the value of the input D
- CK : 0 \rightarrow Q preserve its state


CMOS D-Latch Using Transmission gates

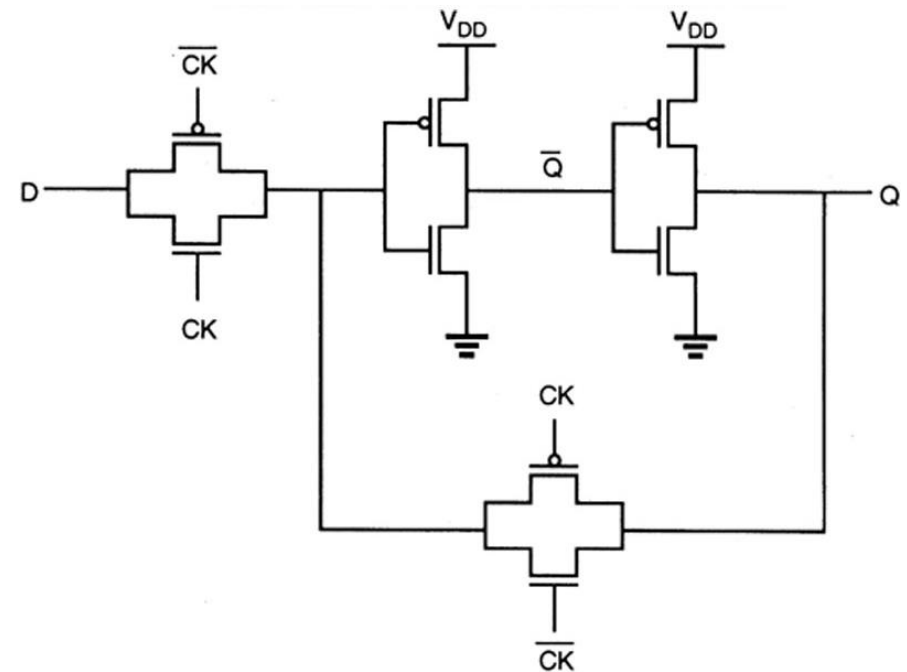- Constructed by Two inverter loop + Two CMOS TG
- CK:1 \rightarrow TG at input is activated
- CK:0 \rightarrow TG at inverter loop is activated



Master-Slave Flip-Flop : Operation

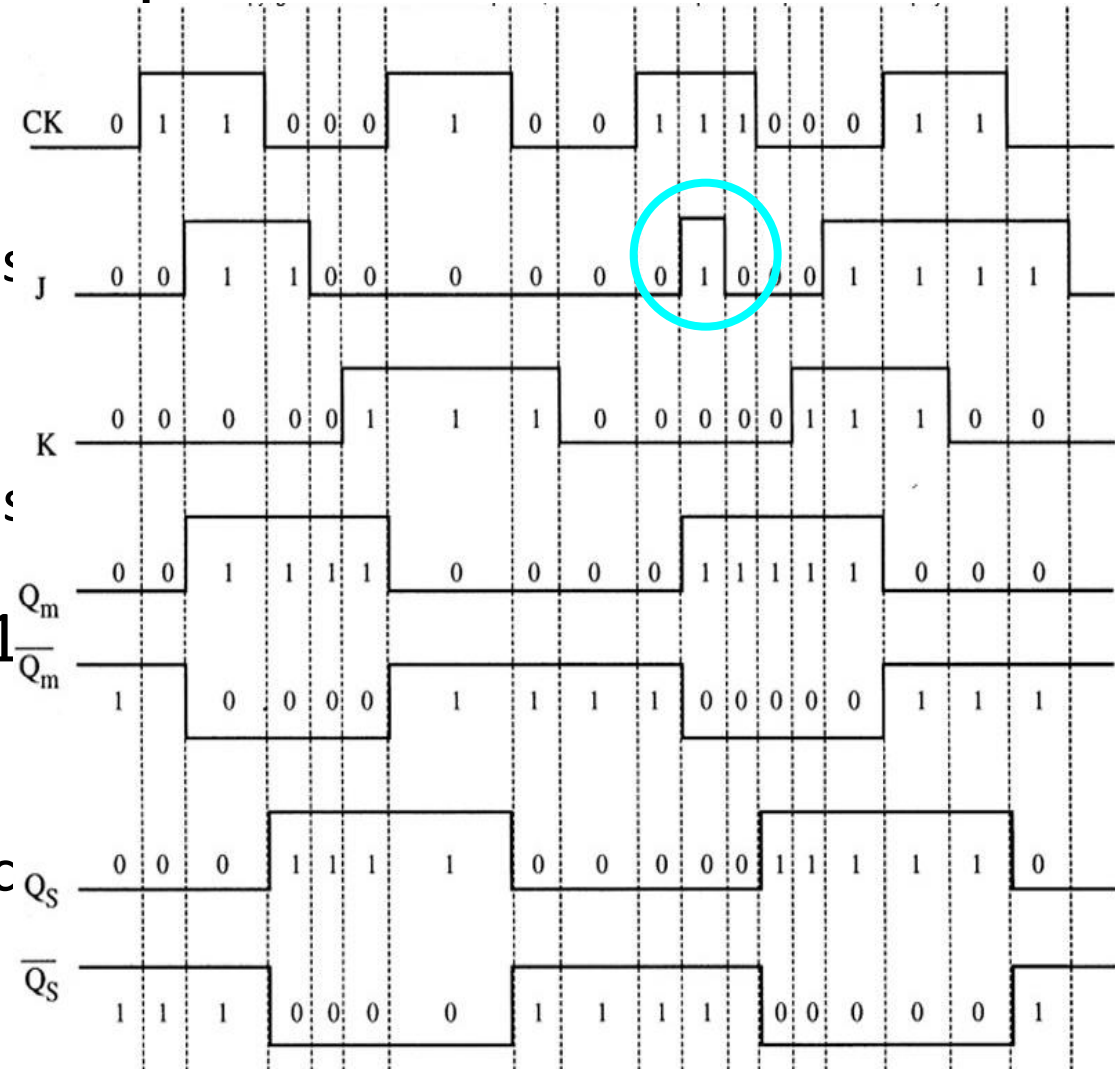
- Clock pulse $\rightarrow 0$
 - Master latch inactive (slave becomes master)
- Clock pulse $\rightarrow 1$
 - Slave latch inactive (master becomes slave)
- No uncontrolled oscillation : $J=K=1$
- Ones catching problem
 - Unwanted o/p transition due to glitch
 - Sol. : edge-triggered



Master-Slave Flip-Flop Problem

- S and/or R are permitted to change while C = 1

- Chances of 0s or 1s catching

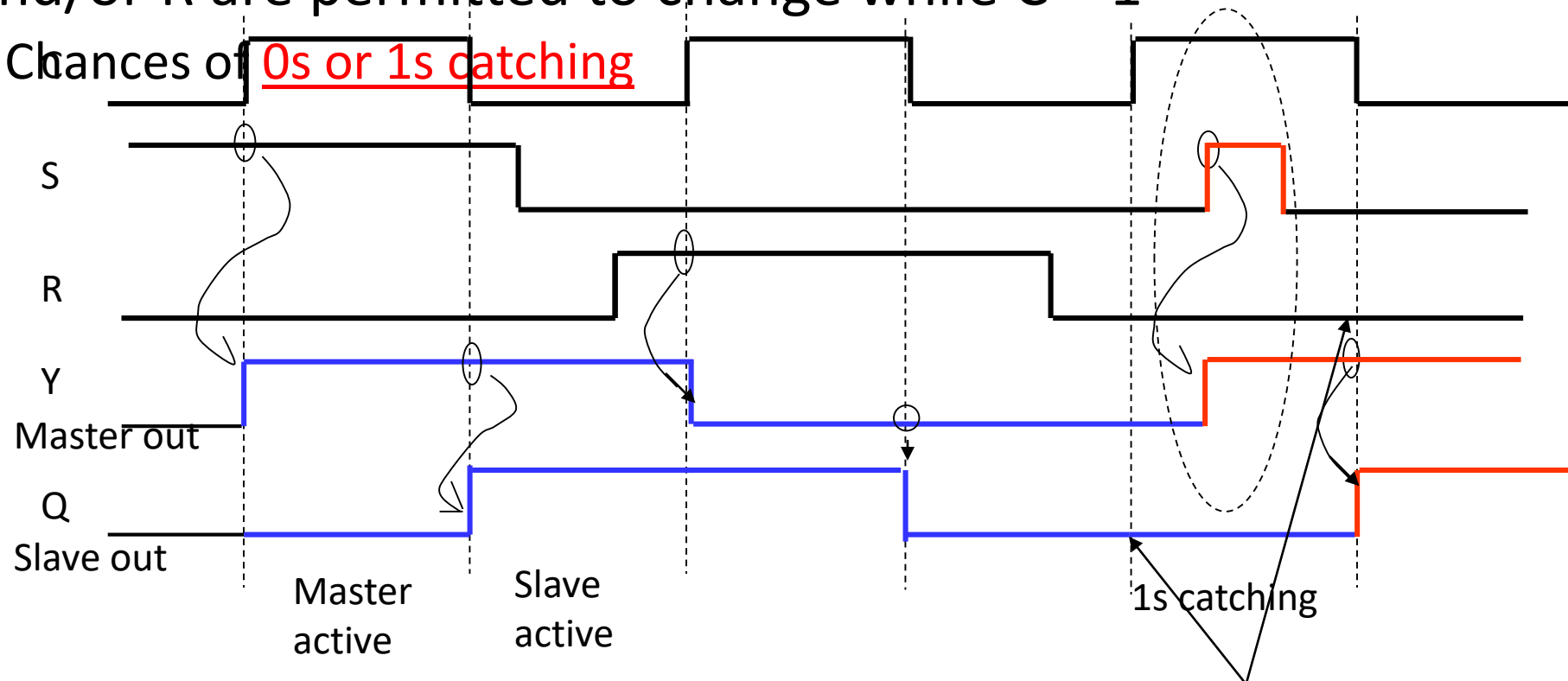


Flip-Flop Solution


- Use *edge-triggering* instead of master-slave
- An *edge-triggered* flip-flop ignores the pulse while it is at a constant level and triggers only during a *transition* of the clock signal
- Edge-triggered flip-flops can be built directly at the electronic circuit level, or
- A *master-slave D flip-flop* which also exhibits *edge-triggered behavior* can be used

Edge-Triggered D Flip-Flop


- *The edge-triggered D flip-flop is the same as the master-slave D flip-flop*
- It can be formed by:
 - Replacing the first clocked SR latch with a clocked D latch or
 - Adding a D input and inverter to a master-slave SR flip-flop
- The 1s and 0s catching behaviors are not present with D replacing S and R inputs
- The change of the D flip-flop output is associated with the negative edge at the end of the pulse
- *It is called a negative-edge triggered flip-flop*

 

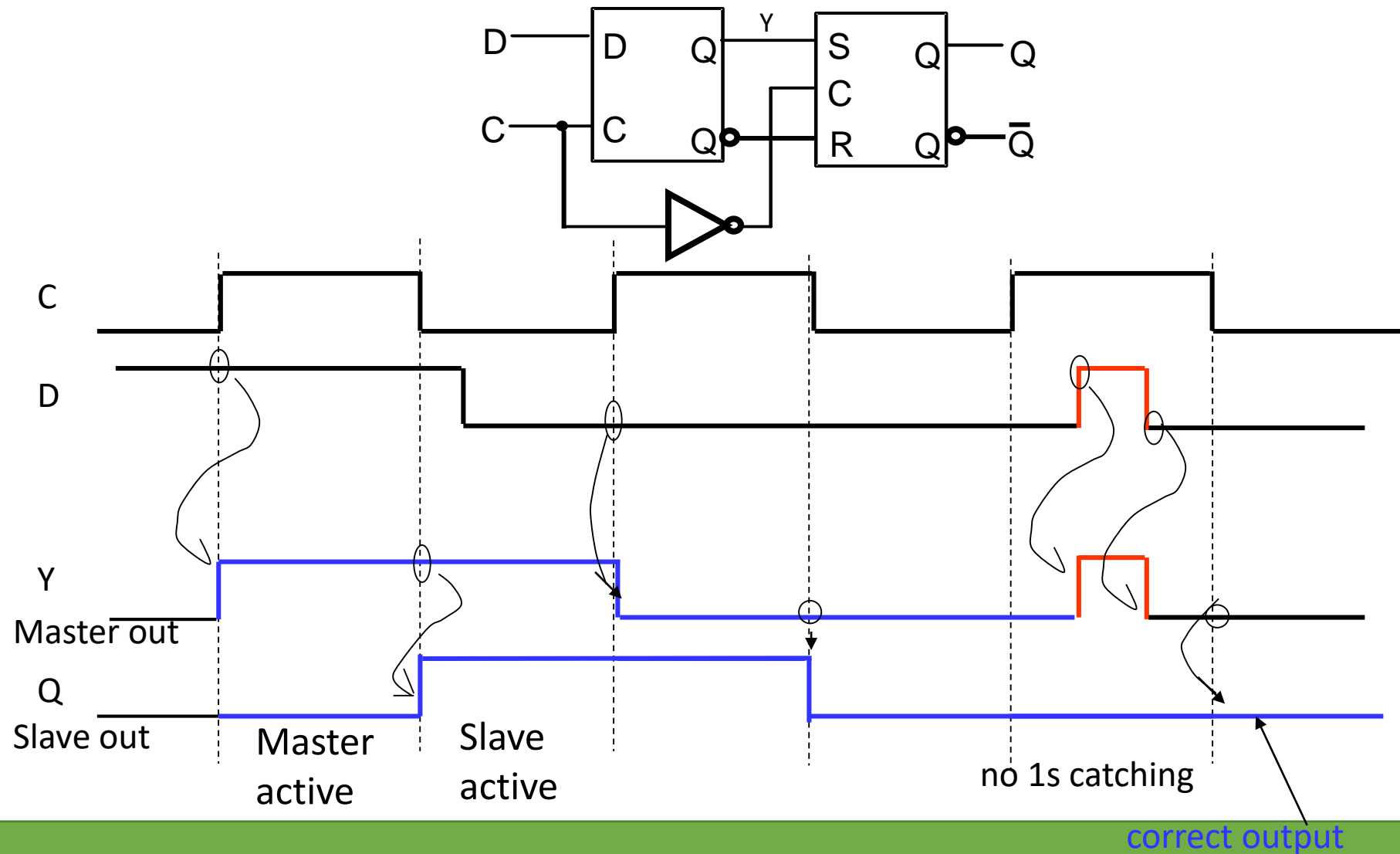No 1s catching in the edge-triggered D Flip-Flops









Setup and Hold time

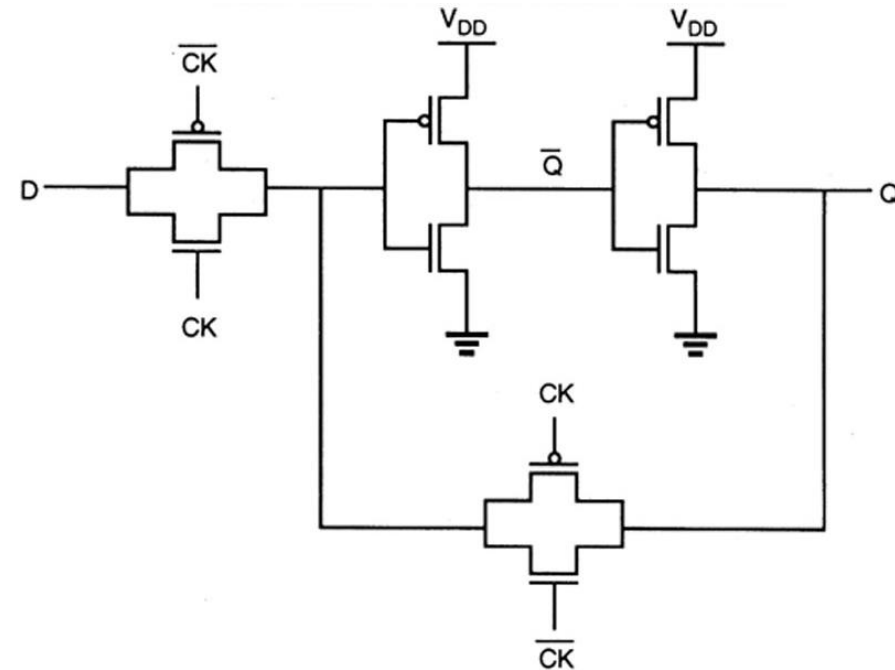

Timing Diagrams


Contamination and Propagation Delays

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk->Q Prop. Delay
t_{ccq}	Latch/Flop Clk->Q Cont. Delay
t_{pdq}	Latch D->Q Prop. Delay
t_{cdq}	Latch D->Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

      

Max-Delay: Flip-Flops
 
$$t_{pd} \leq T_c - \underbrace{\quad}_{\text{sequencing overhead}}$$



Min-Delay: Flip-Flops

$$t_{cd} \geq$$

