

0907534 Digital System Design	Midterm Exam	Fall 2016
7 Problems, 7 Pages	75 Minutes	November 14th, 8:00 AM
الرقم الجامعي:		الاسم:


Problem 1. Determine whether each of the following statements is True or False: **(5 points)**

Statement	T/F
Timing, area and power constraints are determined during the design partition step.	
HDL-based designs are technology dependent.	
Transistor Re-sizing is used to remove timing violations in post-synthesis timing verification.	
During fault simulation, both design errors and process-induced faults are considered.	
Critical real-time systems (e.g. plane wing controller, pacemaker) require high speed and low power. To achieve that, such systems are built as custom circuits.	

Problem 2. Answer the following short questions: **(6 points)**

 a. Given the following sequential circuit. Assume $t_{clk} = 13ns$, $t_{ffPD} = 0.5ns$, $t_{setup} = 0.3ns$, and $t_{hold} = 0.5ns$. Compute the setup and hold time margins:

<i>Setup time margin =</i>
<i>Hold time margin =</i>




b. Given the following procedural blocks and assuming the **current value** of $D_A = 0$, $Q_A = 1$, $D_B = 1$, and $Q_B = 0$. What are the values of Q_A and Q_B **after ΔT of the next positive edge of the clock**:


$Q_A =$
$Q_B =$

<pre>always @ (posedge clk) Q_A <= D_A; always @ (posedge clk) Q_B <= Q_A & D_B;</pre>
--

 c. **Without** the use of any **continuous assignment statements**, the **minimum** number of always procedural blocks required to implement the following circuit in Verilog is _____



 d. Which of the following RTL codes will be synthesized to the circuit given below:



<p>i.</p> <pre>always @ (*) begin S = QA + QB; R = S + C; end</pre>	<p>ii.</p> <pre>always @ (posedge clk) begin S = QA + QB; R = S + C; QA <= A; QB <= B; QR <= R; end</pre>	<p>iii.</p> <pre>always @ (posedge clk) begin QA = A; QB = B; S = QA + QB; R = S + C; QR <= R; end</pre>	<p>iv. None of the above</p>
---	--	---	------------------------------

e. In the code given below, how many latches will be synthesized? _____

<pre>always @ (*) begin G = 1'b0; if (A == 2'b00) begin F = 1'b1; H = 1'b0; end end</pre>	<pre>else if (A == 2'b01) begin F = 1'b0; G = 1'b1; end</pre>	<pre>else if (A == 2'b10) begin F = 1'b0; H = 1'b1; end</pre>	<pre>else begin F = 1'b0; H = 1'b0; end end</pre>
---	---	---	---

Problem 3. Given $F(A, B, C, D)$ below, answer the following questions: **(2.5 points)**

$$F(A, B, C, D) = A \bar{B} \bar{C} + \bar{A} D + C \bar{D}$$

a. In the table below, fill in one scenario that will cause a static 1-hazard at $t = 5$ sec:


<p>t = 0 sec A,B,C,D</p>	<p>t = 5 sec A,B,C,D</p>
<p> </p>	<p> </p>

b. Rewrite $F(A, B, C, D)$ to remove all static 1-hazards:

$F(A, B, C, D) =$

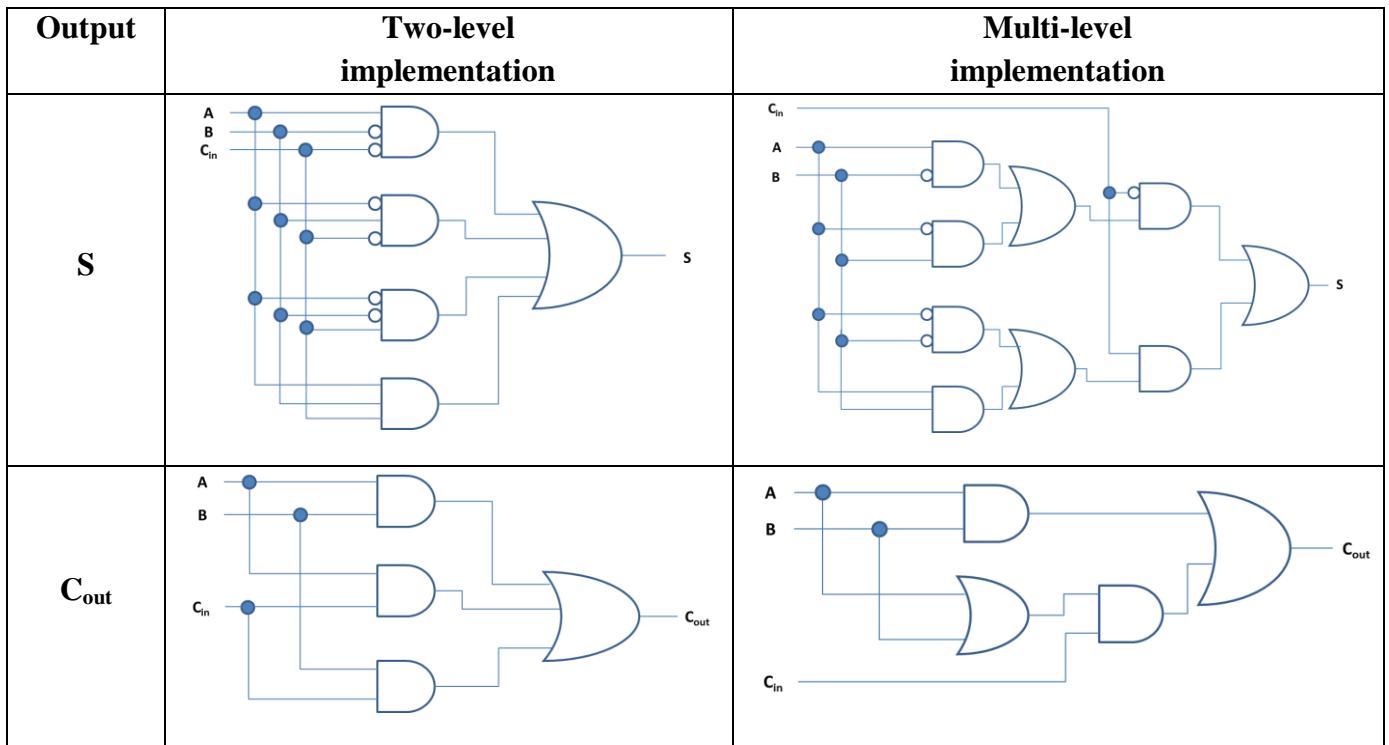Problem 4. A Full adder circuit has three inputs (A , B , C_{in}) and two outputs (S , C_{out}). The **two-level** and **multi-level** implementations of S and C_{out} are given below. Answer the questions below while taking into consideration the following assumptions: **(2 points)**

- When comparing different designs, the **Delay** and **Size** metrics are considered.
- Each gate input requires two transistors.
- All gates have the same delay regardless of gate type and number of inputs.
- Inverters are ignored in Delay and Size calculation.



- a.** Which of the following statements is correct regarding the output S ?
- The delay of multi-level implementation is lower than the delay of two-level implementation.
 - The size of multi-level implementation is smaller than the size of two-level implementation.
 - The multi-level implementation is neither an optimization nor a tradeoff of the two-level implementation.
 - All the above
 - None of the above
- b.** Which of the following statements is correct regarding the output C_{out} ?
- The delay of multi-level implementation is lower than the delay of two-level implementation.
 - The size of multi-level implementation is bigger than the size of two-level implementation.
 - The multi-level implementation is an optimization of the two-level implementation.
 - The multi-level implementation is a tradeoff of the two-level implementation.
 - None of the above

Problem 5. Given $F(x, y, z)$ below, answer the following questions:

(5.5 points)

$$F(x, y, z) = \bar{x} \bar{y} \bar{z} + \bar{x} \bar{y} z + x \bar{y} \bar{z} + x \bar{y} z + x y \bar{z}$$

a. Using Automatic tabular optimization method (Quine McCluskey), fill in the following spaces:

- How many comparisons are needed to generate all 2-literal implicants? _____
- List all 2-literal implicants generated during the process: _____

- How many comparisons are needed to generate all 1-literal implicants? _____
- List all 1-literal implicants generated during the process: _____

Show your steps clearly in here:

b. Using the iterative heuristic optimization method, one can legally expand the term $\bar{x}\bar{y}\bar{z}$ to $\bar{y}\bar{z}$. After that the function $F(x, y, z)$ becomes as follows:


$$F(x, y, z) = \bar{y} \bar{z} + \bar{x} \bar{y} z + x \bar{y} z + x y \bar{z}$$

Determine if the following expansion is legal and update $F(x, y, z)$ accordingly:


Expansion	Legal? Yes/No	$F(x, y, z)$
Expand $\bar{y}\bar{z}$ to \bar{y}		

 Problem 6. The diagram below is for a remote control of a fan. The remote control has 3 input buttons and 2 outputs “XY” which represent the fan speed. The functionality is as follows: **(6 points)**

- At reset the fan is OFF.
- When the fan is OFF and the user presses the “S” button then the fan will turn ON and the speed will be 1 by default (i.e. XY = 01).
- The “H” is used to increase the speed of the fan and “L” button is used to decrease the speed of the fan.
- The maximum speed is 2 (i.e. XY = 10), so if the user presses the “H” and the speed is already 2 then nothing will happen.
- The minimum speed when the fan is ON is 1 (i.e. XY = 01), so if the user presses the “L” and the speed is already 1 then nothing will happen.
- When the fan is ON and the user presses the “S” button then the fan will turn off and the speed will become zero (i.e. XY = 00).
- **If the user presses multiple buttons together, nothing should happen.**



 a. Complete the state transitions of the FSM of the remote control given below:




b. Which state encoding below can be used for the FSM above in order to achieve output encoding:

i. $S_0 = 00, S_1 = 01, S_2 = 10$	ii. $S_0 = 00, S_1 = 11, S_2 = 01$	iii. $S_0 = 01, S_1 = 10, S_2 = 00$
iv. $S_0 = 001, S_1 = 010, S_2 = 100$	v. i or iv	vi. None of the above

c. Which flip-flop would you use to reduce metastability caused by the asynchronous inputs “S”, “H”, and “L” with the **highest probability**:


i. FF with setup/hold time of 0.1ns	ii. FF with setup/hold time of 0.2ns	iii. FF with setup/hold time of 0.05ns
-------------------------------------	--------------------------------------	--

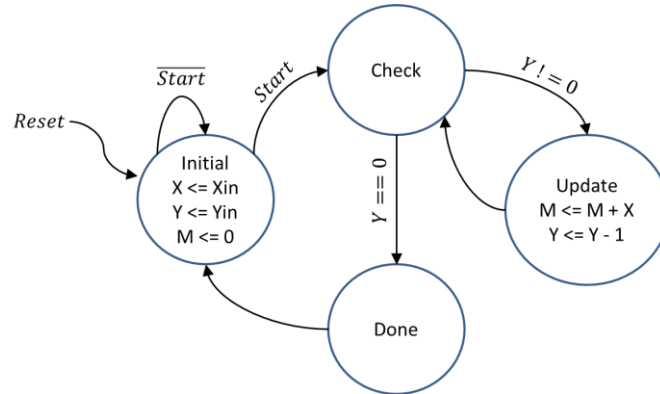Problem 7. The HLSM below is for a multiplier ($M = X * Y$) that uses repeated addition. For example, if $X = 5$ and $Y = 3$ then $M = 5+5+5=15$. Assume that $X \geq 0$ and $Y \geq 0$. (8 points)



a. Given $X_{in} = 3$ and $Y_{in} = 2$, how many cycles the system will be in the Update state? _____

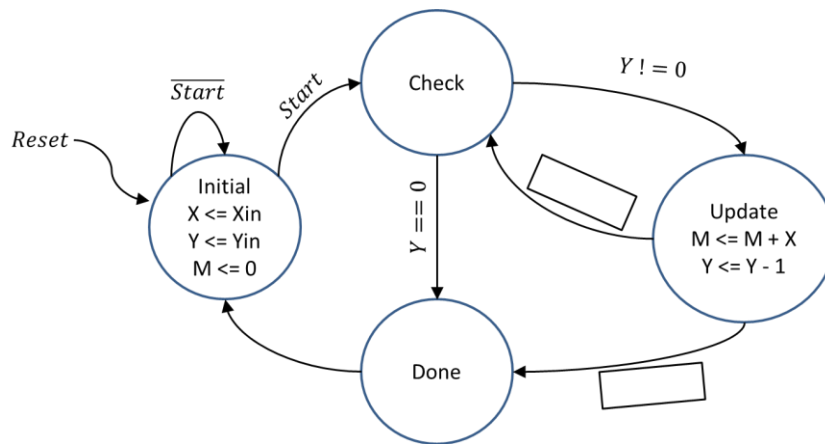
b. The design above can be slightly improved by adding a new transition from Update to Done state as shown in the figure below. Fill in the missing transition conditions:



c. Choose the correct answer. The improvement given above is useful:


i. Only if $Y_{in} = 1$	ii. Only if $Y_{in} = 0$	iii. If $Y_{in} \geq 0$	iv. If $Y_{in} > 0$	v. None of the above
-------------------------	--------------------------	-------------------------	---------------------	----------------------

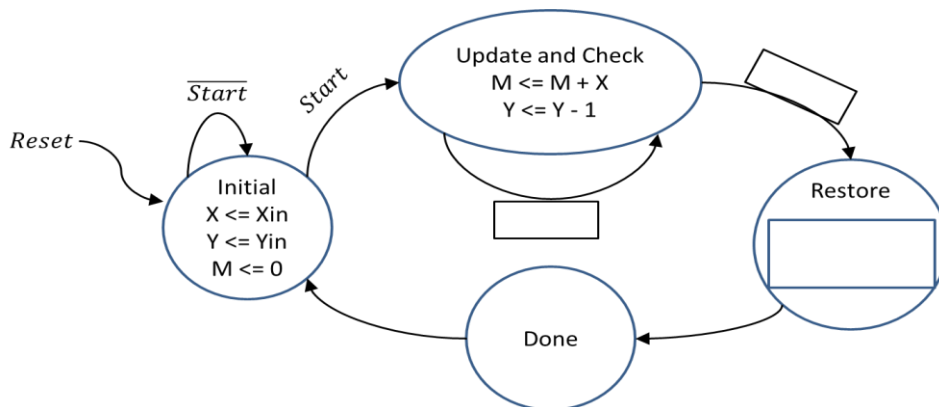d. The design can be significantly improved by merging Update and Check states as shown below. Fill in the statements necessary in the Restore state and all missing transition conditions:



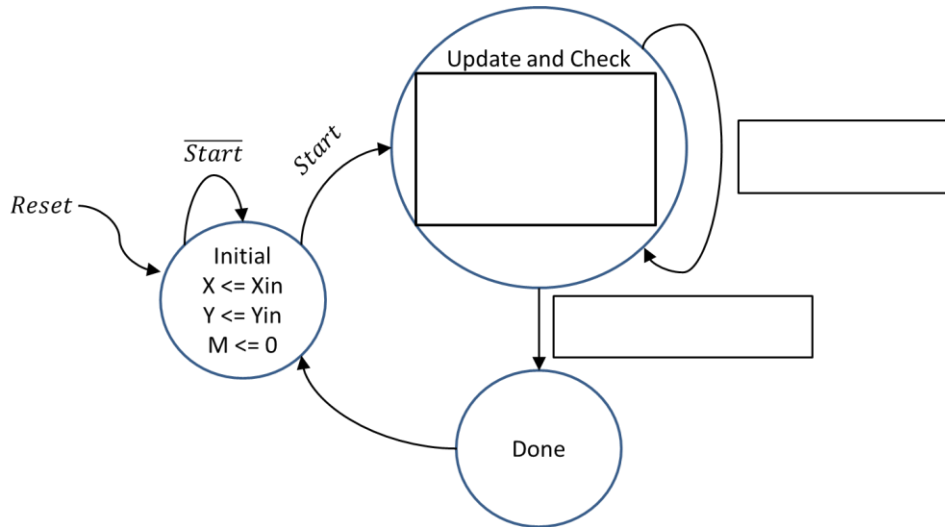e. A mealy HLSM can be used to reduce the number of states. Complete the mealy HLSM given below in order for the multiplier to work properly.

Bonus: if you implement the most efficient design, you get one extra bonus point



f. Assume that $X_{in} = 2$ and $Y_{in} = 100$. In this case, any of the above mentioned designs will need more than 100 cycles to compute the result (i.e. $M = 2+2+2+\dots+2 = 200$) because Y is used as the counter. On the other hand, if X is used as a counter, it would have been much easier to compute the result as $M = 100+100 = 2$ which consume much less cycles. Draw a **Mealy HLSM** that address this issue and help you achieve the best performance based on the values of X_{in} and Y_{in} .