

Problem 1

POWERUNIT

Color	Code
Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Grey	8
White	9
Gold	5%
Silver	10%
None	20%


Answer Question (1) Using the resistance color codes provided in the table shown

4

Question (1): The minimum resistance value (in ohm) for a resistor with (Yellow, black, Yellow, Gold) color is:

(2 Points)

Enter your answer

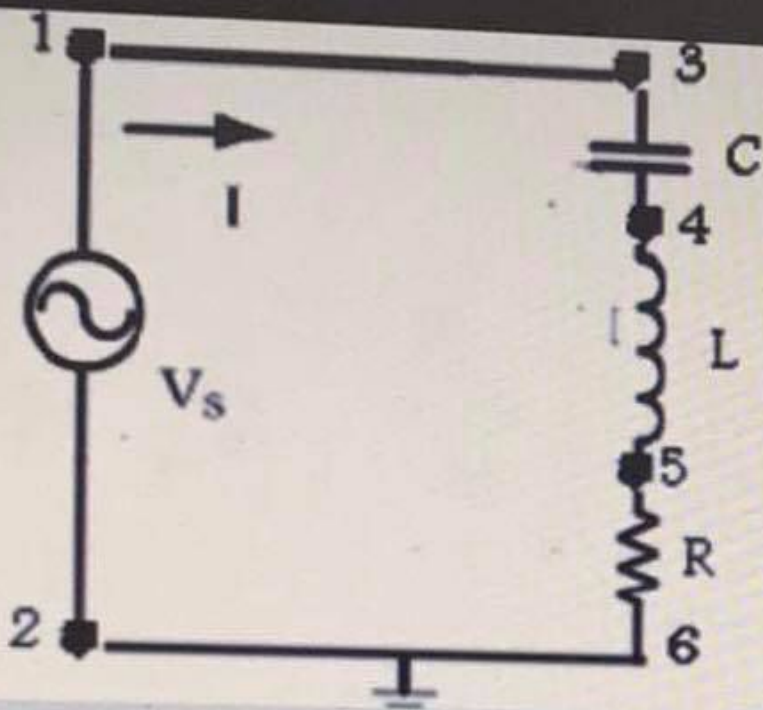

Problem 3

For the RLC circuit shown, answer Questions (5) - (7)

POWERUNIT

8

Question (5): To measure the peak to peak value of V_s , the suitable device to be connected between 1 and 2 is :between 1 and 2 is (2 نقطة)

oscilloscope

I

8

Question (5): To measure the peak to peak value of V_s , the suitable device to be connected between 1 and 2 is:
(2 Points)

oscilloscope using peak to peak value through measure




9

Question (6): To measure the RMS value of V_s , the suitable device to be connected between 1 and 2 is:
(2 Points)

oscilloscope using DC voltage value through measure

10

Question (7): How can you measure the phase shift between V_s and I ? 
(2 Points)

we measure the phase shift between v_s and v_r because v_r is in phase with the current

 POWERUNIT

Back

Next




88%

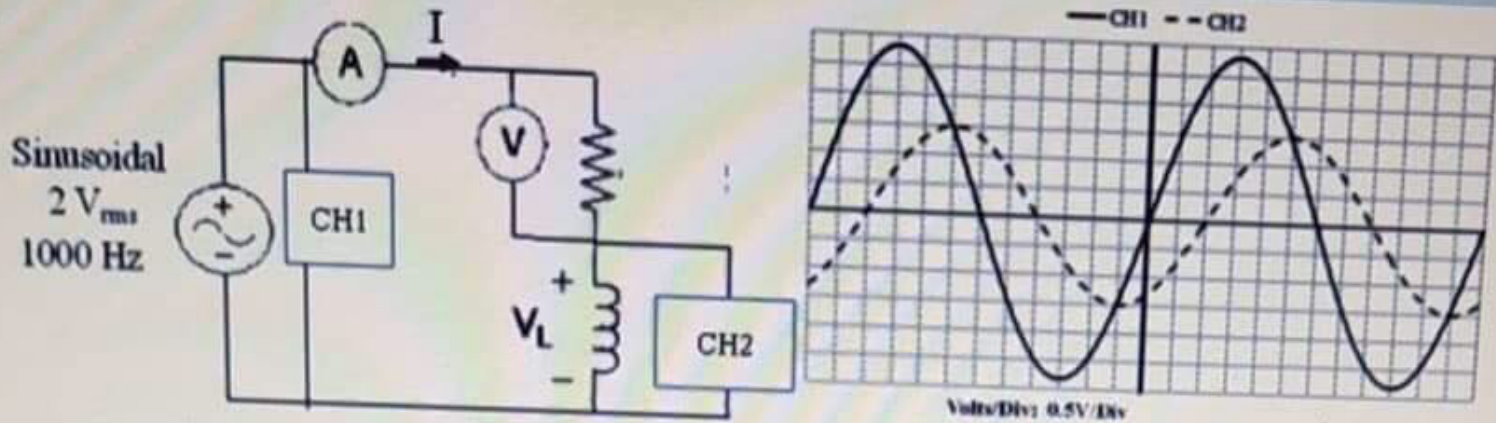Problem 4



For the circuit shown, if the ammeter reading is 3.54 mA rms, then answer Questions (8) - (10).



11

Question (8): The time division of the oscilloscope is:

(2 Points)

Enter your answer

12



Question (9): The approximate value of the inductor (in Henry) is:
(2 Points)

1.35 mH

13