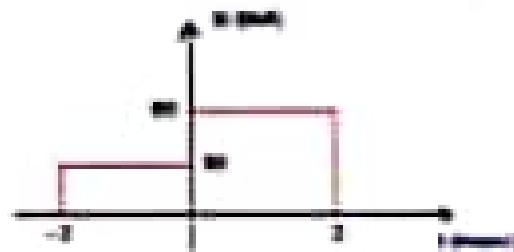



### Question 3/14 (a)

The plot shown in the figure depicts the current through a  $10 \mu F$  capacitor. Find the voltage across the capacitor  $v_c(t=0)$ , given that  $v_c(t=\infty)=0$ .




- 20 V
- None of the choices
- 3 V
- 10 V
- 4 V

Mark as correct

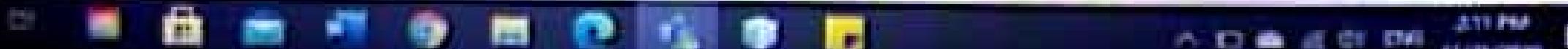
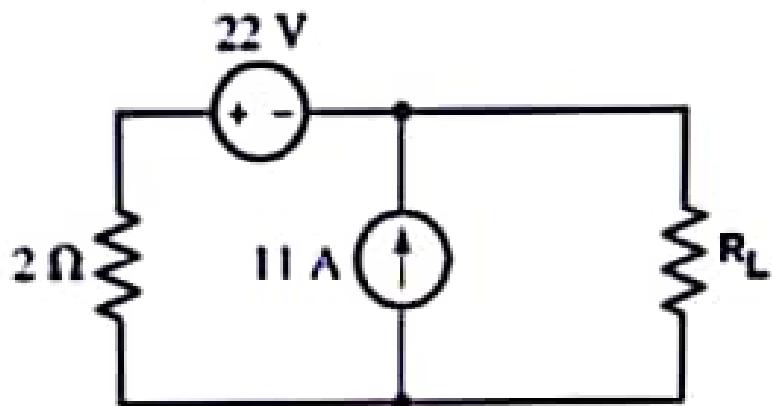
## Question 13/14 (2 p.)

Consider the circuit shown in the figure. What is the maximum power that can be absorbed by  $R_L$  from the circuit?




- 2 W
- 0 W
- None of the choices
- 3 W
- 1 W



SUBMIT ANSWER
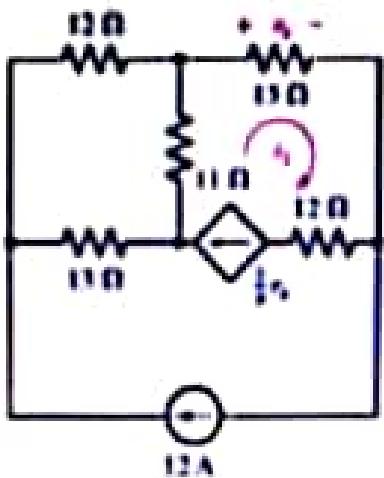
## Question 8/14 (2 p.)

What is the value of the current  $i_1$  in the circuit given below?



- 3.8 A
- 3.8 A
- None of the choices
- 3.2 A
- 3.2 A




SUBMIT ANSWER


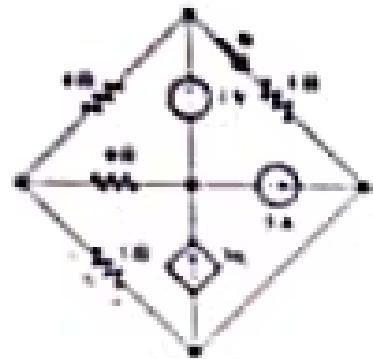
### Question 2/14 (P)

Consider the circuit shown in the figure and find the contribution of the current source 3A only on the value of the current  $i_1$ .




- 7/9 A
- +7/9 A
- None of the choices
- 3/7 A
- 7/9 A

Support analysis


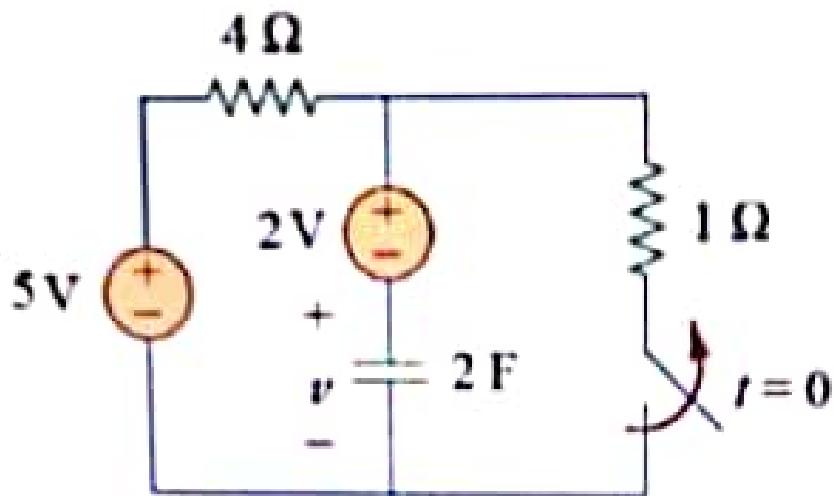
## Question 4/4 (2 p.)

Find the voltage across the capacitor at  $t = 1 \text{ s}$  ( i.e.,  $v(1)$  )




- 4.77V
- None of the choice
- 0.06V
- 0.53V
- 0.53V

SUBMIT ANSWER

## Question 2/4 (2 p.)

The circuit in the figure will produce

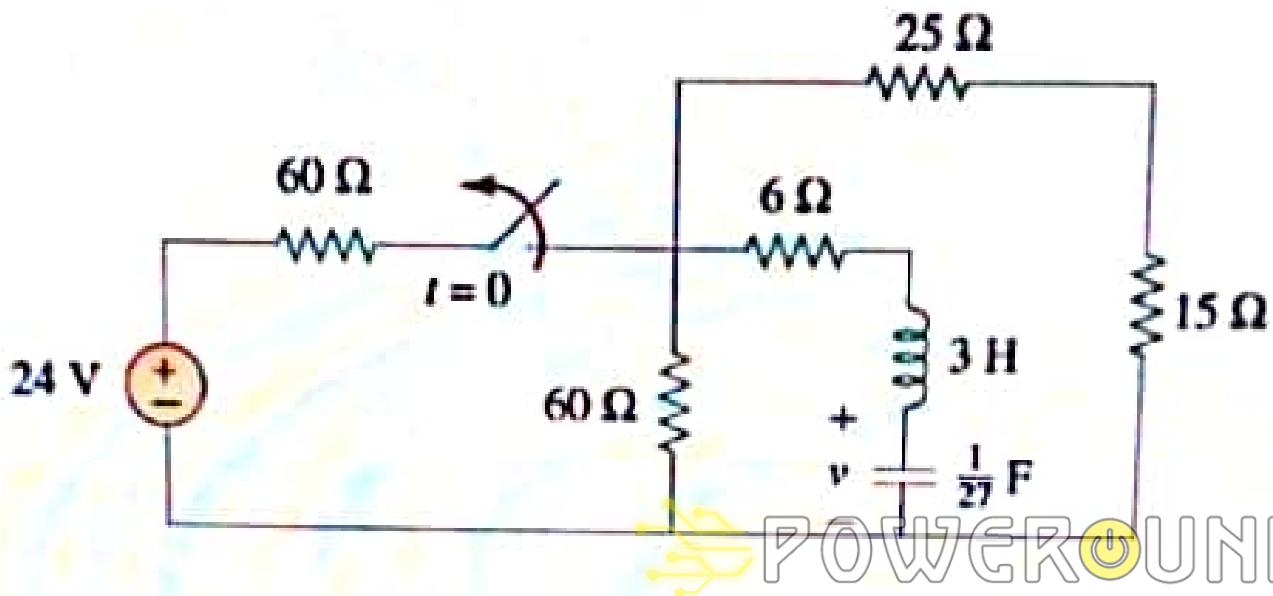


- An underdamped response
- A critically damped response
- None of the choices
- An undamped response
- An overdamped response

SUBMIT ANSWER

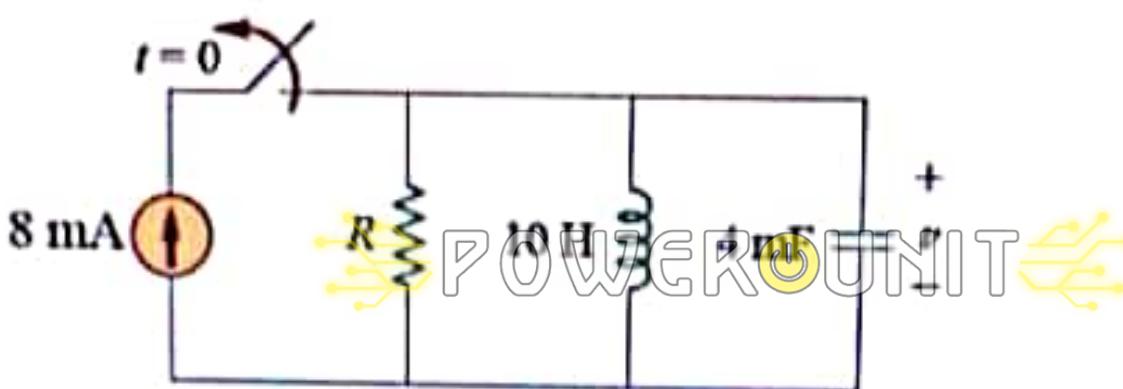
## Question 3/4 (3 p)

The value of the resistor  $R$  is adjusted such that the response is critically damped. Find the voltage across the capacitor  $v(t)$ , for  $t > 0$



- $v(t) = 2e^{-5t} - 5te^{-5t}$ ,  $t > 0$
- None of the choices
- $v(t) = -2e^{-5t} - 5te^{-5t}$ ,  $t > 0$
- $v(t) = -2te^{-5t}$ ,  $t > 0$
- $v(t) = -2e^{-5t} - 5te^{-5t}$ ,  $t > 0$
- $v(t) = -5te^{-5t}$ ,  $t > 0$


SUBMIT ANSWER

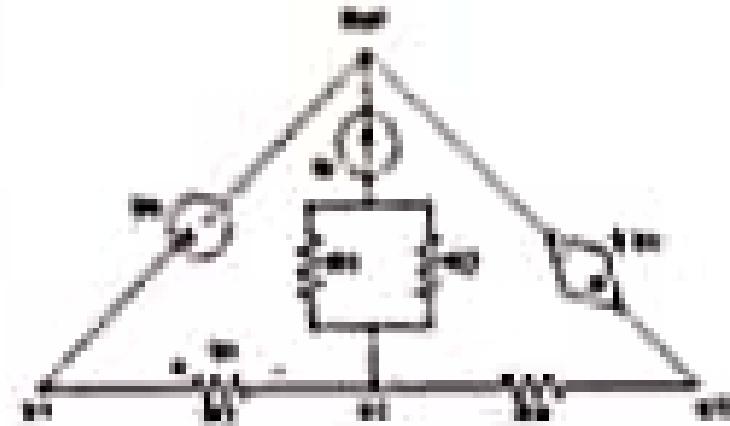

 POWERUNIT

For the circuit shown in the figure ,  $I = 22 \text{ mA}$ ,  $V_1 = 20 \text{ V}$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 4 \text{ k}\Omega$ ,  $R_3 = 1 \text{ k}\Omega$ ,  $R_4 = 1 \text{ k}\Omega$ .  
What is  $V_2$  using nodal analysis.

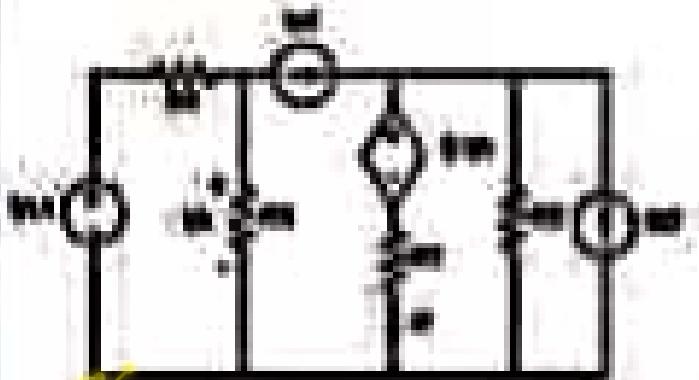- 1)  $-4V$
- 2)  $4V$
- 3) None of the choices
- 4)  $-\frac{1}{4}V$
- 5)  $\frac{1}{4}V$
- 6)  $4V$




POWERUNIT

For the circuit shown in the figure if  $R_1 = 8 \Omega$ ,  $R_2 = 4 \Omega$ ,  $R_3 = 3 \Omega$ ,  $R_4 = 6 \Omega$ ,  $V_1 = 5 V$ ,  $I_1 = 5 A$ ,  $I_2 = 10 A$ . Find the contribution of  $R_2$  only in the value of  $I_1$ .

- 21A.
- 3A.
- 4A.
- None of the above.
- 1A.
- 8A.
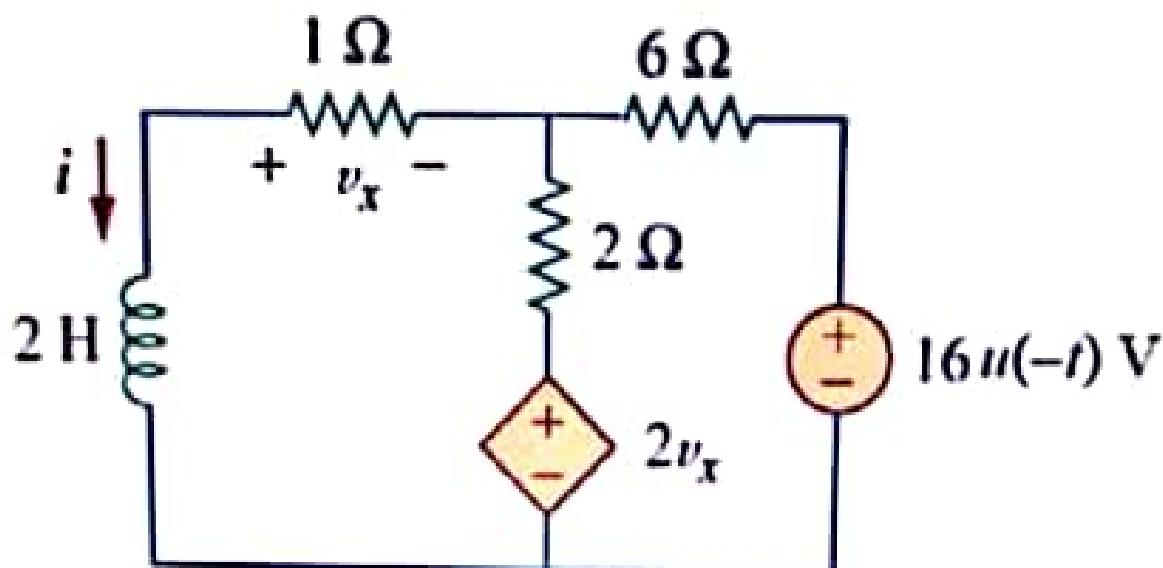
## Question 1/4 (3 p.)

Find the time constant (in seconds) for the circuit in the figure below




- 5
- 0.2
- 4
- 0.25
- 2
- 0.5
- None of the choices


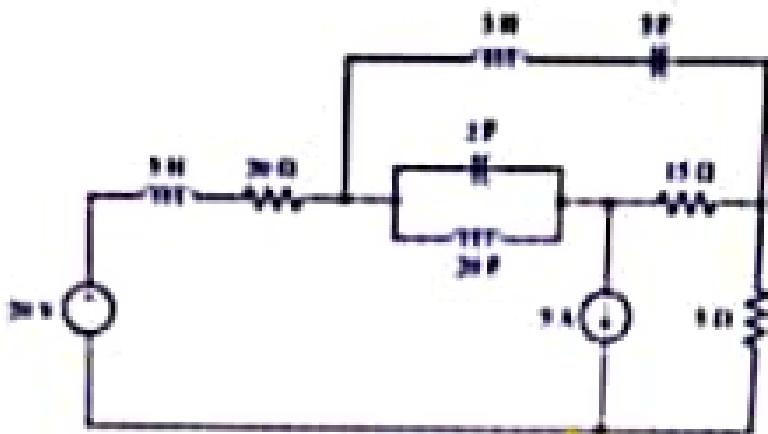
## Question 6/14 (2 p)


What is the value of the generated power by the current source 5 A?

Assume that there is no initial stored energy in the capacitors and inductors.



- 400 W
- 800 W
- 200 W
- 600 W
- None of the choices

SUBMIT ANSWER

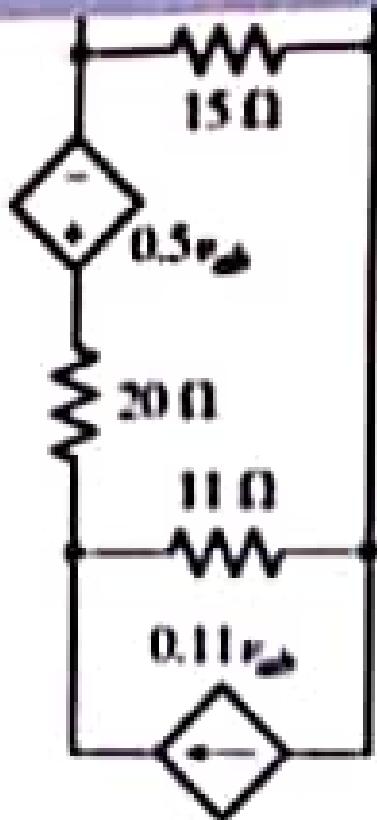


- $\frac{9000}{707} \Omega$
- $\frac{9300}{707} \Omega$
- $\frac{2200}{707} \Omega$
- None of the choices
- ~~$\frac{3000}{707} \Omega$~~

POWERUNIT

SUBMIT ANSWER
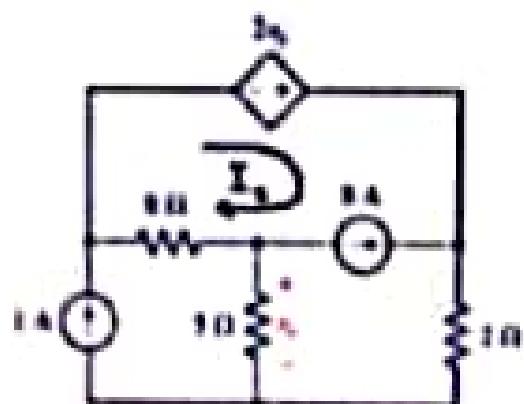
## Question 5/14 (3 p.)

Consider the circuit shown in the figure and find the value of the current  $I_2$ , using mesh analysis.




- 4.25 A
- 4.25 A
- None of the choices
- 4.52 A
- 4.52 A

SUBMIT ANSWER
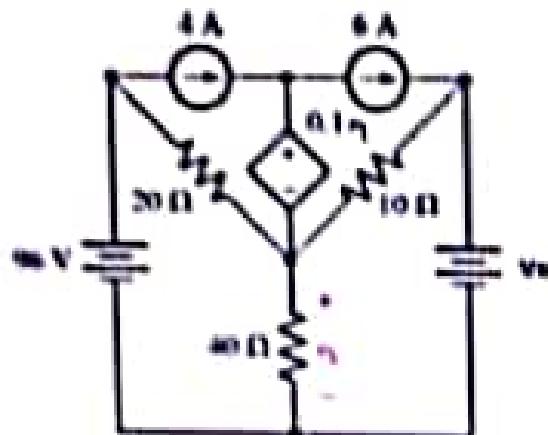
## Question 7/14 (2 p)

Consider the circuit shown in the figure. What is the contribution of the voltage source 96V only on the value of  $v_L$  ?



$\frac{291}{i}$



$\frac{129}{i}$



$\frac{192}{i}$


 None of the choices

$\frac{219}{i}$

SUBMIT ANSWER
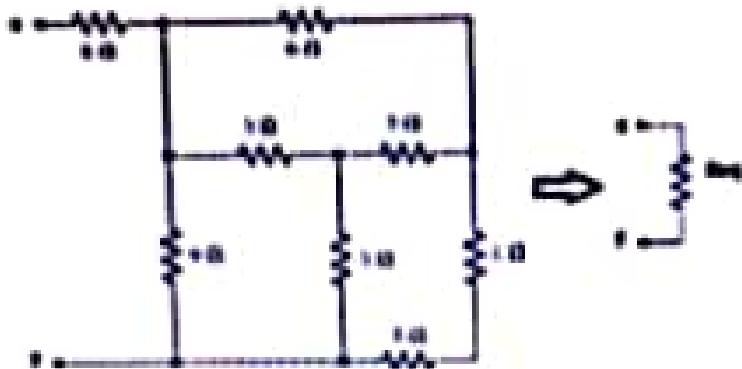
## Question 14/14 (2 p.)

What is the value of  $R_{eq}$  in the figure?



$\frac{140}{13} \Omega$



$\frac{130}{13} \Omega$


None of the choices

$\frac{102}{13} \Omega$

$\frac{130}{14} \Omega$
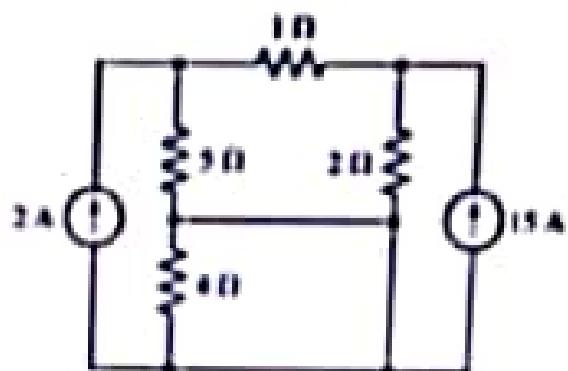
## Question 11/14 (2 p)

Consider the circuit shown in figure, what is the power absorbed



by the  $1\Omega$  resistor ?


- 62.5 W
- 6.25 W
- None of the choices
- 25 W
- 60 W



SUBMIT ANSWER
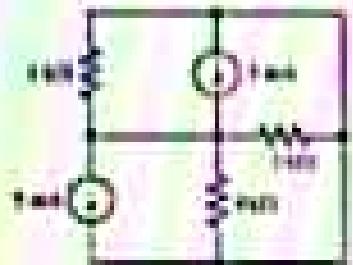
### Question 1/14 (7 p.)

If we simplify the circuit shown in the figure into one voltage source  $V_s$  and one resistor  $R_L$ , then what are the values of  $V_s$  and  $R_L$ ?




POWERUNIT

- Type of the circuit
- $V_s = 8/7$  with  $R = 4/7 \Omega$
- $V_s = 8/7$  with  $R = 4/7 \Omega$
- $V_s = 4/7$  with  $R = 8/7 \Omega$
- $V_s = 4/7$  with  $R = 4/7 \Omega$

Next Question
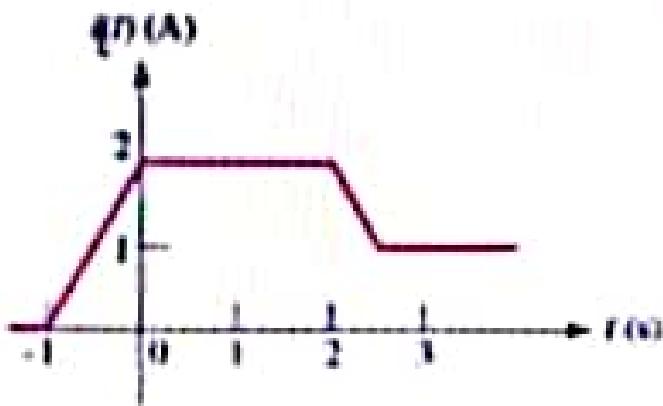
## Question 4/14 (2 p.)

The plot shown in the figure depicts the current through a  $20\text{ mH}$  inductor. Find the maximum stored energy (in  $\text{mJ}$ ) in the inductor given that  $I_L(t=-\infty)=0\text{ A}$ .




- 40
- .04
- None of the choices
- 0.4
- 400

Submit Answer
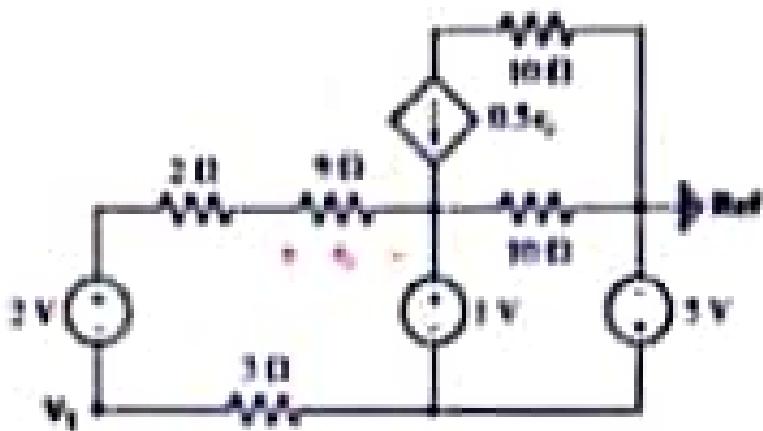
## Question 10/14 (2 p.)

Consider the circuit shown in the figure, what is the value of the voltage  $V_1$ , using nodal analysis?



$\frac{-67}{14} \text{ V}$



$\frac{14}{67} \text{ V}$



$\frac{-14}{67} \text{ V}$


$\frac{67}{14} \text{ V}$

 None of the choices

SUBMIT ANSWER
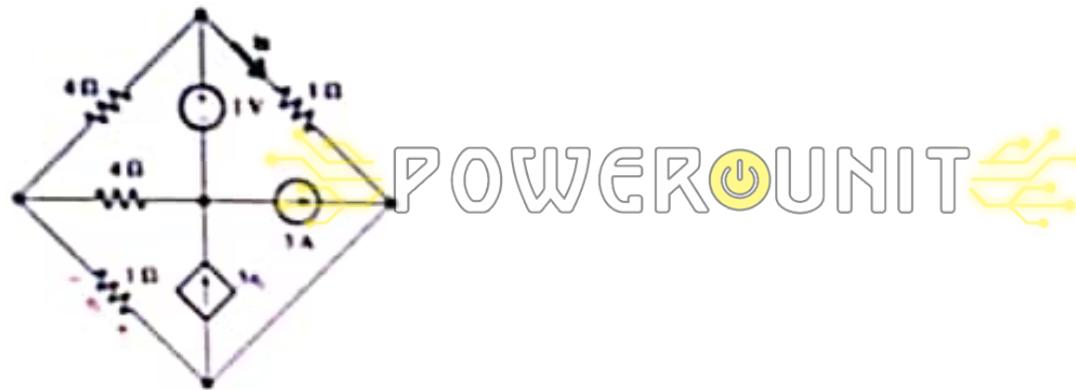
### Question 2/14 (2 p.)

Consider the circuit shown in the figure and find the contribution of the current source 3A only




- 7/9 A
- 9/7 A
- None of the choices
- 9/7 A
- 7/9 A

SUBMIT ANSWER
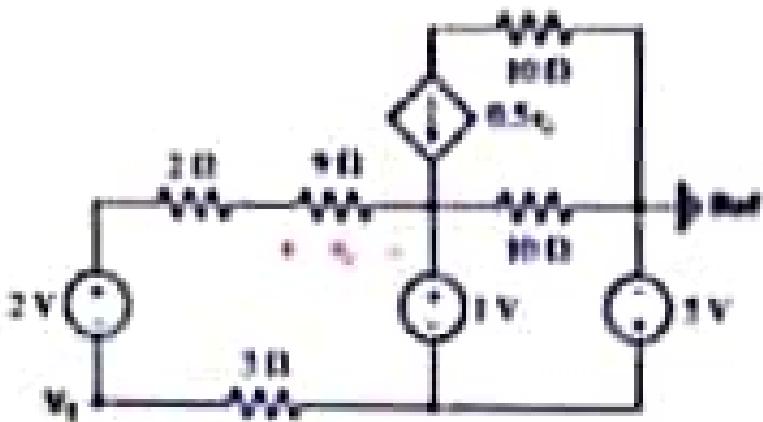
## Question 10/14 (7 p.)

Consider the circuit shown in the figure, what is the value of the voltage  $V_1$ , using nodal analysis?



$\frac{-67}{14} \text{ V}$



$\frac{14}{67} \text{ V}$



$\frac{-14}{67} \text{ V}$


$\frac{67}{14} \text{ V}$

 None of the choices

SUBMIT ANSWER
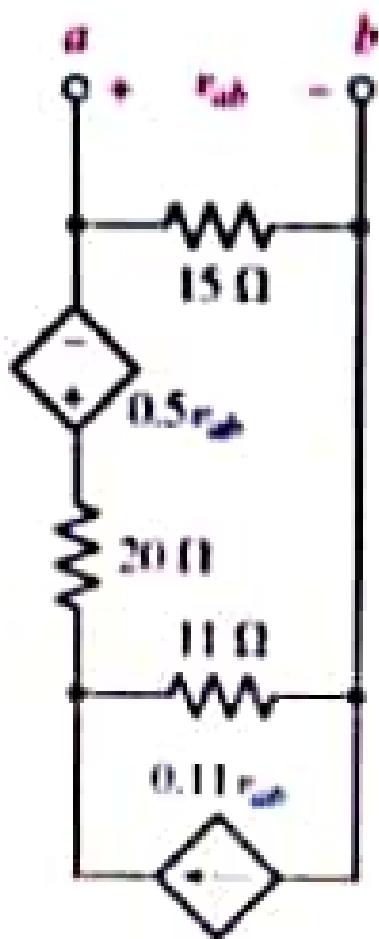
## Question 9/14 (2 p)

Find the Thevenin equivalent resistance  $R_{th}$  as seen by an unspecified element connected between terminals a and b.



POWERUNIT

$\frac{5625}{107}\ \Omega$

$\frac{2222}{107}\ \Omega$

$2222\ \Omega$



For the circuit shown in the figure 1, if  $I_1 = 2 \text{ mA}$ ,  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ ,  $R_3 = 4 \text{ k}\Omega$ ,  $R_4 = 2 \text{ k}\Omega$ ,  $R_5 = 3 \text{ k}\Omega$ , and  $R_6 = 1 \text{ k}\Omega$ . Find the absorbed power by  $R_3$ .

16 mW

40 mW

None of the choices


64 mW

32 mW

80 mW
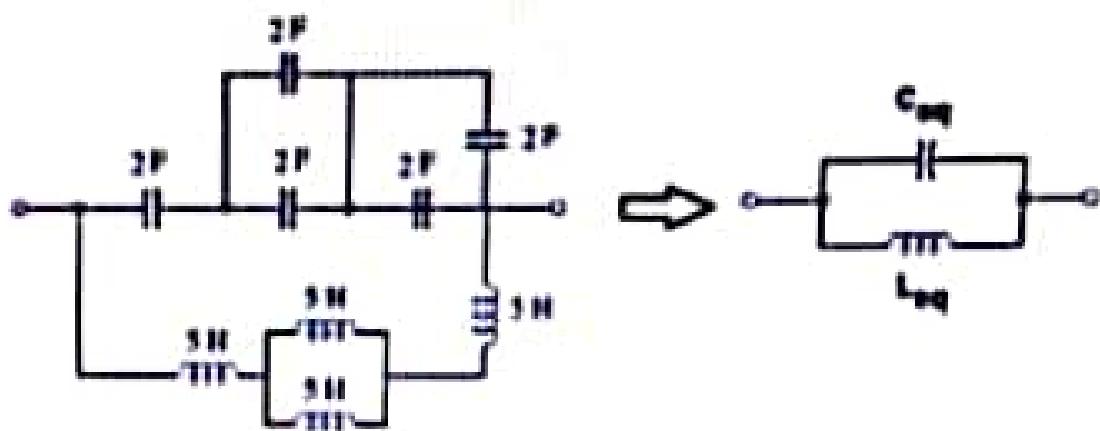
## Question 12/14 (2 p)

Consider the circuit shown in the figure. After simplifying the circuit into one capacitor and one inductor, what are the values of  $C_{eq}$  and  $L_{eq}$



$C_{eq} = 1.75 \text{ F}, L_{eq} = 0.1 \text{ H}$



$C_{eq} = 17.5 \text{ F}, L_{eq} = 1 \text{ H}$

$C_{eq} = 1.75 \text{ F}, L_{eq} = 1 \text{ H}$


None of the choices

$C_{eq} = 1 \text{ F}, L_{eq} = 17.5 \text{ H}$

**SUBMIT ANSWER**
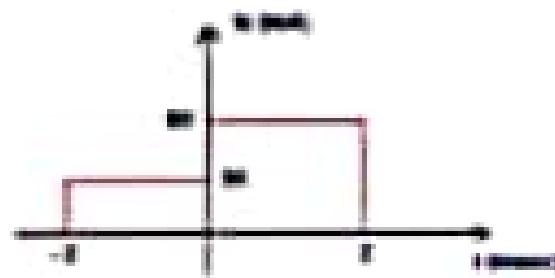
### Question 3/14 (3 p.)

The plot shown in the figure depicts the current through a  $10 \mu F$  capacitor. Find the voltage across the capacitor  $v_c(t=0)$ , given that  $v_c(t=-\infty)=0$ .



- 20 V
- None of the choices
- 1 V
- 40 V
- 8 V

الإجابة الصحيحة

## Question 2/15 (4 p.)

In a series resonant RLC circuit, if the voltage source is  $v_s(t) = 60\sin(\omega t)$  V, the maximum value of the current is 1.1 A and occurs at  $\omega = 100$  K rad/s, and the value of the current at  $\omega = 90$  K rad/s is 7.071 A. Find the values of L and C.



- L = 0.3515 mH, C = 0.284 μF
- L = 0.703 mH, C = 0.142 μF
- L = 0.284 mH, C = 0.3515 μF
- L = 0.142 mH, C = 0.703 μF
- L = 0.142 mH, C = 0.284 μF

\_\_\_\_\_

$v(t) = \cos\left(\frac{t}{\sqrt{LC}}\right) + \frac{\sqrt{L}}{\sqrt{C}} \sin\left(\frac{t}{\sqrt{LC}}\right)$  V


$v(t) = \cos\left(\frac{t}{\sqrt{LC}}\right) - \frac{\sqrt{L}}{\sqrt{C}} \sin\left(\frac{t}{\sqrt{LC}}\right)$  V

$v(t) = \cos\left(\frac{t}{\sqrt{LC}}\right) + \frac{\sqrt{C}}{\sqrt{L}} \sin\left(\frac{t}{\sqrt{LC}}\right)$  V

$v(t) = \cos\left(\frac{t}{\sqrt{LC}}\right) - \frac{\sqrt{C}}{\sqrt{L}} \sin\left(\frac{t}{\sqrt{LC}}\right)$  V

$v(t) = \sin\left(\frac{t}{\sqrt{LC}}\right)$  V

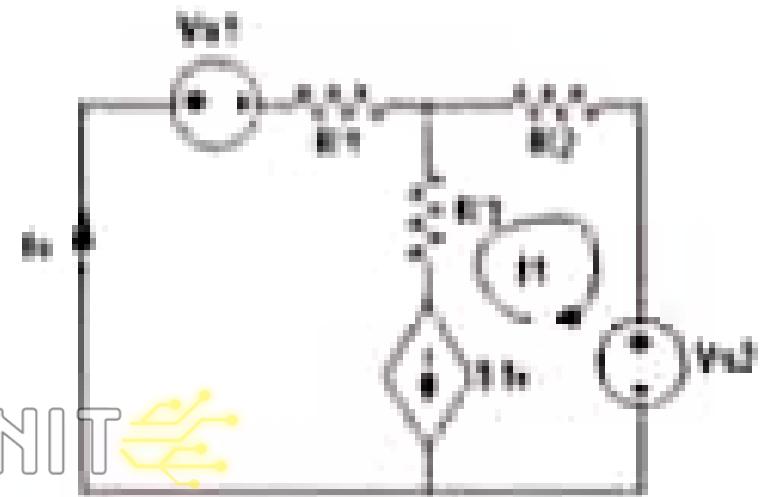$v(t) = \cos\left(\frac{t}{\sqrt{LC}}\right)$  V




**POWERUNIT**

For the circuit shown in the figure, if  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ m}\Omega$ ,  $R_3 = 1 \text{ m}\Omega$ ,  $V_{11} = 5 \text{ V}$ ,  $V_{12} = 11 \text{ V}$ , find it using mesh analysis.

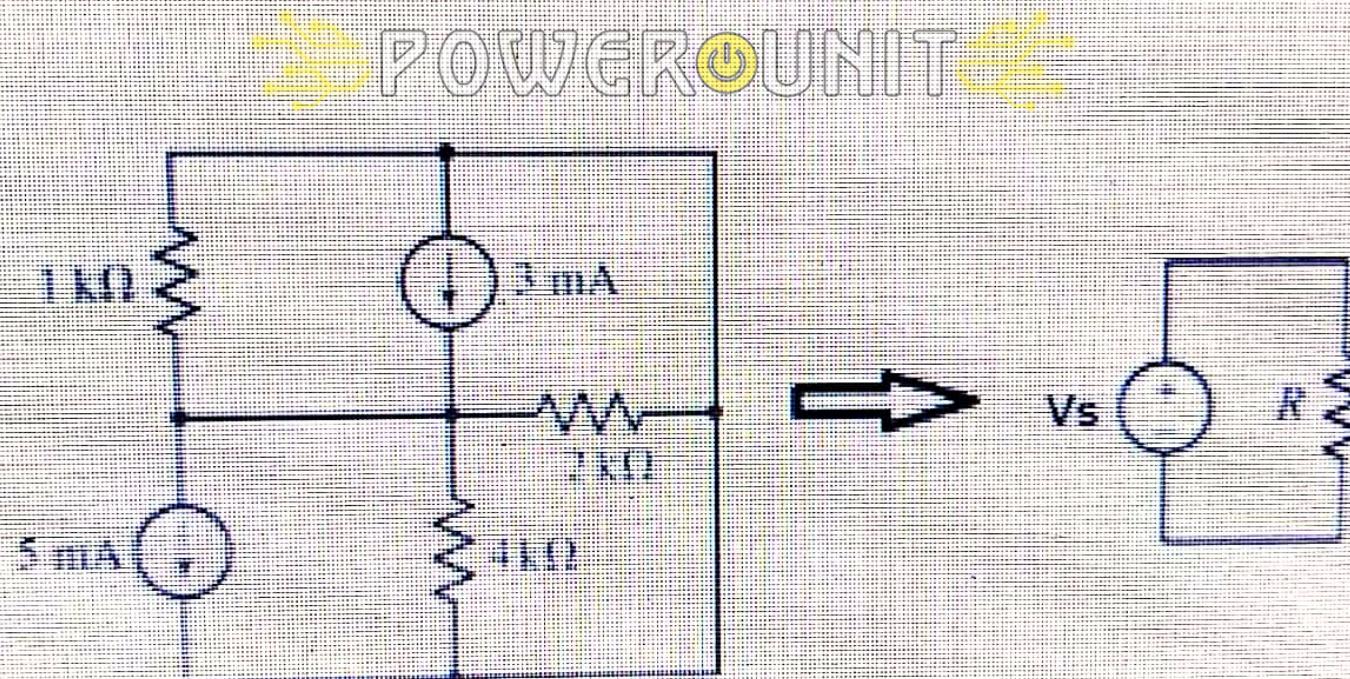
- ١) ٣٧
- ٢) ٣٩
- ٣) ٣٨
- ٤) None of the options
- ٥) ٣٦
- ٦) ٣٥

what are the values of  $V_s$  and  $R$ ?



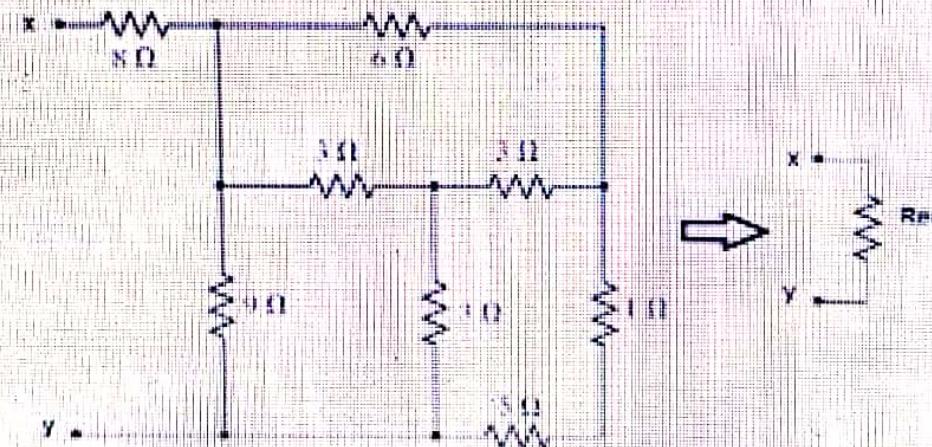
## Question 10/14 (2 p.)


What is the value of  $R_{eq}$  in the figure?



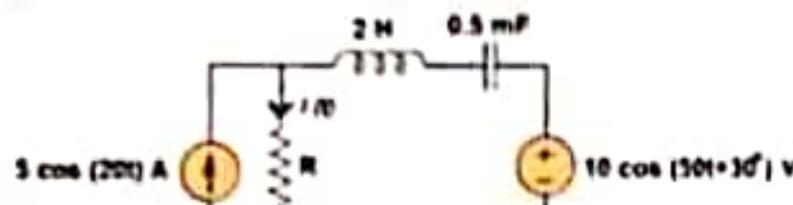Consider the circuit in the figure and find  $i(t)$  when  $R=10 \Omega$



- $i(t) = 3.841\cos(20t - 39.81^\circ) + 0.128\cos(50t - 20.19^\circ) \text{ A}$
- $i(t) = 3.841\cos(20t + 39.81^\circ) + 0.128\cos(50t + 20.19^\circ) \text{ A}$
- $i(t) = 3.841\cos(20t - 39.81^\circ) - 0.128\cos(50t - 20.19^\circ) \text{ A}$
- $i(t) = 4.932\cos(20t - 9.462^\circ) - 0.164\cos(50t - 50.54^\circ) \text{ A}$
- $i(t) = 4.932\cos(20t - 9.462^\circ) + 0.164\cos(50t - 50.54^\circ) \text{ A}$
- $i(t) = 4.932\cos(20t + 9.462^\circ) + 0.164\cos(50t + 50.54^\circ) \text{ A}$

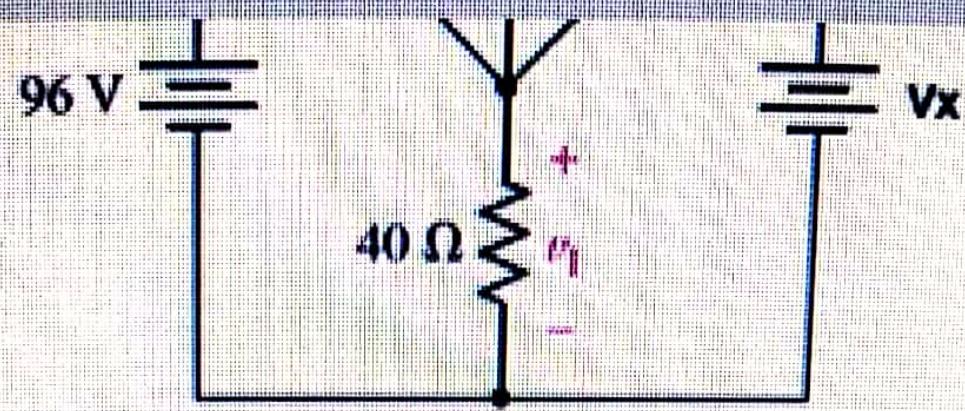

$\frac{192}{7}$


$\frac{219}{7}$

$\frac{291}{7}$

$\frac{129}{7}$


None of the choices

ANSWER

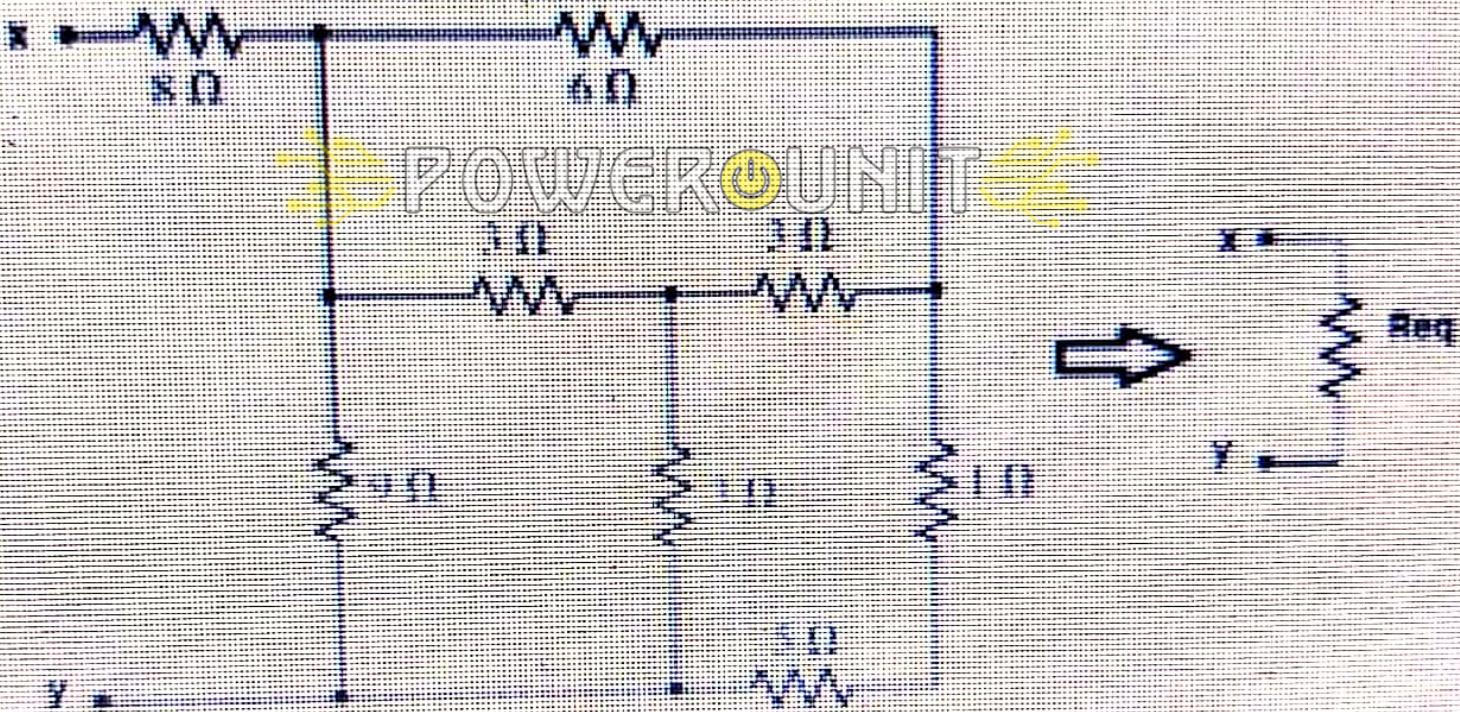

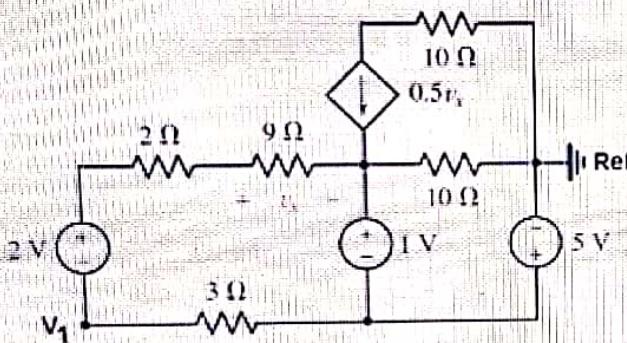
### Question 11/14 (2 p.)

Consider the circuit shown in the figure, what is the value of the voltage  $V_1$  using nodal analysis?



- $\frac{14}{67} \text{ V}$
- $\frac{-67}{14} \text{ V}$

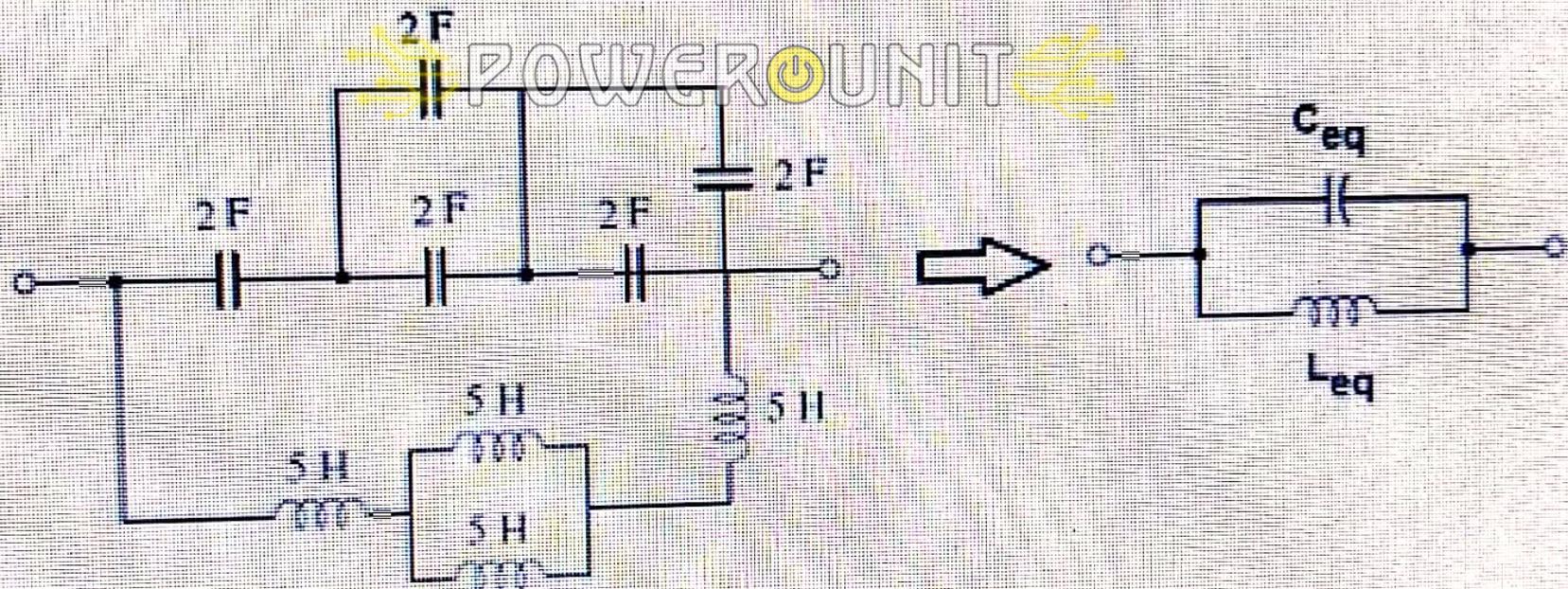
inductor, what are the values of  $C_{eq}$  and  $L_{eq}$



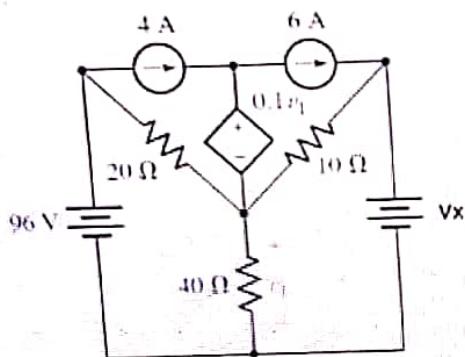
Question 12/14 (2 p.)



Consider the circuit shown in the figure. What is the contribution of the voltage source 96V only on the value of  $v_1$  ?




$\frac{192}{7}$

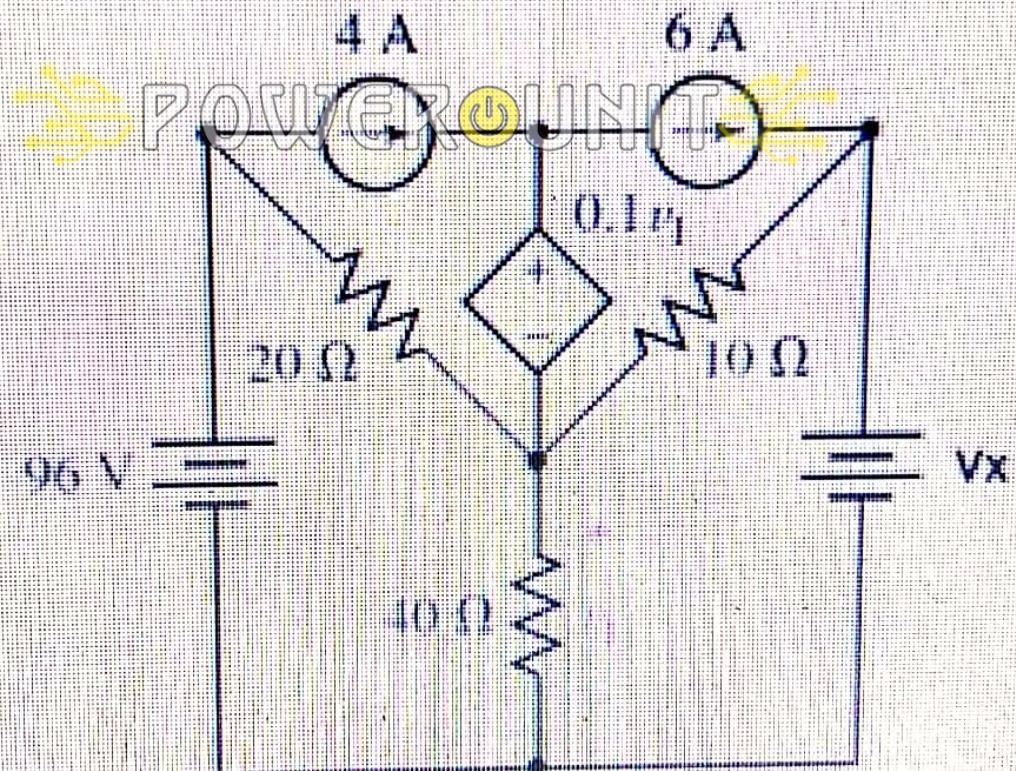

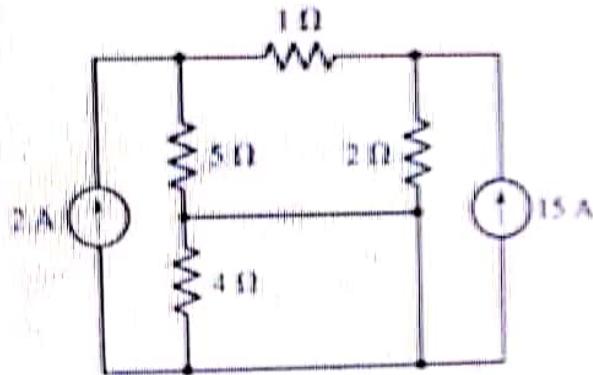
## Question 14/14 (2 p.)

Consider the circuit shown in figure, what is the power absorbed by the  $1\Omega$  resistor ?



- 62.5 W

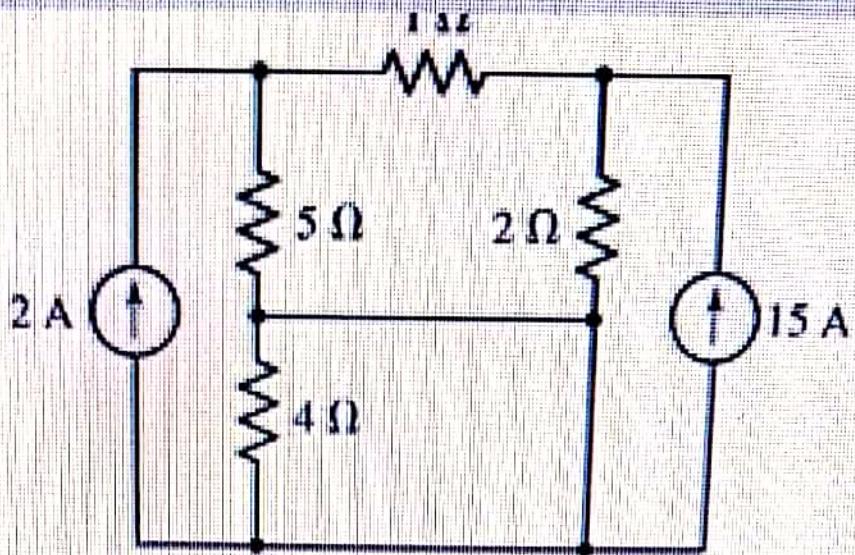


- 62.5 W
- 25 W
- None of the choices
- 60 W
- 6.25 W

POWERUNIT

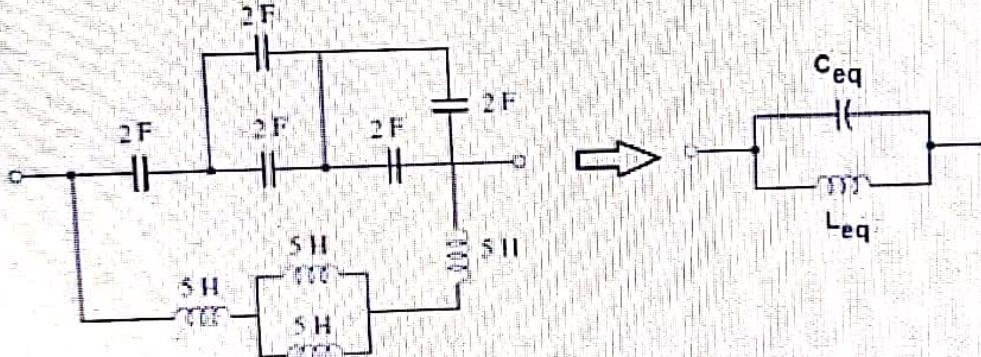
### Question 13/14 (2 p.)

Consider the circuit shown in the figure. After simplifying the circuit into one capacitor and one inductor, what are the values of  $C_{eq}$  and  $L_{eq}$




- None of the choices

Find  $I_1$  when  $R=10 \Omega$ .

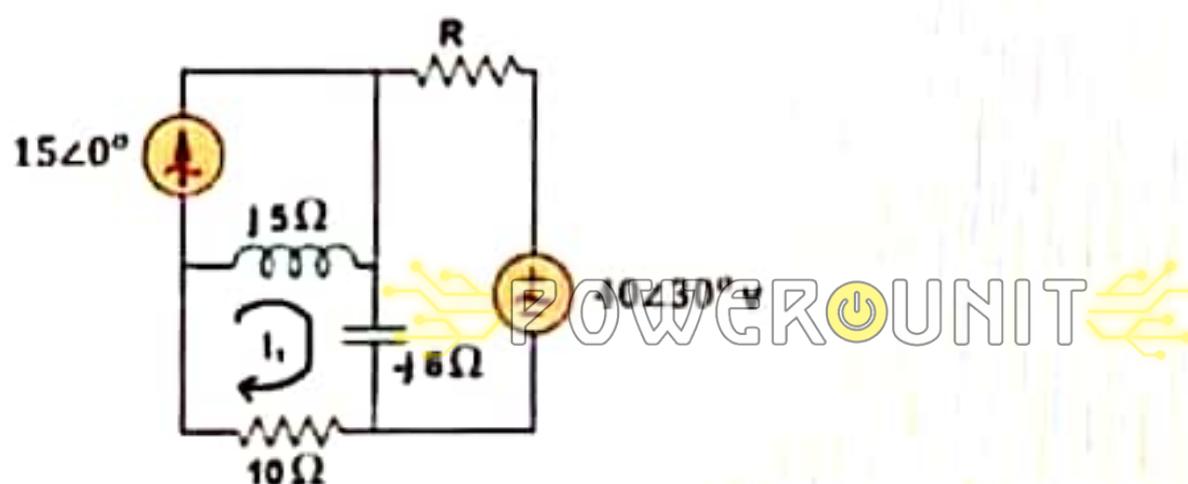

- $I_1 = 8.86\angle99.3^\circ A$
- $I_1 = 6.5\angle99.6^\circ A$
- $I_1 = 6.86\angle99.3^\circ A$
- $I_1 = 5.6\angle99.3^\circ A$

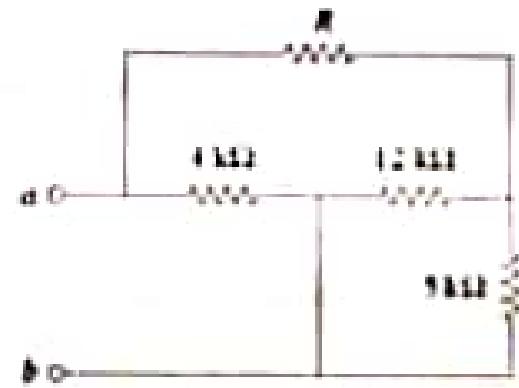If the equivalent resistor at the terminals a-b is  $2.5 \text{ k}\Omega$ . What is the value of the resistor R in the figure?



POWERUNIT

$\frac{416}{17} \text{ k}\Omega$

$\frac{50}{51} \text{ k}\Omega$


$\frac{80}{17} \text{ k}\Omega$

$\frac{208}{17} \text{ k}\Omega$

$\frac{160}{17} \text{ k}\Omega$
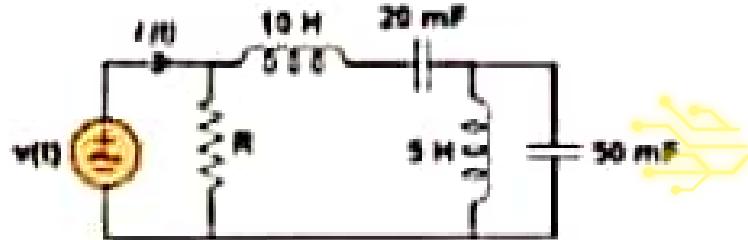
## Question 1/15 (1 p.)

Assume that  $\omega = 10 \text{ rad/s}$  and  $R = 5 \Omega$ . Which of the following statements is true?



POWERUNIT

- $i(t)$  lags  $v(t)$  by  $30.8^\circ$
- $i(t)$  lags  $v(t)$  by  $82.29^\circ$
- None of the choices
- $i(t)$  lags  $v(t)$  by  $30.8^\circ$
- $i(t)$  lags  $v(t)$  by  $28.29^\circ$



- $V_{th}=4 \text{ V}, R_{th}=1 \Omega$



- $V_{th}=2 \text{ V}, R_{th}=1 \Omega$

- $V_{th}=8 \text{ V}, R_{th}=1 \Omega$


- $V_{th}=2 \text{ V}, R_{th}=2 \Omega$

- $V_{th}=8 \text{ V}, R_{th}=8 \Omega$


SUBMIT ANSWER
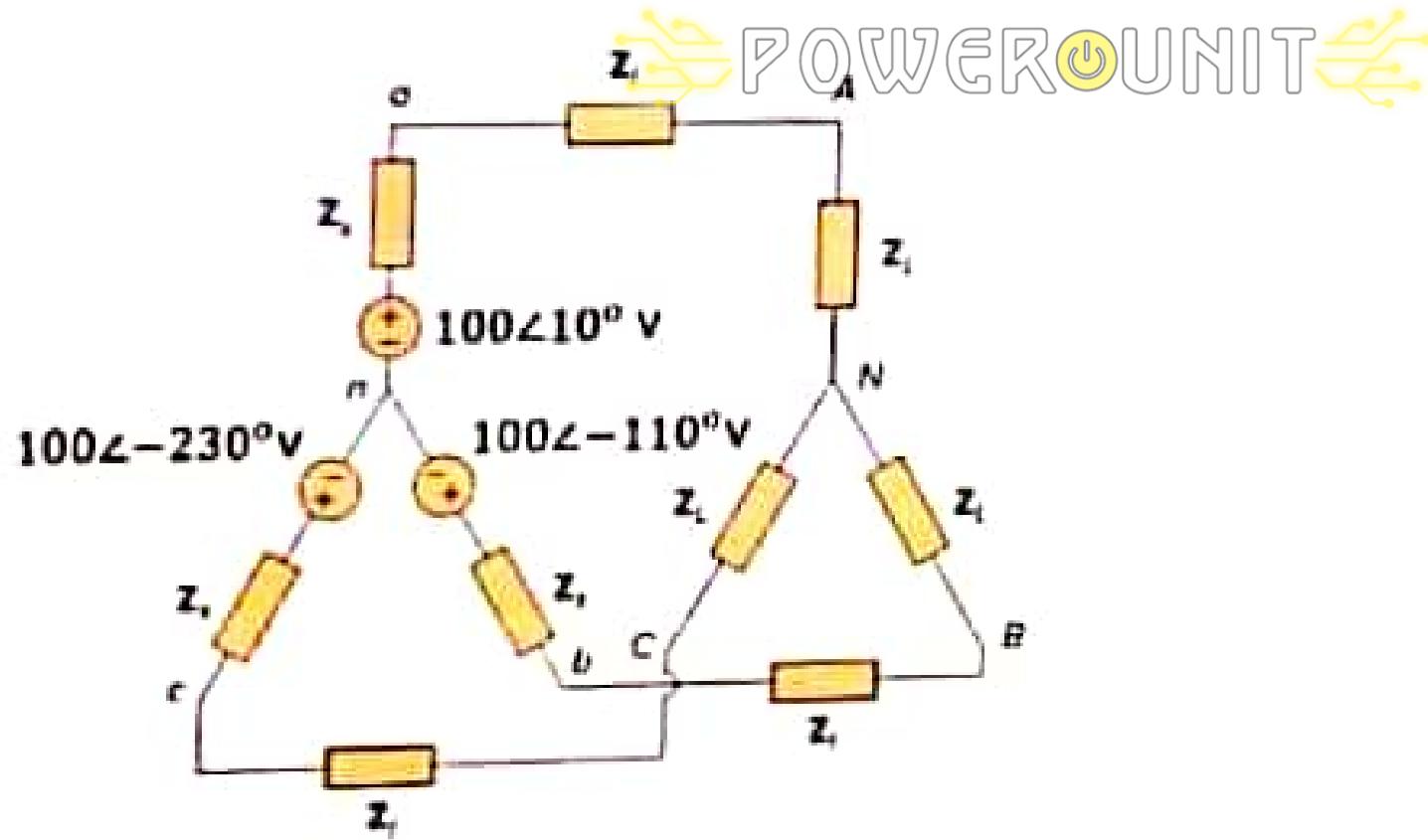
## Question 7/15 (4 p)

Find  $V_{ab}$  if  $Z_s = 10 + j6 \Omega$ ,  $Z_L = 2 - j4 \Omega$ ,  $Z_L = 5 + j2 \Omega$ .



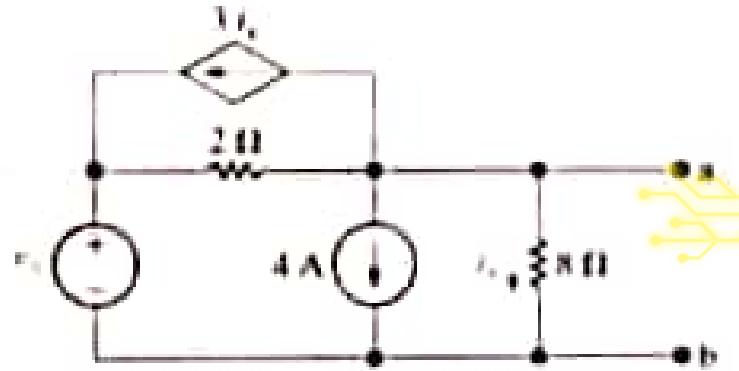Find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown. Assume  $V_b = 24V$



POWERUNIT

$V_{th}=4 \text{ V}, R_{th}=1 \Omega$

$V_{th}=2 \text{ V}, R_{th}=1 \Omega$

$V_{th}=8 \text{ V}, R_{th}=1 \Omega$


$V_{th}=2 \text{ V}, R_{th}=2 \Omega$



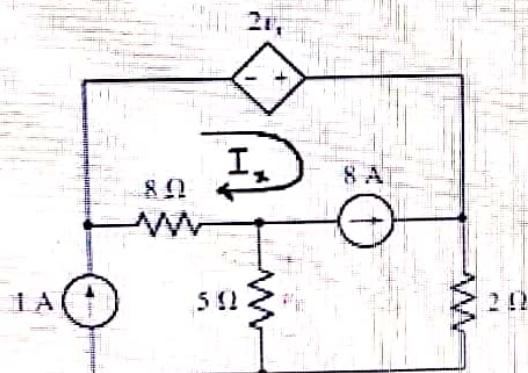
## Question 2/14 (3 p.)



Consider the circuit shown in the figure and find the value of the current  $I_x$  using mesh analysis.



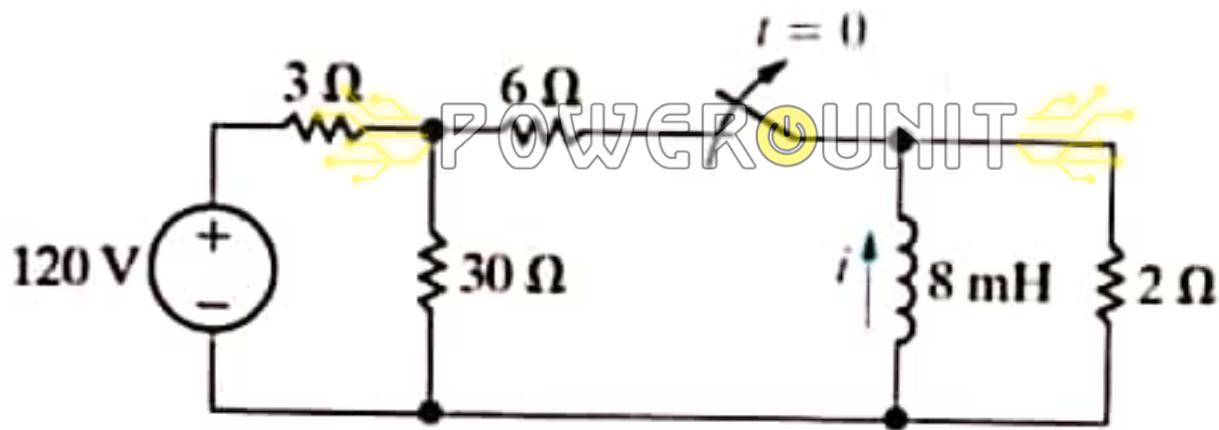Derive an expression for  $i(t)$  for  $t \geq 0$ .




$i(t) = 12.5e^{-250t} \text{ A}$

$i(t) = 12.5e^{-125t} \text{ A}$


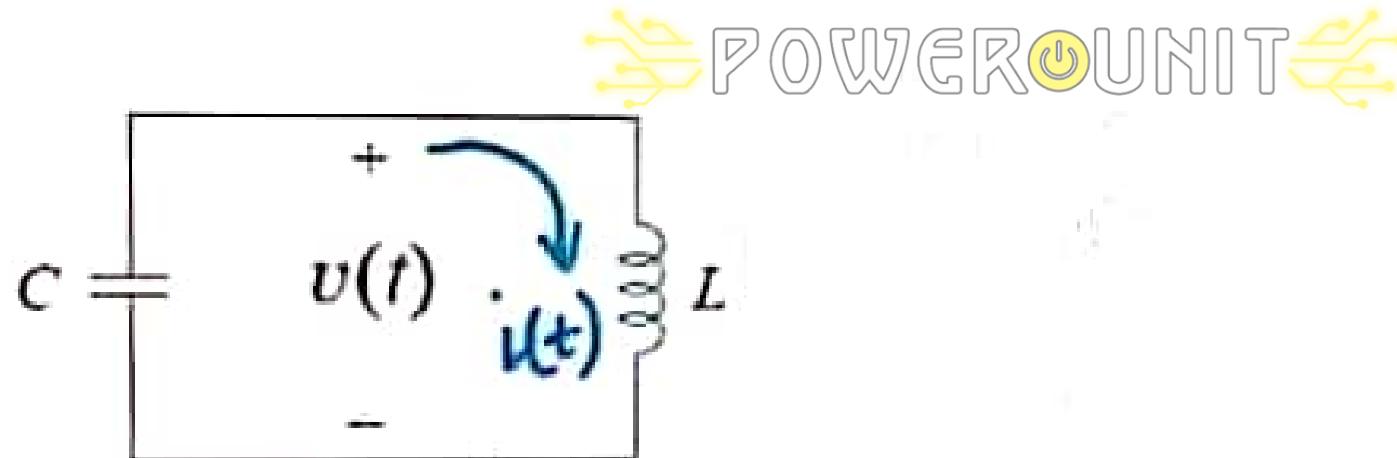
## Question 12/15 (4 p.)

Find an expression for  $v(t)$  in the circuit given that  $i(0) = 1 \text{ A}$ ,  $v(0) = 1 \text{ V}$ .




$v(t) = \cos\left(\frac{1}{\sqrt{LC}}t\right) + \frac{\sqrt{L}}{\sqrt{C}} \sin\left(\frac{1}{\sqrt{LC}}t\right) \text{ V}$

$v(t) = \cos\left(\frac{1}{\sqrt{LC}}t\right) - \frac{\sqrt{L}}{\sqrt{C}} \sin\left(\frac{1}{\sqrt{LC}}t\right) \text{ V}$
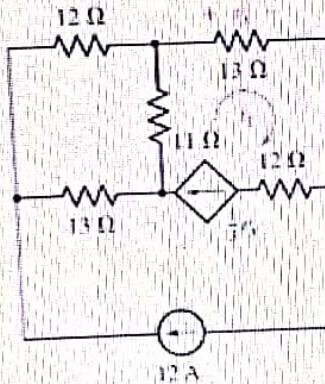
### Question 7/14 (2 p.)

What is the value of the current  $i_1$  in the circuit given below?



3.2 A


-3.8 A

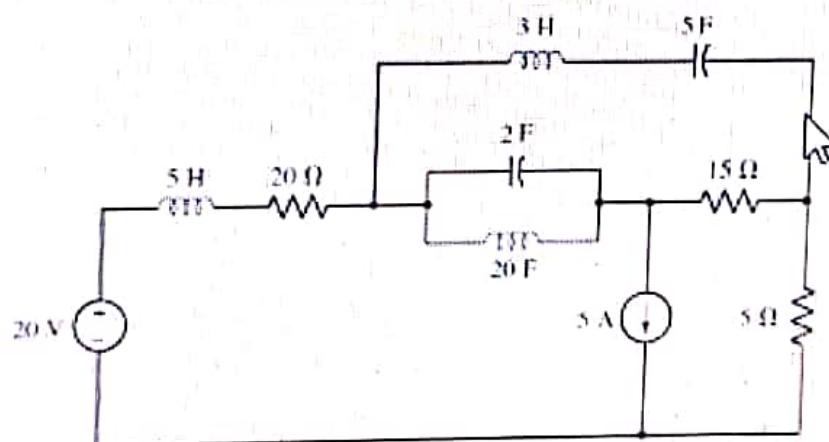**Question 5/14 (2 p.)**

What is the value of the generated power by the current source 5 A?



Assume that there is no initial stored energy in the capacitors and inductors.




- 600 W

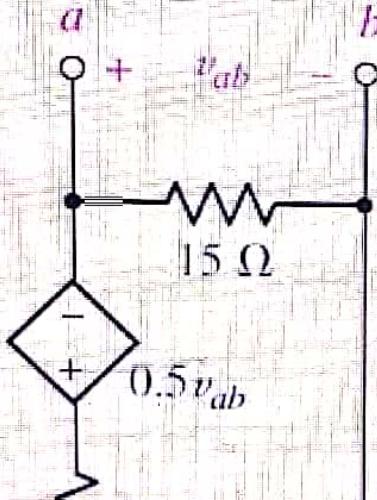Question 4/14 (3 p.)




Find the Thevenin equivalent resistance  $R_{th}$  as seen by an unspecified element connected between terminals a and b.




## Question 7/14 (2 p.)

What is the value of the current

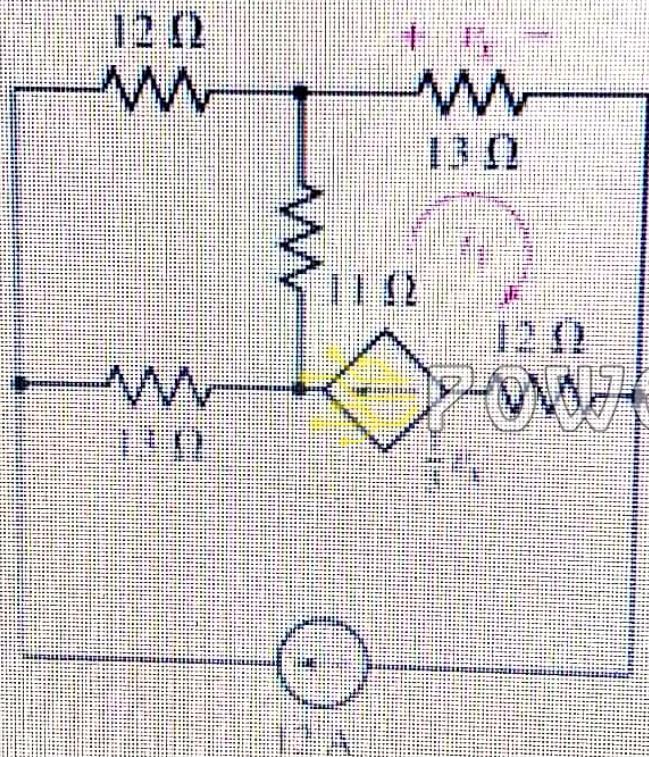

3.2 A

3.8 A

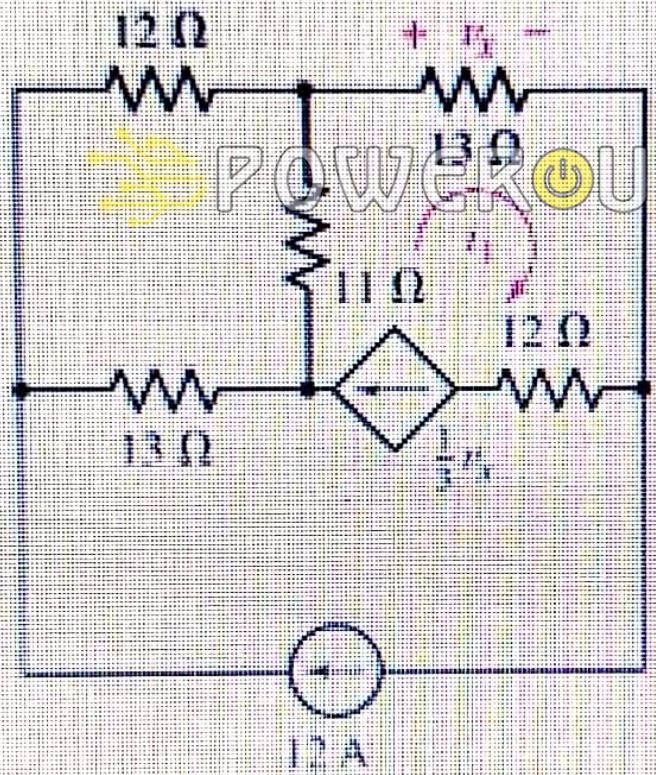

Time left to complete the test: 0 h 24 min. 32 sec.


Test name: EE213 Midterm\_II

EE213-F... ...

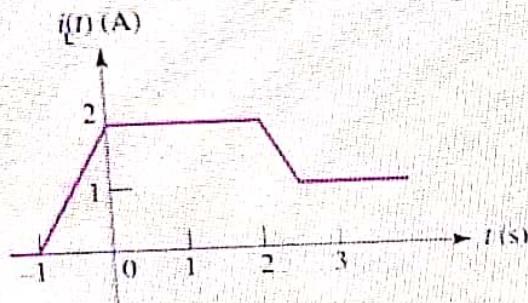Question 8/14 (2 p.)

POWERUNIT


The plot shown in the figure depicts the current through a 20 mH inductor. Find the maximum stored energy (in mJ) in the inductor given that  $I_L(t=-\infty)=0$  A.



0.4
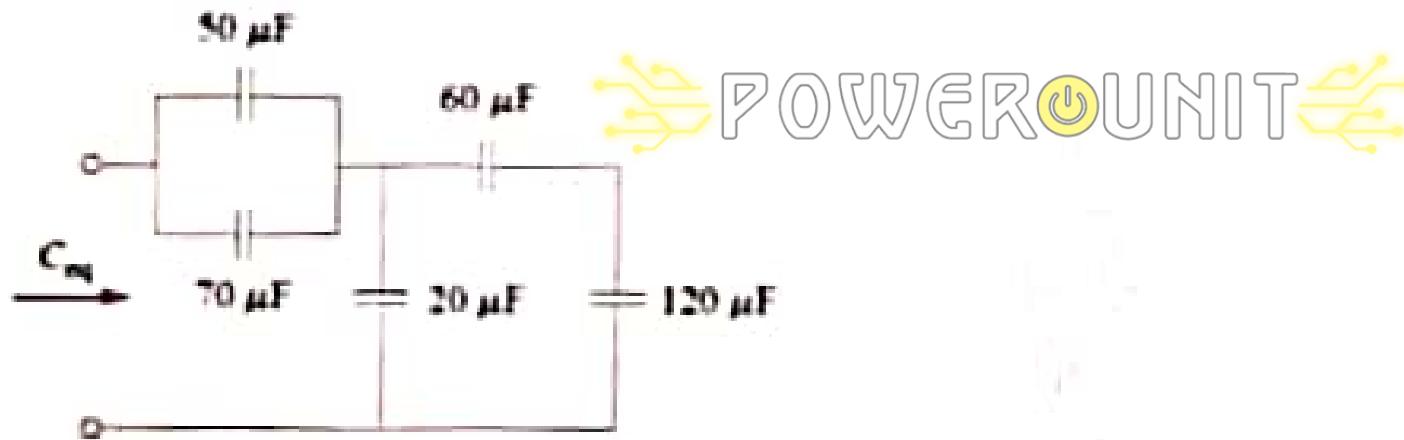
## Question 14/15 (3 p.)

Find the equivalent capacitance seen at the terminals of the circuit in the figure




$60 \mu\text{F}$

$40 \mu\text{F}$

$10 \mu\text{F}$

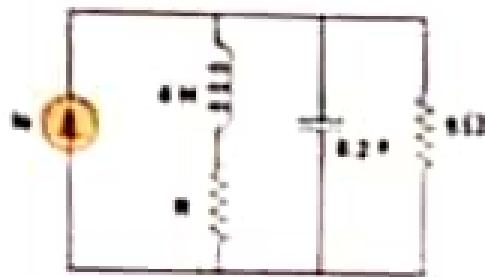Calculate the resonant frequency of the following circuit when  $R = 2 \Omega$




- 1 rad/s
- 0.25 rad/s
- 3.2 rad/s
- 0.5 rad/s
- 0.8 rad/s

SUBMIT ANSWER

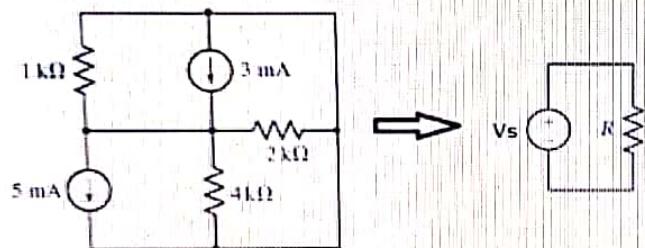
**Question 9/14 (2 p.)**

If we simplify the circuit shown in the figure into one voltage source  $V_s$  and one resistor  $R$ , then what are the values of  $V_s$  and  $R$ ?




- $V_s = -8/7$  volts,  $R = 4/7$  kΩ
- None of the choices


Q1: Find  $v_o$

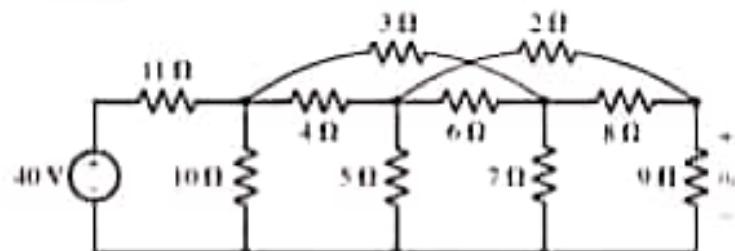

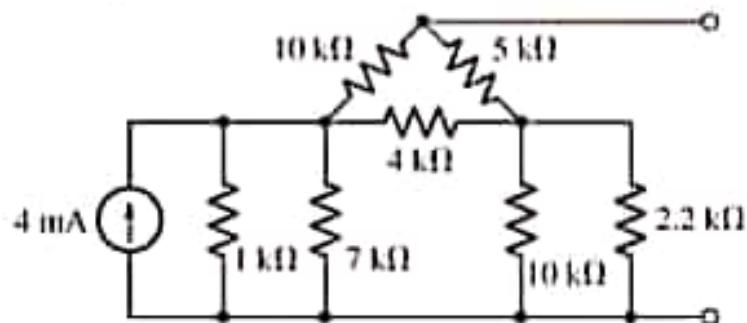
Q2: Find the value of the resistance to be connected on the open circuit terminal to absorb the maximum power and determine the value of the absorbed power.



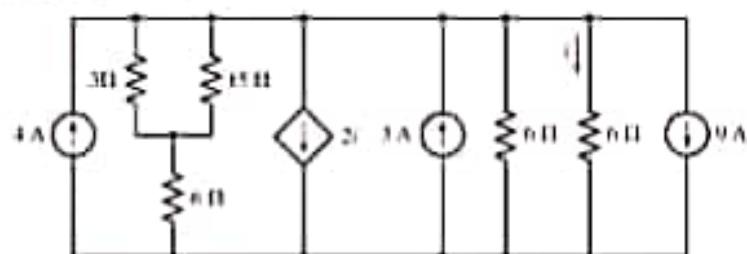Q3: Use super position technique to determine the power absorbed by the 15Ω resistor.



Q4: Draw the dual circuit

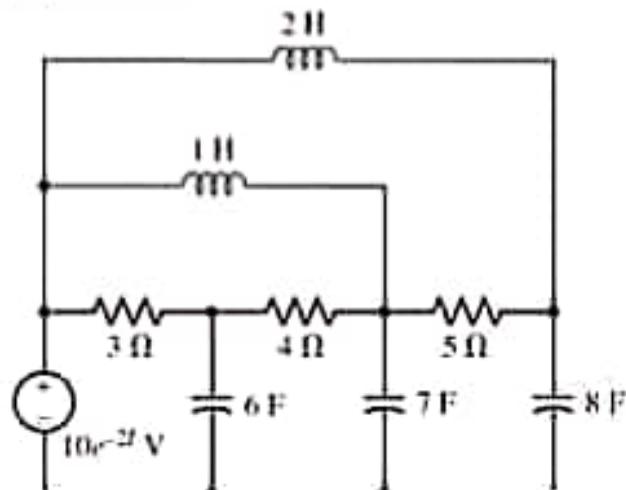



○  $i(t) = 12.5e^{-250t} \text{ A}$

○  $i(t) = 12.5e^{-125t} \text{ A}$


○  $i(t) = 12.5e^{-250t} \text{ A}$

○  $i(t) = 12.5e^{-40t} \text{ A}$

○  $i(t) = -12.5e^{-40t} \text{ A}$

SUBMIT ANSWER

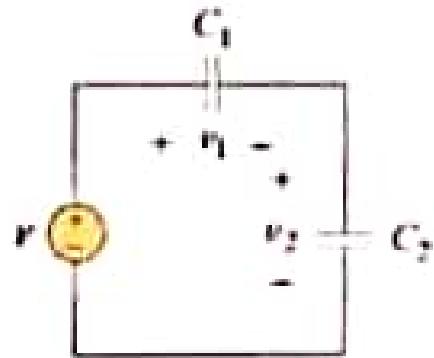Consider the circuit in the figure. Let  $C_1=5F$ ,  $C_2=4F$  and  $V=18 \cos(\omega t)$  volts. Evaluate  $v_1$ .



- $8 \cos(\omega t) V$
- $27 \cos(\omega t) V$
- $0$
- $12 \cos(\omega t) V$
- $15 \cos(\omega t) V$

11

What is a planar circuit  
(1 Point)



Enter your answer

12

Write down Ohm's law  
(1 Point)

Enter your answer

22

The value of 'Vo' due to the AC voltage source  
(3 Points)



- 2.498  $\cos(2t - 30.79^\circ)$
- 2.498  $\sin 30.79$
- 2.498  $\cos(5t - 30.79^\circ)$
- 2.498  $\sin 30.79$
- 2.498  $\cos(2t - 30.79^\circ)$
- 2.498 V
- None of these

Answer the following questions:

Assume a load is disconnected between 'a' and 'b' terminals.

5



Find the Thevenin's resistance  
(1 Point)

Enter your answer!

6

The Thevenin's voltage  
(2 Points)

17

The Thevenin impedance \*   
(3 Points)



- 4.473  $\Omega$  -7.64
- 4.473  $\Omega$  7.64
- 4.473  $\Omega$  -7.64
- None of these
- 4.473  $\Omega$  7.64



18

The Thevenin voltage \*   
(3 Points)




- 11.763±72.9 V
- None of these
- 11.763±72.9 V
- 11.763±72.9 V
- 11.763±72.9 V



Next

Q5. (15 points)

Consider Figure 4 shown

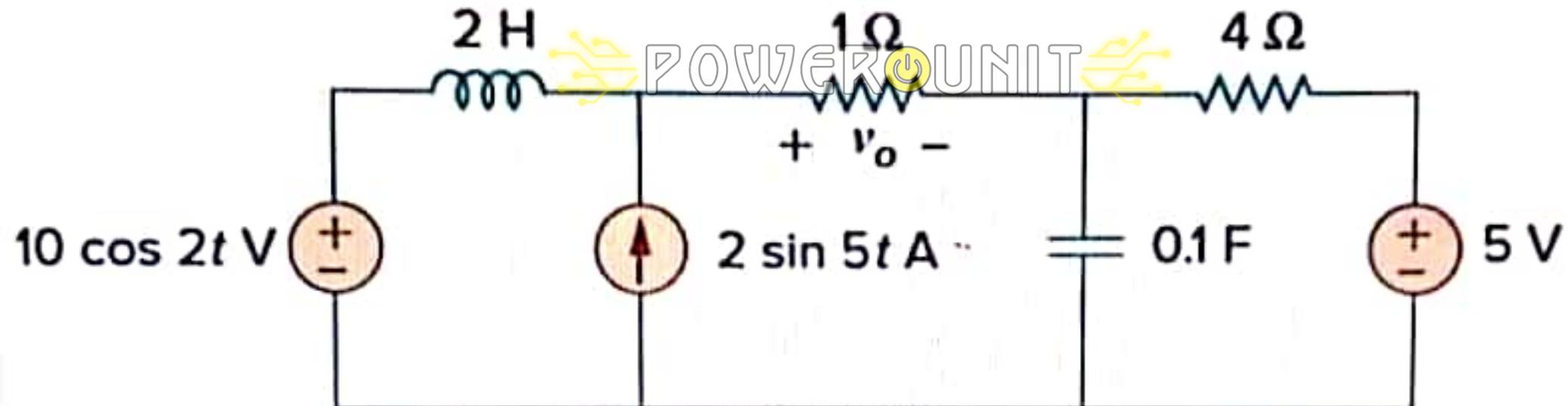

19

The proper method to analyze this circuit is [ ]  
(3 Points)

11

What is a linear circuit  
(1 Point)



Enter your answer

12

Write down Ohm's law  
(1 Point)

Enter your answer

Activate V


Go to Setting

\* Required

Linked MCQs  
Q4. (6 points)



POWERUNIT

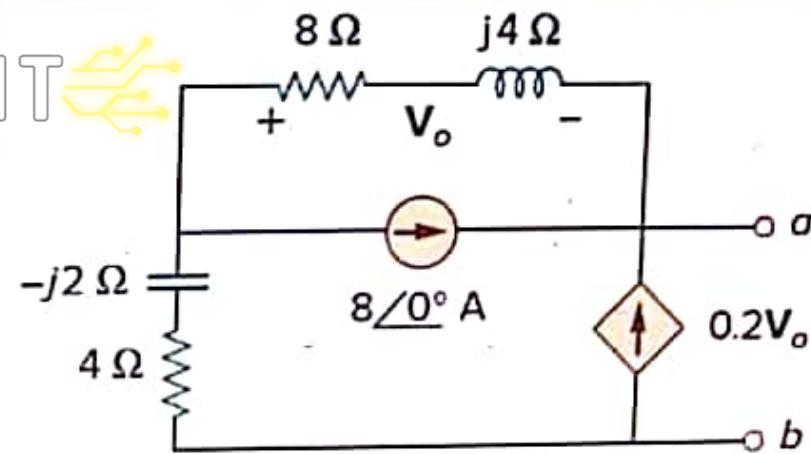

Consider Figure 3 shown

17

The Thevenin impedance \*  
(3 Points)

4


When we should assume a 1 A current source at the output terminals \*  
(2 Points)



Enter your answer

5

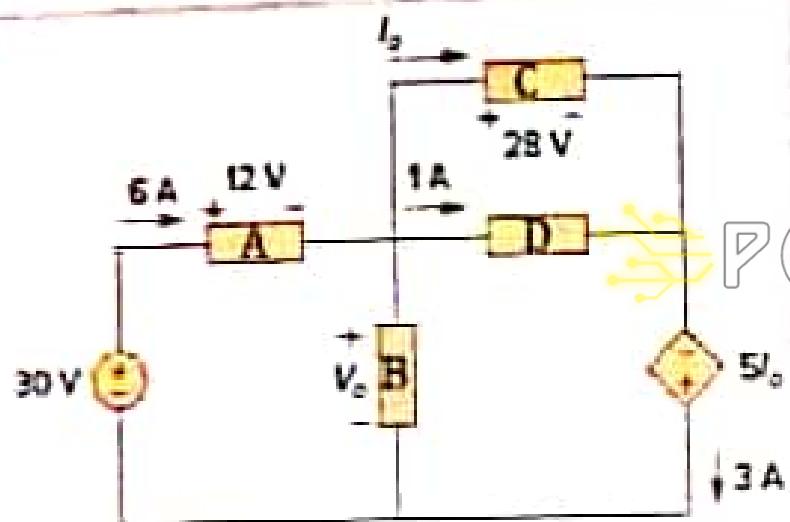What will be the shape of the inductor current in an LC circuit \*




POWER UNIT Answer the following questions

3


VO

(إجابة 1)

أدخل إجابة

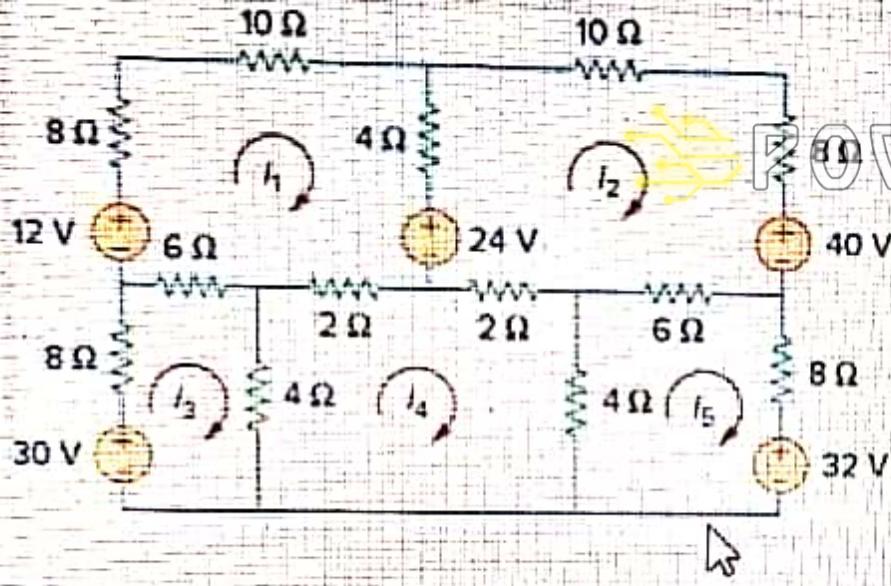

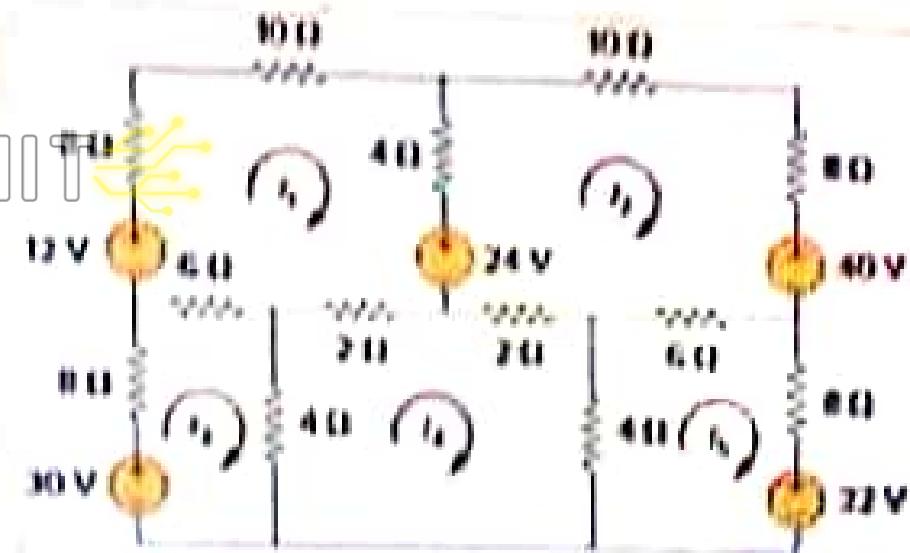□ How many nodal equations are required to find all the nodal voltages  
(نقطة ١)



How many nodal equations are required to find all the nodal voltages  
(1 Point)


21

The value of 'Vo' due to the DC voltage source   
(3 Points)



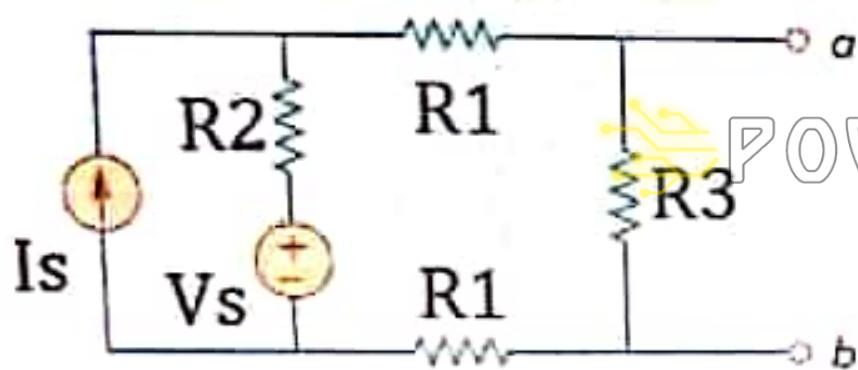- 2 V
- 1 V
- 0
- 1 V
- 5 V
- None of these





POWERUNIT

:Answer the following questions

Take:  $R_1 = 8\Omega$ ,  $R_2 = 4\Omega$ ,  $R_3 = 5\Omega$ ,  $V_s = 12V$

5

[T] Find the Norton resistance  
(ANSWER 1)

- 8*i*<sub>1</sub> - 4*i*<sub>2</sub> = 7 and -12*i*<sub>1</sub> + 3*i*<sub>2</sub> = -5
- 5*i*<sub>1</sub> + 2*i*<sub>2</sub> = 12 and -6*i*<sub>1</sub> + 7*i*<sub>2</sub> = -25




3. For the circuit shown, and based on the superposition principle, the portion of the current  $i_x$  under the effect of the 3.5 V voltage source acting alone is: \*

(2 Points)


- 0.8 A
- 0.5 A
- 3 A
- 0.14 A
- 0.9 A

3

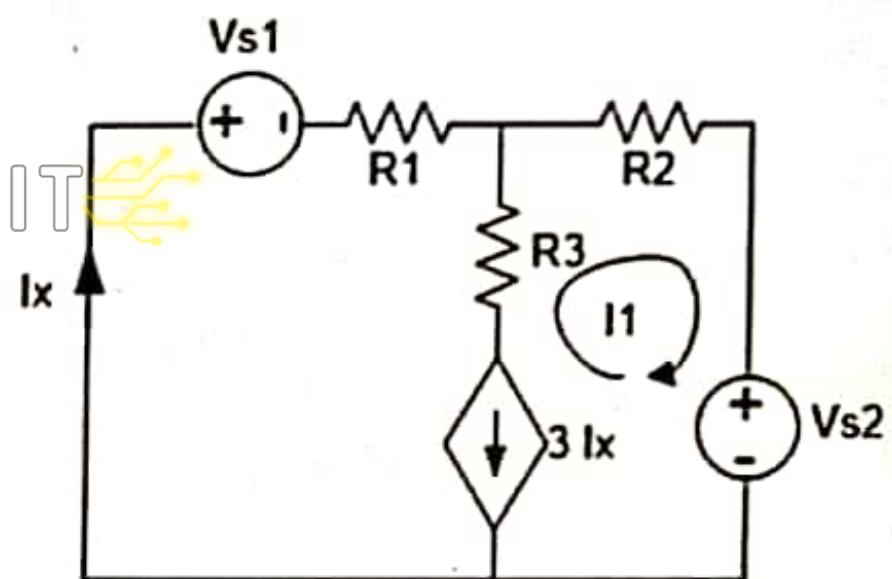 POWERUNIT

For the circuit shown in the figure, if  $R_1=1\text{ k}\Omega$ ,  $R_2 =2\text{ k}\Omega$ ,  $R_3=3\text{ k}\Omega$ ,  $V_{s1}=5\text{ V}$ ,  $V_{s2}=-11\text{ V}$ , find  $I_1$  using mesh analysis. [1]

## Section

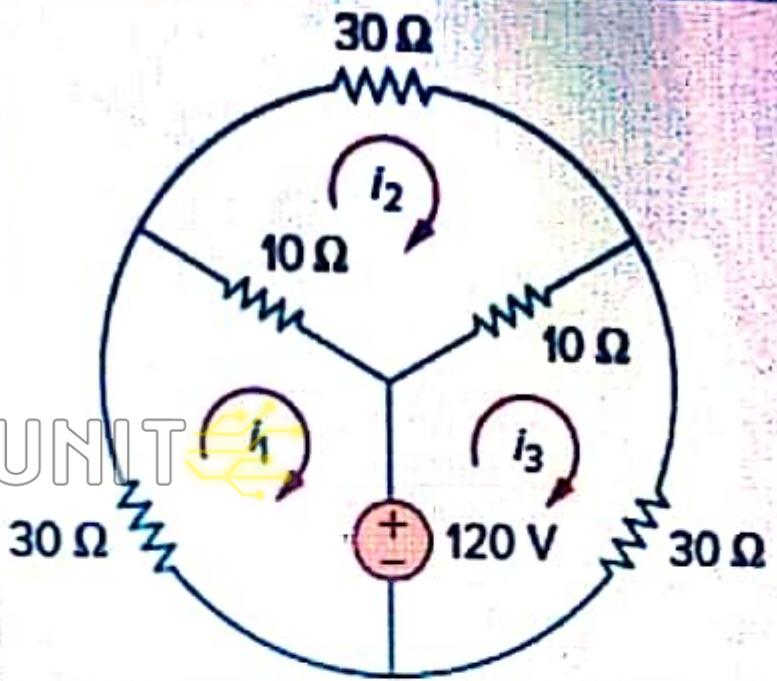

8

Write the mech currents in the simplified forms  
(3 Points)

Enter your answer

2. Find the mesh current equations for the circuit shown: \* 

(3 Points)



- $12i_1 - 2i_2 = 12 \text{ and } -2i_1 + 7i_2 = -4$
- $10i_1 + 2i_2 = 12 \text{ and } 2i_1 - 7i_2 = -14$
- $2i_1 - 12i_2 = 2 \text{ and } -7i_1 + 2i_2 = 4$
- $8i_1 - 4i_2 = 7 \text{ and } -12i_1 + 3i_2 = -5$
- $5i_1 + 2i_2 = 12 \text{ and } -6i_1 + 7i_2 = -25$

3. For the circuit shown, and based on the superposition principle, the portion of the current  $i_x$  under the effect of the 3.5 V voltage source acting alone is: \*

0.14 A

- 0.9 A

4. Using the principle of source transformation, convert the given circuit into a single node circuit with current source  $i$  (with direction from node b to node a) in parallel with resistor  $R$  and connected between nodes a and b. Find  $i$  and  $R$ ? \*   
(3 Points)

$i = -6 \text{ A}, R = 2.182 \Omega$  

$i = -2 \text{ A}, R = 2.182 \Omega$


$i = 2 \text{ A}, R = 2.182 \Omega$

$i = -2 \text{ A}, R = 1.356 \Omega$

$i = 6 \text{ A}, R = 1.356 \Omega$

5. The circuit shown has a

Answer the following questions:

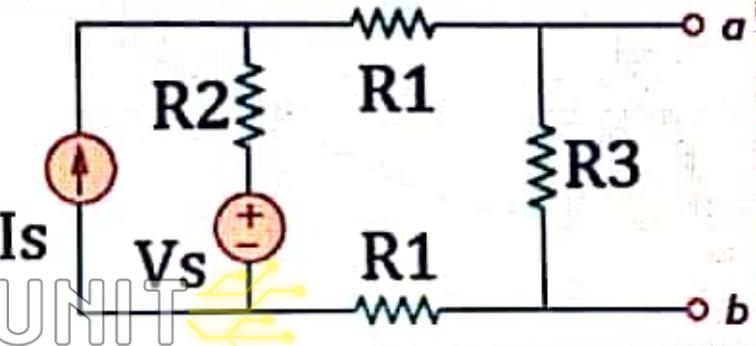

Take:  $R_1=12\Omega$ ,  $R_2=6\Omega$ ,  $R_3=15\Omega$ ,  $V_s=18V$ ,  $I_s=3A$

5

Find the Norton resistance  
(1 Point)

Enter your answer

6

The Thevenin voltage

10

How many branches are there  
(1 Point)




- 12
- 20
- 14
- 18
- None of these

Back


Next

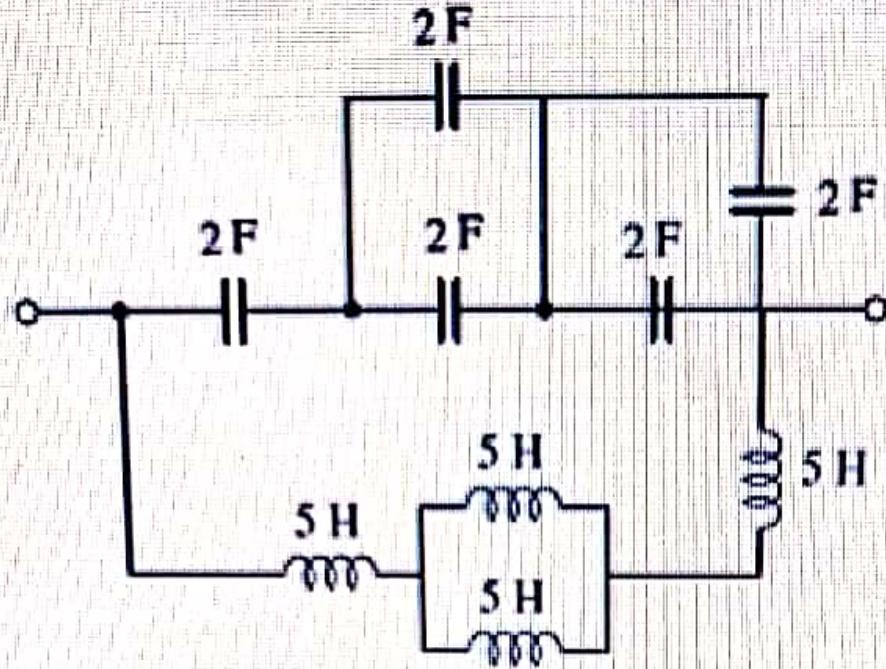ductor, what are the values of  $C_{eq}$  and  $L_{eq}$



- None of the choices
- $C_{eq}=1.75 \text{ F}, L_{eq}=0.1 \text{ H}$
- $C_{eq}=17.5 \text{ F}, L_{eq}=1 \text{ H}$
- $C_{eq}=1 \text{ F}, L_{eq}=17.5 \text{ H}$
- $C_{eq}=1.75 \text{ F}, L_{eq}=1 \text{ H}$

4

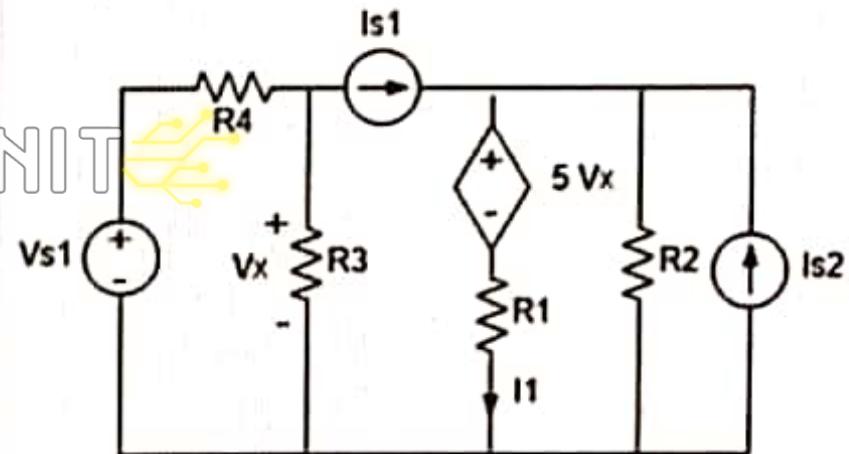

For the circuit shown in the figure if  $R_1 = 8 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ ,  $R_3 = 3 \text{ k}\Omega$ ,  $R_4 = 4 \text{ k}\Omega$ ,  $V_{s1} = 5 \text{ V}$ ,  $I_{s1} = 5 \text{ A}$ ,  $I_{s2} = 10 \text{ A}$ . Find the contribution of  $I_{s2}$  only in the value of  $I_1$ .

\* Required




Q1.

Essay Questions (11 points)

3

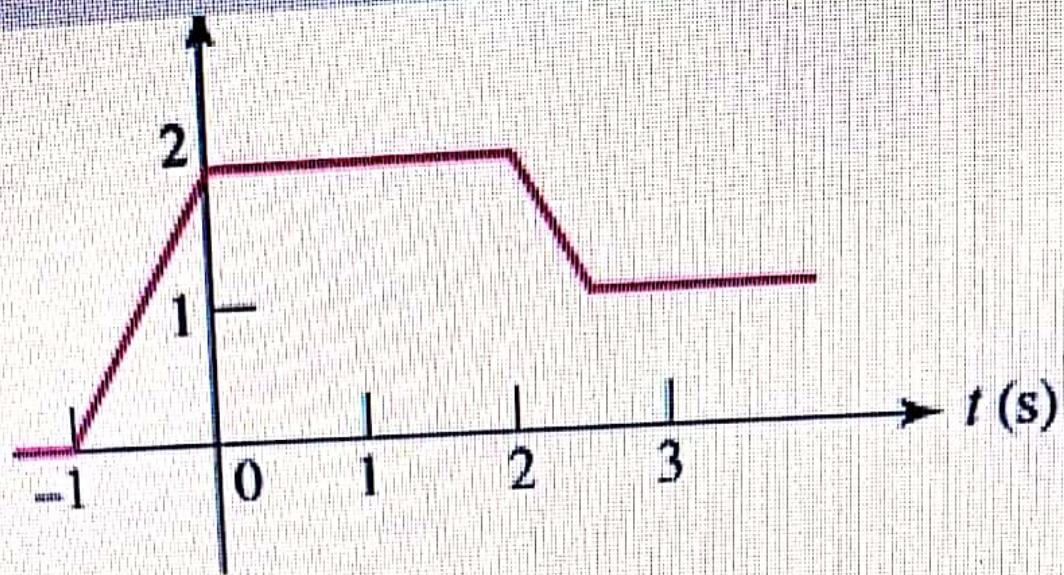What is the purpose of a phasor diagram?   
(2 Points)





0.4

400

.04

40

None of the choices



SUBMIT ANSWER

$\frac{130}{14} \Omega$

$\frac{130}{13} \Omega$


 None of the choices

$\frac{103}{13} \Omega$

$\frac{110}{13} \Omega$

---

[SUBMIT ANSWER](#)

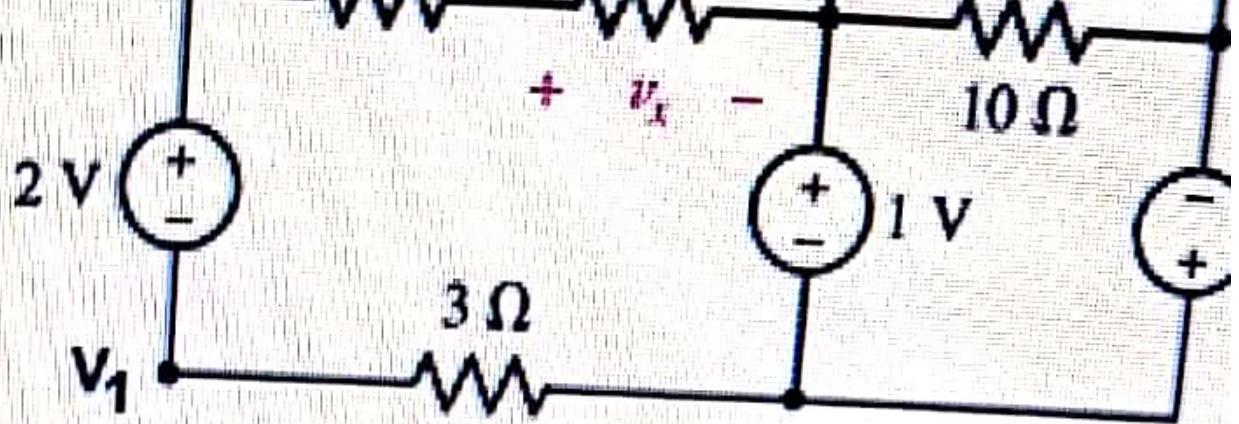

$\frac{14}{67} \text{ V}$


$\frac{-67}{14} \text{ V}$

$\frac{-14}{67} \text{ V}$

None of the choices

$\frac{67}{14} \text{ V}$

POWERUNIT

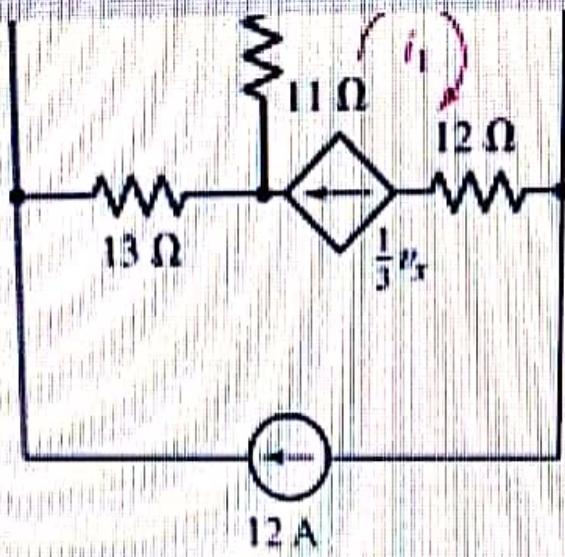

3.2 A

-3.8 A


3.8 A

-3.2 A

None of the choices

POWERUNIT


SUBMIT ANSWER

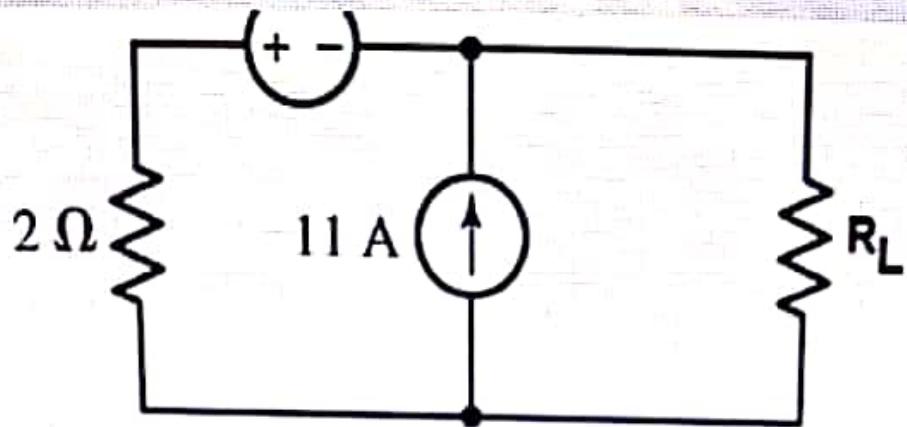

- 1 W
- 3 W
- 0 W
- None of the choices
- 2 W



SUBMIT ANSWER

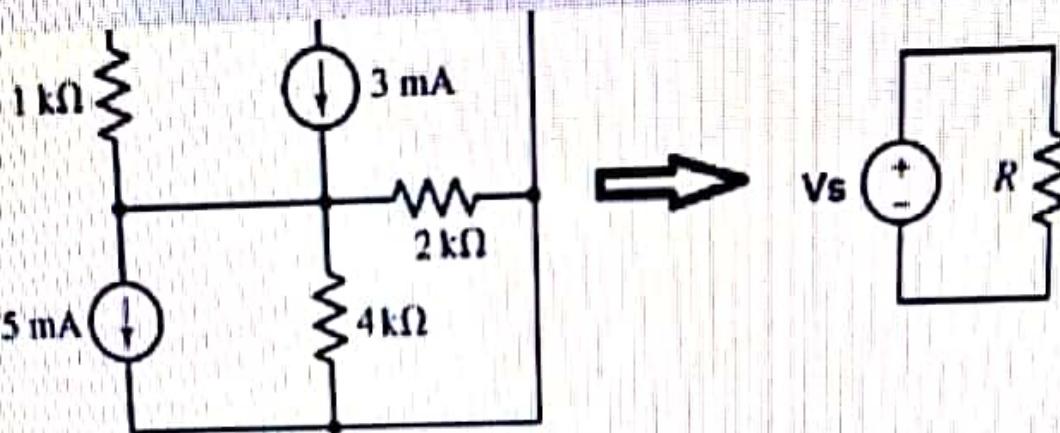

$V_s = -8/7$  volts,  $R = 4/7$  KΩ

None of the choices

$V_s = 8/7$  volts,  $R = 4/7$  KΩ


$V_s = 4/7$  volts,  $R = 8/7$  KΩ

$V_s = -4/7$  volts,  $R = 8/7$  KΩ

SUBMIT ANSWER




between terminals a and b.

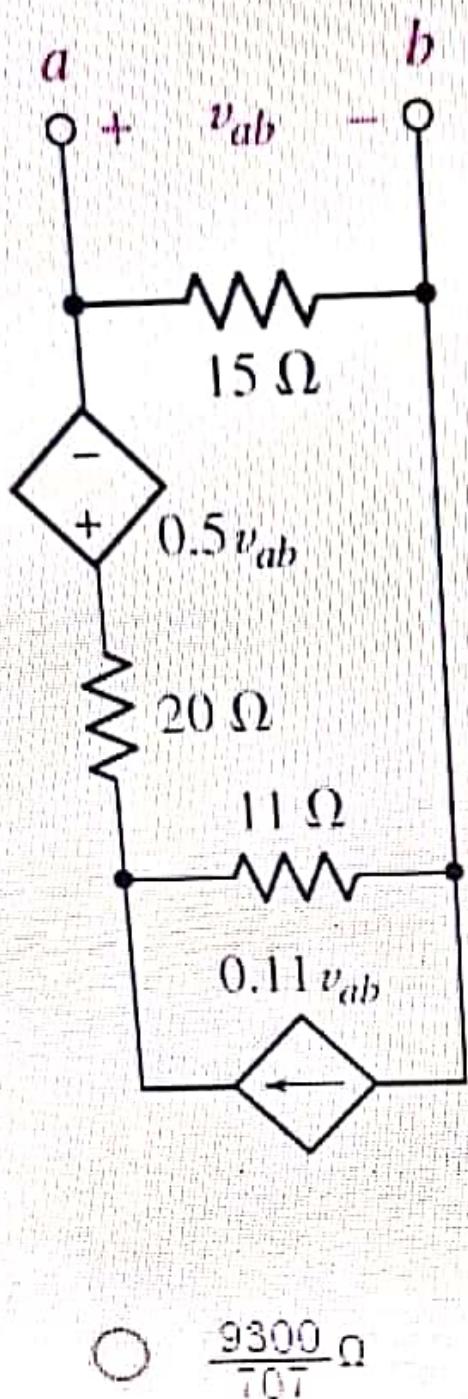


POWERUNIT
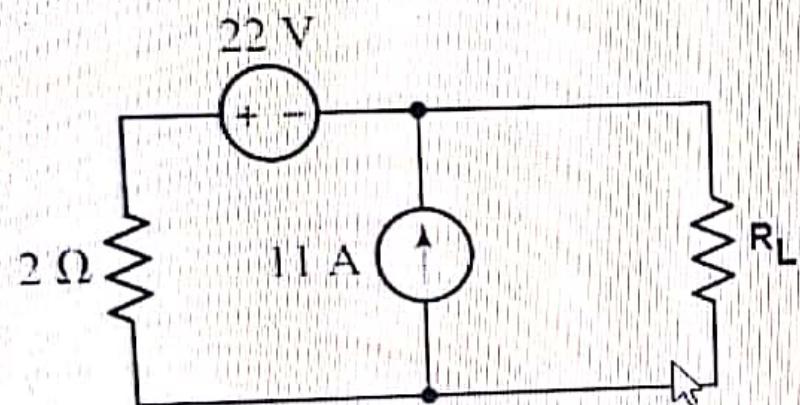
## Question 6/14 (2 p.)

Consider the circuit shown in the figure. What is the maximum power that can be absorbed by  $R_L$  from the circuit?



- 1 W

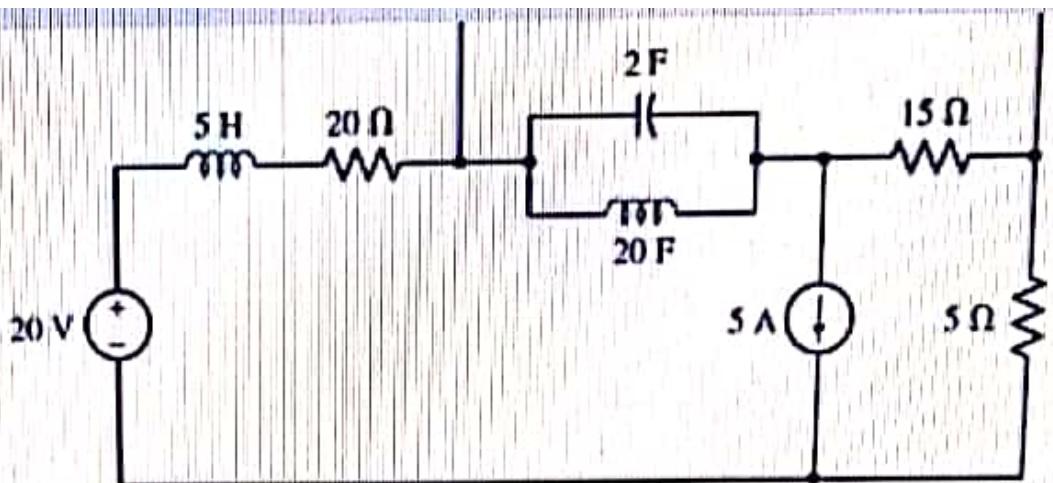

600 W

200 W

400 W

None of the choices


800 W




SUBMIT ANSWER
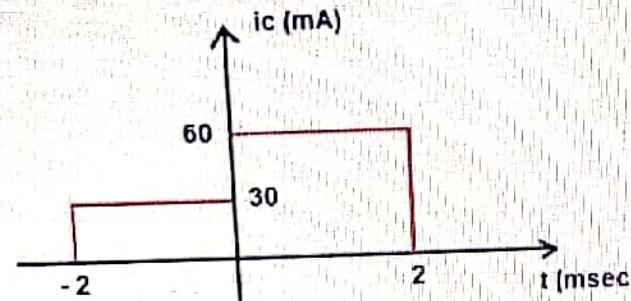
### Question 3/14 (2 p.)

The plot shown in the figure depicts the current through a  $10 \mu\text{F}$  capacitor. Find the voltage across the capacitor  $v_c(t=0)$ , given that  $v_c(t=-\infty)=0$ ,



- 3 V

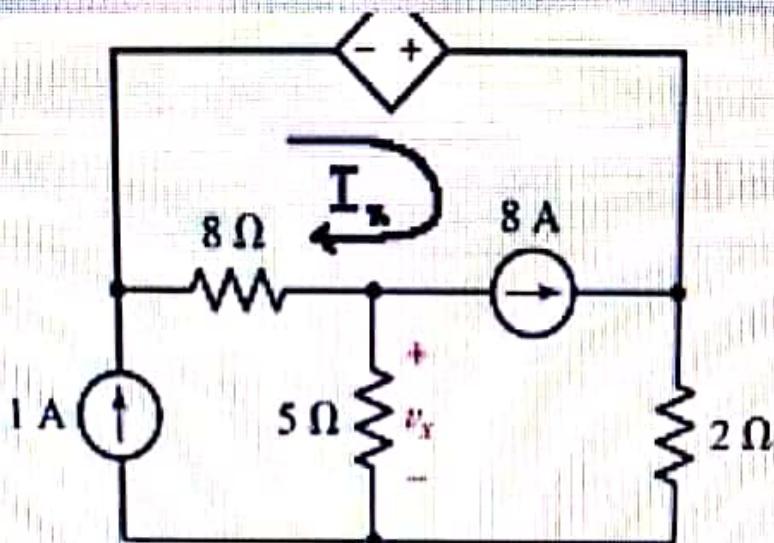

None of the choices

4.25 A


4.52 A

-4.52 A

-4.25 A




SUBMIT ANSWER

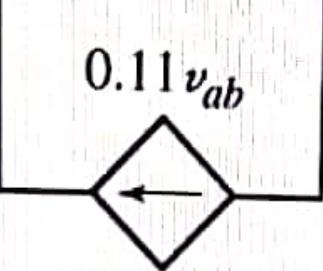

- $\frac{3009}{707} \Omega$
- $\frac{9003}{707} \Omega$
- None of the choices
- $\frac{3900}{707} \Omega$

SUBMIT ANSWER

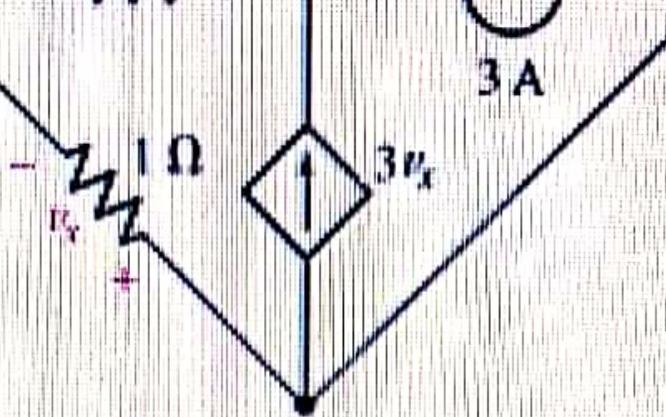


- 7/9 A
- None of the choices
- 7/9 A
- 9/7 A
- +9/7 A


POWERUNIT

SUBMIT ANSWER
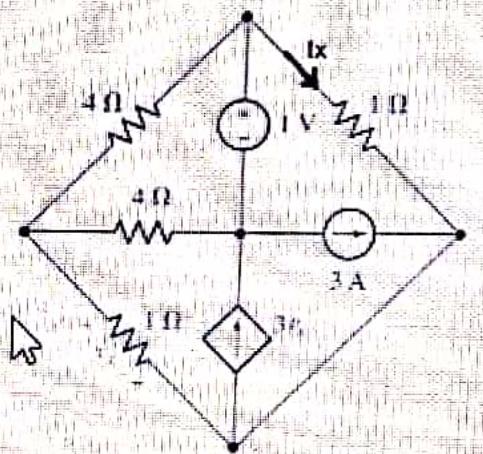
## Question 1/14 (2 p.)

Consider the circuit shown in the figure and find the contribution of the current source 3A only on the value of the current  $I_x$



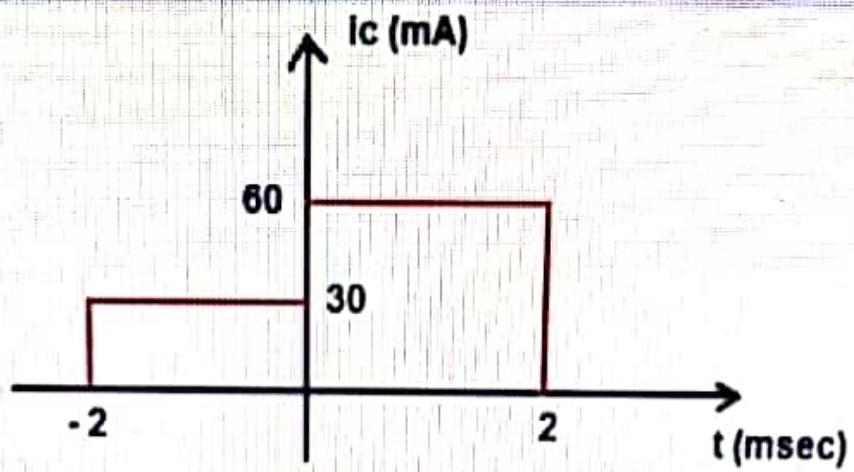


- 3 V
- 60 V
- 30 V
- 6 V
- None of the choices

SUBMIT ANSWER




Answer the following questions

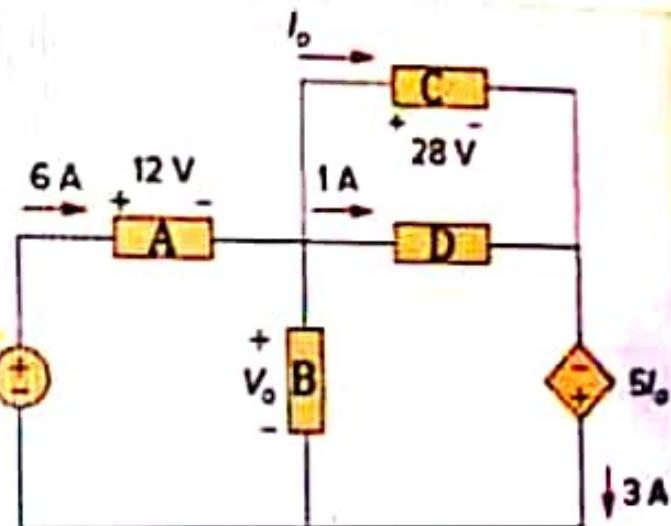

3

$I_o$   
(1 Point)

Enter your answer

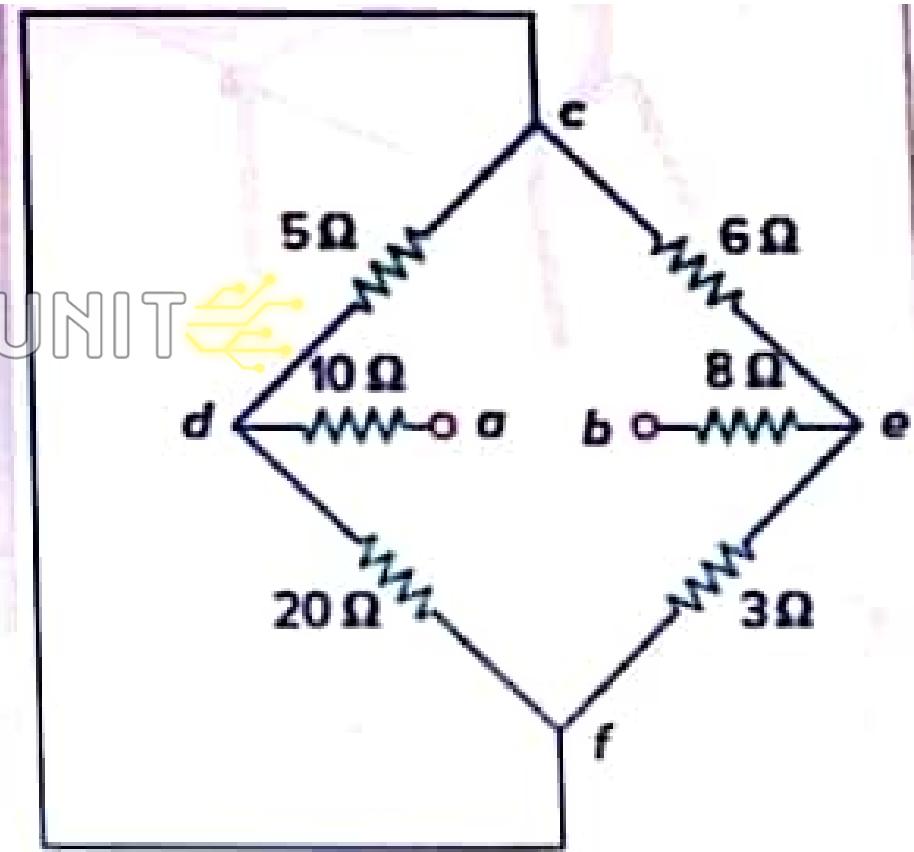

Find the equivalent resistance between 'c' and 'f' terminals  
(1 Point)

Activate Windows  
Go to Settings to activate

$$I = 6 \text{ A}, K = 1.550 \text{ S}$$

5. The circuit shown has: \*   
(2 Points)

- 4 meshes.
- 3 meshes and 1 supermesh.
- 2 meshes and 1 supermesh.
- 2 supermeshes and 1 mesh
- Cannot be determined



Submit