

Methods of Analysis:-

- ① Nodal analysis:- (with no voltage sources) (Determine nodes voltages)
- to find nodes voltages.
 - put a reference node.
 - apply kcl to every nonreference node.
 - you'll get a matrix of $= AV = b$.
 - all current sources are in parallel.
 - nothing in series.

- ② Nodal analysis with voltage source:- (Determine nodes voltages)
(using the concept of a super node)
- supernode always gives you the first equation.
 - apply kcl to super node.

→ here you may have current sources + voltage sources.

Then apply
kcl with these sources

we have no problem with V_s in series with R ← as a single node ← in parallel with resistor

- ③ Mesh analysis (voltage sources in series with other elements)

- Apply kvl to each mesh in terms of ~~V~~ (iR)
- to get n equations of $Ai = b$.

- ④ Mesh analysis with current sources.


- A super mesh requires the application of both kvl and kcl.
- be will be excluded.

- ① case:- current source in 1 mesh, we treat the mesh current as that current (take care of directions)


- ② case:- super mesh
- kvl to meshes excluding the branch of supermesh
 - kcl to a node between 2 meshes.

Delta-Wye connections &

∇ -Y conversion:-

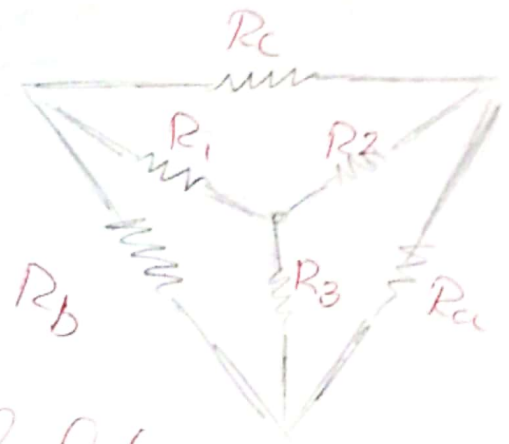

So you can find it this way:-

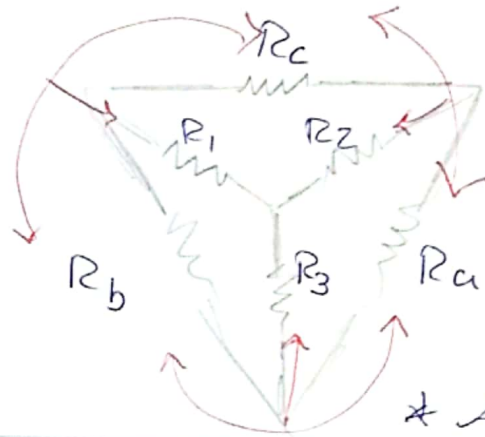

* And for a special case:-

A Balanced ∇ connection
 $R_a = R_b = R_c = R$
 So you have a balanced Y connection:-
 $R_1 = R_2 = R_3 = \frac{R}{3}$ ✓


Y- ∇ conversion:-

$$R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

→ The Trick:-

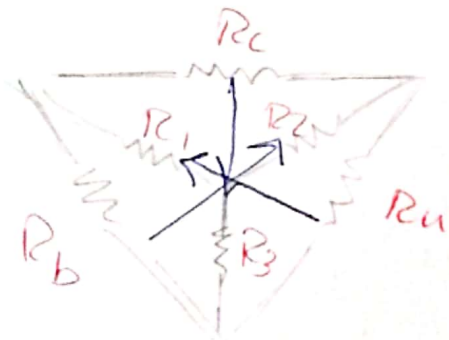

According to Ohm's law \rightarrow

$$V = \begin{cases} \rightarrow i \cdot R \text{ (through } + \rightarrow i) \text{ measured for } V \\ \rightarrow -i \cdot R \text{ (} \leftarrow - \rightarrow i) \text{ through a resistor} \end{cases}$$

$$R = \frac{V}{i} \rho$$

$\rightarrow R = \frac{\rho L}{A}$ when we are mentioning the conductor

ρ = resistivity of material.

Circuits

short $V = i \cdot R$
 $V = 0, R = 0$

\rightarrow no element assuming $R = 0$

\rightarrow we have short when there is no R connected between a and b

i is not 0 necessarily.

open

\rightarrow open terminals so it is as we have a very huge R approaching ∞

$i = 0$ in branch \rightarrow then $i = 0$

but V is not necessarily $= 0$ in this case

$$0 \leftarrow i = \frac{V}{R \rightarrow \infty}$$

The conductance $\left(\frac{1}{R} \right)$

$G = \frac{1}{R}$ → helps to simplify analysis.

Power dissipated by resistors

→ resistors will always absorb power
power is always positive in here ✓

→ remember

$$P = I \cdot V$$

but → $V = I \cdot R$

We say connected in series: sharing same i

" " " " parallel: " " v
and connected to same nodes.

Important: (1) many voltages connected in series (algebraic sum → replace)
(2) many currents " in parallel (" " → replace)

→ Revise the page of connections in the note book.

Kirchhoff's laws

(KCL)

$$\sum i_{\text{entering}} = \sum i_{\text{out}}$$

→ take care of the current source replacement.

$$\sum \frac{V}{R}_{\text{in}} = \sum \frac{V}{R}_{\text{out}}$$

(KVL)

algebraic sum of all voltages across a closed path = 0

$$\sum iR = 0$$

$$\sum U = 0 \quad \text{Identical.}$$

① Trick (signs) →

moving through (+ term) → +v

" " (- term) → -v

remember → sum of drops = sum of rises


connections:-

Series Resistors:-

→ The current stays the same for them all ✓ (all resistors)

→ ① Apply (KVL) to determine how it goes ✓ (it gives V_{eq})

→ ② $R_{eq} = R_1 + R_2 + \dots + R_n$

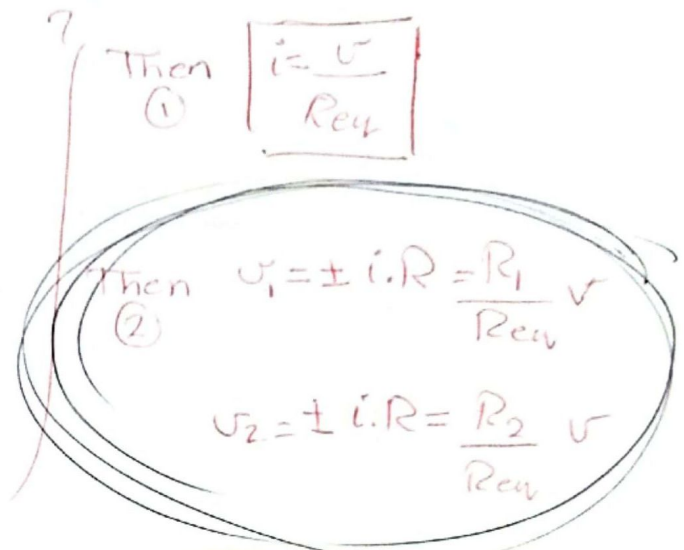

Voltage divider rule

Parallel Resistors:-

→ The voltage stays the same for them all ✓ (all resistors)

→ You can apply (KCL) to see more details.

$$\rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

$$\text{then } R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

A special case when

N=2:-

$$\rightarrow R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

? Using Conductance:-

$$G_k = \frac{1}{R_k} \rightarrow G_{eq} = \frac{1}{R_{eq}}$$

$$G_{eq} = G_1 + G_2 + \dots + G_n$$

Then we substitute that:-

$$i_k = \frac{\frac{1}{R_k} \cdot i}{\frac{1}{R_{eq}}} = \frac{G_k \cdot i}{G_{eq}}$$

↓
For a
branch

The current divider rule

A special case when $N=2$:-

$$i_1 = \frac{R_2}{R_1 + R_2} \cdot i$$

$$i_2 = \frac{R_1}{R_1 + R_2} \cdot i$$

So:-


i_1 is $\propto \frac{1}{R_1}$ and $\propto R_2$

i_2 is $\propto \frac{1}{R_2}$ and $\propto R_1$.

→ See the open and short circuits in the note book ✓

* Chapter 4:

4.2: Linearity Property

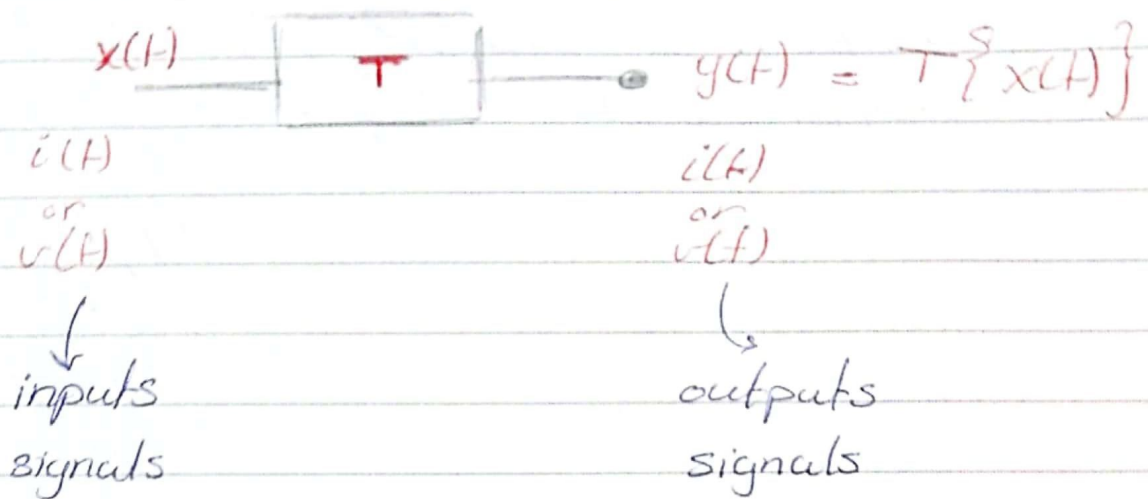

$$\left. T\{\alpha_1 x_1(t) + \alpha_2 x_2(t)\} = \alpha_1 T\{x_1(t)\} + \alpha_2 T\{x_2(t)\} \right\}$$

~~if~~

To be a linear system this should be applied

المدخلات input لا يجب ان تكون خطية، بل يجب ان تكون خطية

When $y(t) = \beta x(t) + \phi$, it's not gonna be linear because of ϕ , it's gonna give a linear equation but not leading to a linear system

Superposition principle

→ to kill a voltage source, replace it with a short circuit.

→ to kill a ~~voltage~~ current source, replace with an open circuit.

Dependent sources are left, because they are controlled by independent ones.

Source Transformation:-

voltage source
in series
with R

current source
in parallel
with R

→ source

$$i_{sc} = \frac{V_s}{R}$$

→ source

$$i_s = i_{sc}$$

$$V_s = i_s R$$

$$i_s = \frac{V_s}{R}$$



same for independent sources

But imagine

→ voltage source presence:-

open circuit

short circuit

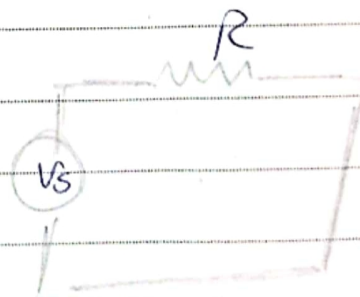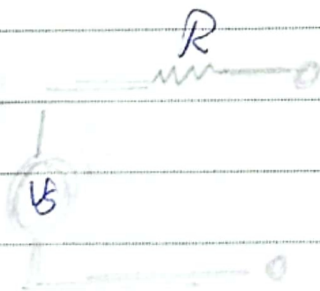

$$i = 0$$

$$V_{op} = V_s$$


$$V_{sh} = V_s$$

$$i_{sh} = \frac{V_s}{R}$$

current source presence :-


open circuit :-

short circuit :-

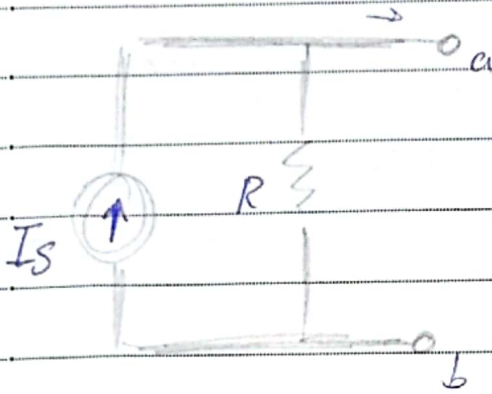

$$I_s = \frac{V_s}{R}$$
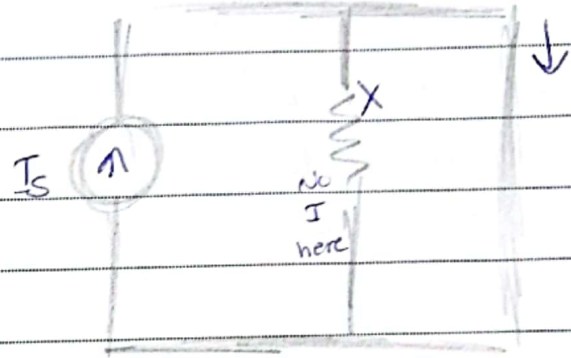
$$V_{op} = I_s \cdot R \\ = \frac{V_s \cdot R}{R} = V_s$$



$$I_{sh} = I_s \\ = \frac{V_s}{R}$$

$$V_{sh} = V_s$$

4.5 Thevenin Theorem

① Case ① No independent sources

case ② No independent source

→ disconnect load

you'll have a circuit with open terminals (a,b)

→ kill all sources (independent)

* → find R_{th}

→ find V_{th}

→ get back the linear circuit without killing any source

~~$V_{ab} = V_{open} = V_{th}$~~

$$V_{ab} = V_{open} = V_{th}$$

For Norton theorem :-

$$\rightarrow i_{ab} = i_{sh} = I_N$$

$$R_N = R_{th}$$

Chapter 6 summarization:-

§ 6.2 : capacitors

Basic

→ How to find capacitance:-

$$C = \frac{q}{V} \quad \text{or} \quad C = \frac{\epsilon d}{A} \quad \begin{array}{l} \text{(A of one plate)} \\ \text{(q " " " ")} \end{array}$$

C is measured in Farad = 1 coulomb / volt.

① i through a capacitor:-

$$i = \frac{C dv}{dt} \rightarrow \text{you'll find } i(t) / \text{function of } t \text{ until they give you } t$$

② $v(t)$ of capacitor:-

$$v(t) = \frac{1}{C} \int_{t_0}^+ i(\tau) d\tau + v(t_0)$$

[Power and Energy:-

* Power

$$\rightarrow p(t) = i(t) \cdot v(t)$$

$$p(t) = C \frac{dv(t)}{dt} \cdot v(t)$$

* Energy stored in capacitor:

$$\rightarrow w = \frac{1}{2} C v^2$$

convert using $C = \frac{q}{V}$

$$\rightarrow \text{or } w = \frac{1}{2} \frac{q^2}{C}$$

→ Series and parallel capacitors:

~~Parallel resistors~~

→ Parallel capacitors:

$$C_{eq} = C_1 + C_2 + C_3 + C_4$$

→ they share same voltage:

→ charge is distributed.

→ Series capacitors:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4}$$

→ They share same q

→ voltage is distributed.

special

for $N=2$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} \quad \equiv \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

Inductors:-

Basics:-

$$\rightarrow \text{Inductance: } L = \frac{N^2 \mu A}{\ell}$$

$$\rightarrow \text{voltage: } v = L \frac{di}{dt}$$

$$\rightarrow \text{current } i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

for special case:

$$t_0 = -\infty \rightarrow i(t_0) = 0$$

$$\text{Then } i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt$$

power and energy:-

$$\rightarrow P = v i = \left(L \frac{di}{dt} \right) i$$

$$\rightarrow W = \frac{1}{2} L i^2$$

Chapter 7:-

first order circuits:-

→ First order differential equation.

RC: circuit of RC and $||$

RL: " " RL and $||$

→ form of 1st ODE:

$$\frac{dy(x)}{dx} + p(x)y(x) = r(x)$$

or $y' + p(x)y = r(x)$

2 types of ODE

Homo

$$y' + p(x)y = 0$$

Non-Homo

$$y' + p(x)y = r(x)$$

r : external force
from heating

v source or
 i source.

§ Source Free RC circuits

of 1st order Homo ODE.

① $v(0) = V_0$ (Both)

② $w_c(0) = \frac{1}{2} C V_0^2$ (capacitor)

③ $v(t) = V_0 e^{-t/RC} = V_0 e^{-t/\tau}$ (Both) ($t \geq 0$)

④ $\tau = RC$ (General)

τ is the time required for the response to decay to a factor of $1/e$ or 36.8% of its initial value

⑤ power dissipated by the resistor

$$p(t) = \frac{V_0^2}{R} e^{-2t/\tau}$$

⑥ energy absorbed by the resistor

$$w = \frac{1}{2} C V_0^2 (1 - e^{-2t/\tau})$$

⑦ $i(t) = \frac{V_0}{R} e^{-t/\tau}$ (Bot)

Steps to Analyze RC circuits:-

① find $v(0) = v_0$

② find $\tau = RC$

③ find $v(t) = v_0 e^{-t/\tau}$

→ Beid line:- Working with switches
while analyzing.



: switch is opened at $t=0$



: " " closed at $t=0$

pay attention:-

$t < 0$, استقرت على v_0

$t > 0$, $i(t)$, $v(t)$ استقرت

The principle is very easy:

→ you should find $V_c(0)$, then if you are given $V_c(0)$, simplify the circuit into a single loop (Free RC), and assume DC conditions.

→ if you have switches:

→ find $V_c(0)$, by assuming that the circuit before closing or opening the switch has been operating for a very long time, and now we are under the DC condition so we can treat $\frac{1}{T}$ as an open circuit.

→ once you find so this is $V_c(0)$

→ consider the case of $t > 0$

remove the switches, then you end up with RC