



.Fill in the blanks in the below modules

```
;module ShiftLeftBy2 (out, in)
```

```
    ;input [1:0] in
```

```
    ;output [3:0] out
```

```
    ;  = assign #4 out
```

```
endmodule
```


```
;module ShiftRightBy2 (out, in)
```

```
    ;input [3:0] in
```

```
    ;output [3:0] out
```

```
    ;  = assign #4 out
```

```
endmodule
```

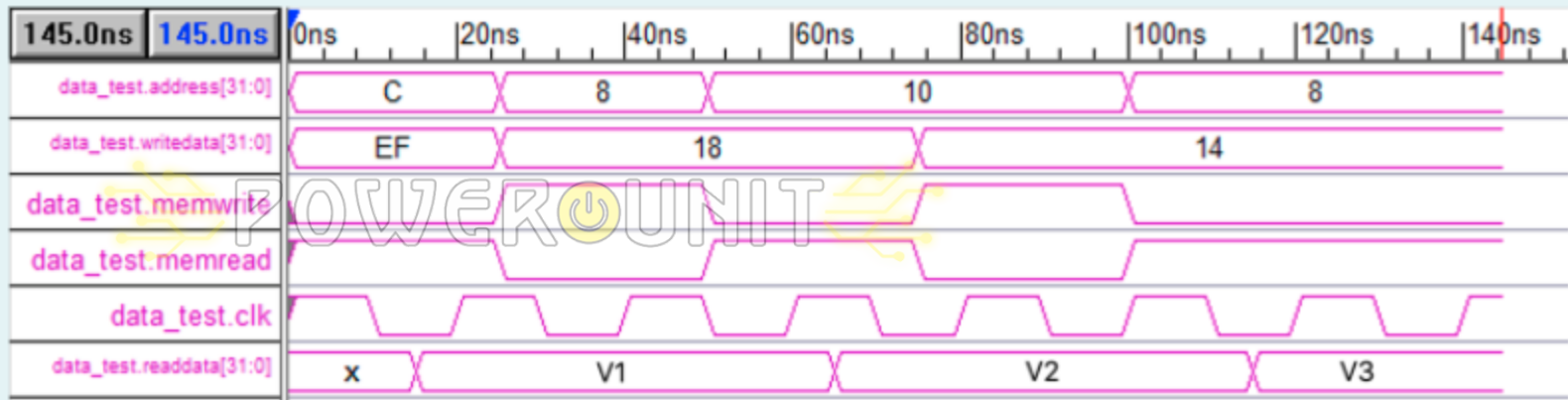


Given the above timing diagram for the data memory module in experiment 4, answer the below questions.

What is the value of v1 ?

?What is the value of v3

?What is the clock cycle time

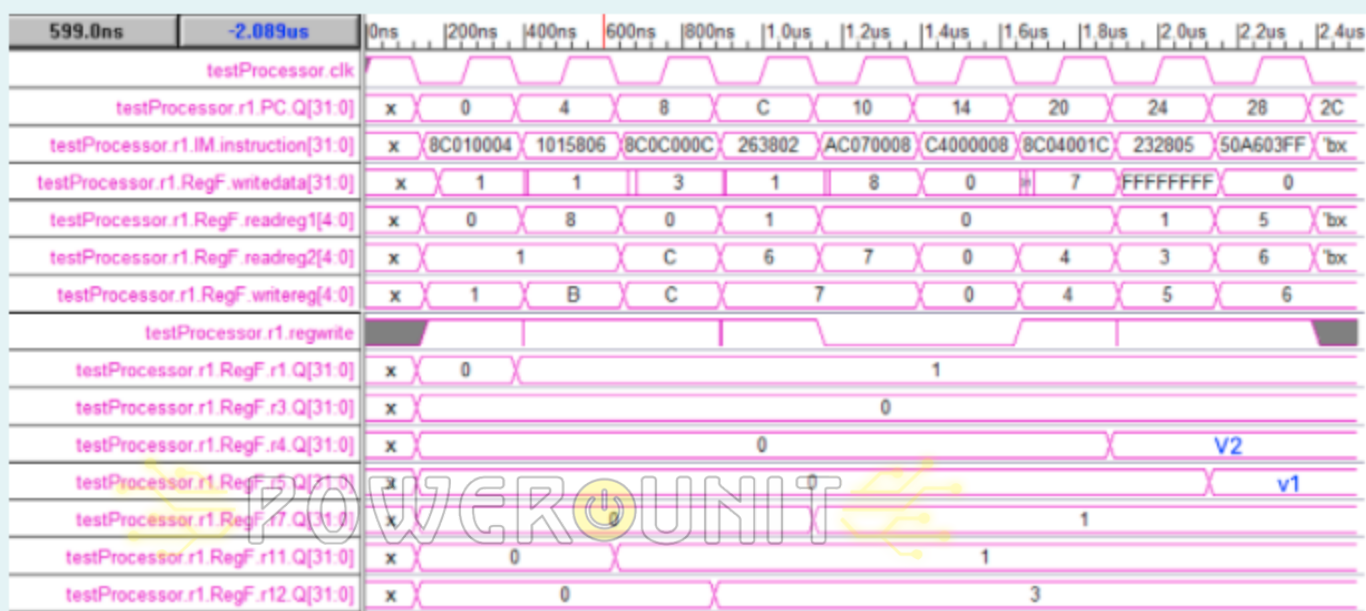

Given the above timing diagram of the single-cycle processor in experiment 6, answer the below questions.


Note: if needed, save the timing diagram to your computer so you can zoom and see the full timing diagram with better clarity.

What is the number of jump/branch instructions ?

What is the number of instructions that write to register R8 ?

? What is the value of V2

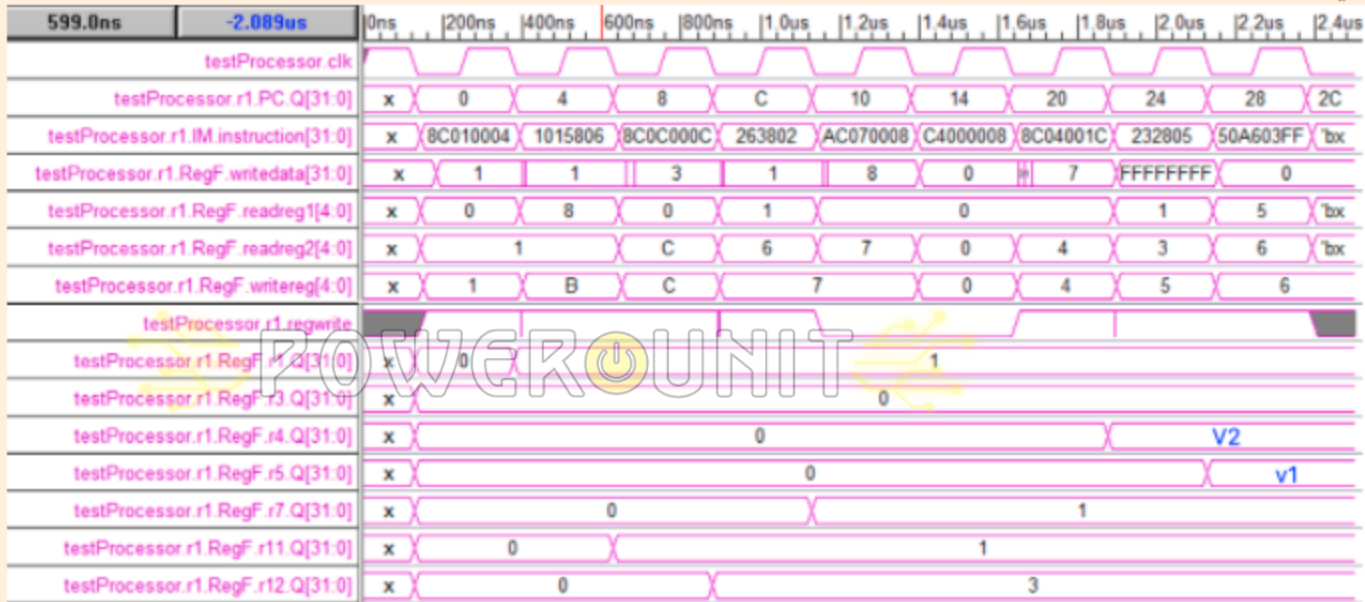What is the number of instructions that read register R5 ?



Given the above timing diagram of the single-cycle processor in experiment 6, answer the below questions.

Note: if needed, save the timing diagram to your computer so you can zoom and see the full timing diagram with better clarity .

What is the number of jump/branch instructions ? [1]

What is the number of instructions that write to register R8 ? [0]

What is the value of V2 ? [7]

What is the number of instructions that read register R5 ? [1]

We want to implement a 2 bit ALU module that supports only two operations: ADD (when m=0) and SUB (when m=1).

Fill the blanks in the below module to complete the code.



```
module ALU_2bit (Result, A, B, m)
    ;input m
    ;input [1:0] A, B
    ;output [1:0] Result
    ;wire x, y, z, w
    XORgate (out, in1, in0)//
; XORgate x0 ( x, m , B[0] )
; XORgate x1 ( y, m , B[1] )
    FullAdder (Sum, Cout, Cin, a, b) //
;FullAdder fa0 ( Result[0] , z , m , A[0] , x )
;FullAdder fa1 ( Result[1] , w, z, A[1] , y )
endmodule
```

```
module Xorgate2 (out, in1, in0)
    ;input in1, in0
    ;out out
    ;assign #2 out = in1 ^ in0
endmodule
```

```
module FullAdder (sum, cout, a, b, cin)
    ;input a, b, cin
    ;out sum, cout
    ;assign #3 sum = a ^ b ^ cin
    ; assign #2 cout = a & b | a & cin | b & cin
endmodule
```

?Assuming we want to use the above xor and full adder modules to implement a 4-bit adder/subtractor circuit, what is the delay

7

8

9

15

10

11

14

17

12

16



الإجابة الصحيحة هي:



The propagation delay of the Control unit implemented in experiment 5 is bigger than the propagation delay of the register file implemented in experiment 3.

Answer the below short answer questions.


Q1. Is the below statement true or false?

? Q2. What is the output of the below Verilog module if the input is in = 3'b100

```
                ;module circuit (out, in)
                ;input [2:0] in
                ;output [1:0] out
                ; assign out[1] = in[1] | ~in[0] & in[2]
                ;assign out[0] = ~in[0] ^ in[2]
                endmodule
```

Q3. Assume the delay for an AND gate is 1, and the delay for an XNOR gate is 2. What is the delay of the below module?

4



```
module circuit (out, a, b);  
  input [2:0] a,b;  
  
  output out;  
  
  wire [3:0] w ;  
  
  XNORgate x0 ( w[0], a[0], b[0] ) ;  
  
  XNORgate x1 ( w[1], a[1], b[1] ) ;  
  
  XNORgate x2 ( w[2], a[2], b[2] ) ;  
  
  ANDgate a0 ( w[3], w[0], w[1] ) ;  
  
  ANDgate a1 ( out, w[2], w[3] ) ;  
  
endmodule
```

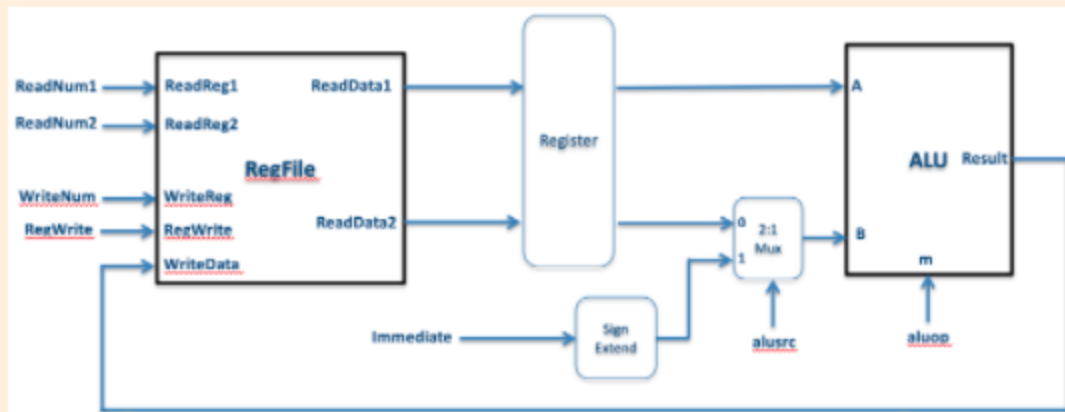

| opcode | function | W |
|--------|----------|---|
| 000000 | 100000 | 0 |
| 000000 | 100010 | 0 |
| 000000 | 100100 | 1 |
| 000000 | 100110 | 1 |
| 000000 | 101000 | 0 |
| 000000 | 101010 | 0 |
| 000000 | 101100 | 1 |
| 000000 | 101110 | 1 |
| 100010 | ----- | 1 |
| 100001 | ----- | 0 |

Given the above truth table, what is the equation of W ?

- $\text{opcode}[5] \& \text{function}[2] \mid \neg \text{opcode}[5] \& \text{opcode}[1]$
- $\neg \text{opcode}[5] \& \text{function}[2] \mid \text{opcode}[5] \& \text{opcode}[0]$
- $\text{opcode}[5] \& \neg \text{function}[2] \mid \neg \text{opcode}[5] \& \text{opcode}[0]$
- $\text{opcode}[5] \& \text{function}[2] \mid \neg \text{opcode}[5] \& \text{opcode}[0]$
- $\neg \text{opcode}[5] \& \neg \text{function}[2] \mid \text{opcode}[5] \& \text{opcode}[0]$
- $\text{opcode}[5] \& \neg \text{function}[2] \mid \neg \text{opcode}[5] \& \text{opcode}[1]$
- $\neg \text{opcode}[5] \& \text{function}[2] \mid \text{opcode}[5] \& \text{opcode}[1]$
- $\neg \text{opcode}[5] \& \neg \text{function}[2] \mid \text{opcode}[5] \& \text{opcode}[1]$

The correct answer is:

Fill in the blanks in the below code.



```
module circuit (immediate, ReadNum1, ReadNum2, WriteNum, RegWrite, alusrc, aluop, clk, reset, enable);
```

```
input [15:0] immediate;
```

```
input [4:0] ReadNum1, ReadNum2, WriteNum;
```

```
input [2:0] aluop;
```

```
input alusrc, clk, reset, enable, RegWrite;
```

```
wire [31:0] w1, w2, w3, w4, w5, w6, w7;
```

```
//RegFile ( ReadData1, ReadData2, ReadReg1, ReadReg2, WriteData, WriteReg, RegWrite, clk, reset)
```

```
RegFile RF ( w1, [w3], ReadNum1, ReadNum2, [w4], WriteNum, RegWrite, clk, reset );
```

```
//SignExtend( out, in )
```

```
SignExtend se ( [w7], immediate );
```

```
//Register ( Q, D, clk, reset, enable )
```

```
Register reg ( {w2, w5}, {w1, w3}, clk, reset, enable );
```

```
//Mux2to1_32bit( out, s, il, io )
```

```
Mux2to1_32bit mux1 ( w6, alusrc, w7, w5 );
```

```
// ALU ( Result, A, B, m )
```

```
ALU alu ( [w4], [w2], [w6], aluop );
```

```
endmodule
```

In this question, you need to use Verilogger pro to write a test module and generate a timing diagram for a given circuit by following these steps:

step 1: download this compressed folder (midterm.zip) from this link:


https://drive.google.com/uc?id=17VXyKrb4fTWGb_f6VZ2CxA_rkGLeKBpU&export=download

step 2: unzip the folder and open the Verilogger project I already provided

step 3: add the verilog files circuit.v and test.v to the project

step 4: note that the top-level module **circuit (in0, in1, in3, out)** is already provided in circuit.v (therefore, do not make any modifications in circuit.v)

 step 5: in test.v, write a test module for **circuit** module to generate the below timing diagram



step 6: Fill-in the blanks in below to write the values of V1, V2 and V3

V1 =

V2 =

V3 =