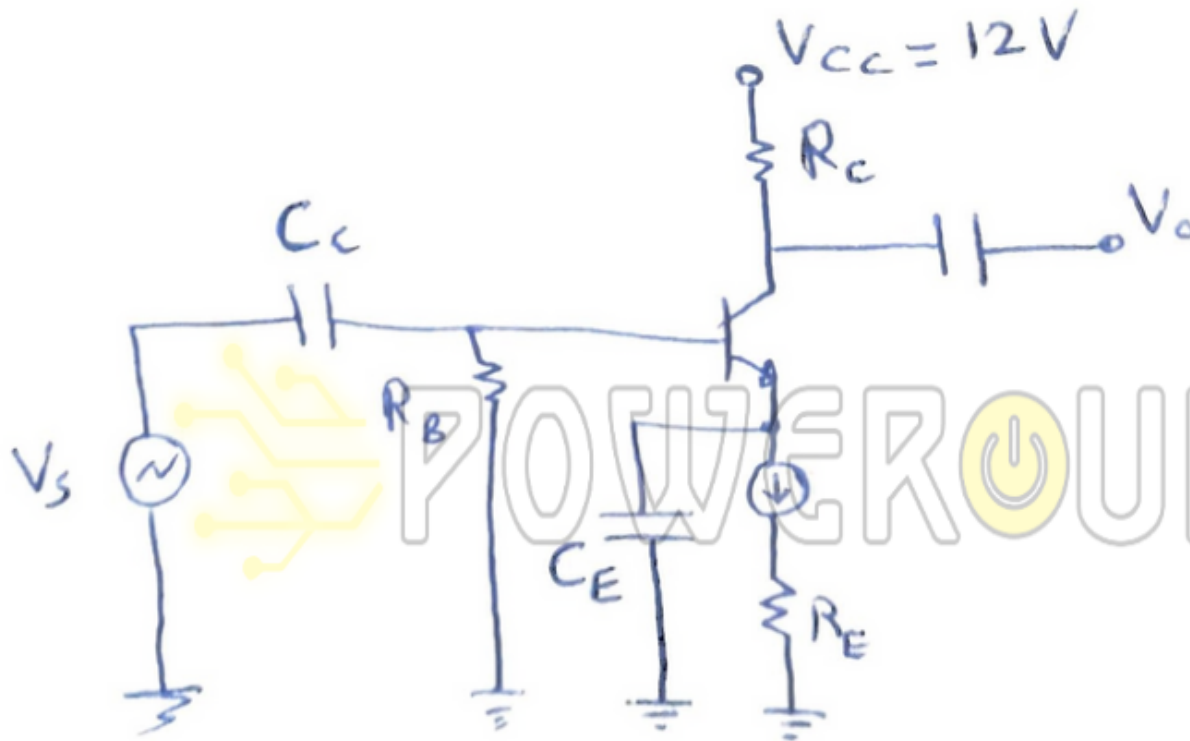


Question 1/4

For the Electronic Circuit shown in the Figure.



[Zoom image](#)

If you Know:

$R_C = 1 \text{ kohm}$, $R_E = 500 \text{ ohm}$, $R_B = 100 \text{ kohm}$, and $I_o = 2 \text{ mA}$

For the Transistor: $V_T = 0.026V$, $V_{BE} = 0.7V$, $V_{CE(SAT)} = 0.2V$, and $\text{Beta} = 100$;

Find the small signal Voltage gain $A_v = V_o/V_s$.

If you Know:

$R_C = 1 \text{ kohm}$, $R_E = 500 \text{ ohm}$, $R_B = 100 \text{ kohm}$, and $I_o = 2 \text{ mA}$

For the Transistor: $V_T = 0.026\text{V}$, $V_{BE} = 0.7\text{V}$, $V_{CE(\text{SAT})} = 0.2\text{V}$, and $\text{Beta} = 100$;

Find the small signal Voltage gain $A_v = V_o/V_s$.

-33

-66


-88

-77

None.

-22



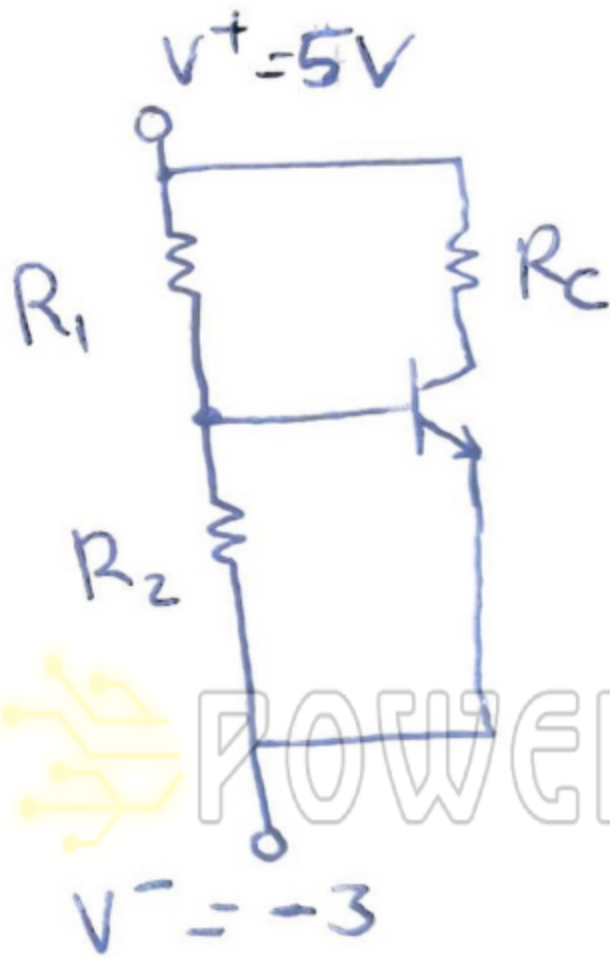

[Zoom image](#)

If you Know:


$R_C = 2 \text{ kohm}$, $R_1 = 90 \text{ kohm}$, $R_2 = 10 \text{ kohm}$.

For the Transistor: $V_T = 0.026V$, $V_{BE} = 0.7V$, $V_{CE(SAT)} = 0.2V$, and $\text{Beta} = 100$;

Find the value of I_{CQ}

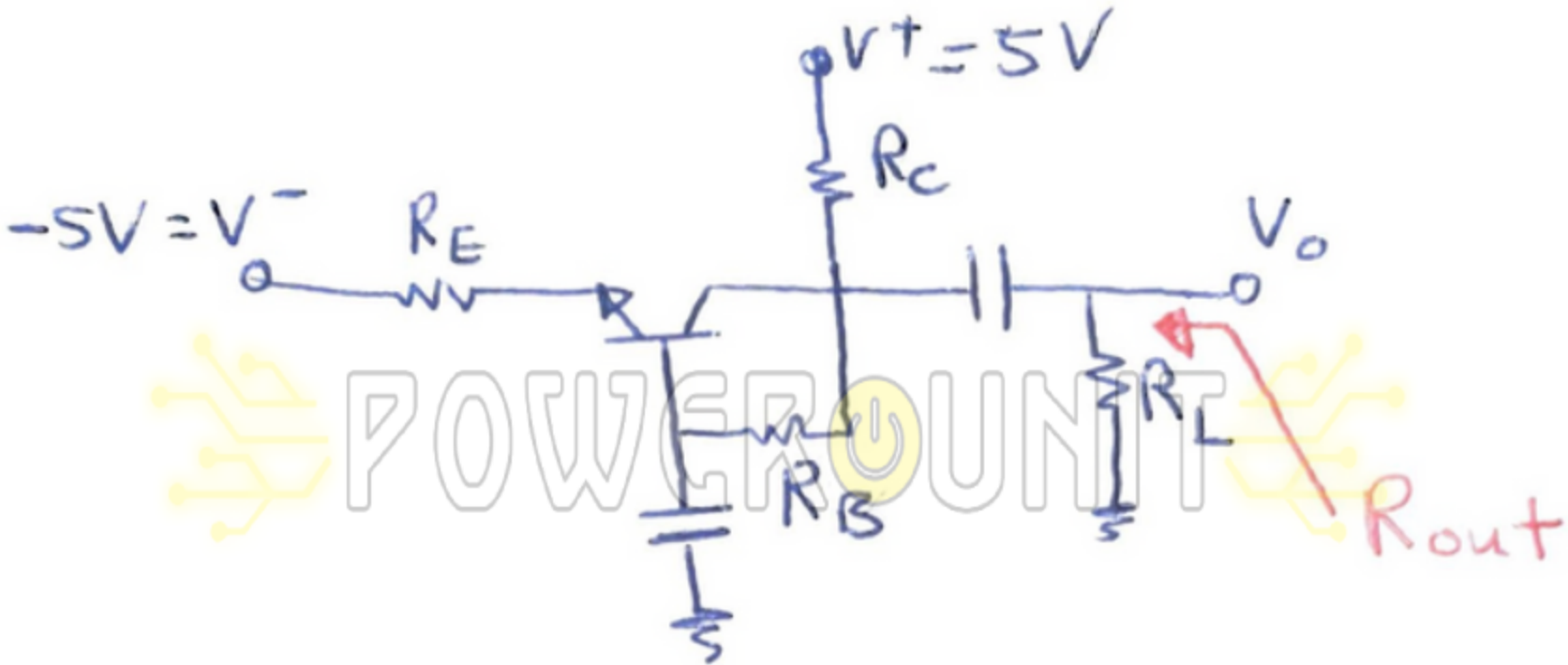Question 3/4

For the Electronic Circuit shown in the Figure.



[Zoom image](#)

If you Know:

$R_C = 2\text{kohm}$, $R_E = 300\text{ ohm}$, $R_B = 100\text{ kohm}$, and $R_L = 1\text{ kohm}$.

For the Transistor: $V_T = 0.026V$, $V_{EB} = 0.7V$, $V_{EC(SAT)} = 0.2V$, and $\text{Beta} = 300$;

Find the indicated output resistance R_{out} .

If you Know:

$R_C = 2\text{ kohm}$, $R_E = 300\text{ ohm}$, $R_B = 100\text{ kohm}$, and $R_L = 1\text{ kohm}$.

For the Transistor: $V_T = 0.026\text{V}$, $V_{EB} = 0.7\text{V}$, $V_{EC(\text{SAT})} = 0.2\text{V}$, and $\text{Beta} = 300$;

Find the indicated output resistance R_{out} .

1.5 kohm

330 ohm

None.

4.2kohm


662 ohm

890 ohm



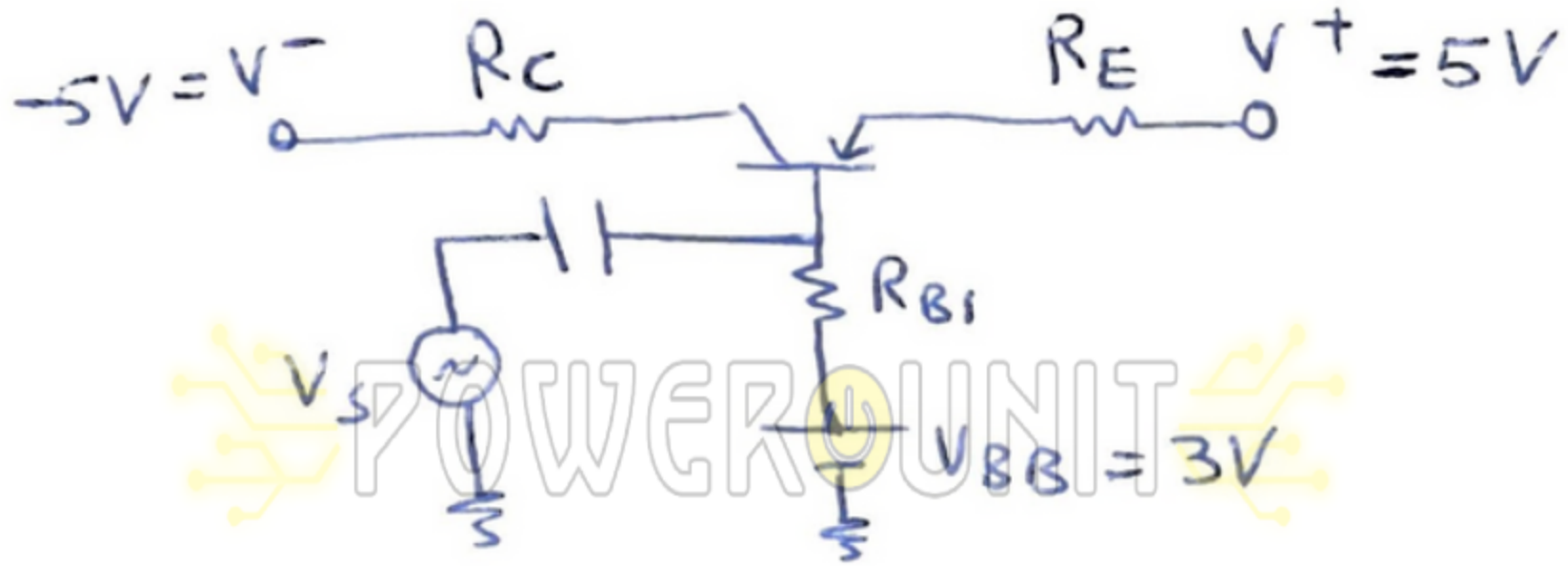Question 4/4

For the Electronic Circuit shown in the Figure.



[Zoom image](#)

If you Know:

$R_C = 2\text{kohm}$, $R_E = 100\text{ ohm}$, and $R_{B1} = 100\text{kohm}$.

For the Transistor: $V_T = 0.026V$, $V_{BE} = 0.7V$, $V_{CE(SAT)} = 0.2V$, and $\text{Beta} = 100$;

Find the small signal r_{pi} .