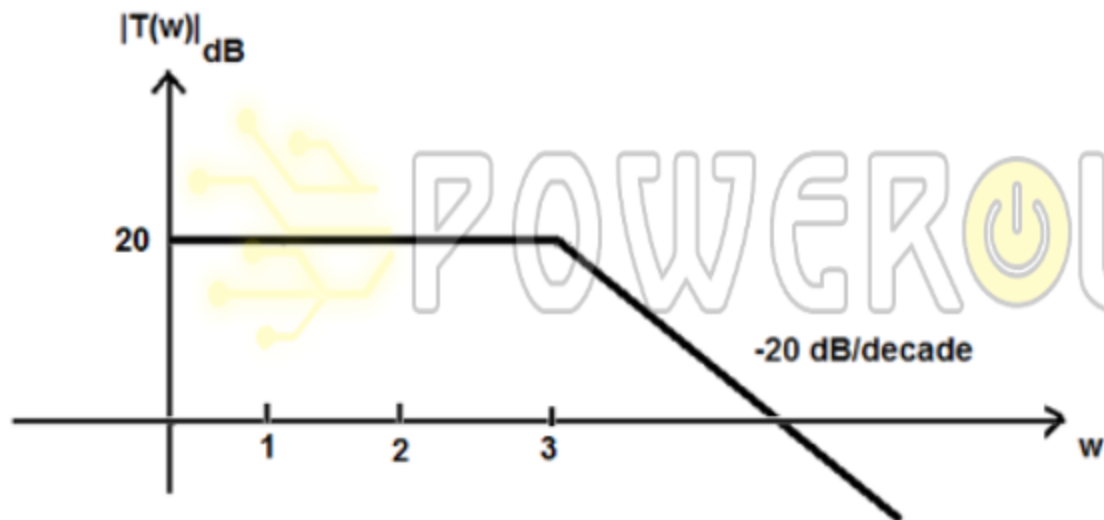


Question 1/4 (3 p.) Answer is mandatory

Consider the Bode plot of a transfer function shown in the following and then find the expression of the transfer function.

\*\* Note that the x-axis is the angular frequency  $\omega$  and  $s = j\omega$



**Question 2/4** (3 p.) **Answer is mandatory**


The parameters of the transistor in the circuit in the Figure are  $\beta = 100$ ,  $V_{BE(on)} = 0.7 \text{ V}$ , and  $V_A = 30\text{V}$ .

Assume  $R_E = 0\Omega$ , and  $C_L = 10\text{pF}$ .

The collector current is calculated for you  $I_{CQ} = 30\text{mA}$ .


Neglect the capacitance effects of the transistor.

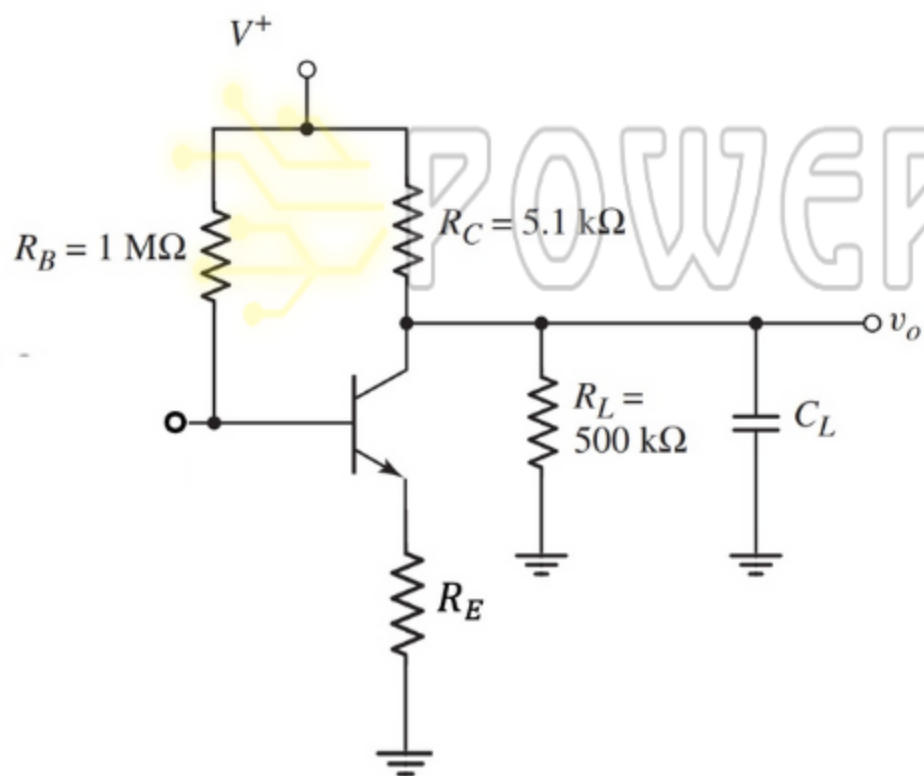Then the cutoff frequency is approximately:



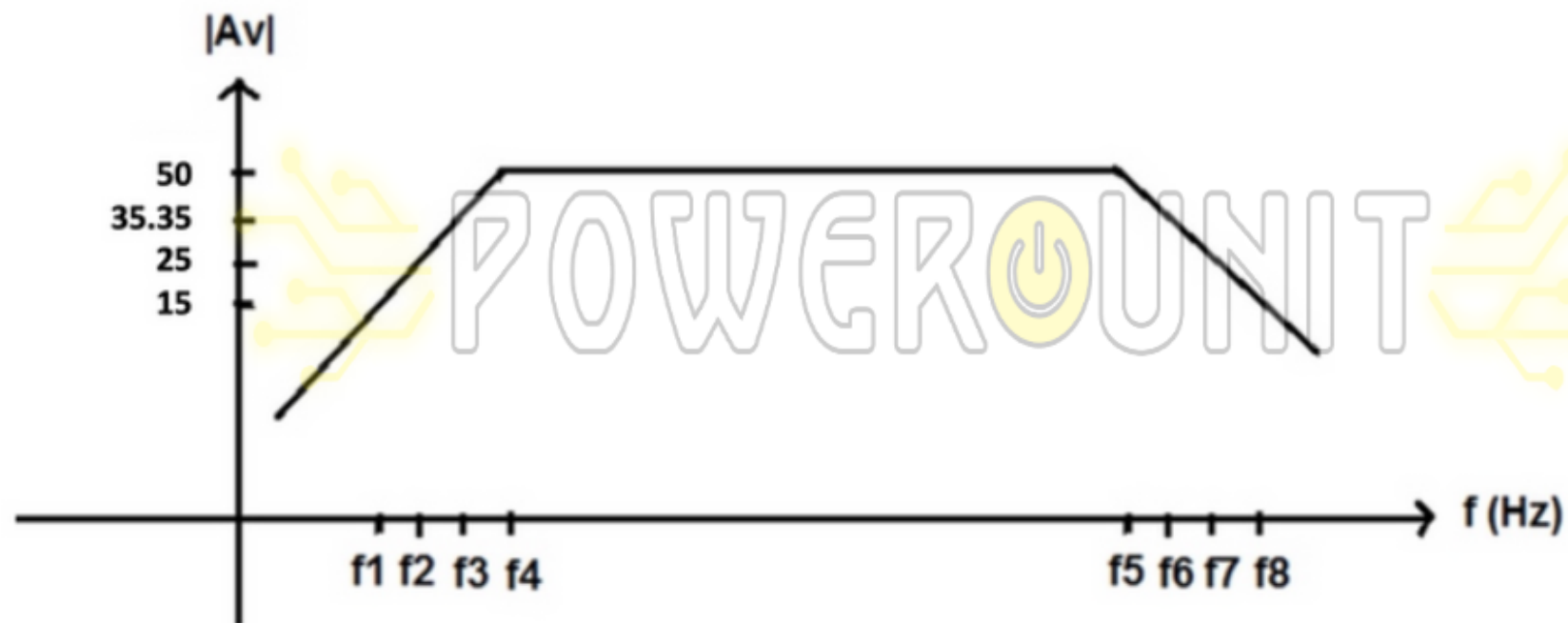Question 3/4 (2 p.) Answer is mandatory

Consider the transfer function of an amplifier shown in the Figure, and then find the bandwidth BW of this amplifier.



Question 4/4 (2 p.) Answer is mandatory

Consider the circuit shown in the Figure, find the 3dB cut-off frequency for it in which  $C_C = 0.5\mu\text{F}$ , given that  $K_n = 2\text{ mA/V}^2$ ,  $V_{TN} = 1\text{V}$ ,  $\lambda = 0\text{ V}^{-1}$ , and  $g_m = 2\text{ mA/V}$ .

