

Question 1/18 (3 p.) Answer is mandatory

Consider the circuit shown in the Figure. The transistor parameters are:


$$\beta = 120, V_{BE(on)} = 0.7V, \text{ and } V_A = \infty.$$

Assume: $I_Q = 0.4mA$, and $V_T = 0.026V$

If you are given the voltage gain as:

$$A_v(s) = \frac{-g_m r_{\pi} R_C}{R_i + r_{\pi} + (1 + \beta) \left(\frac{1}{sC_E} \right)}$$

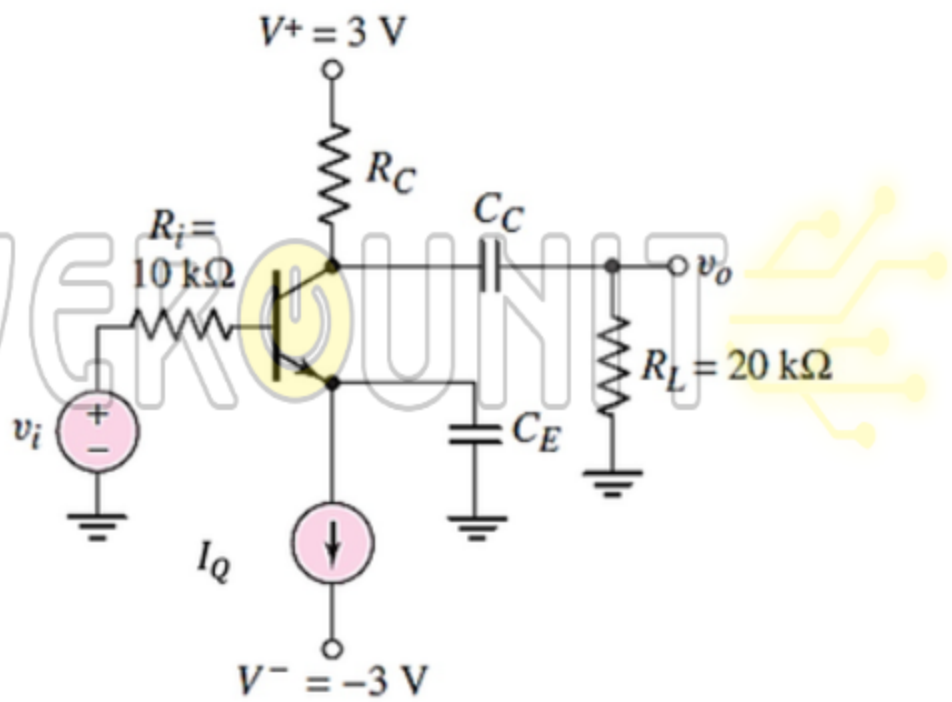Determine C_E such that the corner frequency associated with is $f_E = 10Hz$.



Question 2/18 (2 p.) Answer is mandatory


For any voltage amplifier circuit, if the load resistance R_L happened to become open, then the ac output voltage will:

- Increase
- Equal Zero
- Decrease
- Remain the Same

POWERUNIT

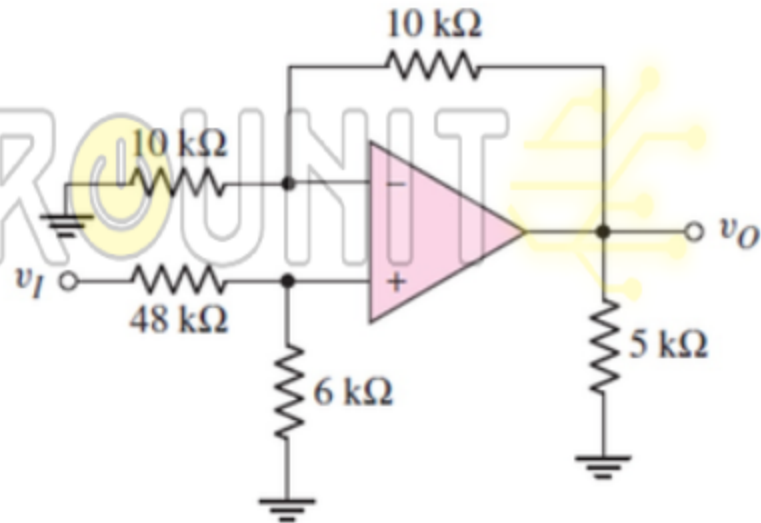Question 3/18 (3 p.) Answer is mandatory

Consider the circuit shown in the Figure.
Determine the output voltage for $v_I = 8.5V$.




Question 4/18 (4 p.) Answer is mandatory

The parameters of the transistor in the circuit shown in the Figure are:

$$V_{BE(on)} = 0.7V, \beta = 120, \text{ and } V_A = \infty.$$

$$\text{Use } V_T = 0.026V.$$

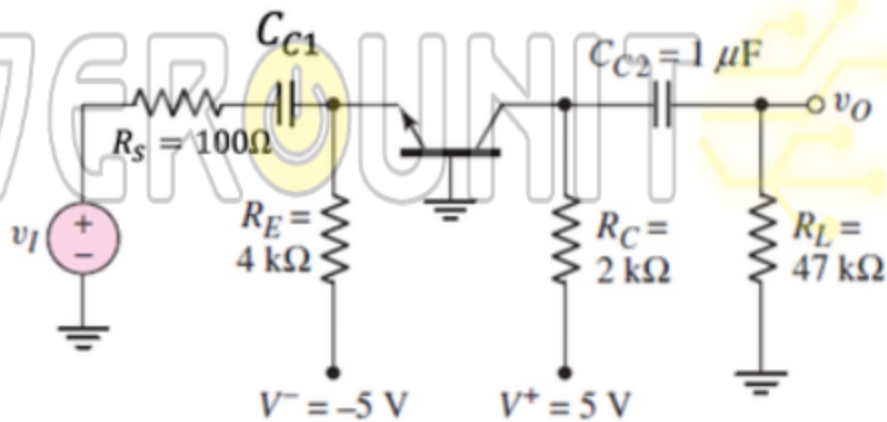
Find the -3 dB frequency associated with $C_{C1} = 9.6\mu F$.



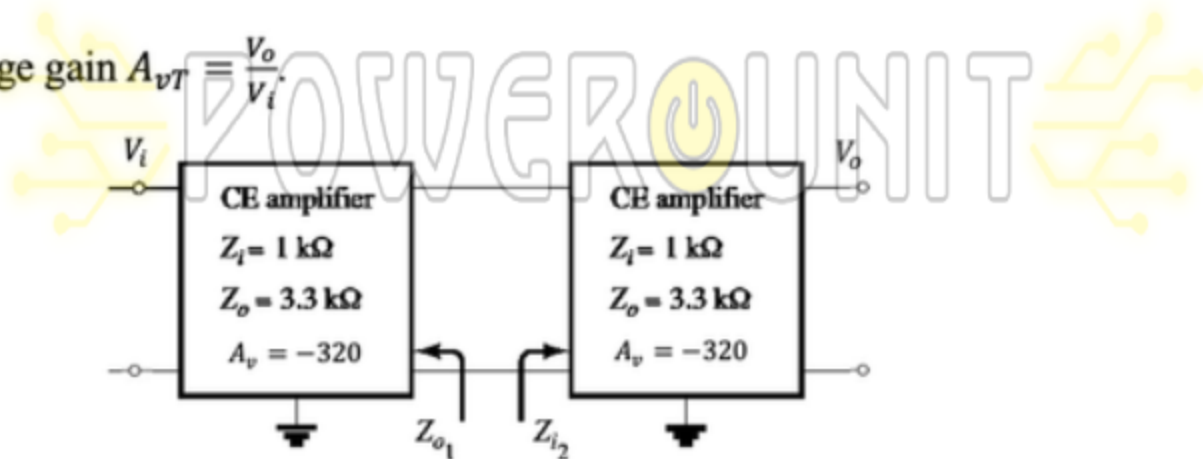Question 5/18 (4 p.) Answer is mandatory

For the cascaded system shown in the Figure with **two identical stages** each has the same A_v , determine:

The total voltage gain $A_{vT} \equiv \frac{V_o}{V_i}$.




Question 6/18 (3 p.) Answer is mandatory

Consider the source follower circuit in the Figure with transistor parameters:

$V_{TN} = 0.8V$, $k'_n = 100\mu A/V^2$, $W/L = 20$, and $\lambda = 0.02V^{-1}$.

Let $I_Q = 3mA$.

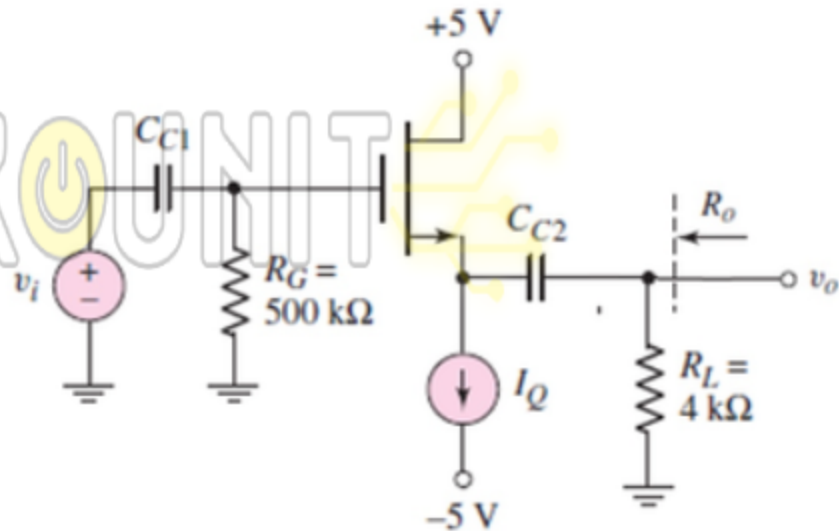Find the small signal output resistance R_o in the Mid-band frequency.



Question 7/18 (2 p.) Answer is mandatory

In an amplifier circuit, the average power dissipated in the transistor decreases when:

V_{CC} is increased

AC signal is applied

AC signal is not applied

R_C is decreased

Question 8/18 (2 p.) Answer is mandatory

For an op-amp circuit, if it has only a positive supply voltage V_{CC} , then its output cannot:

Be Zero

Be ac coupled

Be negative


Saturate

POWERUNIT

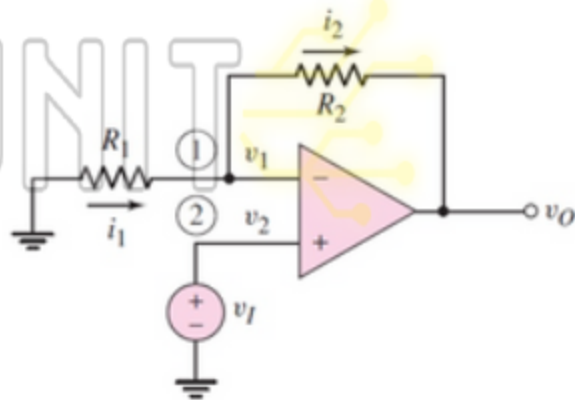Question 9/18 (3 p.) Answer is mandatory

An ideal non-inverting op-amp circuit is to be designed with a closed-loop voltage gain of $A_v = 55$. The largest resistor value to be used is $4\text{ k}\Omega$.

If the simple two-resistor design shown in the Figure is used, what is the value of R_1 ?



Question 10/18 (3 p.) Answer is mandatory

The parameters of the circuit shown in the Figure are:


$$R_1 = 60 \text{ k}\Omega \text{ and } R_2 = 28 \text{ k}\Omega.$$

The transistor parameters are:

$$V_{BE(on)} = 0.7 \text{ V}, \beta = 100, \text{ and } C_{\mu} = 0.45 \text{ pF}.$$

Use $V_T = 0.026 \text{ V}$.

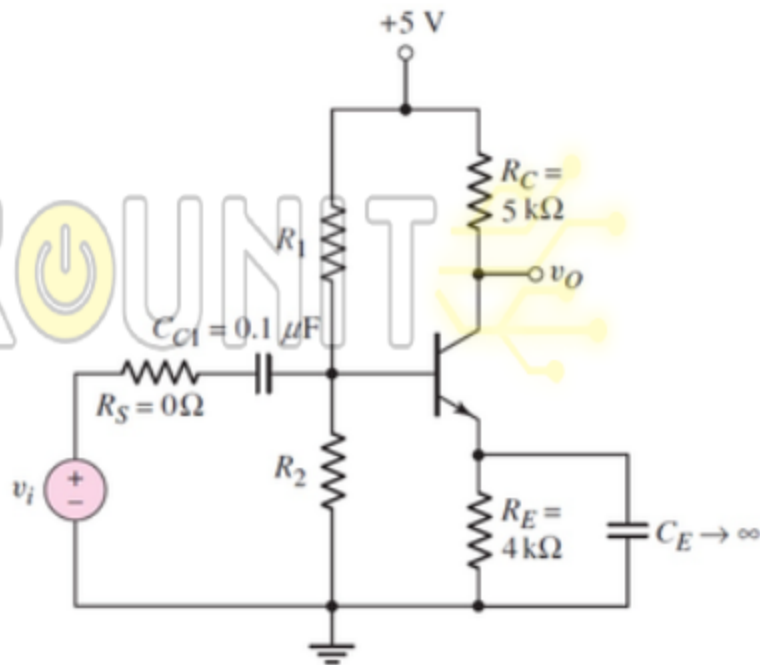
Determine the **Miller** capacitance C_M .



The transistor in the circuit shown in the Figure is biased by $I_{DQ} = 2\text{mA}$, and has the following parameters:

$$V_{TN} = 0.4\text{V}, K_n = 50\mu\text{A}/\text{V}^2, \text{ and } \lambda = 0.05\text{V}^{-1}.$$

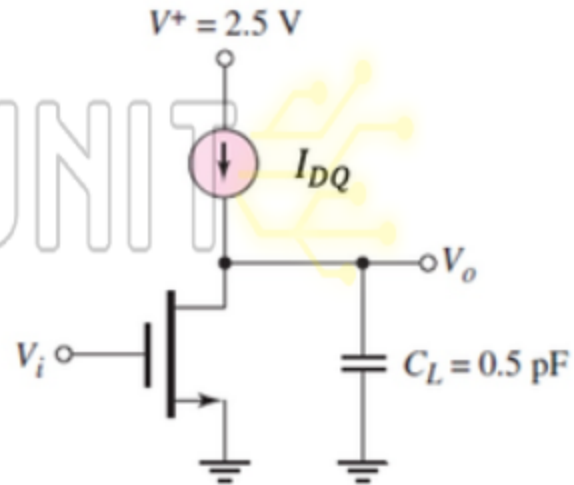Approximately, what is the bandwidth of the frequency response for the amplifier circuit shown?




Question 12/18 (3 p.) Answer is mandatory

The small-signal parameters of the NMOS transistor in the **ac equivalent common-gate** circuit shown in the Figure are:

$$V_{TN} = 0.6 \text{ V}, K_n = 4 \text{ mA/V}^2, \text{ and } \lambda = 0.$$

The quiescent drain current was found as: $I_{DQ} = 1 \text{ mA}$.

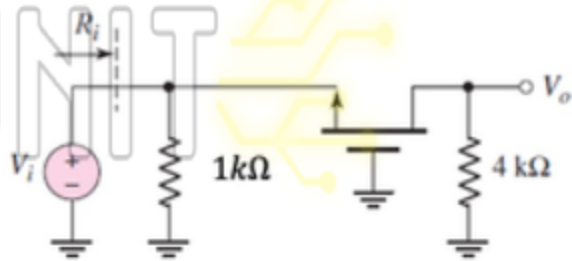Determine the small-signal input resistance R_i .



Question 13/18 (3 p.) Answer is mandatory

The parameters of the transistor in the circuit shown in the Figure are:


$\beta = 100$, $V_{BE}(on) = 0.7 V$, $V_A = \infty$.
Use $V_T = 0.026 V$.

***Hint:** Neglect the capacitance effects of the circuit and the transistor.

When $R_S = 0 \Omega$, we calculated:


$$A_{mid} = -219.4.$$

If we set $R_S = 1 k\Omega$, now determine the new value of $|A_{mid}|_{dB}$:

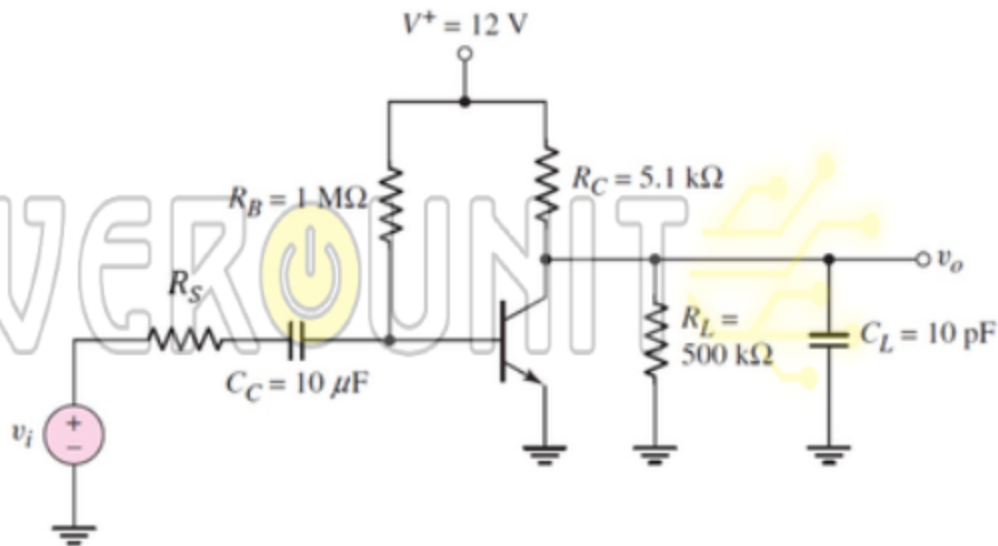

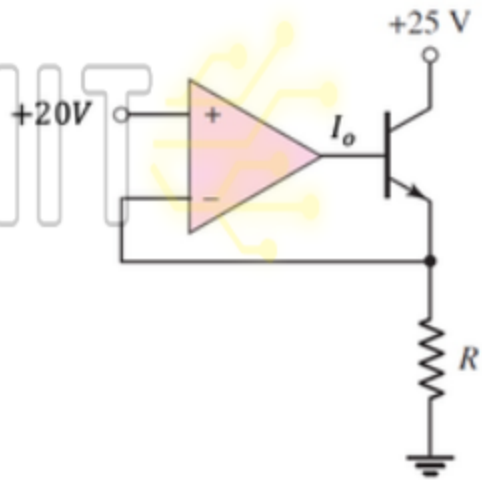Question 14/18 (4 p.) Answer is mandatory

The output current of the op-amp shown in the Figure is $I_o = 2.2 \text{ mA}$. Assume the transistor $V_{BE}(\text{on}) = 0.7$, and current gain $\beta = 50$. Determine the resistance value R .



Question 15/18 (2 p.) Answer is mandatory

For a voltage amplifier, if the voltage gain increases by a factor of 14 (e.g. $A_{\text{new}}=14 \cdot A_{\text{old}}$), the decibel (dB) voltage gain increases by:

A factor of 14

23 dB

30 dB

14 dB

POWERUNIT

Question 16/18 (2 p.) Answer is mandatory

The voltage gain of an amplifier decreases 60 dB per decade above the high cut-off frequency $f_H=30$ kHz.

If the midband voltage gain was 110 dB, what will be the magnitude of the voltage gain A_v at 3MHz?

-10 dB

-30 dB

10 dB

30 dB

Question 18/18 (2 p.) Answer is mandatory

The output resistance of a MOSFET common gate amplifier equals to:

- Base resistor
- Drain resistor
- Gate resistor
- Source resistor

POWERUNIT