

Time left 0:59:42

Question 1

Not yet answered

Marked out of 1.00

Flag question

Suppose the gate delay for an **AND** gate is 0.3ns, for an **OR** gate is 0.2ns, and for an **inverter** is 0.1ns, what is the total delay between the time the inputs appear at the first level gates, and the output appears at the last gate if the circuit is described as  $(x+y)'(y+z)'$

Total Delay is  ns.

Next page

Time left 0:41:30

Question 4

Not yet answered

Marked out of 2.00

Flag question

Given the four variable function  $F(wxyz) = \prod_m(3, 7, 12, 15)$ , the product of maxterm expression consists of the following maxterms:

- $(w + x + y + z')$
- $(w + x' + y + z')$
- $(w + x + y + z)$
- $(w' + x' + y + z)$
- $(w' + x + y + z)$
- $(w' + x' + y + z')$
- $(w' + x + y + z')$
- $(w' + x' + y' + z')$
- $(w + x' + y' + z')$
- $(w + x' + y + z)$
- $(w' + x + y' + z')$
- $(w + x + y' + z)$
- $(w + x + y' + z')$
- $(w' + x' + y' + z)$
- $(w' + x + y' + z)$
- $(w + x' + y' + z)$

Time left 0:33:33

Question 5

Not yet answered

Marked out of 1.00

Flag question

The following numbers in two different number systems are equal. Find the base number x:

$$(313)_x = (513)_7$$

$$x = 12 \downarrow$$

**Hint:** the roots of a quadratic equation are  $\frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$

Next page

Time left 0:17:45

Question 11  
Not yet answered  
Marked out of 2.00  
Flag question

Given the following four variable k-map, answer the questions that follow:

	1		1
1		1	
	1		1
1		1	

The number of prime implicants is

The number of essential prime implicants is

Next page

Time left 0:51:06

Question 2

Not yet answered

Marked out of 1.00

Flag question

Which of the following functions can be implemented using a two-level circuit?

(Do not modify/simplify the expression when giving your answer)

Select one or more:

$F(A, B, C) = (A+B+C) \cdot (B'+C') \cdot A$

$F(A, B, C) = (AB+C) \cdot (A'B'+C')$

$F(A, B, C) = B'(A+C) + A(B'+C')$

$F(A, B, C) = A \cdot B' \cdot C' + A' \cdot B' \cdot C' + A \cdot B$

$F(A, B, C) = A \cdot B + B \cdot C' \cdot (A'+C')$

Next page

Time left 0:21:40

Question 10

Not yet answered

Marked out of 2.00

Flag question

What is the **L**, **G**, and **GN** cost of the following circuit? Do not simplify the circuit. Do not manipulate the circuit inputs. Assume inputs inside the parenthesis are connected to the same gate.

$$F = x(yz' + wx) + z'$$

L =

G =

GN =



Next page

Time left 0:27:26


Question 7

Not yet answered

Marked out of 1.00

Flag question

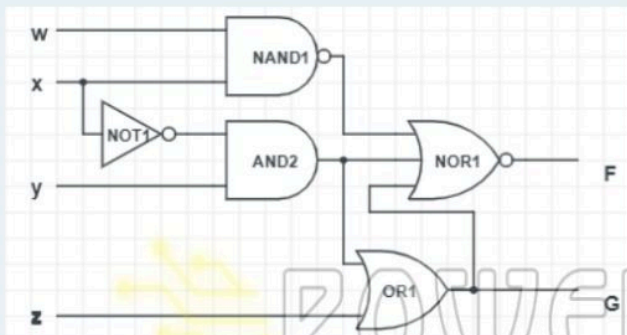What are the outputs **F** and **G** of the following multi-output circuit if the input pattern  $wxyz = 0000$  :



- F = 1, G = 1
- F = 0, G = 1
- F = 0, G = 0
- F = 1, G = 0

Next page

Time left 0:33:13

Question 6

Not yet answered

Marked out of 1.00

Flag question

Given that the **fan-in** for the **AND** and **OR** gates is **2**, and a **fan-out** of **3** for all gates, how many AND/OR/NOT gates are needed to implement the function  $F = abc + bc' + a'bc'$ .

*Do not simplify the expression and assume we want to implement it as is.*

Number of gates is

Next page



Time left 0:08:26

Question 15

Not yet answered

Marked out of 1.00

Flag question

The dual of the function  $F = (x'y + w) + z'$  is:

- $(x' + yw)z'$
- none of the other options
- $x' + ywz'$
- $(x + y)w'z$
- $(x' + y)wz'$

Next page

Time left 0:14:42

Question 14

Not yet answered

Marked out of 1.00

Flag question

Which of the expressions below is equivalent to the following expression:

$$f(x, y, z) = x'y + y'z$$

- $(x+y).(y+z)$
- $(x+y+z).(x'+y'+z)$
- $\sum_m(0, 4, 6, 7)$
- $x'yz + xy'z$
- $\prod_m(0, 4, 6, 7)$



Next page

Time left 0:15:17

Question 13

Not yet answered

Marked out of 1.00

Flag question

What is the result of converting the decimal fraction 0.7512 to base-7? Assume we truncate when we have five fractional digits in the final answer.

- 0.51544
- 0.50232
- None of the other options
- 0.43013
- 0.41550
- 0.33342

Next page

Time left 0:23:52

Question 8

Not yet answered

Marked out of 1.00

Flag question

Given the special relationship between base-3 and base-9 similar to that between base-2 and base-8/base-16, what is the result of converting the number  $(121110)_3$  to base-9?

- 861
- 208
- 785
- 430
- None of the other options
- 543

[Clear my choice](#)

Next page

Time left 0:16:49

Question 12

Not yet answered

Marked out of 1.00

Flag question

In a system that encodes the numbers 0–13 using Gray code, what is the code of the number 10?

Select one:

- 1111
- 1101
- 1010
- 1000
- 1110
- 1100
- 1001
- 1011

[Clear my choice](#)

## Question 16

Not yet answered

Marked out of 1.00

Flag question

Which of the expressions below is the simplified PoS expression of the function  $F(W,X,Y,Z)$  represented by the following K-map?

		<b>Y</b>			
<b>X</b>		<b>0</b>	<b>0</b>	<b>1</b>	<b>x</b>
		<b>0</b>	<b>x</b>	<b>1</b>	<b>x</b>
		<b>0</b>	<b>1</b>	<b>1</b>	<b>x</b>
		<b>0</b>	<b>1</b>	<b>1</b>	<b>x</b>
<b>W</b>					
		<b>0</b>	<b>1</b>	<b>1</b>	<b>x</b>
		<b>Z</b>			

- $Z(W+Y)$   
  $Y'(W'+Z')$   
  $Z(W+X+Y)$

Time left 0:44:25

Question **3**  
Not yet answered  
Marked out of 1.00  
Flag question

The minimum number of digits required in order to represent the decimal numbers 0-250 using base 3 is



Next page