

4. When a diode is ON, it behaves as *
(2 Points)

- A pure resistance.
- An excellent pure conductor.
- An ideal current source.
- A pure capacitance.
- None of the above or below

POWERUNIT

None of the above or below.

5. A zener diode in a circuit is used in the forward biased mode. *
(2 Points)

Such kind of biasing is not possible.

Can be done but not justified.

No point as it will act as a short circuit. Option 3

none of the above or below.

No point as it will act as an open circuit.

6. A current-voltage relationship of a particular diode is given by
 $i_D = 0.05 \cdot v_D - 0.0335$.

7. Given the graph shown. The diode forward bias resistance at 3.5mA is about (see ee261stMidtermGraphs in files) *
(2 Points)

- 0.116Ω
- 11.6Ω
- 0.8Ω
- 8.57Ω
- 85.7Ω

POWERUNIT

8. refer to the graph, when 2mA passes through the diode, the power dissipated in the diode is
(2 Points)

9. Find I_D ,and V_o in the circuit shown given $V_\gamma=0.7V,r_f=0\Omega$.
(see ee261stMidtermGraphs in files) *
(2 Points)

$I_D=465\mu A$,and $V_o=4.3V$

$I_D=0A$,and $V_o=5V$

$I_D=465\mu A$,and $V_o=-4.3V$

$I_D=0A$,and $V_o=-5V$

$I_D=0A$,and $V_o=0V$

10. Consider the circuit shown where $I_D = 0.4\text{mA}$, and the diode turn-on voltage is 0.7V . Calculate the diode forward resistance r_f (see ee261stMidtermGraphs in files) * (2 Points)

$6.5\ \Omega$

$1.75\ \Omega$

$50\ \Omega$

$0\ \Omega$

$0.125\ \Omega$

POWERUNIT

11. Consider the circuit shown where $V_\gamma = 0.7V$, and $r_f = 0\Omega$. The supply voltage is $-2V$.
The current in the resistance is.
(see ee261stMidtermGraphs in files) *
(2 Points)

1.625mA

-8.75mA

8.75mA

-13.375mA

The diode is OFF, Current is zero.

12. Consider the circuit shown where $V_Z=6.8V$, $r_Z=0\Omega$. Calculate the Zener current.
(see ee261stMidtermGraphs in files) *
(2 Points)

3.4mA

6.8mA

3m

None of the above or below.

With circuit values, the diode blows up

POWERUNIT

8. refer to the graph, when 2mA passes through the diode, the power dissipated in the diode is *

(2 Points)

- About 1.35mW
- About 2.45mW
- About 2.42mW, i.e. delivering power.
- About 2.4mW
- About -1.35mW, i.e. delivering power.

POWERUNIT

9. Find I_D , and V_o in the circuit shown given $V_v=0.7V, r_f=0\Omega$.

3. A generic diode with breakdown voltage of 100V can be used as *
(2 Points)

An amplifier of low gain $15/0.7$

A 15V rectifier

An amplifier of gain $100/15$

None of the above, or below.

All of the above, or below.

4. When a diode is ON, it behaves as *

2. A motion detection circuit using diodes may involve. *
(2 Points)

- A forward biased infra-red diode together with a reverse biased infra-red photo diode.
- An infra-red LED diode together with a photo diode both reverse biased.
- Two zener diodes.
- Two Shottky diodes because they are fast.
- A zener diode for voltage regulation and and a fast diode for detection.

3. A generic diode with breakdown voltage of 100V can be used as *

11.7

15. Consider the circuit shown where both diodes are assumed ON. Given that $R_1 = 10\text{ K}\Omega$, $R_2 = 30\text{ K}\Omega$, $V_\gamma = 0.7\text{ V}$, $r_f = 0\Omega$. Calculate I_{D1} , I_{D2} , and V_0 . (see ee261stMidtermGraphs in files) *
(4 Points)

13. Consider the circuit shown .


Determine the diode voltage and diode current given that $V_g=0.6V, r_f=50\Omega$

(see ee261stMidtermGraphs in files) *

(2 Points)

Enter your answer

14. Consider the LED circuit shown where $V_y=1.8V$, $r_f=20\Omega$. Acceptable LED light intensity is obtained when the LED current is $10mA$. If $R=150\Omega$, determine V which results in such minimum current.

(see ee261stMidtermGraphs in files) * 

(2 Points)

Enter your answer

15. Consider the circuit shown where both diodes are assumed ON. Given that

$R_1=10K\Omega, R_2=30K\Omega,$

$V_y=0.7V, r_f=0\Omega$

Calculate I_{D1}, I_{D2} , and V_O .